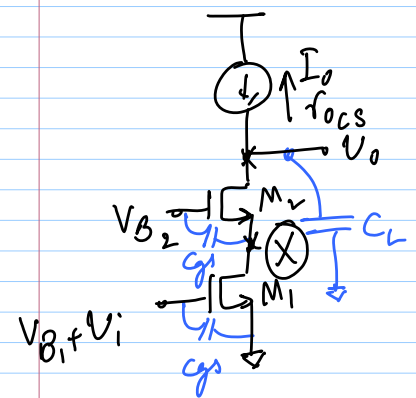


22/1/14

Lec 4

$$\frac{1}{r_{ds} C_{gs}} \quad v_{D.} \quad \frac{g_m}{C_{gs}}$$




gain = $-(g_m r_{ds})^2$

- * P_{diss}
- * R_{out}
- * Freq. Response

$$|W_{p1}| = \frac{1}{r_{out} \cdot C_L}$$

$$|W_{p2}| = \frac{g_m}{C_{gs}}$$

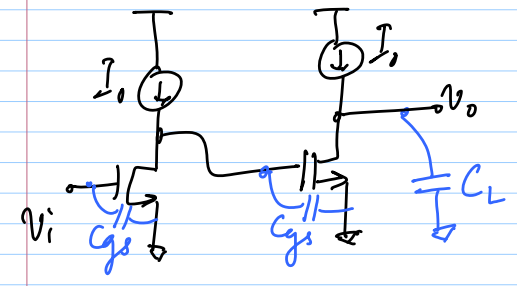


2 poles:

$$|W_{p1}| = \frac{1}{r_{ds} C_{gs}}$$

$$|W_{p2}| = \frac{1}{r_{ds} C_L}$$

2 dominant poles

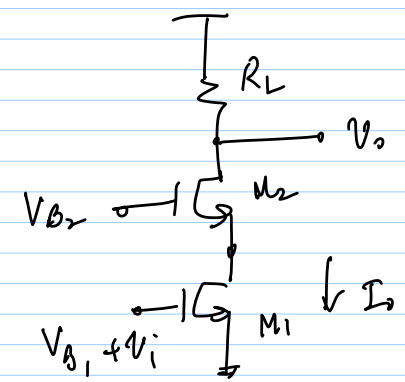


$V_{B2} = ?$

- * M_1 in sat. (min v_o)
- * M_2 in sat. (max. v_o)



$$I_0 (V_{as2} + V_{as1}) \leq V_{B2} \leq (V_{T2} + v_{D0} - I_0 R_L)$$

$$V_{B1} = V_{as1} @ I_0$$


cascode C-S.

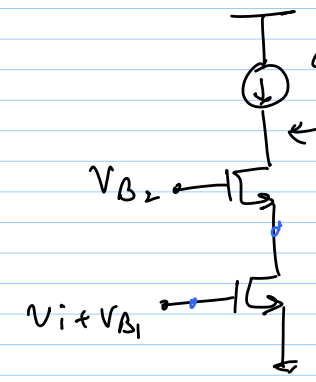

$$r_o = \frac{g_m r_{ds}^2}{2}$$

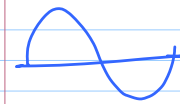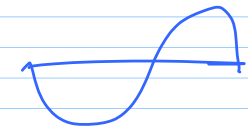

Folded Cascode

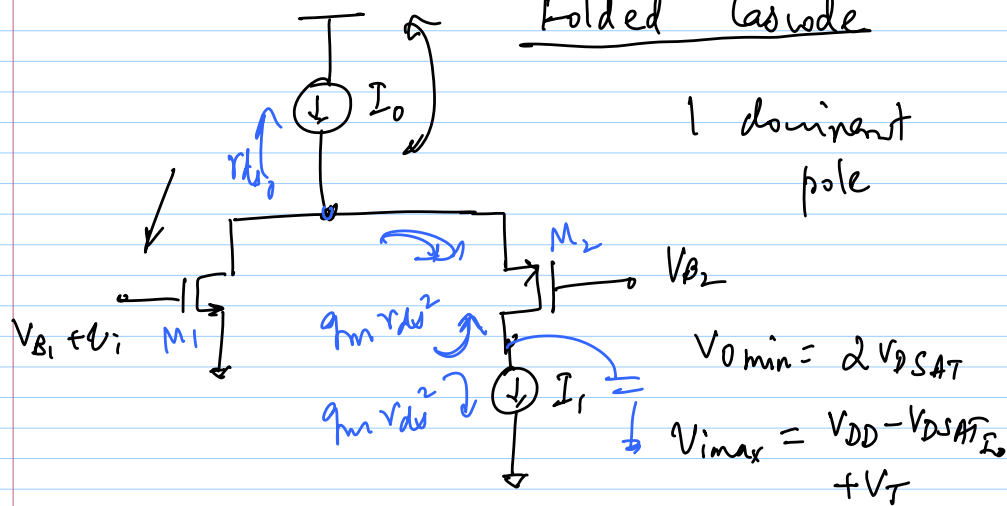


1 dominant pole

$$V_{Omin} = 2V_{DSAT}$$

$$V_{Omax} = V_{DD} - V_{DSAT2} + V_T$$

NMOS CS + PMOS C.G.

* Input CM is disconnected from o/p CM

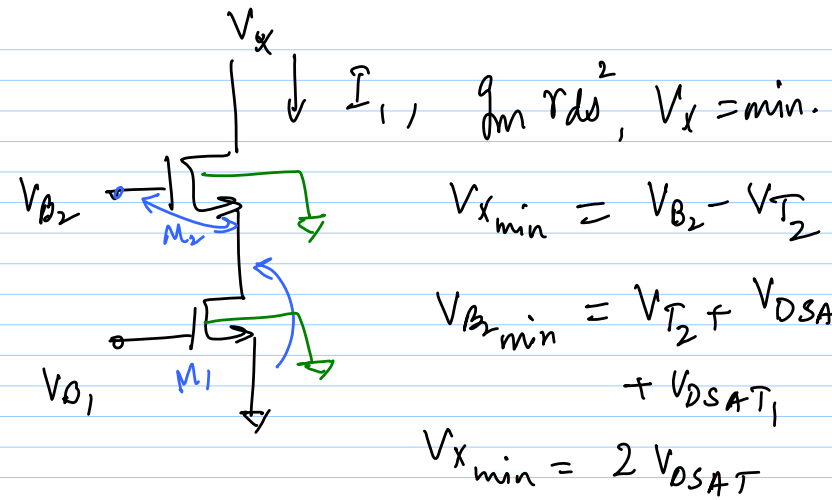


$$g_m r_{ds}^2, V_x = \min.$$

$$V_{x \min} = V_{B2} - V_{T2}$$

$$V_{B2 \min} = V_{T2} + V_{DSAT2} + V_{DSAT1}$$

$$V_{x \min} = 2V_{DSAT}$$

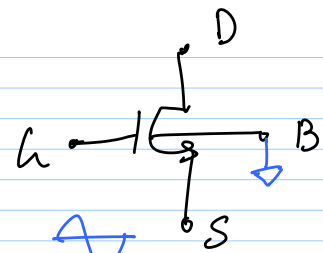

$$V_B \neq V_S$$

$$V_T = V_{T0} + \gamma \left[\sqrt{2\phi_F + V_{SB}} - \sqrt{2\phi_F} \right]$$

* $V_T > V_{T0}$

* Small-signal behaviour

24/1/14

Lec 5





$$g_m = \left. \frac{\partial I_D}{\partial V_{GS}} \right|_{V_{DS} = \text{const.}, V_{SB} = \text{const.}}$$

$$g_{m_{bs}} = \frac{\partial I_D}{\partial V_{BS}} = \frac{\partial I_D}{\partial V_T} \cdot \frac{\partial V_T}{\partial V_{BS}} = -g_m \cdot \frac{\partial V_T}{\partial V_{BS}}$$


$$g_{mbs} = -g_m \cdot \frac{-\gamma/2}{\sqrt{2\phi_F + V_{SB}}}$$

$$= k \cdot g_m$$

← 0.2

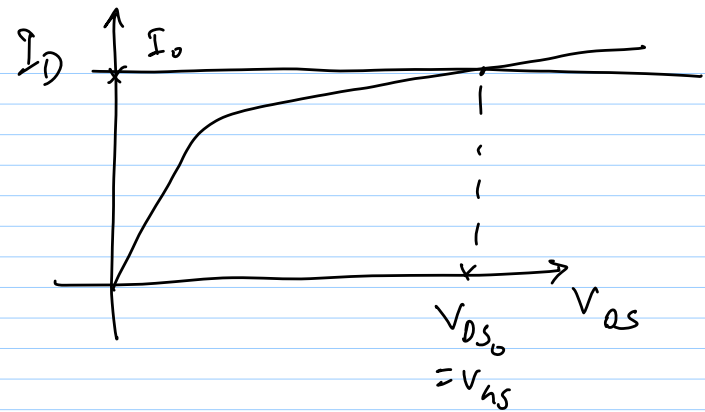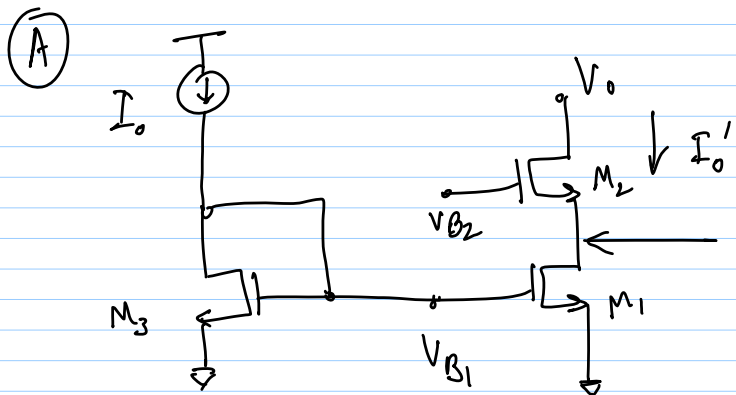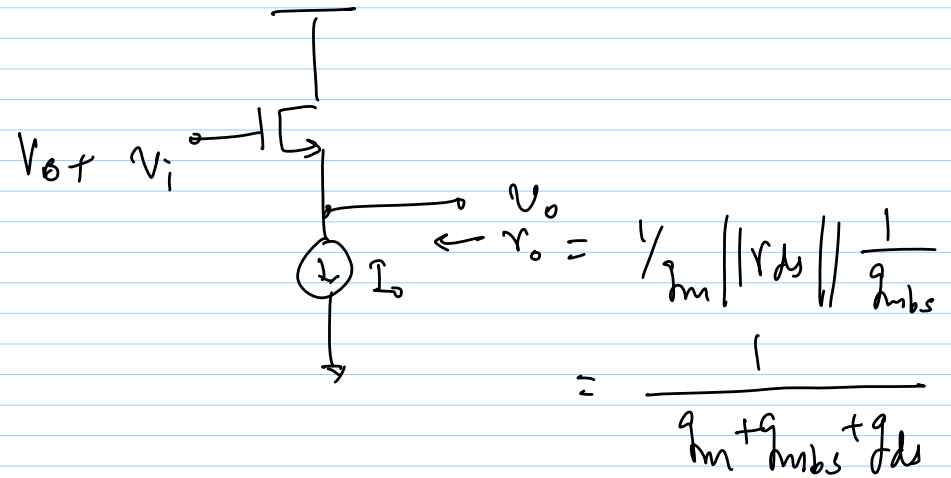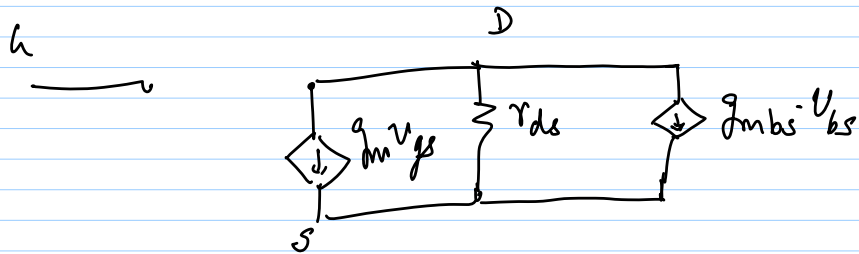

(B)

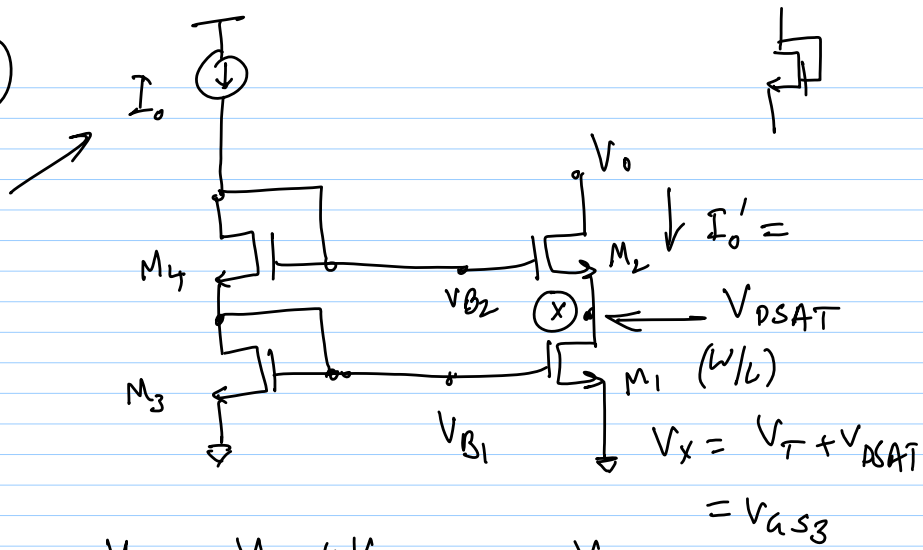


$$V_{B1} = V_T + V_{DSAT} = V_{AS1}$$

$$V_{B2} = 2V_T + 2V_{DSAT} = V_{AS3} + V_{AS4}$$

$$V_{0min} = V_T + 2V_{DSAT}$$


0.4 - 0.7V → 100mV

We want $V_{B2} = V_T + 2V_{DSAT}$

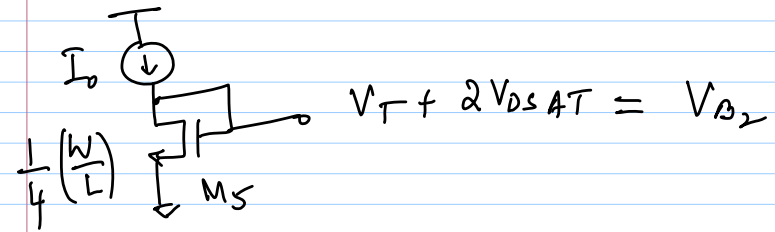

$$V_T + 2V_{DSAT} = V_{B2}$$


(C)

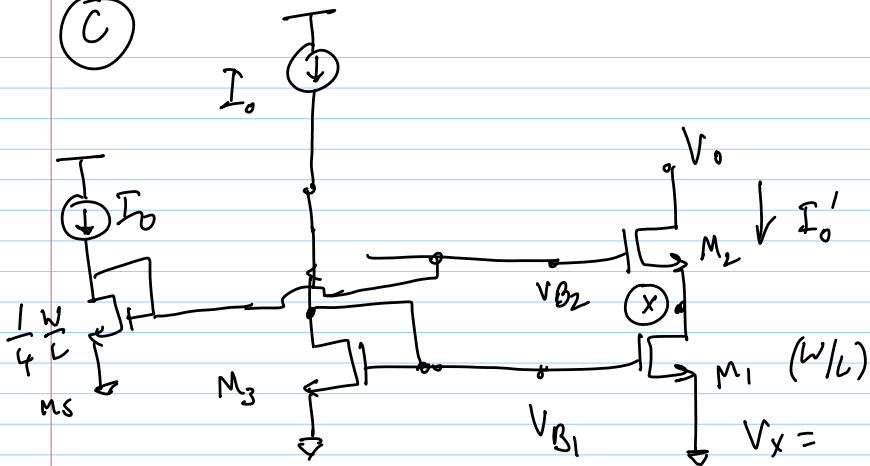


(D)

$$V_{0min}, I_0' = I_0 \Rightarrow V_{DS3} = V_{DSAT}$$
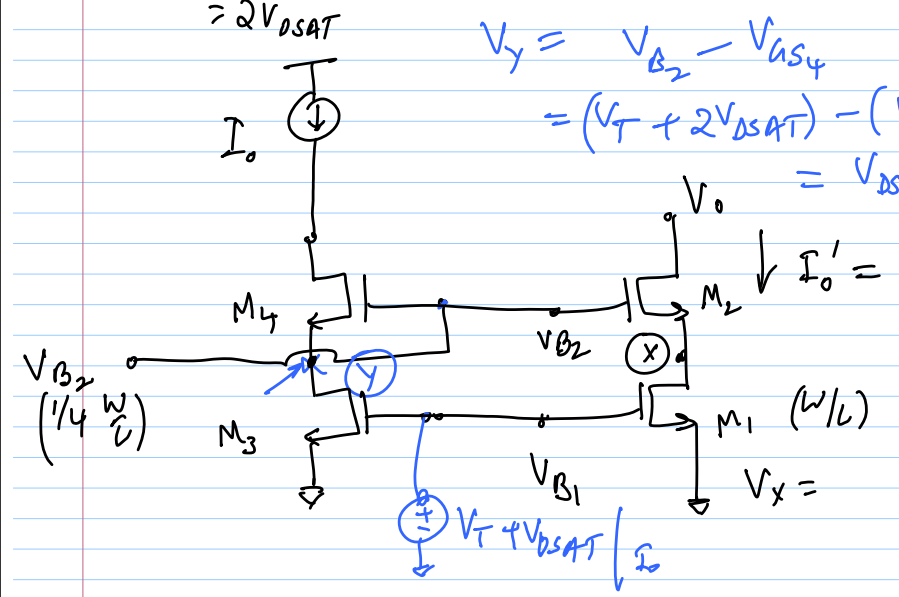
$$V_y = V_{B2} - V_{AS4} = (V_T + 2V_{DSAT}) - (V_T + V_{DSAT}) = V_{DSAT}$$



as long as $V_T \gg V_{DSAT}$

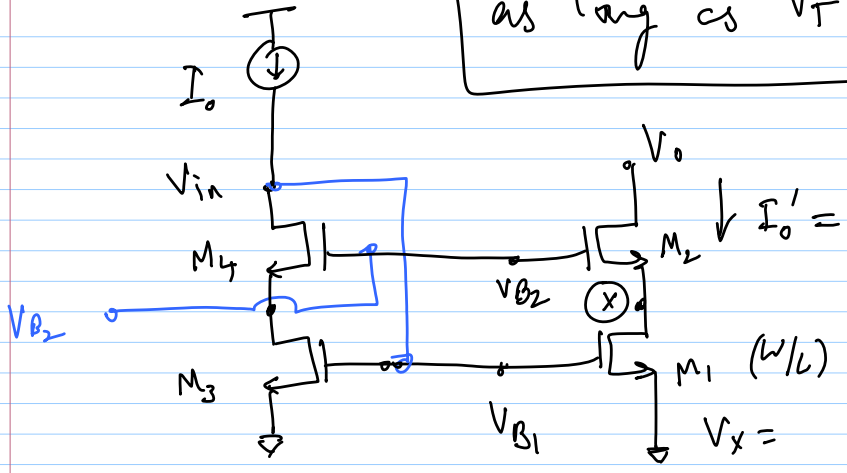

$V_{DS4} < V_{DSAT} \iff M_4$ triode

$V_{D4} = V_T + V_{DSAT}$; $V_{S3} = V_{DSAT}$

