
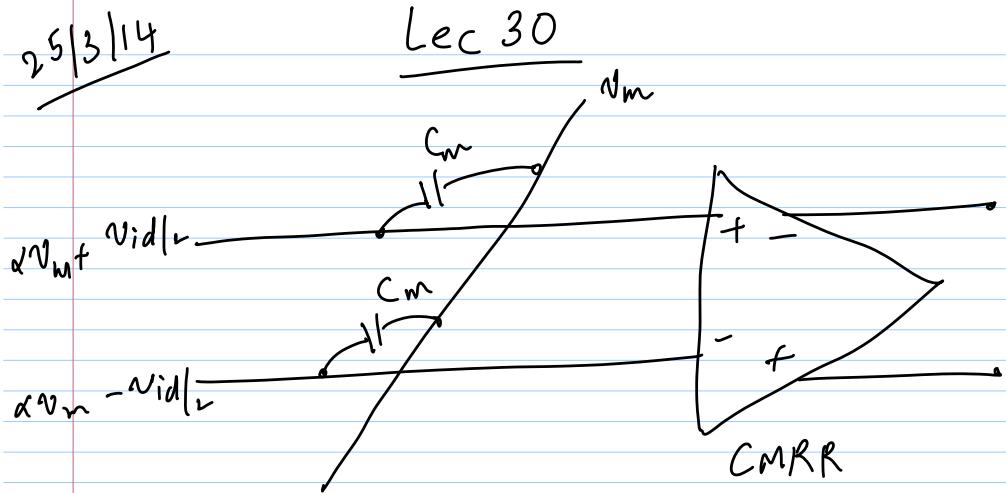


25/3/14


Lec 30

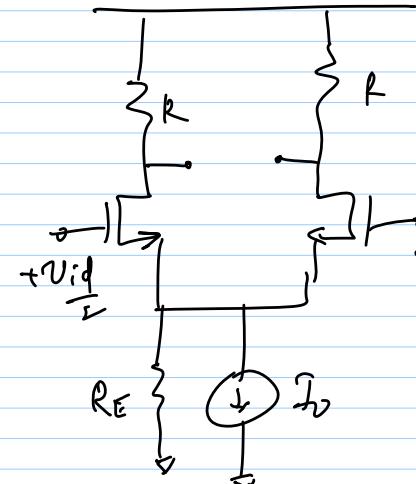

diff ckt



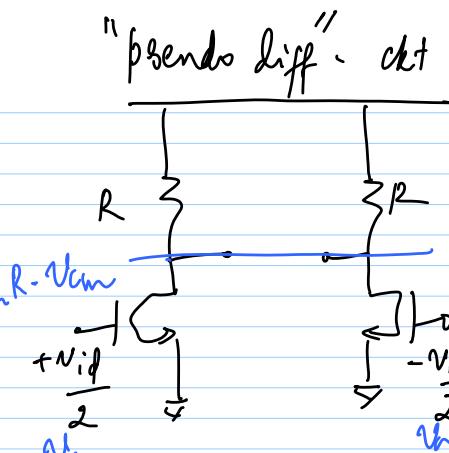
$$CM\text{ gain} = \frac{g_m R}{1 + 2 g_m R_E}$$




$$CM\text{ gain} = \frac{g_m R}{1 + 2 g_m R_E}$$



$CMRR = 1$  or  $0 \text{ dB}$

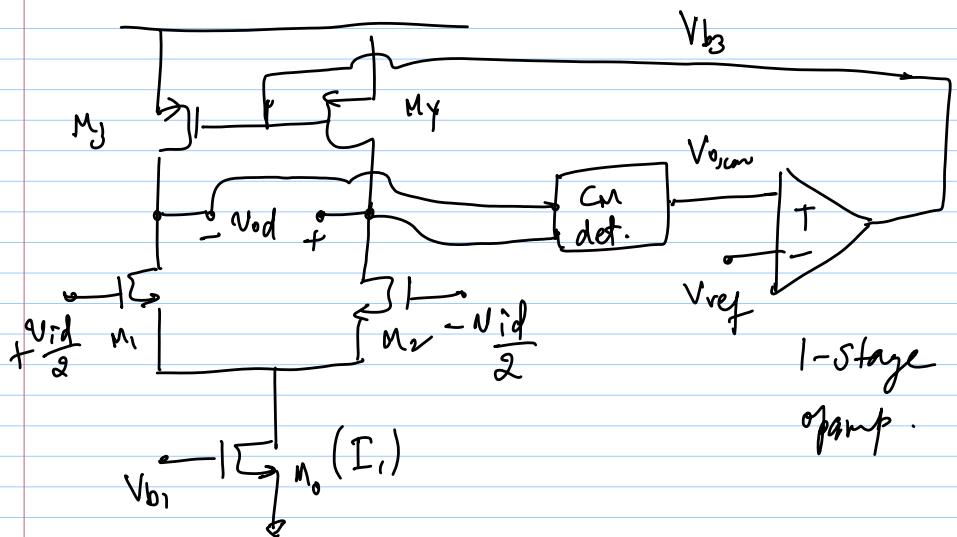



1-stage  
opamp.




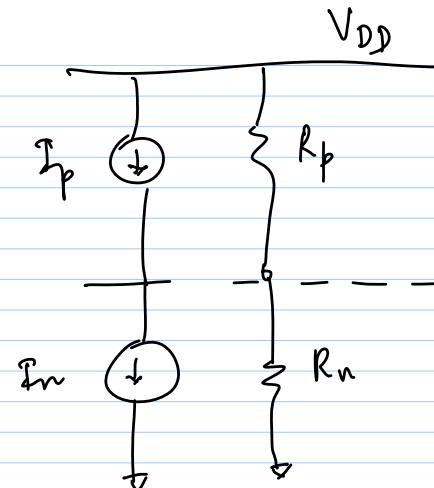



DC not  
well defined

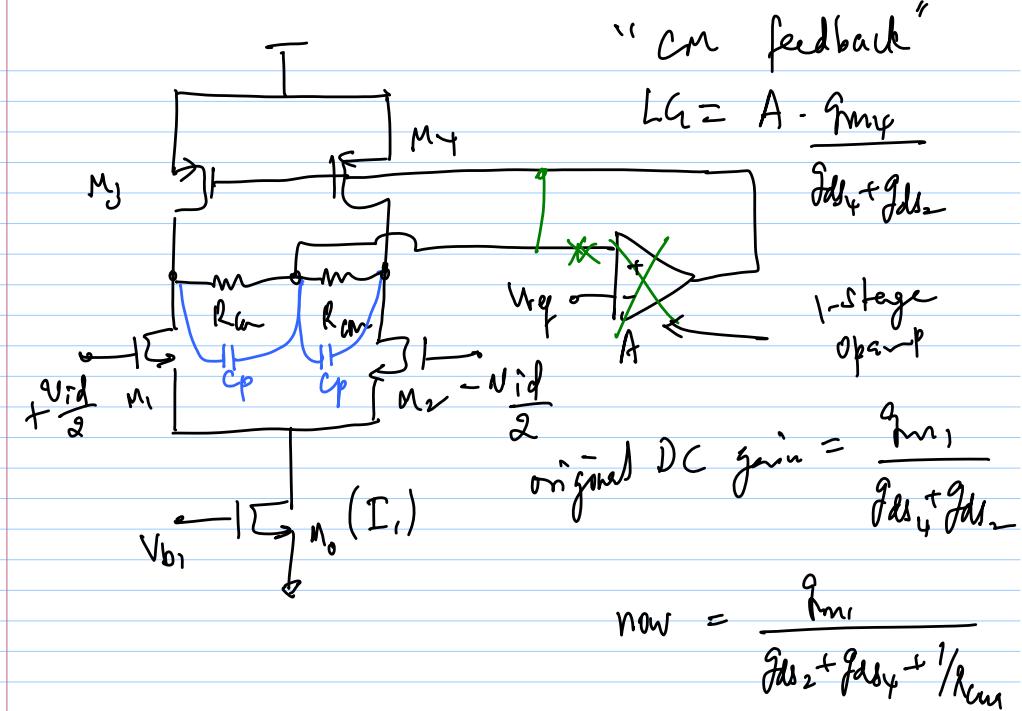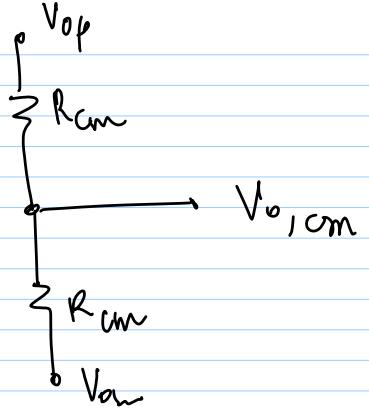

We want large  $R_{cm}$

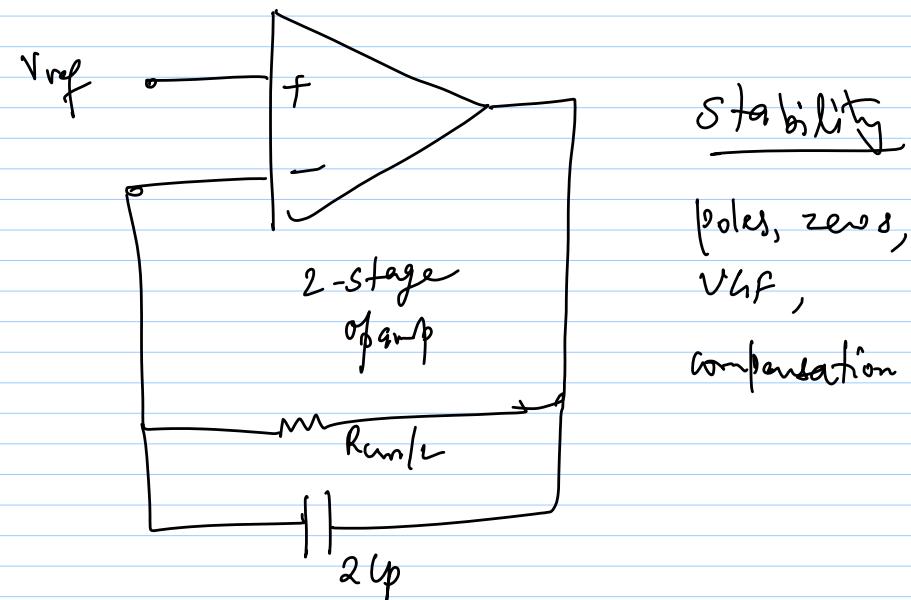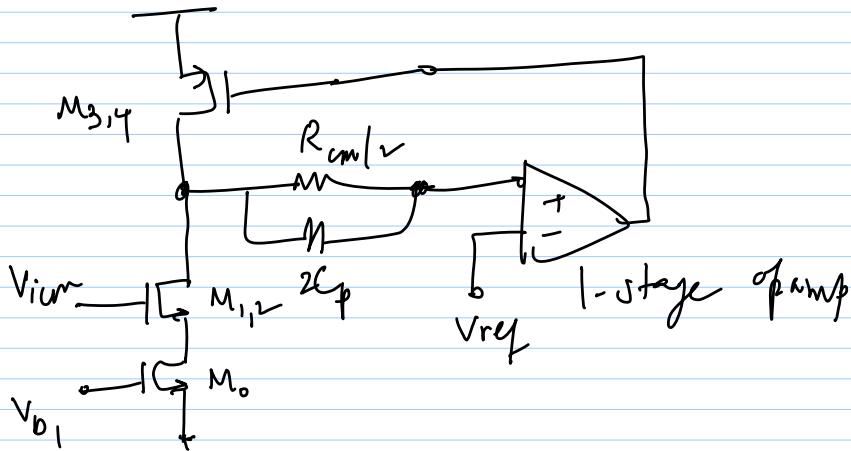

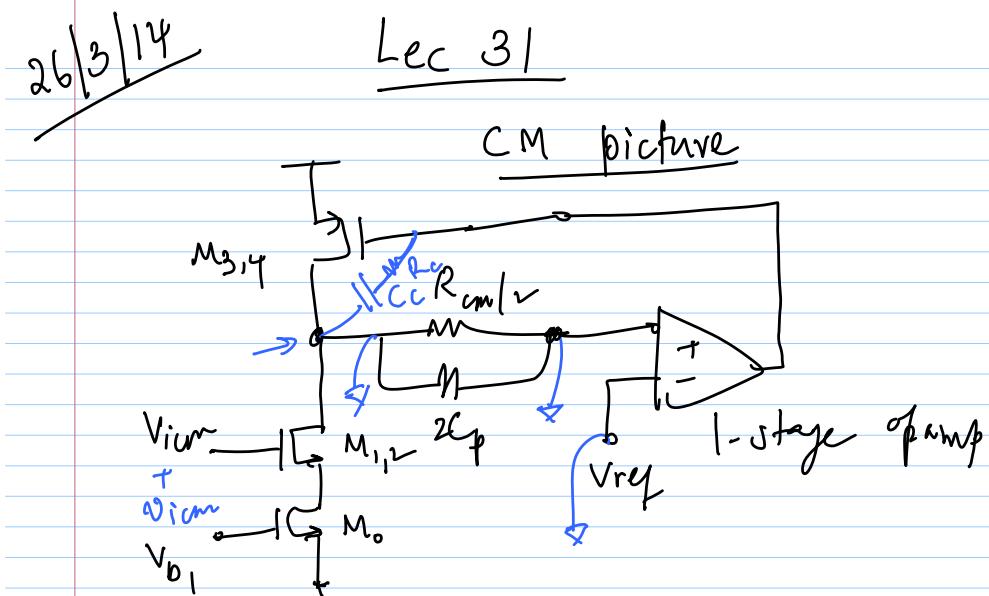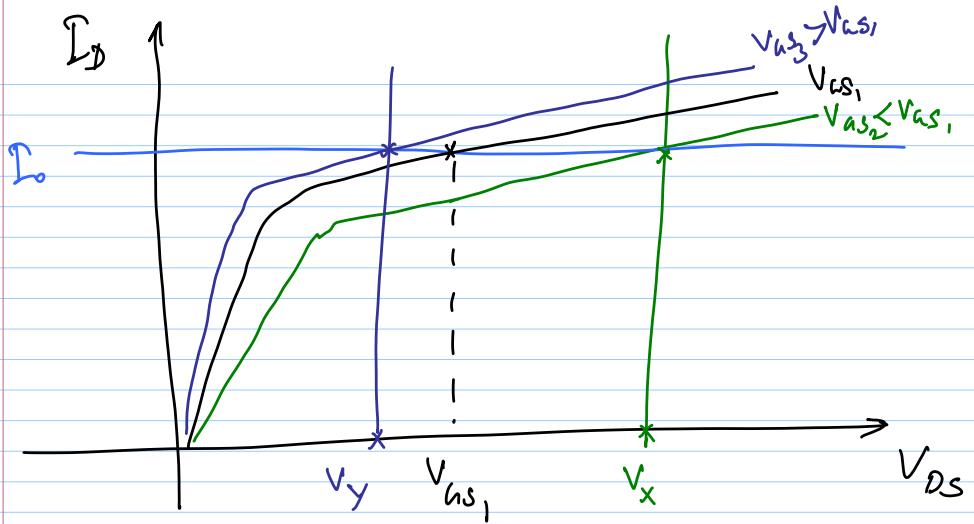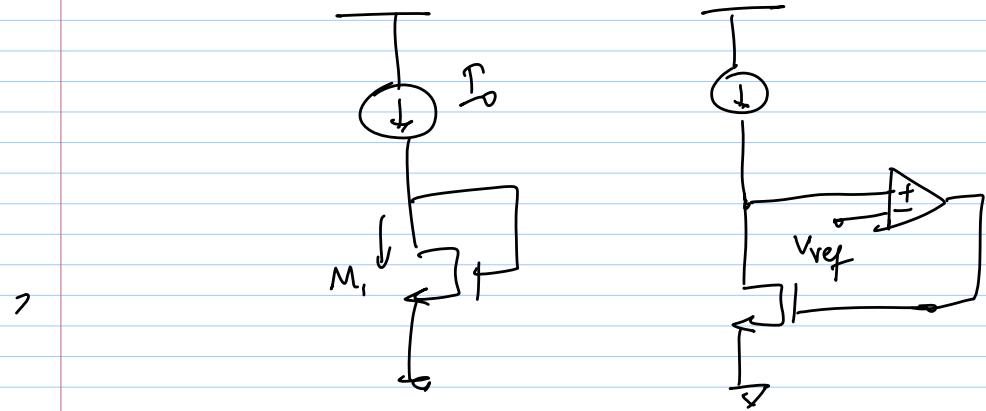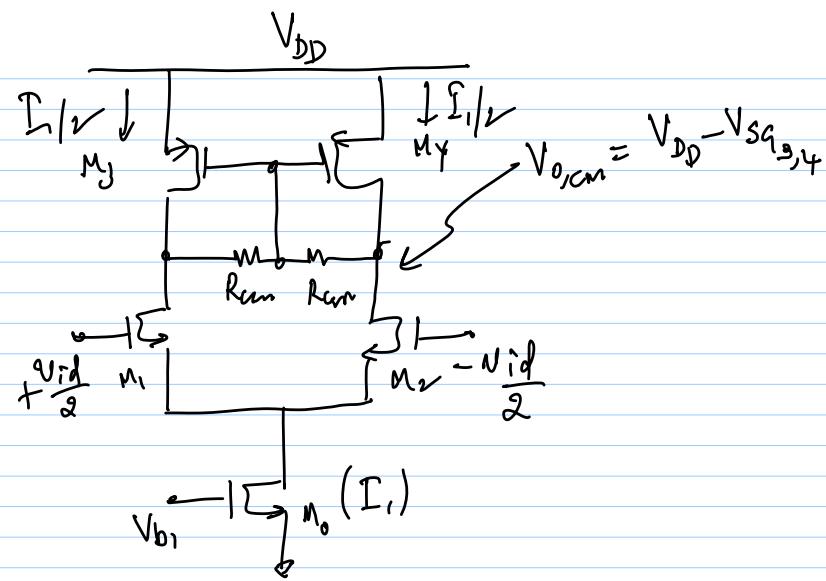


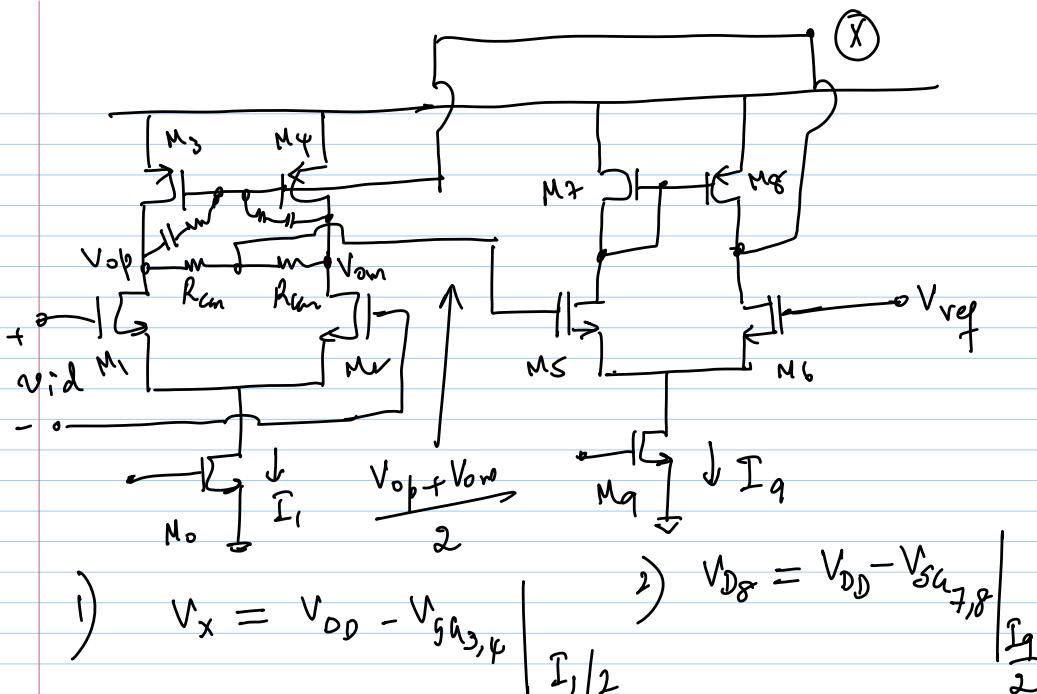


# Measure  $V_{0,cm}$

- + ve f.b. to ensure that  $V_{com} \rightarrow V_{ref}$
- $(V_{com} - V_{ref})$  depends on  $L - h_{CMFB}$


$$\left. \frac{V_{DD} - V_{SG_{3,4}}}{I_2} \right|_{\frac{T_1}{2}} = \left. \frac{V_{DD} - V_{SG_{7,8}}}{I_2} \right|_{\frac{T_1}{2}}$$

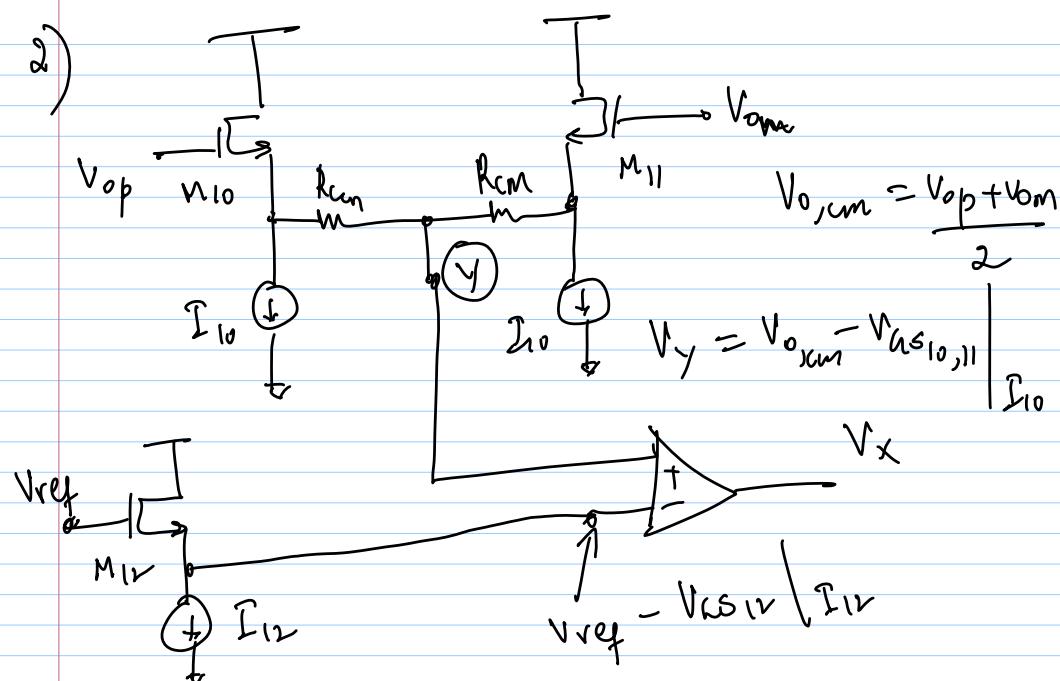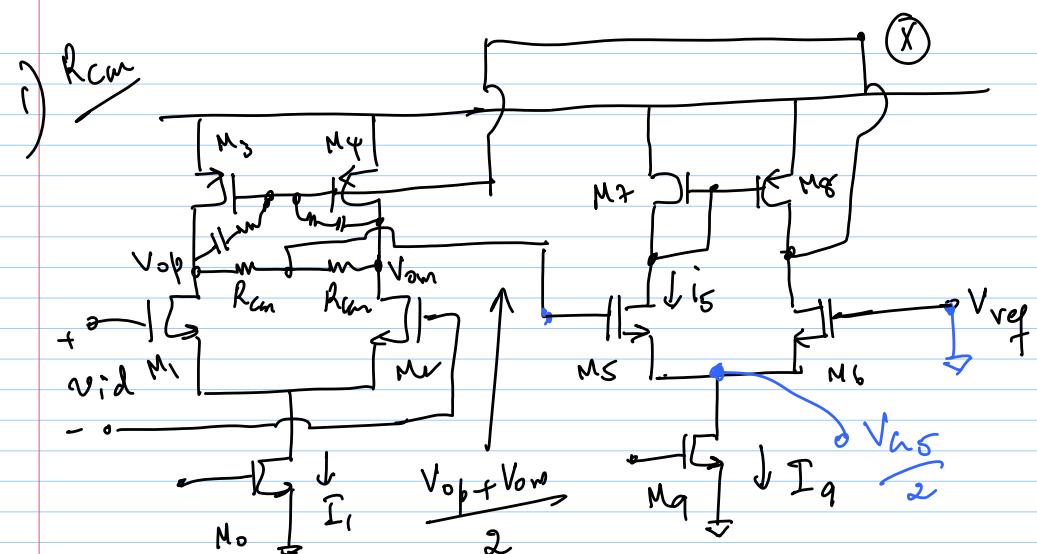$\Rightarrow$  equal current densities in  
 $M_{3-4}$  &  $M_{7-8}$




$$V_{CS,10,11} \left| I_{10} \right. = V_{MS,12} \left| I_{12} \right.$$

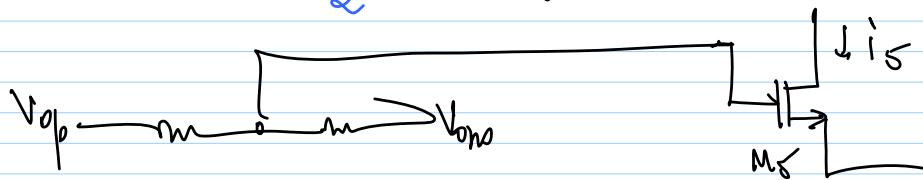3)  $i_S = \frac{g_{MS}}{2} \left[ \frac{V_{op} + V_{om}}{2} \right]$




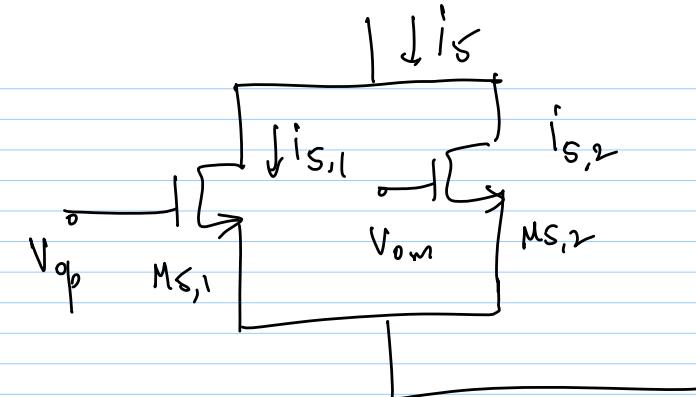+ (2) & (3) can be used only when swings are low.



$$i_S,1 = \frac{g_{MS}}{2} \cdot V_{op}; i_S,2 = \frac{g_{MS}}{2} \cdot V_{om}$$
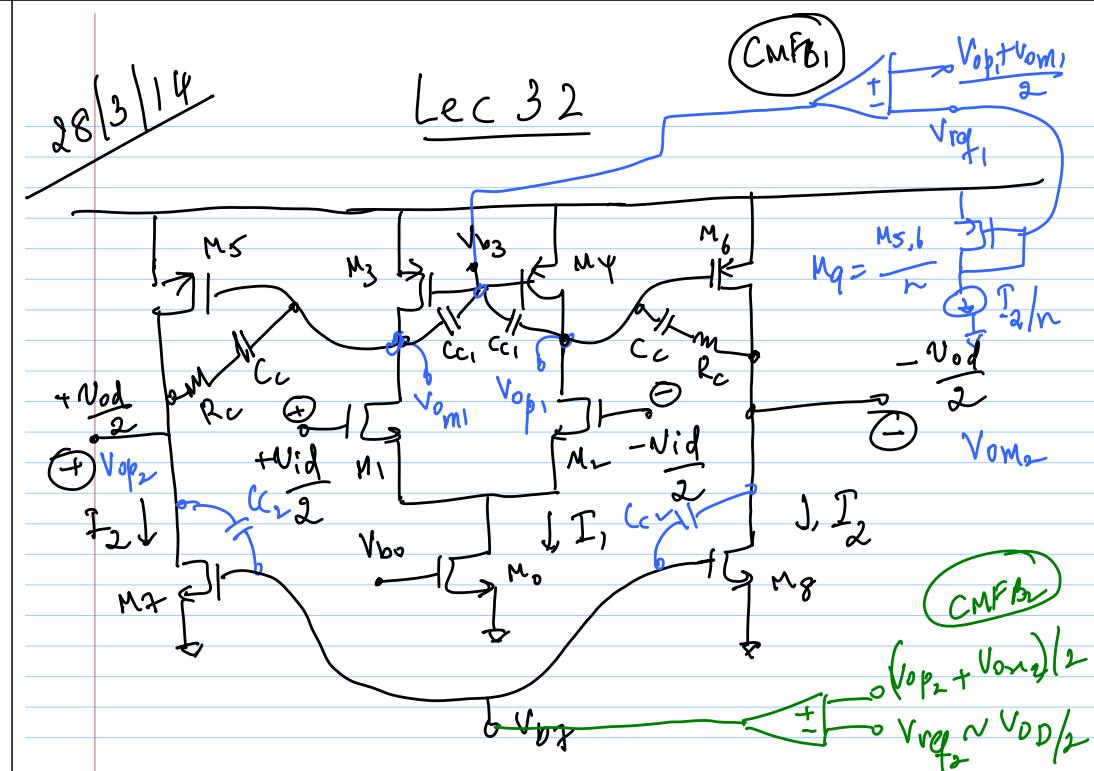
$$i_S = i_S,1 + i_S,2 = \frac{g_{MS}}{2} \left[ \frac{V_{op} + V_{om}}{2} \right]$$



$$V_{o,cm_1} = V_{DD} - V_{S_{CM3,4}} \Big|_{I_1/I_2} = V_{DD} - V_{S_{CM5,6}} \Big|_{I_2}$$

$$V_{o,cm_2} = \frac{V_{DD}}{2} \text{ (usually)}$$

- \*  $M_9$  &  $M_{5,6}$  have same current density
- \* Resistive CM detector for 2nd stage  
→ large swings  
→ DC gain from the 1st stage
- \* Active CM det. for 1st stage  
→ small swings  
→ DC gain

- \*  $V_{o,cm_1}$  → set by gates of  $M_0$  or  $M_{3-4}$
- \*  $V_{o,cm_2}$  → set by gates of  $M_{7-8}$ ,  $M_{5-6}$  or  $M_{3-4}$
- \* Single CMFB loop to set both  $V_{o,cm_1}$  &  $V_{o,cm_2}$  is possible
- \* Single  $R_C - C_C$  to compensate both CM & DM

- \* CMFB, opamp → nmos i/p stage,  
same I density ← pmos active cm load  
as  $M_{3-4}$
- \* CMFB, opamp → pmos i/p stage  
same I density ← nmos CM load  
as  $M_{7-8}$

