
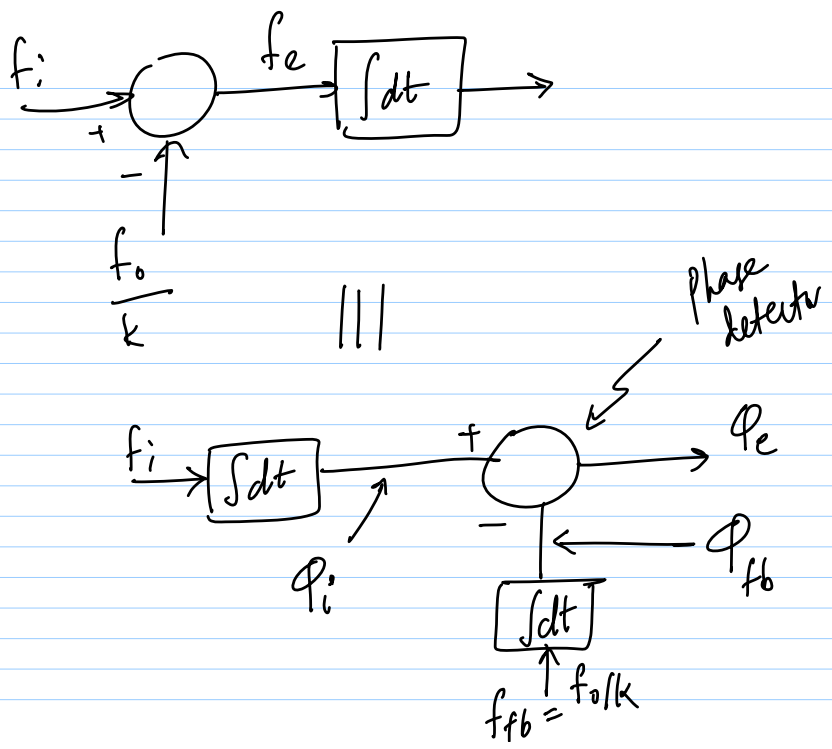
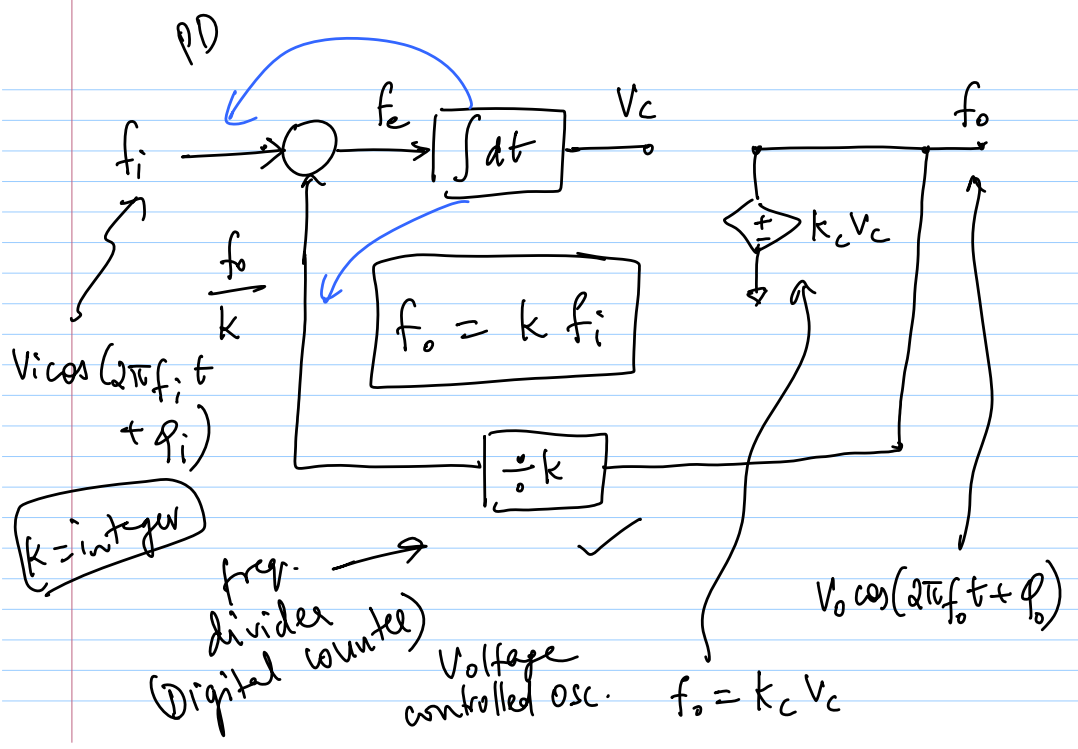


7/4/14

Lec 33

Phase locked loops

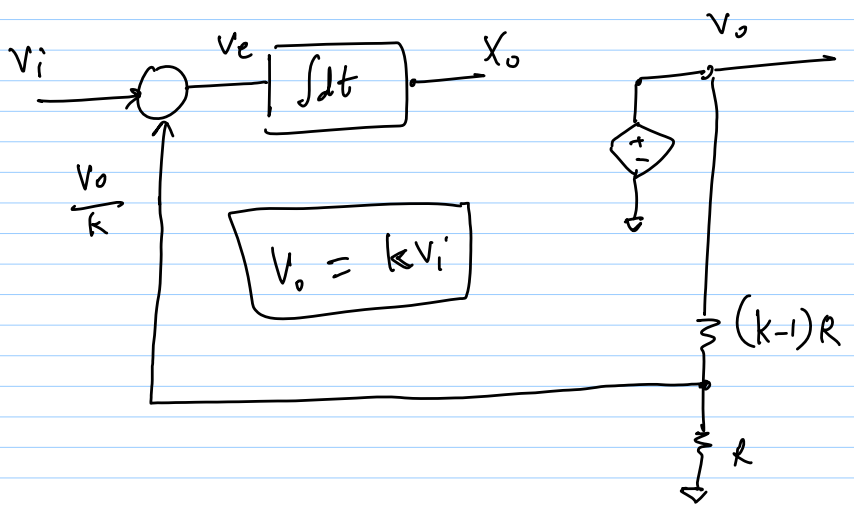


$$V = V_i \cos(2\pi f_i t + \theta)$$

$$\phi_i = 2\pi f_i t + \theta$$


$$f = \frac{1}{2\pi} \frac{d\phi_i}{dt} = f_i + \frac{1}{2\pi} \frac{d\theta}{dt}$$

VCO

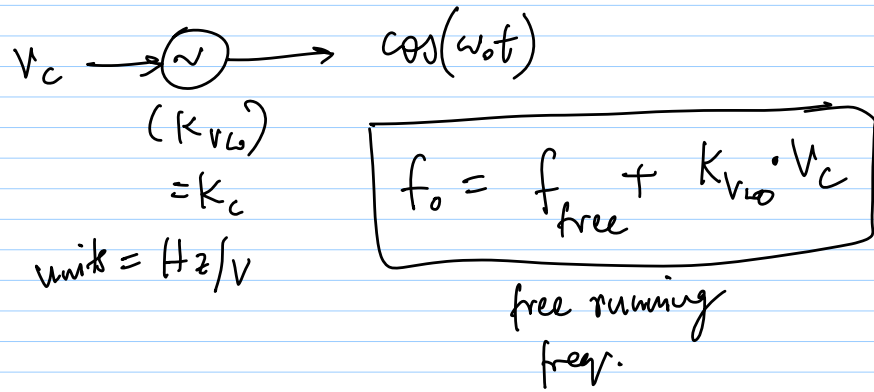

1) PD

a) Multiplier type PD

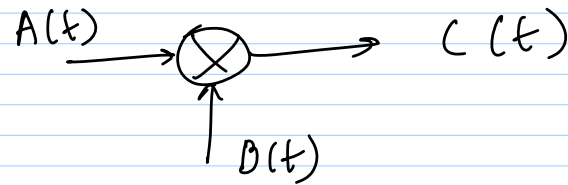


$$A(t) = A \sin(\omega_a t + \theta_a) \quad (\text{Sine})$$
$$B(t) = B \left[\frac{4}{\pi} \cos(\omega_b t + \theta_b) \quad (\text{sq. wave}) \right. \\ \left. + \frac{4}{5\pi} \cos(3\omega_b t + \theta_b) + \dots \right]$$

$$C(t) = A(t) \times B(t)$$

$$= \frac{4AB}{\pi} \left[\sin(\omega_a t + \theta_a) \cdot \cos(\omega_b t + \theta_b) \right. \\ \left. + \frac{1}{3} \sin(\omega_a t + \theta_a) \cos(3\omega_b t + \theta_b) \right. \\ \left. + \dots \right]$$

$$= \frac{2}{\pi} AB \left[\sin\{(\omega_a - \omega_b)t + \theta_a - \theta_b\} \quad \text{DC or } \omega_b \\ + \sin\{(\omega_a + \omega_b)t + \theta_a + \theta_b\} + \dots \right]$$

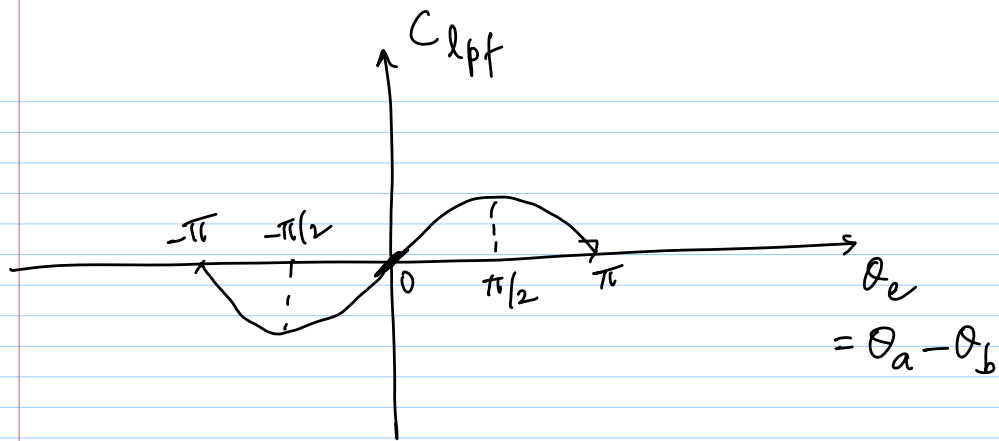
LPF gives $(\omega_a - \omega_b)t$ & $(\theta_a - \theta_b)$
term



8/4/14

Lec 34

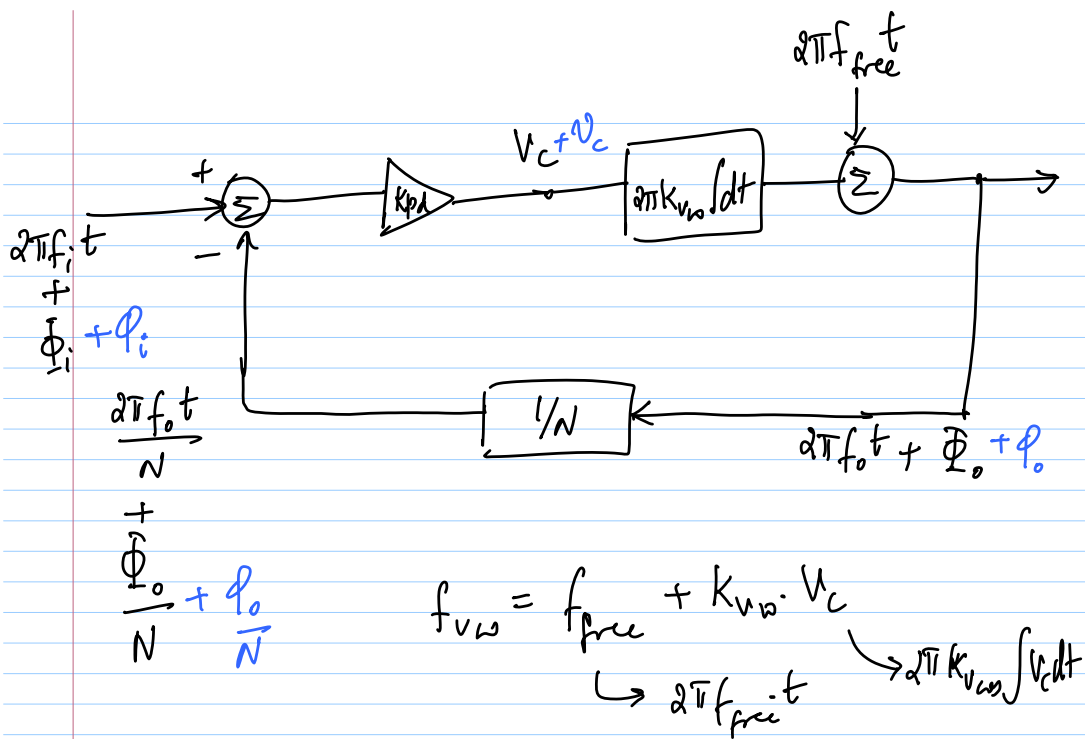- b) XOR PD
- c) Digital PFD (phase freq. det.)




In steady state

$$f_o = f_i \cdot N$$

$$V_c = k_{pd} \left[\Phi_i - \frac{\Phi_o}{N} \right]$$

$$= \left[\frac{N f_i - f_{free}}{k_{vco}} \right]$$

Incremental picture


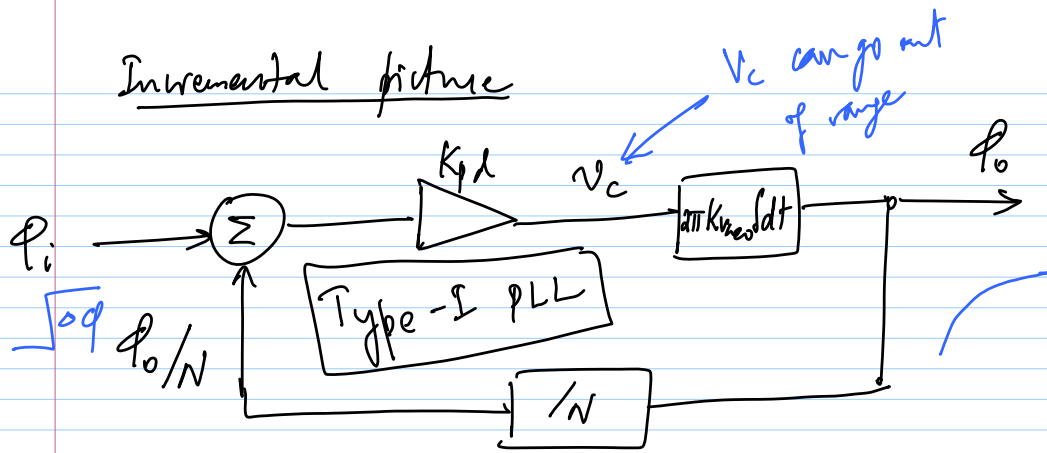



$$\text{Loop gain } L(s) = \frac{2\pi K_p K_{vco}}{Ns}$$


$$\frac{\phi_o}{\phi_i}(s) = N_o \frac{1}{1 + \frac{Ns}{2\pi K_p K_{vco}}}$$



$$\text{CL BW } f_{3dB} = \frac{K_p K_{vco}}{N}$$
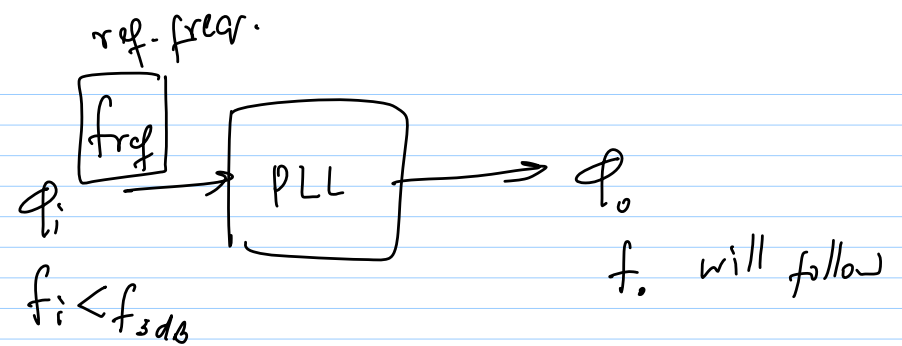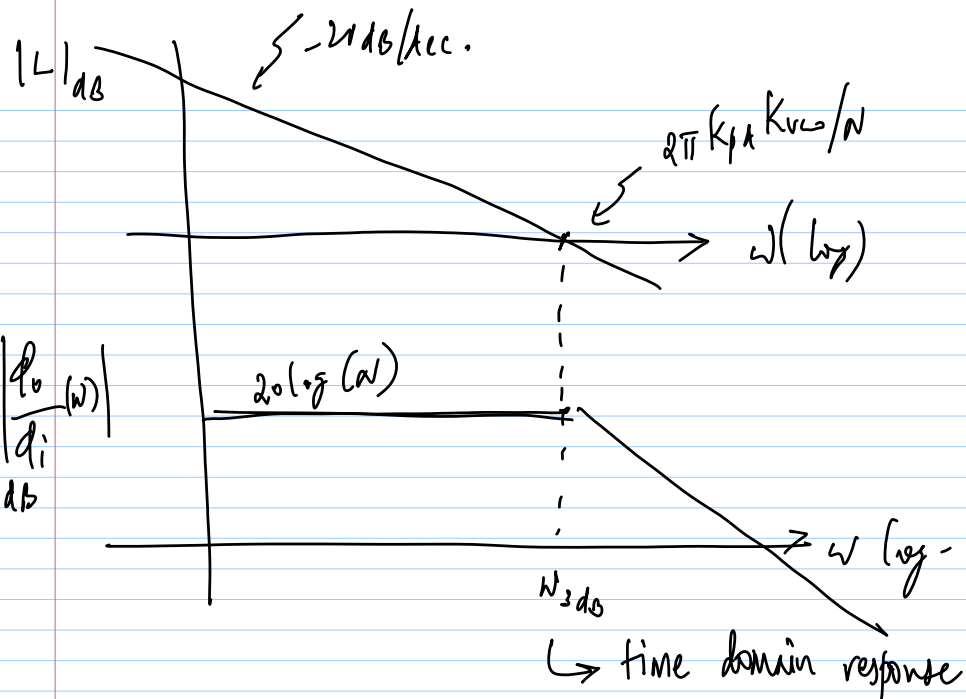
$$\omega_{3dB} = \frac{2\pi K_p K_{vco}}{N}$$



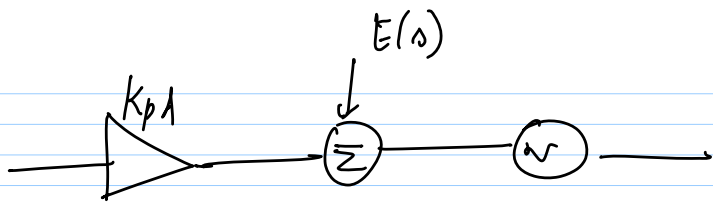

$V_c + \Delta V_c$

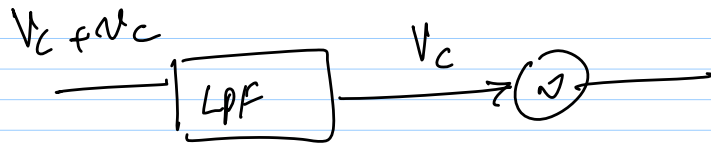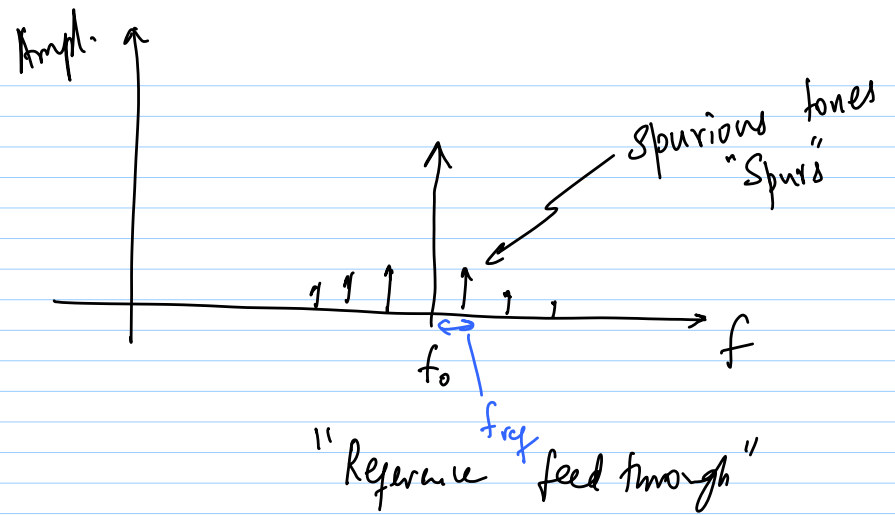 $f_o = f_{free} + K_{VCO} \cdot V_c$
 $\cos(2\pi f_o t)$




↳ affects ω_{sdb}
 slows down PLL
 stability

9/4/14

Lec 35



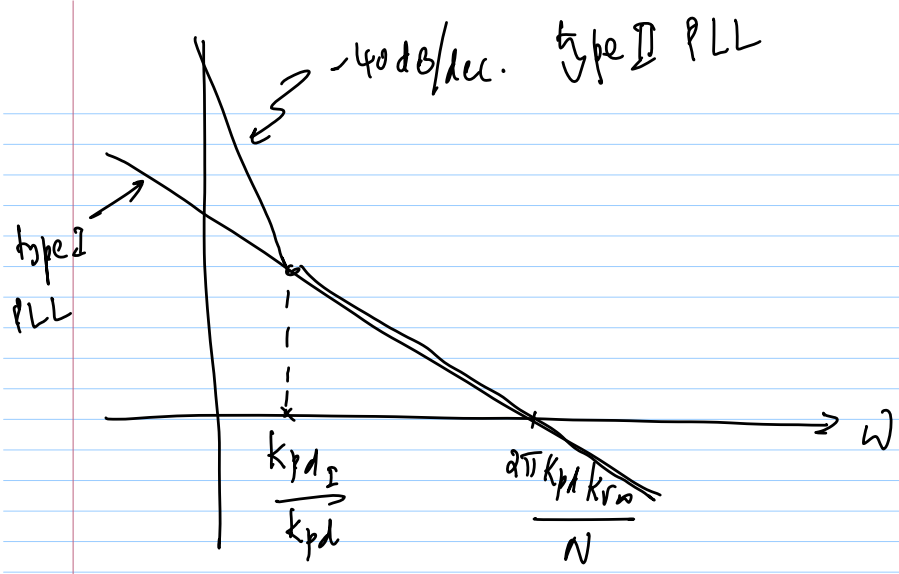
ref. feedthrough \leftrightarrow BW of PLL
 $\uparrow f_{sdb} \Rightarrow$ ref. feedthrough gets worse




$$L(s) = \frac{2\pi K_{pdI} K_{vco}}{N s^2} \left[1 + \frac{K_{pd} \cdot s}{K_{pdI}} \right]$$

$$\frac{\Phi_{out}}{\Phi_{in}}(s) = N \cdot \frac{\left(1 + \frac{K_{pd} \cdot s}{K_{pdI}} \right)}{s^2 \cdot \frac{N}{2\pi K_{pdI} K_{vco}} + s \frac{K_{pd}}{K_{pdI}} + 1}$$
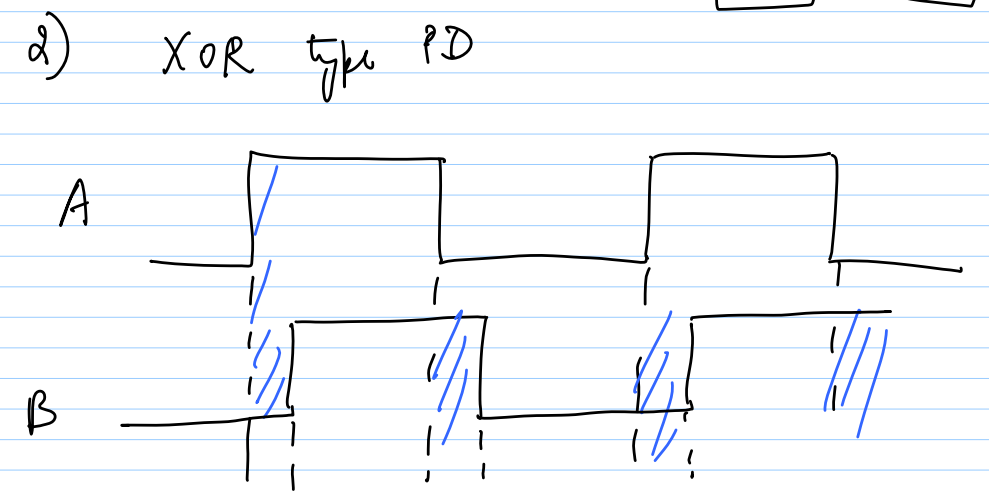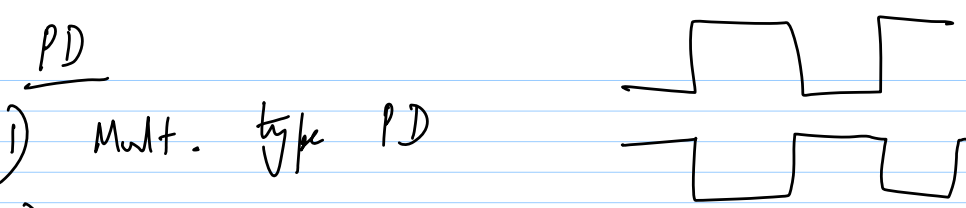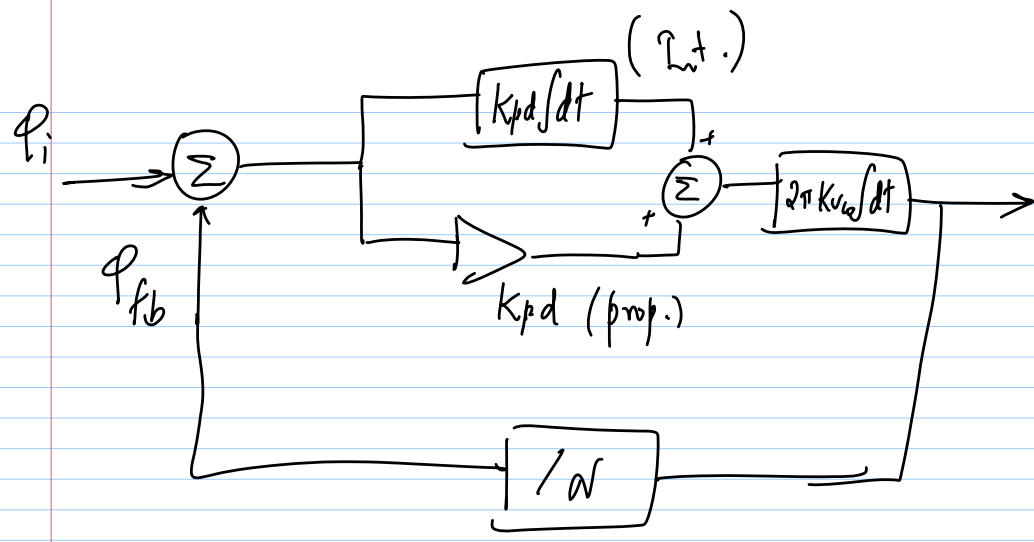
$$\omega_n = \sqrt{\frac{2\pi K_{pdI} K_{vco}}{N}} ; Q = \frac{\sqrt{N K_{pdI} / 2\pi K_{vco}}}{K_{pd}}$$




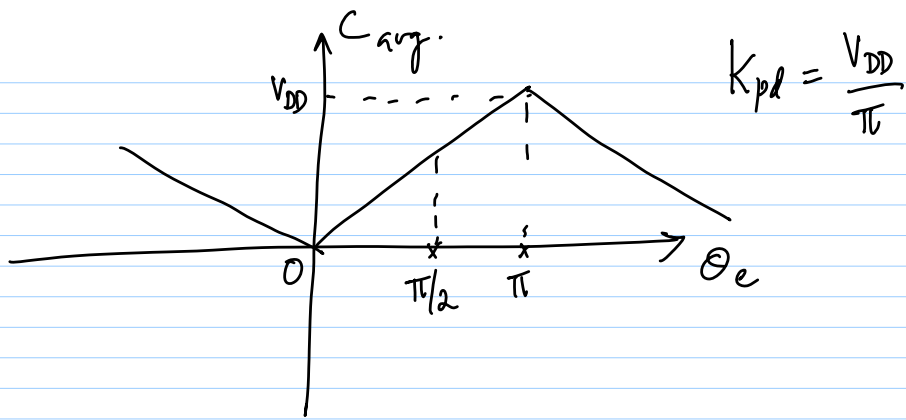



disadv.

- a) monotonic over only certain ranges
- b) operation is a function of duty cycle

3) Tristate PFD

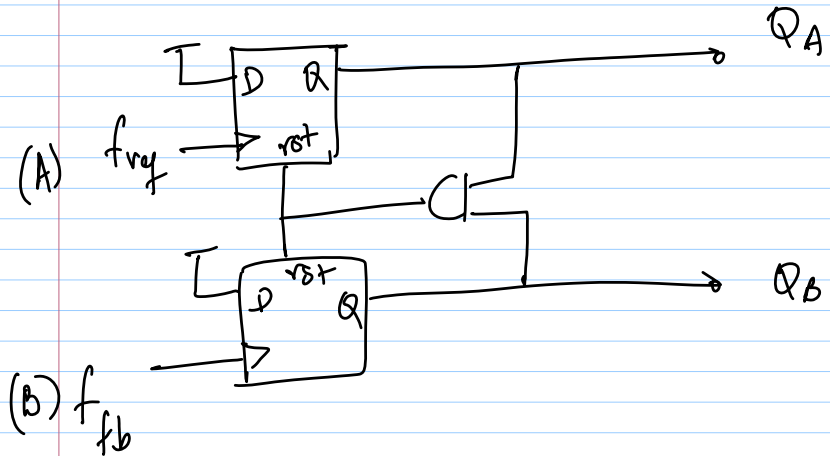


Q_A	Q_B	State	$\theta_e = 0$
0	0	0	$\Rightarrow \text{avg.}(Q_A - Q_B) = 0$
0	1	-1	
1	0	+1	
1	1	prohibited (reset)	


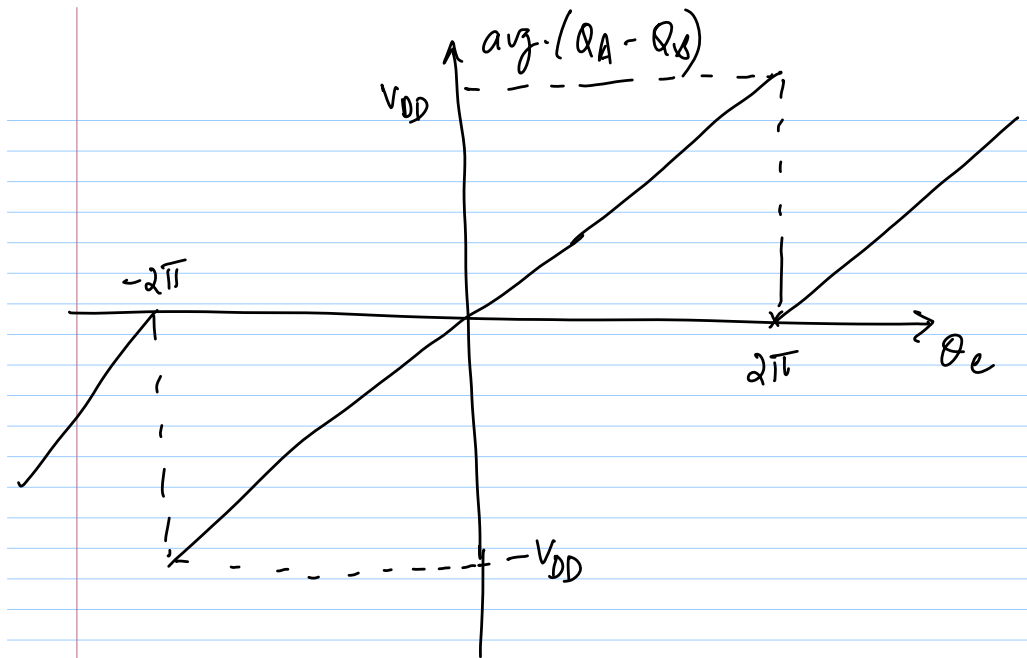
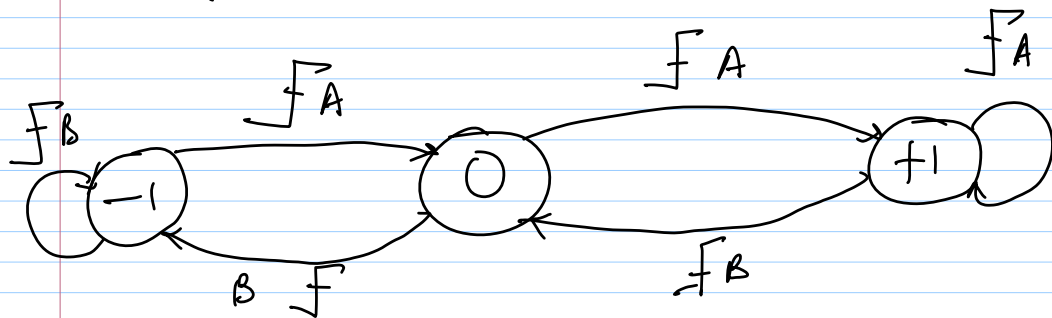


11/4/14


Lec 36


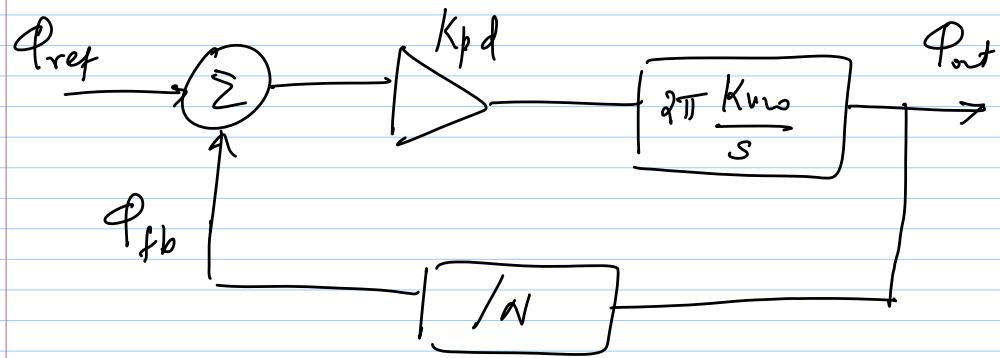

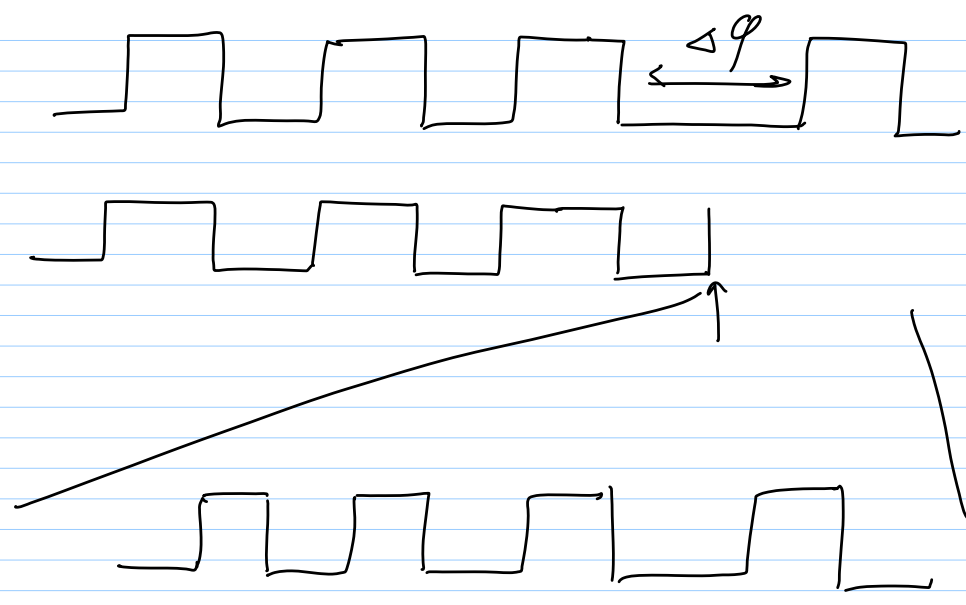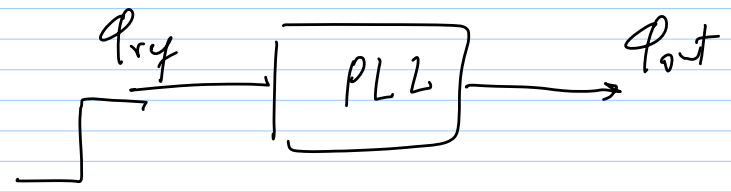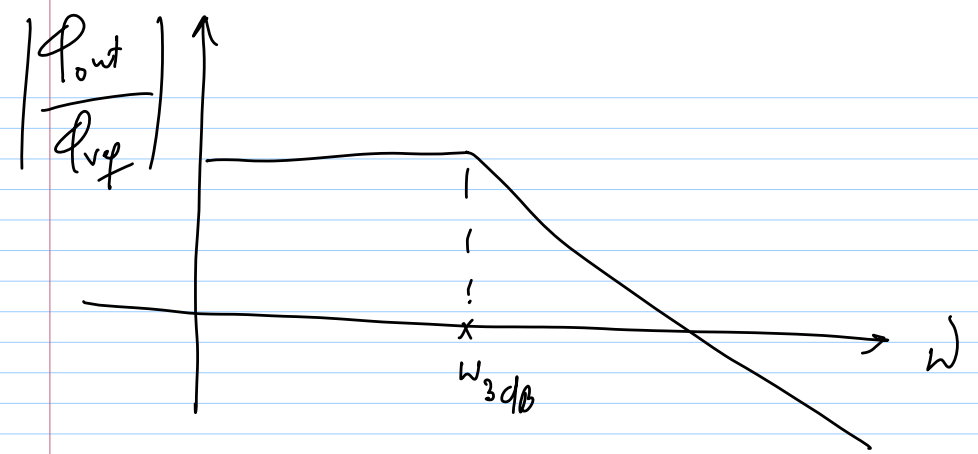
$$\frac{\phi_{out}}{\phi_{ref}}(\lambda) = N \frac{1}{1 + \frac{Ns}{2\pi K_{pd} K_{vco}}}$$



2) Ref feedthrough

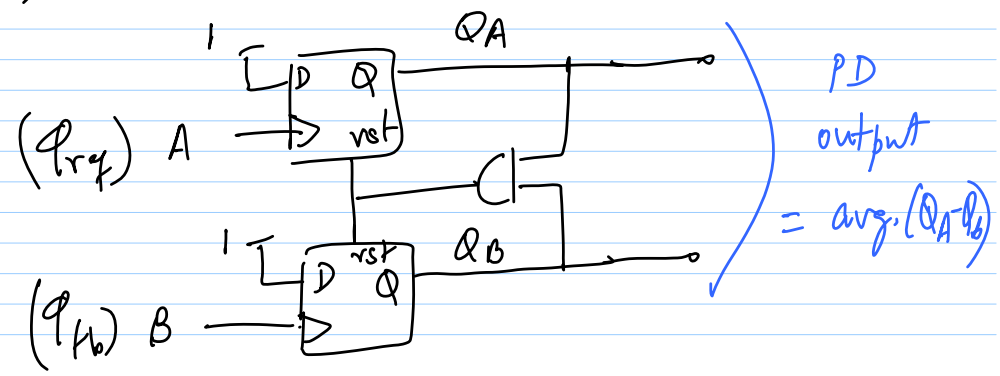

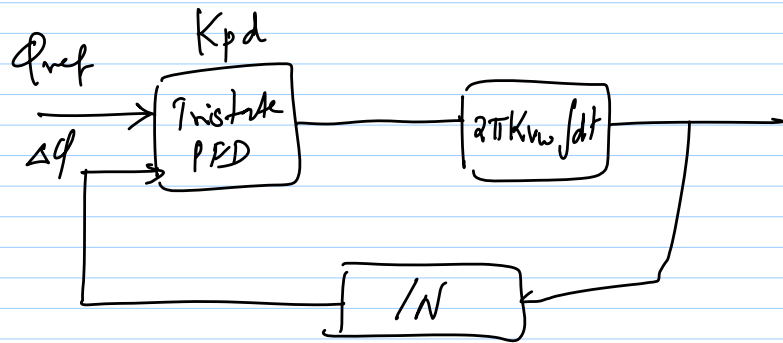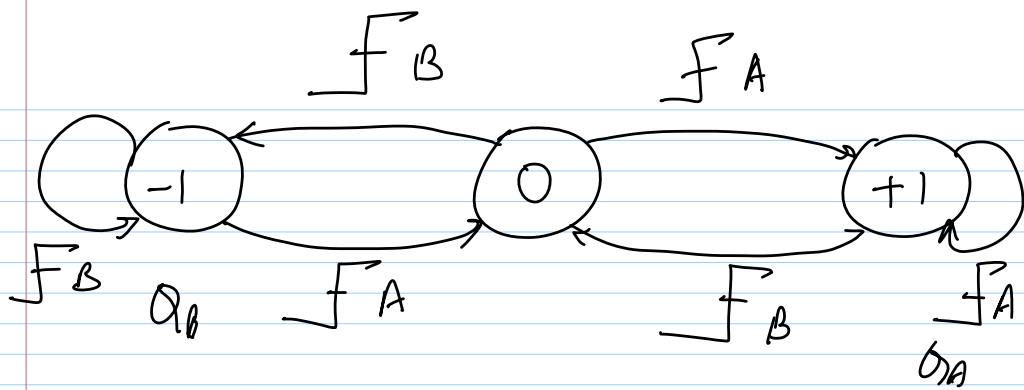


$$N f_{ref} = f_{out}$$

$$f_{out} = f_{free} + K_{vco} \cdot V_c$$

in steady state

$$V_c = \frac{N f_{ref} - f_{free}}{K_{vco}}$$
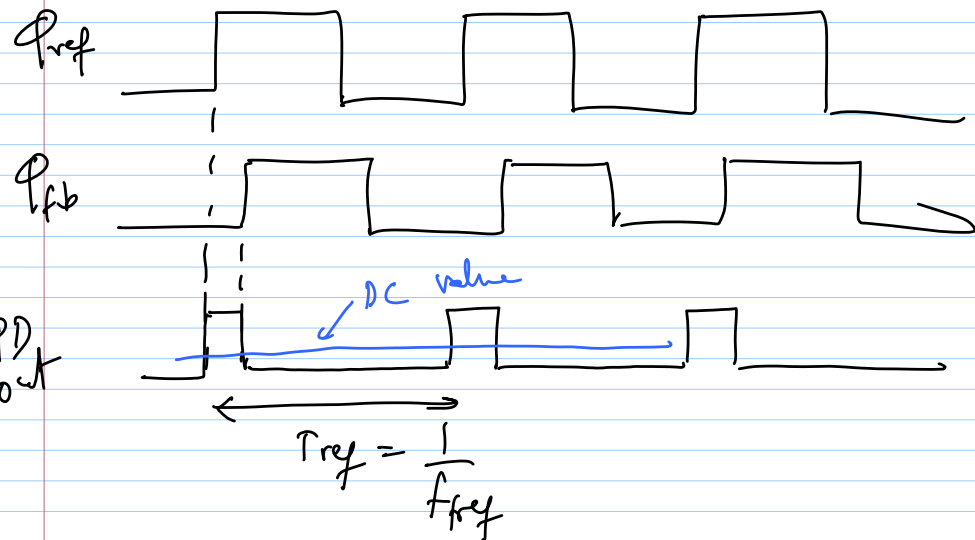
$$\Delta\phi = \frac{N f_{ref} - f_{free}}{K_{pd} K_{vco}}$$



$$V_c = V_{co} + v_c(t)$$

$$V_c(f) \rightarrow f_{ref}, 2f_{ref}, \dots$$

* Consider 1 term @ f_{ref}

$$V_{out}(t) = \cos[2\pi N f_{ref} t + b_1 \sin(2\pi f_{ref} t)]$$

assume b_1 is small


$$f_{out} = f_{free} + K_{vco} \cdot V_c$$

$$= f_{free} + K_{vco} \cdot V_{co} + K_{vco} \cdot v_c(t)$$

$$V_{out}(t) = \cos(2\pi N f_{ref} t) \cos(b_1 \sin(2\pi f_{ref} t)) \\ - \sin(2\pi N f_{ref} t) \sin(b_1 \sin(2\pi f_{ref} t))$$

If b_1 is small
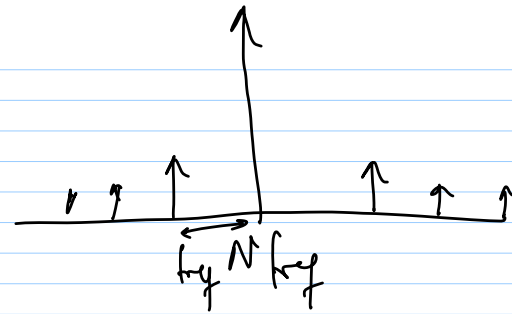
$$V_{out}(t) = \cos(2\pi N f_{ref} t) \\ - b_1 \sin(2\pi N f_{ref} t) \sin(2\pi f_{ref} t) \\ = \cos(2\pi N f_{ref} t) - \frac{b_1}{2} \cos(2\pi(N \pm 1) f_{ref} t)$$




o/p of V_{LO} is no longer periodic
@ $N f_{ref}$

$$f_{out} = f_{free} + K_{VLO} \cdot V_{CO} \\ + K_{VCO} v_c(t)$$
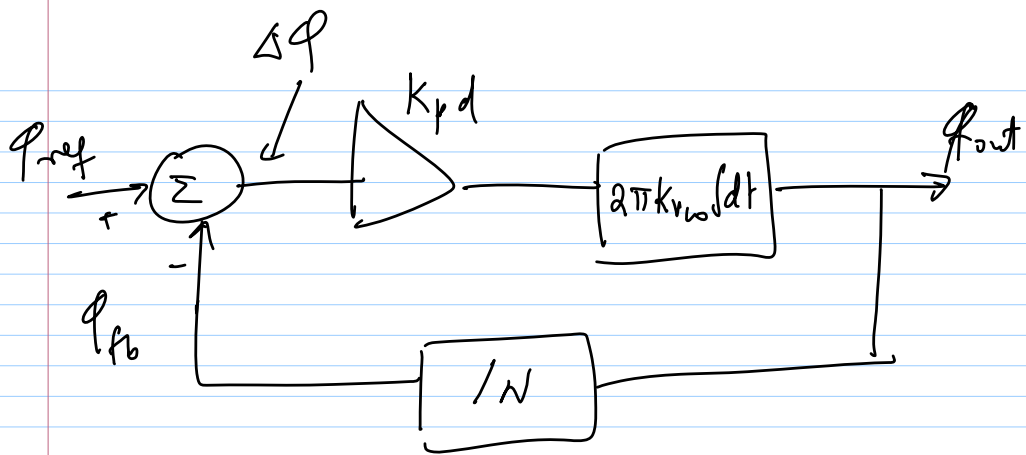
$$V_{out}(t) = \cos \left[2\pi f_{free} t + K_{VLO} \int v_c(t) dt \right]$$







$$\Delta\phi = \frac{Nf_{ref} - f_{free}}{K_{pd} K_{vco}}$$

$$\Delta\phi = 0 \text{ when } Nf_{ref} = f_{free}$$

We want $\Delta\phi = 0$ always

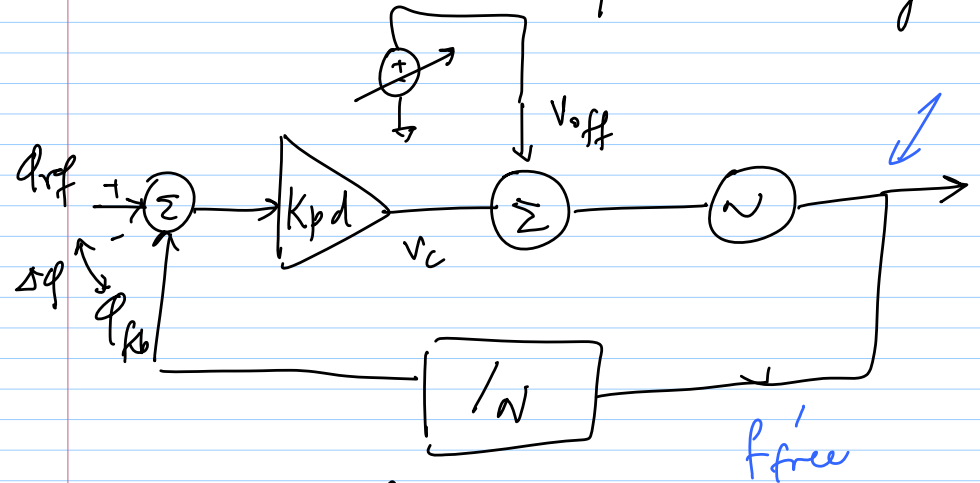

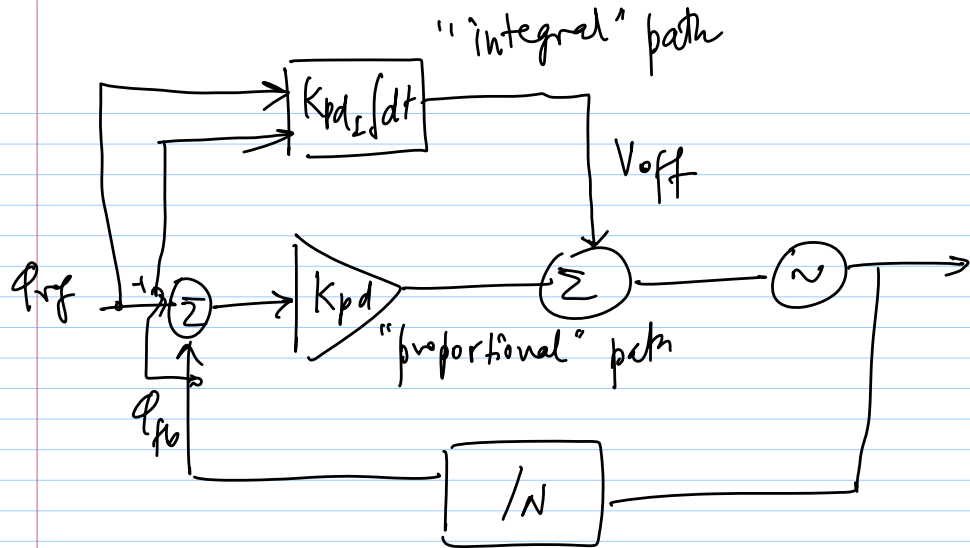
$$f_{out} = (f_{free} + K_{vco} \cdot v_{off}) + K_{vco} \cdot v_c$$





in steady state: $v_{off} = \frac{f_{out} - f_{free}}{K_{pd} K_{vco}}$

15/4/14



Lec 37

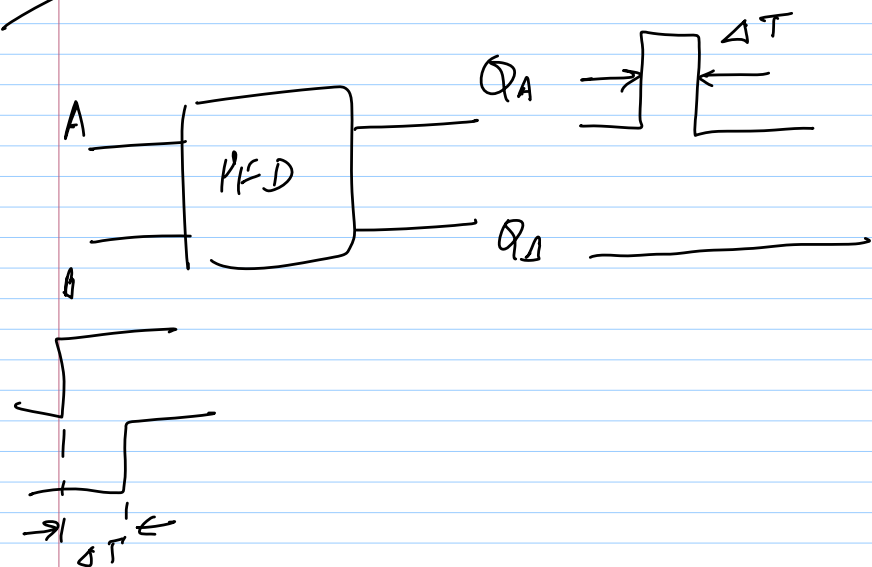


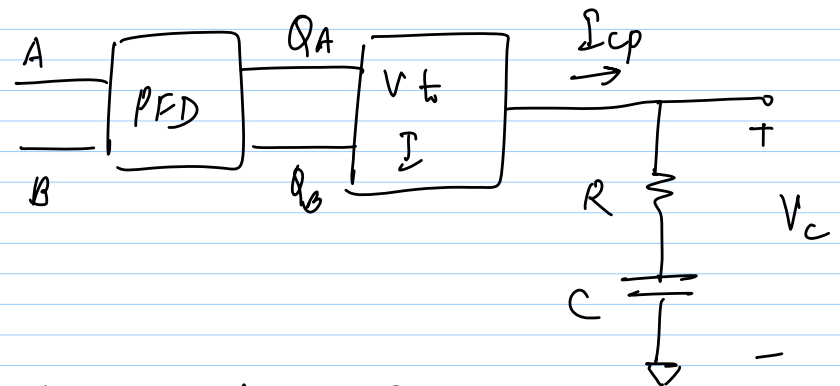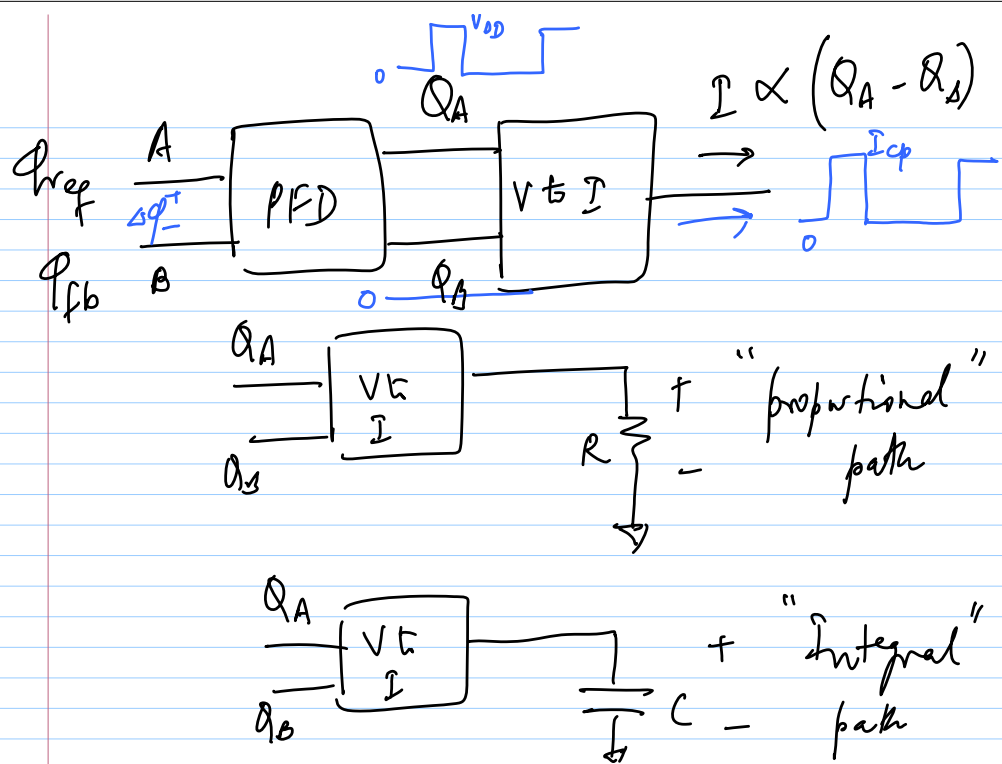

$$K_{pd} = \frac{V_{DD}}{2\pi} \cdot \frac{I_{cp}}{V_{DD}} \cdot R = \frac{I_{cp} R}{2\pi}$$


$$K_{pdz} = \frac{I_{cp}}{2\pi C}$$

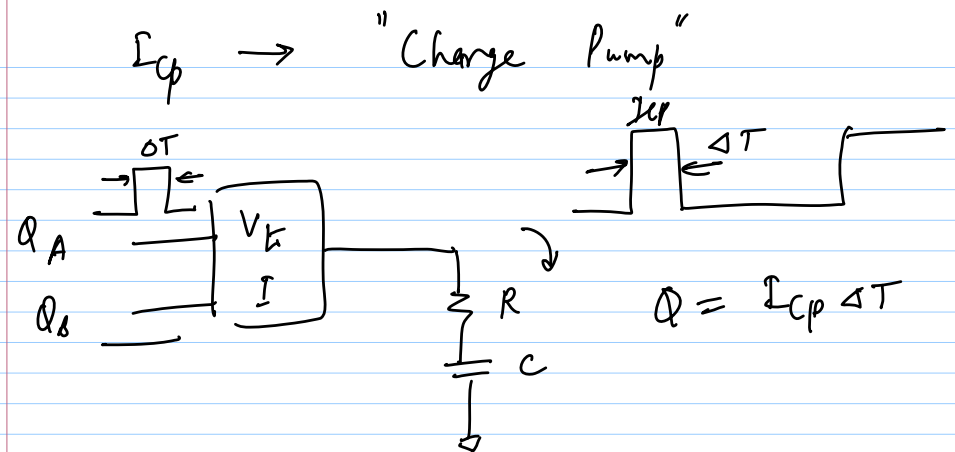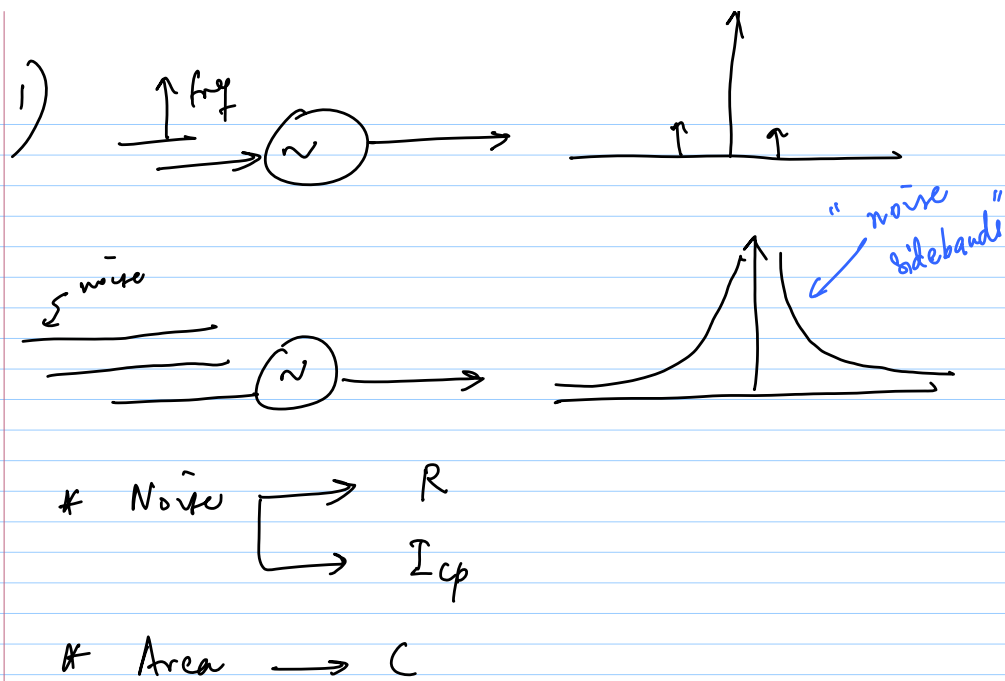

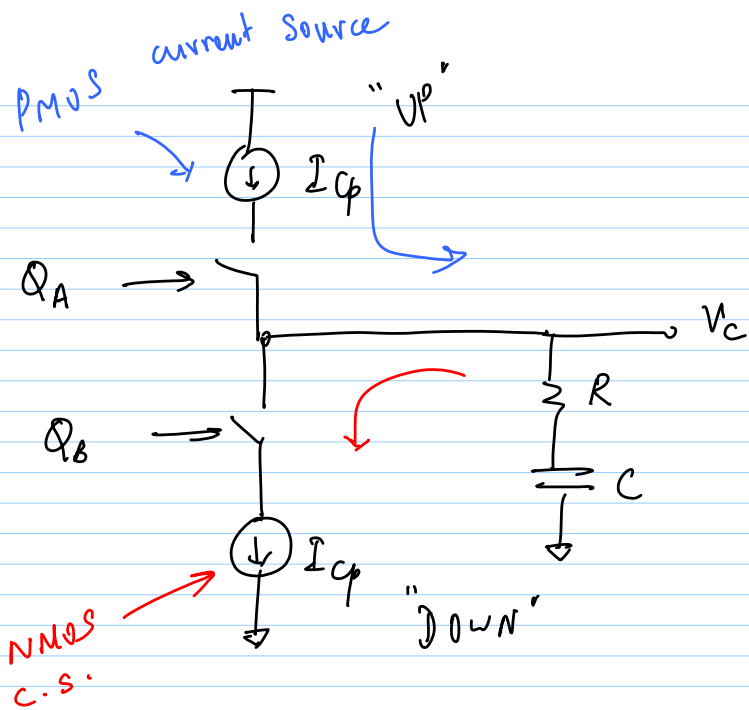

16/4/14

Lec 38


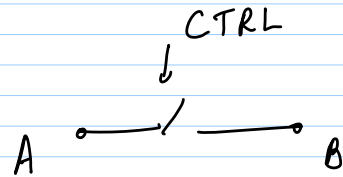







$V_A = \text{small}$ (e.g. $0 - V_{DD}/2$)




↳ NMOS switch

$V_A = \text{large}$ (e.g. $V_{DD}/2 - V_{DD}$)

↳ PMOS switch

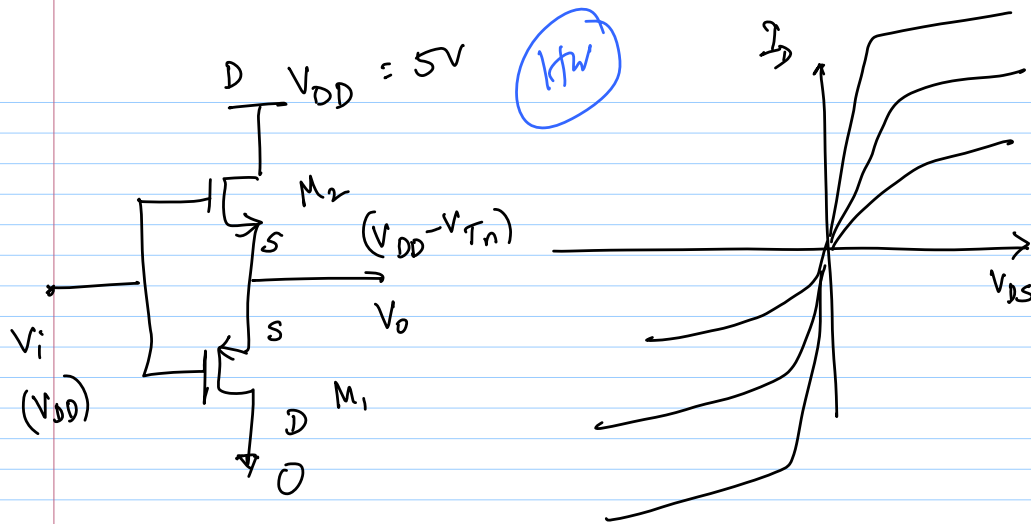
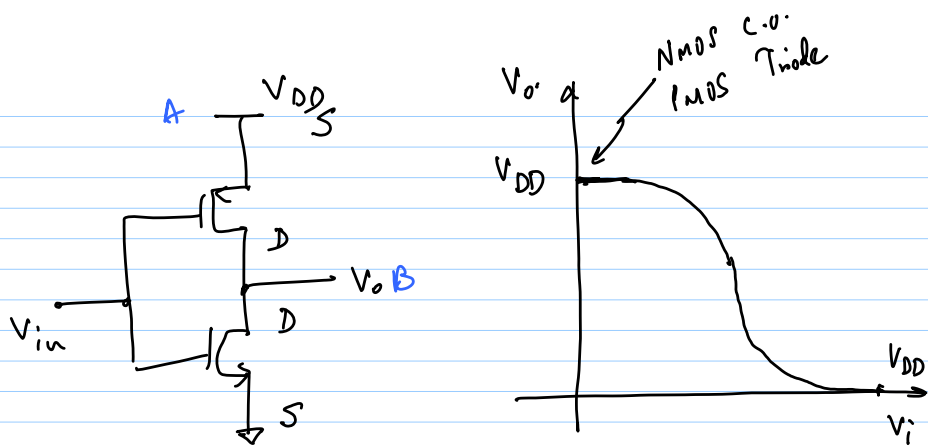


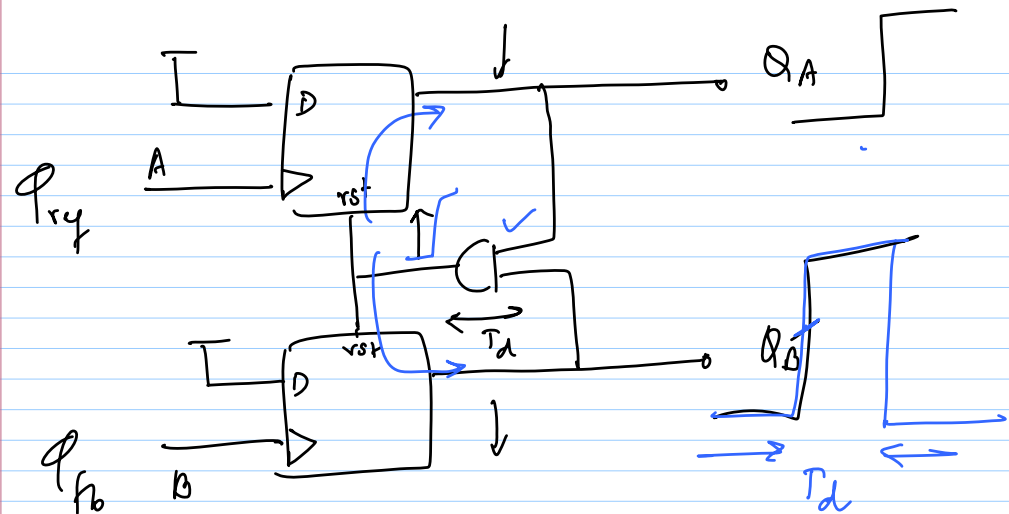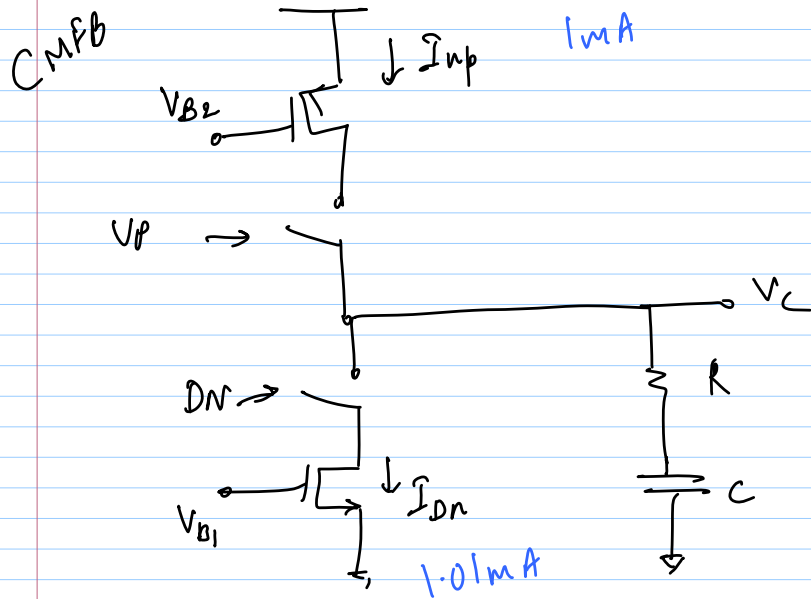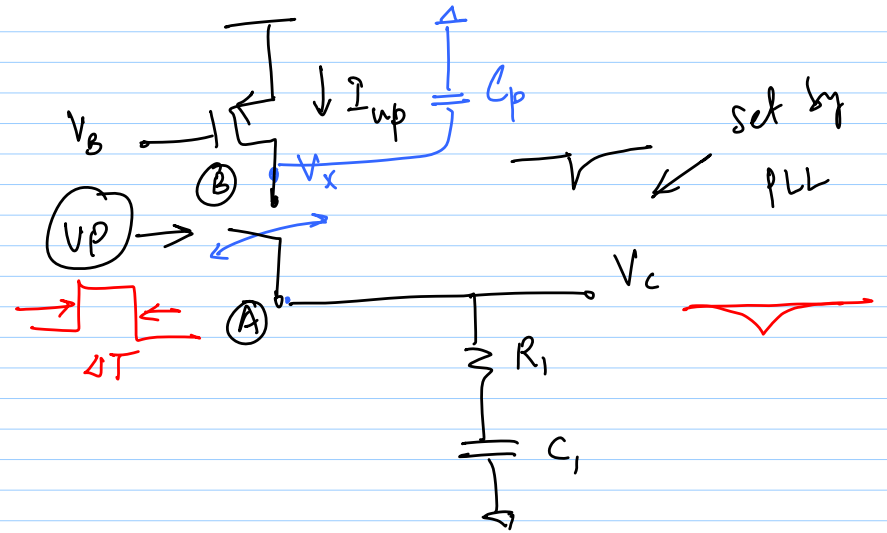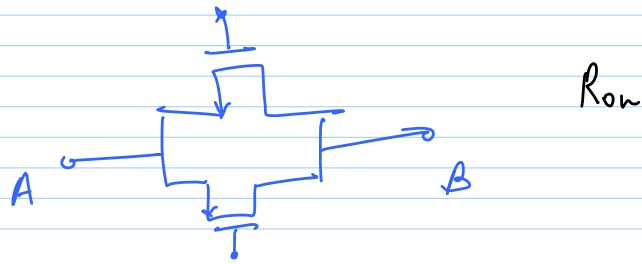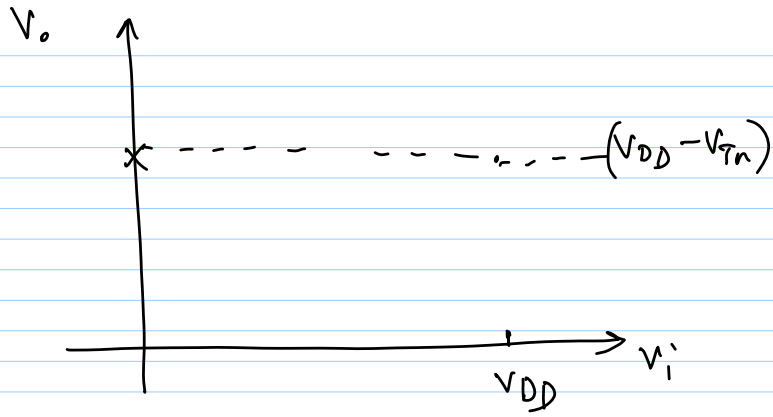

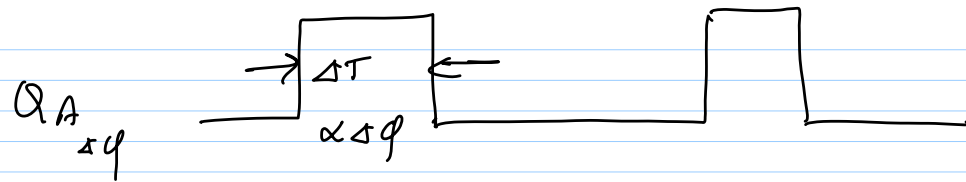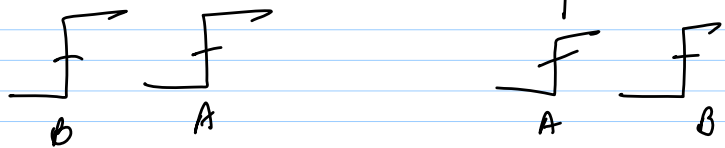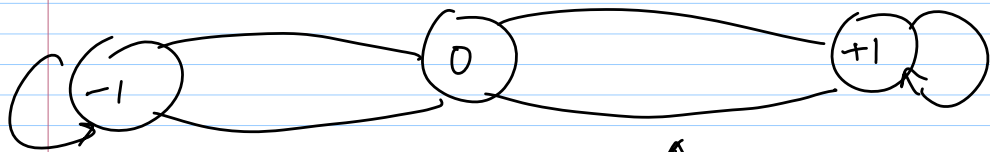


22/4/14




Lec 39

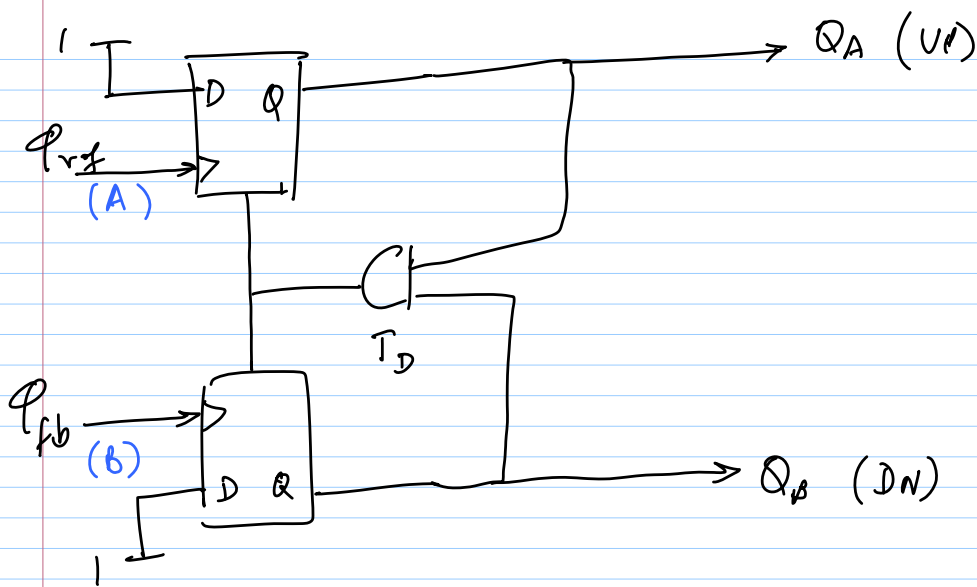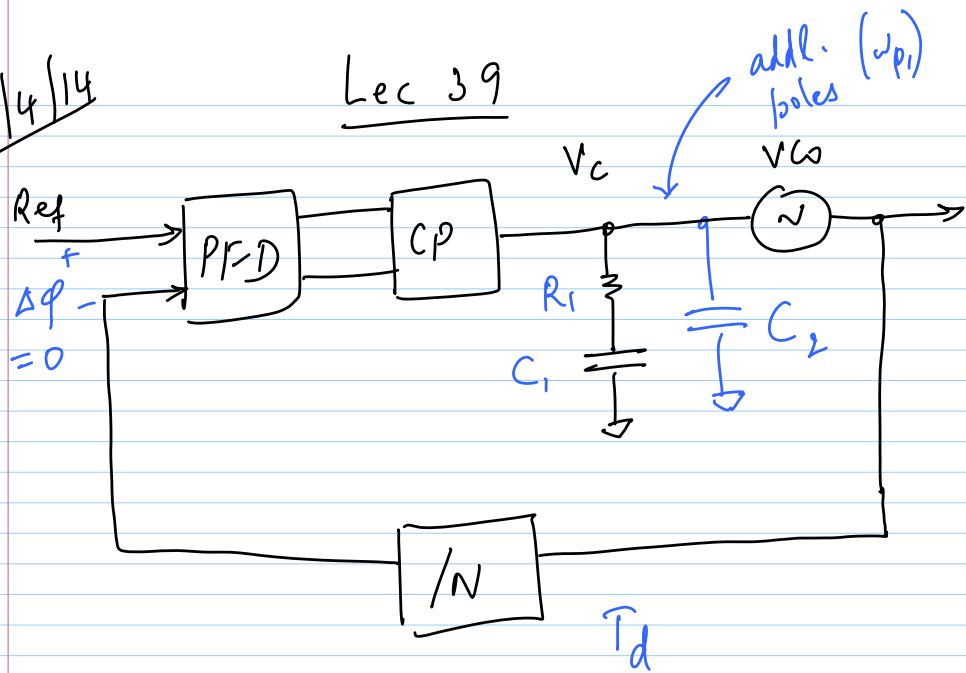


$Q_A = Q_B = 1$ X

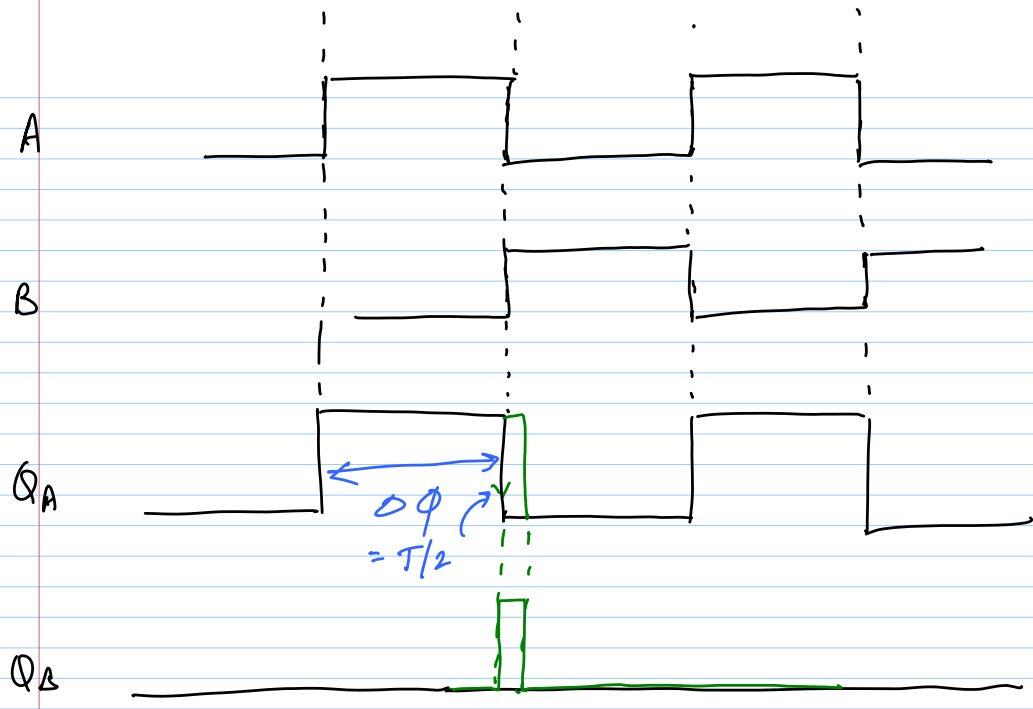


$\Delta q_{final} = 0$

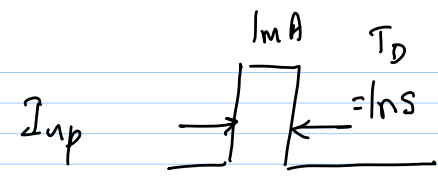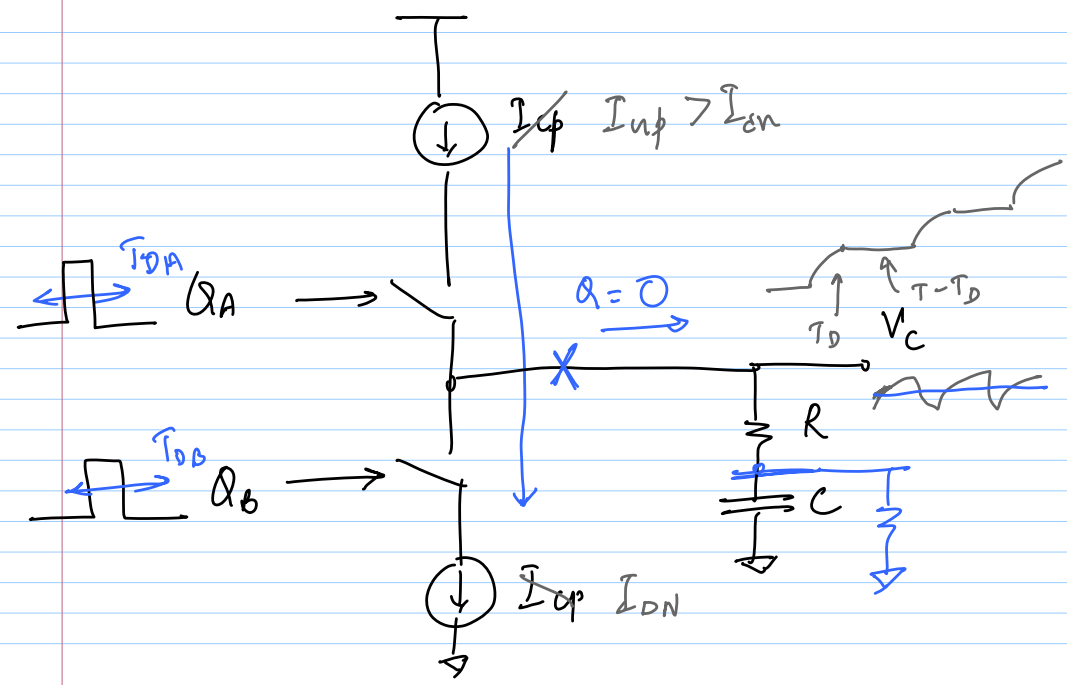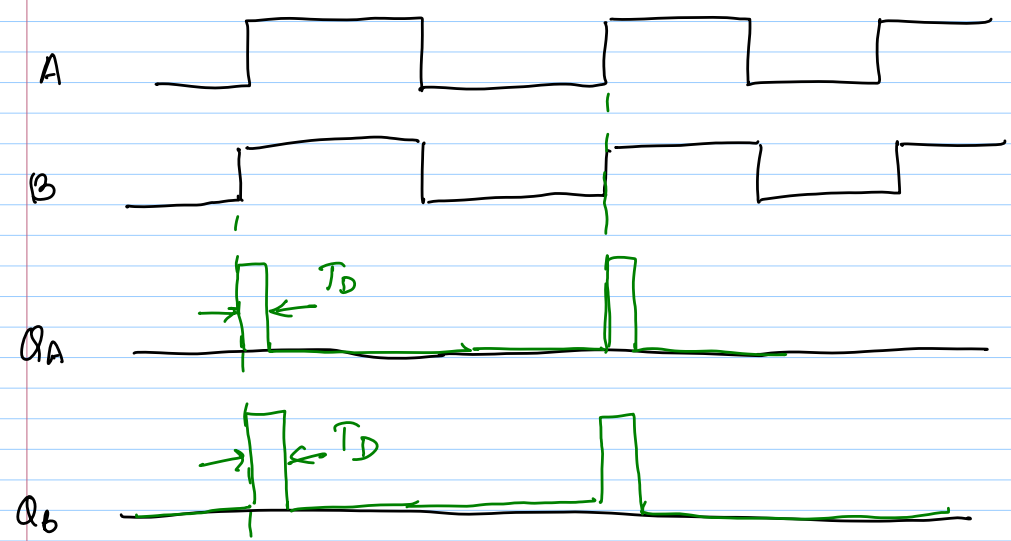

UP Charge = $1mA \times 1ns$



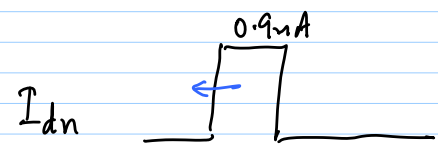


DN charge = $0.9mA \times 1ns$

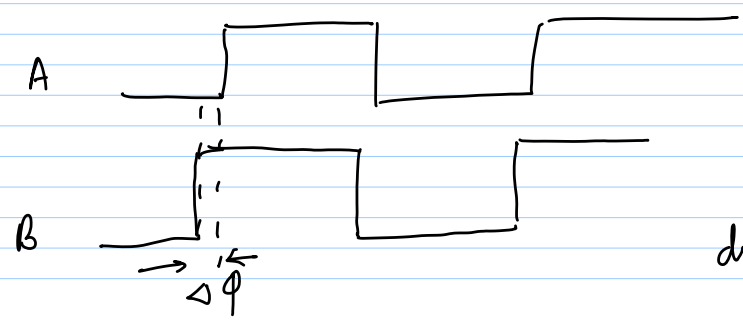

static phase error due to CP mismatch


* Use CMFB to set $I_{np} = I_{dn}$

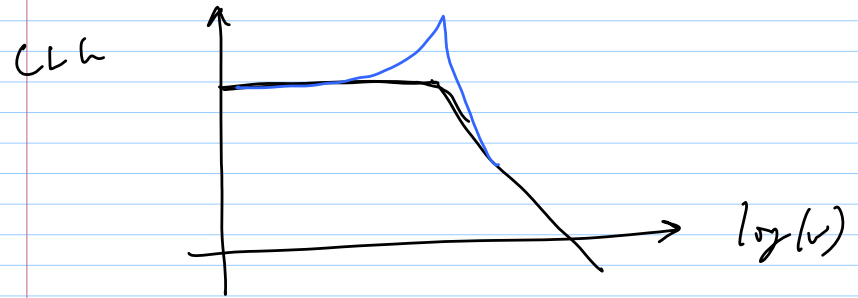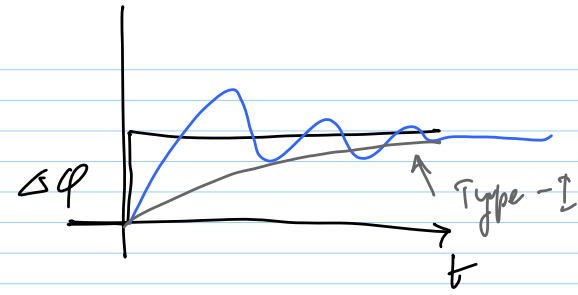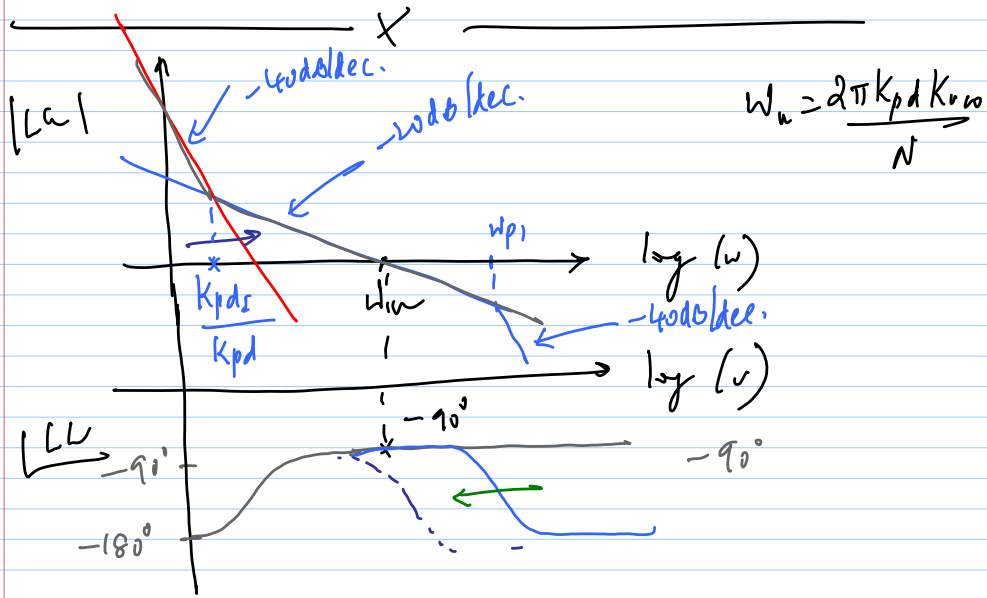


VCOs

$V_c \rightarrow \text{VCO} \rightarrow f_{rco} = f_{free} + K_{vro} \cdot V_c$

LC Oscillator


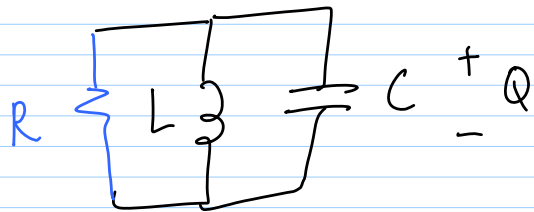


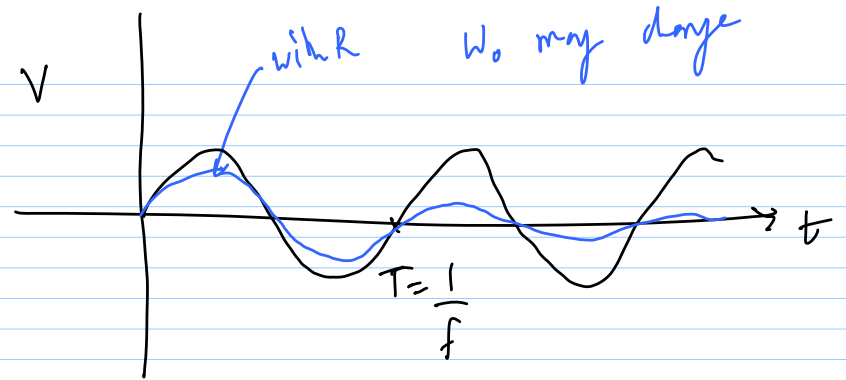$f = \frac{1}{2\pi\sqrt{LC}}$
 resonant freq.











23/4/14

Lec 40

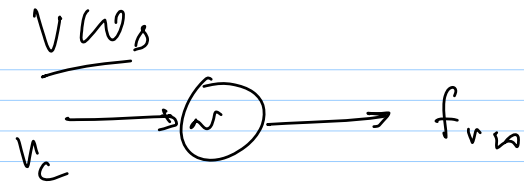
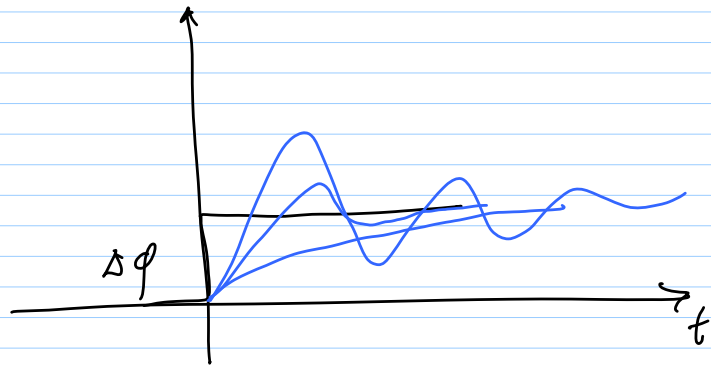

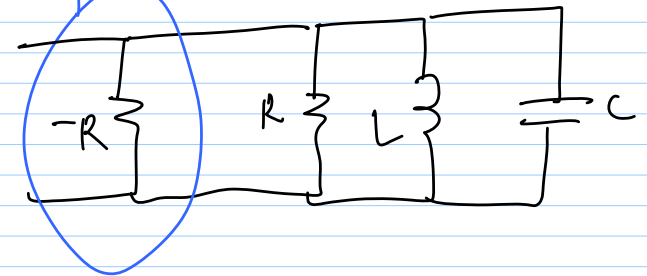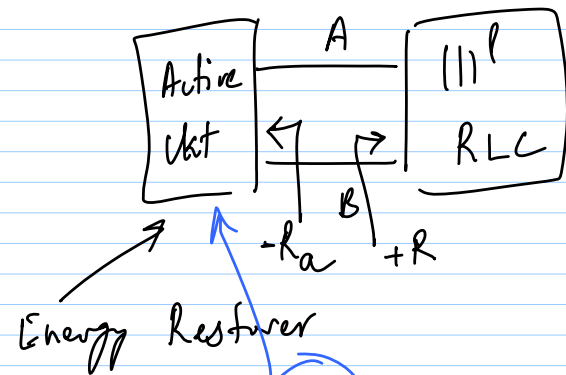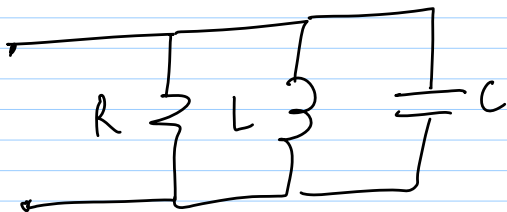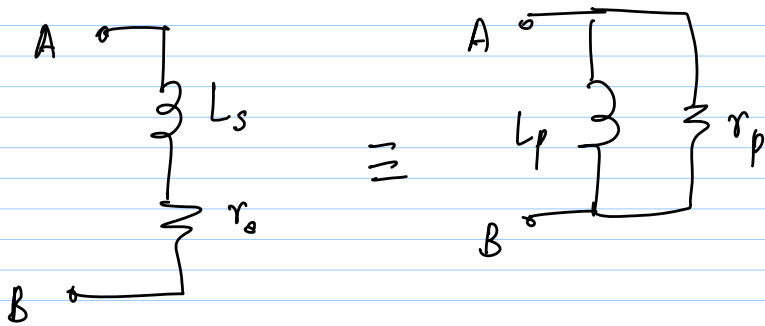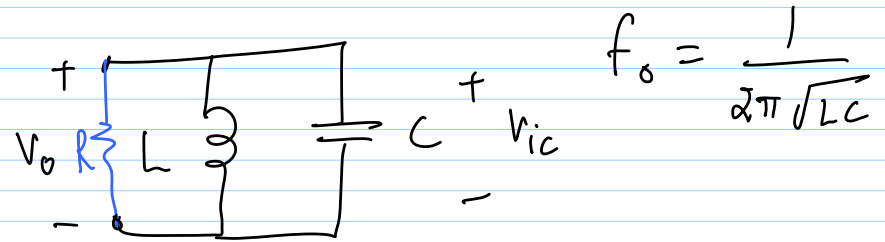
$$f_{vso} = f_{free} + K_{vw} \cdot V_c$$



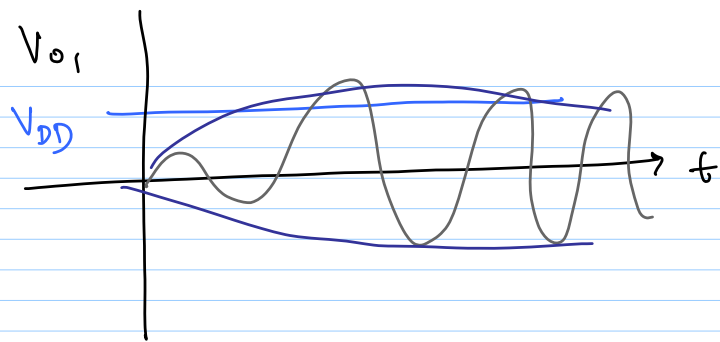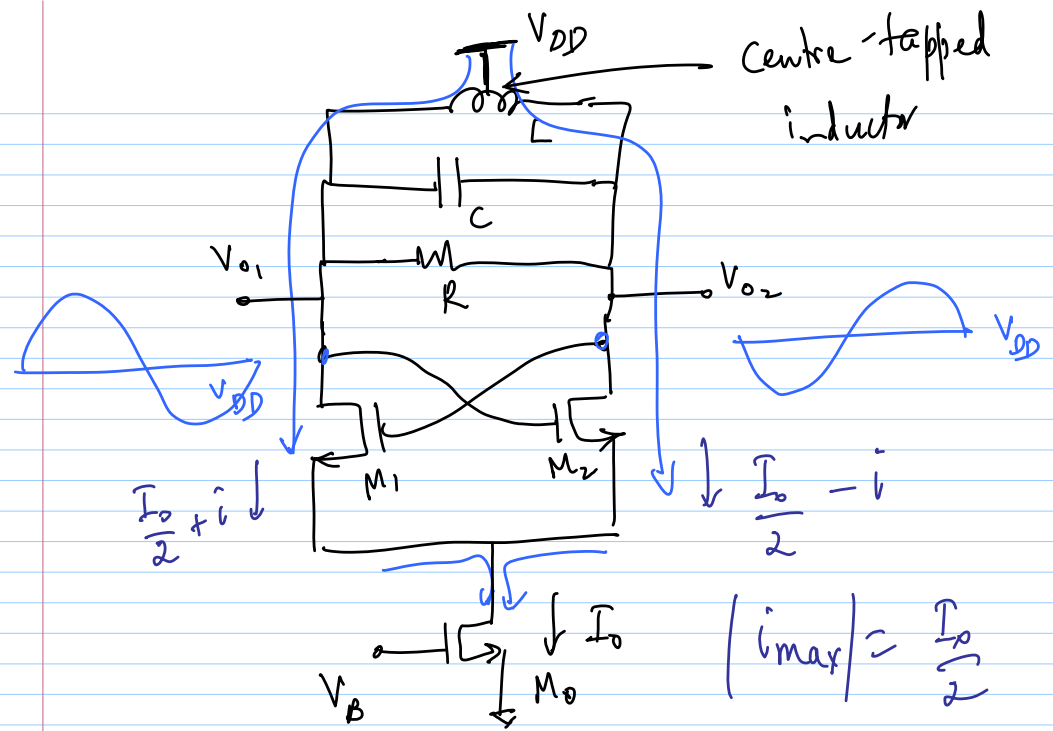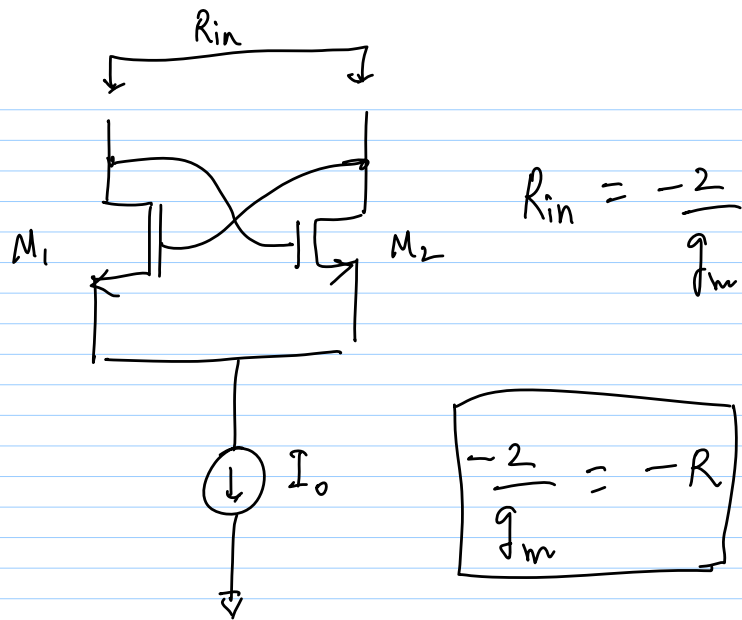

$R_a < R$

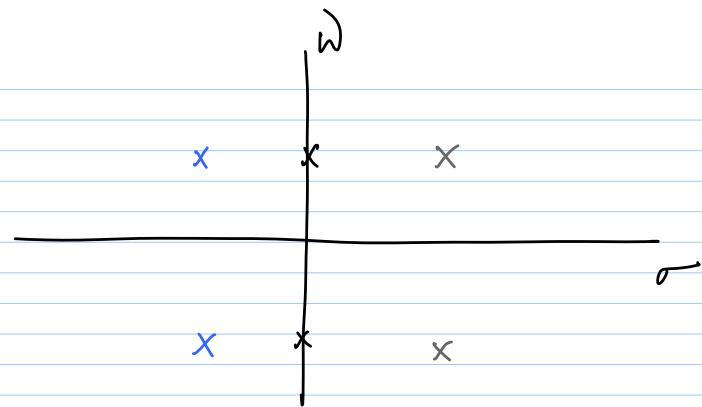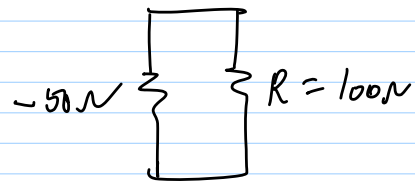

$$f_0 = \frac{1}{2\pi \sqrt{LC}}$$

tuning: 1) var. biased diode

2) MOS varactor
V.C. cap