

25/4/2014


Lec 41

PLL Design Example

\* Type-II 2<sup>nd</sup> order Charge Pump PLL  
 Given:  $f_{ref} = 10\text{kHz}$ ,  $f_{out} = 1\text{MHz}$ ,  
 loop BW = 500Hz,  $\zeta = \frac{1}{\sqrt{2}} = 0.707$   
 $K_{vco} = 500\text{kHz/V}$

\*  $Q = \frac{1}{2\zeta} = 0.707$

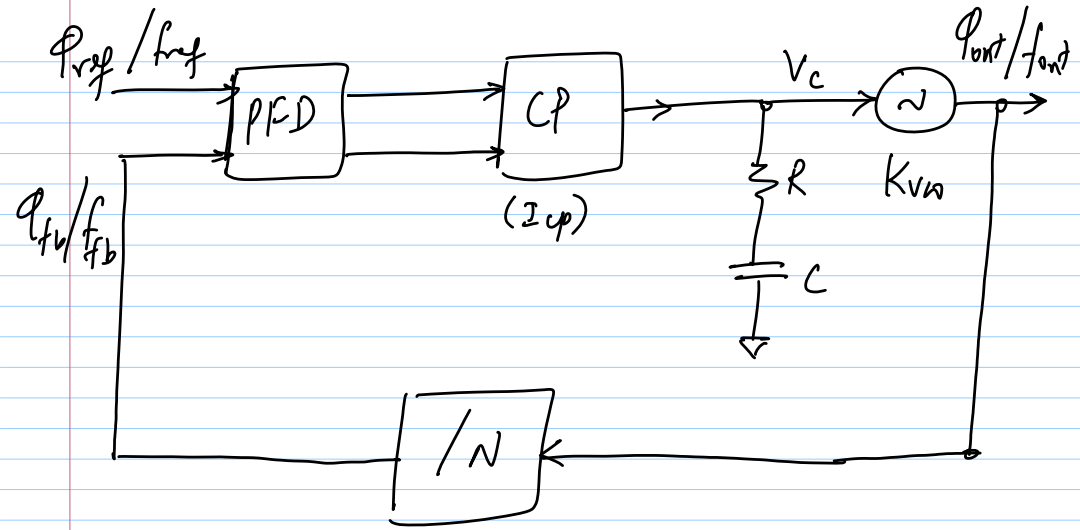\*  $\zeta$  or  $Q$  are specified based on loop locking transient



LG for  $\phi_{out}/\phi_{ref}$ :

$$L(s) = \frac{1}{2\pi} \cdot I_{cp} \cdot \left[ R + \frac{1}{sC} \right] \cdot \frac{2\pi K_{vco}}{s} \cdot \frac{1}{N}$$

$$= \frac{I_{cp} \cdot K_{vco} (1 + sCR)}{s^2 NC}$$

$$CLL \quad H(s) = N \cdot \frac{L(s)}{1 + L(s)}$$

$$= N \cdot \frac{I_{cp} K_{vco} (1 + sCR) / s^2 NC}{1 + I_{cp} K_{vco} (1 + sCR) / s^2 NC}$$

$$= N \cdot \frac{I_{cp} K_{vco} (1 + sCR)}{s^2 + \frac{I_{cp} K_{vco} R}{N} s + \frac{I_{cp} K_{vco}}{NC}}$$

Compare with  $s^2 + 2\zeta \omega_n s + \omega_n^2$

Std. form

$$\omega_n = \sqrt{\frac{I_{cp} K_{vco}}{NC}} ; \zeta = \frac{R}{2} \sqrt{\frac{I_{cp} C K_{vco}}{N}}$$

Step 1: Design VCO and get  $K_{vco}$   
 (here  $K_{vco}$  is given);  $N = \frac{f_{out}}{f_{ref}}$

Step 2 : Use relation between  $\omega_{-3dB}$  and  $\omega_n$  (can be derived based on CLN expression)\*

$$\omega_{-3dB}^2 = \omega_n^2 \cdot \left[ (2\zeta^2 + 1) + \sqrt{(2\zeta^2 + 1)^2 + 1} \right]$$

$$\hookrightarrow f_{-3dB} = \omega_{-3dB} / 2\pi = \text{loop BW}$$

\* Refer to F.M. Gardner, "Phase Lock Techniques", Second ed., Wiley, 1979

Step 3 : Choose  $I_{cp}$   
 $\rightarrow$  based on noise and area considerations

Step 4 : Set  $\zeta$  and calculate R & C

Step 5 : Iterate if required based on noise and area considerations

Here :  $f_{-3dB} = 500 \text{ Hz}$ ,  $\zeta = \frac{1}{\sqrt{2}}$   
 $\Rightarrow \omega_{-3dB} = 3140 \text{ rad/s}$ ,  $\zeta^2 = 0.5$

$$(3140)^2 = \omega_n^2 [2 + \sqrt{5}]$$

$$\omega_n = 1525.6 \text{ rad/s}$$

Choose  $I_{cp} = 10 \mu\text{A}$

$$N = \frac{f_{out}}{f_{ny}} = 100$$

$$\omega_n = \sqrt{\frac{I_{cp} K_{vco}}{NC}}$$

$$(1525.6)^2 = \frac{10e^{-6} \times 500e^3}{100C}$$

$$\Rightarrow C = 21.48 \text{ nF}$$

$$\zeta = \frac{R}{2} \sqrt{\frac{I_{cp} K_{vco} C}{N}}$$

$$\Rightarrow R = 43.15 \text{ k}\Omega$$

Notes

1) zero is located @  $\omega_z = \frac{1}{2\pi RC} = 171.8 \text{ Hz}$

$$2) f_n = \frac{K_{pd} K_{vm}}{N}$$

$$3) K_{pd} = \frac{I_{cp} R}{2\pi}$$

$$4) K_{pdI} = \frac{I_{cp}}{2\pi C}$$

5) Spec. can be in terms of phase margin, i.e., relative values of  $K_{pd}$  &  $K_{pdI}$  (position of zero) and  $f_n$ .

F. M. Gardner, "Phaselock Techniques," Second Edition, Wiley

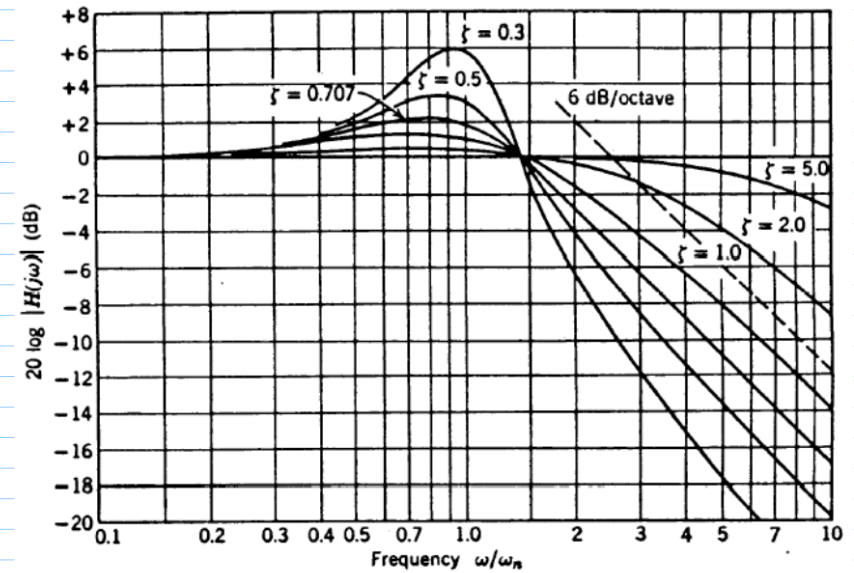


Figure 2.3 Frequency response of a high-gain second-order loop.