

- ① The current mirror shown on the right delivers a current I_0 to the load. The reference branch current can be tailored using the parameter α .

- * The transistors must be sized to allow a minimum voltage of $V_{out,min}$ in saturation region.
- * The total current must be I_{tot}


- * The signal (current in the load) to the noise (rms current in a bandwidth f_B) has to be maximized.

Determine W/L , α , output signal & noise rms in terms of the given parameters.

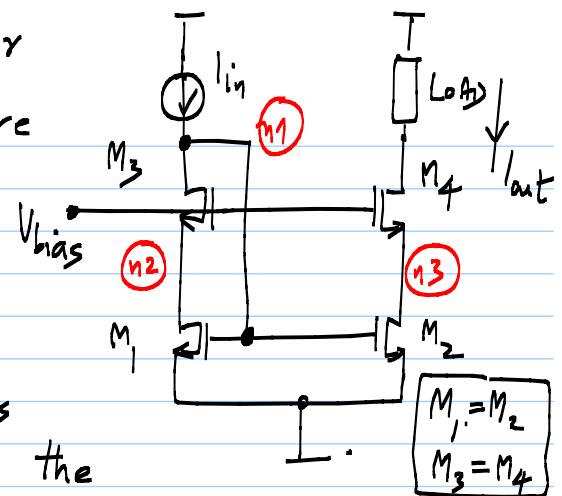(2) In the cascode current mirror shown here, all transistors are in saturation region.

Model $M_{1,2}$ by g_m , $g_{ds} = 0$

Model $M_{3,4}$ by g_m for all transistors



(i) Determine the noise PSD of the output current due to each transistor separately

(ii) Determine the current error in the output due

to $\Delta V_{T_{12}}$ & $\Delta V_{T_{34}}$ separately


(iii) Determine $\frac{I_{out}(s)}{I_{in}(s)}$ by including a parasitic capacitor C_p to nodes n^1 , n^2 , and n^3 , one at a time

(Not to be submitted:

Reason out why the above results come out the way they do)


③ For the RC filter,
determine

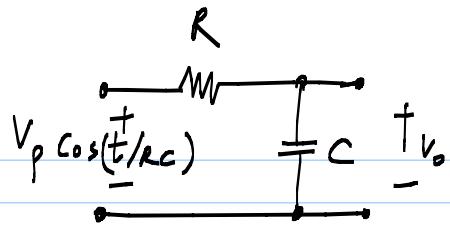- Mean squared o/p signal (s)
- Mean squared o/p noise (n)
- Ratio s/n
- Power dissipated in the resistor (P_d)
- Bandwidth in Hz (f_B)




Express the power dissipated (P_d) in terms of
the signal to noise ratio and the bandwidth

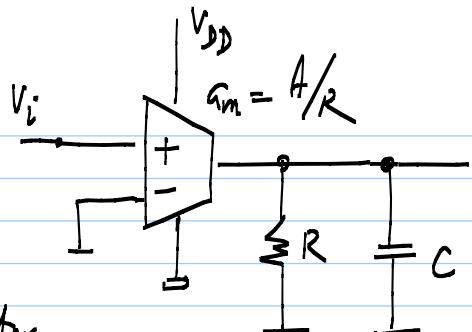(4) (a) For the amplifier shown here, calculate the mean squared output noise voltage assuming that the transconductor g_m has an input referred noise voltage PSD of $4kT/g_m$



(b) Assuming that $v_i = \frac{V_p}{A} \cos \omega t$, and a low frequency ω , calculate the output mean squared signal voltage

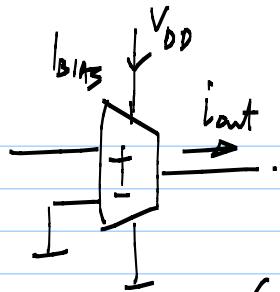(c) Assuming a "class A" transconductor, determine the power drawn (average power over one output cycle) from the supply for the above signal




$$I_{BIAS} = \max(|i_{out}|)$$

["class A"]

(d) Express the power dissipated (P_d) in terms of the signal to noise ratio and the bandwidth

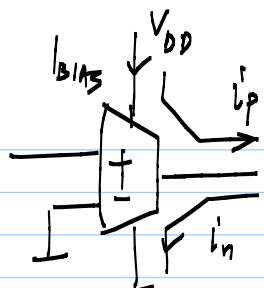(e) Assuming a "class B" transconductor, determine the power drawn (average power over one output cycle) from the supply for the above signal



- positive i_{out} from V_{DD}
 - negative i_{out} into ground
- [class "B"]

(f) Express the power dissipated (P_d) in terms of the signal to noise ratio and the bandwidth

(5) What do you infer from the relationships between P_d , $\frac{\sigma}{N}$, and f_B in the previous problems?

(6) Calculate the output noise PSD & the input referred noise PSD due to the opamp noise ($PSD = \sigma_{v,opA}$), with and without R_2 .

