

### EE6320 RF Integrated Circuits Homework 3

1. Impedance transformation networks are widely used in power amplifier designs to enable a specific amount of power to be delivered to a load. Owing to supply voltage limitations, a downward impedance transformation of the antenna resistance is usually necessary. Let us take the example of WiFi, where the PA is required to deliver 1W of power to a  $50\Omega$  antenna at 1GHz. Suppose that the power amplifier is able to support a maximum peak-to-peak output swing of 5V across its load resistance.

- a) What is the maximum power that can be delivered to the load without a matching network?
- b) What impedance should the PA be designed to drive so as to deliver the desired power with the rated voltage swing.
- c) Design a high-pass L-match network using ideal passive components to match the antenna impedance to the value from (b) above.
- d) Verify the above results of (c) using Eldo or Spectre. Plot  $S_{11}$  (magnitude in dB) and  $Z_{in}$  (real and imaginary parts in  $\Omega$ ) versus frequency from 500MHz-2GHz. Also, determine the  $-3\text{dB}$  bandwidth of impedance magnitude from your simulation, and compare the Q derived from the BW definition with the Q that you designed for.
- e) Design a high-pass T-match network with a  $Q=5$  using ideal passive components to match the antenna impedance to the value from (b) above.
- f) Verify the above results of (e) using Eldo or Spectre. Plot  $S_{11}$  (magnitude in dB) and  $Z_{in}$  (real and imaginary parts in  $\Omega$ ) versus frequency from 500MHz-2GHz. Also, determine the  $-3\text{dB}$  bandwidth of impedance magnitude from your simulation, and compare the Q derived from the BW definition with the Q that you designed for.
- g) Now, assume that all spiral inductors in this process have a Q of approximately 15. Add an ideal resistor of appropriate value in parallel with the ideal inductor in (d) above and re-run the L-match network simulation to see how the impedance matching has been affected. Again, plot  $S_{11}$  (magnitude in dB) and  $Z_{in}$  (real and imaginary parts in  $\Omega$ ) versus frequency from 500MHz-2GHz.
- h) Ungraded question: See if you can optimize the value of the L-match network components to improve the matching with lossy inductors.