

EE6320 Project 4: Power Amplifier Design

In this project, you are asked to design a single ended power amplifier (PA) that meets or exceeds the specifications given below. Use the IBM 0.13 μm CMOS process parameters used by you earlier.

Design the PA for the following specs:

- $f_{\text{RF}} = 5170$ to 5320 MHz
- $V_{\text{DD}} = 1.2\text{V}$
- Minimum output $P_{\text{ldB}} = 10$ mW (+10 dBm)
- Maximum AM-PM deviation at $P_{\text{ldB}} = 5$ degrees
- Minimum PA voltage gain from gate to drain = 2 V/V
- Maximum number of inductors = 2.
- There is no specification on S_{22} (output matching is not required).
- You may use a matching network to transform the 50Ω load to a lower impedance so that PA drives a smaller impedance and can therefore deliver more power. However, you should design the PA to deliver the appropriate power to the 50 Ohm load after accounting for matching network loss (based on the Q below).
- Minimise overall power consumption

Note 1: No ideal inductors are allowed! Add a resistor in parallel with each of the inductors in your circuit so that it has a Q of 20 at 5245 MHz. All capacitors can be assumed to be ideal.