

Textbook : "RF Microelectronics" by Behzad Razavi (2<sup>nd</sup> ed.)

Grading : Final exam: 50%.


Assignments: up to 10%.

Projects : 40%. → LNA, mixer, VCO, PA


Pre-req : EE3002/5310 → MOS operation

Signals & Systems

RF = radio freq = wireless

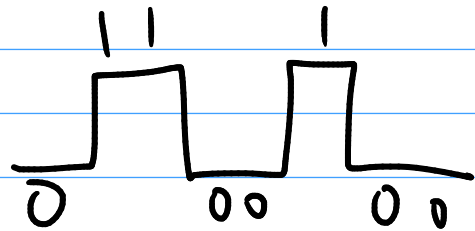

≡

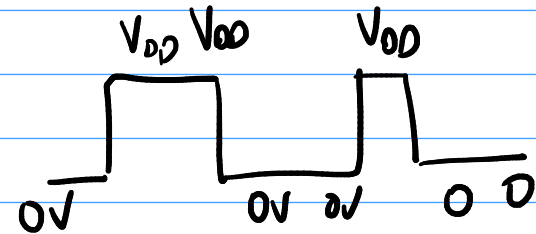

Optical - fibre

Wireline - Cu wire

dedicated medium

Wireless


free space




shared medium

Multiple Access  $\rightarrow$  1) FDMA Frequency Division Multiple Access

2) TDMA - time division MA


3) CDMA - Code division MA

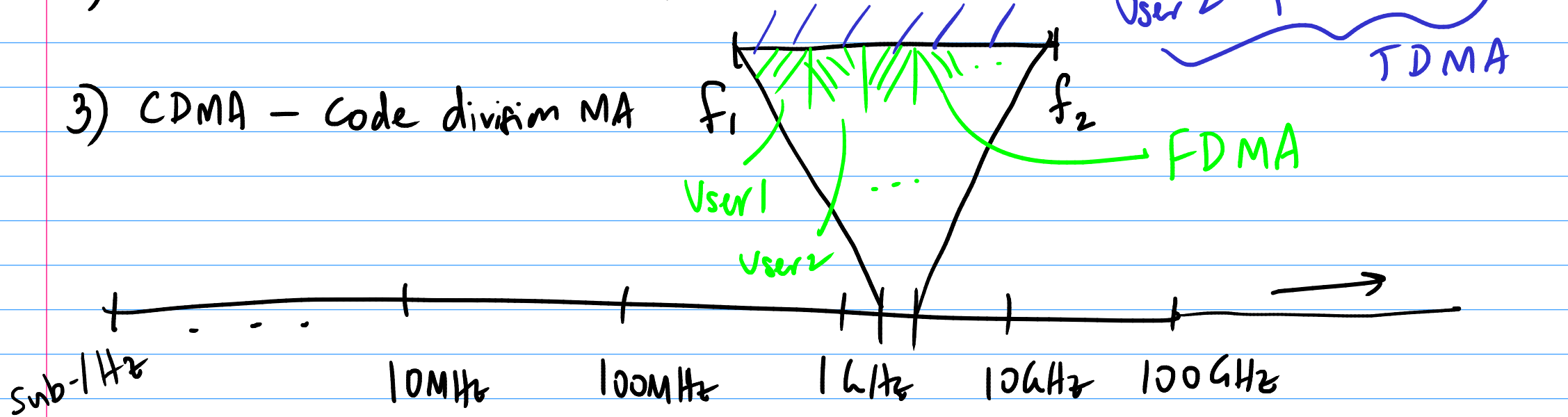

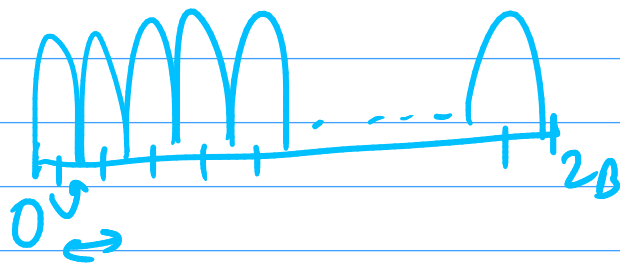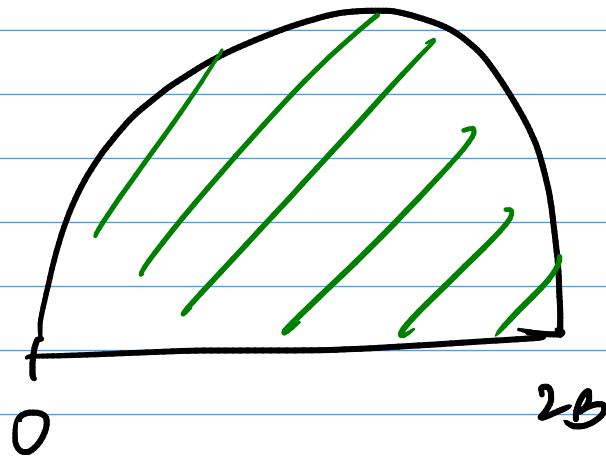
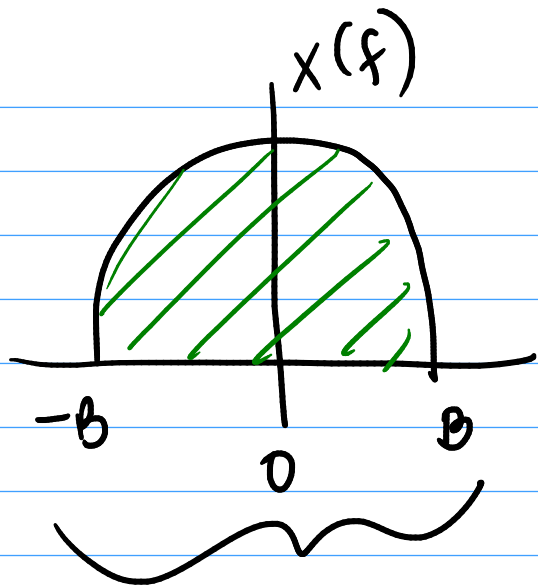


OFDM



# Duplexing

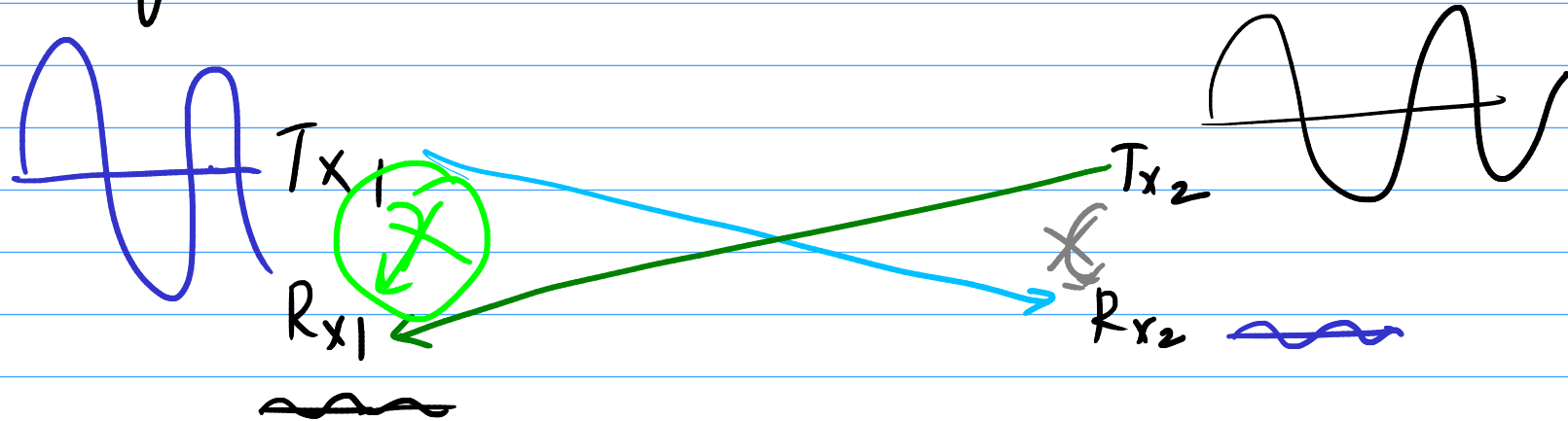

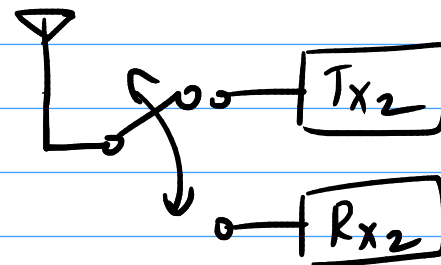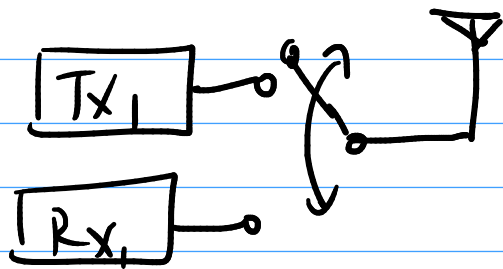- 1) TDD Time division Duplex
- 2) FDD Freq. " "




TDD

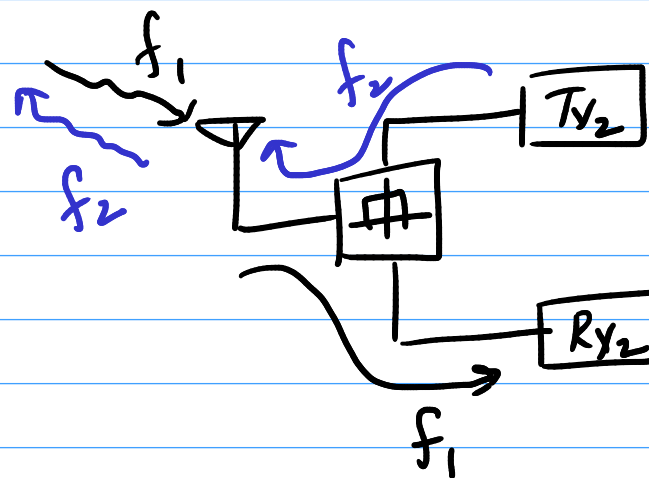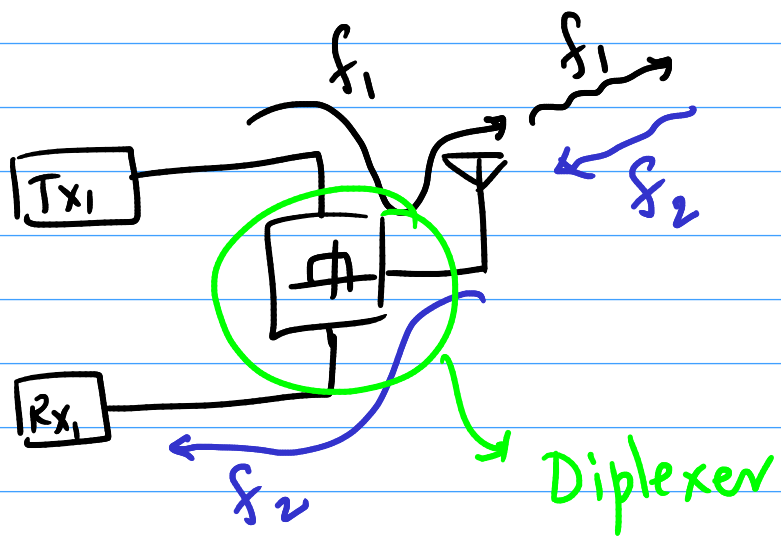

FDD




Sine

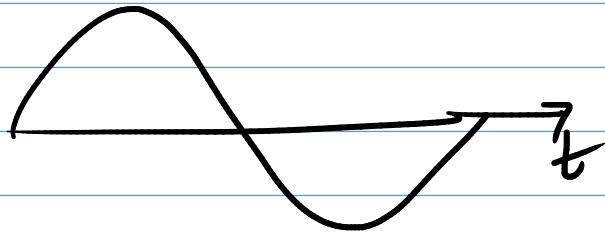


$$A \cos(\omega t + \phi)$$

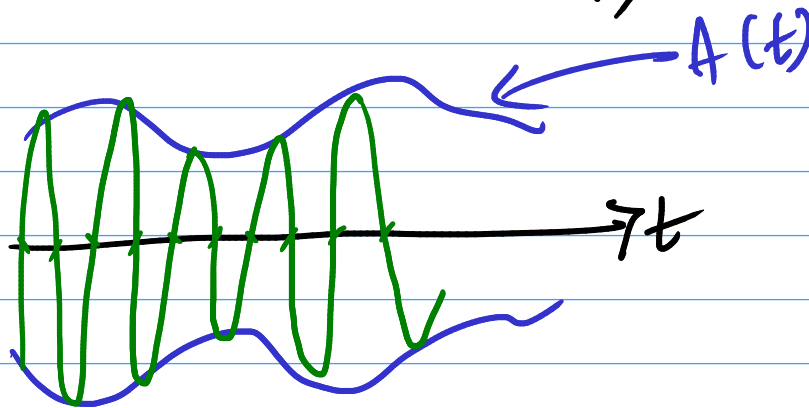1) AM  $\rightarrow A(t) \cos(\omega_0 t + \phi_0)$





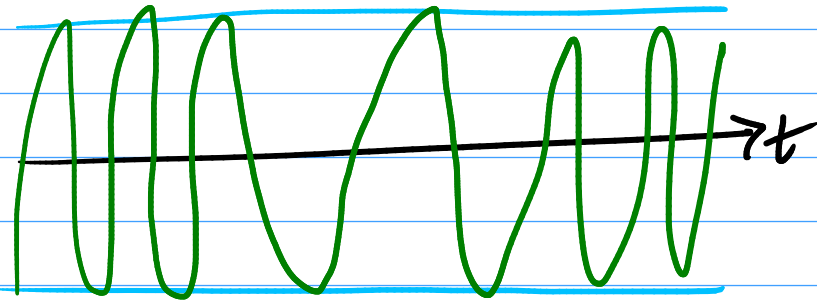2) FM:  $x(t) = A_0 \cos(\omega(t) \cdot t + \varphi_0)$



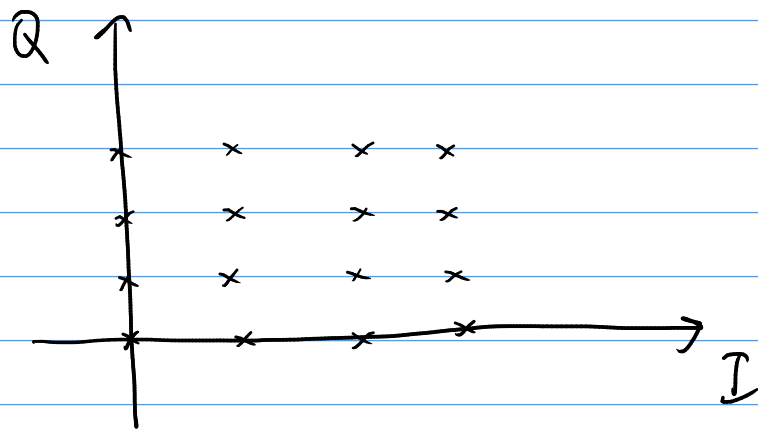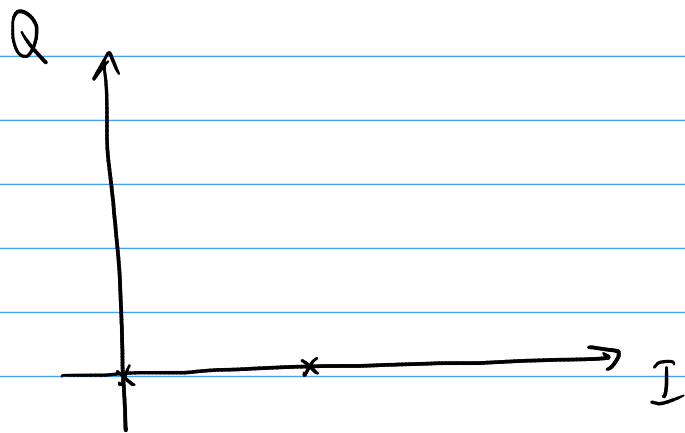
3) PM:  $x(t) = A_0 \cos(\omega_0 t + \varphi(t))$

In general  $\rightarrow$  Information is Amplitude & Freq.  
(or) Amp. & phase





QAM - 16


$$\tilde{x}(t) = x_I(t) + j x_Q(t)$$


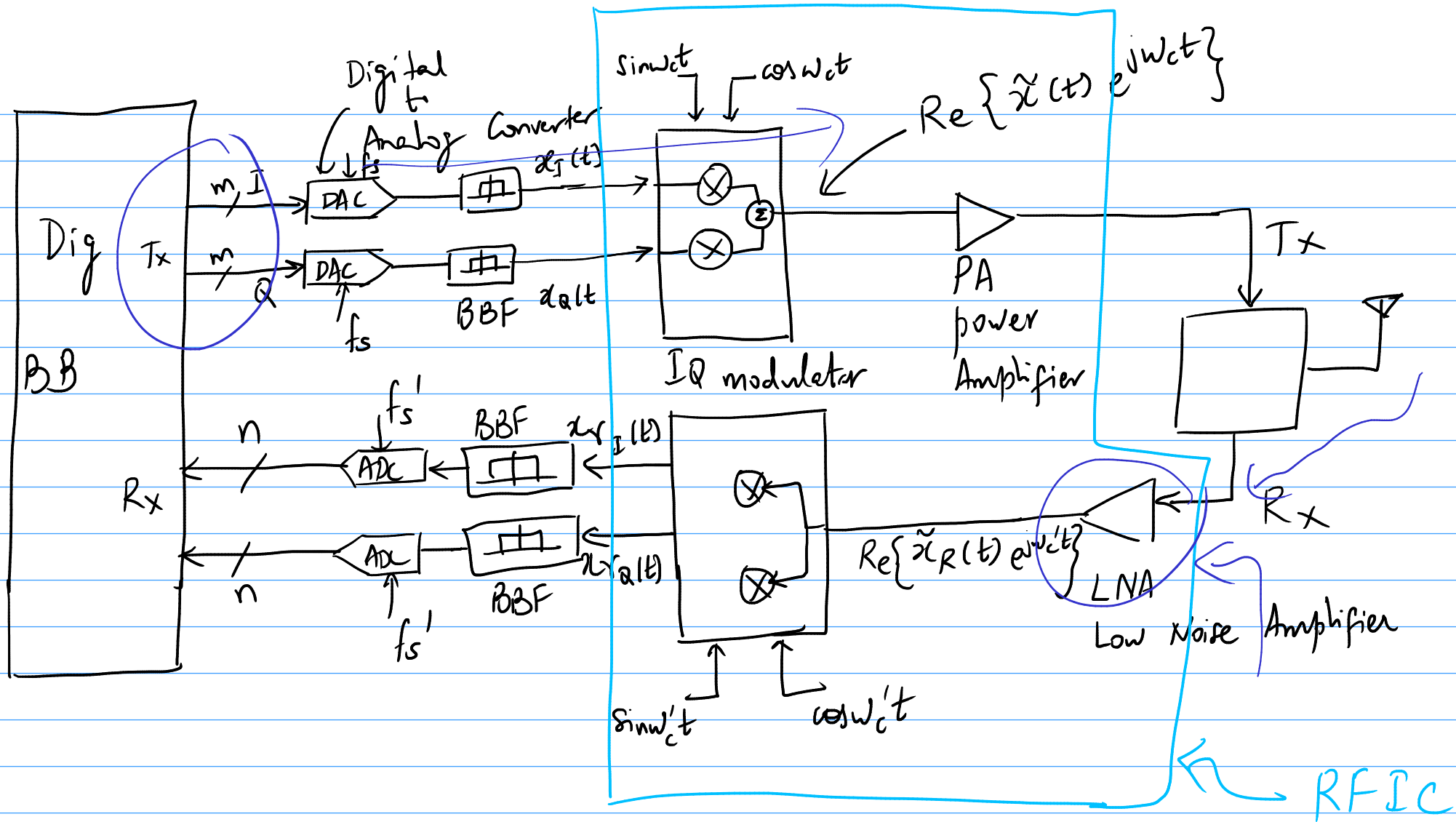


DAC

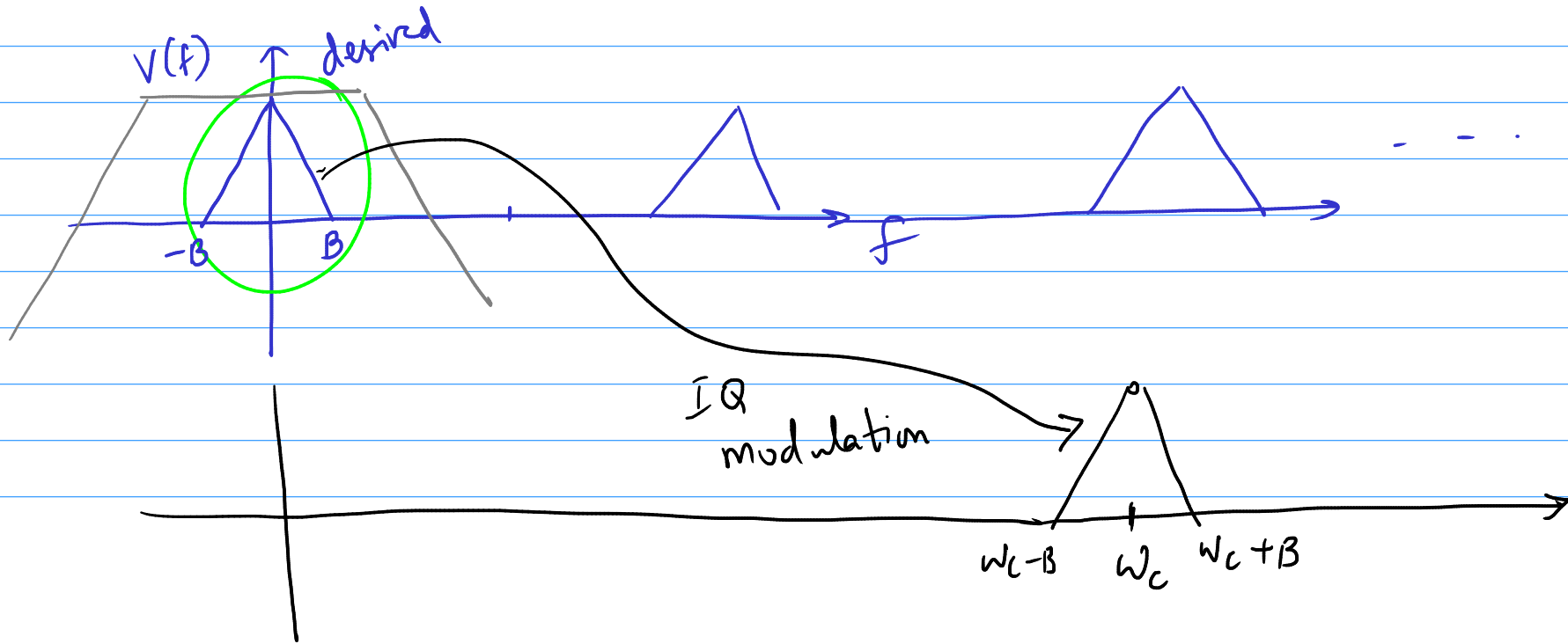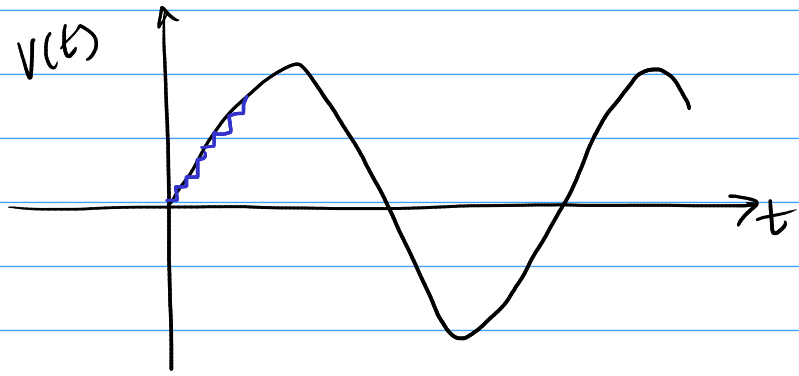


ADC


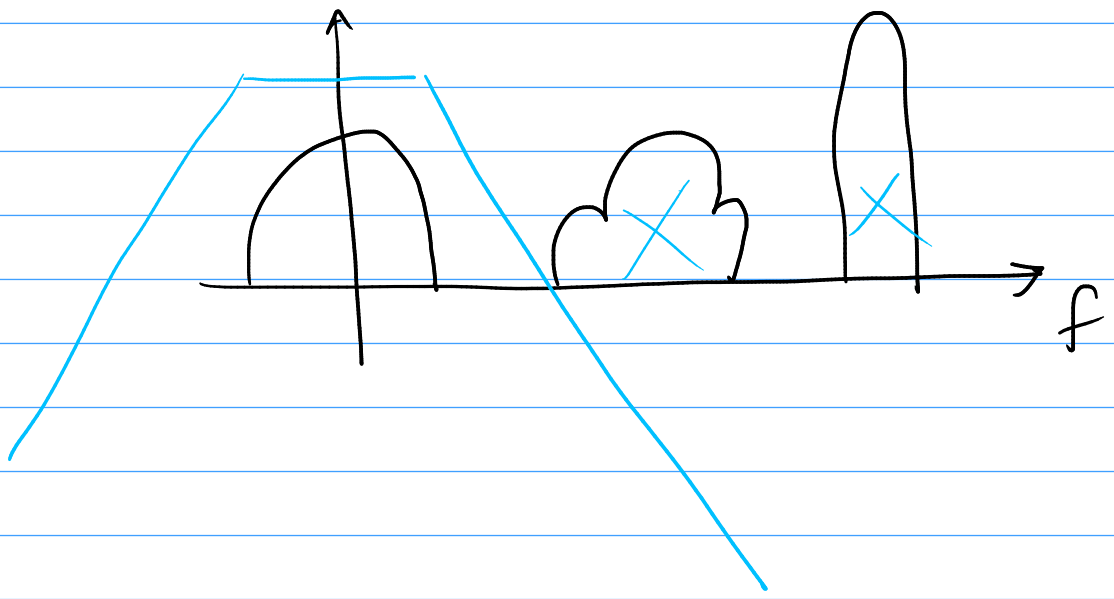


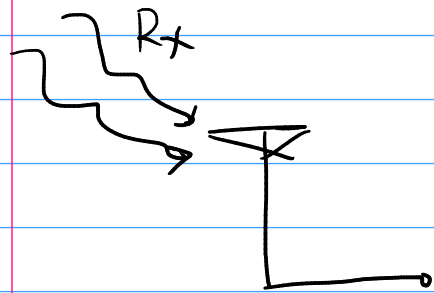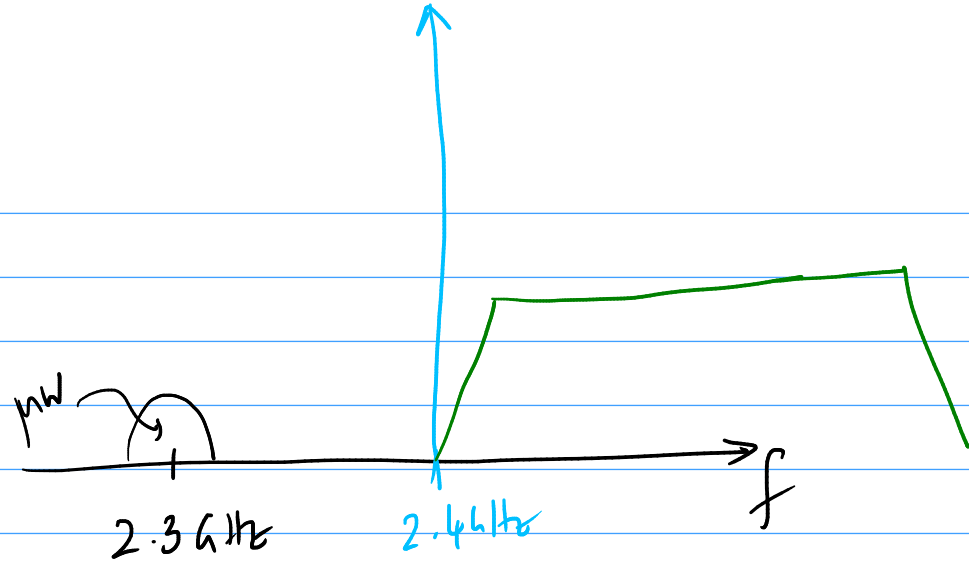



|||

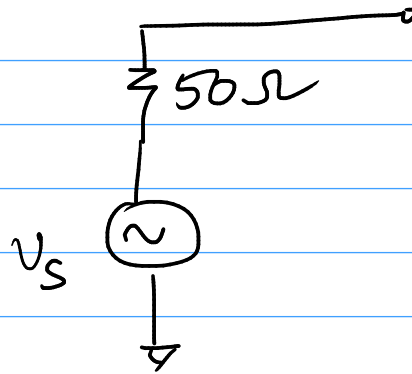


Rx mode

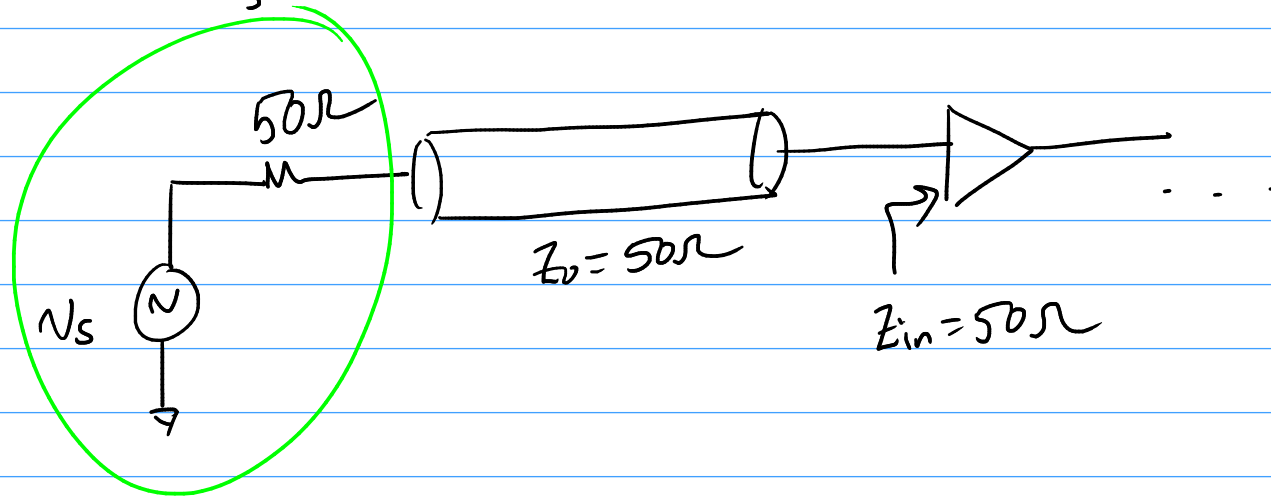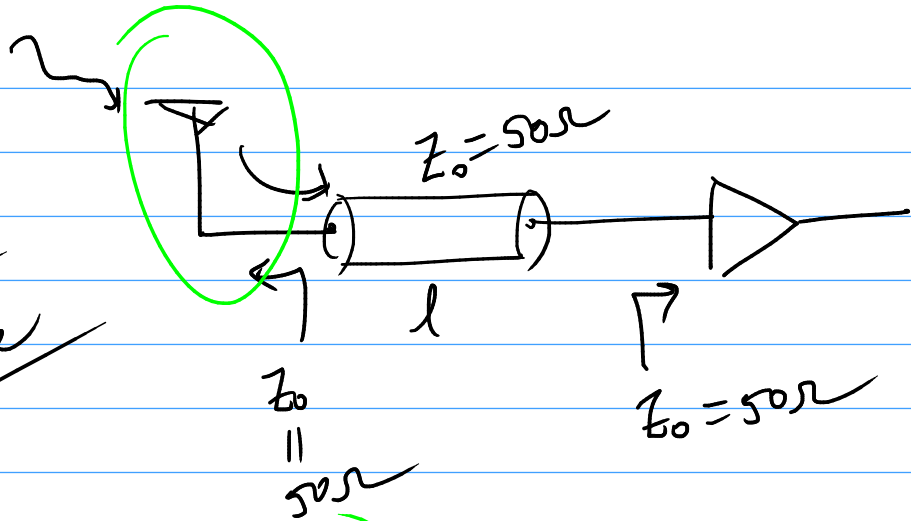


Tx Mode

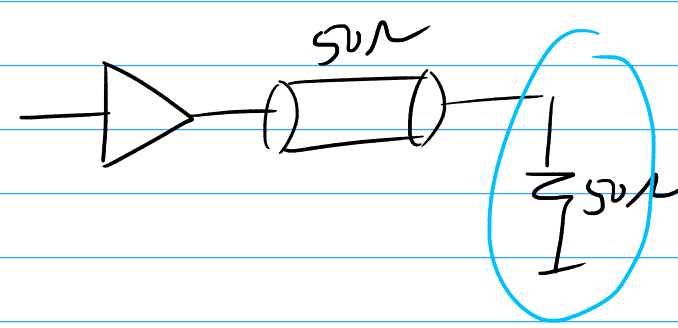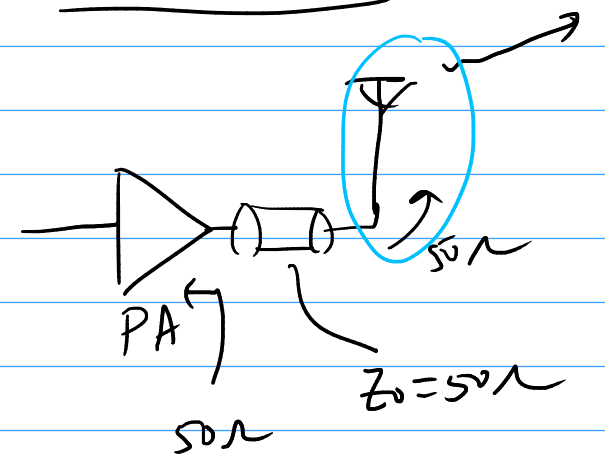

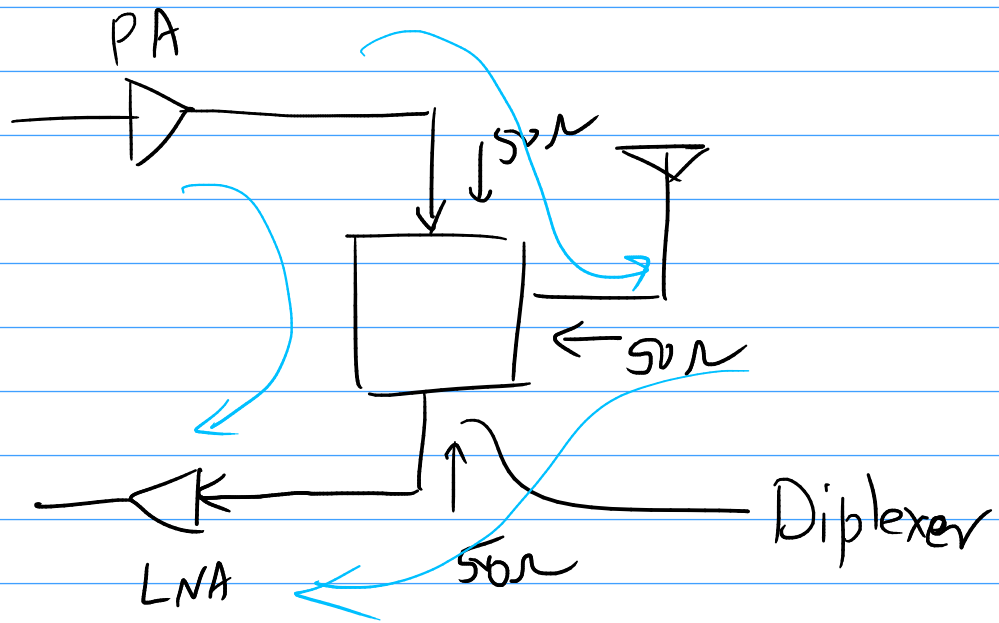

# S-parameters

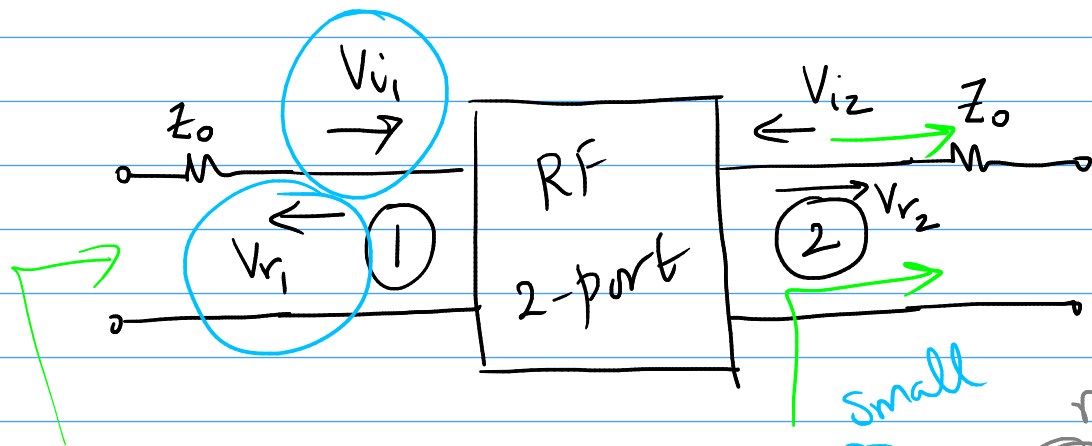

$\Gamma_1$  = reflection coeff.

$$\begin{bmatrix} V_{r1} \\ V_{r2} \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \begin{bmatrix} V_{i1} \\ V_{i2} \end{bmatrix}$$

power gain (in dB) small reverse transmission gain small

## Units

1) dBm

Power  $P$  mW

$$P_{\text{dBm}} = 10 \log_{10} \left( \frac{P \text{ mW}}{1 \text{ mW}} \right)$$

$$P_1 = 1 \text{ mW}$$

$$P_1 \text{ dBm} = 0 \text{ dBm}$$



$$P_2 = 10 \text{ mW}$$



$$P_2 \text{ dBm} = 10 \text{ dBm}$$

$$P_3 = 100 \mu\text{W}$$

$$P_3 \text{ dBm} = -10 \text{ dBm}$$

2) dBc

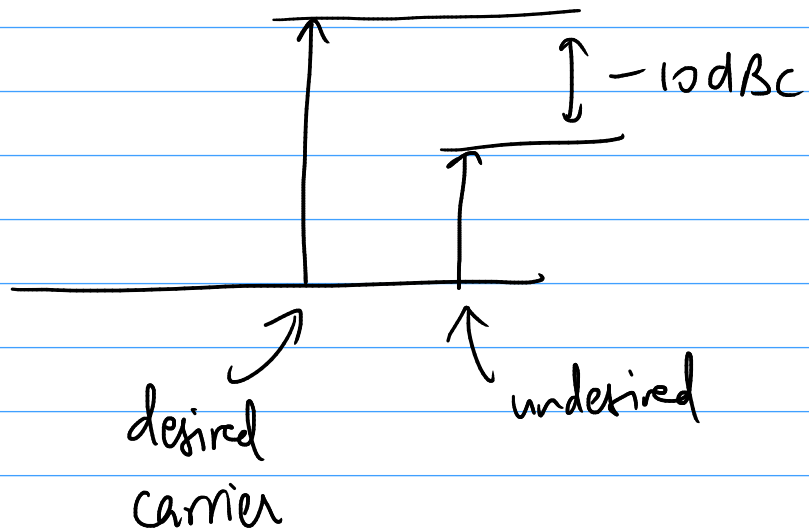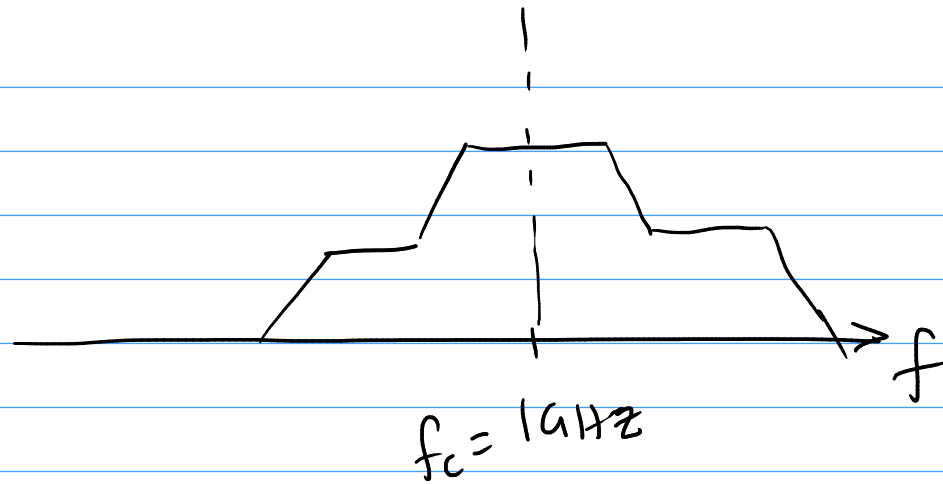


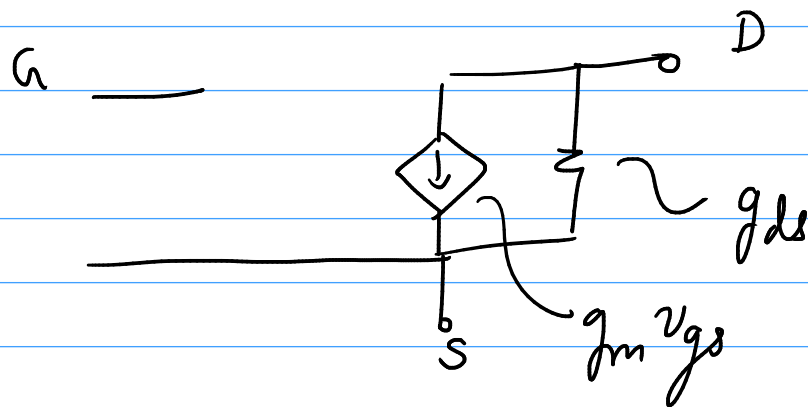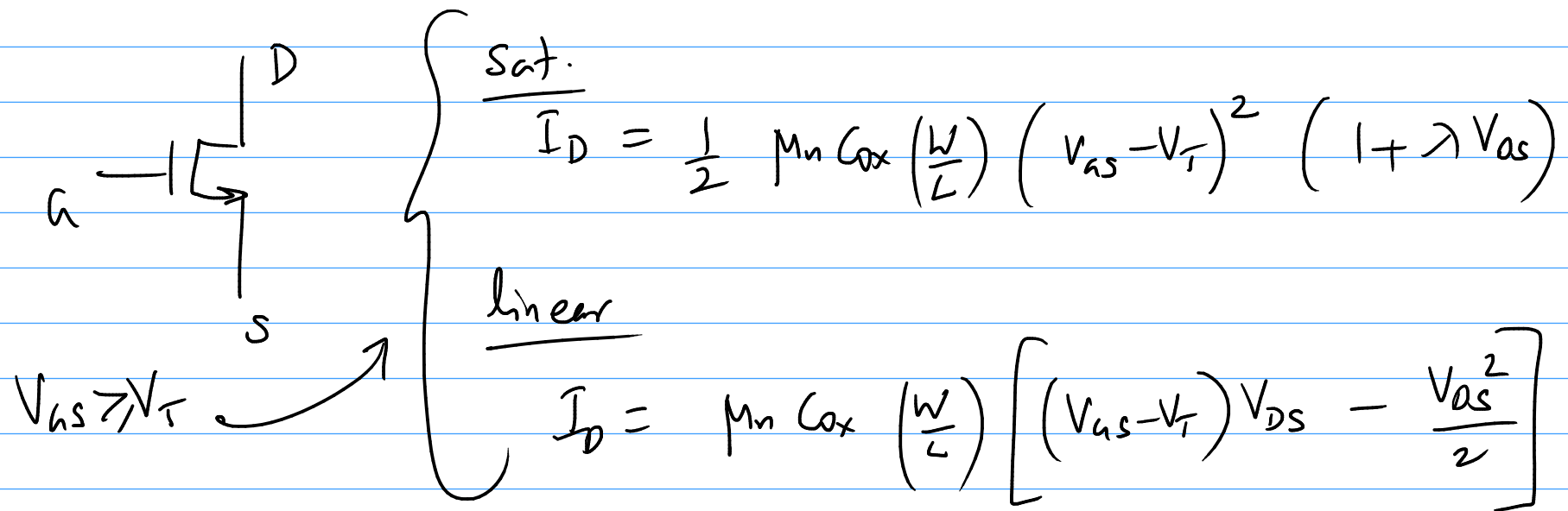



$$g_m = \frac{\partial \bar{I}_D}{\partial V_{GS}} = \mu_n C_{ox} \left(\frac{W}{L}\right) (V_{GS} - V_T)$$



$$g_{ds} = \lambda \bar{I}_D$$

$$g_{mbs} = ?$$

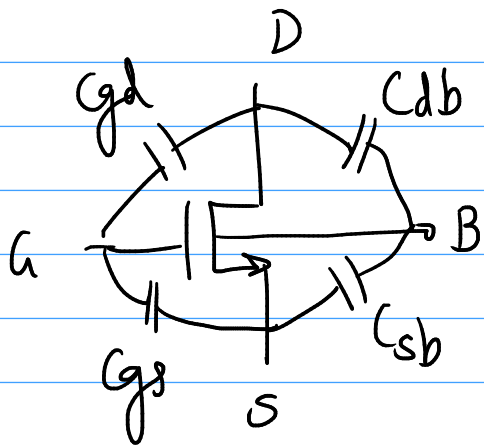

	Sat.	linear
$C_{gd}$	$W \cdot L_{ov} \cdot C_{ox}$	$\frac{1}{2} WL C_{ox}$
$C_{gs}$	$\frac{2}{3} W \cdot L \cdot C_{ox}$	$\frac{1}{2} WL C_{ox}$
$C_{db}$	$C_{jdb} + C_{swdb}$	$C_{db,lin}$
$C_{sb}$	$C_{jsb} + C_{swsb}$	$C_{sb,lin}$

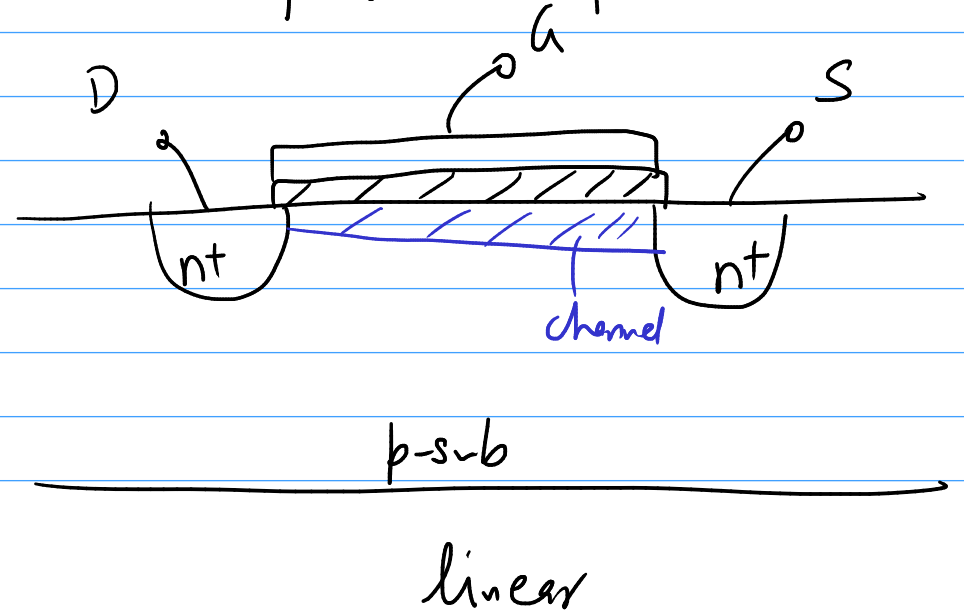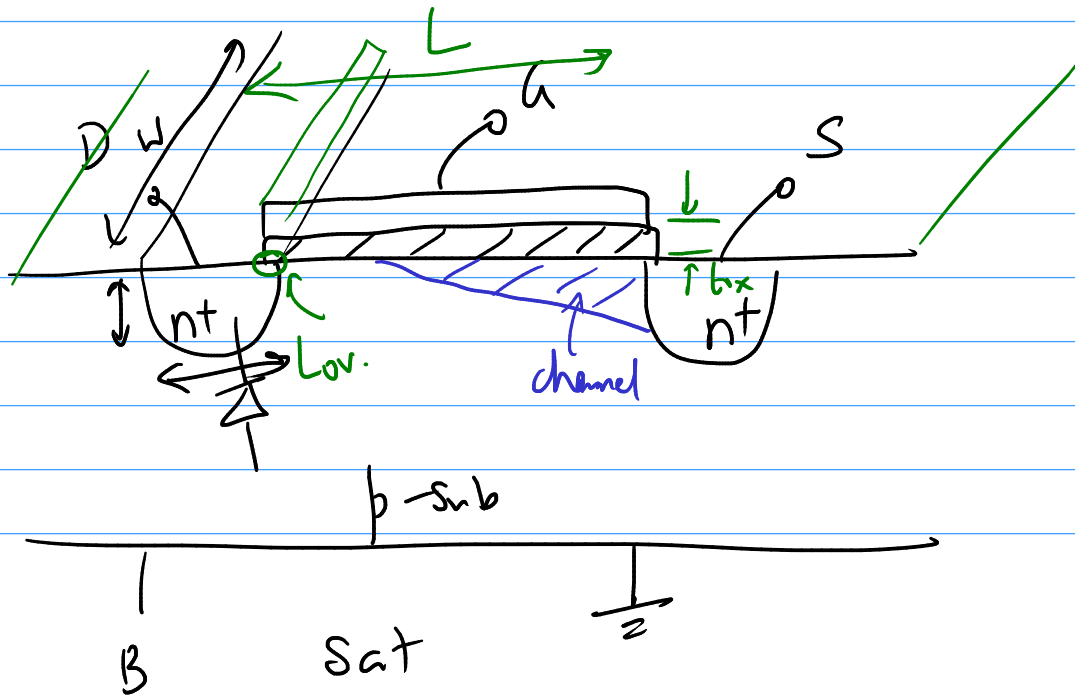

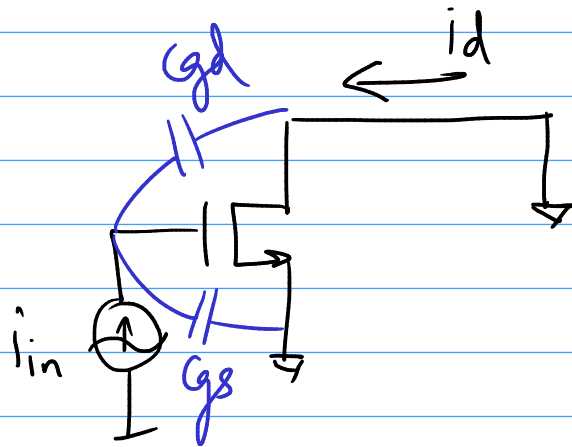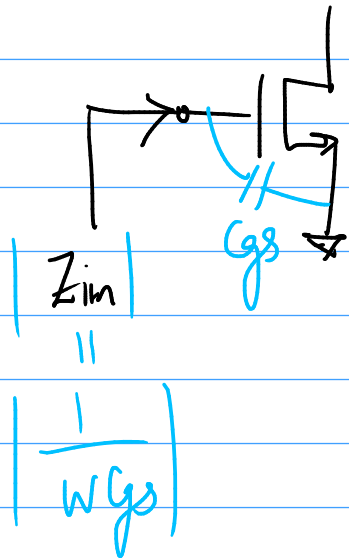

$$f_T = \frac{g_m}{2\pi(C_{gs} + C_{gd})}$$

$$\left| \frac{i_d}{i_{in}} \right| = \left| \frac{i_d}{v_{gs}} \right| \cdot \left| \frac{v_{gs}}{i_{in}} \right|$$

$$= g_m \cdot \frac{1}{\omega C_{gs}}$$


$$\omega_T \equiv \text{freq. @ which } \left| \frac{i_d}{i_{in}} \right| = 1 \implies \omega_T = \frac{g_m}{C_{gs}}$$


$$f_T = \frac{\omega_T}{2\pi}$$

# Noise

- Unwanted signal?

↳ Random sources

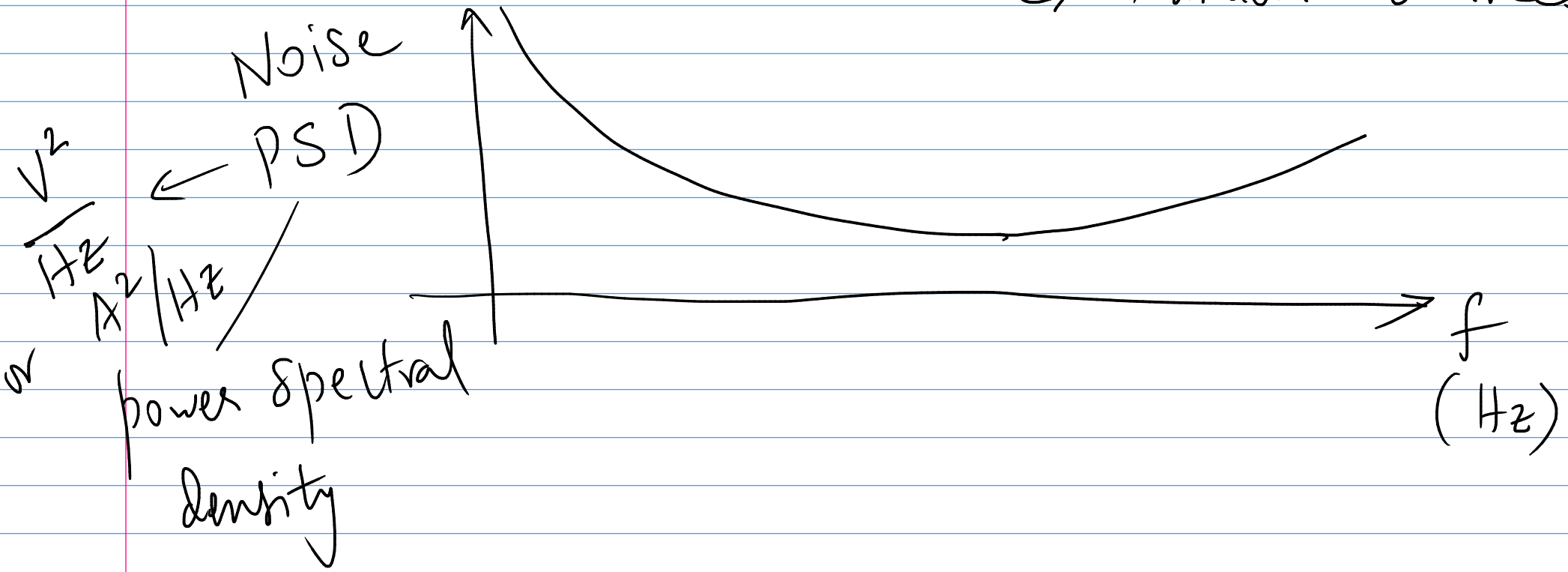

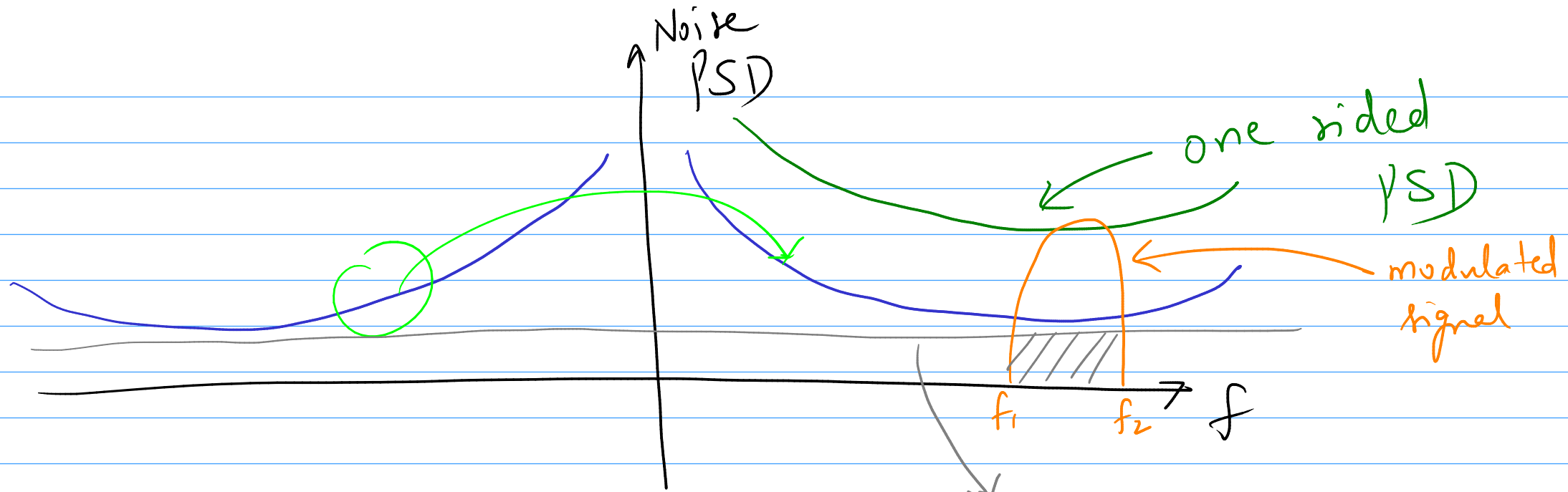

AWGN — additive white Gaussian Noise


degrade BER  
 $\updownarrow$   
 SNR

Noise PSD



$\frac{1}{f}$  → flicker Noise

coloured Noise





white / thermal Noise

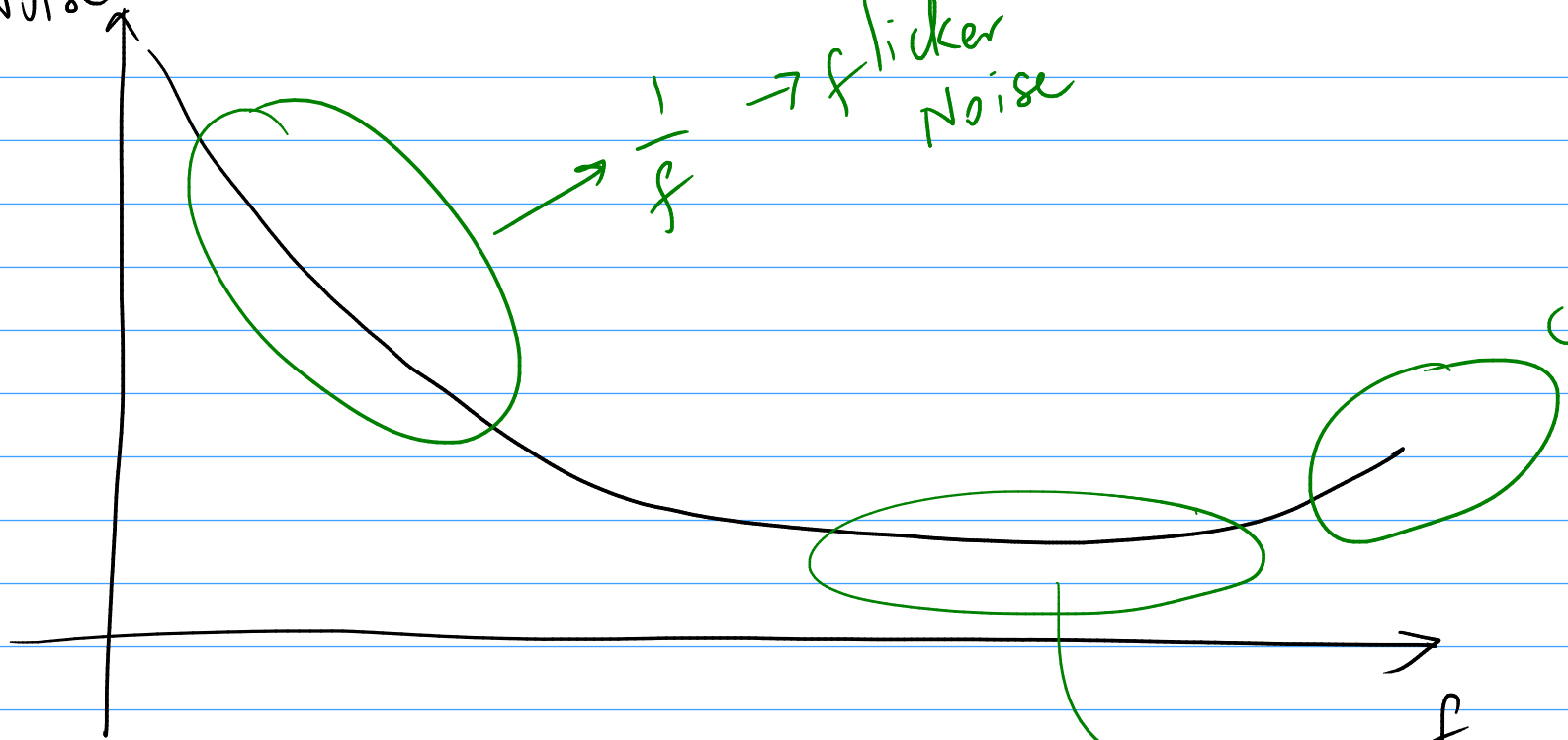

# Resistor thermal noise

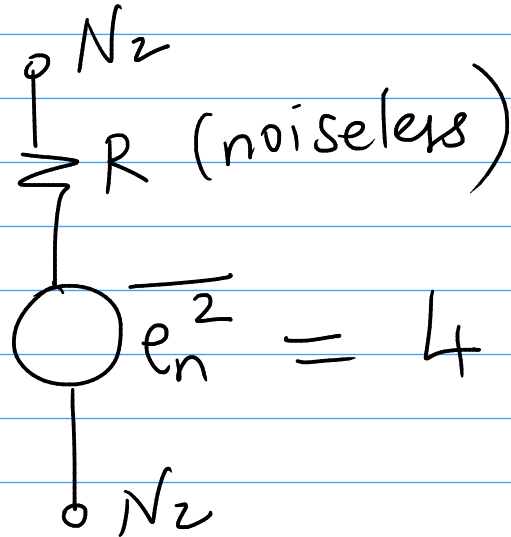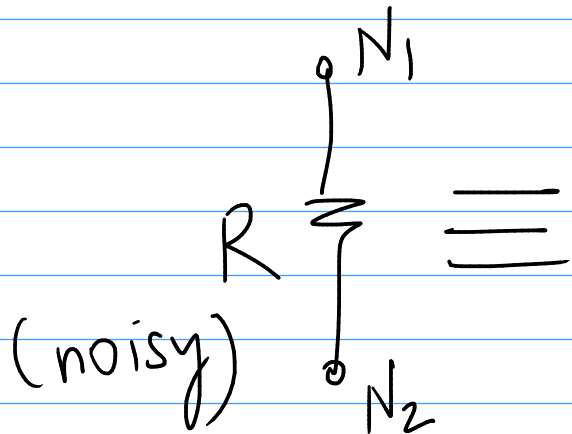
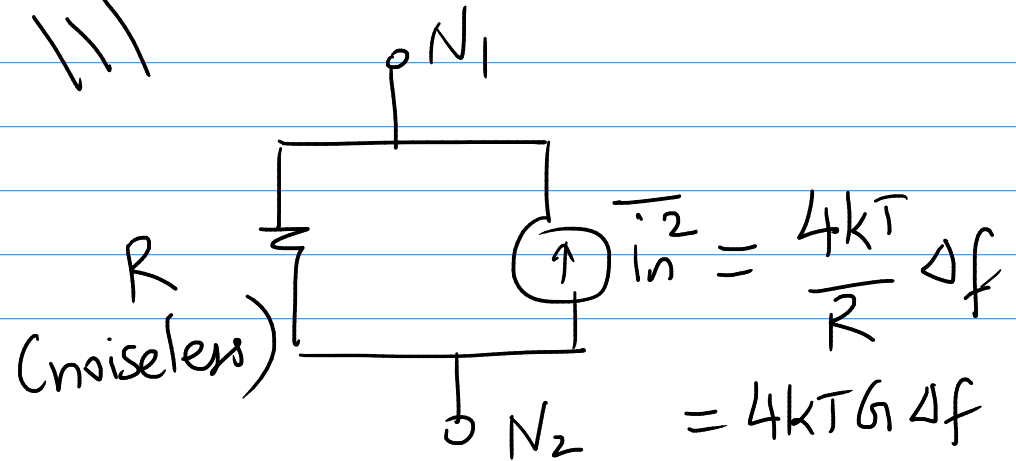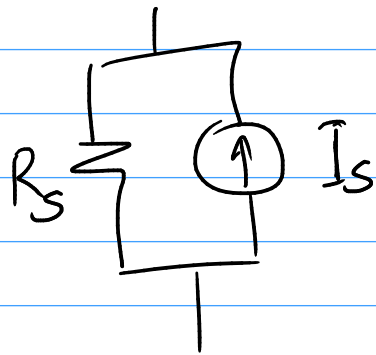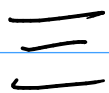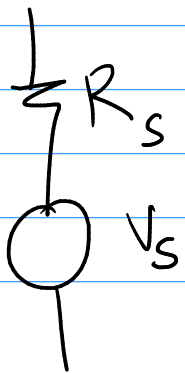
$$\overline{e_n^2} = 4kTR \Delta f \quad V^2$$



$$\overline{i_n^2} = \frac{4kT}{R} \Delta f = 4kTG \Delta f$$

e.g.  $1\text{ k}\Omega \rightarrow \frac{\overline{e_n^2}}{\Delta f} = 1.6 \times 10^{-17} \frac{\text{V}^2}{\text{Hz}}$

$\swarrow$  ms




$$\frac{\overline{i_n^2}}{\Delta f} = 1.6 \times 10^{-23} \frac{\text{A}^2}{\text{Hz}}$$

rms  $\rightarrow \frac{e_n}{\sqrt{\Delta f}} = 4\text{ nV}/\sqrt{\text{Hz}}$

$50\Omega \rightarrow \frac{\overline{e_n^2}}{\Delta f} = 8 \times 10^{-19} \frac{\text{V}^2}{\text{Hz}}$

$\swarrow$  ms

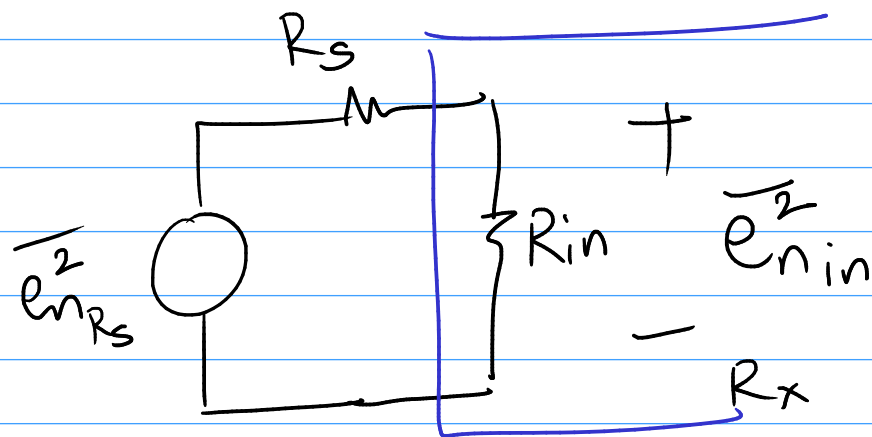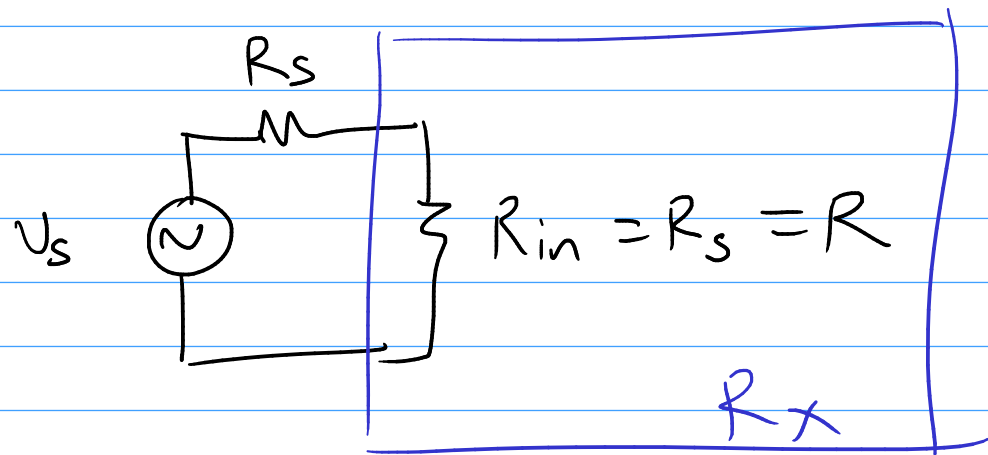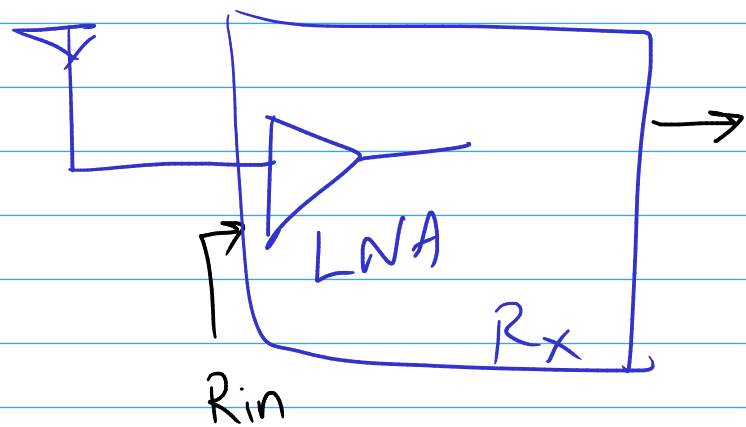rms  $\rightarrow \frac{e_n}{\sqrt{\Delta f}} = 0.9\text{ nV}/\sqrt{\text{Hz}}$



$$\overline{P_{in}} = \overline{P_{Rs}} \cdot \frac{R_{in}}{R_s + R_{in}}$$

$$\overline{P_{in}} = \frac{1}{4} \overline{P_{Rs}}$$

$$\overline{e_{n_{in}}^2} = \frac{4kTR \cdot B}{4} \quad \leftarrow \begin{array}{l} \text{bandwidth} \\ V^2 \end{array}$$


$$\overline{P_{n_{in}}} = \frac{4kTR \cdot B}{4R_{in}} = kTB \quad \text{(Watts)}$$



↑ available noise power

$$\left. \begin{array}{l} \text{Input Noise} \\ \text{PSD} \end{array} \right\} = kT \quad \text{W/Hz}$$

$$= 4.1 \times 10^{-21} \text{ W/Hz @ RT}$$



$$= -174 \text{ dBm/Hz}$$

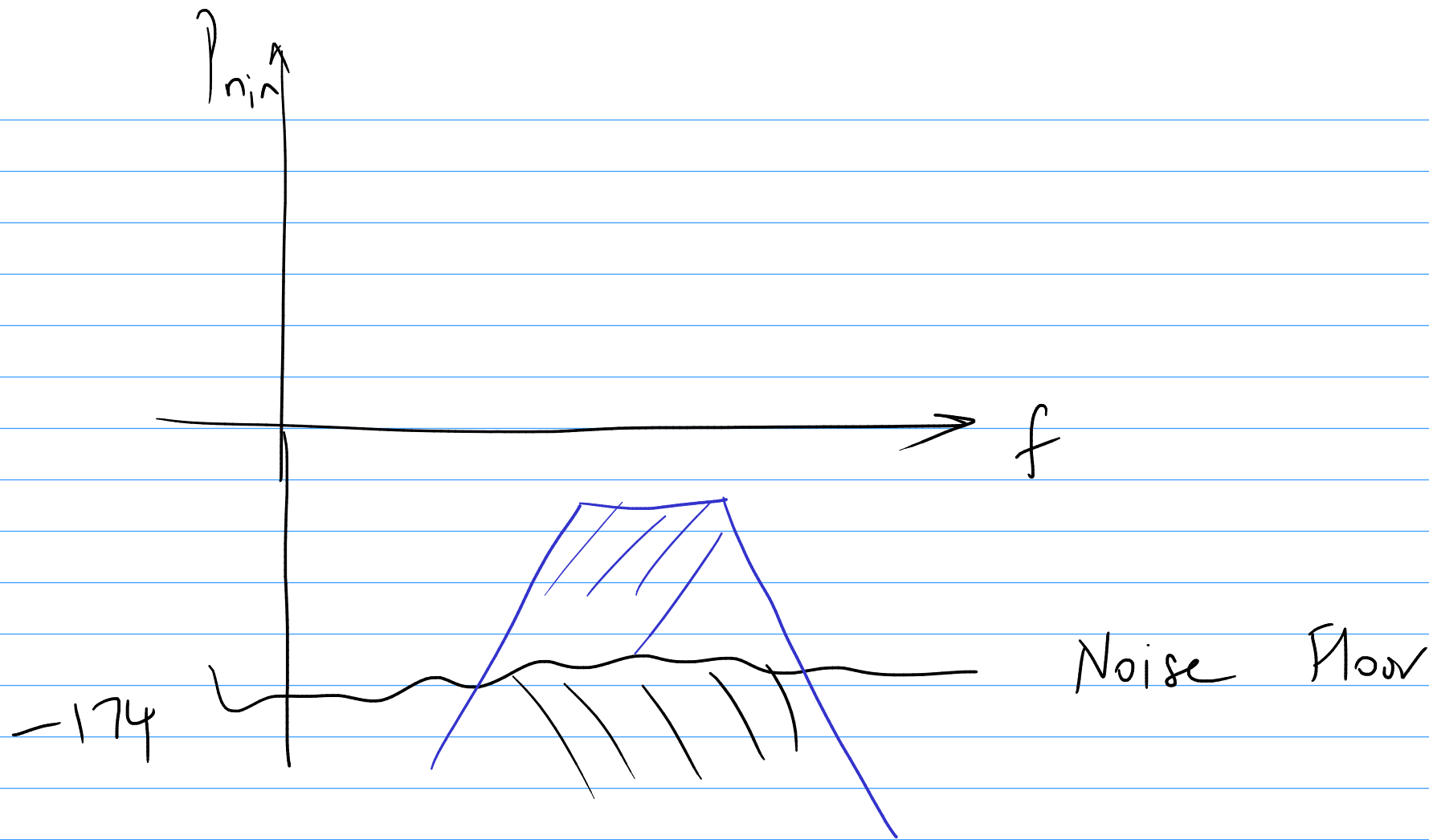

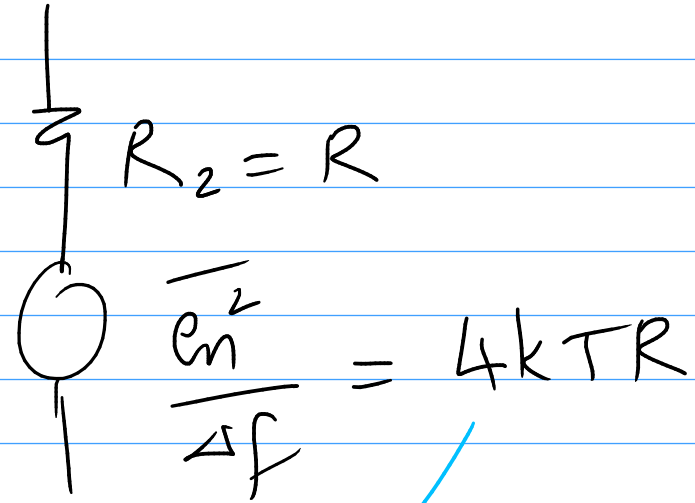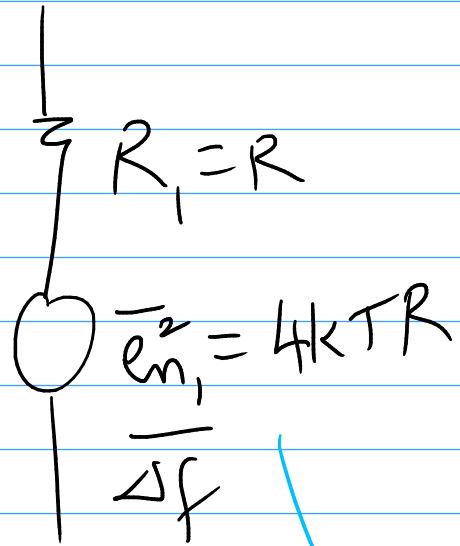


un-correlated
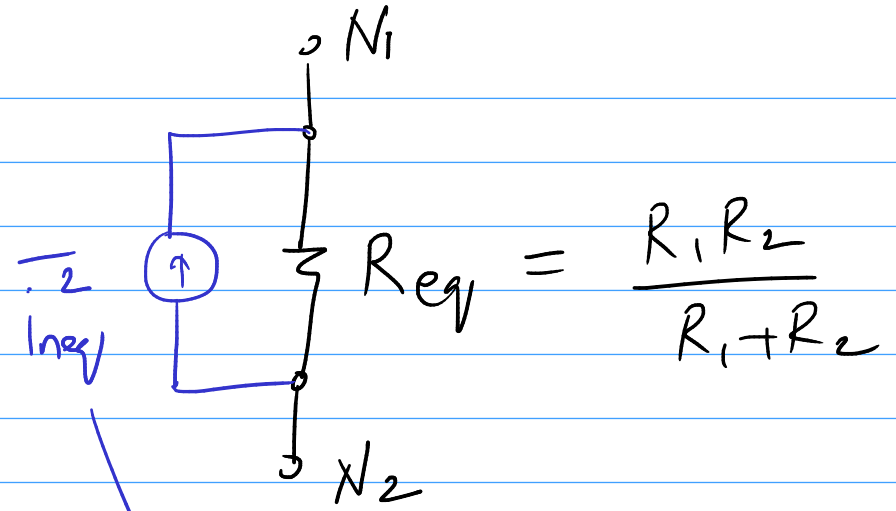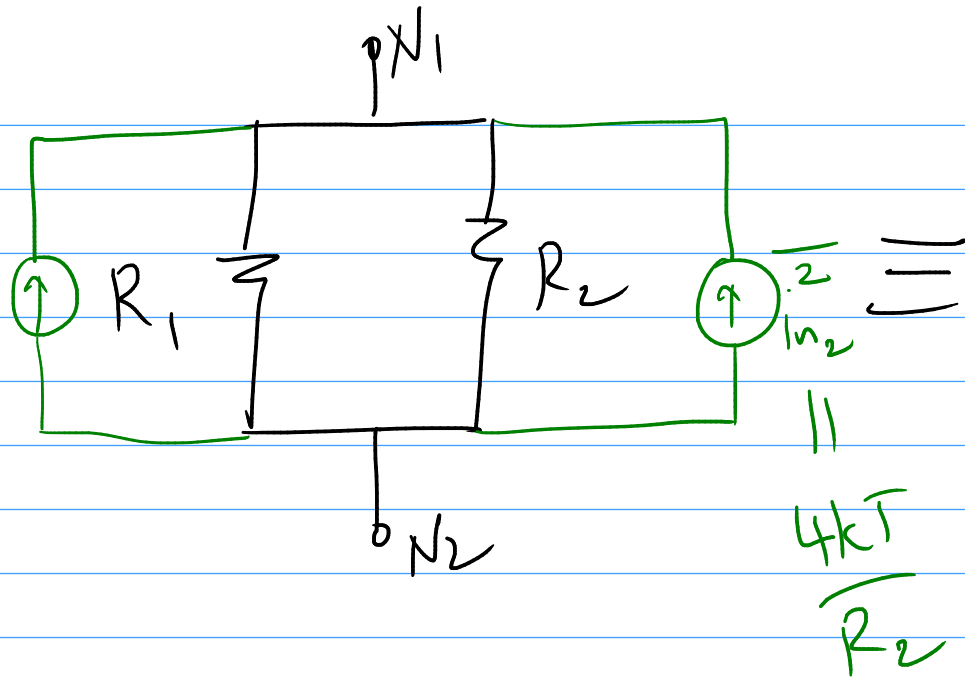
$$\frac{4kT}{R_1} \parallel \frac{4kT}{R_2}$$



$$4kT \left( \frac{1}{R_1} + \frac{1}{R_2} \right)$$


$$= \frac{4kT}{R_{eq}}$$

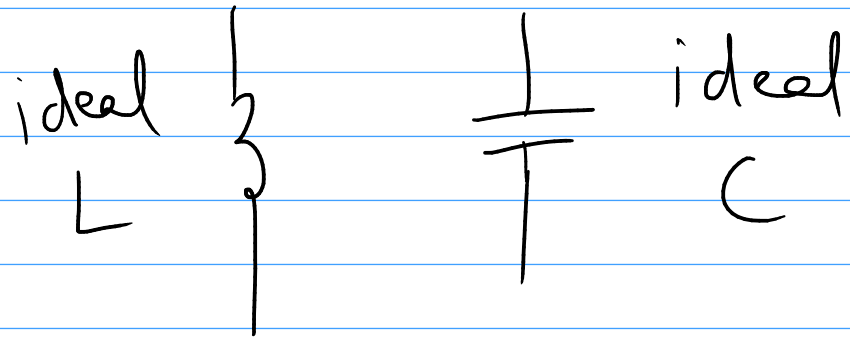

→ No noise

Thermal  
Noise

MOSFETS

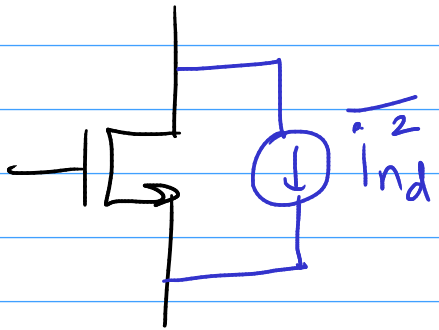

1) Triode :  $\overline{i_{dn}^2} = 4kT g_{do} \Delta f$   
 $\left\{ \text{or } 4kT \gamma^2 g_{do} \Delta f ; \right.$   
 $\left. \gamma = 1 \right\}$

$$g_d = \frac{\partial I_D}{\partial V_{DS}}$$


$$= \frac{\partial}{\partial V_{DS}} \left[ \mu_n C_{ox} \left( \frac{W}{L} \right) (V_{GS} - V_T) \cdot V_{DS} - \frac{V_{DS}^2}{2} \right]$$

in

$$g_d = \mu_n C_{ox} \left( \frac{W}{L} \right) (V_{GS} - V_T - V_{DS})$$

$$g_{do} = \mu_n C_{ox} \left( \frac{W}{L} \right) (V_{GS} - V_T)$$

In Sat. region


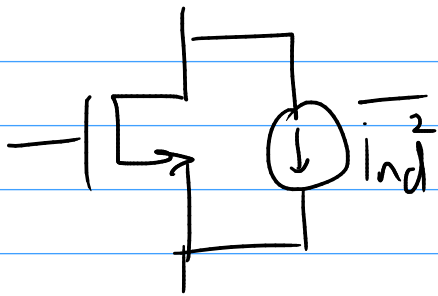


$$\overline{i_{nd}^2} = 4kT \gamma^2 g_{do} \Delta f \quad \rightarrow = g_{m \text{ sat.}}$$


$$\gamma = \frac{2}{3} \quad \text{for long channel device}$$

$$\overline{i_{nd}^2} = \frac{8kT}{3} g_m \Delta f$$

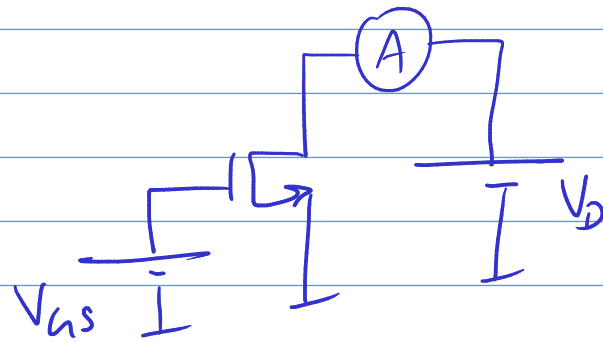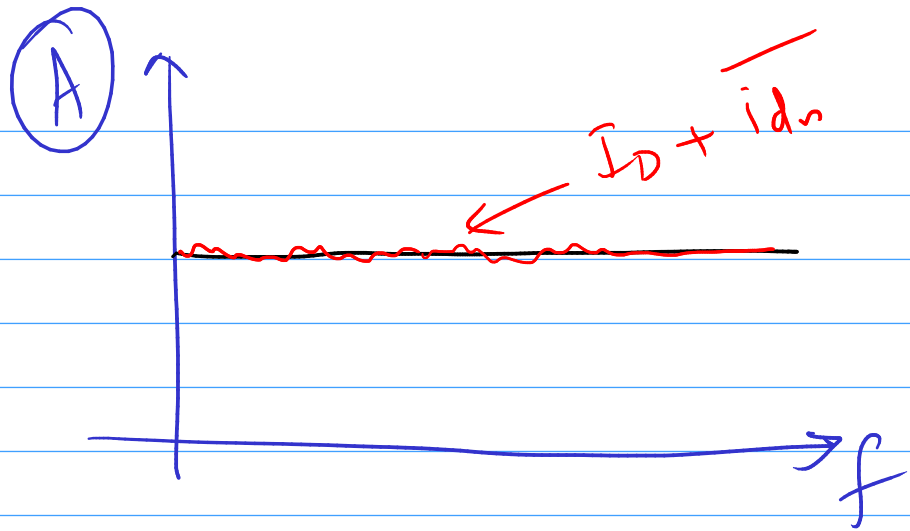short channel devices  $\rightarrow \gamma = 2-3$




# Flicker Noise

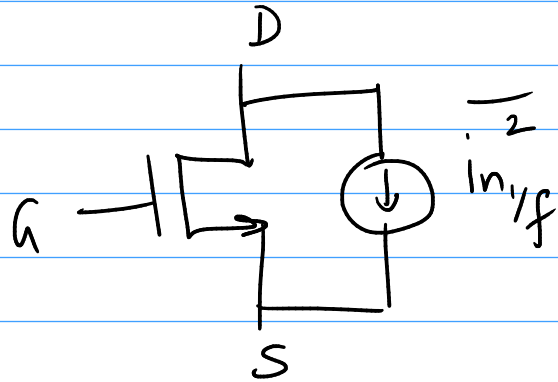


$$\overline{i_{n,1/f}^2} = \frac{k_f}{WLCox} g_m^2 \cdot \frac{1}{f} \cdot \Delta f$$

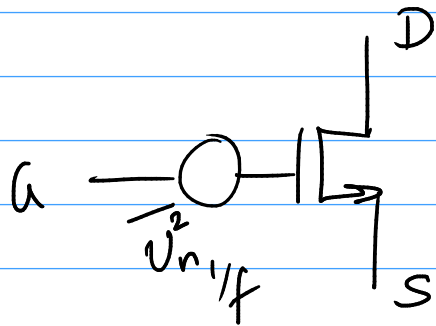
Lower flicker noise  
if you increase gate area







$$\overline{v_{n,1/f}^2} = \frac{k_f}{WLCox} \cdot \frac{1}{f} \cdot \Delta f$$

$i_{n2}^2$   
 $i_{n1}^2$

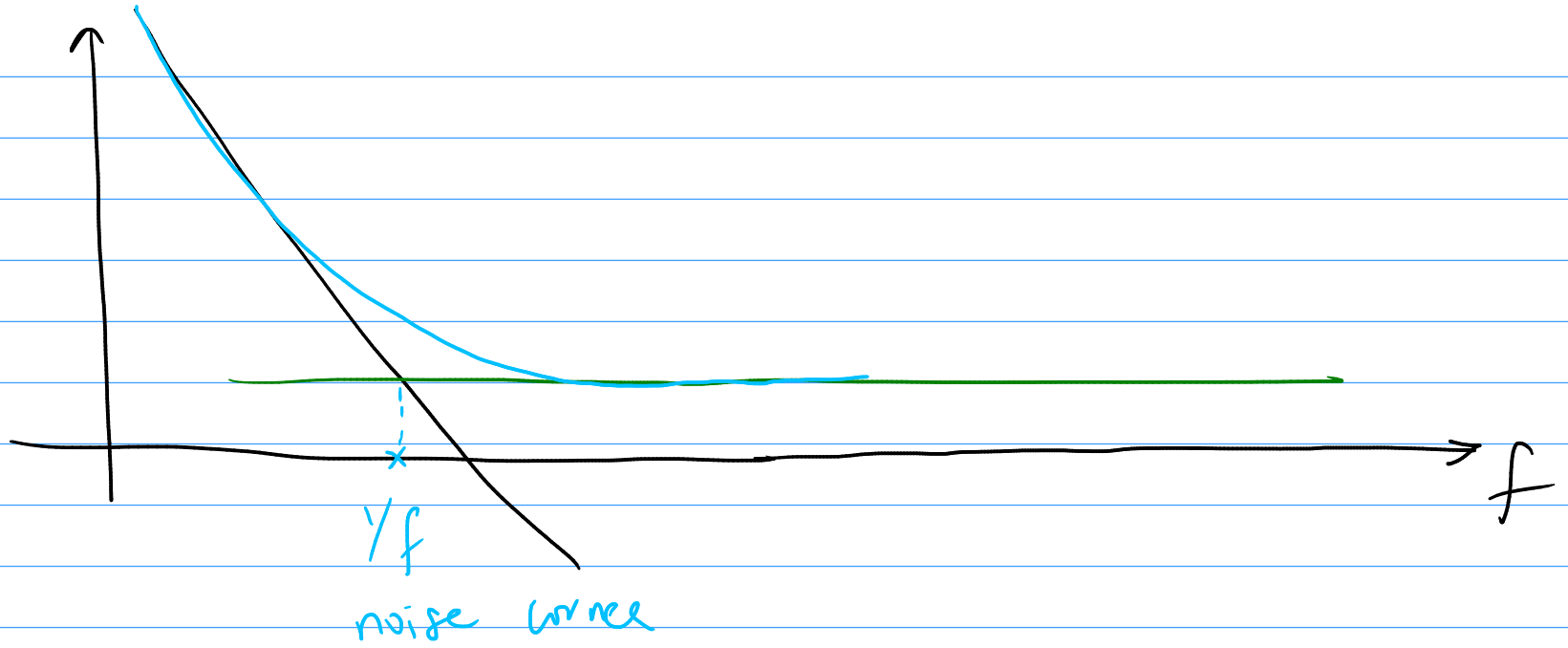


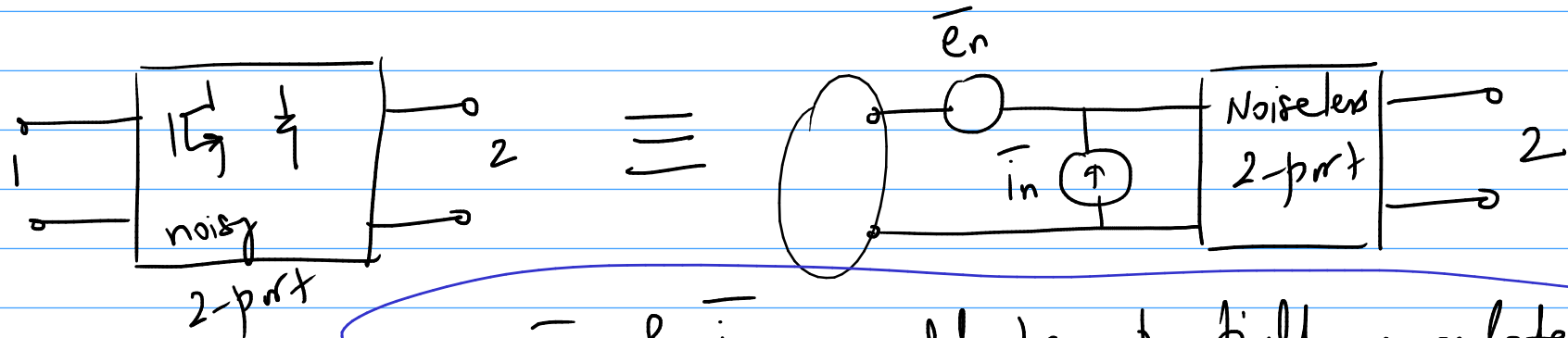


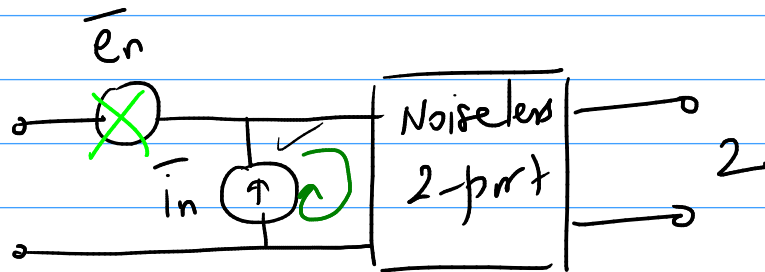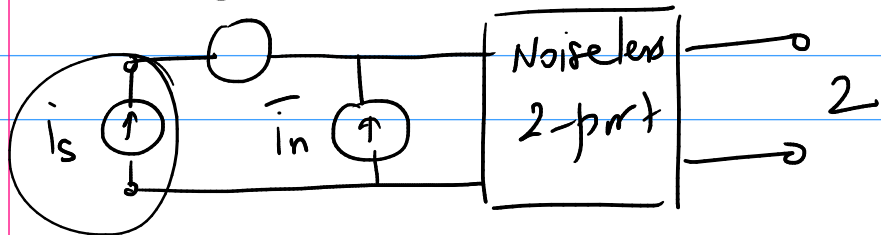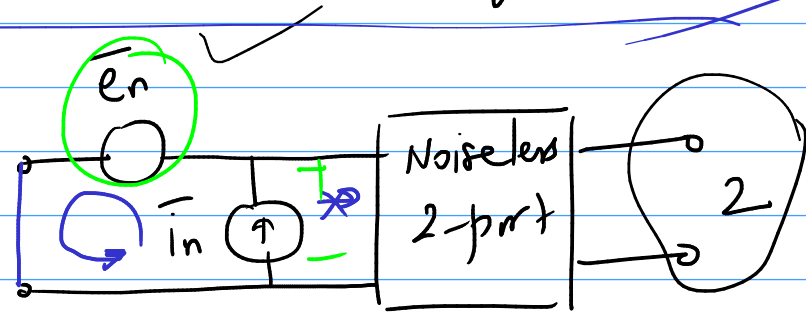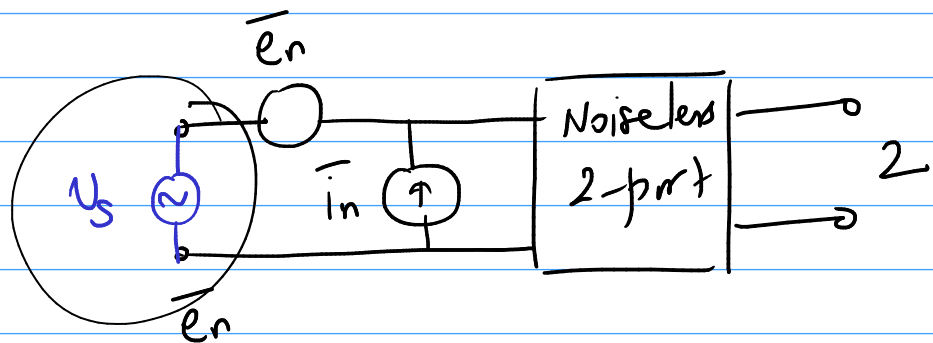
$\bar{e}_n$  &  $\bar{i}_n$  could be partially correlated



\* Need both  $\bar{e}_n$  &  $\bar{i}_n$   $\rightarrow$  esp. for RF circuits

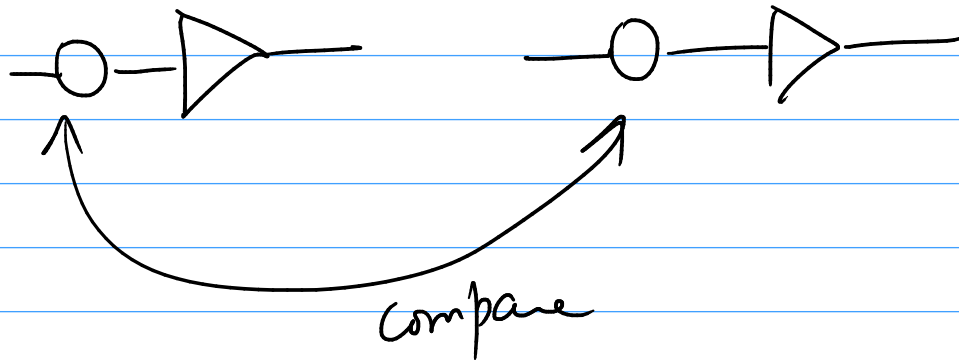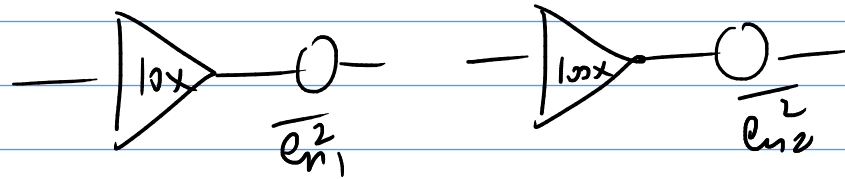\*  $\bar{e}_n$  &  $\bar{i}_n$  are fictitious sources



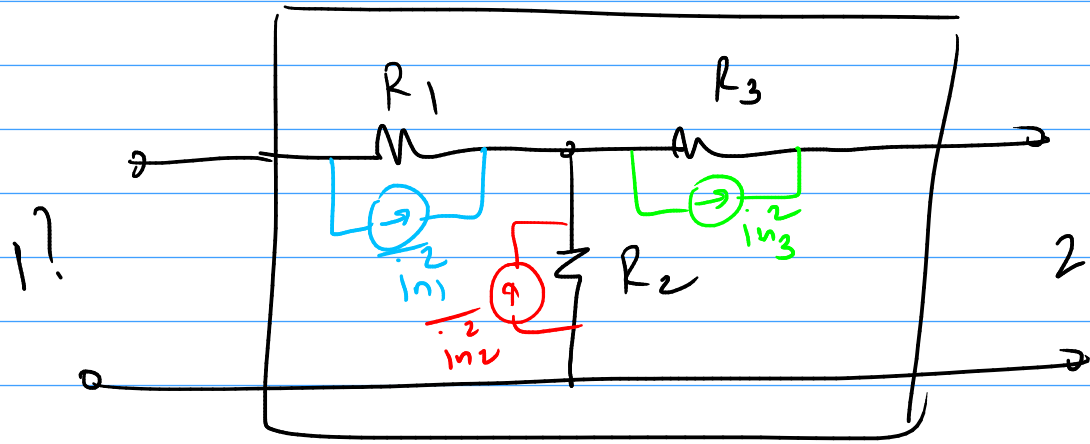

\* apply ideal is @ port 1

\* ...  
\* calculate  $\bar{i}_n$

?  
\* Apply a "convenient" load  
@ port 2 e.g. S.C. or O.C.



\* Apply ideal  $V_s$  @ port 1

\* calculate noise due to  $\bar{e}_n$  @ port 2 (A)


\* Do the same for actual network (B)

\* Apply  $\bar{i}_{n1}, \bar{i}_{n2}, \bar{i}_{n3}$   
in turn

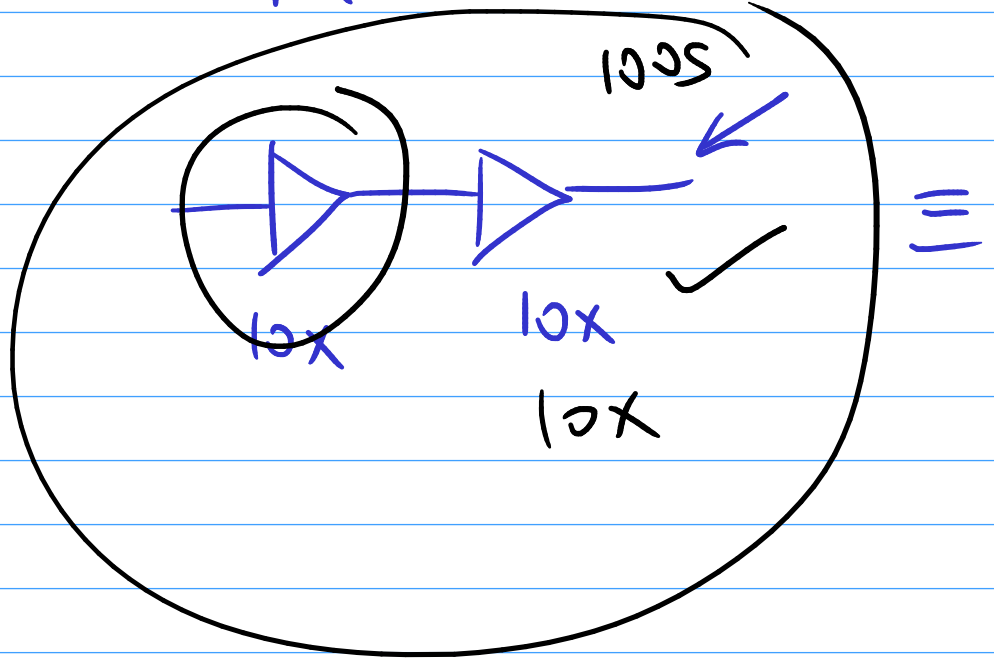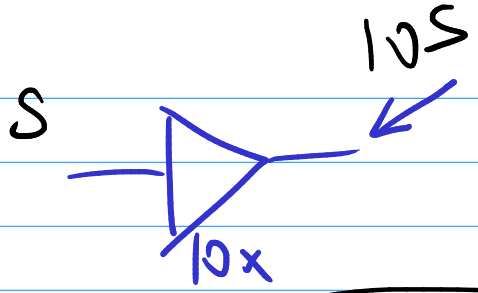
\* Equate (A) & (B)  $\rightarrow$  gives us  $\bar{e}_n$



$\equiv$

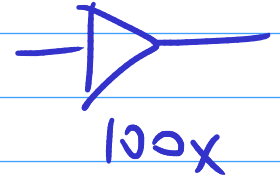

# Example #1

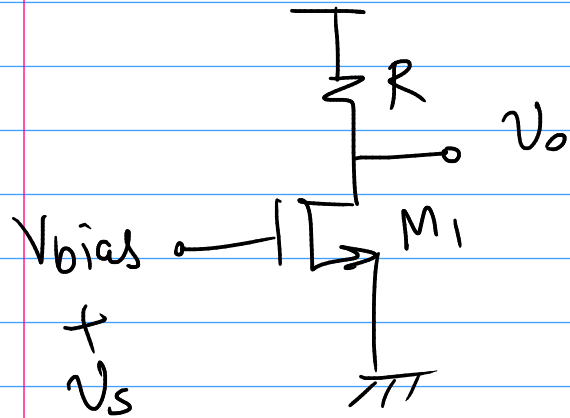


I

$\overline{e_n}, \overline{i_n} = ?$  @ low freq.

$Z_{in} = \infty$  @ low freq.


$\Rightarrow \overline{i_n} = 0$

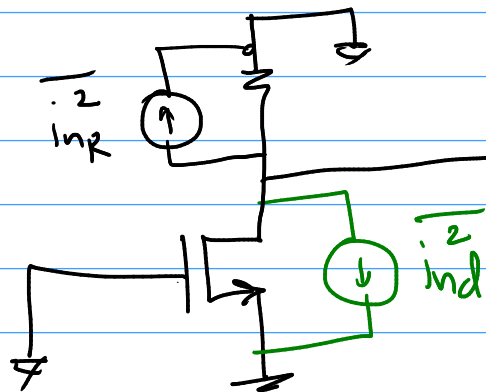


$$\overline{i_{nsc,1}^2} = \overline{i_{nR}^2} + \overline{i_{nd}^2}$$

$$\frac{\overline{i_{nsc,1}^2}}{\Delta f} = \frac{4kT}{R} + 4kT \alpha^2 g_m$$

II

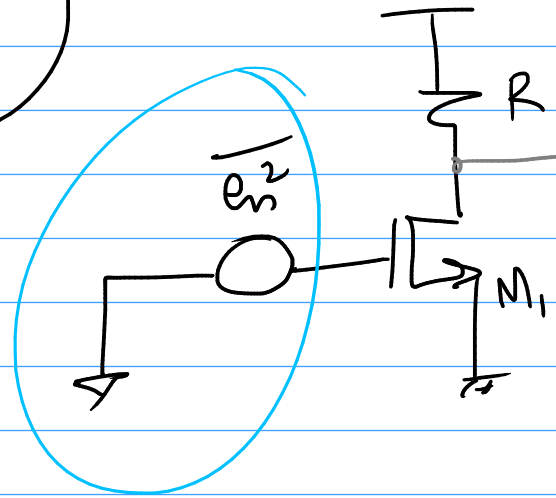
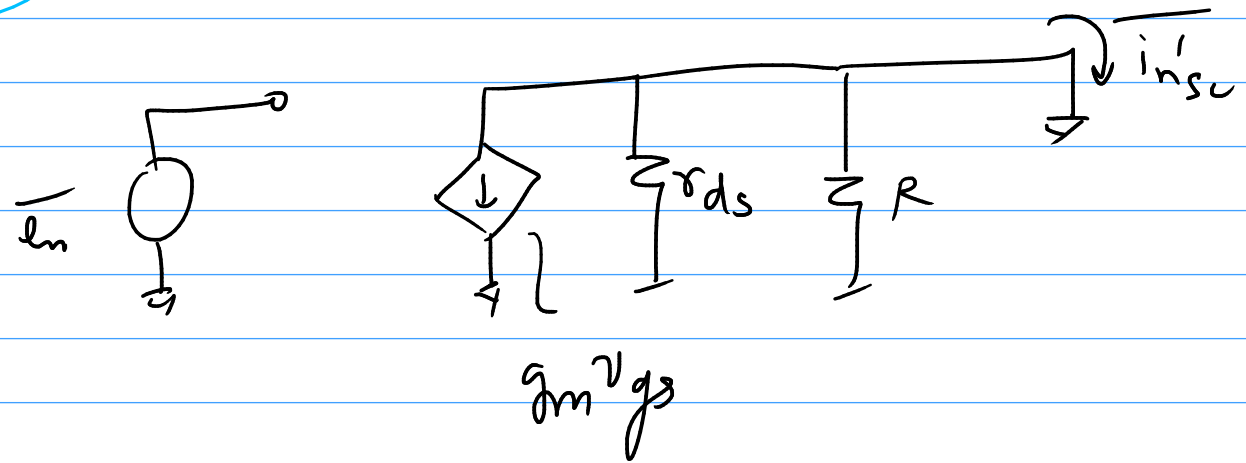
$$\overline{i_{nsc}^2} = \overline{e_n^2} \cdot g_m^2$$



Equation


$$\overline{i_{nsc}^2} = \overline{e_n^2}$$

$$g_m^2 \frac{\overline{e_n^2}}{\Delta f} = \frac{4kT}{R} + \frac{4kTg_m}{\mu}$$

$$\frac{\overline{e_n^2}}{\Delta f} = \frac{4kT}{g_m^2 R} + \frac{4kTg_m}{g_m}$$


↑  $g_m \Rightarrow$  ↓  $e_n$

Ex 2

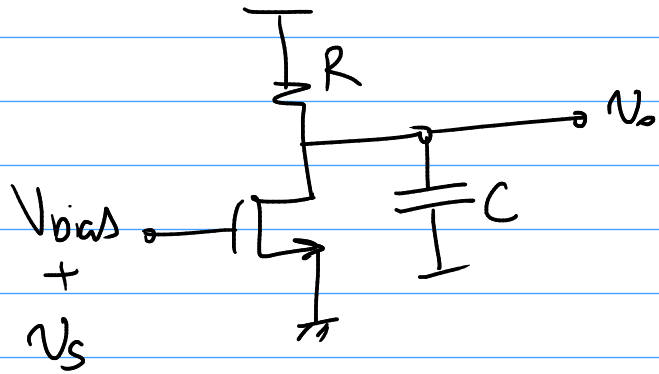


$$\overline{i_n^2} = 0$$

$e_n^2 =$  same as before

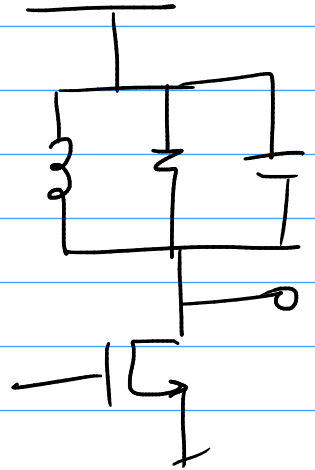

Ex 3

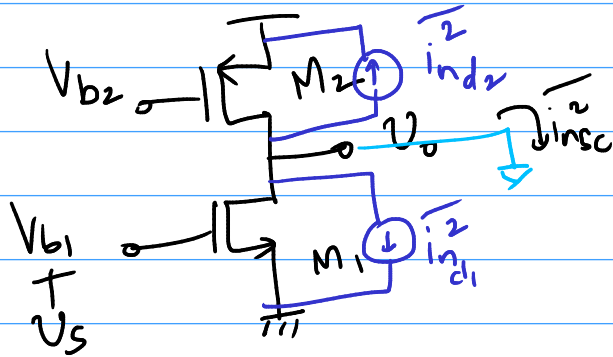

$$\overline{i_n^2} = 0$$

$$\overline{e_n^2} =$$


$$\frac{\overline{i_{nsc}^2}}{g_{m1}^2} =$$

$$4kT \gamma_1^2 g_{m1} + 4kT \gamma_2^2 g_{m2}$$

$$g_{m1}^2$$


$$\frac{|e_n^2|}{\Delta f} = \frac{4kT\gamma_1}{g_{m1}} + 4kT\gamma_2 \cdot \frac{g_{m2}}{g_{m1}^2}$$

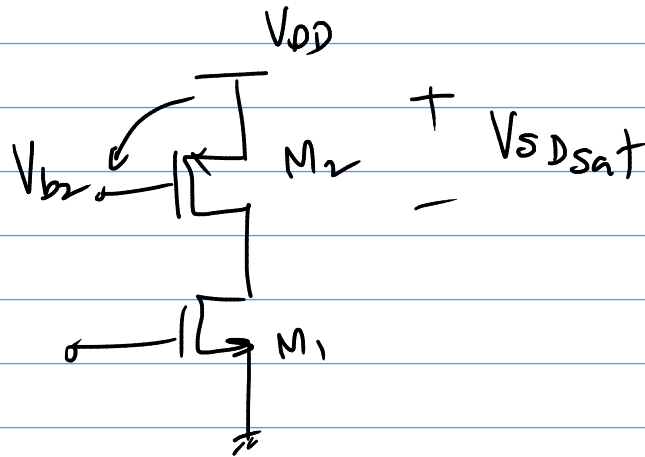for low noise  $\rightarrow$   $\uparrow g_{m1}$ ,  $\downarrow g_{m2}$   $\rightarrow V_{GS} - V_T \uparrow$   
 keep  $I_{bias}$  constant




$\uparrow \left(\frac{W}{L}\right)_1 \rightarrow (V_{GS} - V_T)_1 \downarrow$

Ex 4

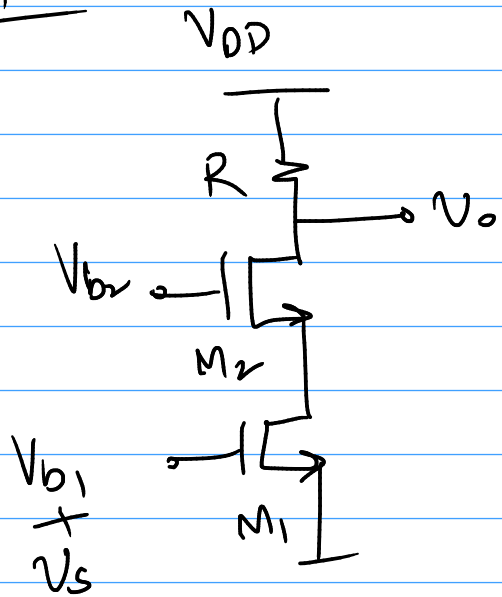


$\overline{e_n^2} = ?$


(I)

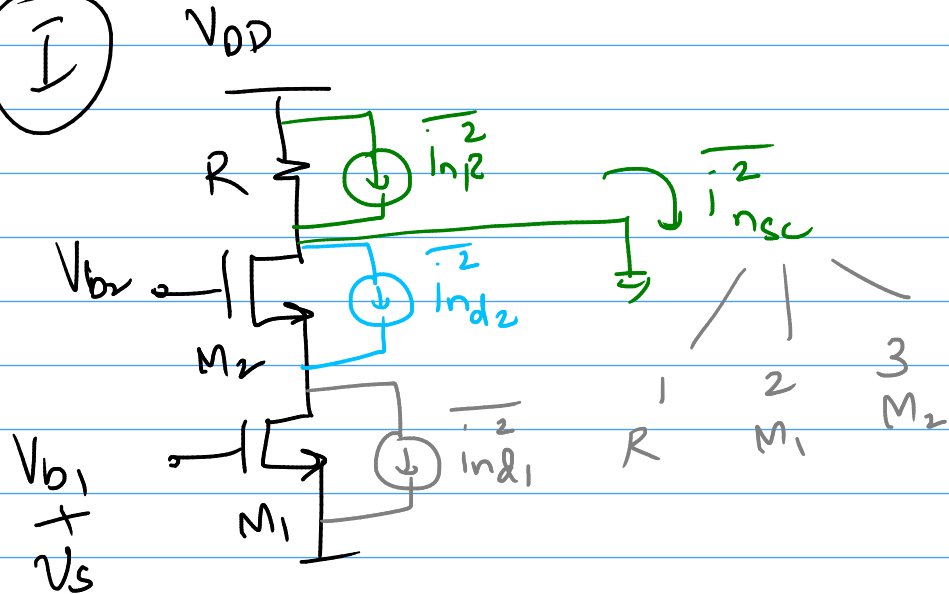

(II)

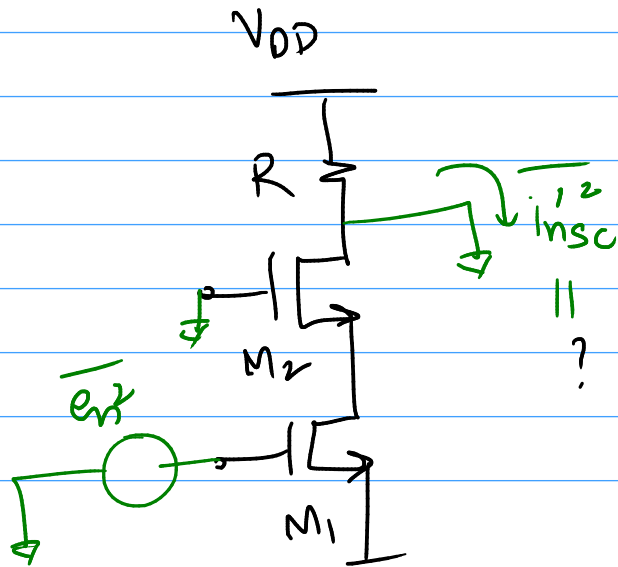


II

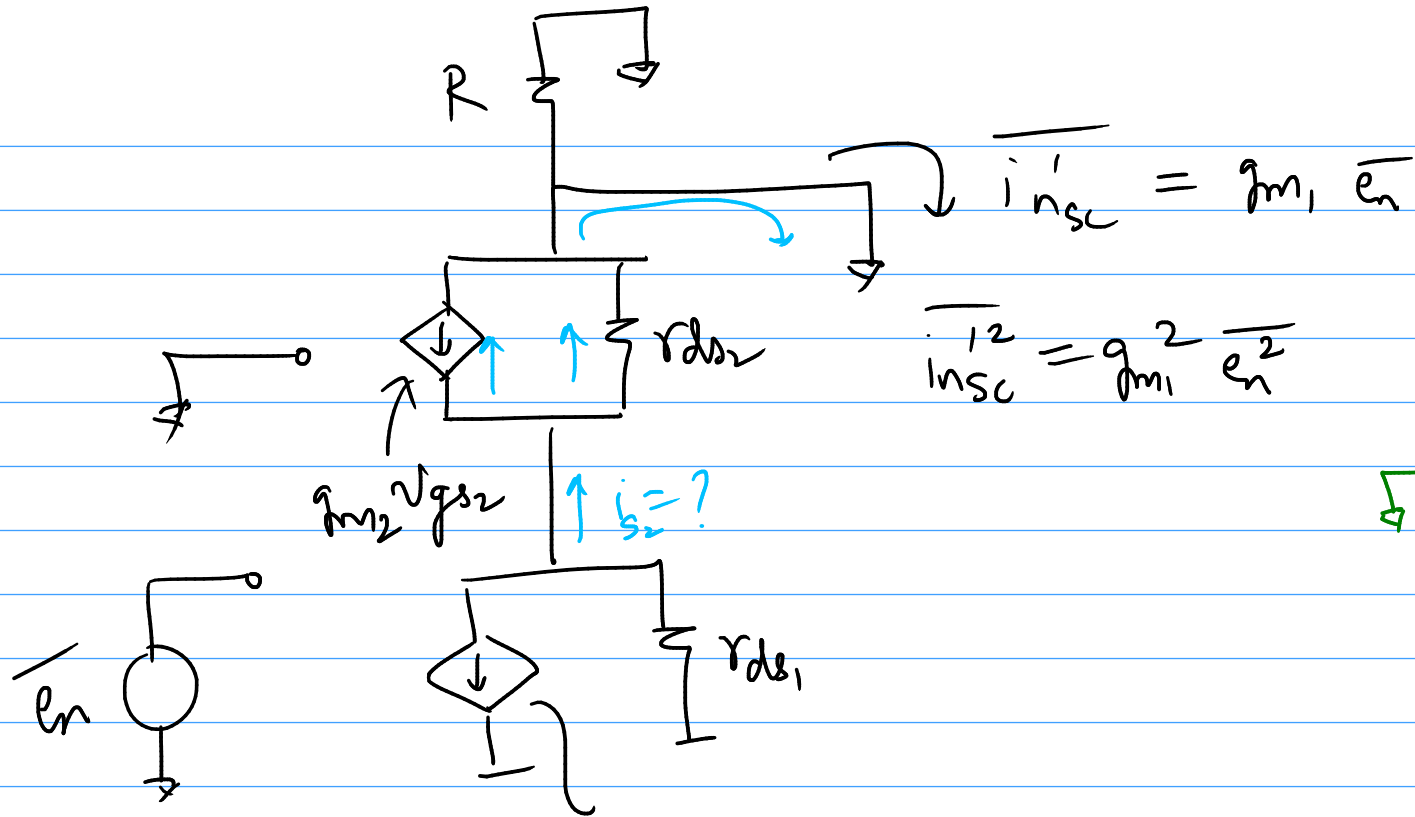

$$\overline{i'_{nsc}} = g_{m1} \overline{e_n}$$
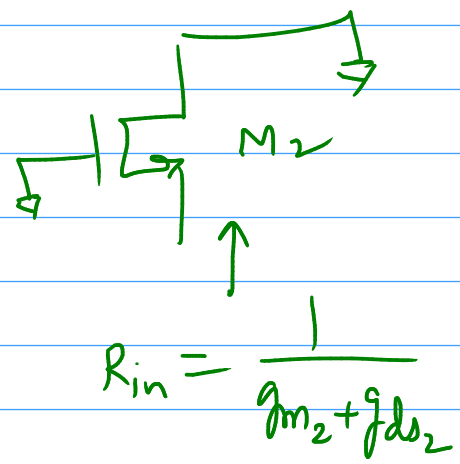
$$\overline{i_{nsc}^2} = g_{m1}^2 \overline{e_n^2}$$



$$R_{in} = \frac{1}{g_{m2} + g_{ds2}}$$

$$g_{m1} V_{gs1} = g_{m1} \overline{e_n}$$



$$\overline{i_{s2}} = g_{m1} \overline{e_n} \times \frac{r_{ds1}}{r_{ds1} + \frac{1}{g_{m2} + g_{ds2}}} \approx g_{m1} \overline{e_n}$$


(I)

a)  $\overline{i_{nr}^2} = 0$      $\overline{i_{nsc_a}^2} = \overline{i_{nr}^2}$


b)  $\overline{i_{nd_1}^2} = 0$      $\overline{i_{nsc_b}^2} = \overline{i_{nd_1}^2}$

c)  $\overline{i_{nd_2}^2} = 0$

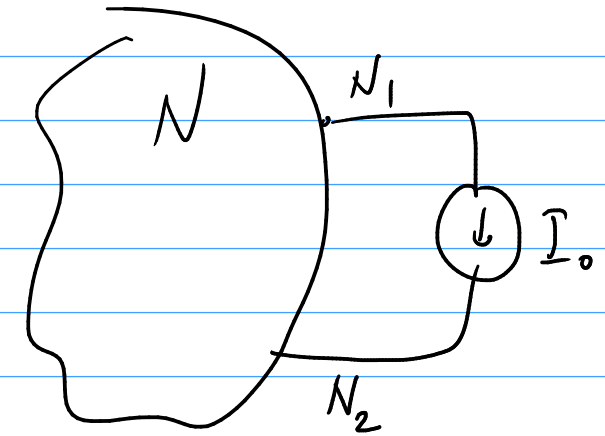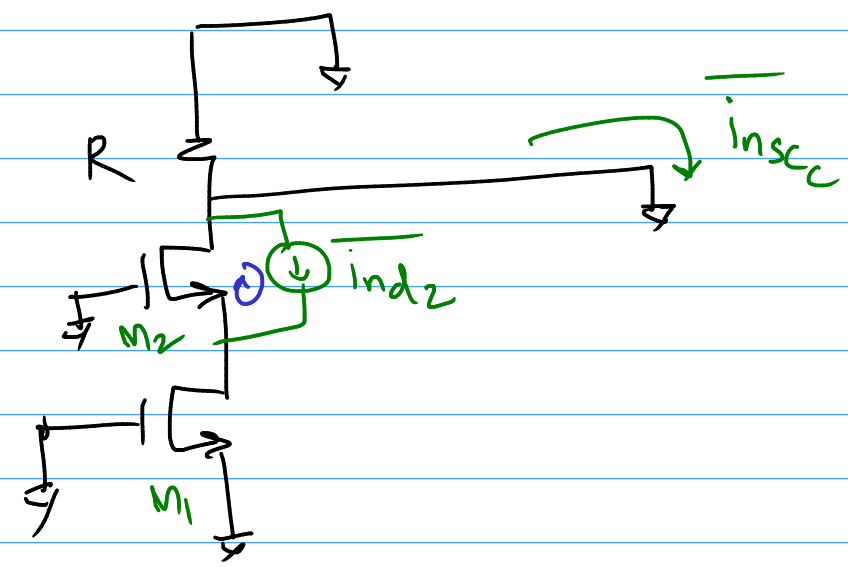


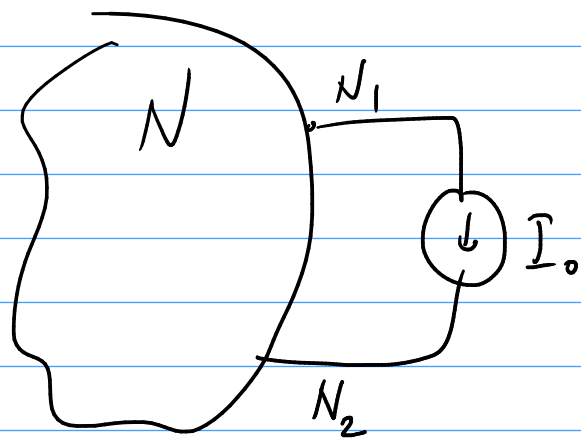


$\equiv$

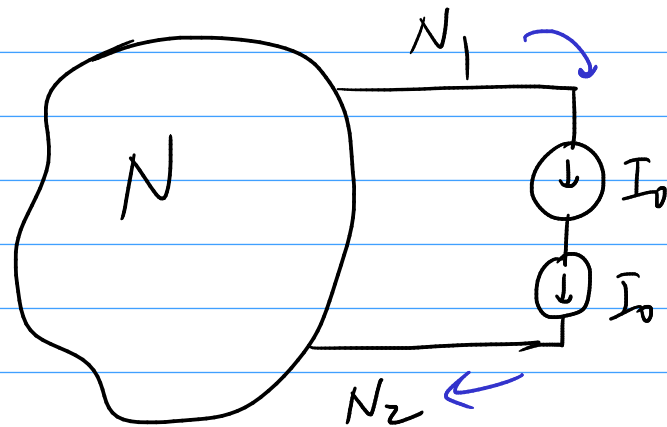


$\equiv$

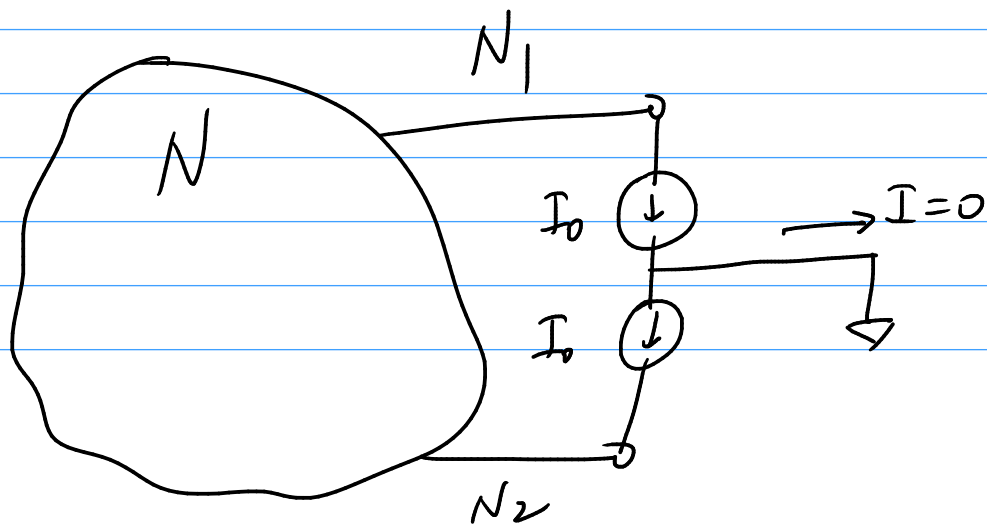

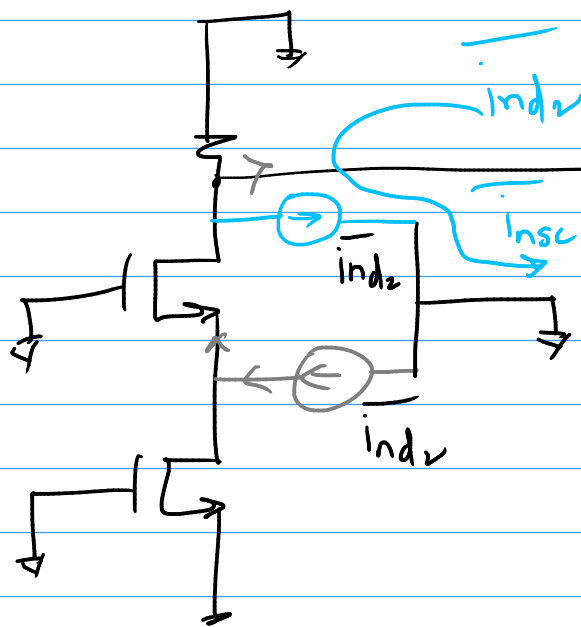

$$i_{nsc} = i_{nsc} + i_{nsc}$$

$$-i_{ind2} + i_{ind2} = 0$$

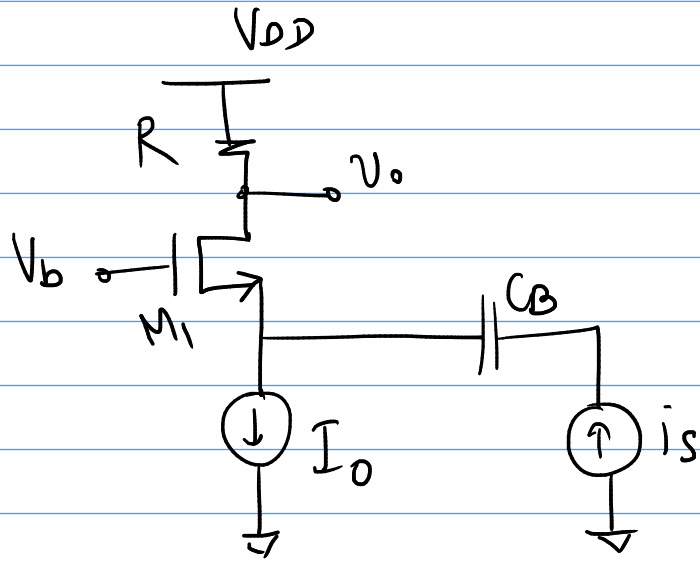


$$\overline{e_n} = ? \quad (\text{HW})$$

$$\overline{i_n} = ? \quad (\text{HW}) \longrightarrow$$

Output referred noise due to  $\overline{i_n}$




||

Output referred noise due to R & M1

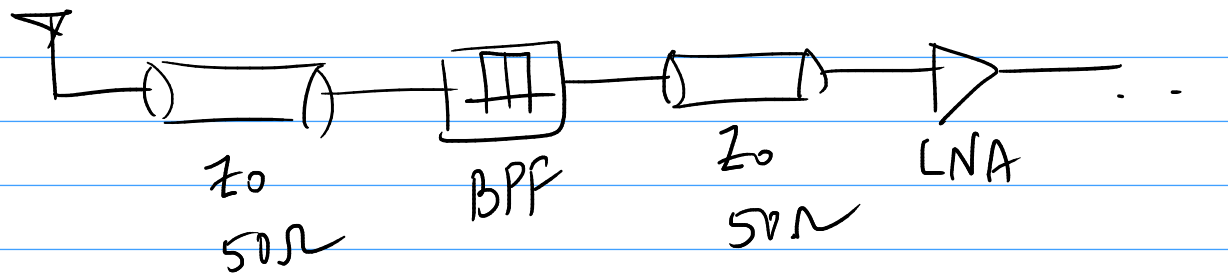


In RF Systems  $\rightarrow$  Use "Noise Figure"
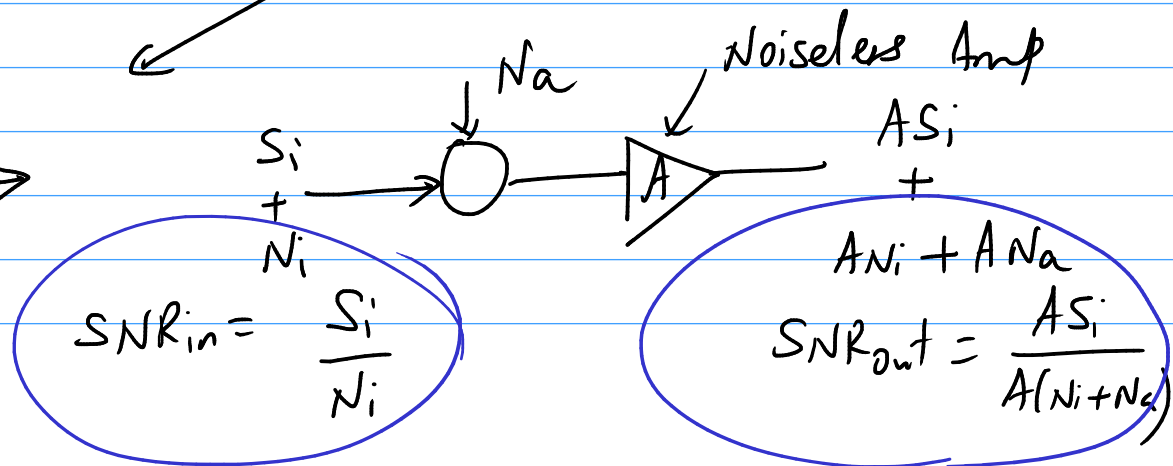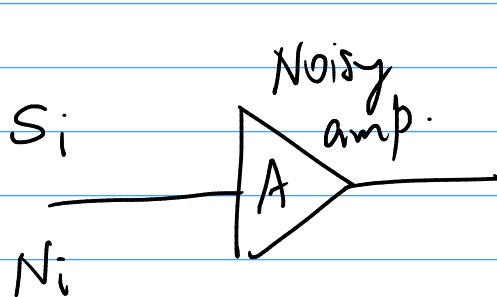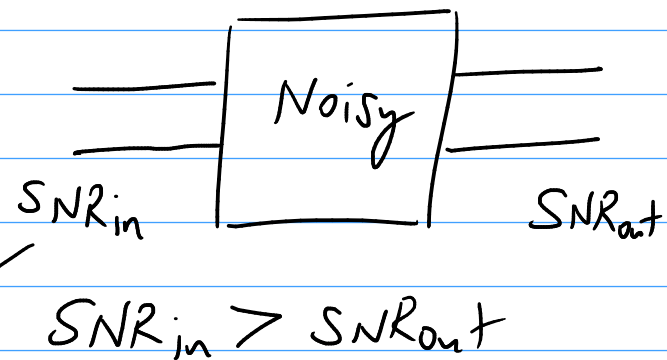
$$\text{Noise Factor "F"} = \frac{SNR_{in}}{SNR_{out}}$$



$$\text{Noise Figure} = 10 \log_{10} (F) = \text{SNR}_{in} (\text{dB}) - \text{SNR}_{out} (\text{dB})$$

"NF" (dB)

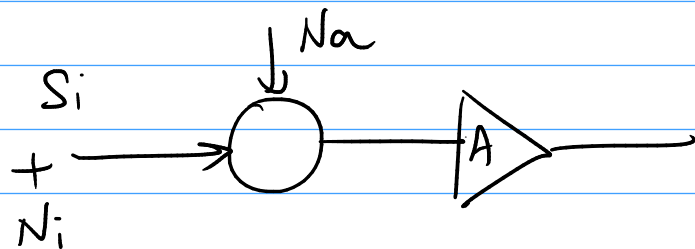

$$F = \frac{\text{SNR}_{in}}{\text{SNR}_{out}} = \frac{S_i / N_i}{A S_i / A (N_i + N_a)}$$


$$F = \frac{N_i + N_a}{N_i} = \frac{A (N_i + N_a)}{A N_i}$$

$$F = \frac{\text{Total output-referred noise}}{\text{Output noise due to source alone}}$$

$$\hookrightarrow F = 1 + \frac{N_a}{N_i}$$

$\hookrightarrow$  depends on  $R_s$ ,  
&  $N_i$

## Noise Temperature

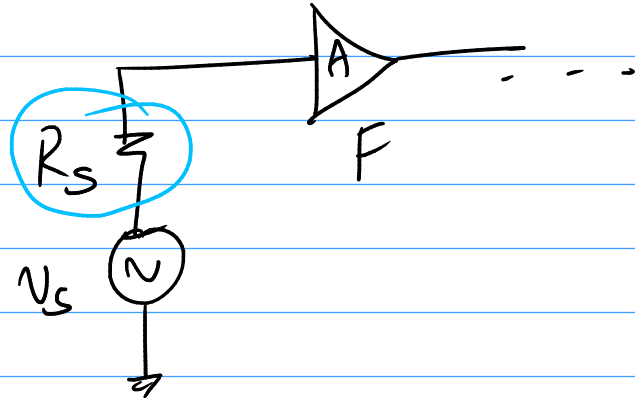

Noise temp.  $T_N$


|||

increase in temp of  $R_s$  to

account for  $F$  i.e.  $N_a$

$$F = 1 + \frac{T_N}{T_{ref}}$$

# Low - Noise Amplifiers

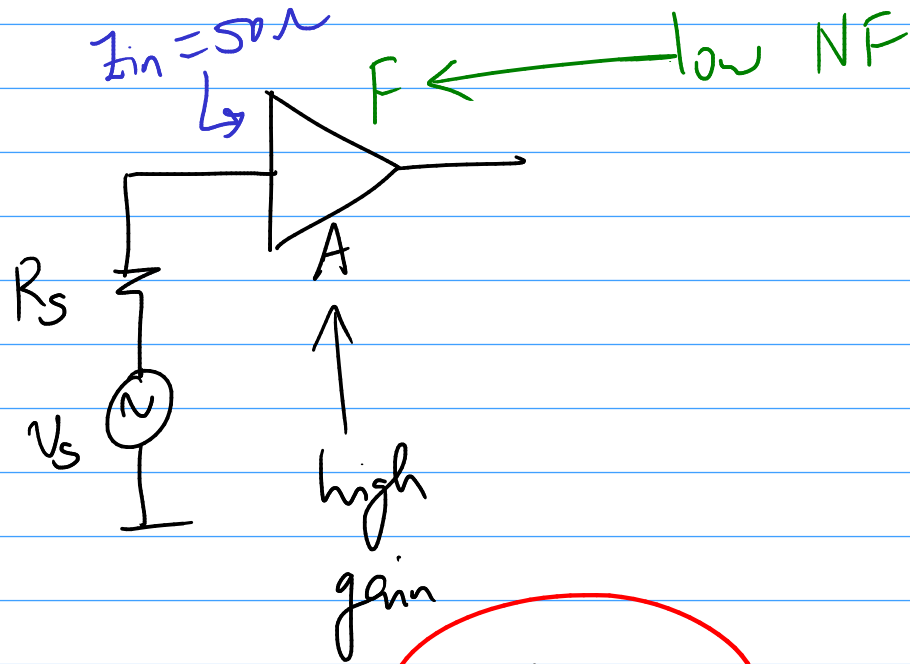


freq.  $\therefore$   $f_0 \pm \Delta f$   
 (Narrow band LNA)

- 1) CSA ✓
- 2) CGA ✓
- 3) CDA ✗
- 4) Cascode

$Z_{in} = \infty$  /  $C_{in}$   
 high gain

$Z_{in}$  is finite  
 low gain

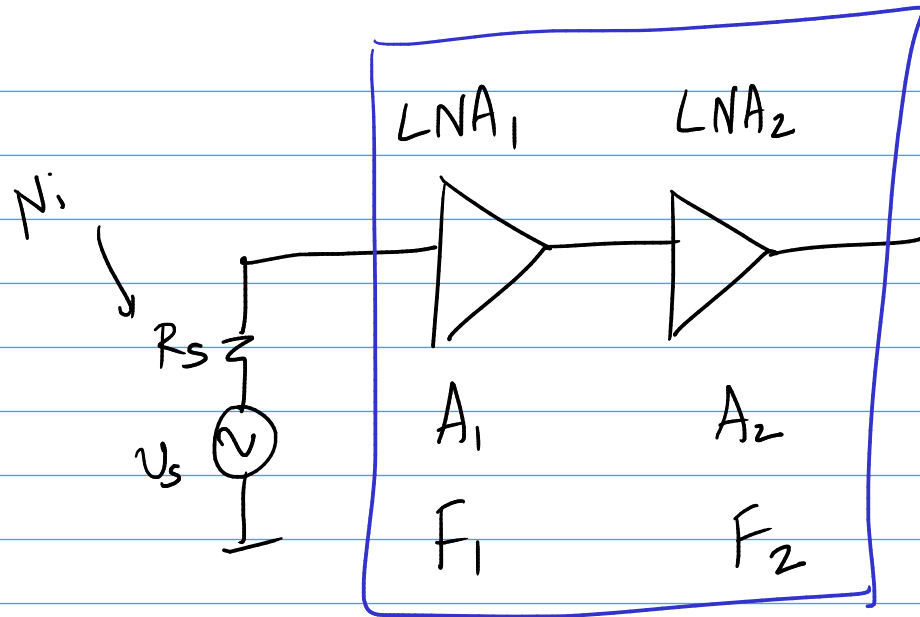

$A, F$   
 $\rightarrow A = A_1 \cdot A_2$

$F = ?$


$$F = \frac{N_{out}}{A_1 \cdot A_2 \cdot N_i}$$

$$= \frac{A_1 A_2 N_i + A_1 A_2 N_{a1} + A_2 N_{a2}}{A_1 A_2 N_i}$$

$$= 1 + \frac{N_{a1}}{N_i} + \frac{N_{a2}}{A_1 N_i}$$

$$F = 1 + (F_1 - 1) + \frac{F_2 - 1}{A_1}$$

$$F = F_1 + \frac{F_2 - 1}{A_1}$$

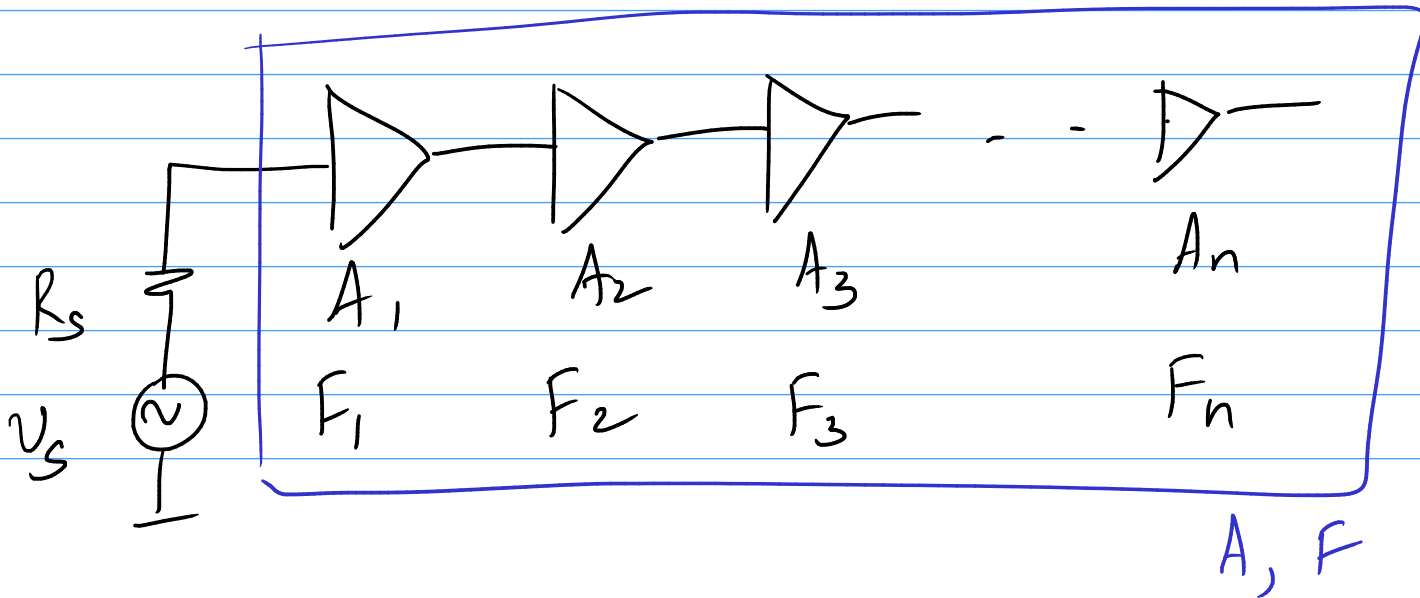


$$F = F_1 + \frac{F_2 - 1}{A_1} + \frac{F_3 - 1}{A_1 A_2} + \dots + \frac{F_n - 1}{A_1 A_2 \dots A_{n-1}}$$


FRIIS EQUATION

low NF  
LNA


High gain LNA

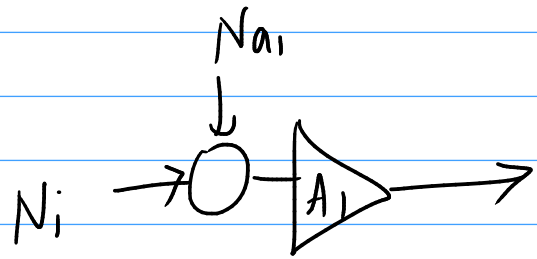

$$F_1 = 1 + \frac{N_{a1}}{N_i}$$

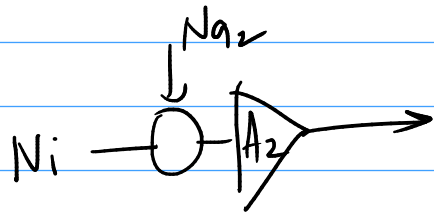


$$F_2 = 1 + \frac{N_{a2}}{N_i}$$

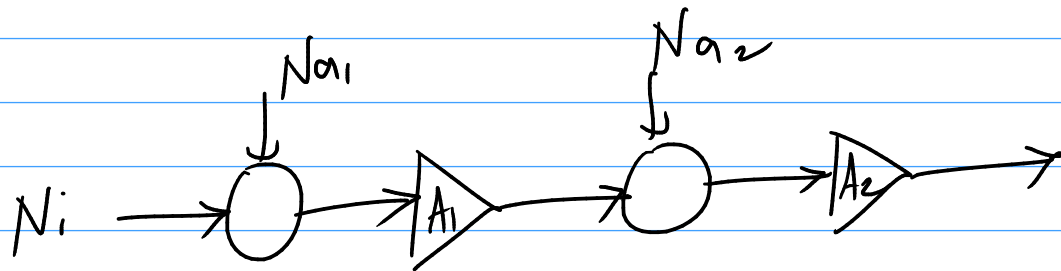

$$N_{out} = A_1 A_2 N_i + A_1 A_2 N_{a1} + A_2 N_{a2}$$

# Common-gate Amp.

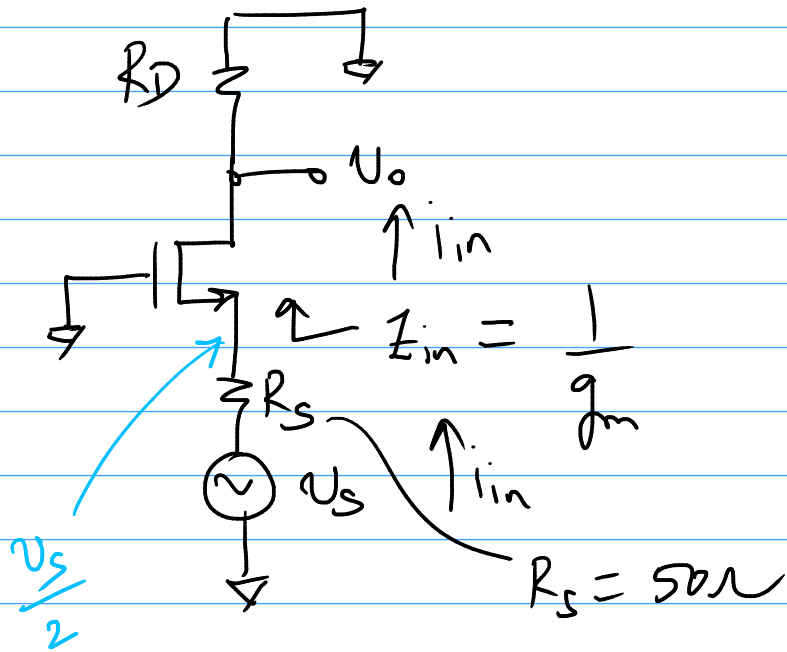


$$\frac{1}{g_m} = 50\Omega \Rightarrow g_m = 20\text{mS}$$



$$V_o = ?$$

$$i_{in} = \frac{V_s}{2R_s}$$


$$\Rightarrow \frac{V_o}{V_s} = \frac{R_D}{2R_s}$$

$$\frac{V_o}{V_s} = \frac{R_D}{100}$$

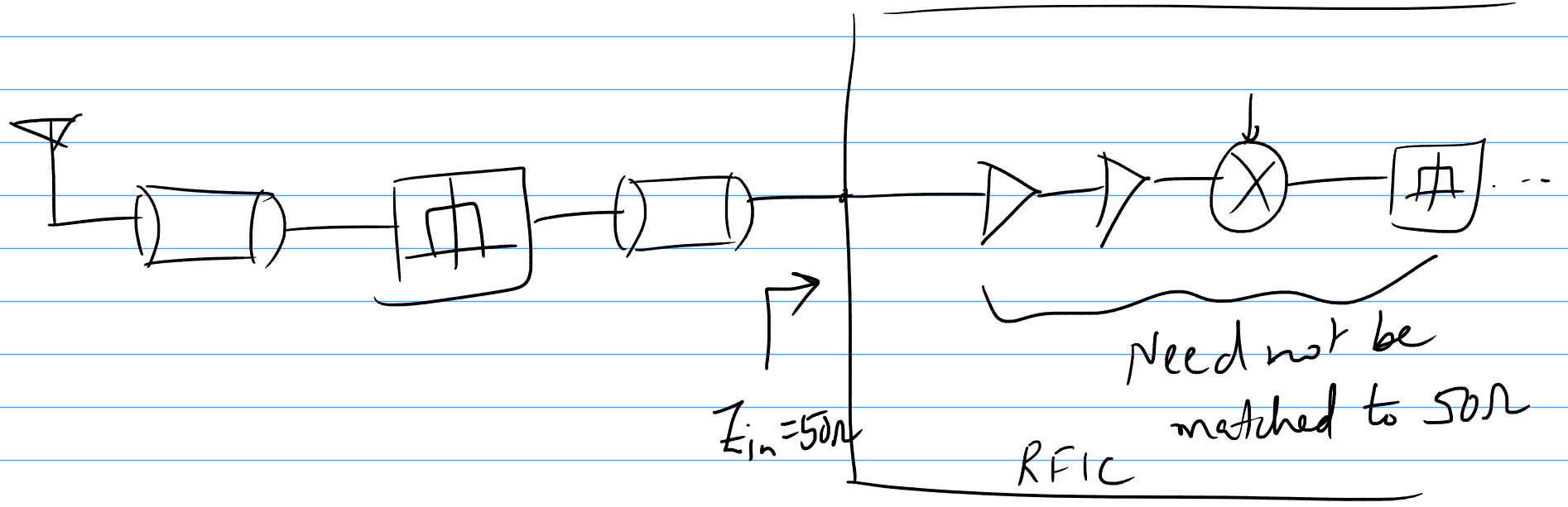


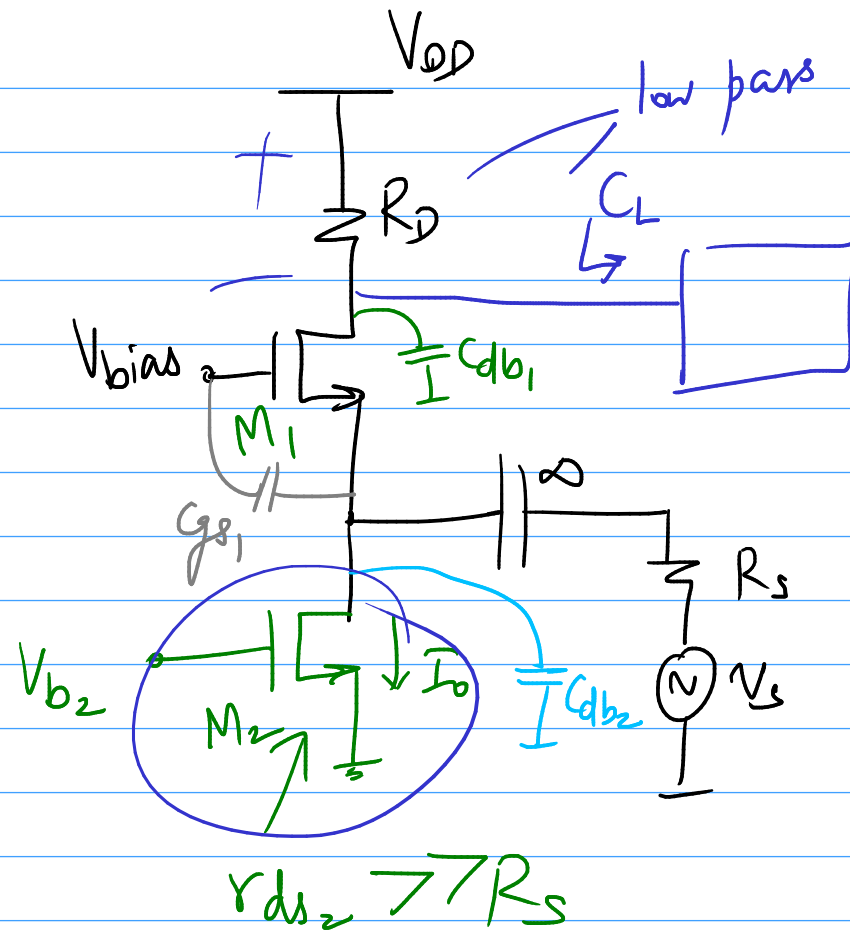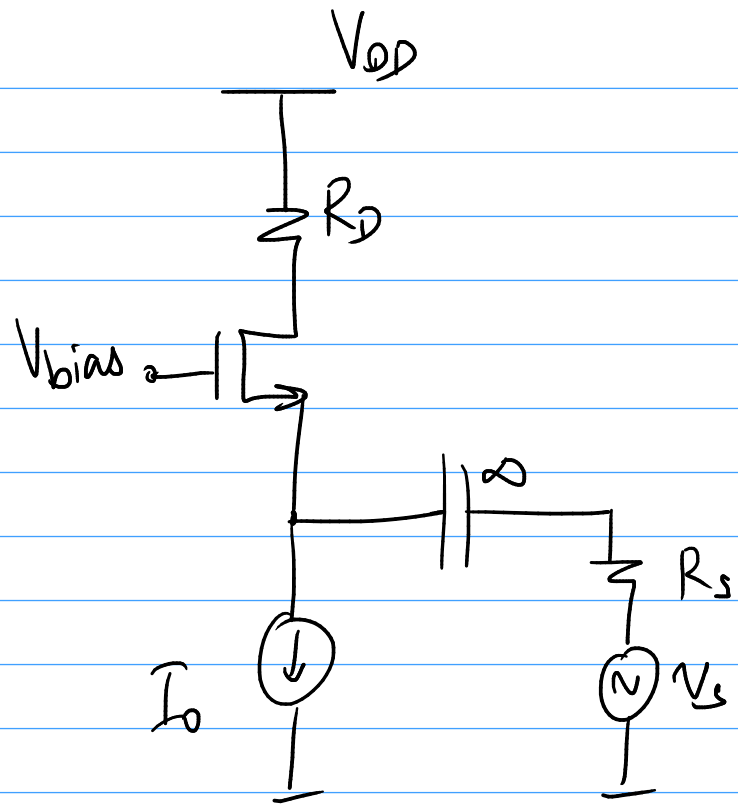

# Narrowband CGA

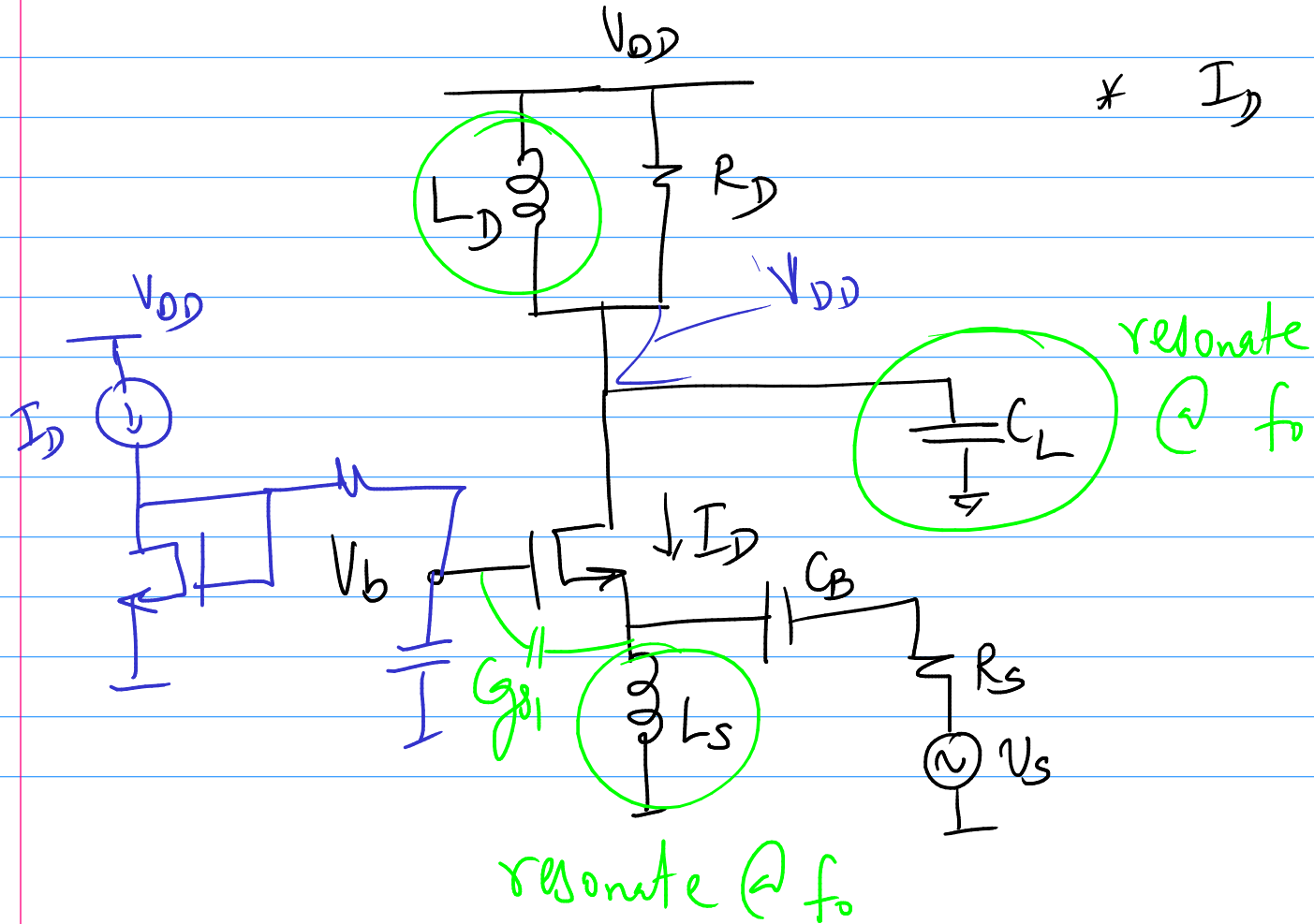

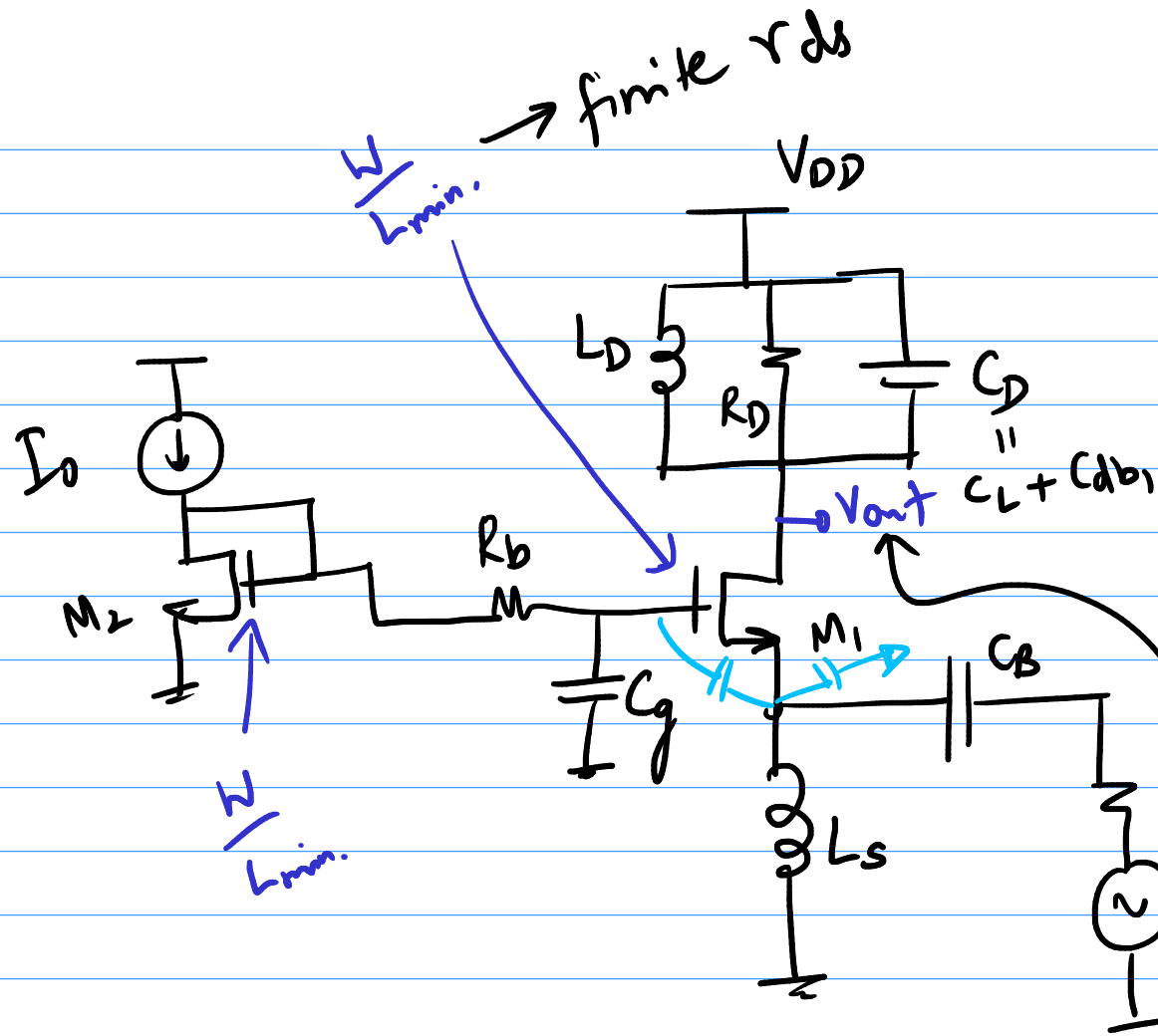\*  $I_D$  is set by  $V_b$  &  $\frac{W}{L}$






$$f_0 = \frac{1}{2\pi \sqrt{L_s \cdot (C_{gs1} + C_{sb1})}}$$

$$Z_{in}(f_0) = \frac{1}{g_{m1}} = R_s \quad (= 50 \Omega)$$

$$i_{in} = \frac{V_s}{2R_s} \quad g_{m1} = 20 \text{ mS}$$


$$f_0 = \frac{1}{2\pi \sqrt{L_D C_D}}$$

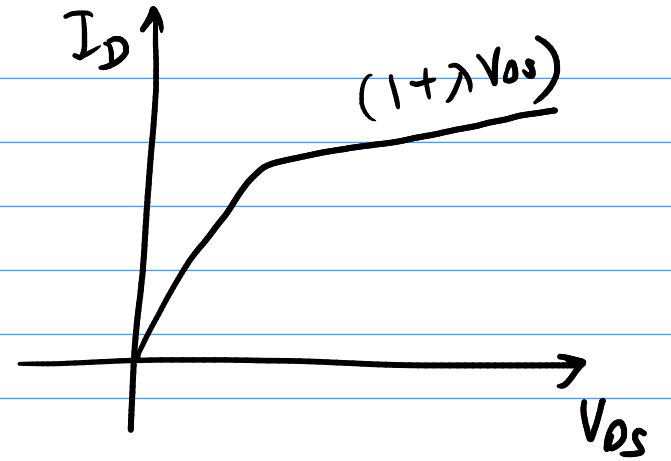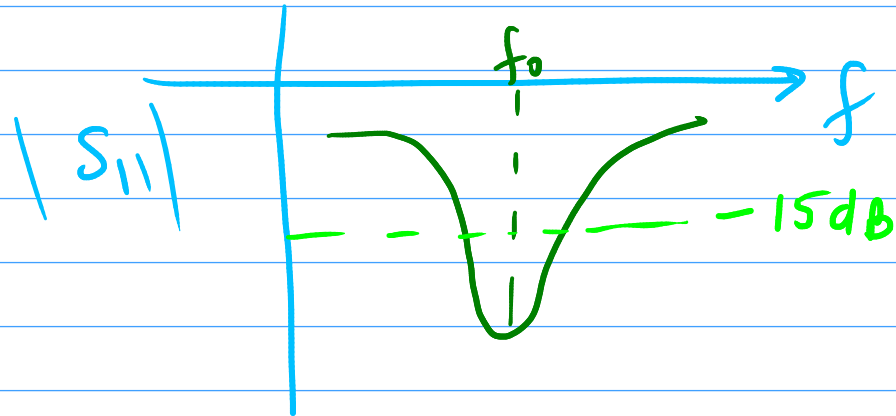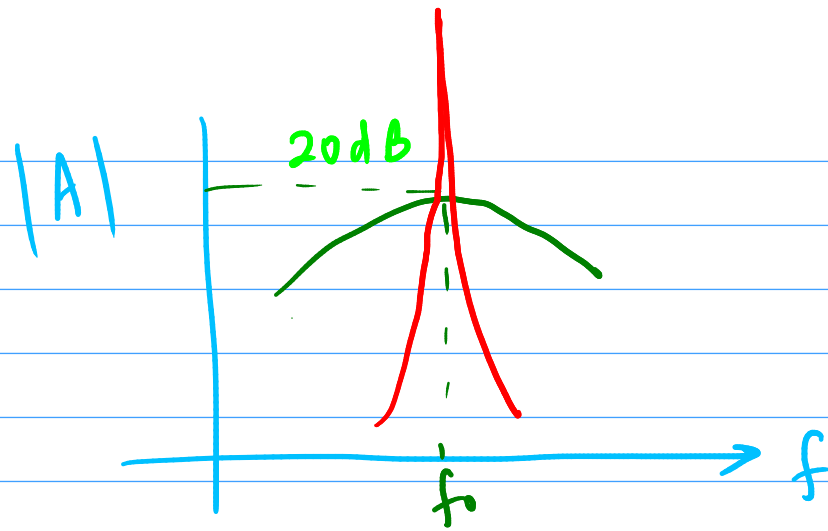


15

$$I_D = \frac{1}{2} \mu C_{ox} \frac{W}{L_{\text{actual}}} (V_{GS} - V_T)^2$$

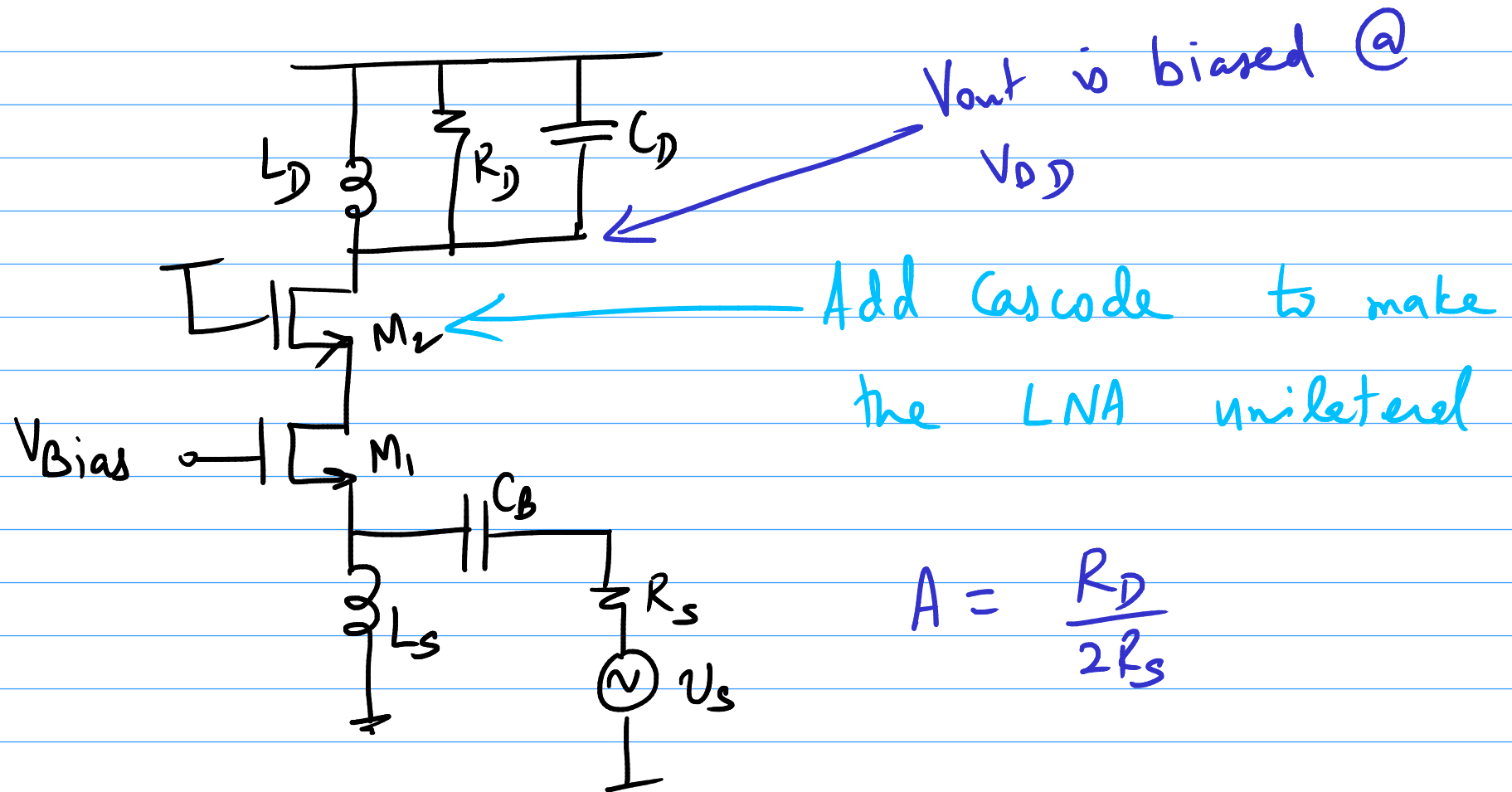$L_{\text{actual}} = L \left(1 - \frac{\Delta L}{L}\right)$







side view

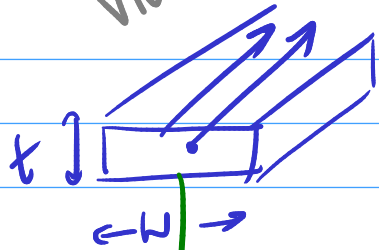


Quality factor

$V_{DD}$

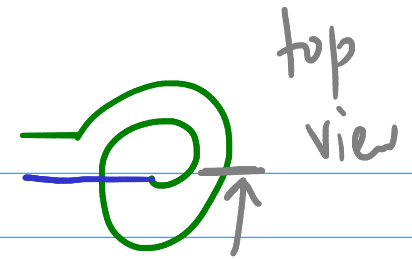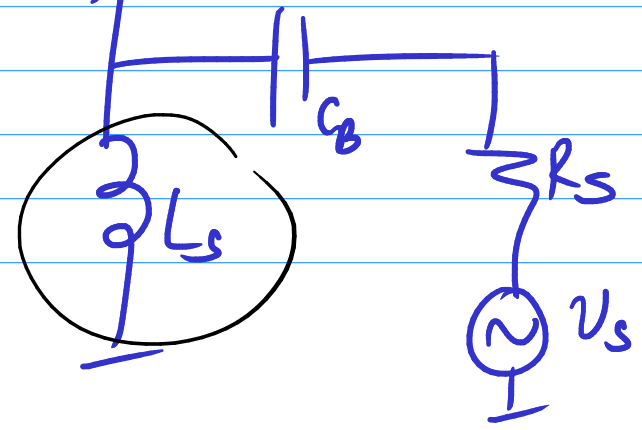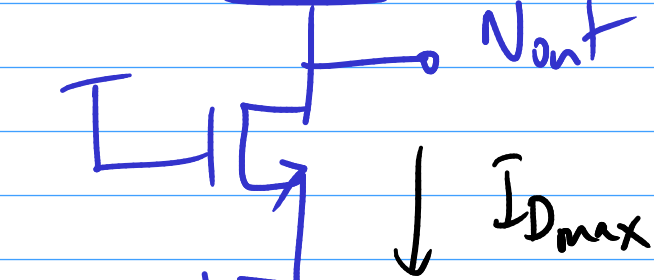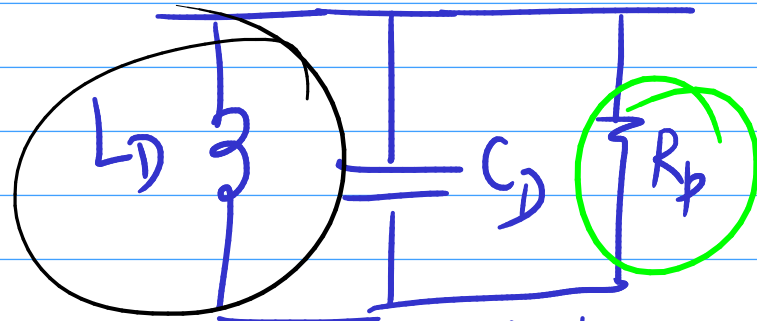

$A = \infty$  X

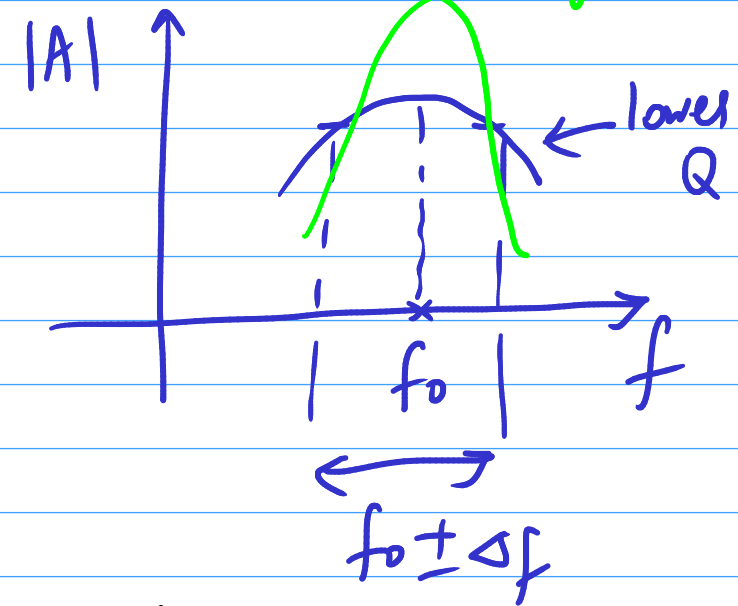

$$A = \frac{R_p}{2R_s}$$


1) 
$$W_T = \frac{g_m}{g_s} \begin{matrix} \rightarrow \propto \sqrt{W} \\ \rightarrow \propto W \end{matrix} \left. \vphantom{\frac{g_m}{g_s}} \right\} W_T \downarrow$$

2) Device into moderate inversion

3)  $L_D, L_S \downarrow \leftarrow$  layout parasitics  
EM sim. limits

# NF of CG LNA



@  $f_0$

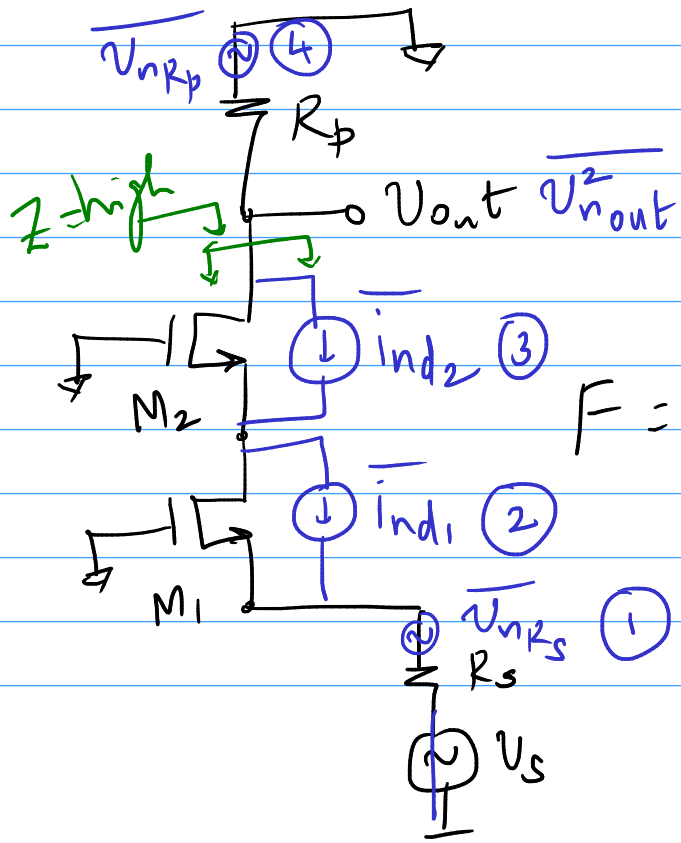

$$|A| = \frac{R_p}{2R_s}$$

$$Z_{in} = \frac{1}{g_m} = R_s$$
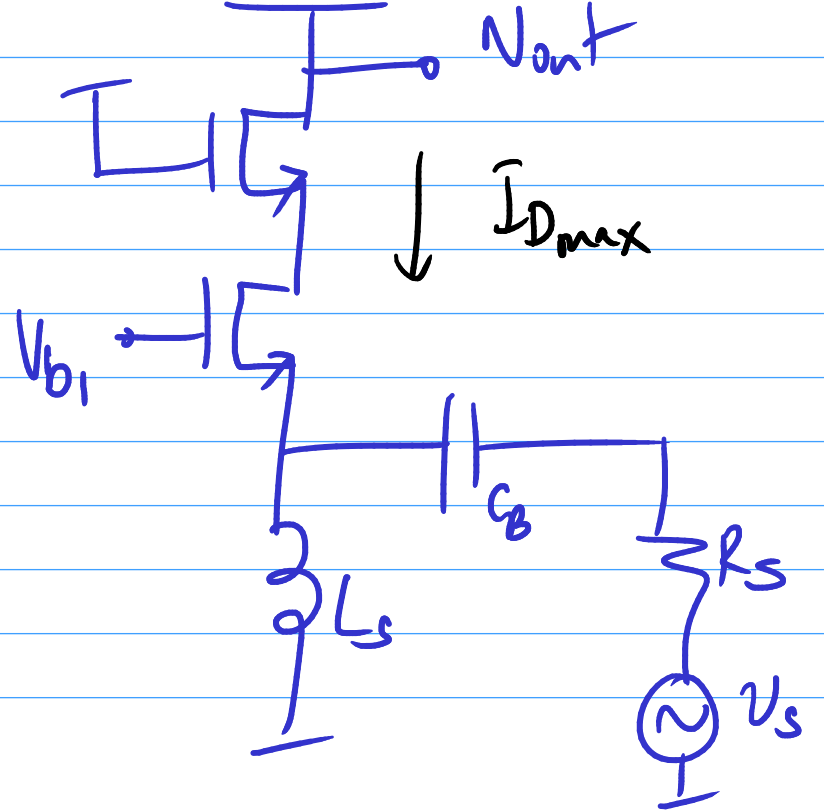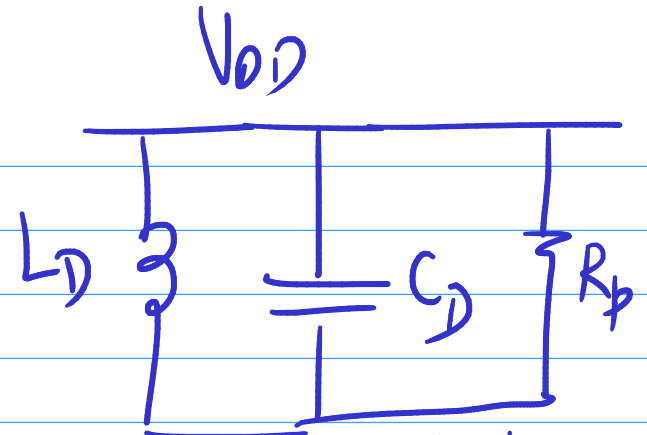
$$F = \frac{\text{Total } N_{out}}{N_{out}(R_s)}$$





$$1) \overline{V_{out,1}^2} \text{ due to } R_s = \frac{R_p^2}{4R_s^2} \cdot \overline{V_{nr,s}^2}$$

①


$$2) \overline{V_{out,2}^2} \text{ due to } M_1 = \overline{ind_1^2} \cdot \frac{R_p^2}{4}$$

②

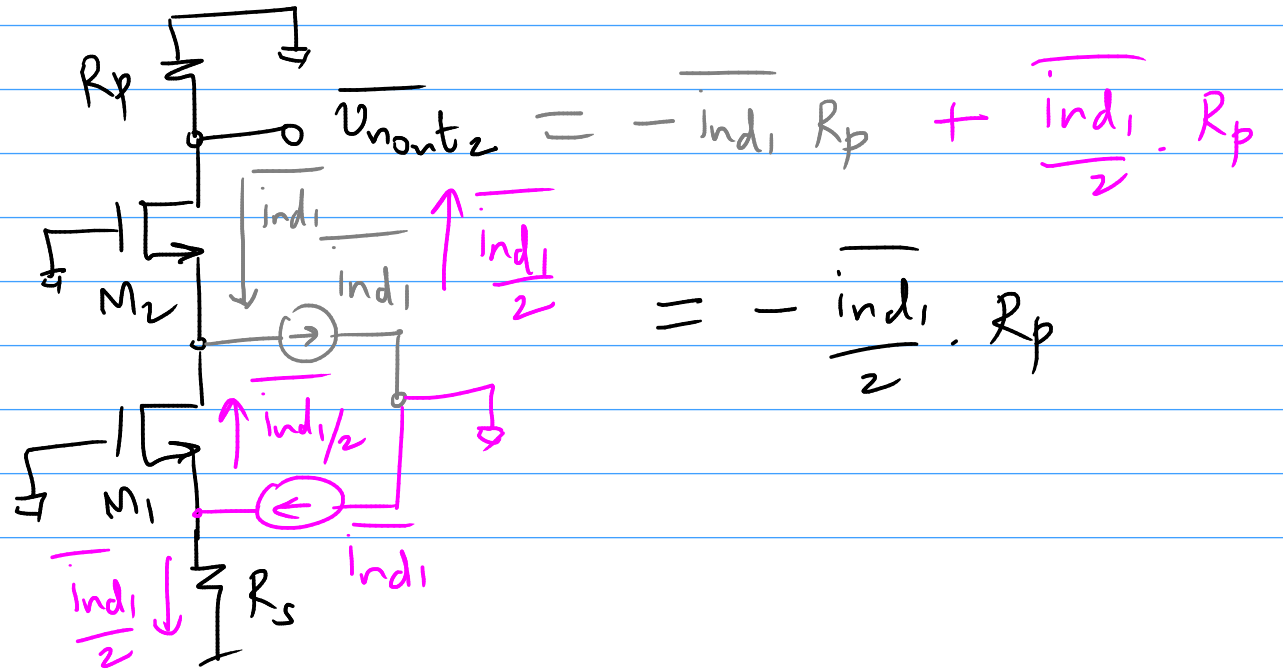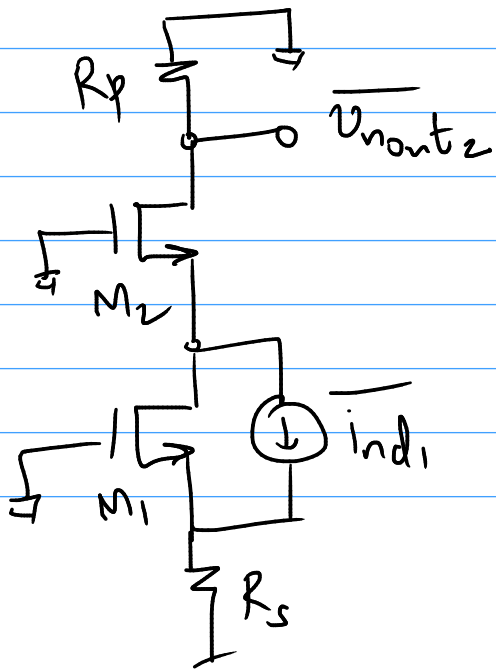

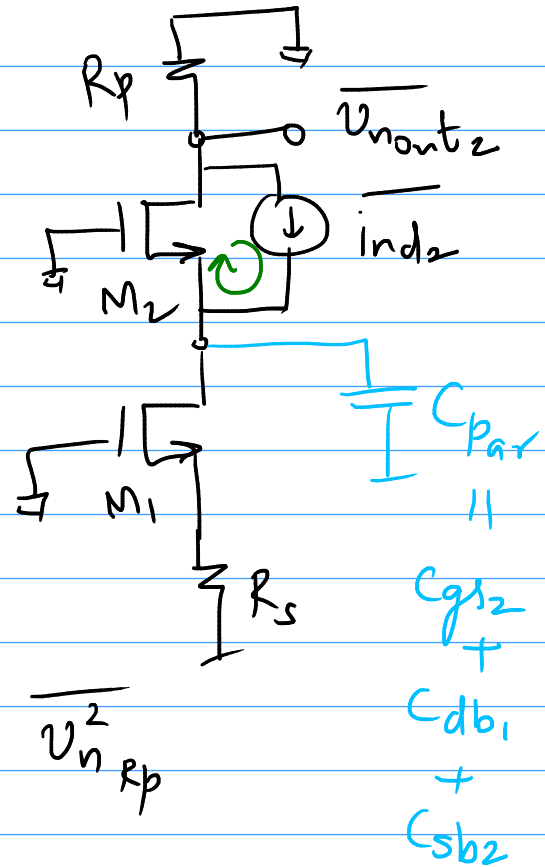
3)  $\overline{V_{nout3}^2}$  due to  $M_2 \approx 0$   
 (3)

exceptions: 1)  $r_{ds1,2}$  too low  
 2)  $C_{par}$



4)  $\overline{V_{nout4}^2}$  due to  $R_p = \overline{V_{nRp}^2}$   
 (4)

HW  
 ind2 with  $C_{par}$

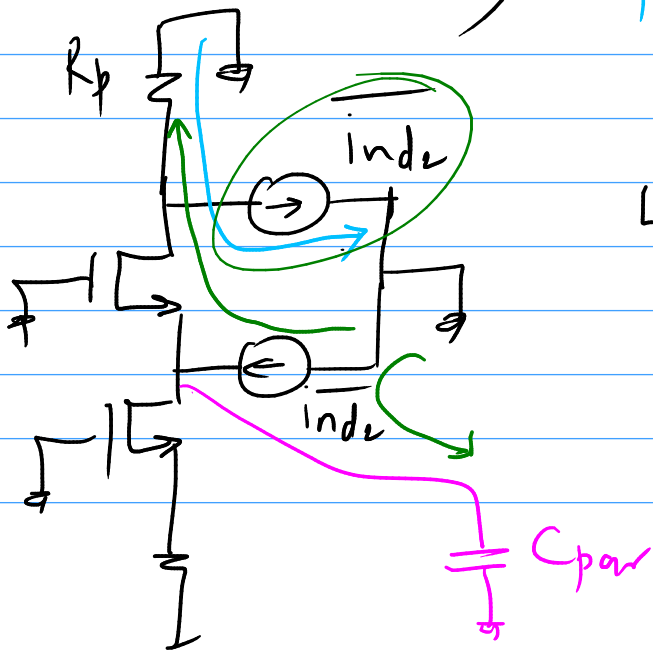

Noise Factor

$$F = 1 + \frac{\overline{i_{nd,1}^2} \cdot \frac{R_p^2}{4} + \overline{V_{n,Rp}^2}}{\frac{R_p^2}{4R_s^2} \cdot \overline{V_{n,Rs}^2}}$$

$$\overline{V_{n,Rs}^2} = 4kT R_s \Delta f$$

$$\overline{V_{n,Rp}^2} = 4kT R_p \Delta f$$

$$\overline{i_{nd,1}^2} = 4kT \alpha^2 g_{m,1} \Delta f$$

$$F = 1 + \frac{\cancel{4kT} \gamma g_{m1} \cdot \frac{R_p^2}{4} \cancel{\Delta f} + \cancel{4kT} R_p \cancel{\Delta f}}{\dots}$$

$$\frac{R_p^2}{4R_s^2} \times \cancel{4kT} R_s \cancel{\Delta f}$$

$$= 1 + \gamma \underbrace{g_{m1} R_s}_{=1} + \frac{4R_s}{R_p}$$

$$F = 1 + \gamma + \frac{4R_s}{R_p}$$

Noise Factor of CGLNA

Upper limit :  $R_p \gg R_s$


$$\gamma = \frac{2}{3}$$

$$F = 1 + \frac{2}{3} = 1.67$$

$$NF = 10 \log_{10}(F) = 2.2 \text{ dB}$$

Upper limit  
for CCLNA



# CS LNA

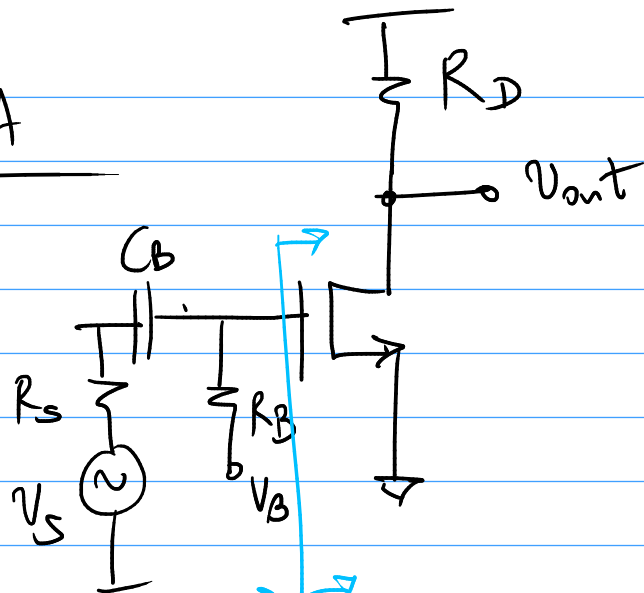


$$Z_{in} = \frac{1}{j\omega C_b}$$

either  $R_b = 50\Omega$

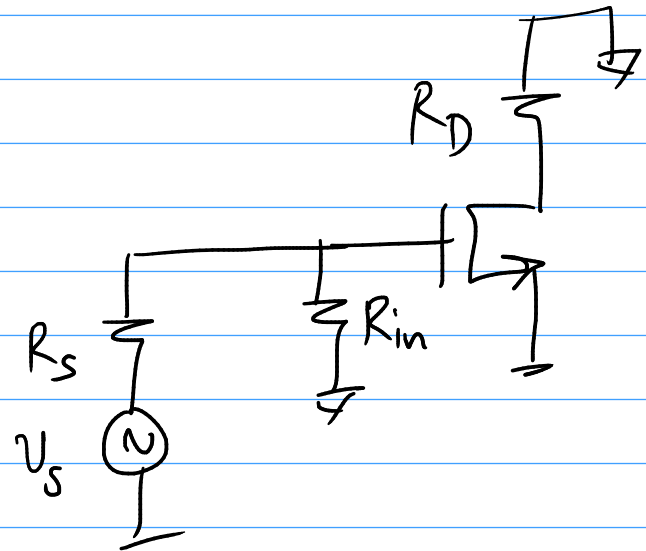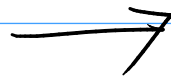(or) add  $R_{in} = 50\Omega$  in shunt across gate


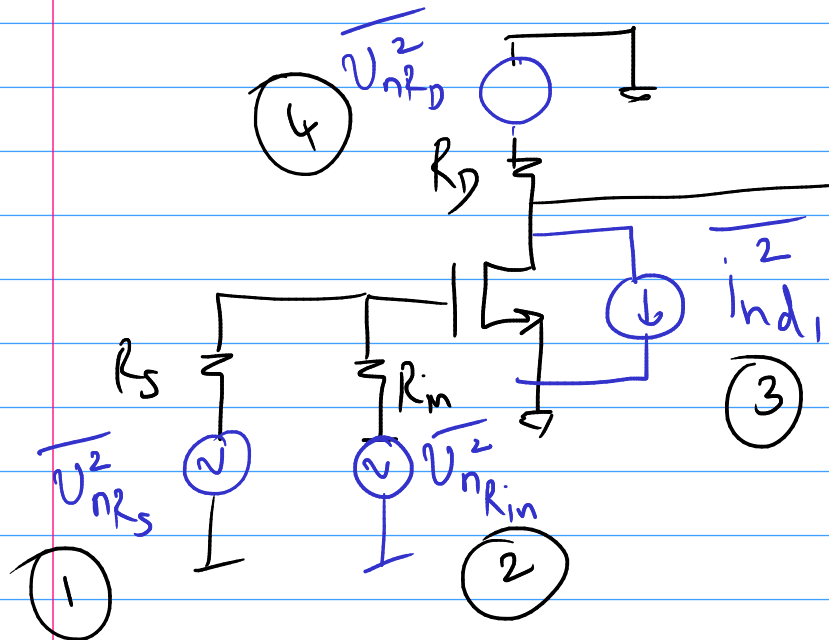
$$A = -g_m R_D \times \frac{R_{in}}{R_s + R_{in}}$$
$$= -\frac{1}{2} g_m R_D$$



$U_{n_{out}}^2 = ?$      $F = ?$

①  $\Rightarrow U_{n_{out1}}^2 = \frac{1}{4} g_m^2 R_D^2 \cdot U_{nR_S}^2$

②  $\Rightarrow U_{n_{out2}}^2 = \frac{1}{4} g_m^2 R_D^2 \cdot U_{nR_{in}}^2$

③  $\Rightarrow U_{n_{out3}}^2 = i_{nd1}^2 \cdot R_D^2$

④  $\Rightarrow U_{n_{out4}}^2 = U_{nR_D}^2$


$$F = 1 + \frac{\frac{1}{4} g_m^2 R_D^2 \cdot \overline{U_{n,fin}^2} + \overline{I_{n,D_1}^2} R_D^2 + \overline{U_n^2} R_D}{\frac{1}{4} g_m^2 R_D^2 \cdot \overline{U_{n,R_s}^2}}$$

$$F = 2 + \frac{\quad}{\quad}$$

→ min NF = 3 dB




$$F = 2 + \frac{\cancel{4kT} \cancel{g_m} \cancel{R_D}^2}{\cancel{\frac{1}{4}} \cancel{g_m}^2 \cancel{R_D}^2 \cdot \cancel{4kT} R_s} + \frac{\cancel{4kT} \cancel{R_D}}{\cancel{\frac{1}{4}} \cancel{g_m}^2 \cancel{R_D}^2 \cdot \cancel{4kT} R_s}$$
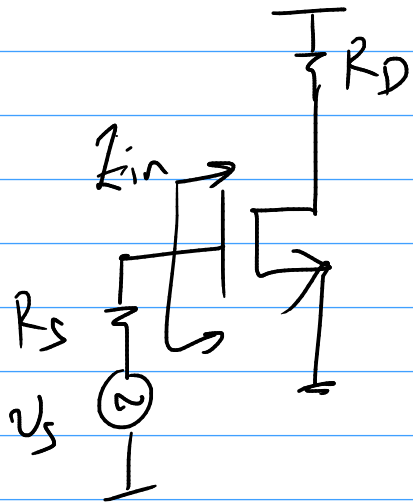
$$F = 2 + \frac{4\gamma}{g_m R_s} + \frac{4}{g_m^2 R_D R_s}$$



high gain ✓  
low  $\bar{e}_n$  ✓
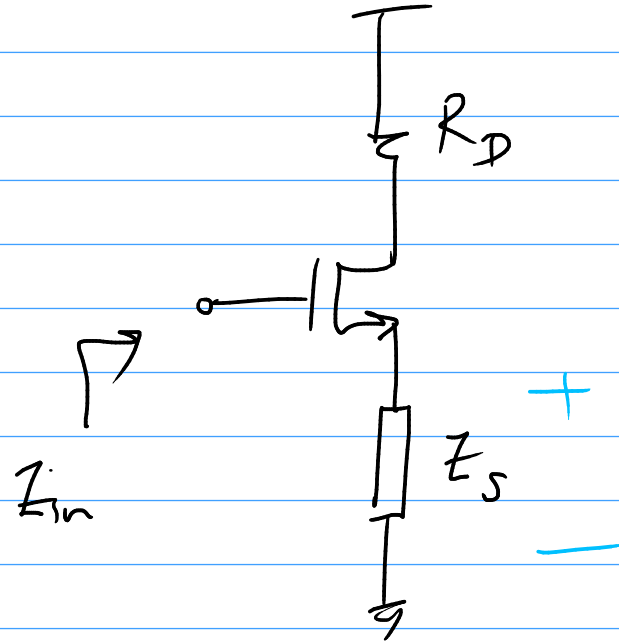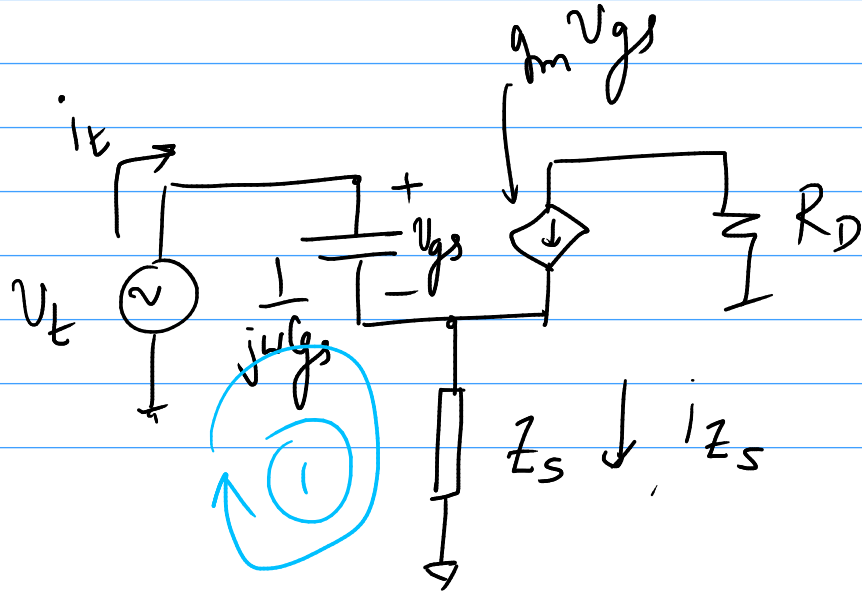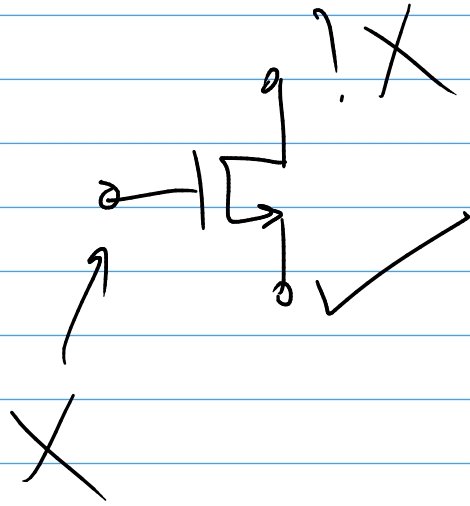
$$Z_{in} = \frac{1}{j\omega C_{gs}} \quad \times$$




$$Z_{in} = \frac{v_t}{i_t}$$

KCL @ Source of  $M_1$

$$i_{Z_s} = i_t + g_m v_{gs}$$

$$v_{gs} = i_t \cdot \frac{1}{j\omega C_{gs}}$$

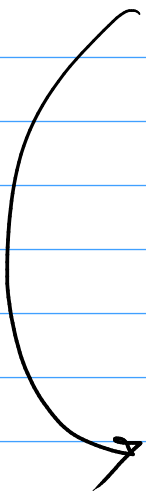
$$\frac{v_t - v_{gs}}{Z_s} = i_t + g_m v_{gs}$$

$$v_t - v_{gs} = Z_s i_t + g_m Z_s \cdot v_{gs}$$

KVL @ Loop ①

$$v_t = v_{gs} + i_{Z_s} \cdot Z_s$$

$$V_t = Z_s i_t + v_{gs} (1 + g_m Z_s)$$

$$= Z_s i_t + (1 + g_m Z_s) \cdot \frac{i_t}{j\omega C_{gs}}$$

$$\frac{V_t}{i_t} = Z_{in} = Z_s + \frac{1}{j\omega C_{gs}} + \frac{g_m}{j\omega C_{gs}} \cdot Z_s$$


---

---

Case 1  $Z_S = R$

$$Z_{in} = R + \frac{1}{j\omega C_{gs}} + \frac{g_m R}{j\omega C_{gs}}$$

*noise*

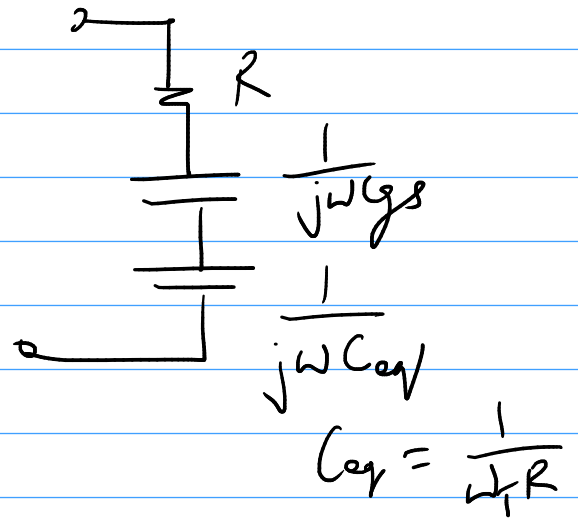

Case 2  $Z_S = \frac{1}{j\omega C}$


$$Z_{in} = \frac{1}{j\omega C} + \frac{1}{j\omega C_{gs}} + \frac{-g_m}{\omega^2 C_{gs} \cdot C}$$

← -ve resistance

✗ instability

case 3  $Z_s = j\omega L_s$

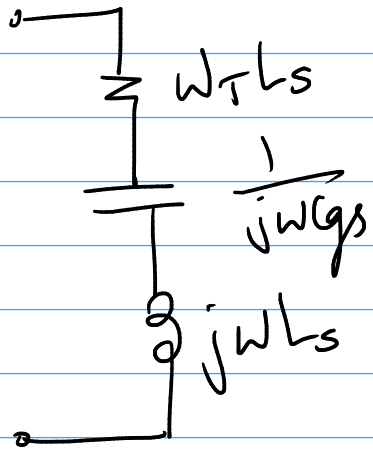
$$Z_{in} = j\omega L_s + \frac{1}{j\omega C_{gs}} + \frac{g_m \cdot j\omega L_s}{j\omega C_{gs}}$$



resonance  $\neq f_0$

$$\frac{g_m}{C_{gs}} \cdot L_s = \omega_T L_s \quad \checkmark$$
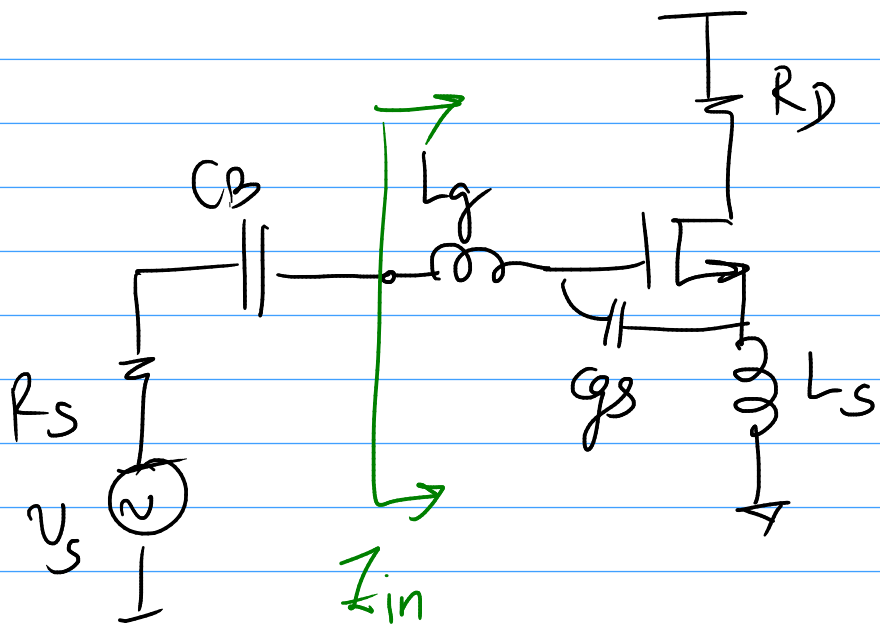
$$Z_{in} = j\omega L_s + \frac{1}{j\omega C_{gs}} + \underbrace{\omega_T L_s}_{\omega R_s}$$




$$Z_{in} = j\omega L_g + j\omega L_s + \frac{1}{j\omega C_{gs}}$$

$$+ \omega_T L_s$$


$$f_0 = \frac{1}{2\pi \sqrt{(L_s + L_g) C_{gs}}}$$

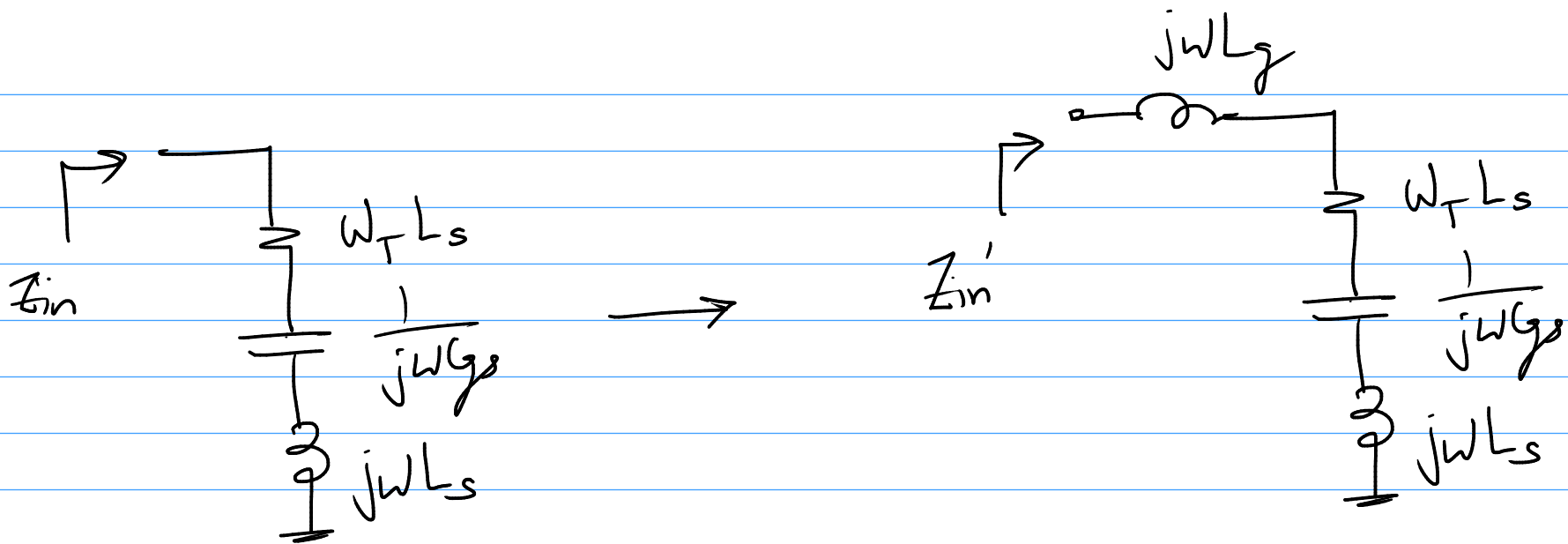$\downarrow \omega_T \rightarrow \uparrow L$ ; add  $C \parallel C_{gs}$ ;






$$Z_{in}'(\omega_0) = \omega_T \cdot L_s = R_s$$
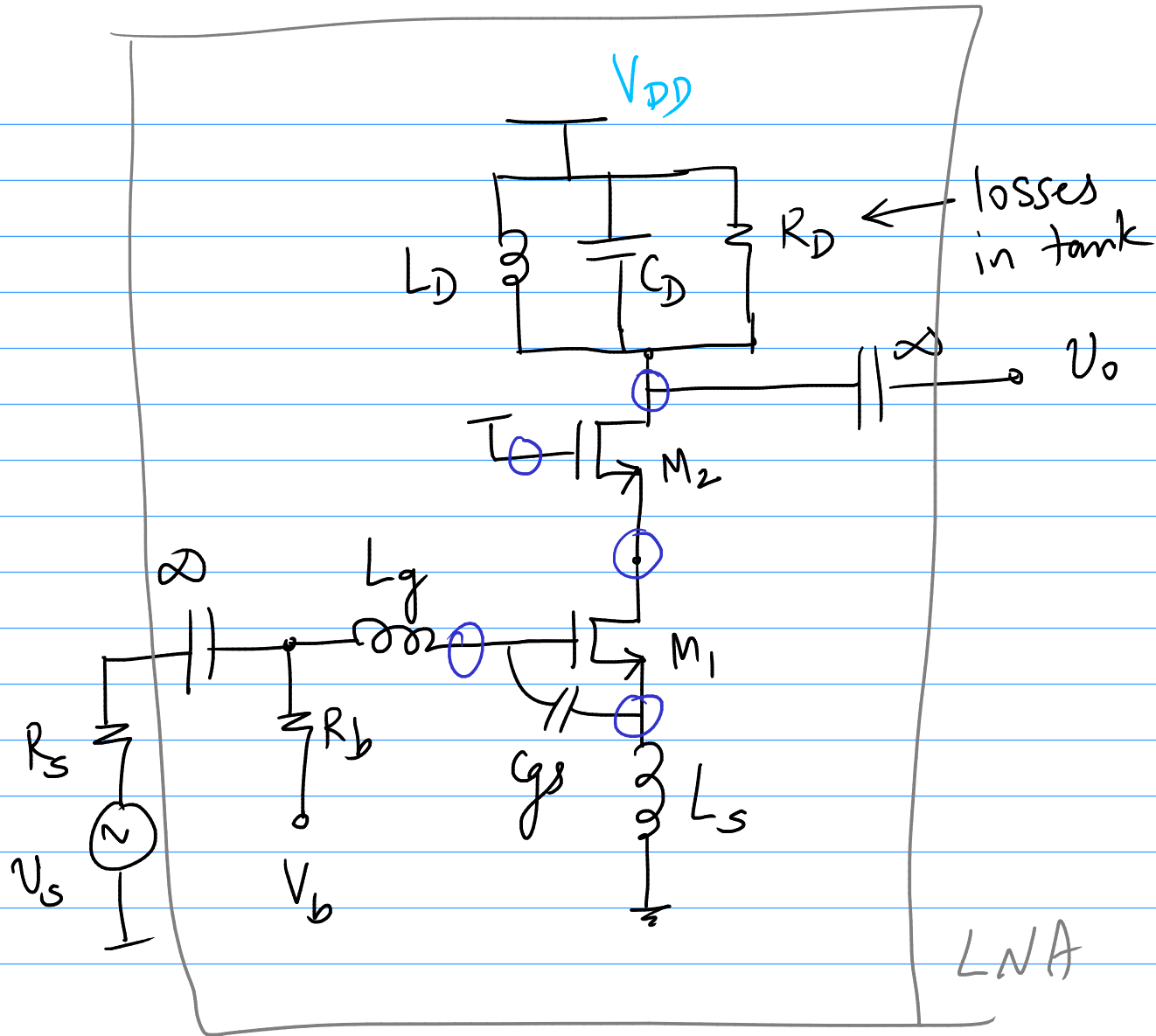
$$\omega_0 = \frac{1}{\sqrt{C_g(L_g + L_s)}} \quad \leftarrow \text{desired freq. of operation}$$



LNA

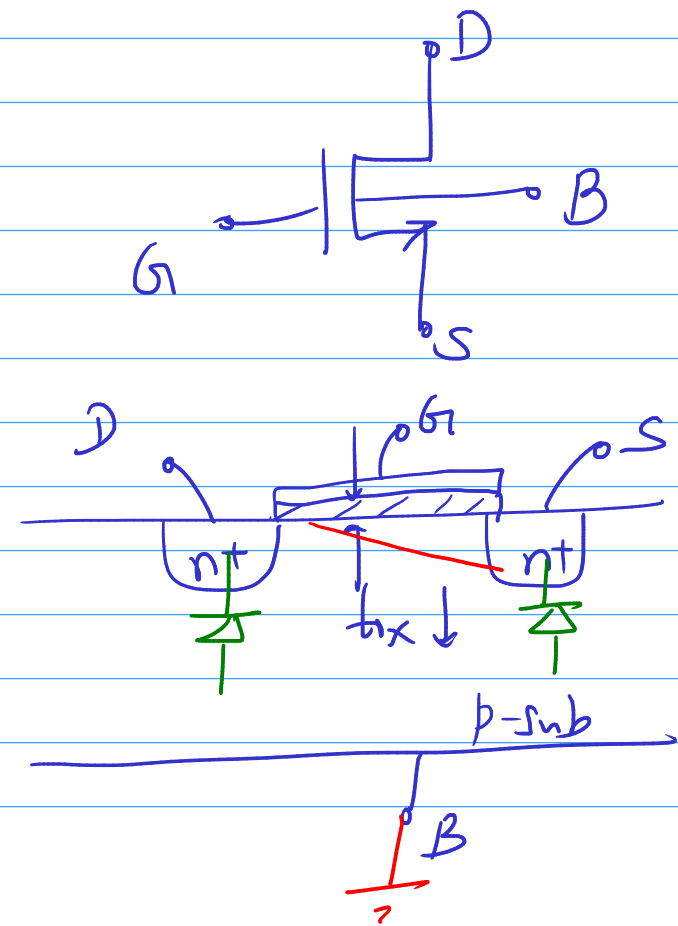


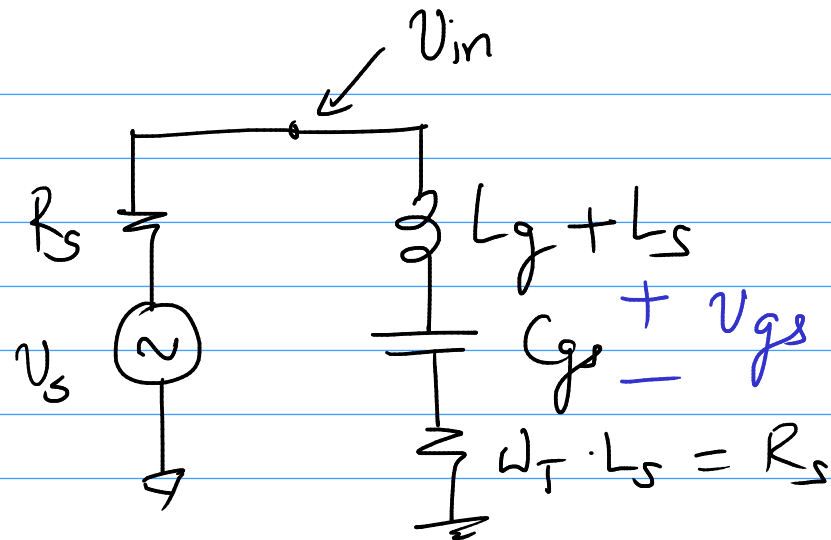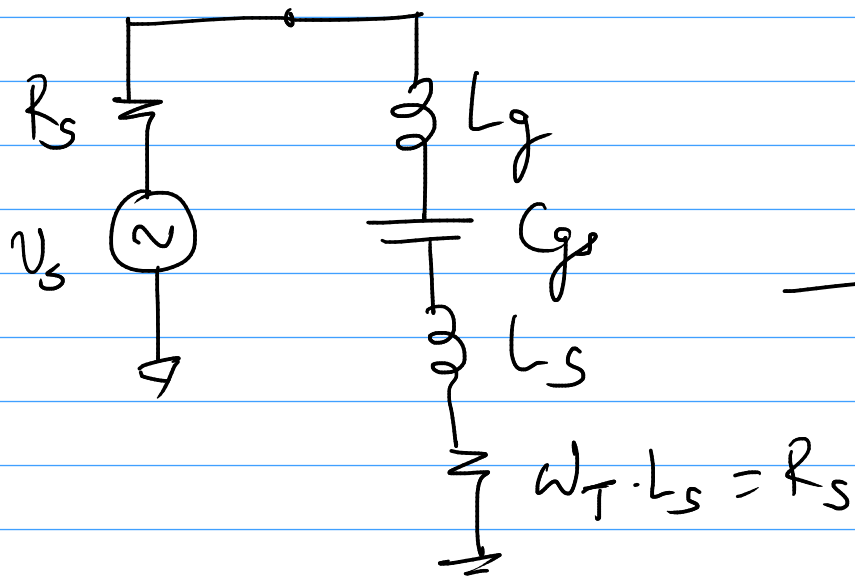

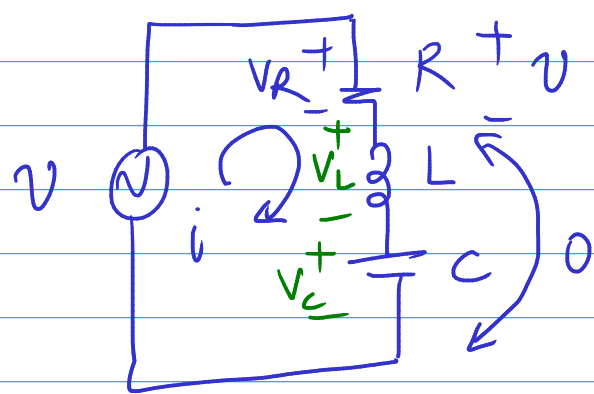(a)  $\omega_0 : v_{in} = \frac{v_s}{2}$


$$V_L = \frac{v}{R} \cdot j\omega L$$

$$V_C = \frac{v}{R} \cdot \frac{1}{j\omega C} = \frac{v}{R} \cdot \frac{-j}{\omega C}$$





$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$i = \frac{v}{R}$$

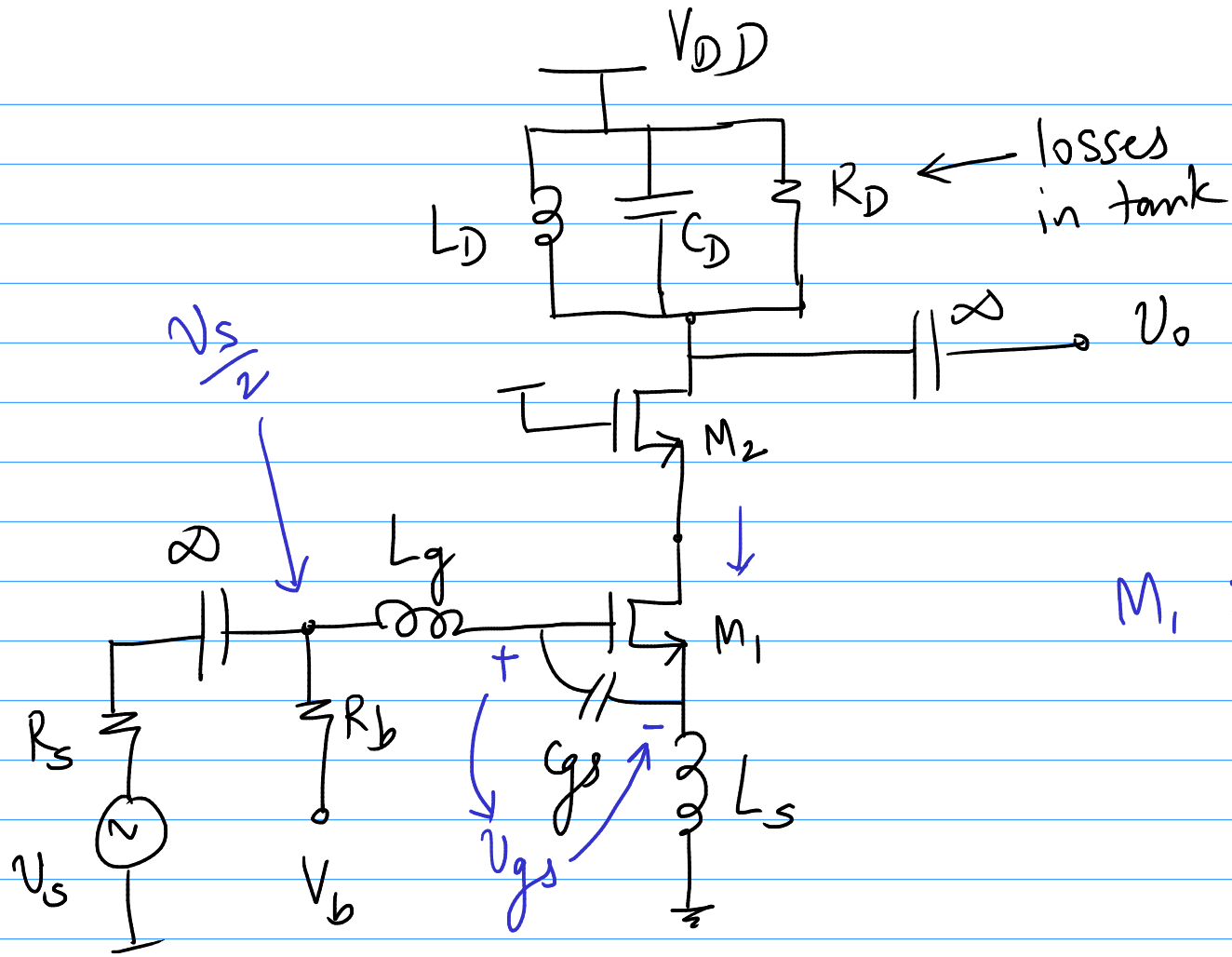

$M_1$  :

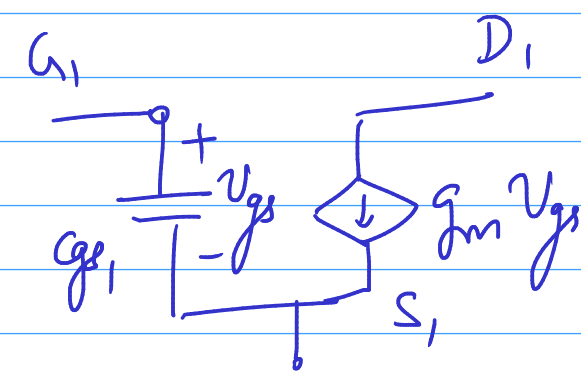

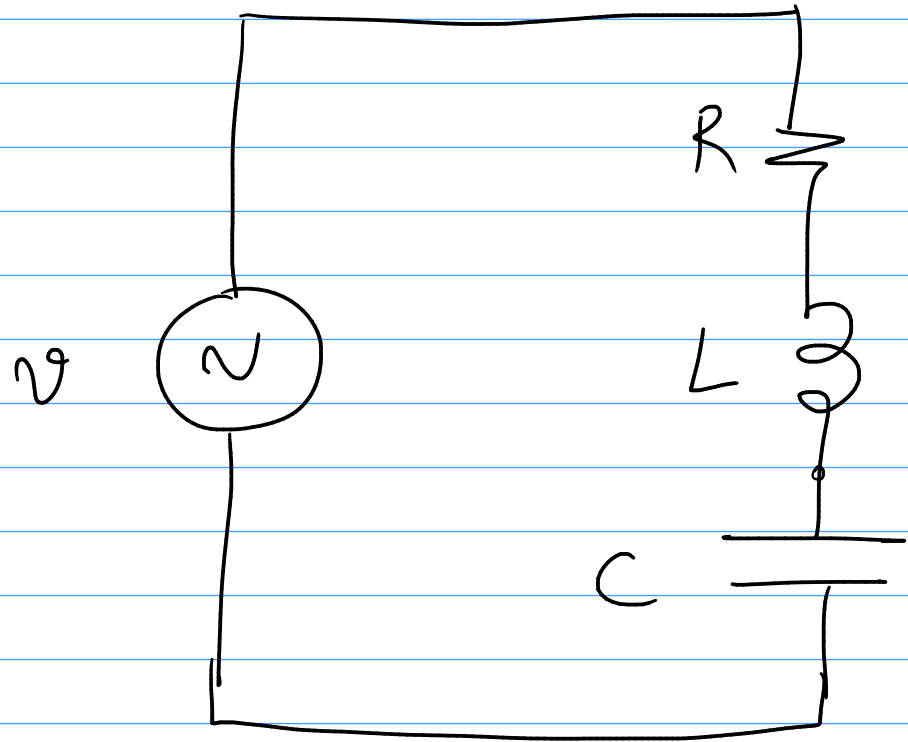


$$+ \quad v_R = v$$

$$+ \quad |v_L| = v \cdot \frac{\omega L}{R}$$


$$+ \quad |v_C| = v \cdot \frac{1}{\omega C R}$$

$$Q = \frac{\omega L}{R} = \frac{1}{\omega C R}$$

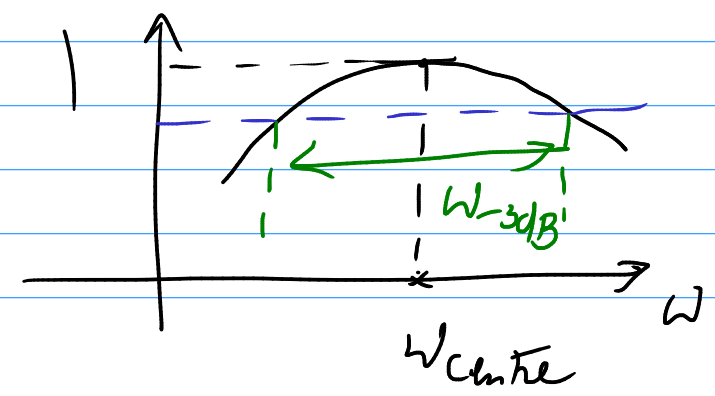1)  $Q = \frac{\omega_{\text{centre}}}{\omega_{-3\text{dB}}}$   
 quality factor



2)

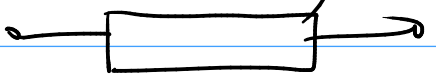
$$Z(\omega) = R + jX$$

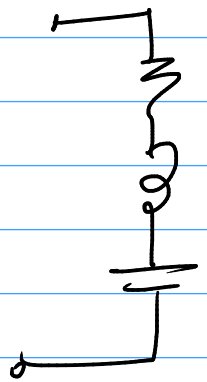
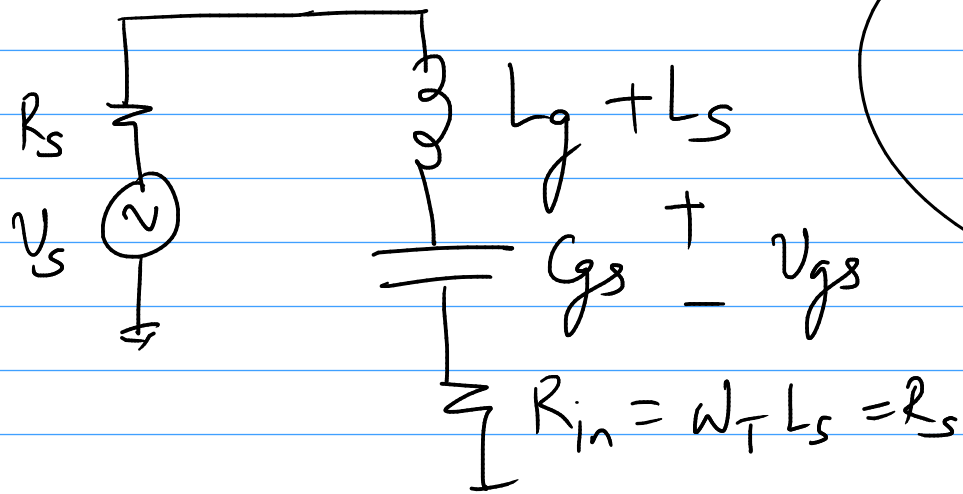
$$Q = 2\pi \cdot \frac{\text{peak energy stored}}{\text{energy dissipated/cycle}}$$

R L  
series

3)

$$Q = \frac{\text{Im}(Z)}{\text{Re}(Z)}$$






$$Q = \frac{1}{\omega_0 C_{gs} (2R_s)}$$

$$V_{gs} = Q \cdot V_s = \frac{V_s}{2\omega_0 C_{gs} R_s} \quad \text{can be } > V_s$$

if  $Q > 1$

→ low NF possible


$$\omega_0 = \frac{1}{\sqrt{L_D C_D}}$$

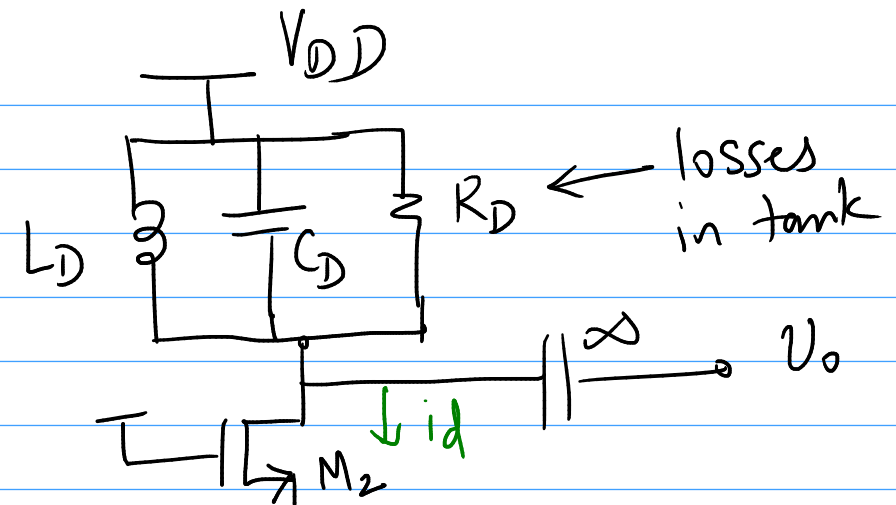

$$i_d = g_{m1} \cdot v_{gs} = g_{m1} \cdot Q_{in} \cdot v_s$$

$$V_o = -g_{m1} R_D \cdot Q_{in} \cdot v_s$$
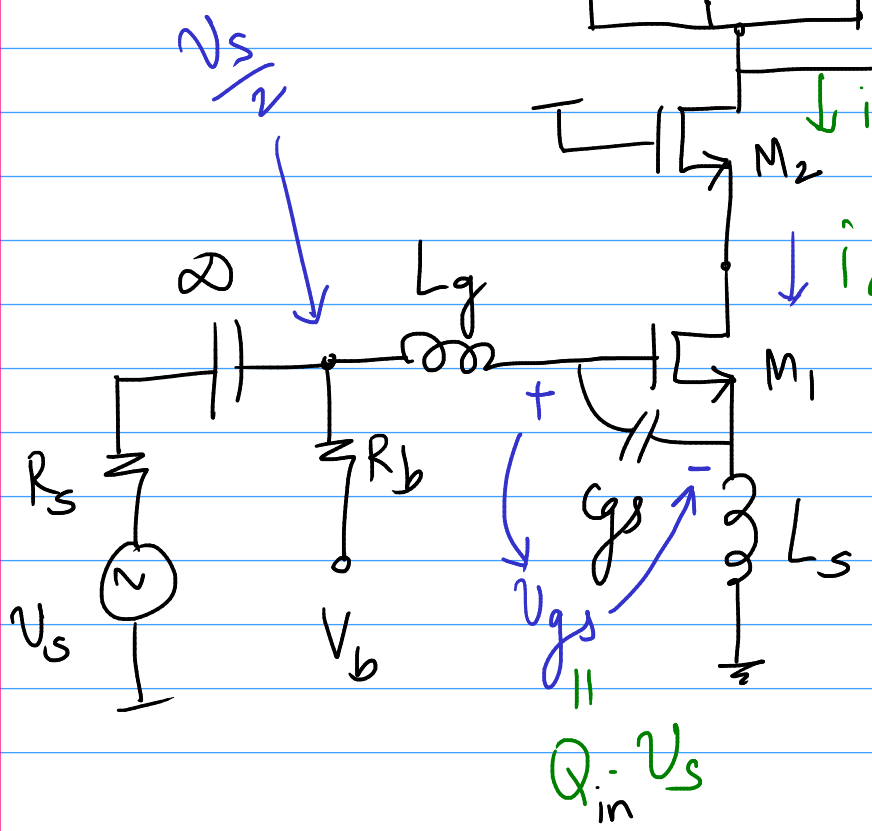
$$\frac{V_o}{v_s} = -g_{m1} R_D \cdot Q_{in}$$




$$\frac{V_o}{V_s} = -g_{m1} R_D \cdot Q$$

$$\frac{V_o}{V_s} = \frac{-g_{m1} R_D}{2 \omega_0 C_{gs} R_s}$$

$$\frac{g_{m1}}{C_{gs}} = \omega_T$$

$$\frac{V_o}{V_s} = -\frac{1}{2} \frac{\omega_T}{\omega_0} \cdot \frac{R_D}{R_s}$$

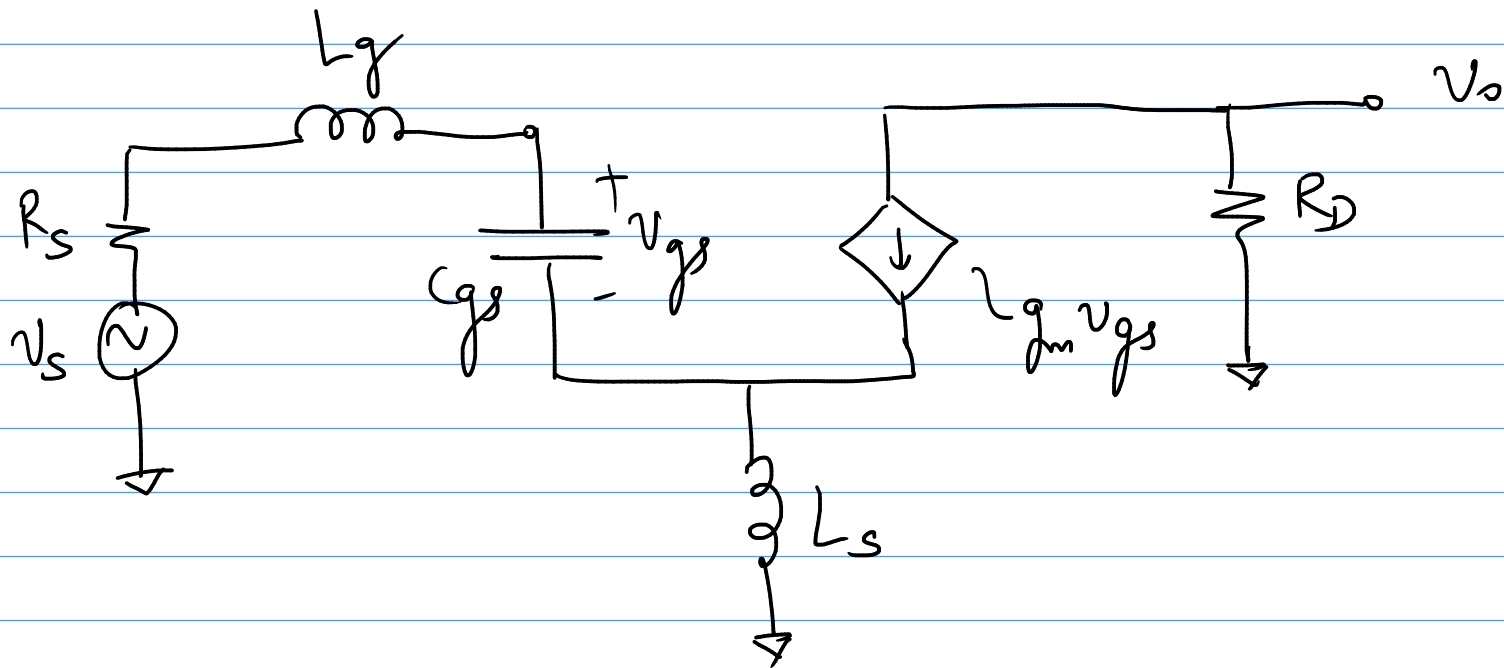
$$G_{m, LNA} = \frac{1}{2 R_s} \cdot \frac{\omega_T}{\omega_0}$$




\* Ignore effect of cascode for gain & noise  
 ↳ only for reverse isolation

Noise Figure [Section 5.3.4 Razavi's textbook]
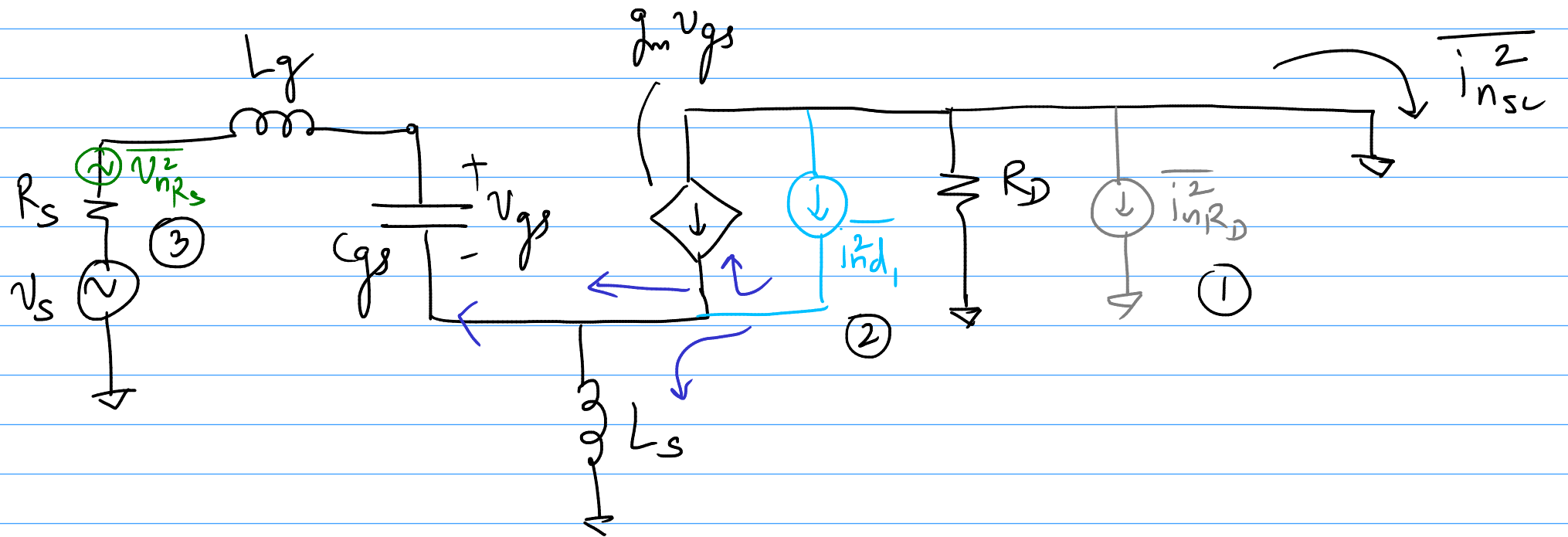
$$F = \frac{\text{Total } N_{out}}{N_{out}(R_s)}$$


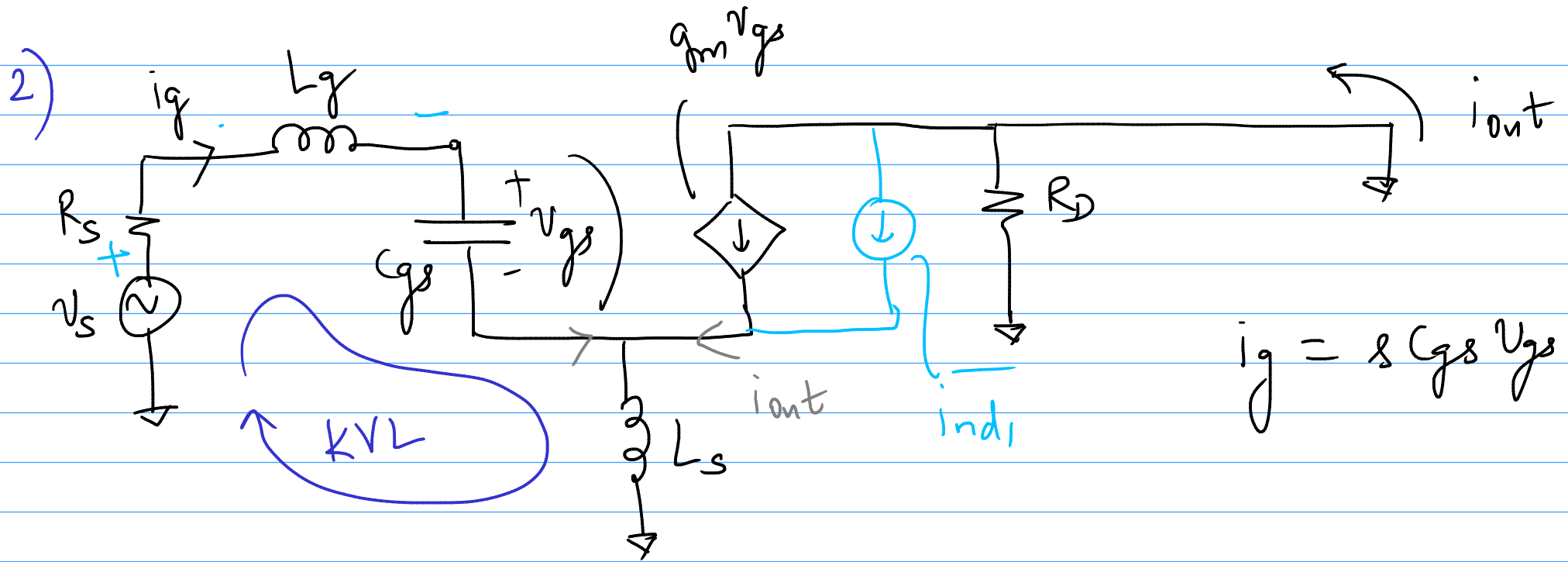
$$* \quad \overline{i_{nsc,1}^2} = \overline{i_{nR_D}^2}$$



$$i_{out} = \bar{i}_{ind1} + g_m v_{gs} \Rightarrow v_{gs} = \frac{1}{g_m} (i_{out} - \bar{i}_{ind1})$$

$$v_s = \underbrace{(R_s + sL_g)}_{\text{blue wavy line}} i_g + v_{gs} + sL_s (i_g + i_{out})$$

$$V_s = (R_s + sL_g) s C_{gs} V_{gs} + V_{gs}$$

$$+ sL_s (sC_{gs} V_{gs} + i_{out})$$

$$= sL_s i_{out} + \left[ R_s \cdot sC_{gs} + s^2 L_g C_{gs} + s^2 L_s C_{gs} + 1 \right] V_{gs}$$

$$s = j\omega \quad \Big| \quad \omega = \omega_0 \Rightarrow \omega_0^2 = \frac{1}{C_{gs} (L_s + L_g)}$$

$\parallel$   
 $\circ$   
 $\text{@ } \omega_0$

$$V_s = j\omega_0 L_s \cdot i_{out} + j\omega_0 C_{gs} R_s \cdot V_{gs}$$

$$= j\omega_0 L_s i_{out} + j\omega_0 C_{gs} R_s \cdot \frac{1}{g_m} (i_{out} - \overline{i_{nd,1}})$$

$$= i_{out} \left[ j\omega_0 L_s + \frac{j\omega_0 C_{gs} R_s}{g_m} \right] - \overline{i_{nd,1}} \cdot \left[ \frac{j\omega_0 C_{gs} R_s}{g_m} \right]$$

$$\frac{C_{gs}}{g_m} = \frac{1}{\omega_T}$$

$$V_s = i_{out} \left[ j\omega_0 L_s + j \frac{\omega_0 R_s}{\omega_T} \right] - \overline{i_{nd_1}} \left[ \frac{j\omega_0 R_s}{\omega_T} \right]$$

(A)

$$\rightarrow \text{If } \overline{i_{nd_1}} = 0$$

for output signal component only


$$G_{m_{out}} = \left| \frac{i_{out}}{V_s} \right| = \left| \frac{\omega_T}{j\omega_0 \omega_T L_s + j\omega_0 R_s} \right| = \frac{\omega_T}{\omega_0} \cdot \frac{1}{2R_s}$$

(B) Set  $V_s = 0 \Rightarrow i_{out}$  noise component only  $\left( = \overline{i_{nsc}} \right)$   
(due to  $M_1$ )

Set  $V_s = 0$   $= 2j\omega_0 R_s$

$$0 = \overline{I_{sc}} \left[ \frac{j\omega_0 L_s \omega_T + j\omega_0 R_s}{\omega_T} \right] - \overline{I_{nd1}} \left[ \frac{j\omega_0 R_s}{\omega_T} \right]$$
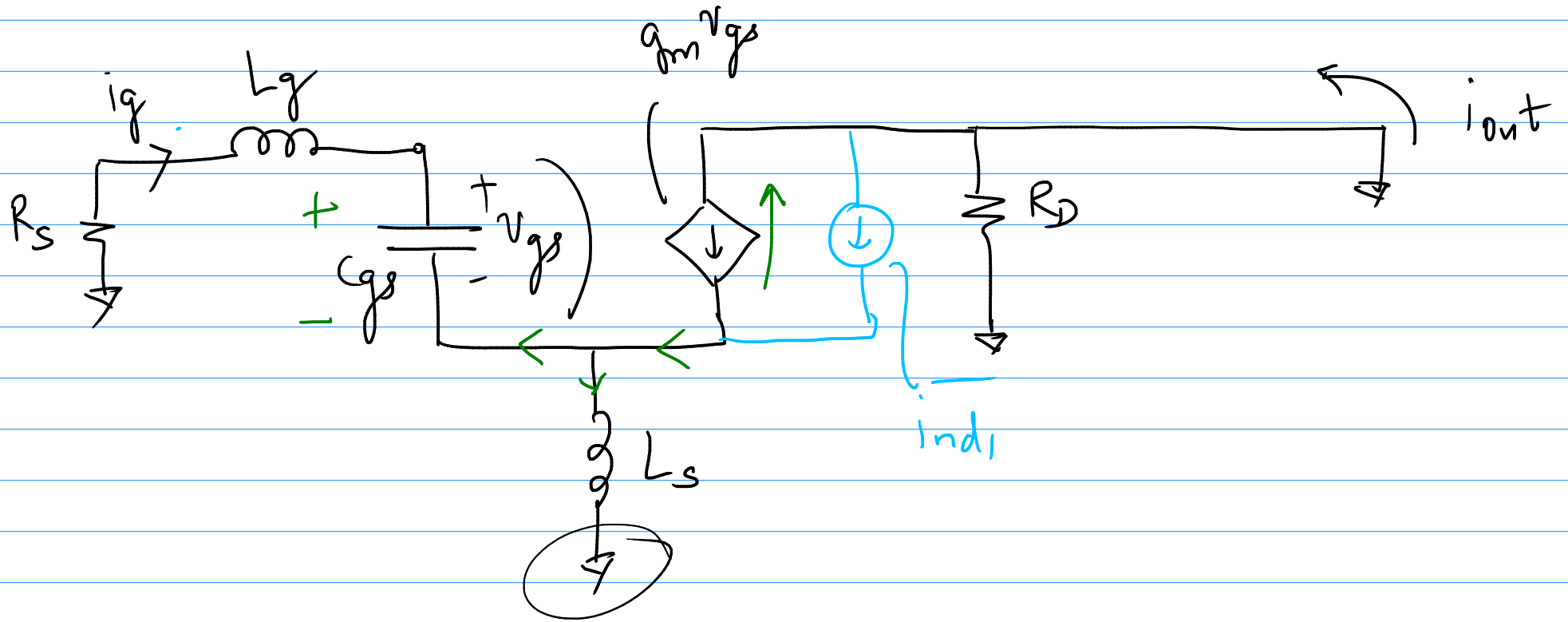
$$\overline{I_{sc}} = \frac{1}{2} \overline{I_{nd1}}$$



$$* \overline{i_{nsc_2}^2} = \frac{1}{4} \overline{i_{ind,1}^2}$$

$$* \overline{i_{nsc_3}^2} = G_m^2 \cdot \overline{v_{nr_s}^2}$$

$$F = \frac{G_m^2 \overline{v_{nr_s}^2} + \frac{1}{4} \overline{i_{nd_1}^2} + \overline{i_{nR_D}^2}}{G_m^2 \overline{v_{nr_s}^2}}$$

$$= 1 + \frac{1}{4} \cdot 4kT \alpha^2 g_m + \frac{4kT}{R_D}$$

$$G_m^2 \cdot 4kT R_s$$

$$F = 1 + \frac{\gamma^2 g_m}{4 G_m^2 R_s} + \frac{1}{G_m^2 R_s R_D}$$

$$G_m = \frac{W_T}{W_0} \cdot \frac{1}{2R_s}$$

$$F = 1 + \frac{\gamma^2 g_m}{4 \left( \frac{W_T}{W_0} \right)^2 \times \frac{1}{4R_s^2} \times R_s} + \frac{1}{\left( \frac{W_T}{W_0} \right)^2 \times \frac{1}{4R_s^2} \times R_s R_D}$$

$$F = 1 + 2g_m R_s \left( \frac{\omega_0}{\omega_T} \right)^2 + \frac{4R_s}{R_D} \left( \frac{\omega_0}{\omega_T} \right)^2$$

\* F can be small if  $\omega_0 \ll \omega_T$

$$\omega_T \propto \frac{1}{L^2}$$



Max gain, Min NF  $\Rightarrow$  max  $\omega_T \Rightarrow L = L_{\min}$ .

Example.


$$f_T = 200 \text{ GHz}$$

$$L_s = ?$$
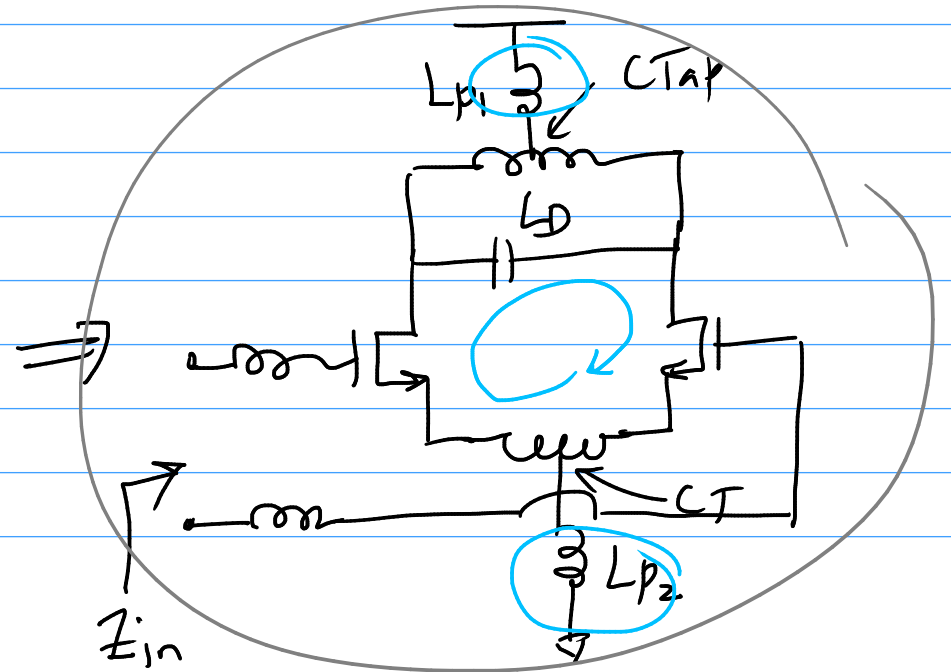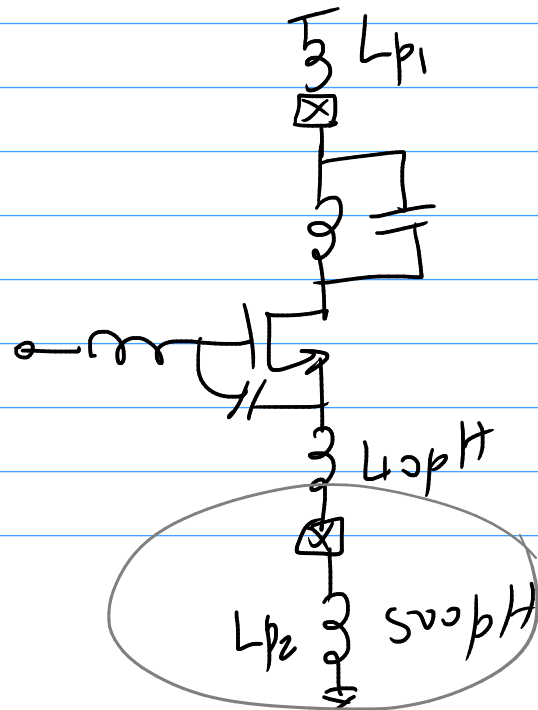
$$2\pi f_T \cdot L_s = 50 \Omega \Rightarrow L_s \approx 40 \text{ pH}$$



$M_1 \equiv M_2$

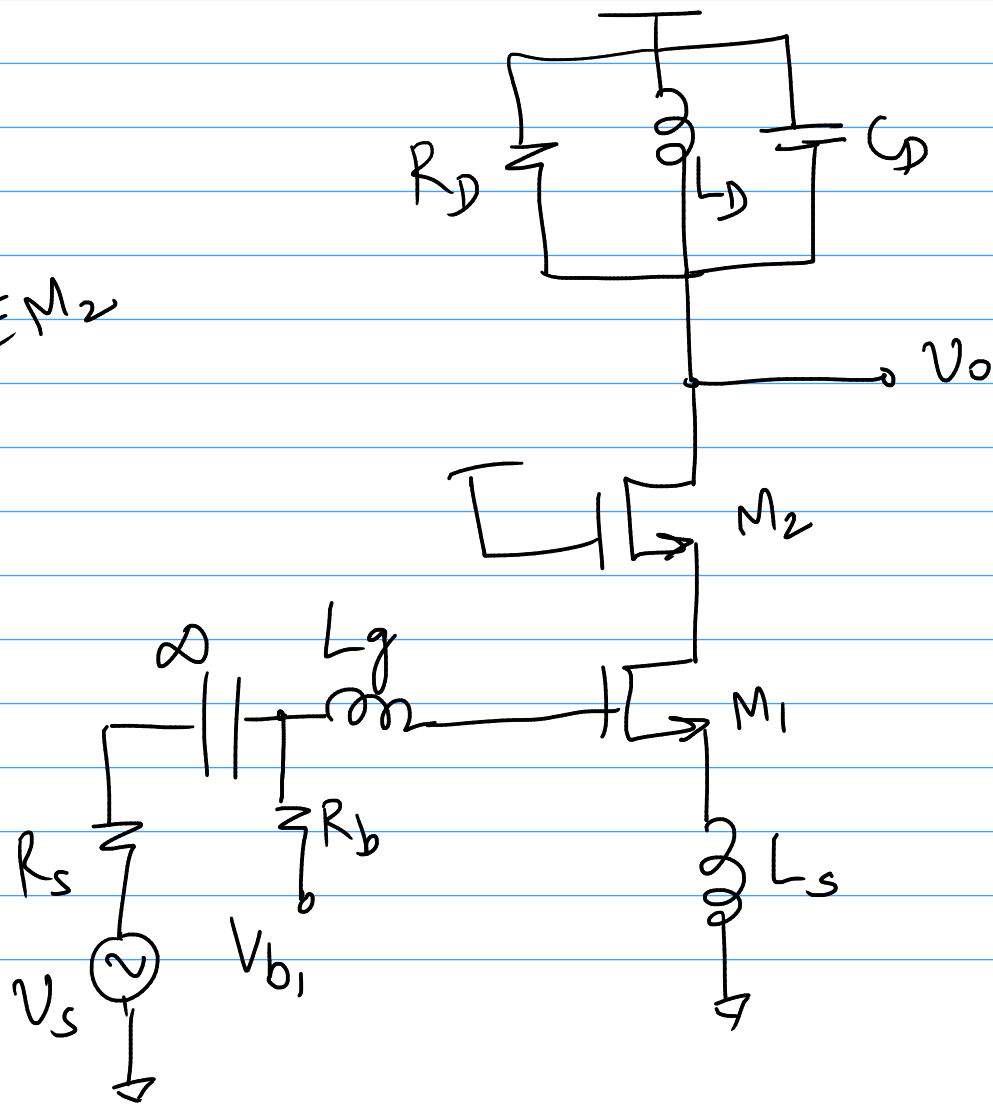

Set  $L_D, C_D, w_{12}, L_g, L_s,$   
 $(V_{GS} - V_T)$


1)  $L_D, C_D, R_D$  → depends on  
 $C_L$  ←  $C_{db2}$  fixed  $Q$  of  $L_D$

$$@ \omega_0: Q_{L_D} = \frac{R_D}{\omega_0 L_D}$$

maximise  $Q_{L_D}$  ✓

maximise  $L_D$  with  $C_{D, \min}$ .


$$R_D = Q_{L_D} \cdot \omega_0 L_D$$

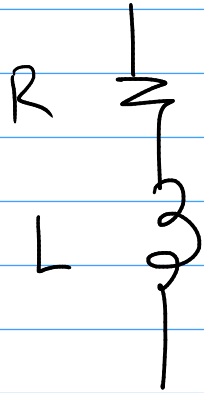

$$Q = \frac{\omega L}{R}$$

$$Q = \frac{\text{Im}(Z)}{\text{Re}(Z)}$$

$Z_{\text{in}}$

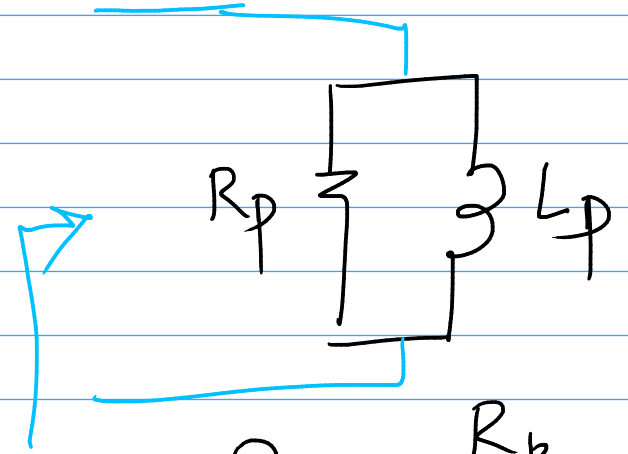

$$Q = \frac{R_p}{\omega L_p}$$

$$f_0 = \frac{1}{2\pi\sqrt{L_D C_D}}$$

2)  $P_{max} \rightarrow$  bias current  $I_0$

$$3) \frac{2I_0}{V_{GS} - V_T} = g_m$$

$$I_0 = \frac{1}{2} \mu C_{ox} \left(\frac{W}{L}\right) (V_{GS} - V_T)^2$$

4) Min gain =  $A_0$

$$| \text{gain} | = g_{m1} R_D \cdot Q_{in}$$

$\swarrow$   $\searrow$   $\rightarrow$   
 $k_1 \sqrt{W_1}$       fixed by  $L_D$

$$\frac{k_2}{W_1}$$

gives  
max  $W_1$   
to meet  
gain


5) calculate  $W_T, C_{gs}$

6)  $R_S = W_T \cdot L_S$   
(calculate  $L_S$ )



7)

$$W_0 = \frac{1}{\sqrt{C_{gs} (L_g + L_S)}}$$


(calculate  $L_g$ )

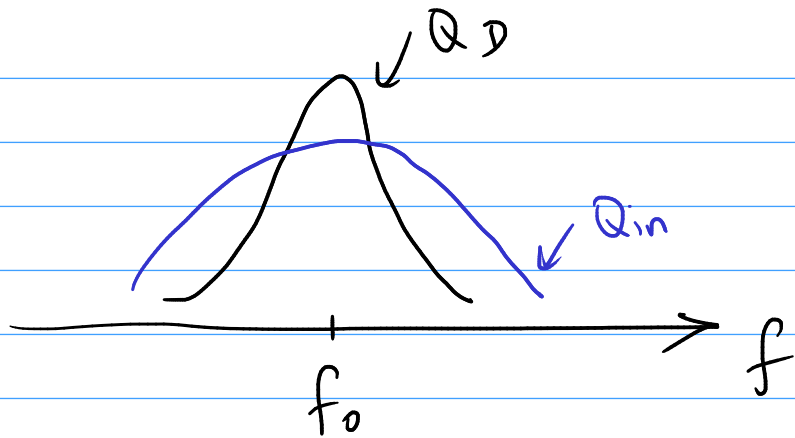

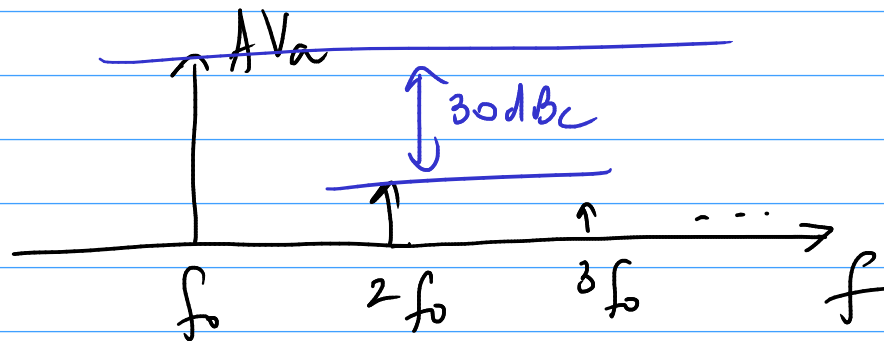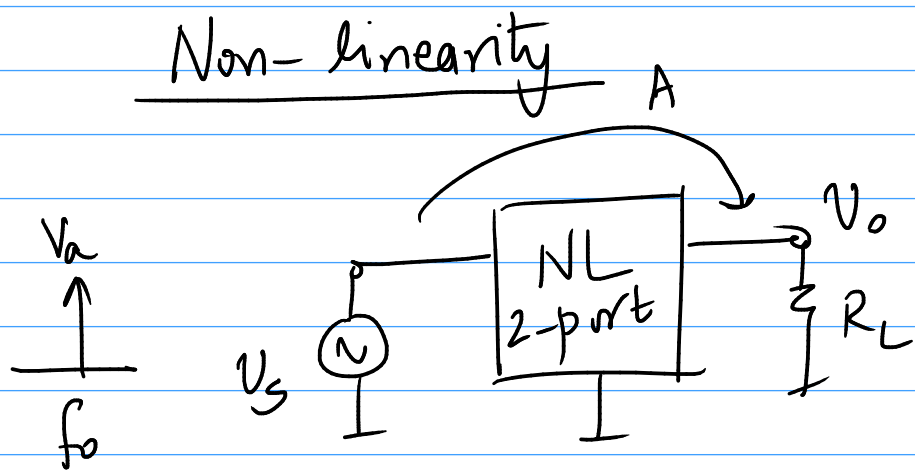$Q = \frac{W_s}{BW} \approx$  limited by narrower of the two resonances





THD = total harmonic distortion

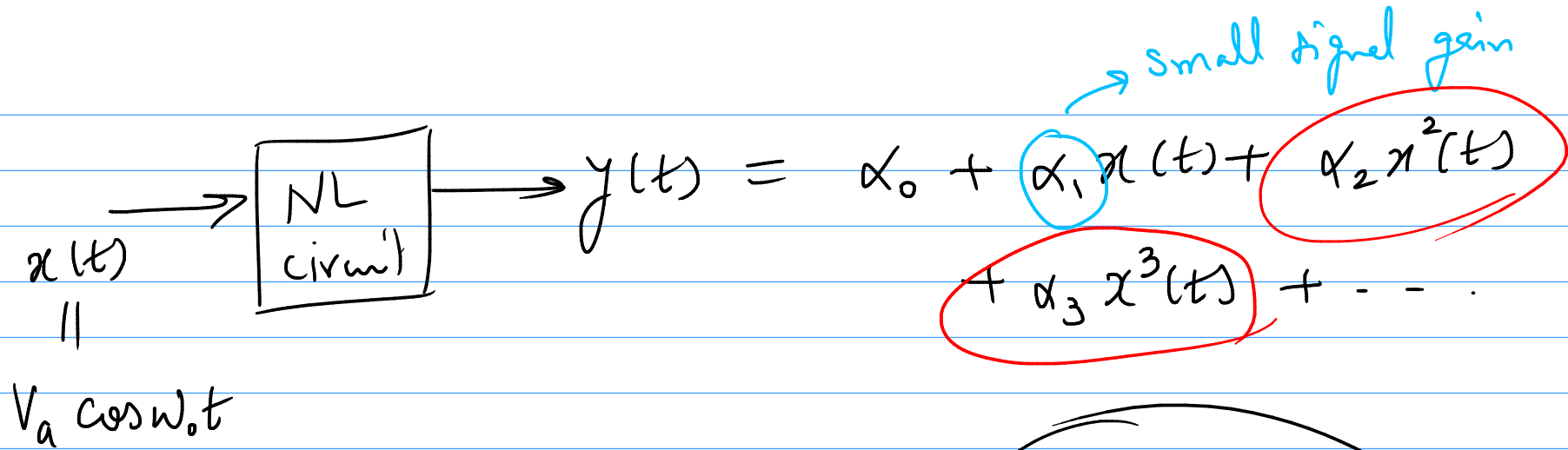

$$y(t) = \alpha_0 + \alpha_1 V_a \cos \omega_0 t + \alpha_2 V_a^2 \cos^2 \omega_0 t + \alpha_3 V_a^3 \cos^3(\omega_0 t)$$

$$\frac{\alpha_3 V_a^3}{4} \left( \underbrace{\cos 3\omega_0 t}_{3^{\text{rd}} \text{ harmonic}} + \underbrace{3 \cos \omega_0 t}_{\text{small signal gain}} \right)$$
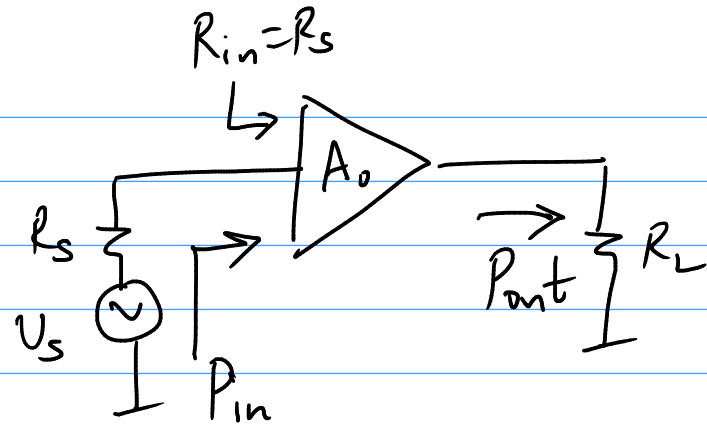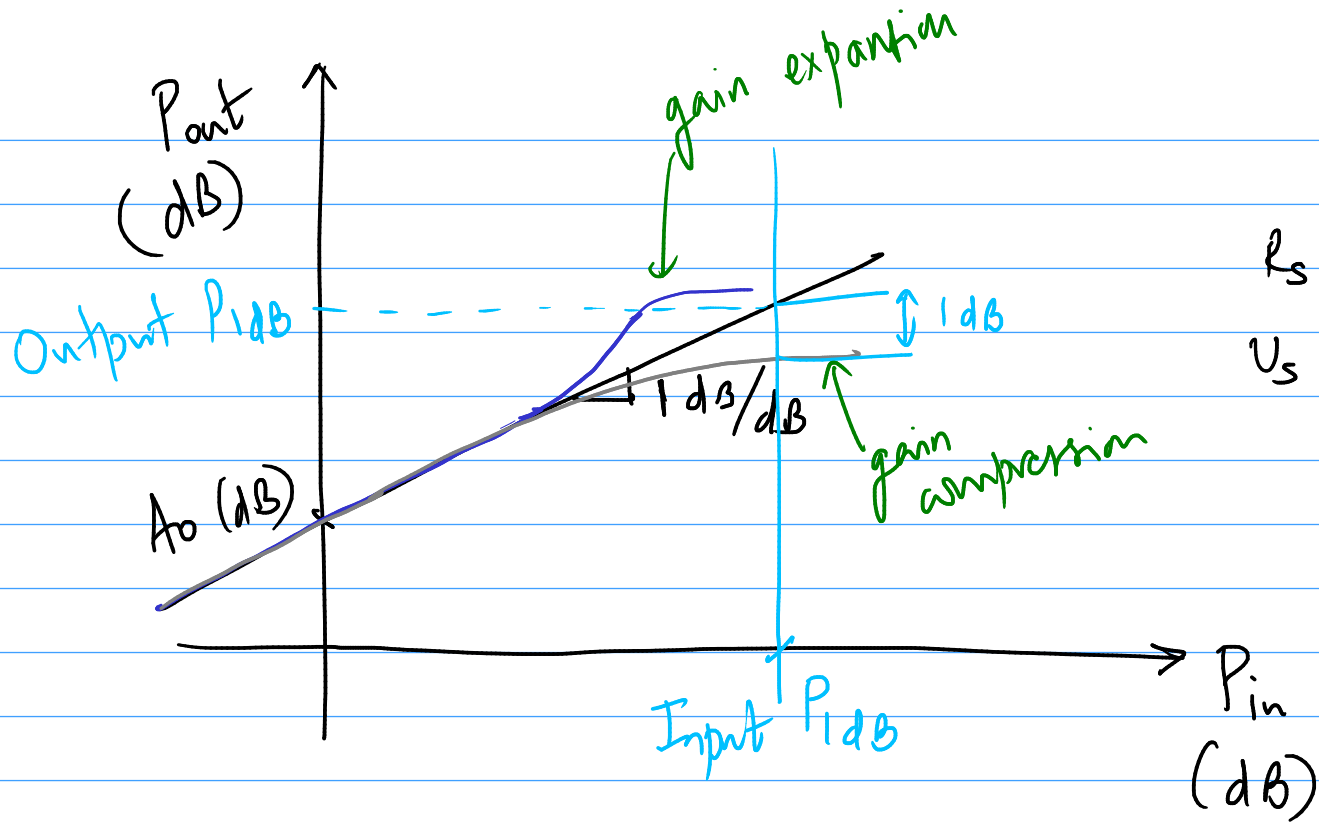
$$\parallel \frac{\alpha_2 V_a^2}{2} (1 + \underbrace{\cos 2\omega_0 t}_{2^{\text{nd}} \text{ harmonic}})$$



$$P_{out} = A_0 \cdot P_{in}$$

$$P_{out} \text{ (dB)} = A_0 \text{ dB} + P_{in} \text{ (dB)}$$

NL amplifiers :

$$y(t) = \alpha_0 + \alpha_2 \frac{V_a^2}{2} + \left\{ \alpha_1 V_a + \frac{3\alpha_3 V_a^3}{4} \right\} \cos \omega_0 t$$

$$+ \frac{\alpha_2 V_a^2}{2} \cos(2\omega_0 t) + \frac{\alpha_3 V_a^3}{4} \cos 3\omega_0 t + \dots$$

*Small* (pointing to the  $\alpha_3 V_a^3$  term)




$$20 \log |\alpha_1| - 1 \text{ dB} = 20 \log \left| \alpha_1 + \frac{3\alpha_3 V_a^2}{4} \right|$$

$V_a = V_{a, 1\text{-dB}}$

Input  $P_{1\text{dB}}$  = Input-referred 1-dB compression point



=  $P_{in}$  where the actual  $P_{out}$  vs  $P_{in}$  curve

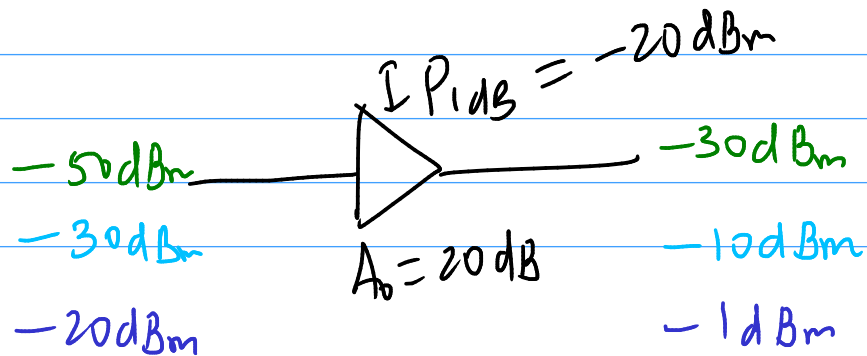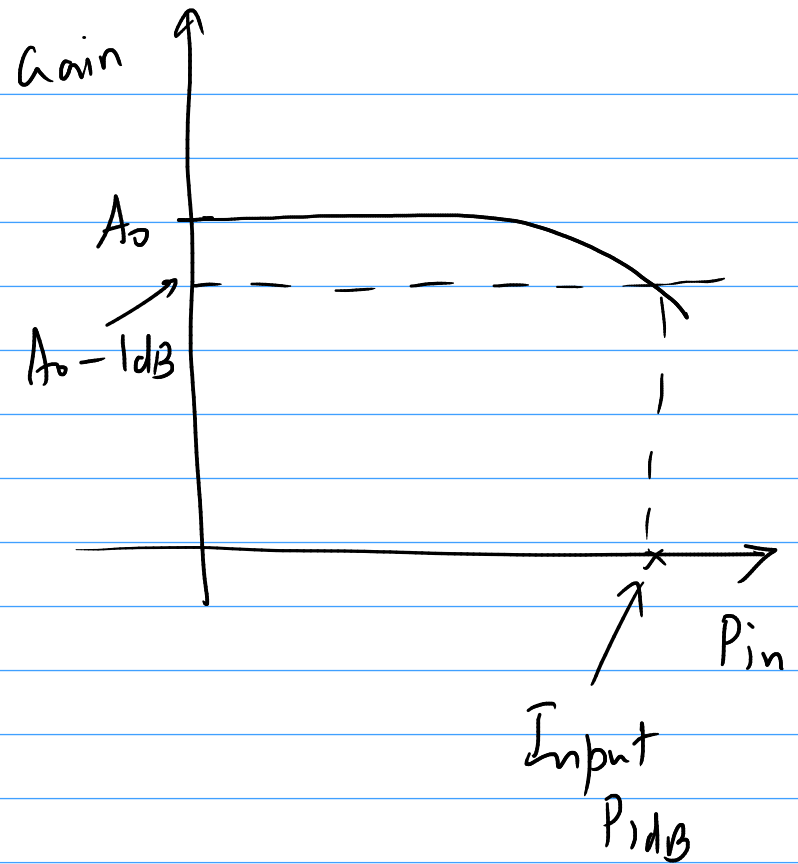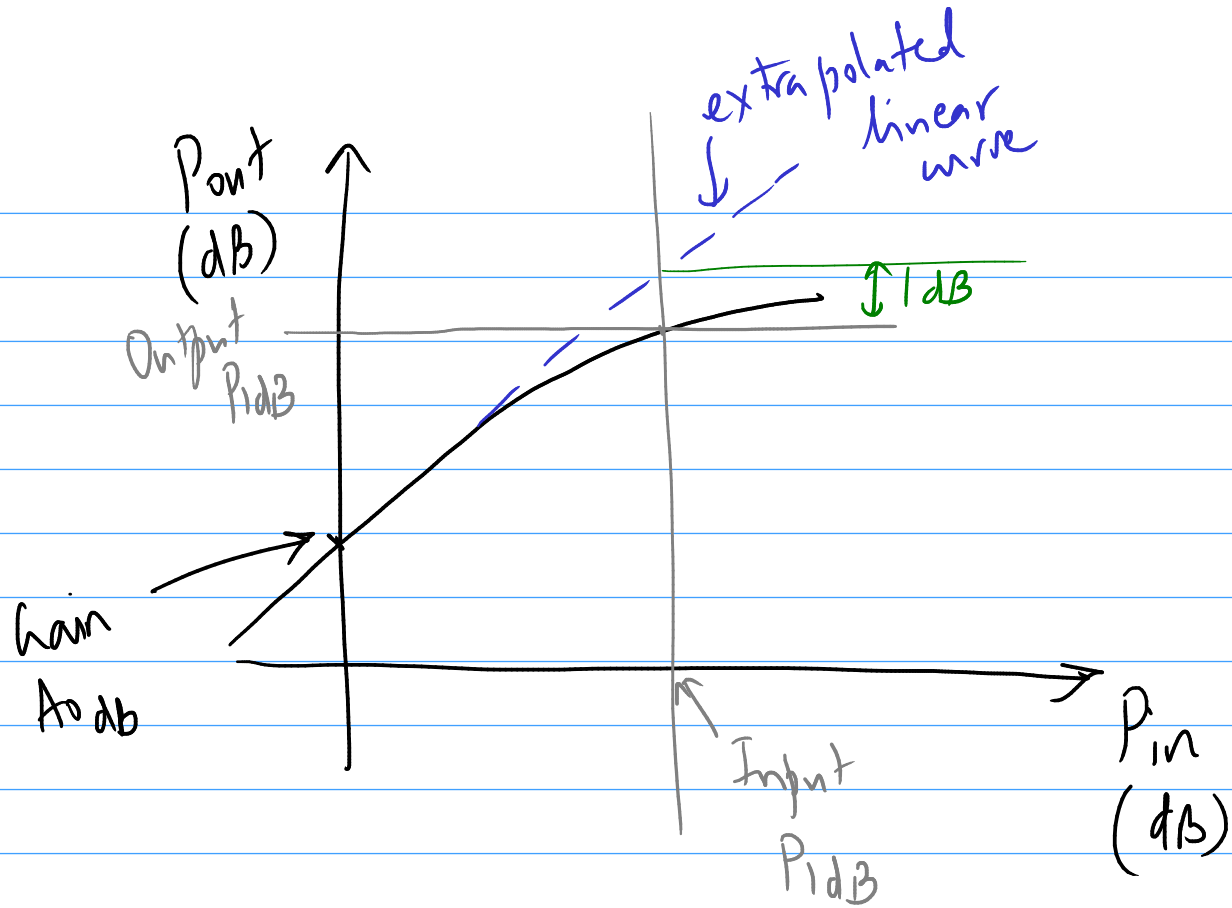falls 1dB below the extrapolated small-signal linear plot.




$$20 \log \left| \alpha_1 + \frac{3}{4} \alpha_3 A_{1-dB}^2 \right| = 20 \log |\alpha_1| - 1 \text{ dB}$$

$$A_{1-dB} = \sqrt{0.145 \left| \frac{\alpha_1}{\alpha_3} \right|}$$

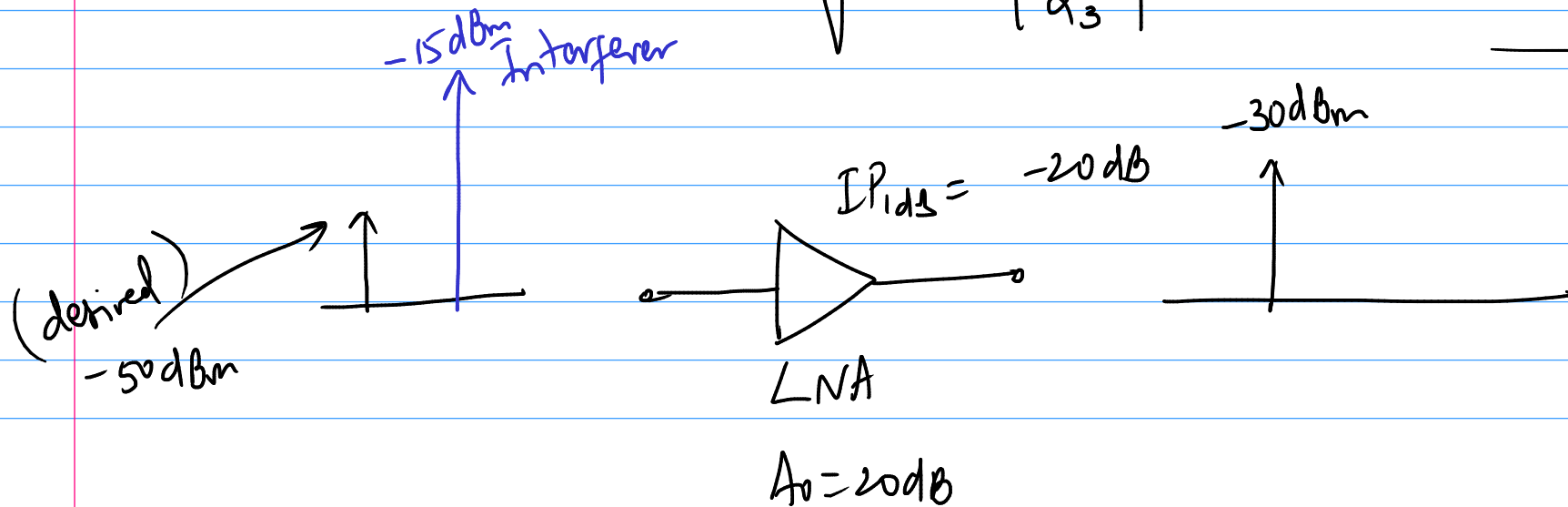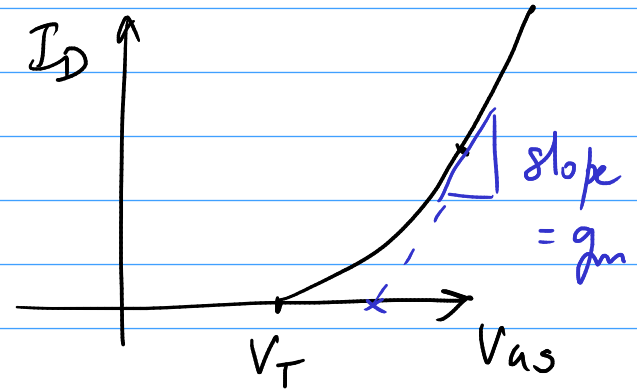

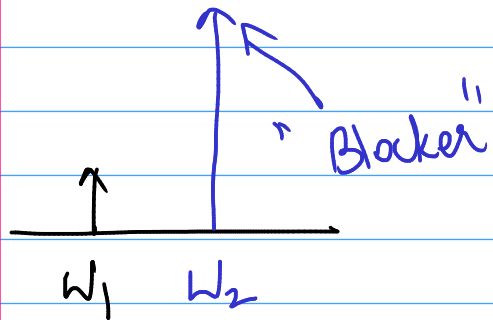
$$x(t) = A_1 \cos \omega_1 t + A_2 \cos \omega_2 t \quad A_1 \ll A_2$$



(desired)


(Int.)

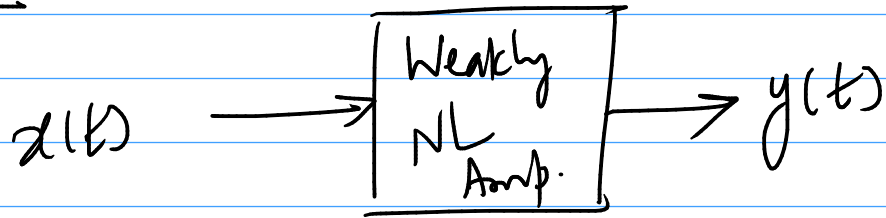

HW

$$y(t) = \left( \alpha_1 + \frac{3}{2} \alpha_3 A_2^2 + \dots \right) A_1 \cos \omega_1 t + \dots$$

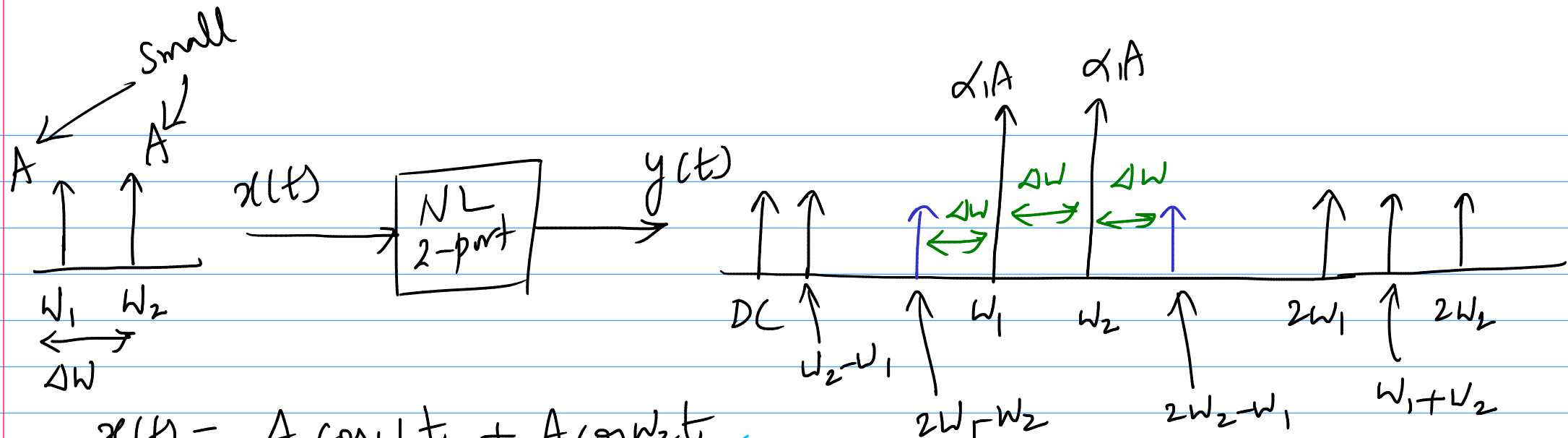$\alpha_3$  - small & negative but  $A_2$  is large  
 $\Rightarrow$  gain is reduced drastically  $\Rightarrow$  "Desensitizing"



$$x(t) = A \cos \omega_1 t + A \cos \omega_2 t$$

$$y(t) = \alpha_0 + \alpha_1 x(t) + \alpha_2 x^2(t) + \alpha_3 x^3(t)$$

$$\alpha_1 A \cos \omega_1 t + \alpha_1 A \cos \omega_2 t$$

$$DC + 2\omega_1 + 2\omega_2$$

$$+ 2\alpha_2 A^2 \cos \omega_1 t \cos \omega_2 t$$

$$3\omega_1, 3\omega_2$$

$$2\omega_1 \pm \omega_2; 2\omega_2 \pm \omega_1$$


$p\omega_1 \pm q\omega_2 = \text{"intermodulation" terms} \rightarrow \text{IM}_{p+q}$

$\left. \begin{array}{l} 2\omega_2 \pm \omega_1 \\ 2\omega_1 \pm \omega_2 \end{array} \right\} \text{3rd order intermodulation (IM}_3\text{) terms}$

$\left. \begin{array}{l} 2\omega_2 - \omega_1 \leftarrow \omega_2 + \Delta\omega \\ 2\omega_1 - \omega_2 \leftarrow \omega_1 - \Delta\omega \end{array} \right\} \text{If you choose small } \Delta\omega \rightarrow \text{IM}_3 \text{ terms fall in band}$

$|M_3$  terms are:  $\frac{3}{4} \alpha_3 A^3 \cos(2\omega_1 - \omega_2)t$

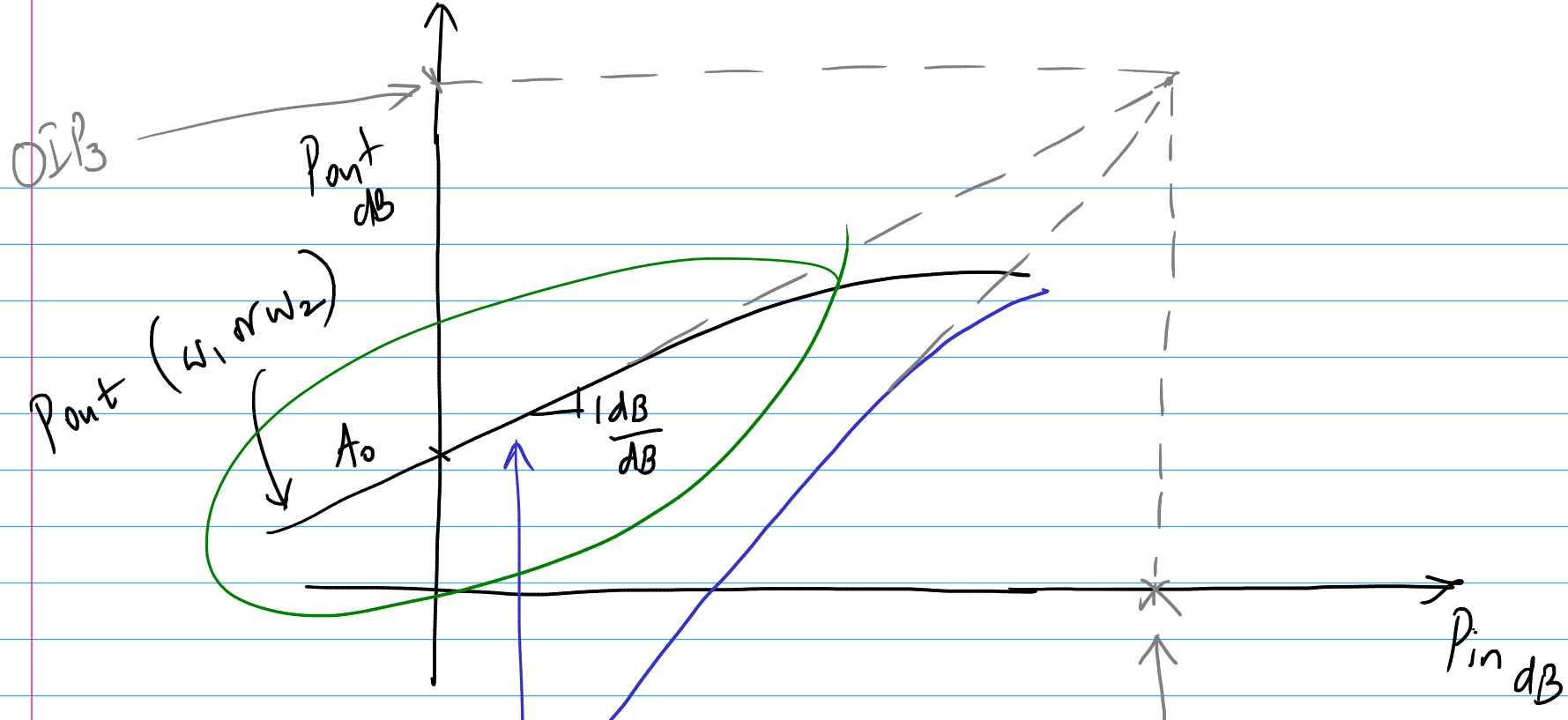+  $\frac{3}{4} \alpha_3 A^3 \cos(2\omega_2 - \omega_1)t$   
HW



$OIP_3$

$P_{out\ dB}$

$P_{out}(\omega_1, \omega_2)$

$A_0$

$1\ \frac{dB}{dB}$

$P_{in\ dB}$

$IIP_3$

input-referred 3rd order intercept point

$P_{out}(IM_3)$

either

$2\omega_1 - \omega_2$   
or  
 $2\omega_2 - \omega_1$

$$|\alpha_1 A_{IP_3}| = \left| \frac{3}{4} \alpha_3 A_{IP_3}^3 \right| \quad @ \quad IIP_3$$

$$A_{IP_3}^2 = \frac{4}{3} \frac{\alpha_1}{\alpha_3}$$



$$IIP_3 = \frac{A_{IP_3}^2}{2R_s} = \frac{2}{3} \frac{\alpha_1}{\alpha_3} \cdot \frac{1}{R_s}$$


$$A_{1dB} = \sqrt{0.145 \left| \frac{\alpha_1}{\alpha_3} \right|}$$

$$A_{IP3} = \sqrt{\frac{4}{3} \left| \frac{\alpha_1}{\alpha_3} \right|}$$

$$\frac{A_{IP3}}{A_{1dB}} = \sqrt{\frac{4}{3} \times \frac{1}{0.145}} = 3.03$$

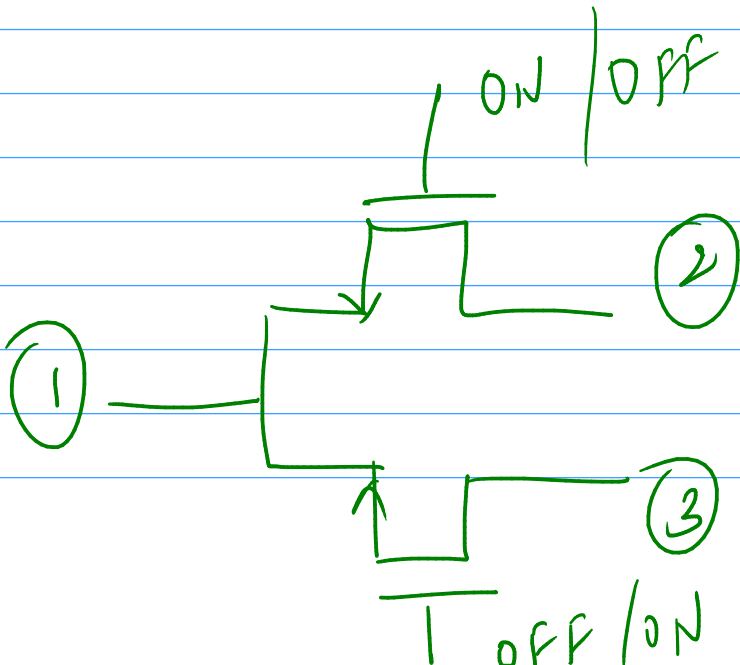
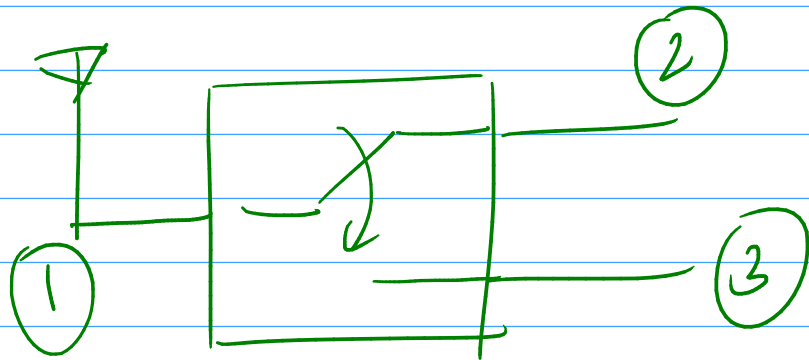
$$IP3_{dB} = IP_{1dB} + 9.63 \text{ dB}$$




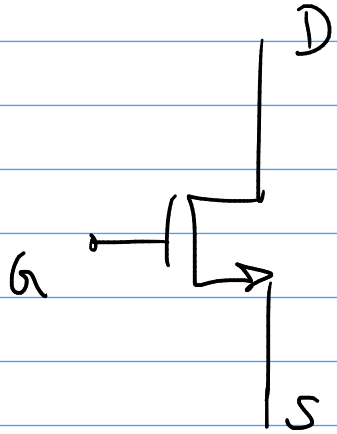

$$I_D = \frac{1}{2} \mu C_{ox} \left( \frac{W}{L} \right) (V_{GS} - V_T)^2 (1 + \lambda V_{DS})$$

$\hookrightarrow IIP_3 = \infty$  ??

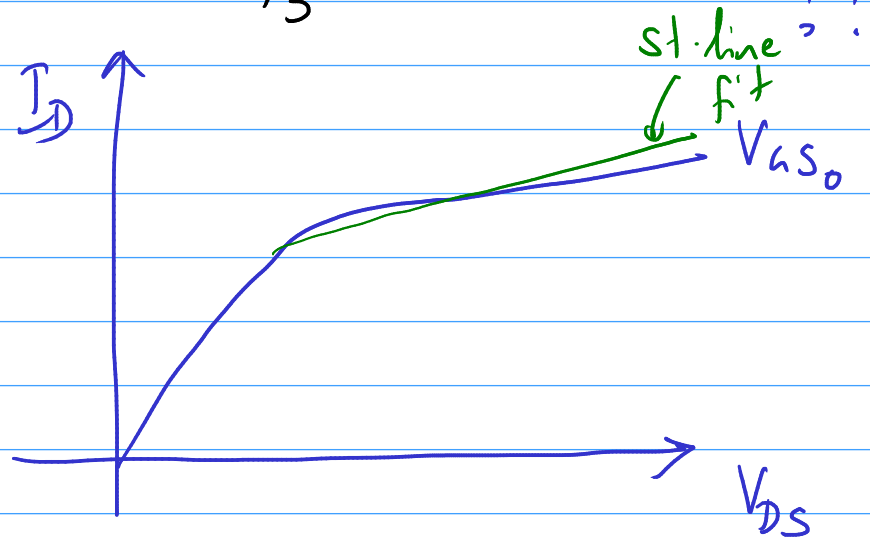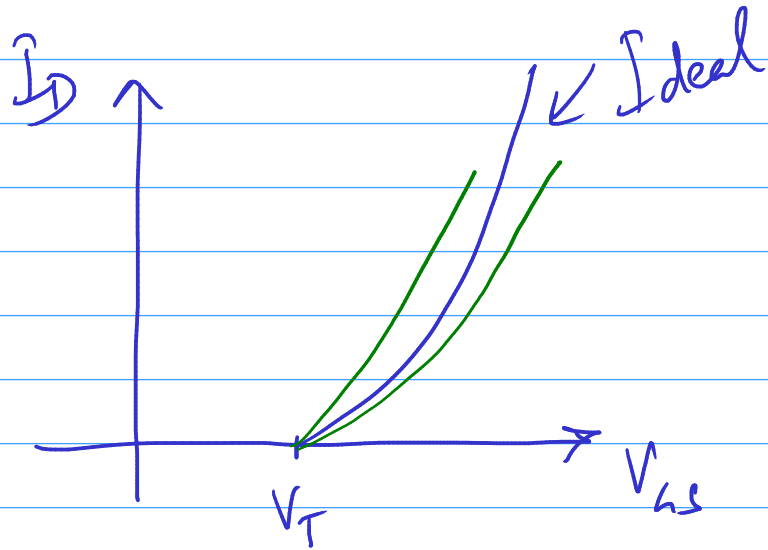

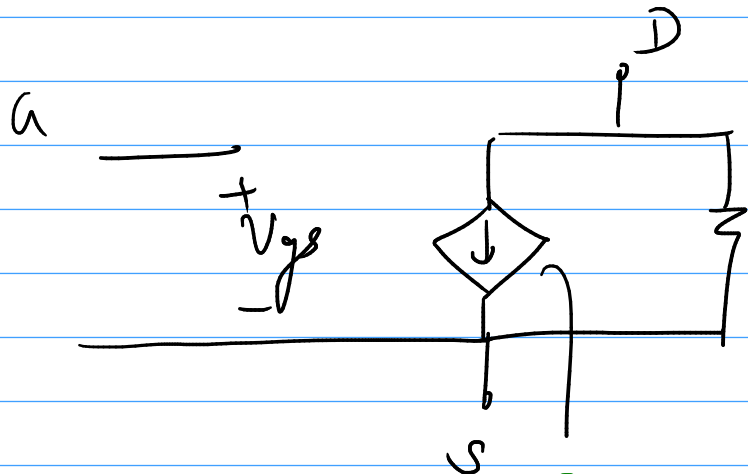


$$g_m v_{gs}$$



$$r_{ds}$$


$$i_{d1} = g_{m1} v_{gs} = g_{m1} Q_{in} v_s$$

$$v_{d1} = -i_{d1} \cdot \frac{1}{g_{m2}} \approx -\frac{g_{m1}}{g_{m2}} \cdot Q_{in} v_s$$

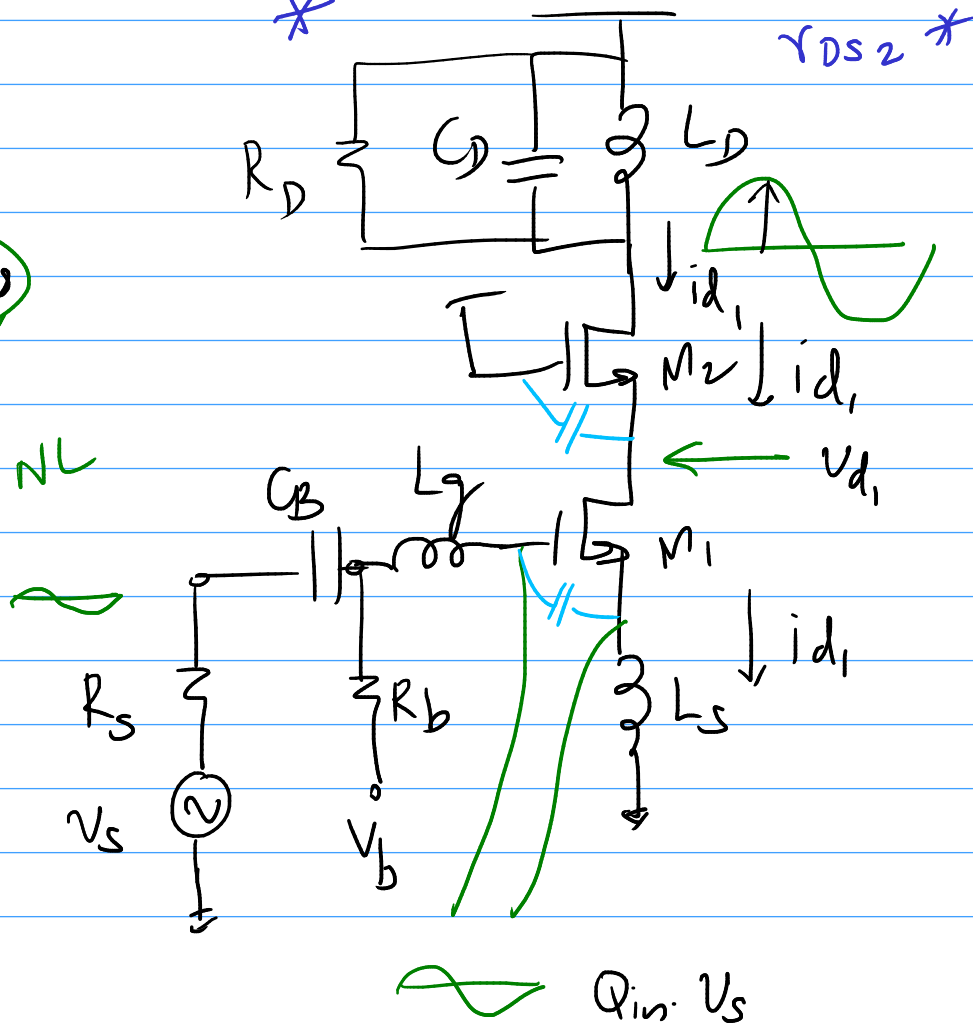
$$v_{out} = -g_{m1} R_D \cdot Q_{in} v_s$$





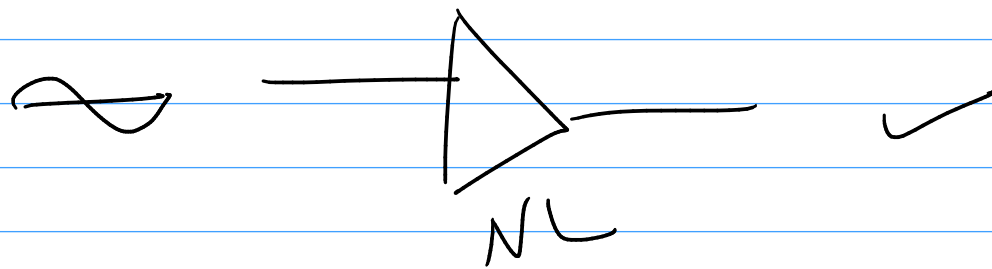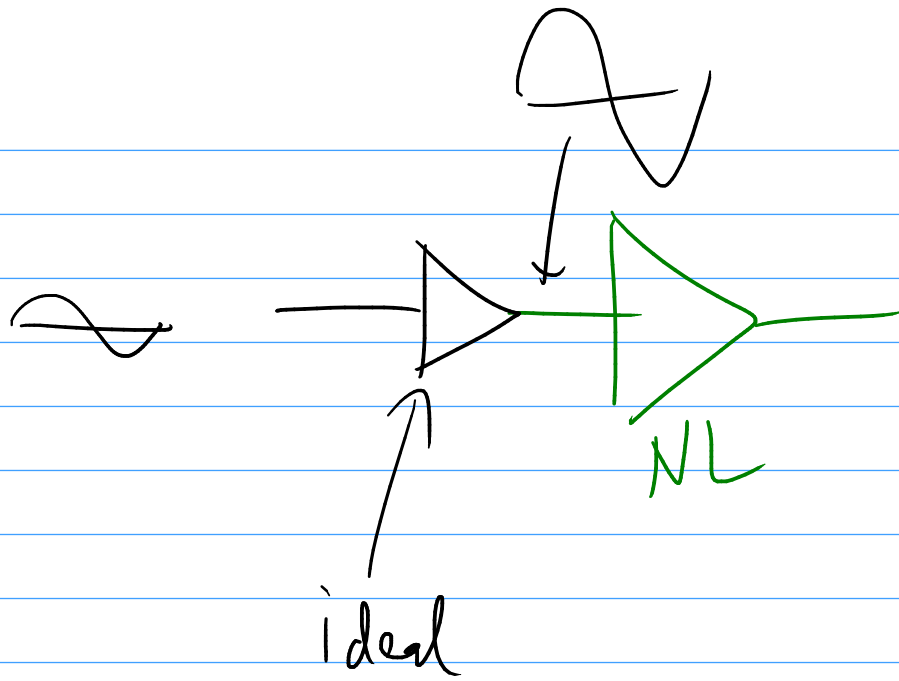

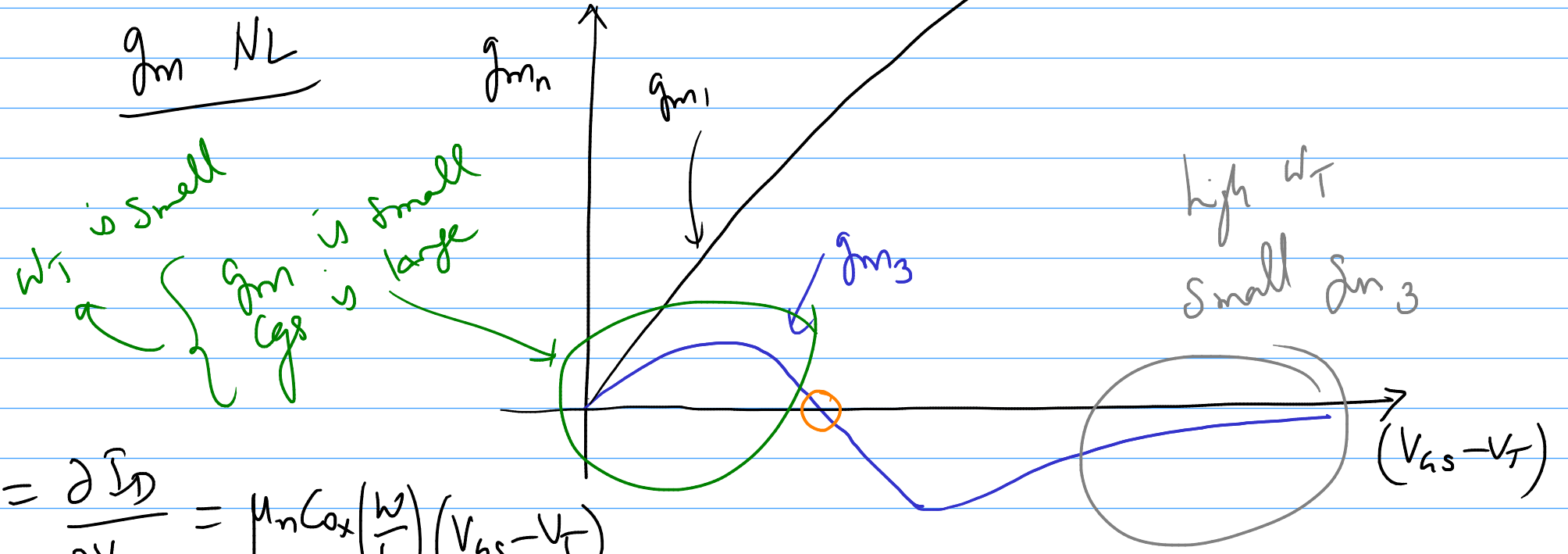



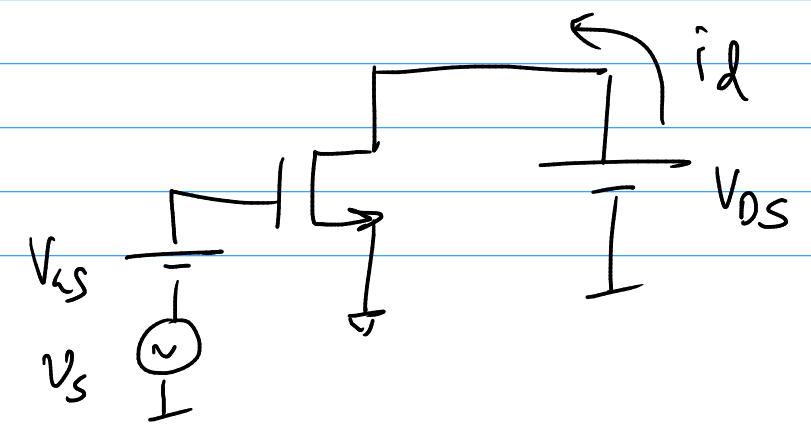
$$g_{m1} = \frac{\partial I_D}{\partial V_{GS}} = \mu_n C_{ox} \left( \frac{W}{L} \right) (V_{GS} - V_T)$$



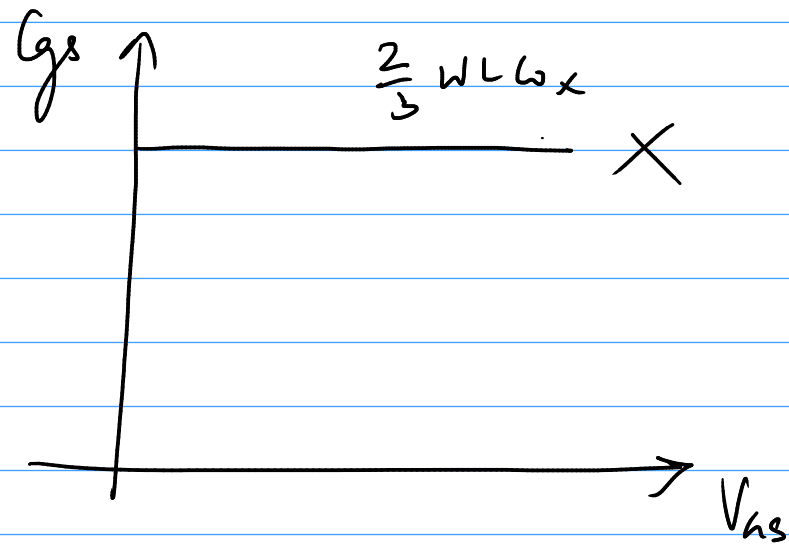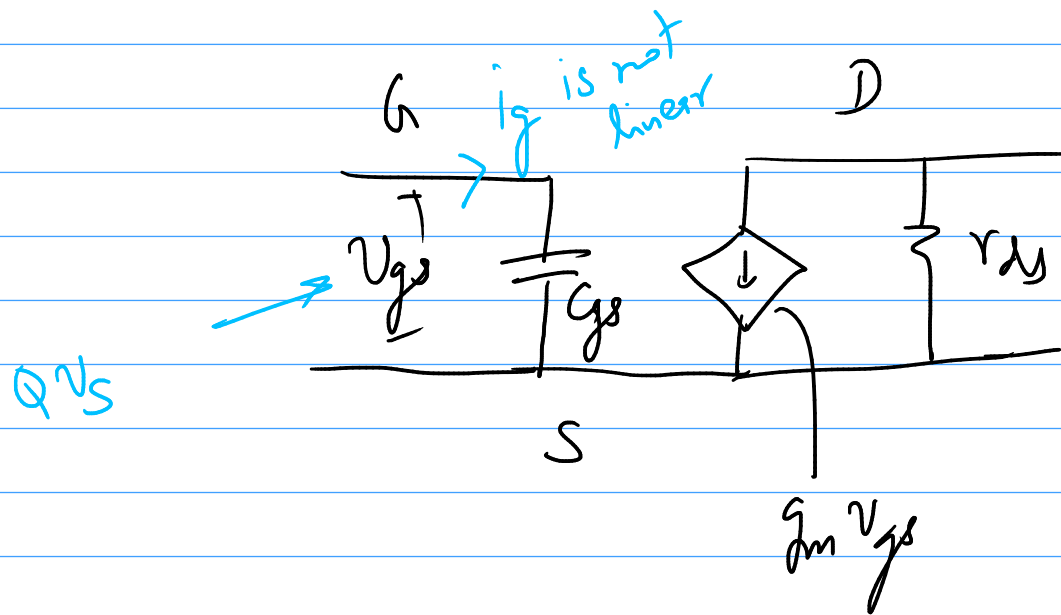


$$C_{gs} = \frac{2}{3} WL C_{ox}$$

# 1/3 of cascaded NL Systems

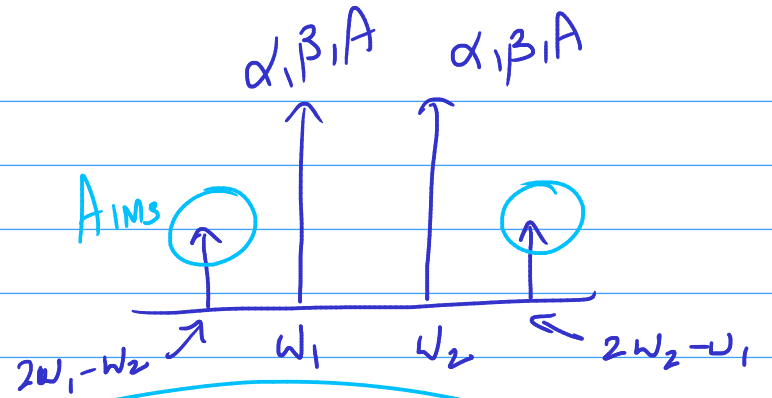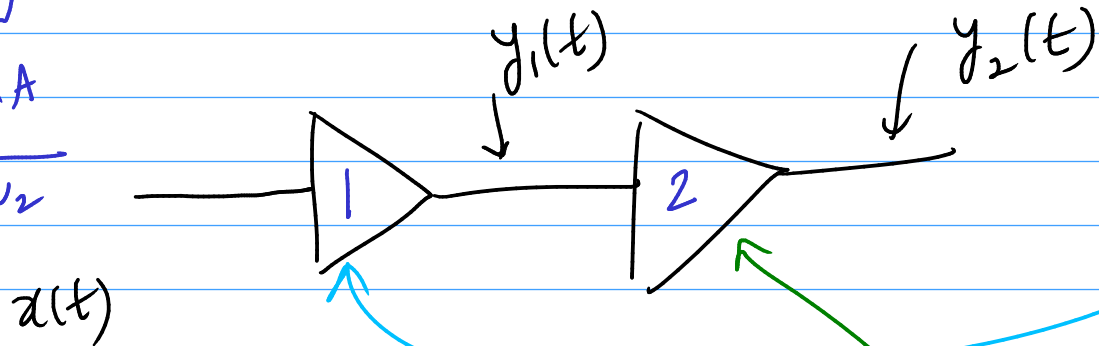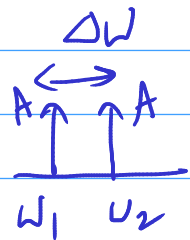

$$y_1(t) = \alpha_0 + \alpha_1 x(t) + \alpha_2 x^2(t) + \alpha_3 x^3(t)$$
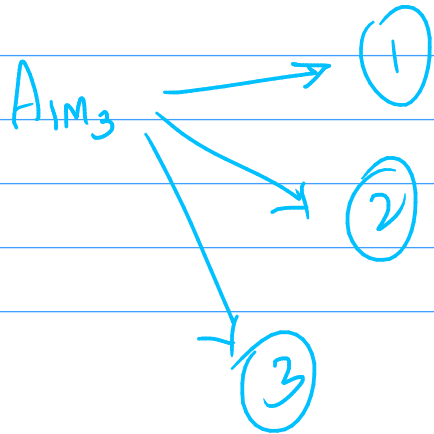
$$y_2(t) = \beta_0 + \beta_1 y_1(t) + \beta_2 y_1^2(t) + \beta_3 y_1^3(t)$$



$$A_{IP_3} = \sqrt{\frac{4}{3} \left| \begin{array}{c} ( ) \\ ( ) \end{array} \right|}$$

Small signal gain

3rd order term

$$= \sqrt{\frac{4}{3} \left| \begin{array}{c} \alpha_1 \beta_1 \\ \alpha_3 \beta_1 + 2 \alpha_1 \alpha_2 \beta_2 + \alpha_1^3 \beta_3 \end{array} \right|}$$

Worst case  $1/p_3 \approx$

$$A_{1/p_3} = \sqrt{\frac{4}{3} \frac{|\alpha_1 \beta_1|}{|\alpha_3 \beta_1| + |2\alpha_1 \alpha_2 \beta_2| + |\alpha_1^3 \beta_3|}}$$

$$\frac{1}{A_{1/p_3}^2} = \frac{3}{4} \frac{|\alpha_3 \beta_1| + |2\alpha_1 \alpha_2 \beta_2| + |\alpha_1^3 \beta_3|}{|\alpha_1 \beta_1|}$$


$$\frac{1}{A_{\beta}^2} = \frac{1}{A_{\beta_1}^2} + \frac{3}{4} \frac{\begin{vmatrix} 2 & \alpha_2 \beta_2 \\ & \beta_1 \end{vmatrix}}{\beta_1} + \frac{\alpha_1^2}{A_{\beta_2}^2}$$

$\approx 0$  for narrow band  
amp.

$$\frac{1}{A_{\beta}^2} \approx \frac{1}{A_{\beta_1}^2} + \frac{G_1^2}{A_{\beta_2}^2} + \frac{G_1^2 G_2^2}{A_{\beta_3}^2} + \dots$$


Low Noise Figure  $\rightarrow$  Have high gain up front  
in the chain

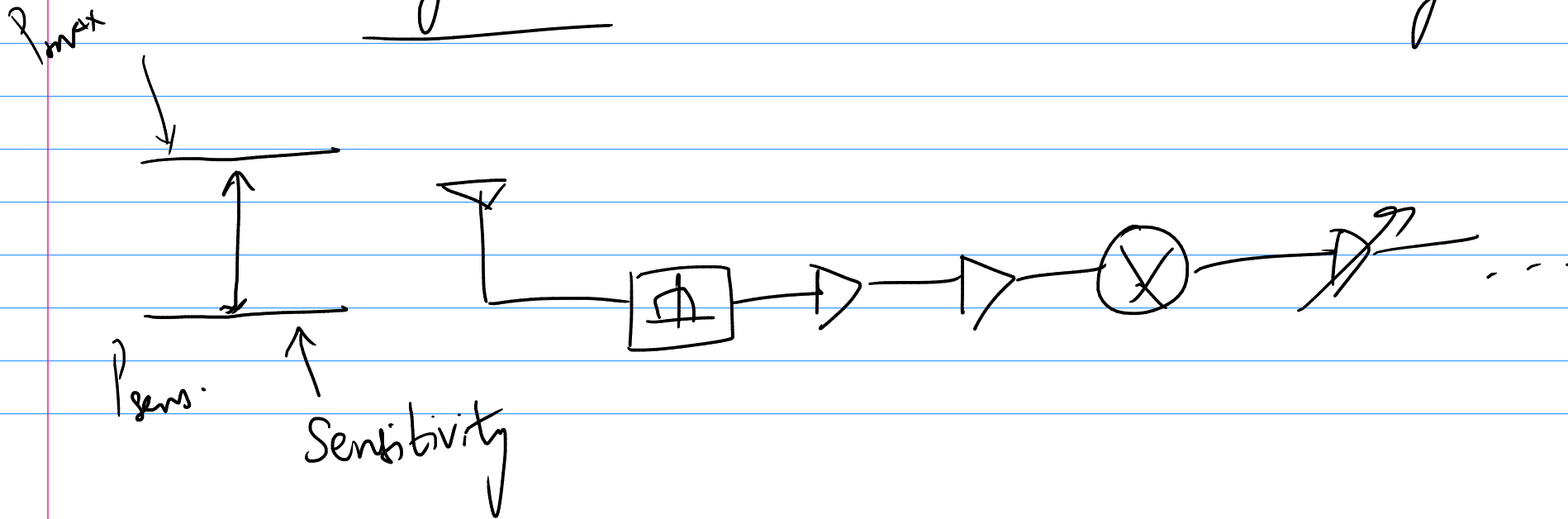High  $1/P_3$   $\rightarrow$  Not too much gain up front




$P_{\text{sensitivity}}$  (P<sub>min.</sub>) = Minimum power that the receiver can receive while meeting a required SNR (BER)
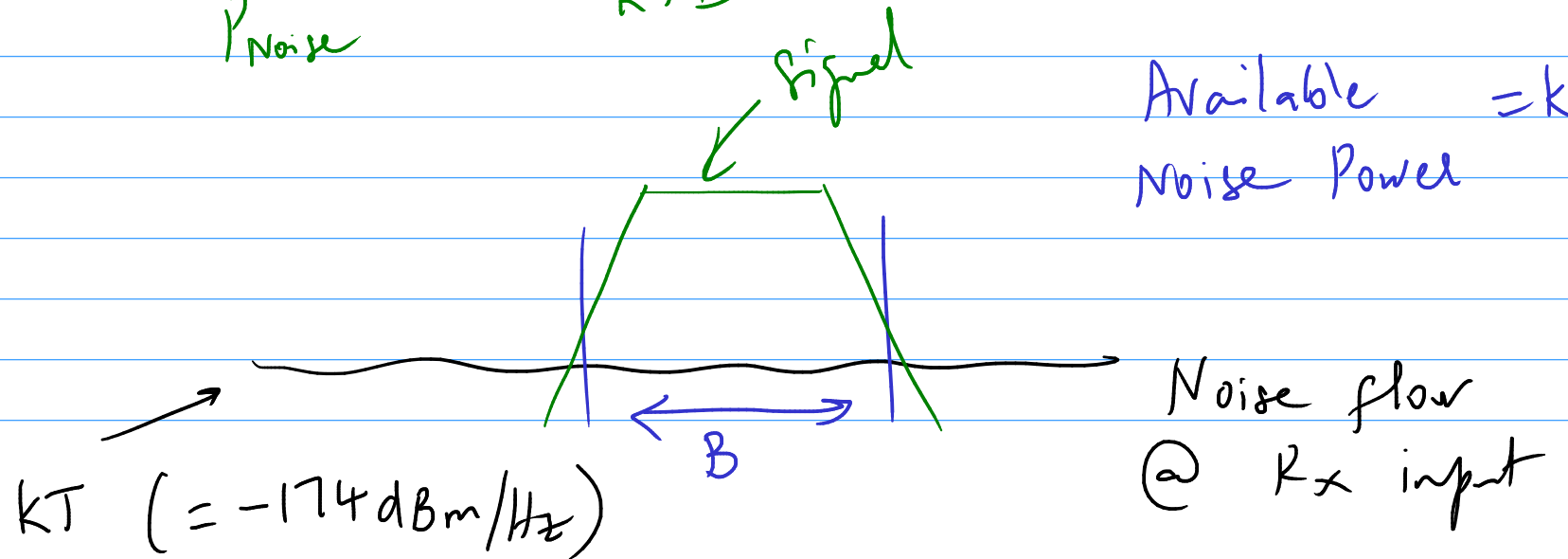
$$\text{SNR} = \frac{P_{\text{sig}}}{P_{\text{noise}}} = \frac{P_{\text{sig}}}{kTB \cdot F}$$




$$SNR_{min.} = \frac{P_{sens.}}{KTB \cdot F}$$
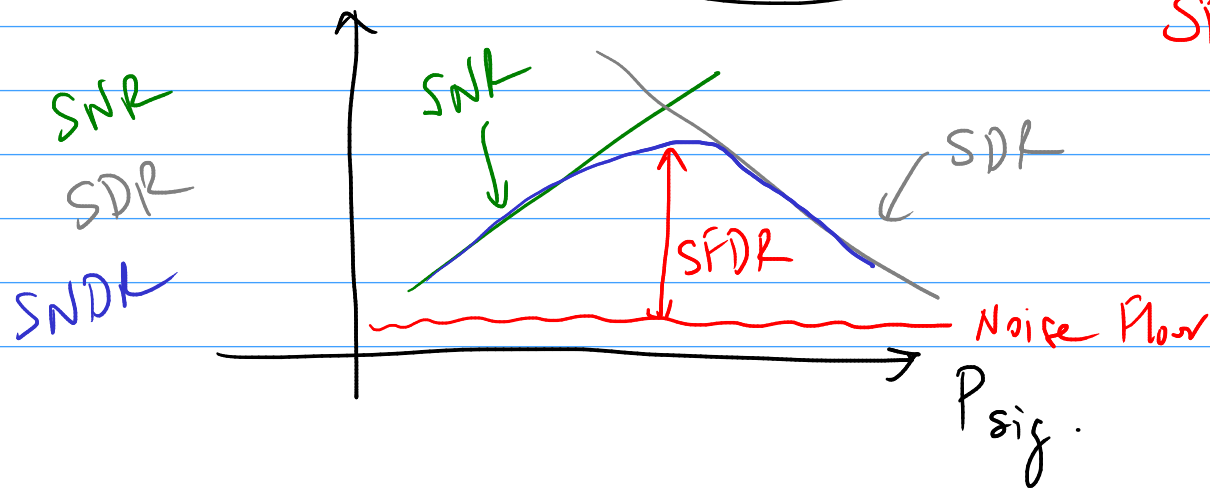
$$P_{sens.} (dB) = -174 \text{ dBm/Hz} + 10 \log(B) + NF + SNR_{min.}$$



SFDR = Spurious free  
dynamic Range

## Parallel Resonance

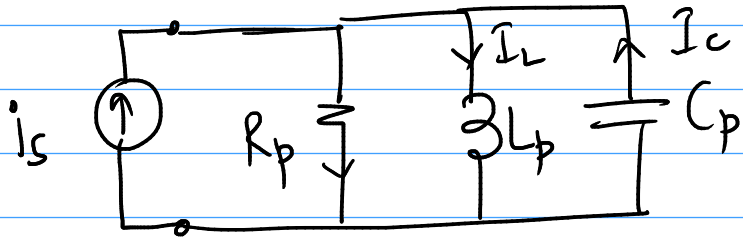


$$\omega_0 = \frac{1}{\sqrt{L_p C_p}}$$

$$Z_{\text{resonance}} = R_p$$

$$|I_L| = |I_C| = Q \cdot i_s \text{ @ } \omega_0$$

## Series Resonance

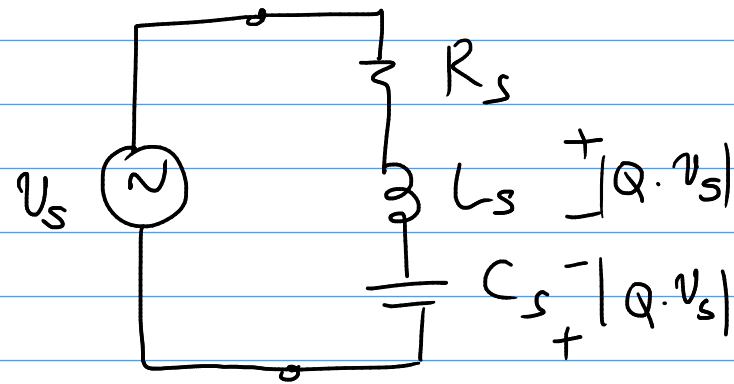


$$\omega_0 = \frac{1}{\sqrt{L_s C_s}}$$

$$Z_{\text{resonance}} = R_s$$


$$|V_L| = |V_C| = Q \cdot v_s \text{ @ } \omega_0$$

Parallel

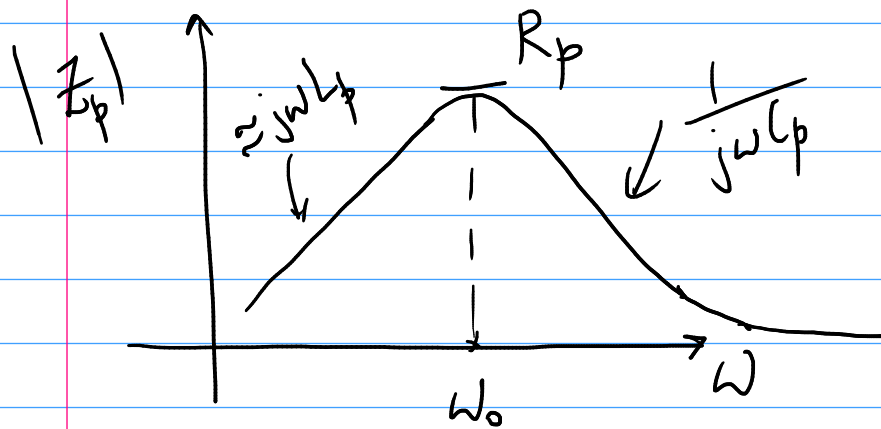


$$Q_p = \frac{R_p}{\omega_0 L_p} = \frac{R_p}{\sqrt{\frac{L_p}{C_p}}}$$


Series

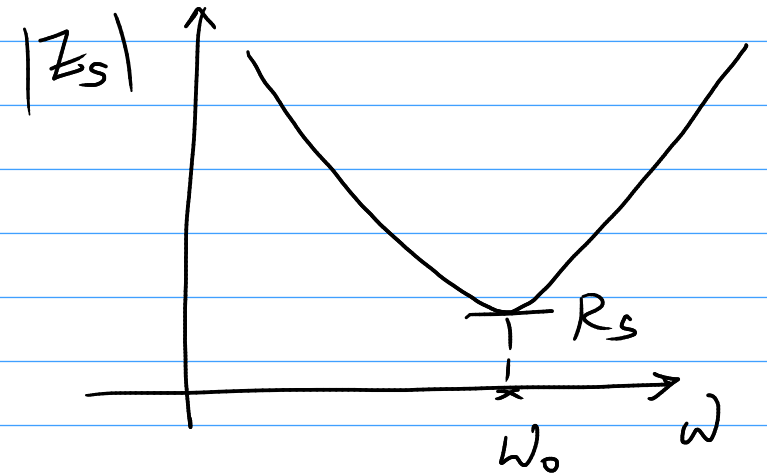


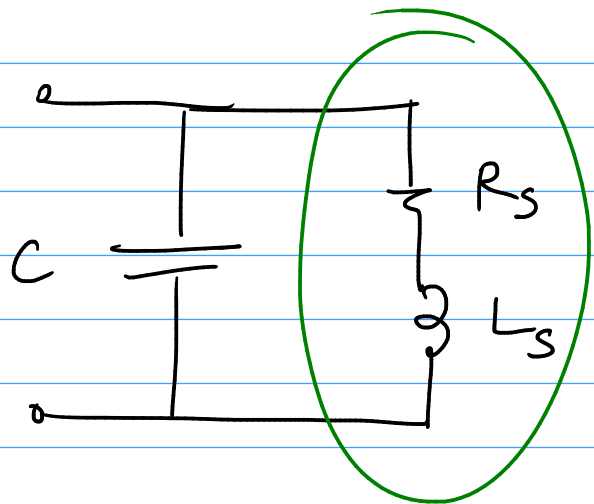
$$Q_s = \frac{\omega_0 L_s}{R_s} = \frac{\sqrt{\frac{L_s}{C_s}}}{R_s}$$




≡

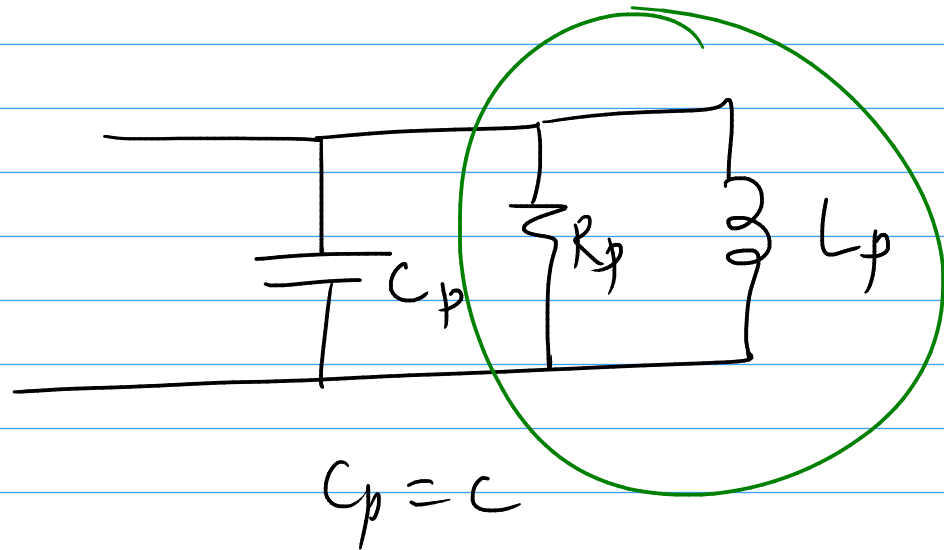

$$C_p = C$$

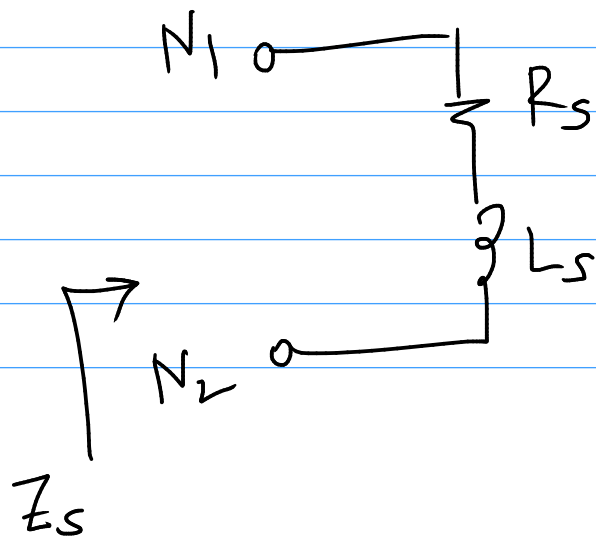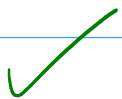

≡

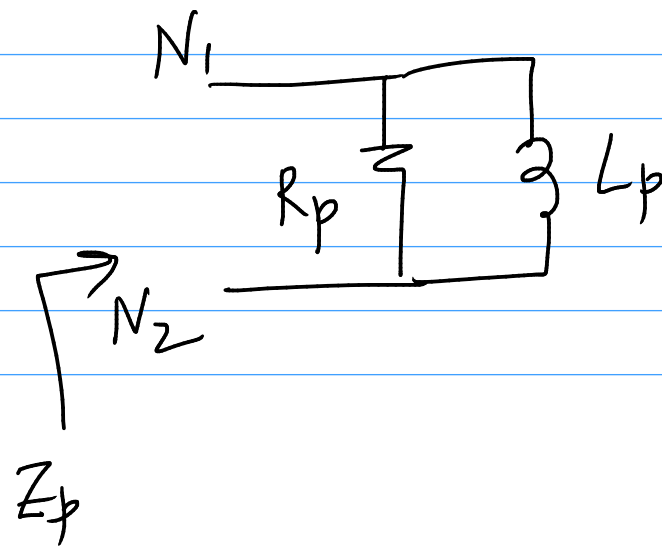

$$Z_s = R_s + j\omega L_s$$

$$Z_p = \frac{R_p \cdot j\omega L_p}{R_p + j\omega L_p}$$

$$= \frac{(R_p - j\omega L_p) \cdot j\omega L_p R_p}{R_p^2 + \omega^2 L_p^2}$$

$$= \frac{\omega^2 L_p^2 R_p}{R_p^2 + \omega^2 L_p^2} + \frac{j\omega L_p R_p^2}{R_p^2 + \omega^2 L_p^2}$$


$$Y_s(j\omega) = \frac{1}{R_s + j\omega L_s} = \frac{R_s - j\omega L_s}{R_s^2 + \omega^2 L_s^2}$$

$$Y_p(j\omega) = \frac{1}{R_p} + \frac{1}{j\omega L_p} = \frac{1}{R_p} - \frac{j}{\omega L_p}$$

$$\begin{aligned} \frac{1}{R_p} &= \frac{R_s}{R_s^2 + \omega^2 L_s^2} = \frac{1}{R_s} \cdot \frac{R_s^2}{R_s^2 + \omega^2 L_s^2} \\ &= \frac{1}{R_s} \cdot \frac{1}{1 + \omega^2 L_s^2 / R_s^2} \end{aligned}$$

$$R_p = R_s(1 + Q^2)$$

(a)

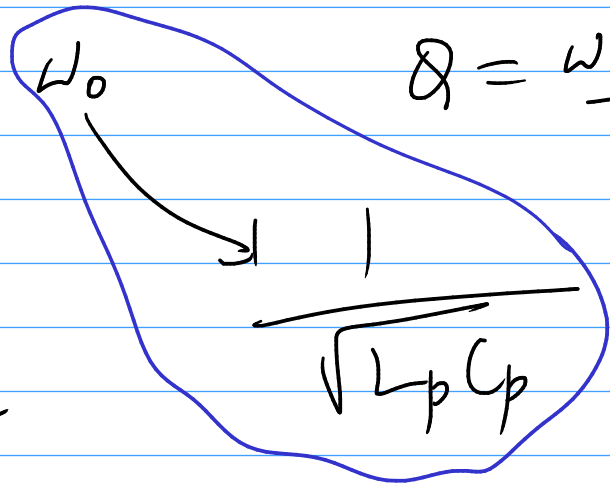


$$Q = \frac{\omega_0 L_s}{R_s}$$

$$\frac{-j}{\omega L_p} = \frac{-j\omega L_s}{R^2 + \omega^2 L_s^2}$$

$$\frac{1}{\omega L_p} = \frac{1}{\omega L_s} \cdot \frac{\omega^2 L_s^2}{R^2 + \omega^2 L_s^2}$$


$$L_p = L_s \frac{(1 + Q^2)}{Q^2}$$

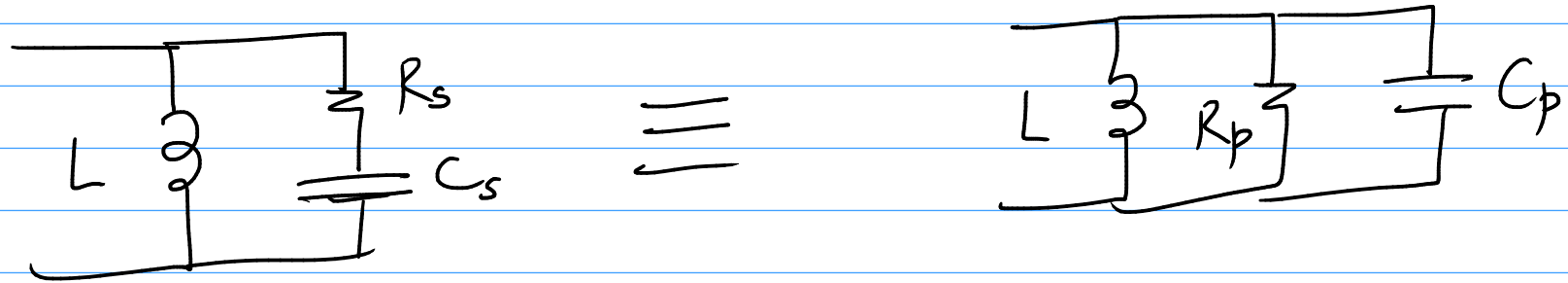


$$Q = \frac{1}{\omega R_s C_s}$$


$$R_p = R_s (1 + Q^2)$$

$$C_p = C_s \cdot \frac{Q^2}{1 + Q^2}$$

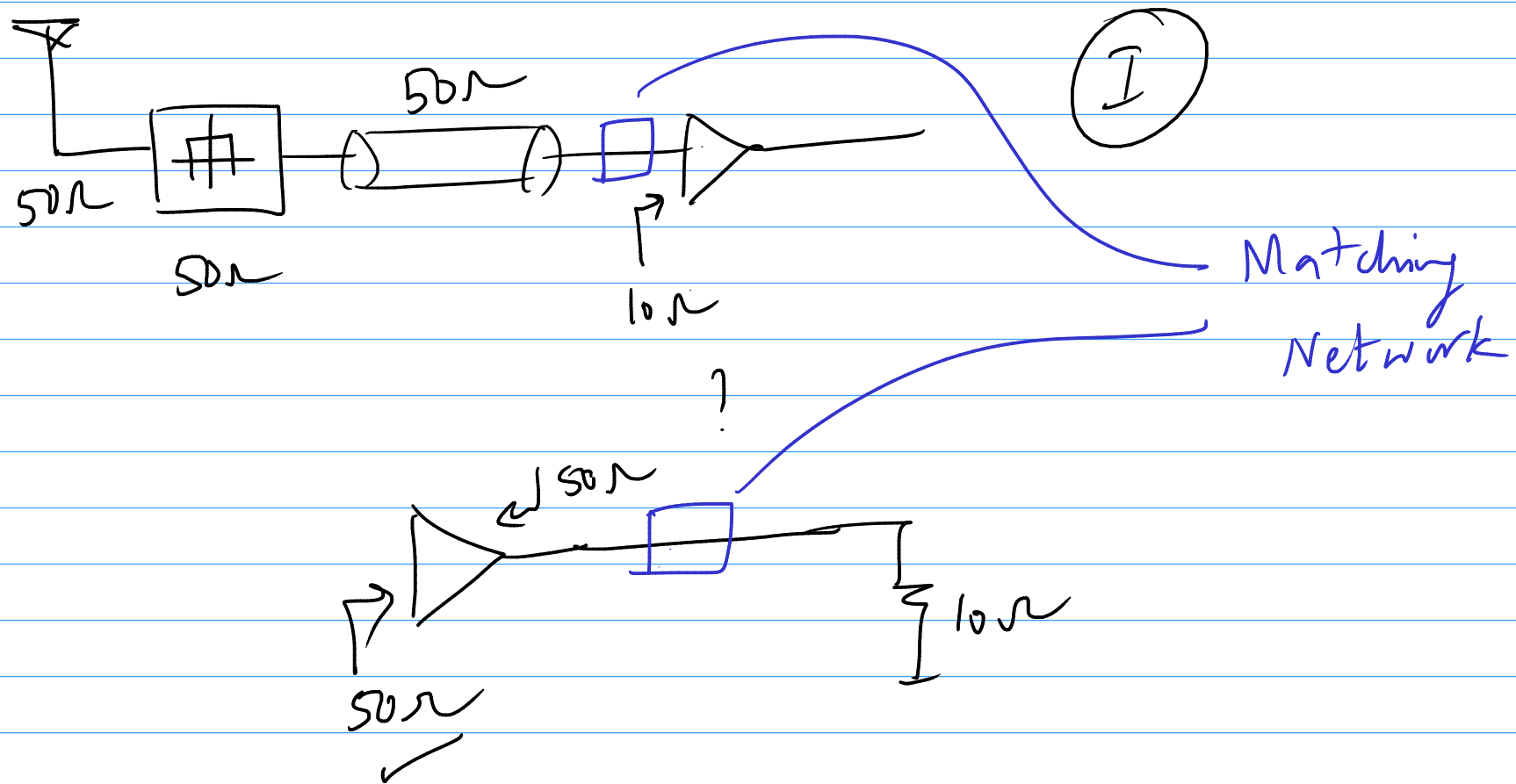

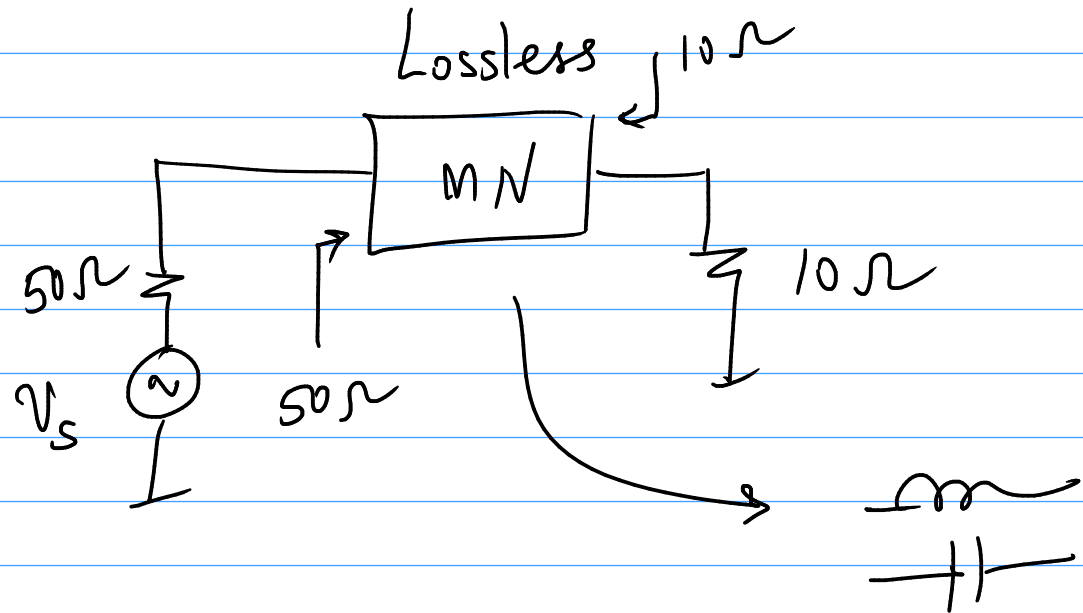


1)


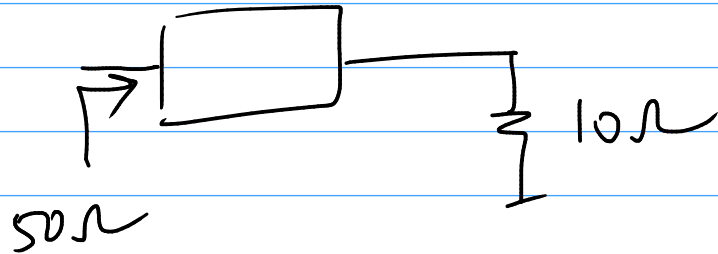


2)  $\omega_0 = \text{desired freq.}$

$$\frac{R_L}{R_S} \text{ i.e. } Q$$

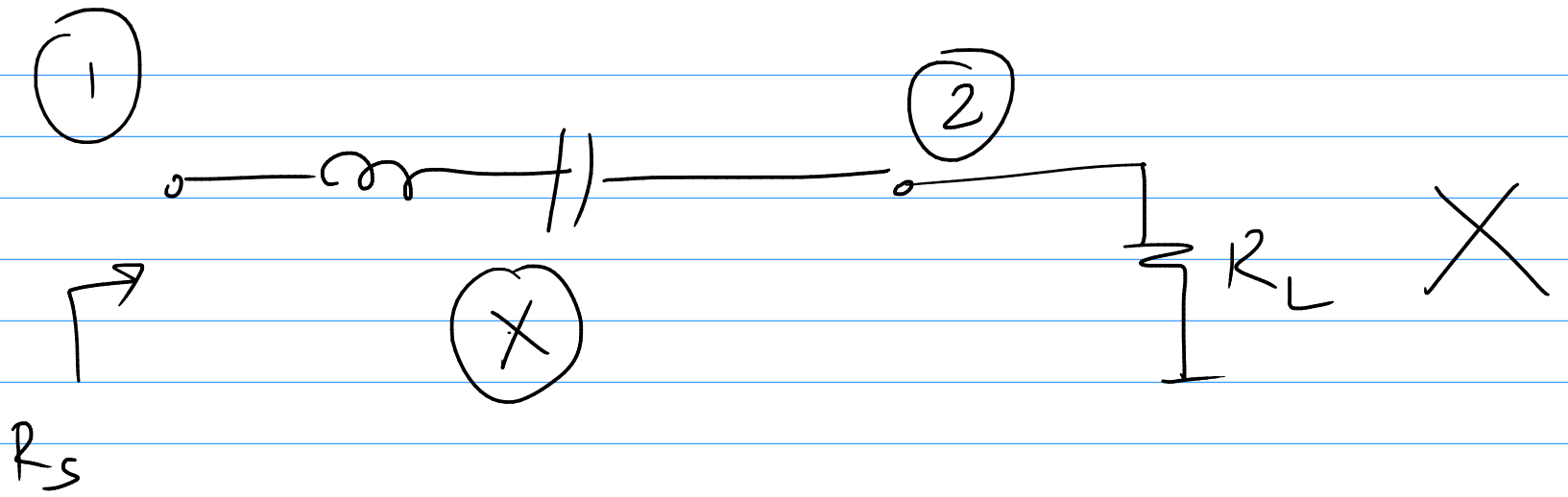


A & B  
Upward  
matching network

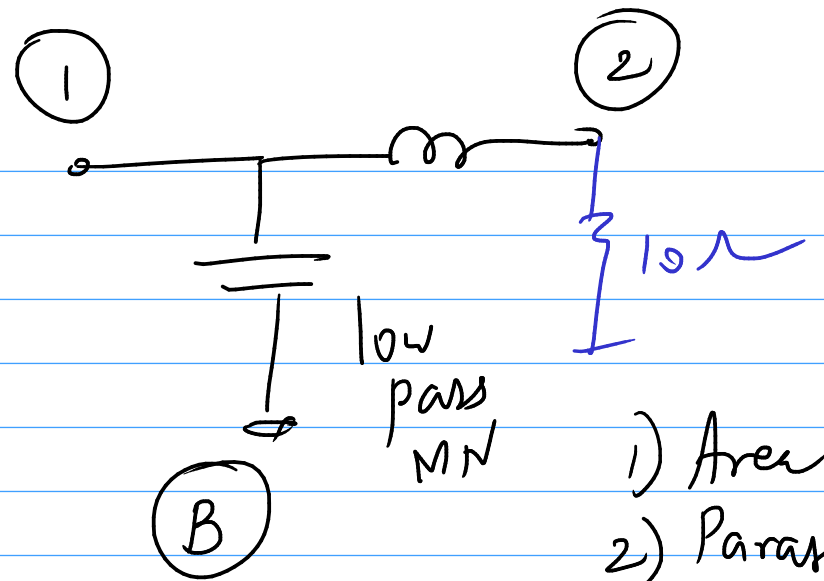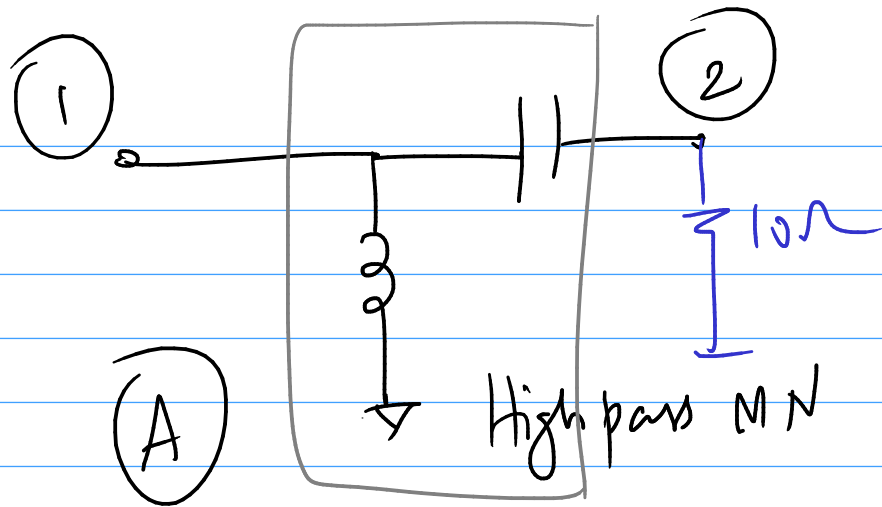




- 1) Area
- 2) Parasitics
- 3)

C & D  
downward  
MN.

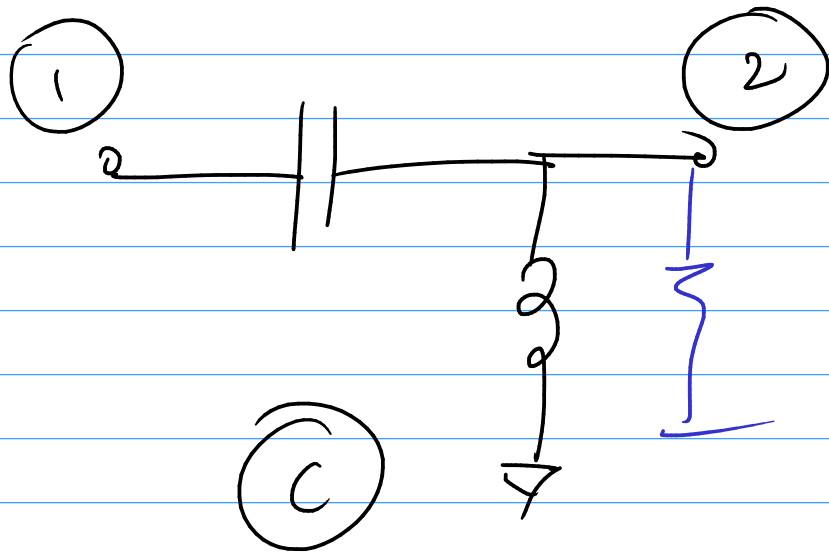

"L-match"  
Networks

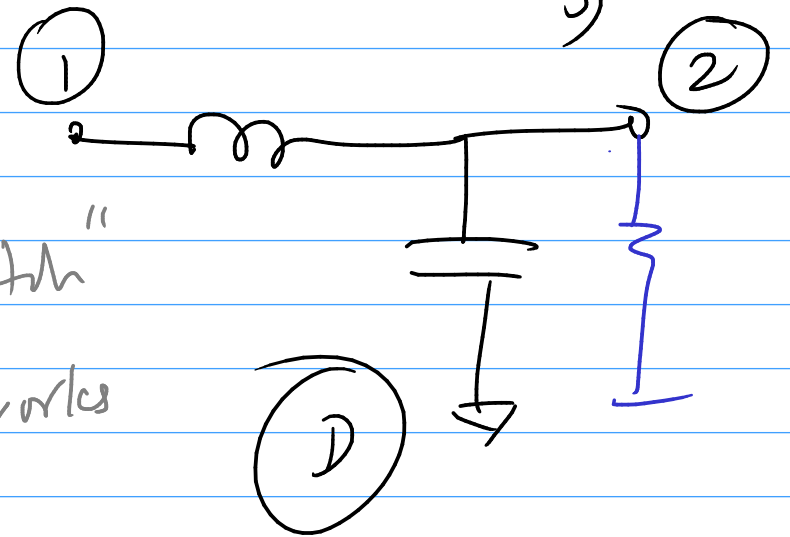


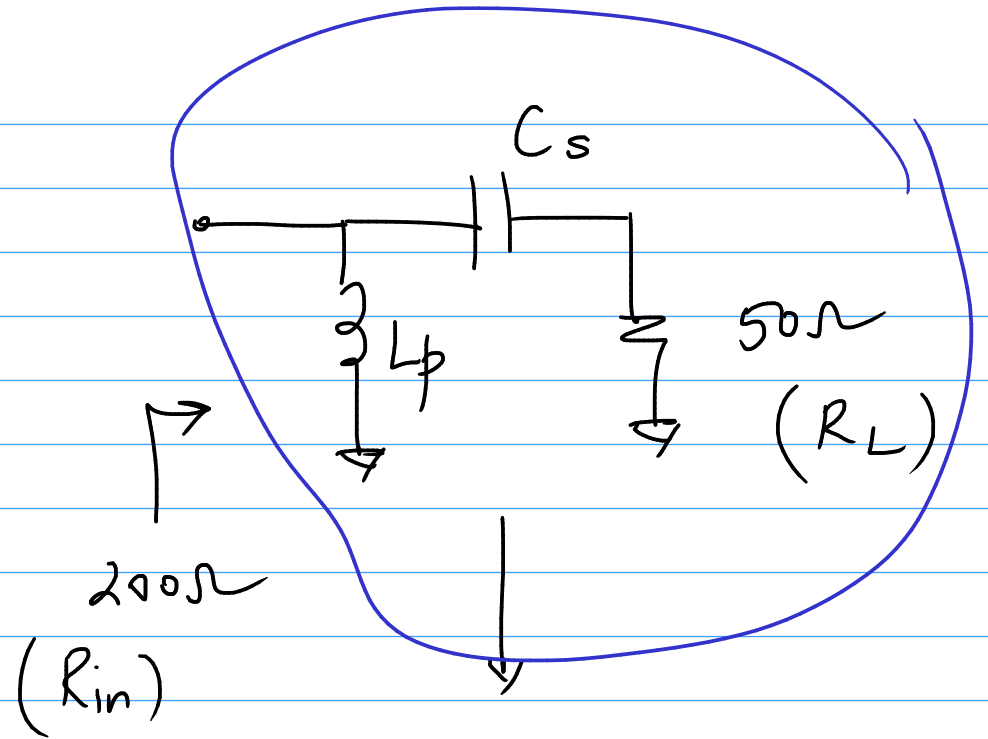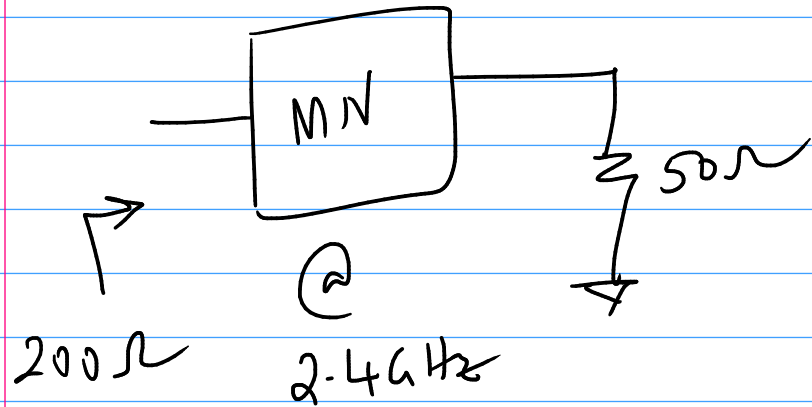

$$R_p = R_{in}$$

$$\omega_0 = \frac{1}{\sqrt{L_p C_p}}$$
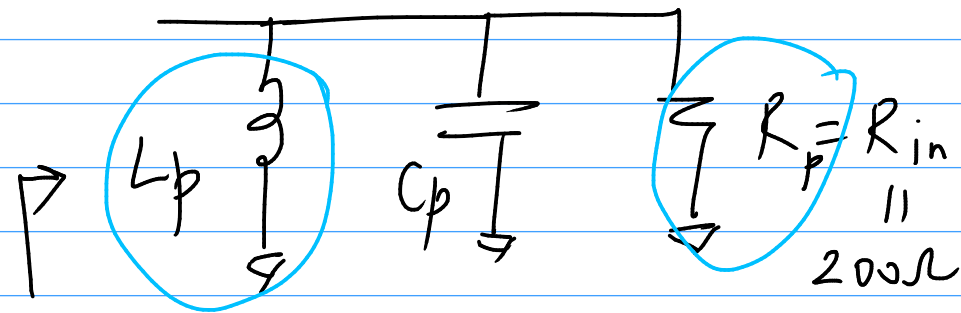
$$Q = \sqrt{\frac{R_p}{R_s} - 1} = \sqrt{3} = 1.73$$




$$\frac{R_p}{\omega_0 L_p} = Q = \sqrt{3} \Rightarrow L_p = 7.66 \text{ nH}$$

$$\omega_0 = 2\pi \times 2.4 \text{ GHz}$$

$$\omega_0 = \frac{1}{\sqrt{L_p C_p}} \Rightarrow C_p = 575 \text{ fF}$$
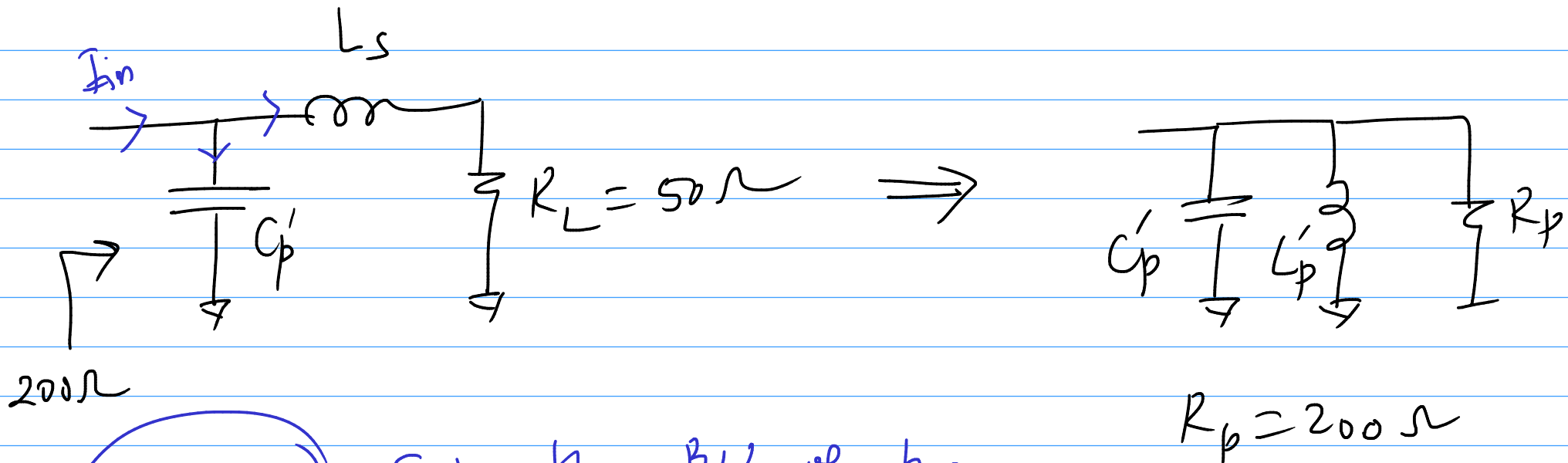
$$C_s = C_p \cdot \frac{(1+Q^2)}{Q^2} = 766 \text{ fF}$$





$200 \Omega$

$$Q = \sqrt{3}$$

Sets the BW of the Match


$$Q = \omega_0 C_p' R_p \Rightarrow 1.732 = 2\pi \times 2.4 \text{ GHz} \times C_p' \times 200$$

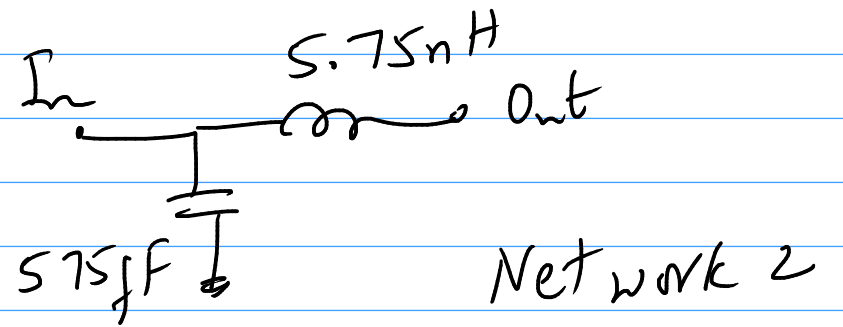
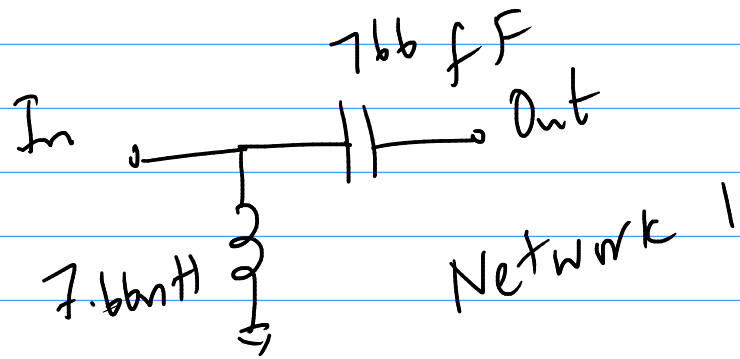
$$C_p' = 575 \text{ fF} \Rightarrow L_p' = 7.66 \text{ nH} \Rightarrow L_s = 5.75 \text{ nH}$$




Choice

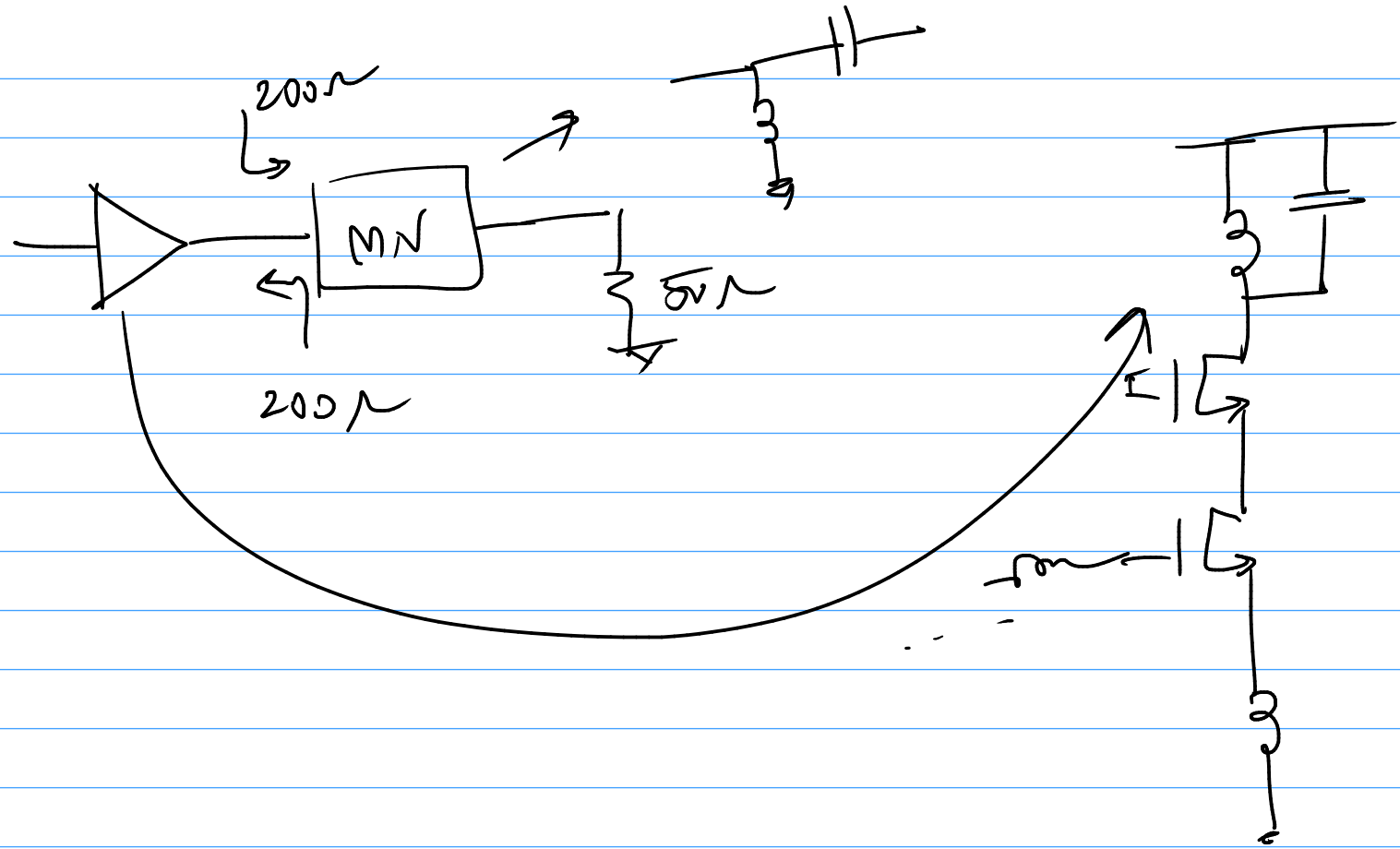
- 1) 2 has lower area ✓
- 2) 1 →  $I_n$  is <sup>DC</sup> shorted to gnd  
Out is ac coupled to  $I_n$
- 2 → Out is dc coupled to  $I_n$
- 3) Absorb <sup>(portion of)</sup> MW into circuit



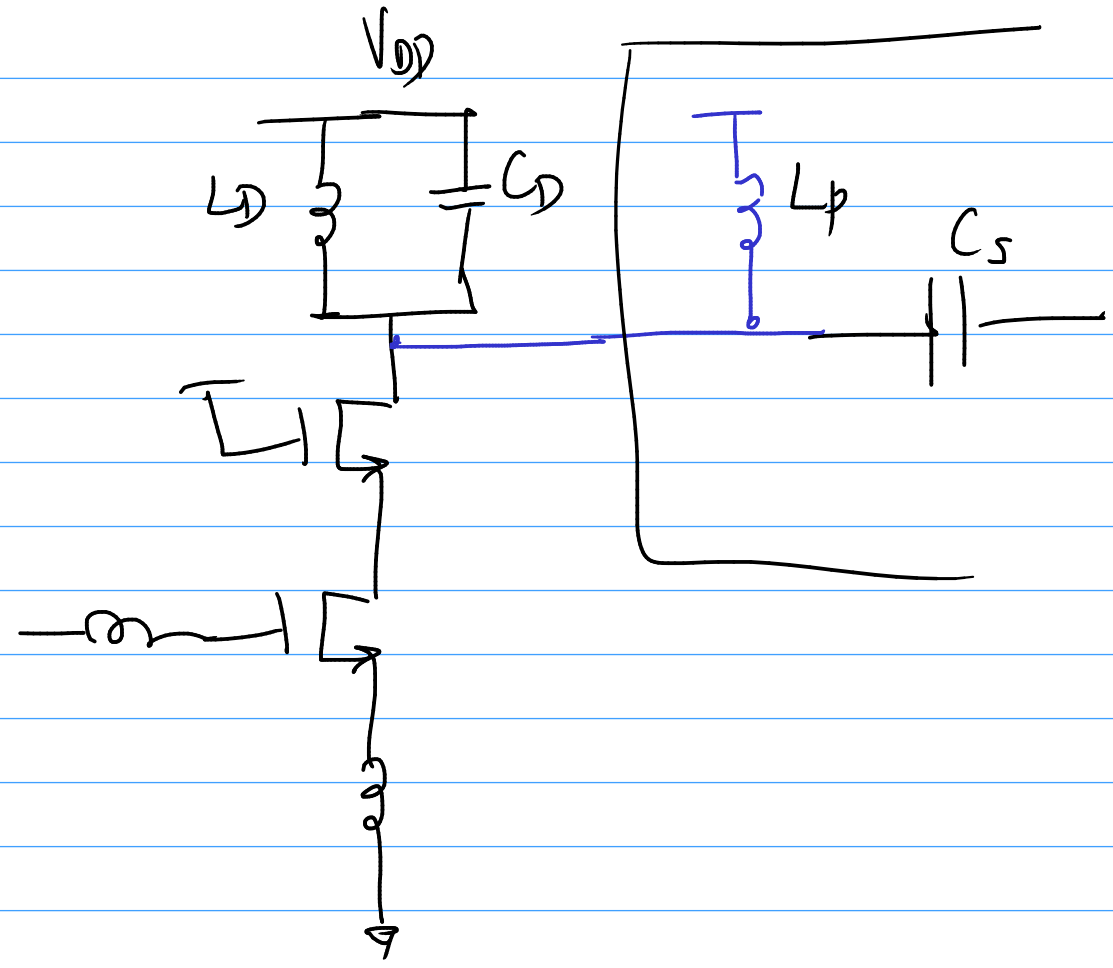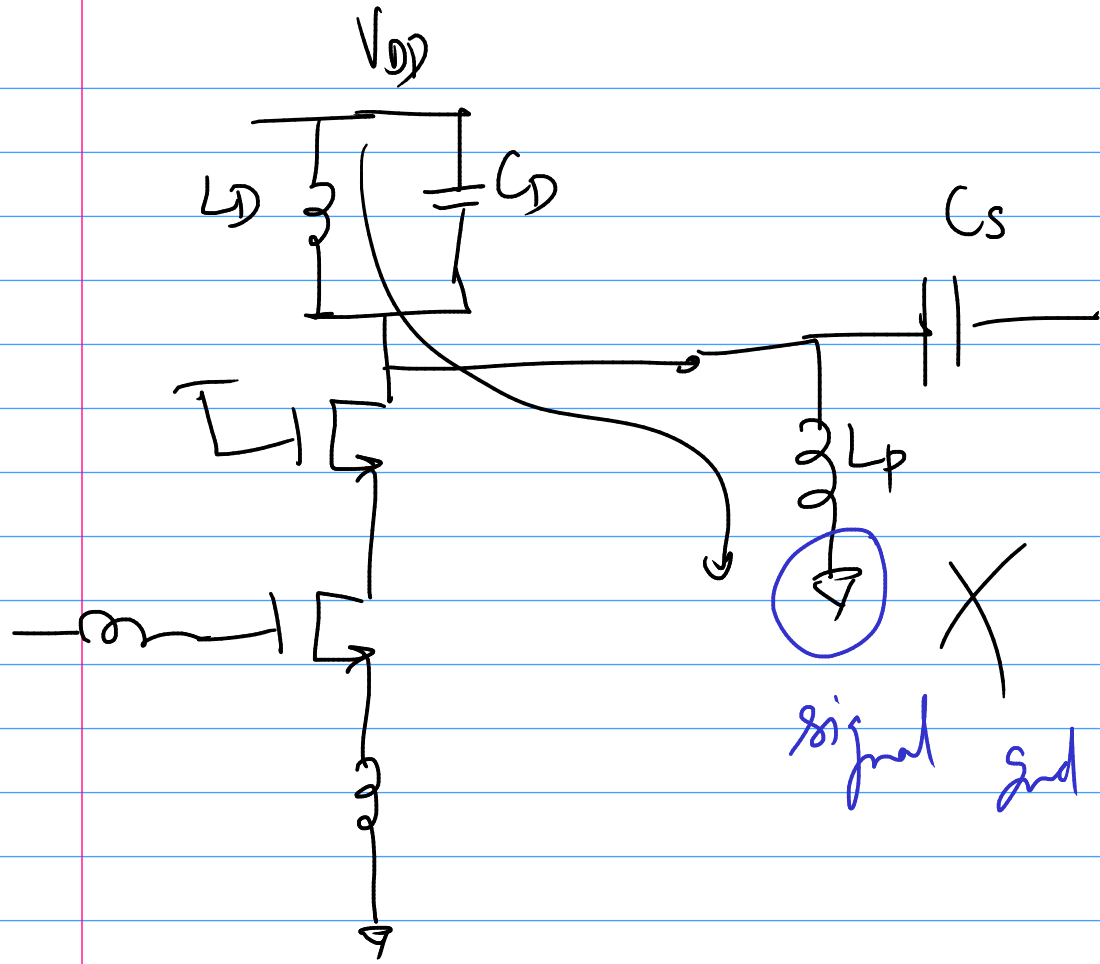

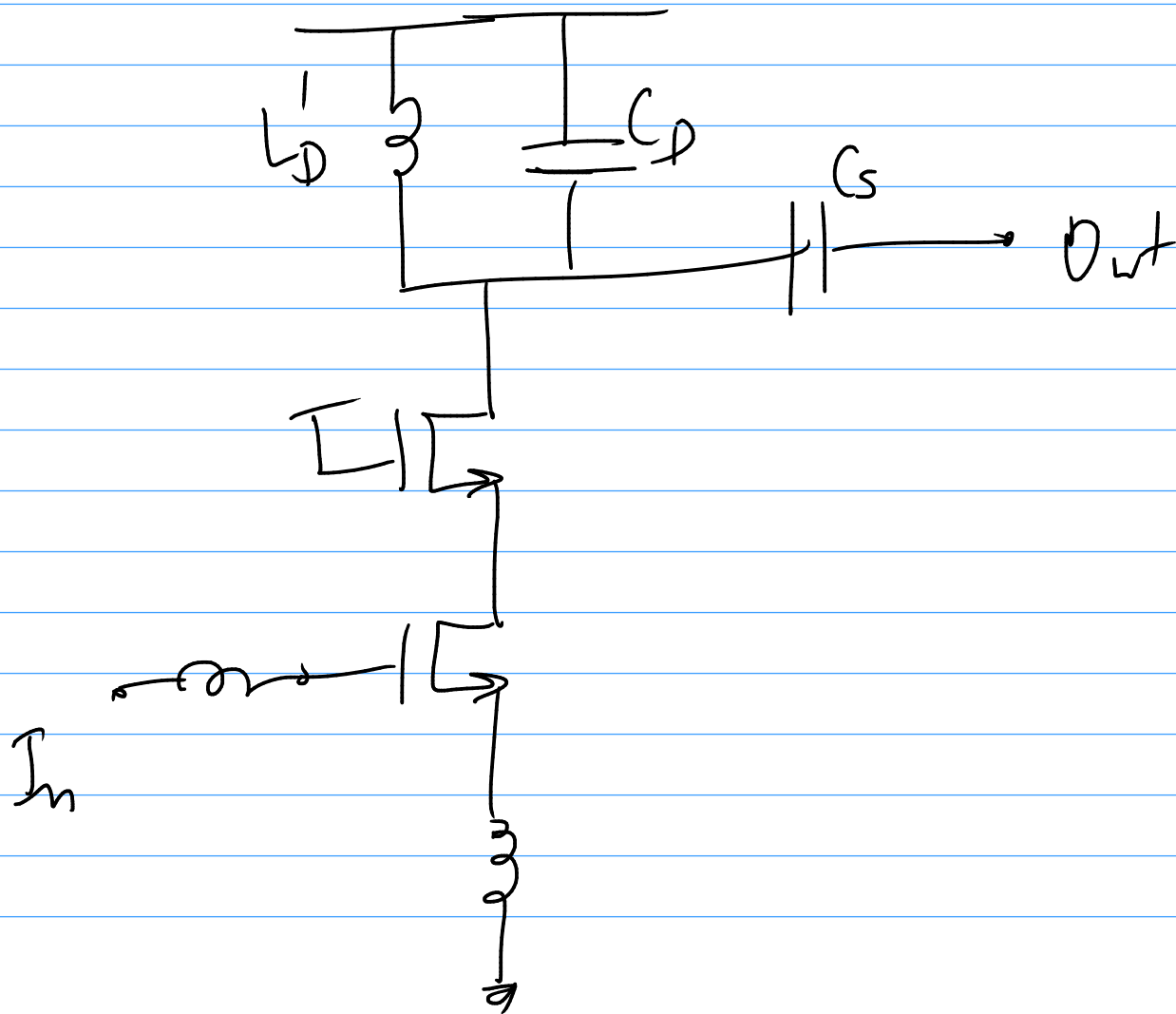


$$L_D' = L_D \parallel L_p$$

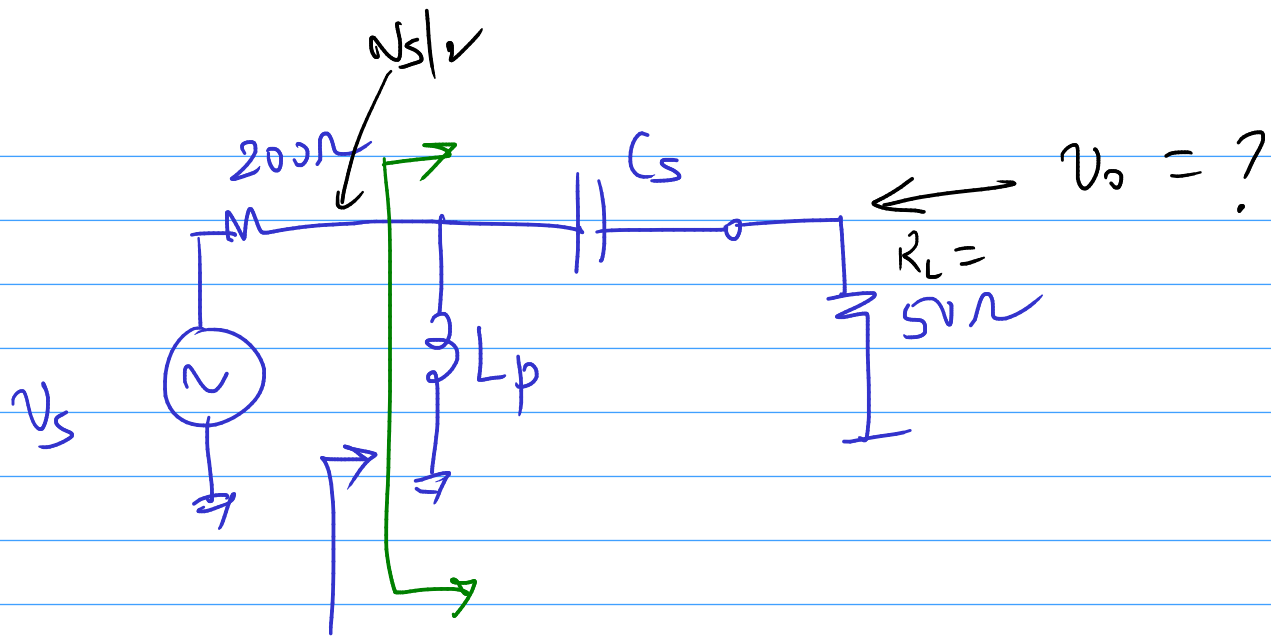


$$R_{in} = 200\Omega$$

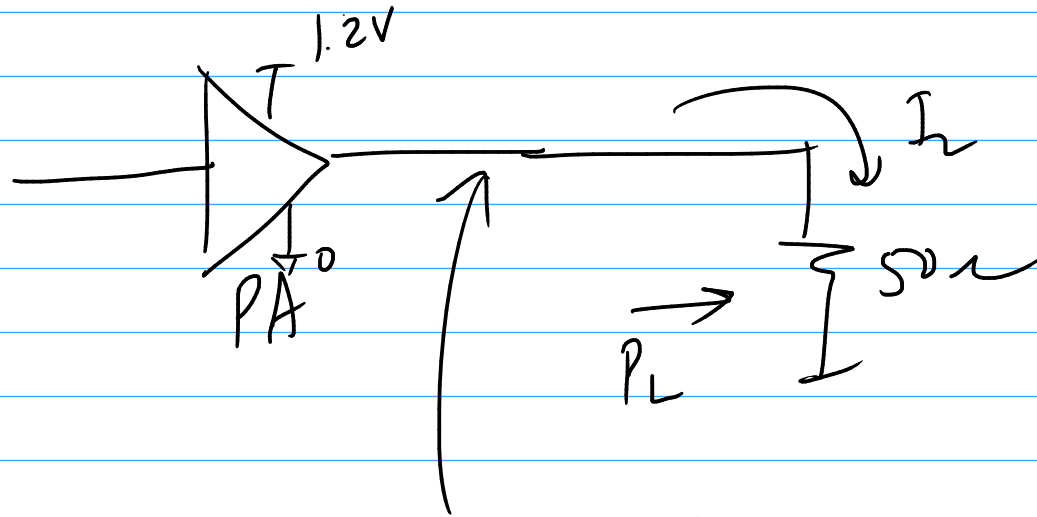
$$\frac{\left(\frac{v_s}{2}\right)^2}{2} \times \frac{1}{R_{in}} = \frac{v_o^2}{2R_L} \Rightarrow v_o = \frac{v_s}{4}$$



$$P_L = \frac{1^2}{2} \times \frac{1}{50\Omega}$$

$$= 10\text{mW}$$

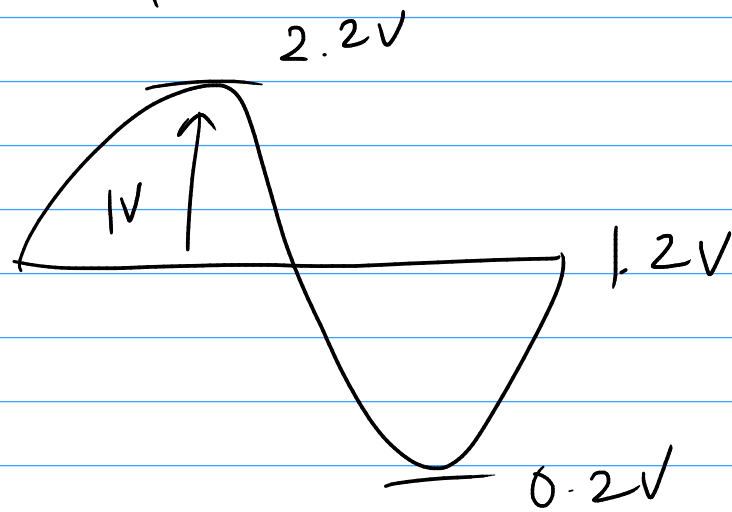


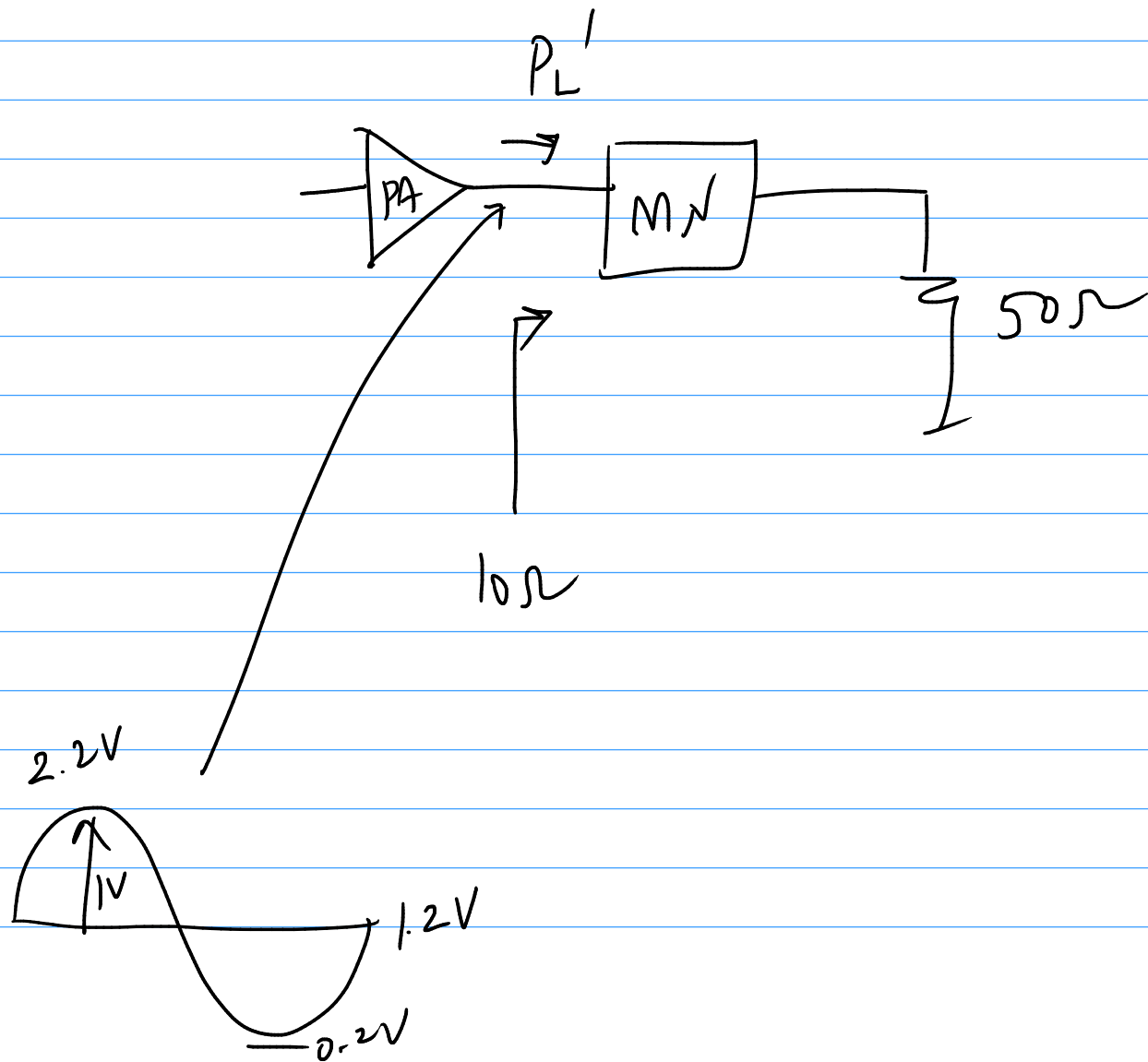


$$P_L' = \frac{1^2}{2} \times \frac{1}{10\Omega}$$

$$= 50mW$$

@ 2.4 GHz

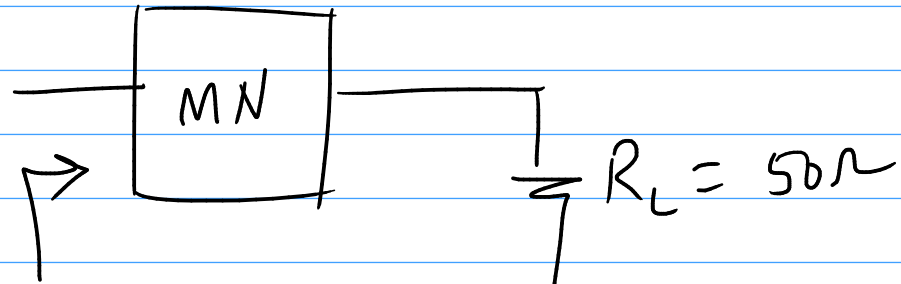




$R_{in} = 200\Omega$

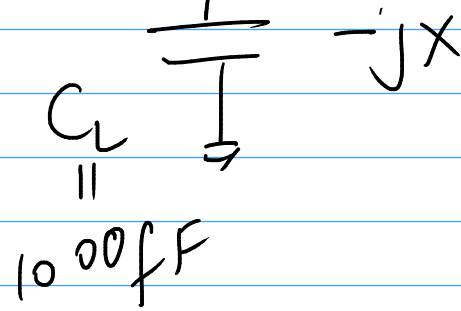



$L_p = 7.66\text{nH}$

$C_s' = 766\text{fF} = C_s \parallel C_L$

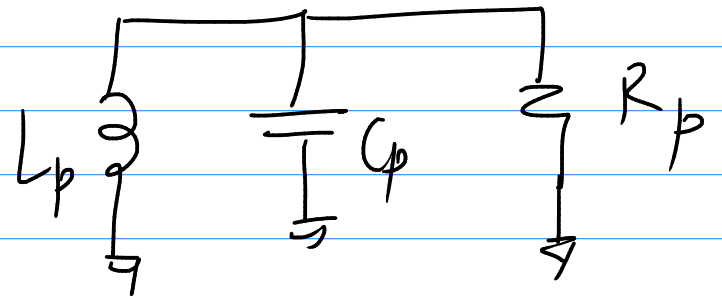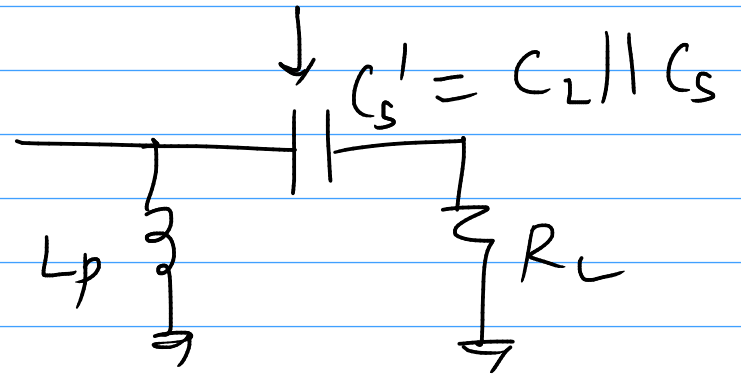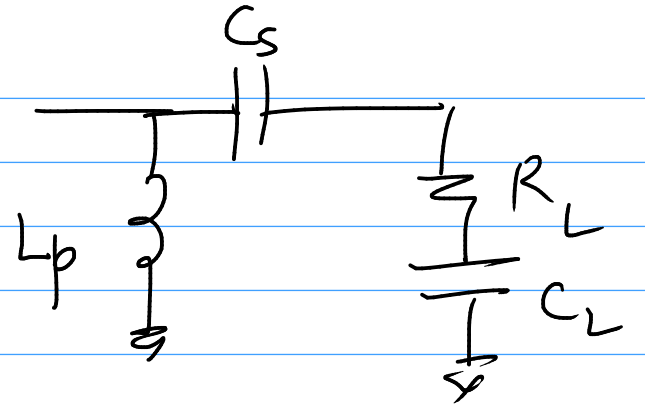
$$\frac{1}{766\text{fF}} = \frac{1}{C_s} + \frac{1}{C_L (= 1000\text{fF})}$$



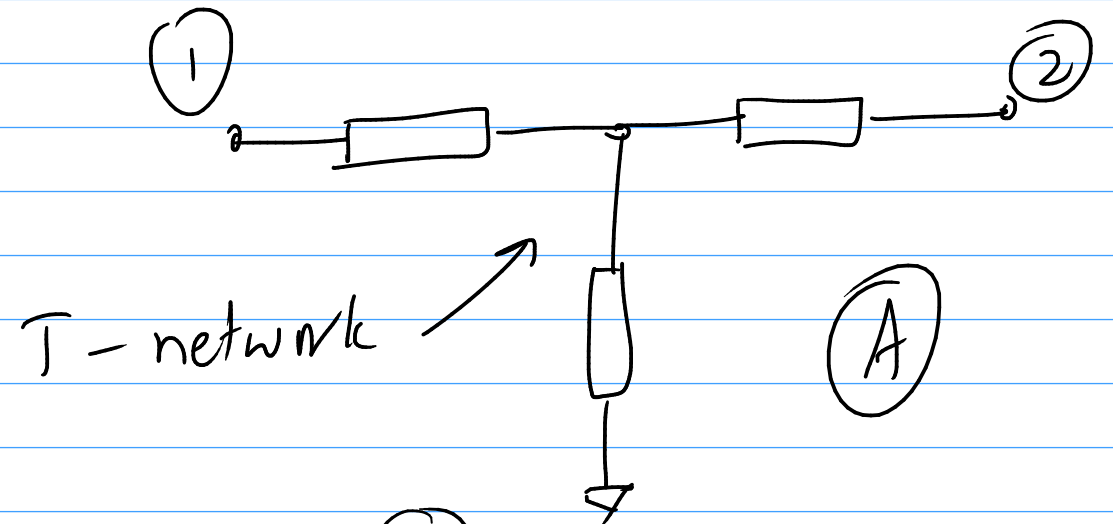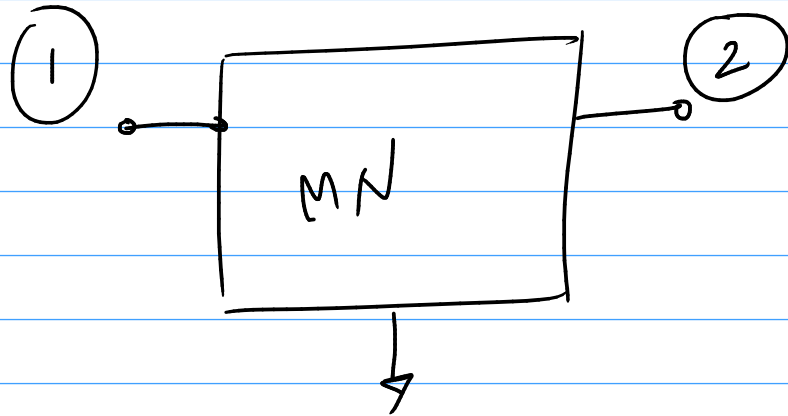
Want to set  $Q$ ,  $\frac{R_p}{R_s}$ ,  $f_0 \rightarrow$  3 element match




T-network

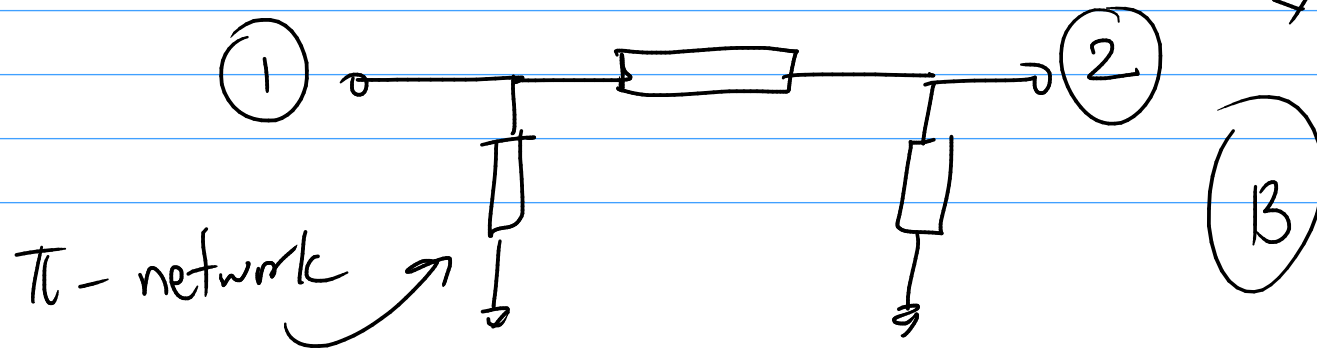


$\pi$ -network

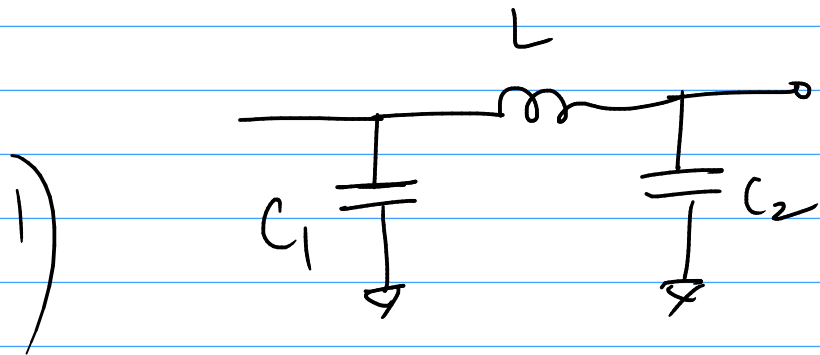


Low pass

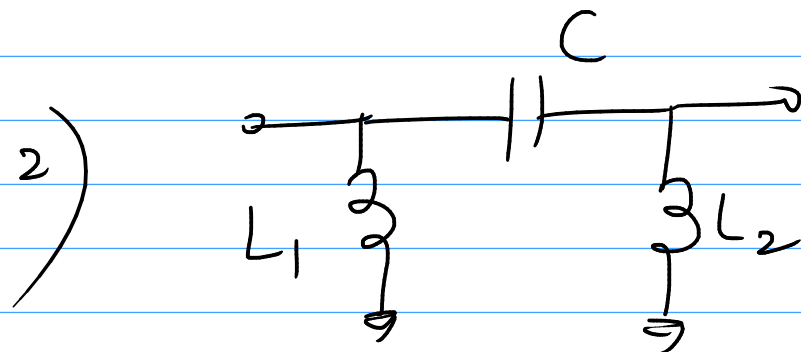

High pass


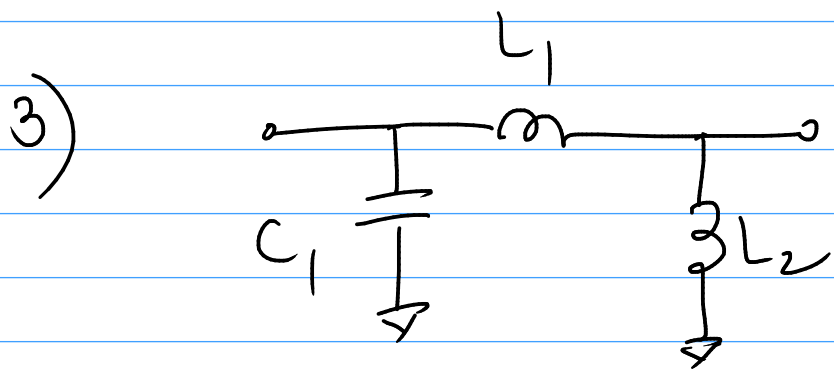


tapped -ind. MN



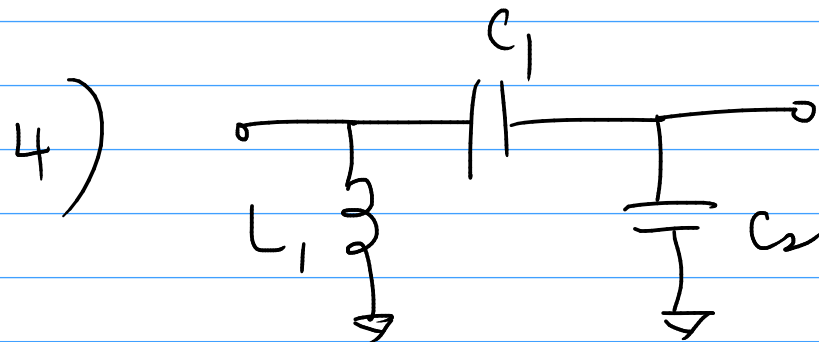


tapped cap. MN




$\pi$ -match  
 $R_I < R_{in}, R_L$

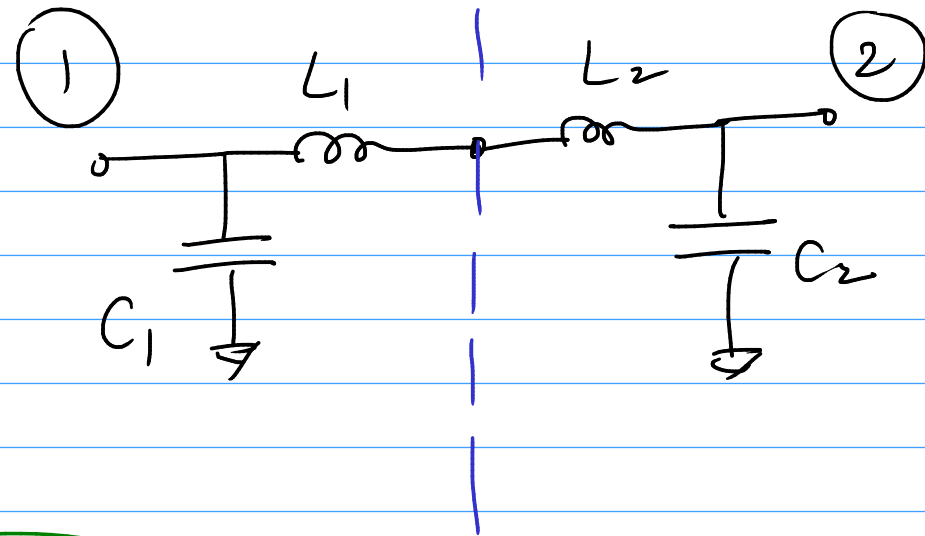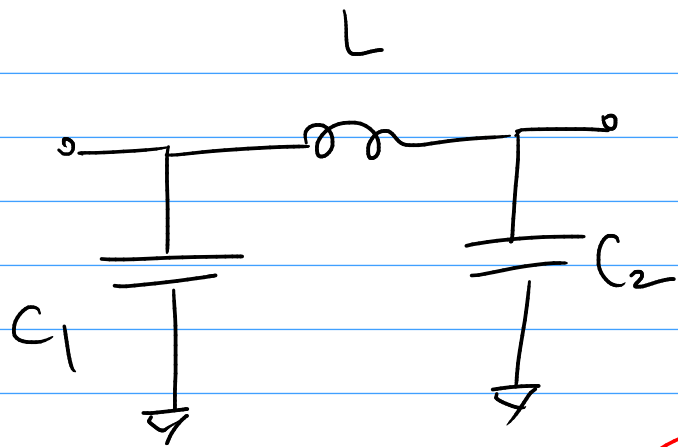


$R_{in}$

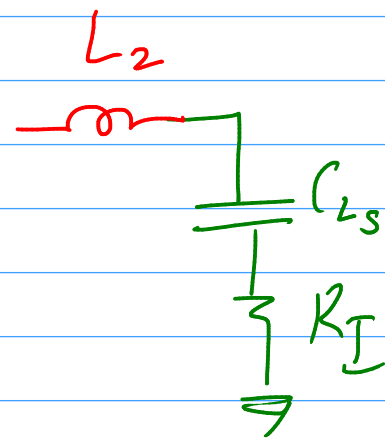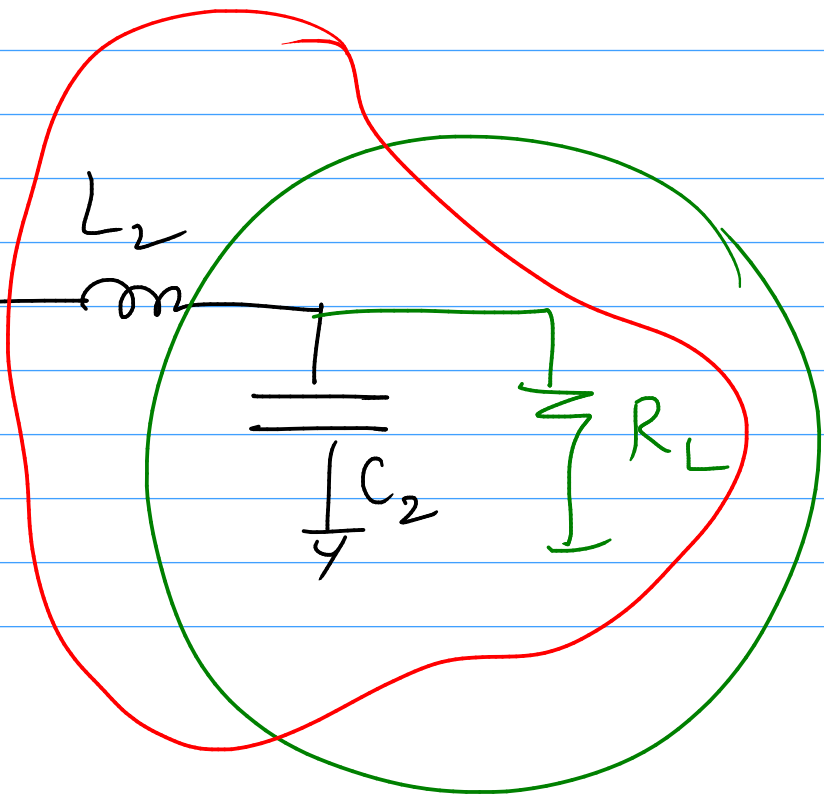
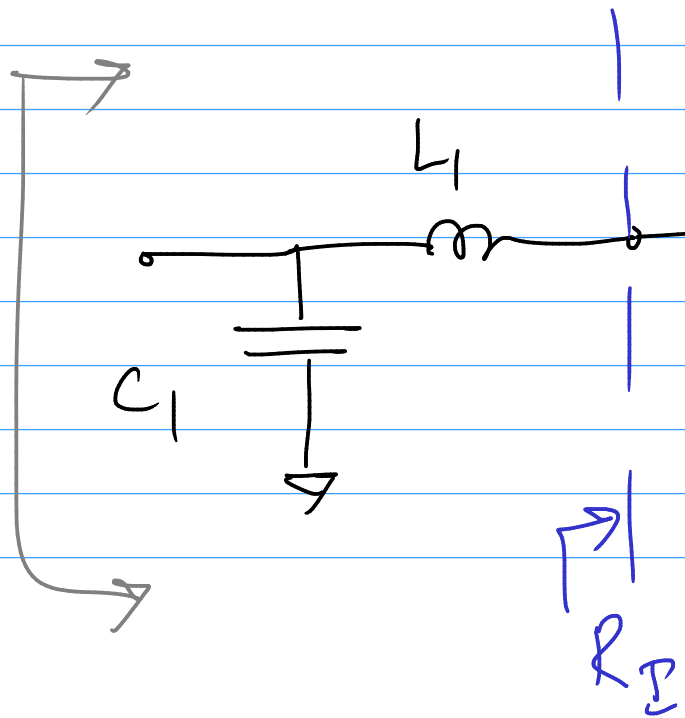


# T-match Networks

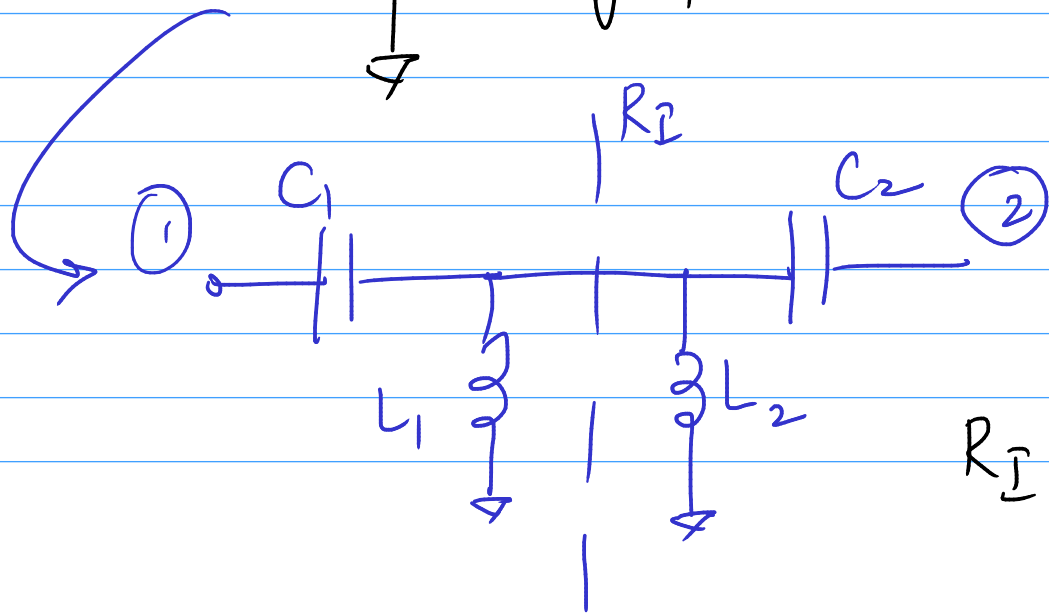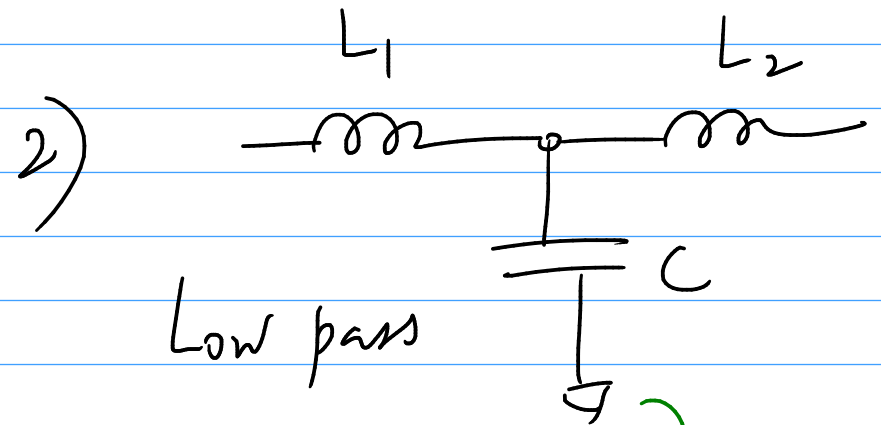
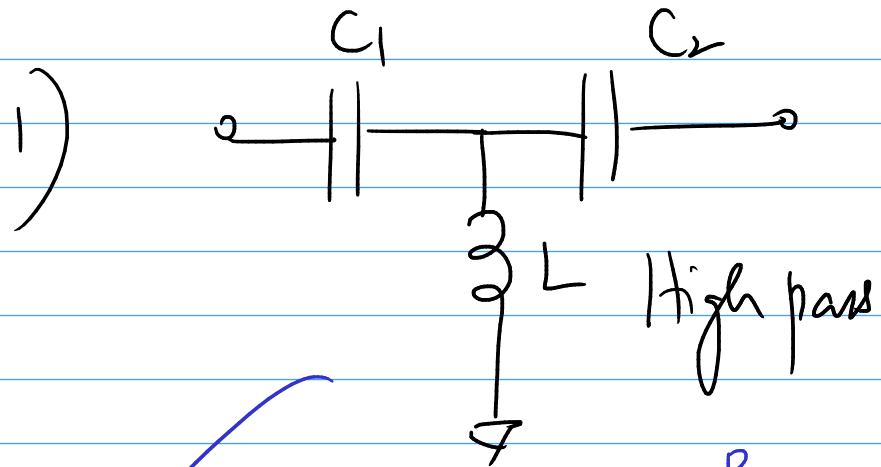


$$R_J > R_{in}, R_L$$

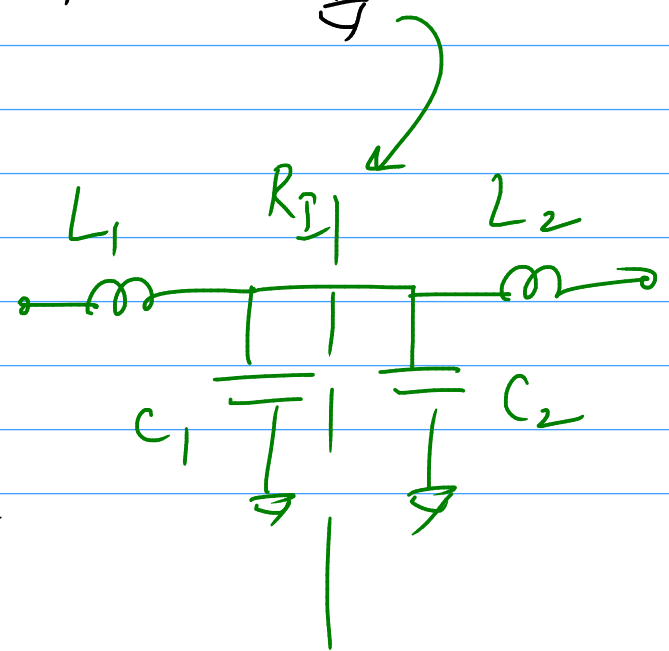

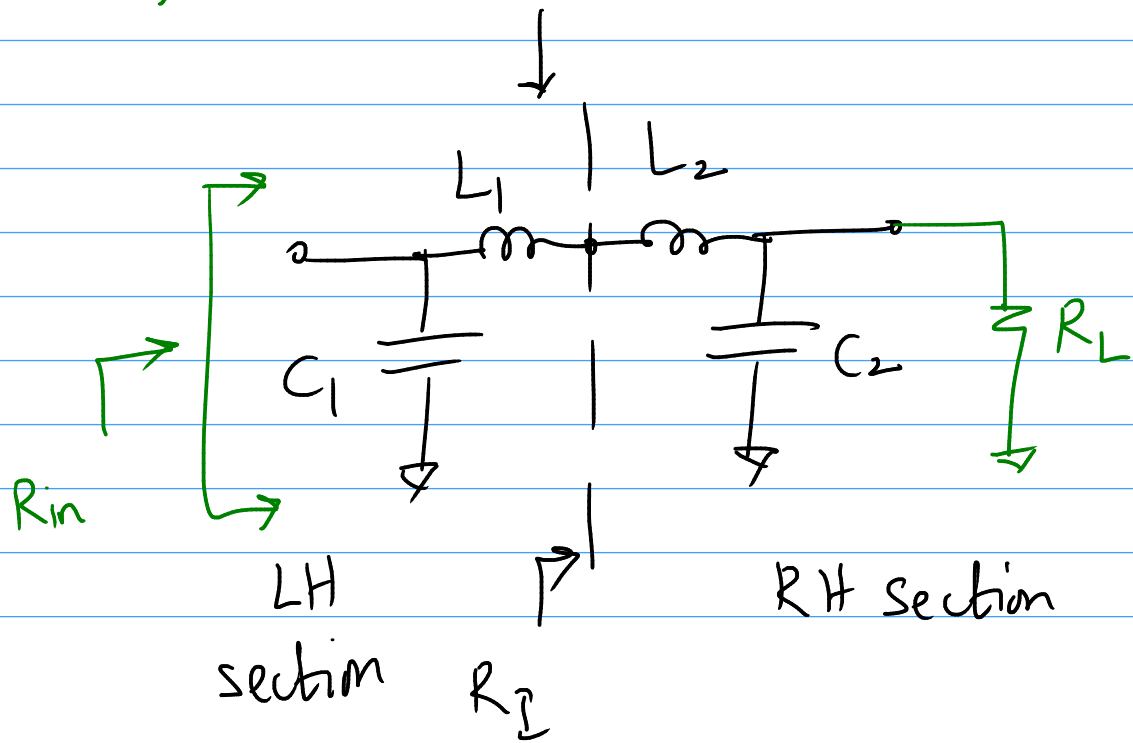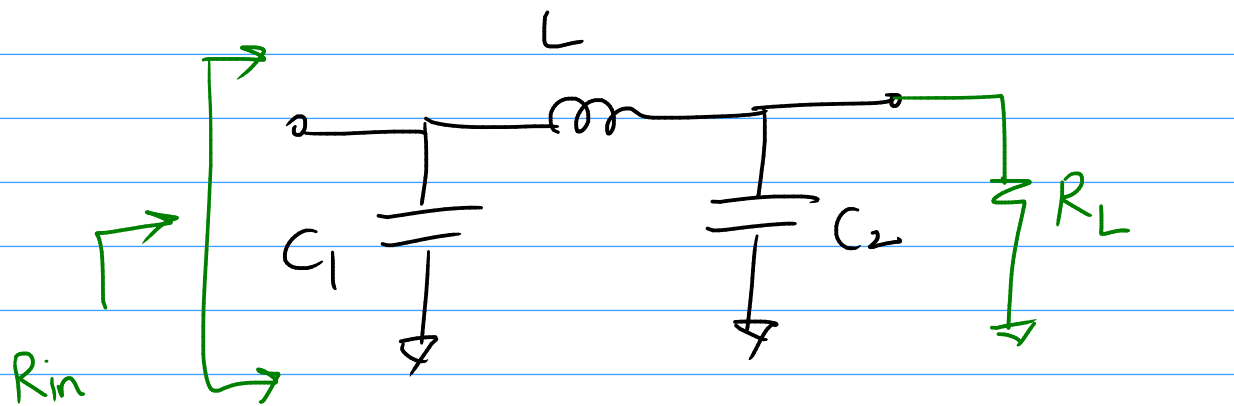


RH Section

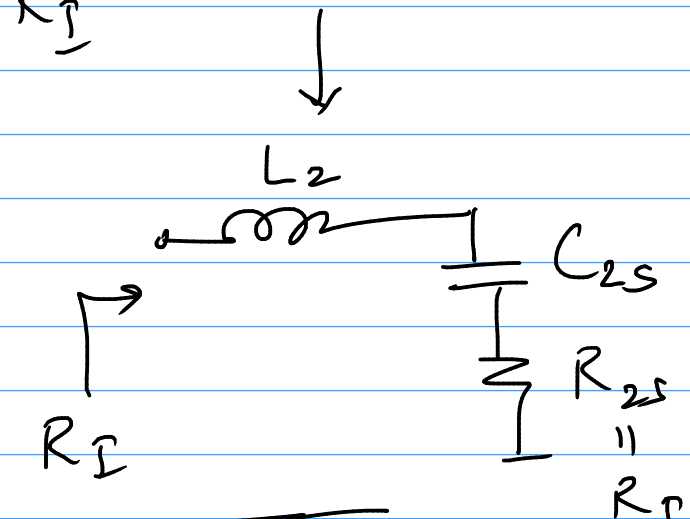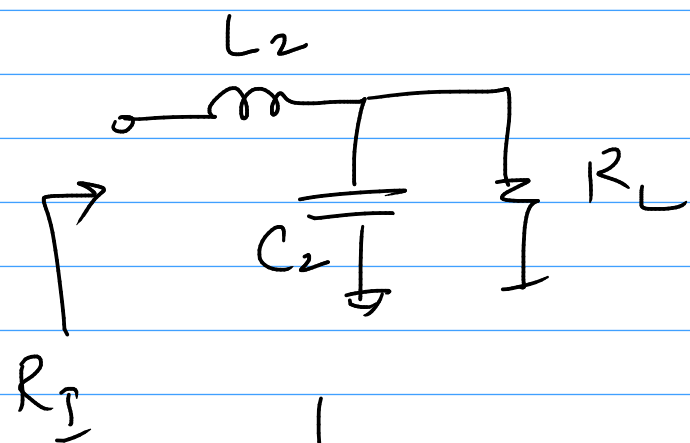

$$Q_R = \sqrt{\frac{R_L}{R_I} - 1} = \frac{\omega_0 L_2}{R_I}$$

LH Section

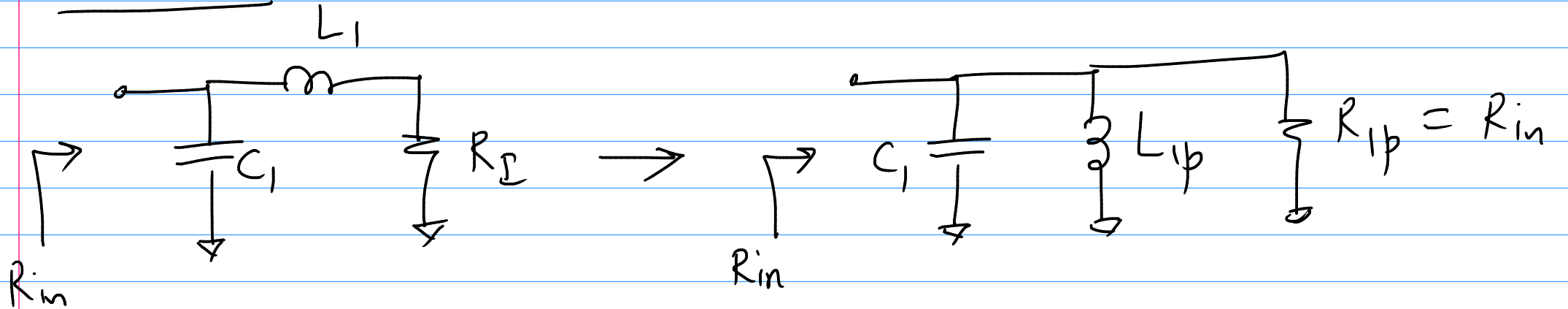

$$Q_L = \sqrt{\frac{R_{in}}{R_I} - 1} = \omega_0 C_1 R_{in} = \frac{\omega_0 L_1}{R_I}$$

$$\omega_0 = \frac{1}{\sqrt{L_2 C_2}} \quad ; \quad \omega_0 = \frac{1}{\sqrt{C_1 L_{1p}}}$$

$$Q_{total} = Q_L + Q_R$$


$$Q_{\text{total}} = \frac{\omega_0 (L_1 + L_2)}{R_I}$$

$$Q_{\text{tot.}} = \sqrt{\frac{R_{\text{in}}}{R_I} - 1} + \sqrt{\frac{R_L}{R_I} - 1}$$

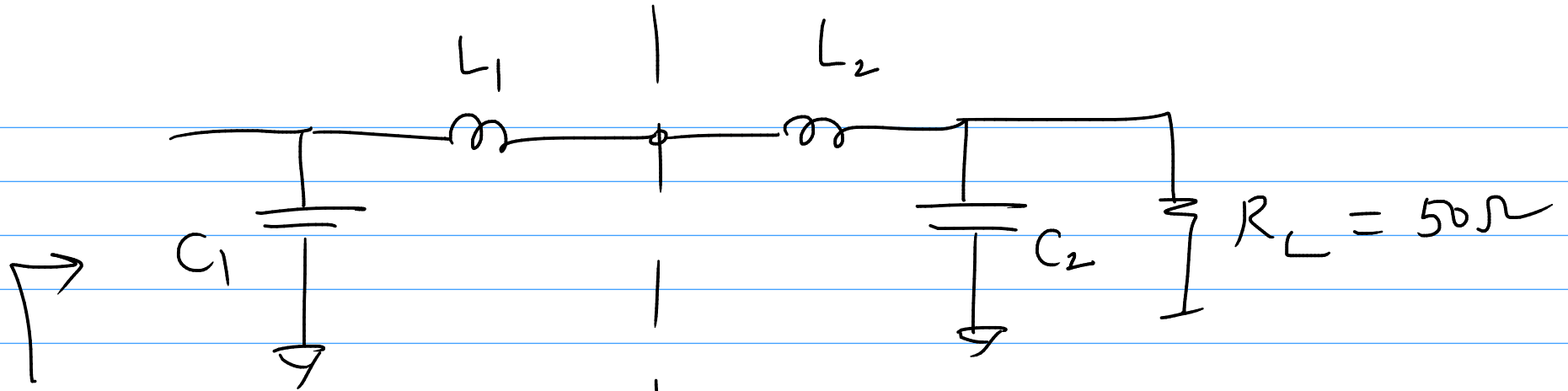Example 1  $R_L = 50 \Omega$ ,  $R_{\text{in}} = 200 \Omega$ ,  $f_0 = 2.4 \text{ GHz}$ ,  $Q = 10$

$$Q = Q_L + Q_R$$

$$10 = \sqrt{\frac{200}{R_I} - 1} + \sqrt{\frac{50}{R_I} - 1} \Rightarrow \underline{\underline{R_I = 4.3 \Omega}}$$



$$R_{in} = 200 \Omega$$

$$Q_L = 6.74$$

$$R_I = 4.3 \Omega$$

$$Q_R = 3.26$$

$$C_2 = \frac{Q_R}{\omega_0 R_L}$$

$$= 4.32 \text{ pF}$$

$$L_2 = \frac{Q_R \cdot R_I}{\omega_0}$$


$$= 0.93 \text{ nH}$$

$$C_1 = \frac{Q_L}{\omega_0 R_{in}}$$


$$= 2.23 \text{ pF}$$

$$L_1 = \frac{R_I Q_L}{\omega_0}$$

$$= 1.92 \text{ nH}$$

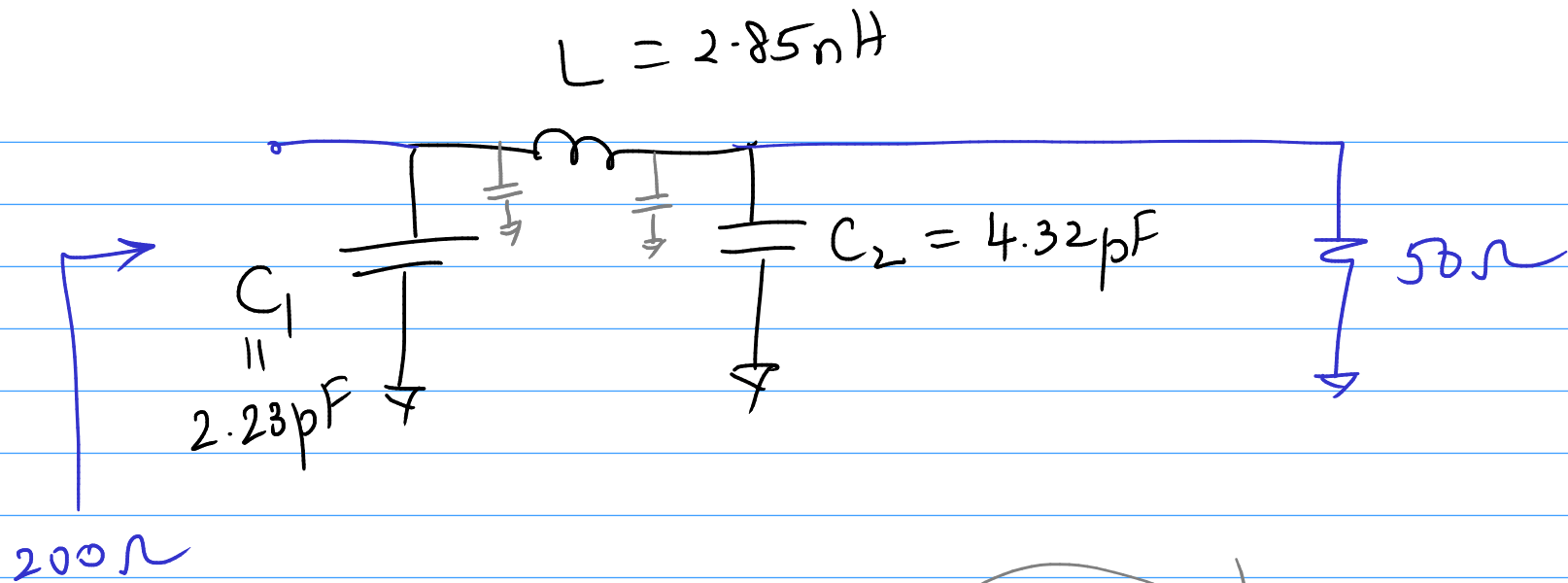



HW

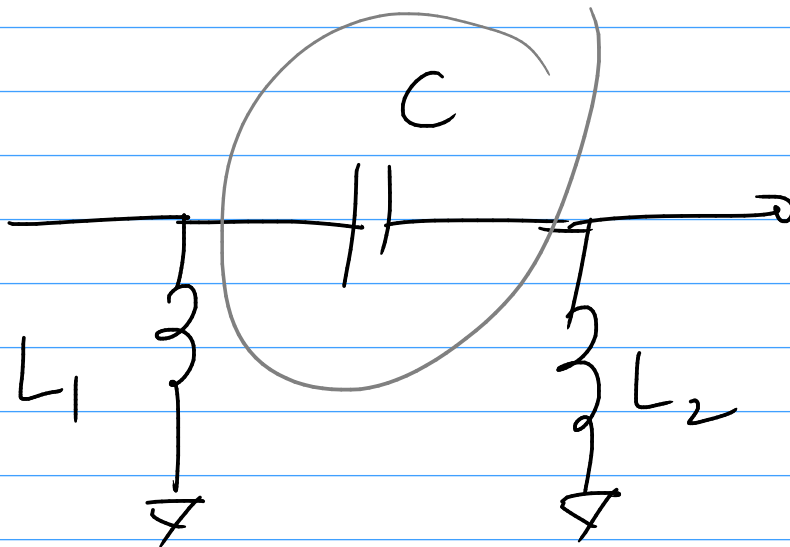

Example 2

$R_L = 50\Omega$ ,  $R_{in} = 200\Omega$ ,  $f_0 = 2.4\text{ GHz}$ ,  $Q = 10$

T-match

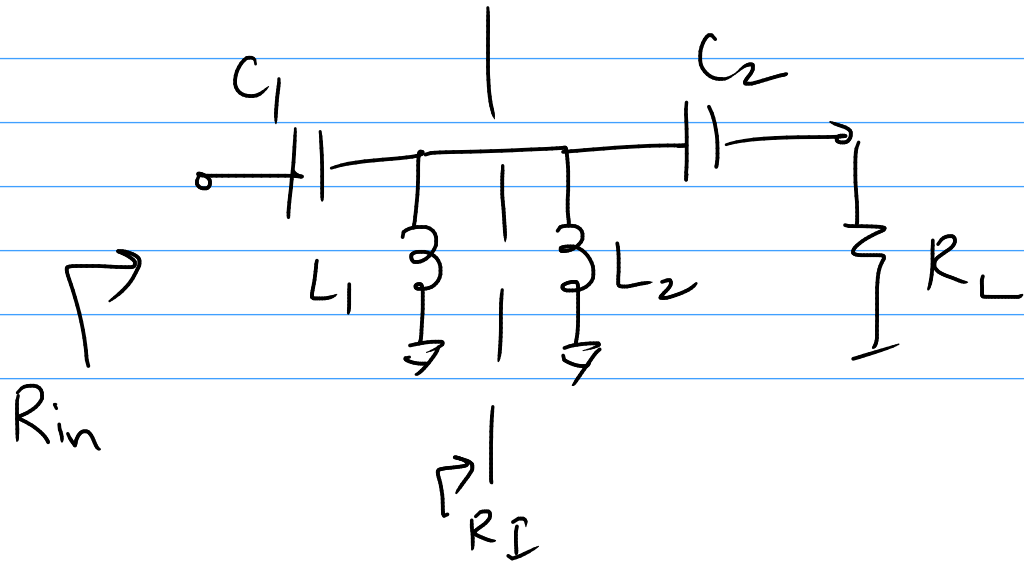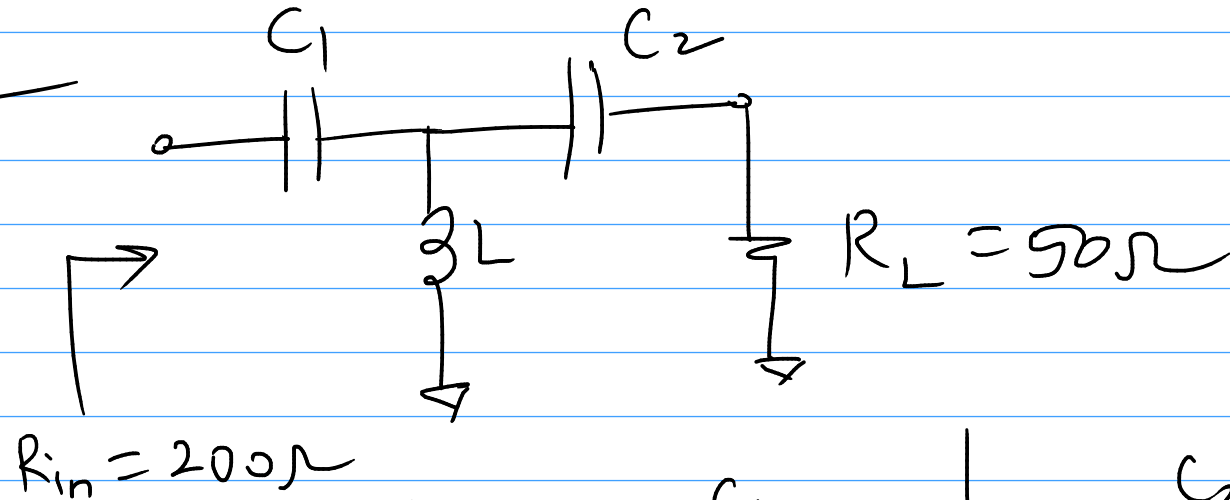

$$Q = \sqrt{\frac{R_I}{R_{in}} - 1} + \sqrt{\frac{R_I}{R_L} - 1}$$

$Q_L \qquad \qquad \qquad Q_R$

$$10 = \sqrt{\frac{R_I}{200} - 1} + \sqrt{\frac{R_I}{50} - 1}$$

$$R_I = 2.32 \text{ k}\Omega$$

$$Q_L = 3.26$$

$$Q_R = 6.74$$


$$C_1 = 0.1 \text{ pF}$$


$$L_1 = 47.2 \text{ nH}$$

$$C_2 = 0.19 \text{ pF}$$

$$L_2 = 22.8 \text{ nH}$$


$$L = 15.3 \text{ nH}$$

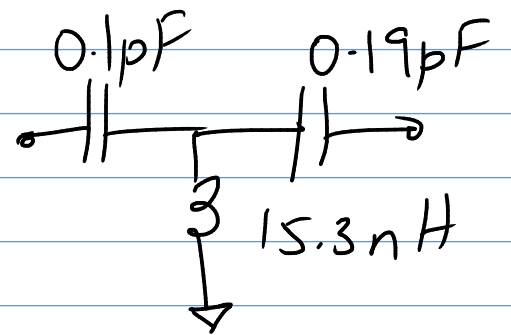

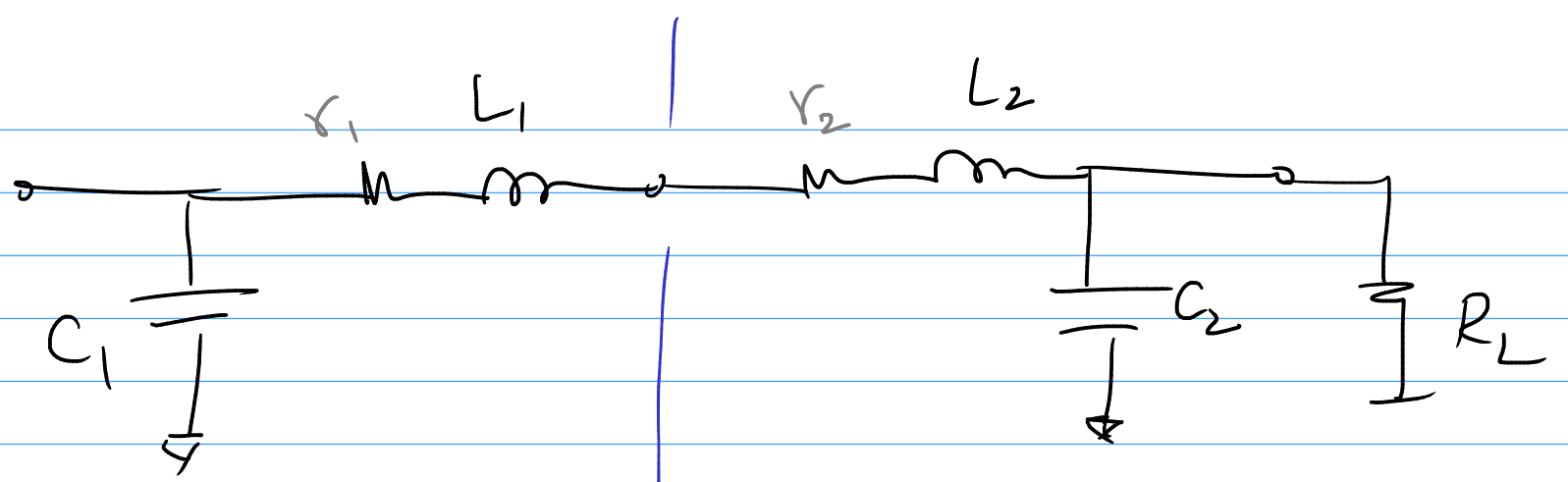


$R_I \gg r_2, r_1$


# Tapped Cap. MN

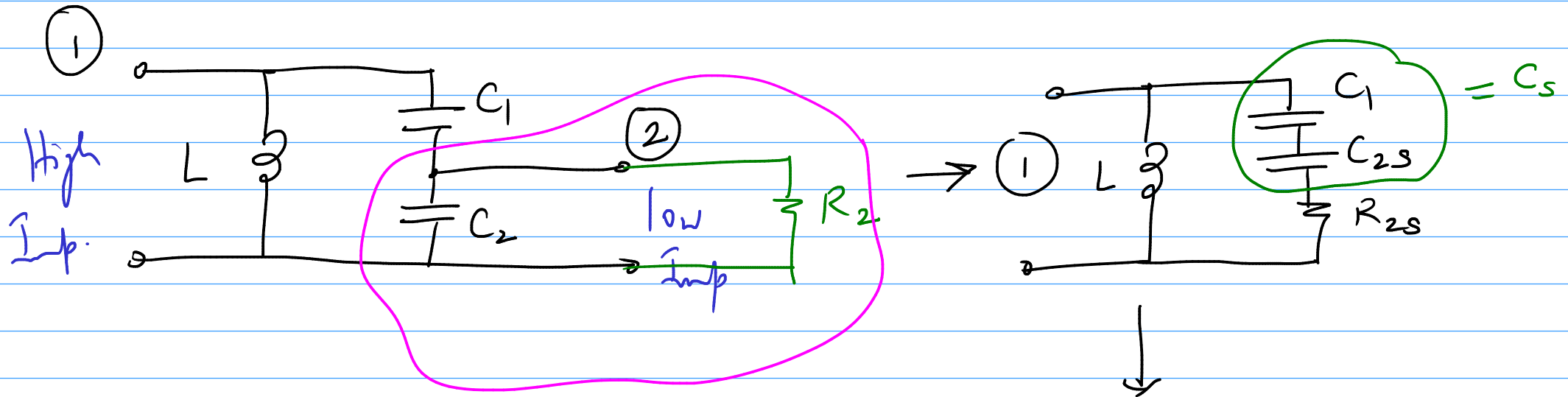

$$R_{in} = R_p \quad \left| \quad \omega_0 = \frac{1}{\sqrt{L C_p}} \right.$$

$$Q = \omega_0 C_p R_p \quad \left| \quad Q = \frac{R_p}{\omega_0 L} \right.$$

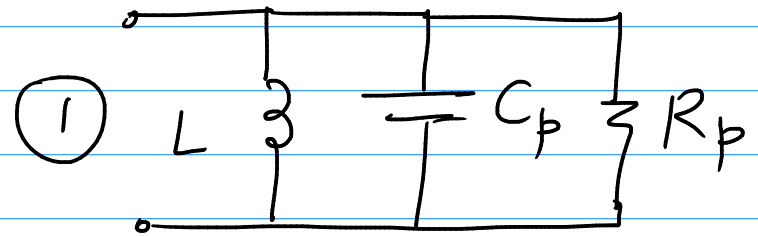

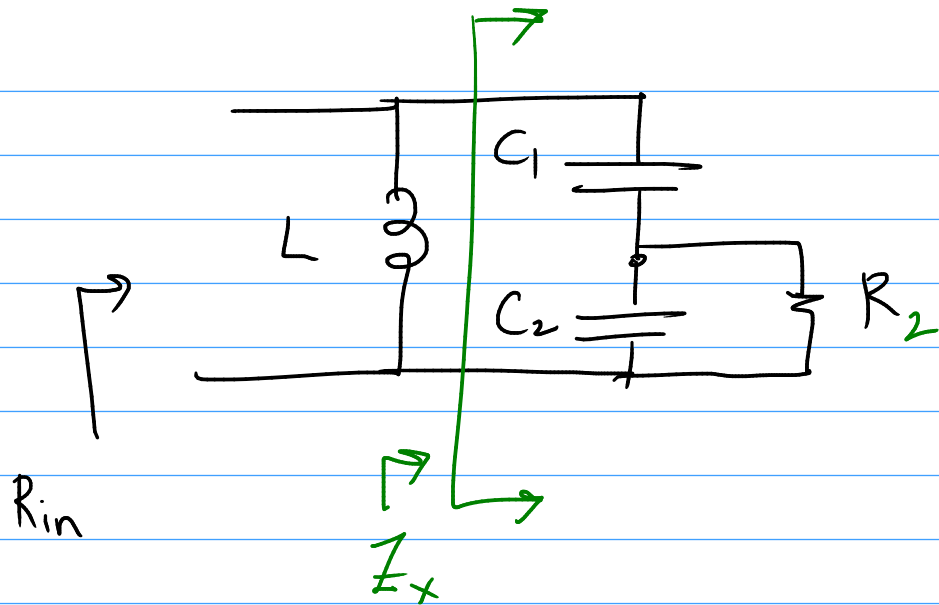

$$Z_x(s) = \frac{1}{sC_1} + \frac{R_2}{1 + sC_2R_2}$$

$$= \frac{1 + sC_2R_2 + sC_1R_2}{sC_1 + s^2C_1C_2R_2}$$

$$Y_x(j\omega) = \frac{1}{Z_x(j\omega)} = \frac{j\omega C_1 - \omega^2 C_1 C_2 R_2}{1 + j\omega R_2 (C_1 + C_2)}$$

$$= \frac{j\omega C_1 + \omega^2 \underline{C_1 R_2} (C_1 + \underline{C_2}) - \omega^2 \underline{C_1 C_2 R_2} - j\omega^3 C_1 C_2 R_2^2 (C_1 + C_2)}{1 + \omega^2 R_2^2 (C_1 + C_2)^2}$$

$$\frac{1}{R_p} = G_p = \frac{\omega^2 C_1^2 R_2}{1 + \omega^2 R_2^2 (C_1 + C_2)^2} \approx \frac{\omega^2 C_1^2 R_2}{\omega^2 R_2^2 (C_1 + C_2)^2}$$

→


$$G_p \approx G_2 \cdot \left( \frac{C_1}{C_1 + C_2} \right)^2 = \frac{G_2}{n^2} \rightarrow R_p \gg R_2$$

$$n = \text{tap ratio} = \frac{C_1 + C_2}{C_1}$$

$$B_p = \frac{\omega C_1 - \omega^3 C_1 C_2 R_2^2 (C_1 + C_2)}{1 + \omega^2 R_2^2 (C_1 + C_2)^2}$$


$$\approx \frac{-\omega^3 C_1 C_2 R_2^2 (C_1 + C_2)}{\omega^2 R_2^2 (C_1 + C_2)^2} \quad \text{@ high freq.}$$
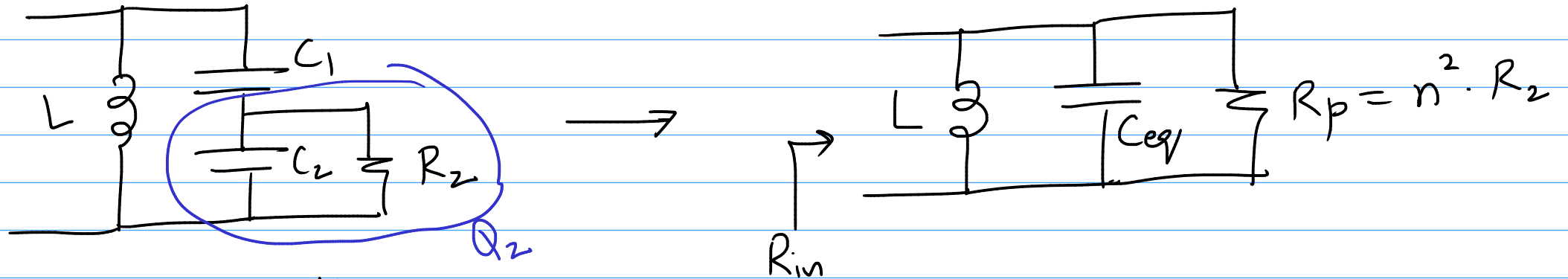
$$\approx -\omega \cdot \frac{C_1 C_2}{C_1 + C_2} \approx -\omega C_{eq}$$



Design equations
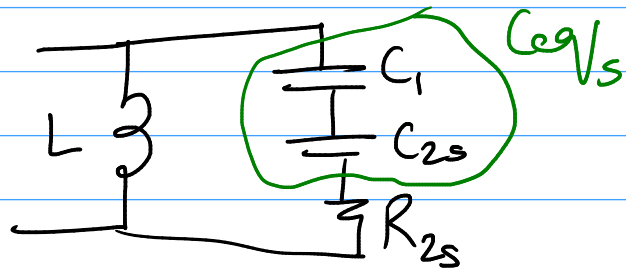
$$1) \quad Q = \frac{R_{in}}{\omega_0 L} \Rightarrow \boxed{L = \frac{R_{in}}{\omega_0 Q}}$$



$$C_{2s} = C_2 \times \left( \frac{1 + Q_2^2}{Q_2^2} \right)$$

$$Q_2 = \omega_0 C_2 R_2$$

$$R_{in} = R_{2s} (1 + Q^2)$$

$$\frac{R_2}{1 + Q_2^2} = \frac{R_{in}}{1 + Q^2}$$

$$2) \quad Q_2 = \sqrt{\frac{R_2}{R_{in}} (1 + Q^2) - 1}$$

$$3) \quad C_2 = \frac{Q_2}{\omega_0 R_2}$$

$$C_{eq/s} = \frac{C_1 \cdot C_{2s}}{C_1 + C_{2s}}$$




$$Q = \frac{1}{\omega_0 C_{eq/s} \cdot R_{2s}} = \frac{C_1 + C_{2s}}{\omega_0 R_{2s} \cdot C_1 C_{2s}}$$


4)

$$C_1 = \frac{C_2 (1 + Q^2)}{Q Q_2 - Q_2^2}$$

HW

Tapped-L  
match

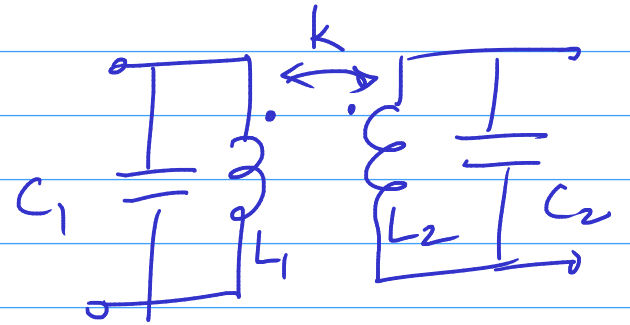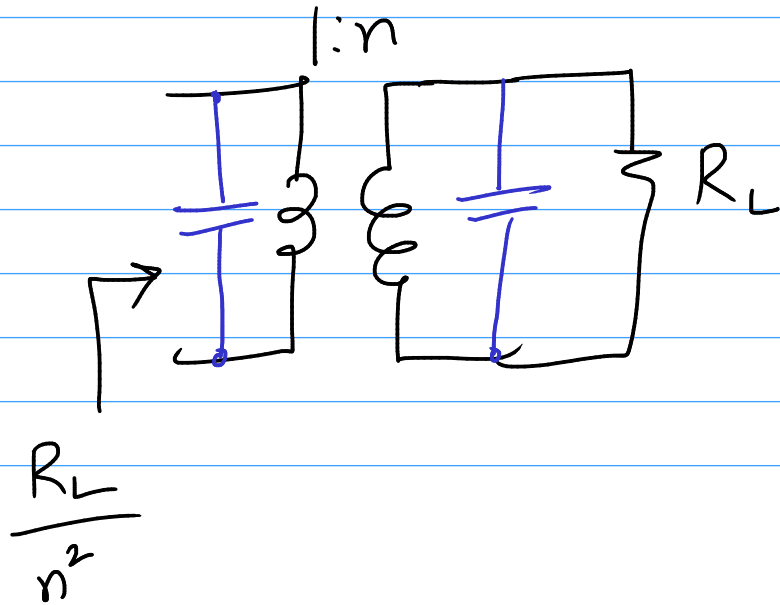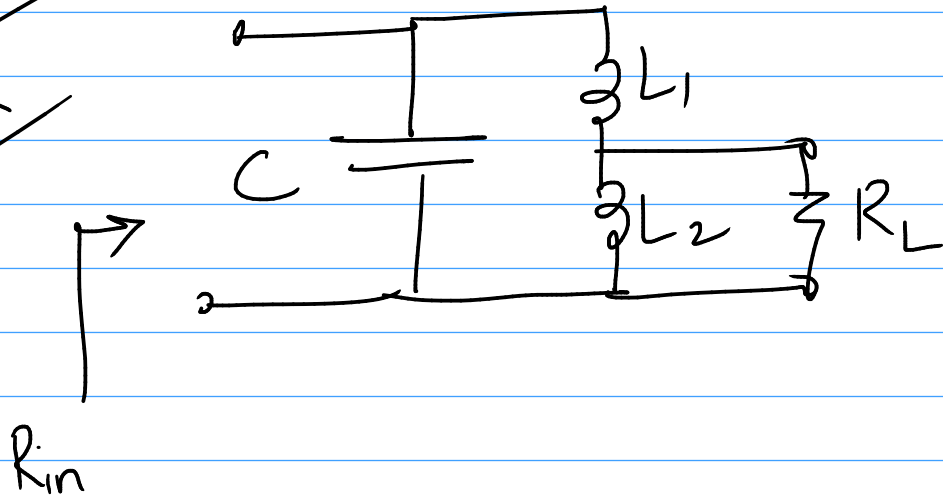

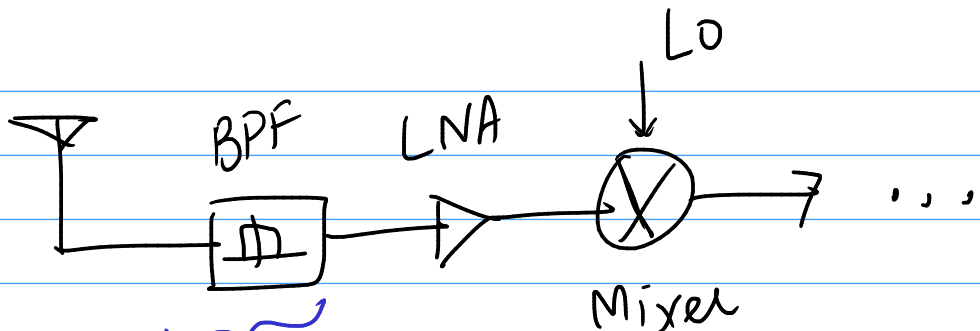


$IIP_3$  (passive) =  $\infty$  (ideal)

= +50dBm (100W)

$L = \text{loss}$   
 $F_o = ?$   
 $IIP_3 = ?$

$A_1$	$A_2$
$F_1$	$F_2$
$IIP_{3,1}$	$IIP_{3,2}$




$F_o = ?$

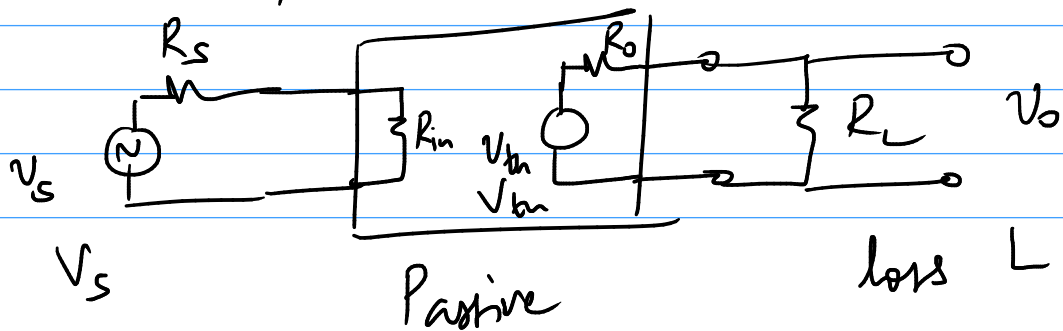


$R_{in} = R_s$   
 $R_o = R_L$

loss  $L = \frac{P_{in}}{P_{out}} = \frac{V_s^2 / 4R_{in}}{V_{th}^2 / 4R_L}$
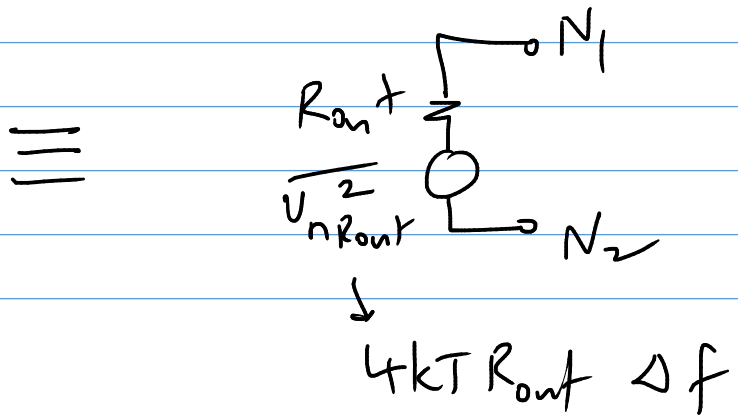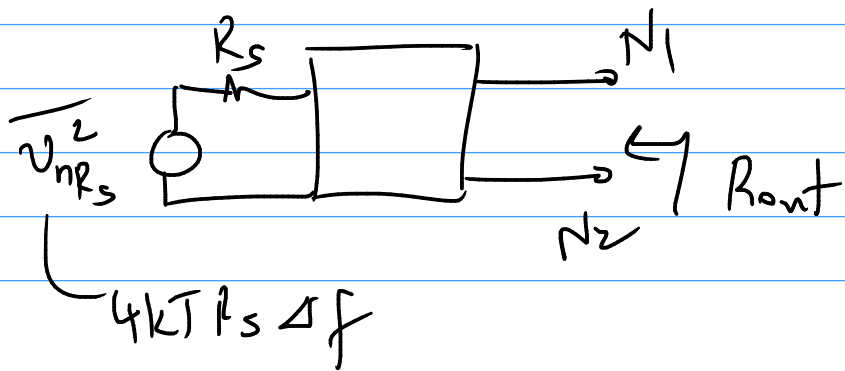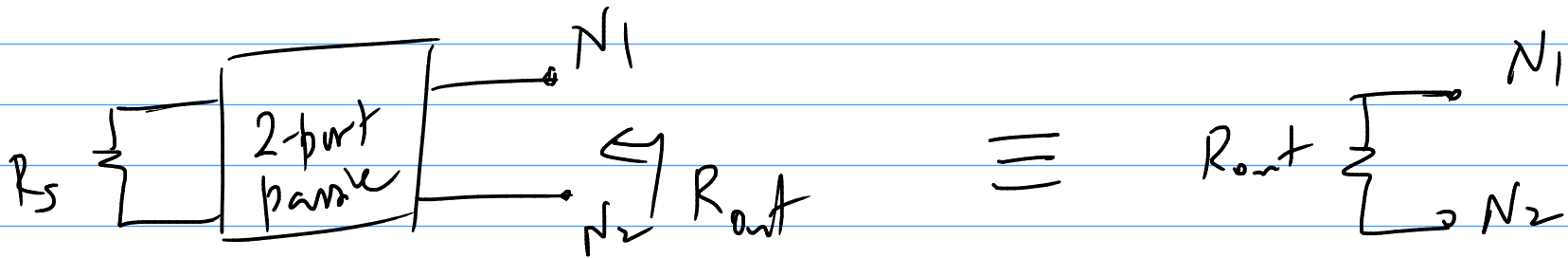
$$L = \frac{V_s^2}{V_{in}^2} \cdot \frac{R_L}{R_{in}}$$



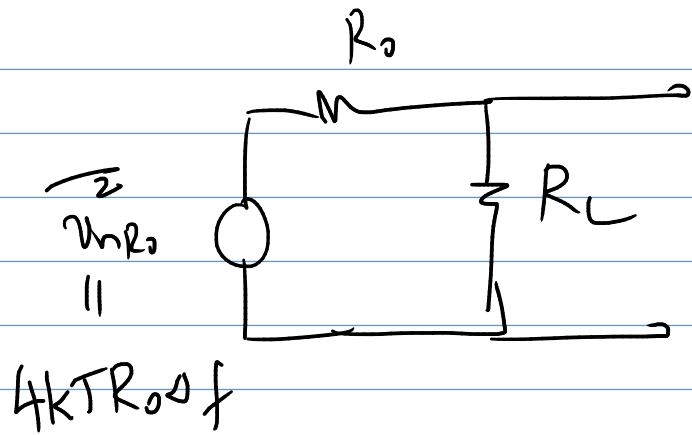


$$\overline{v_{n_L}^2} = 4kTR_o\Delta f \times \left( \frac{R_L}{R_L + R_o} \right)^2$$

$$A_v = \frac{V_{th}}{V_s} \cdot \left( \frac{R_L}{R_L + R_o} \right)$$

$$F = \frac{\overline{v_{n_L}^2}}{\overline{v_{n_{R_s}}^2} \cdot A_v^2} = \frac{4kTR_o\Delta f \left( \frac{R_L}{R_L + R_o} \right)^2}{4kTR_s\Delta f \cdot \left( \frac{V_{th}}{V_s} \right)^2 \left( \frac{R_L}{R_L + R_o} \right)^2}$$

$$F = \left( \frac{V_s}{V_{th}} \right)^2 \cdot \frac{R_o}{R_s} = L$$

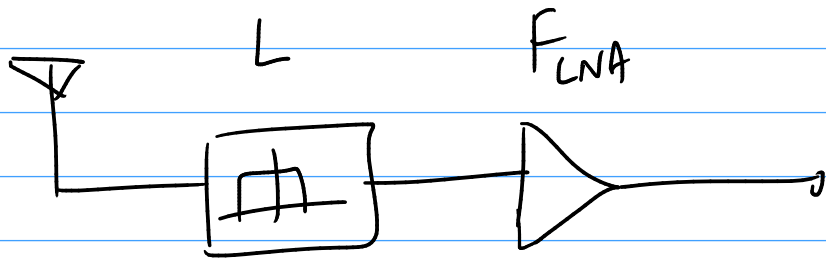Noise Factor of a Passive Block = Loss of the block




$$NF_{tot.} = L_{dB} + NF_{LNA}$$

$$F = L + \frac{F_{LNA} - 1}{1/L}$$




$$= L + L(F_{LNA} - 1)$$


$$F = L \cdot F_{LNA}$$

# Mixers


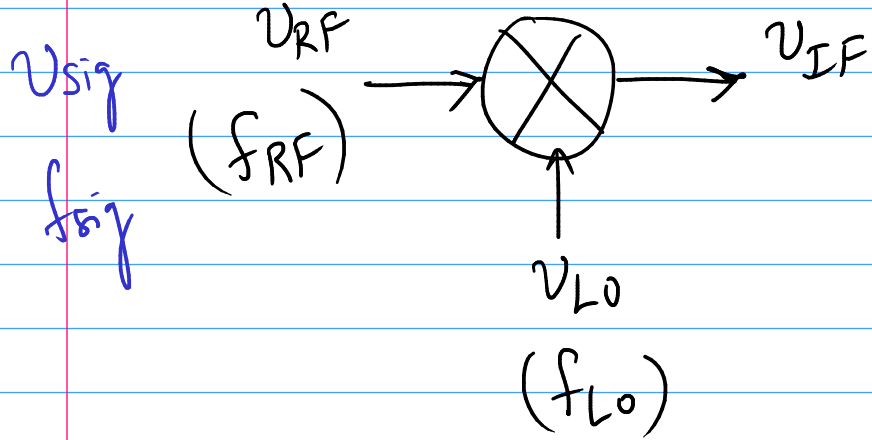



$$f_{LO} + f_{RF}$$
$$f_{LO} - f_{RF}$$

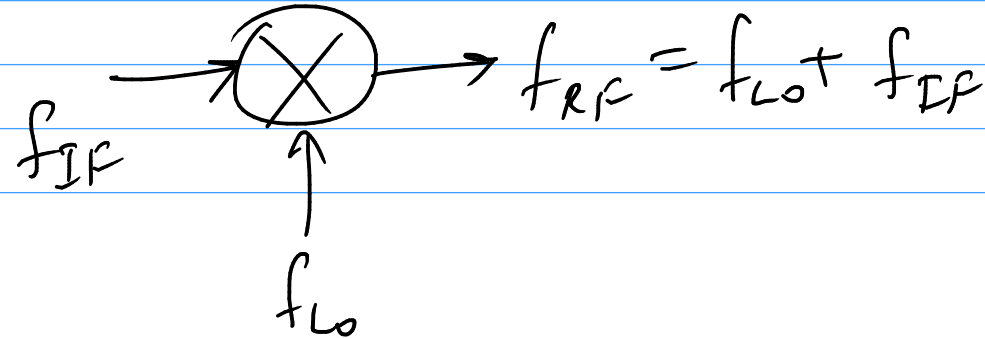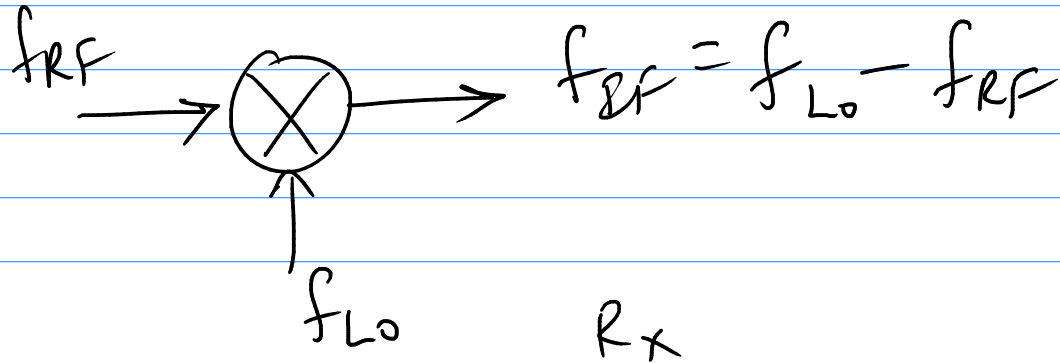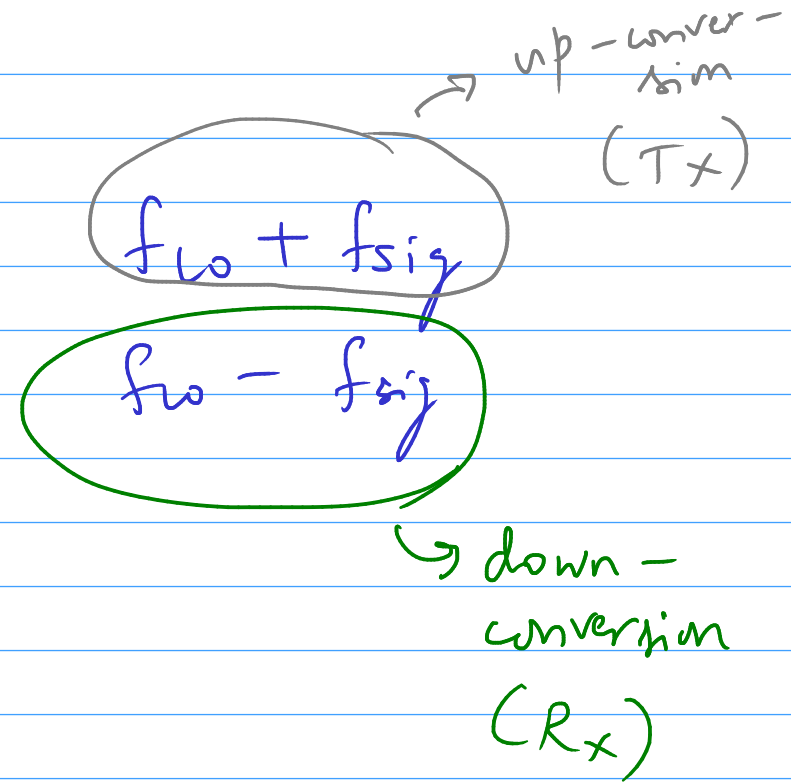

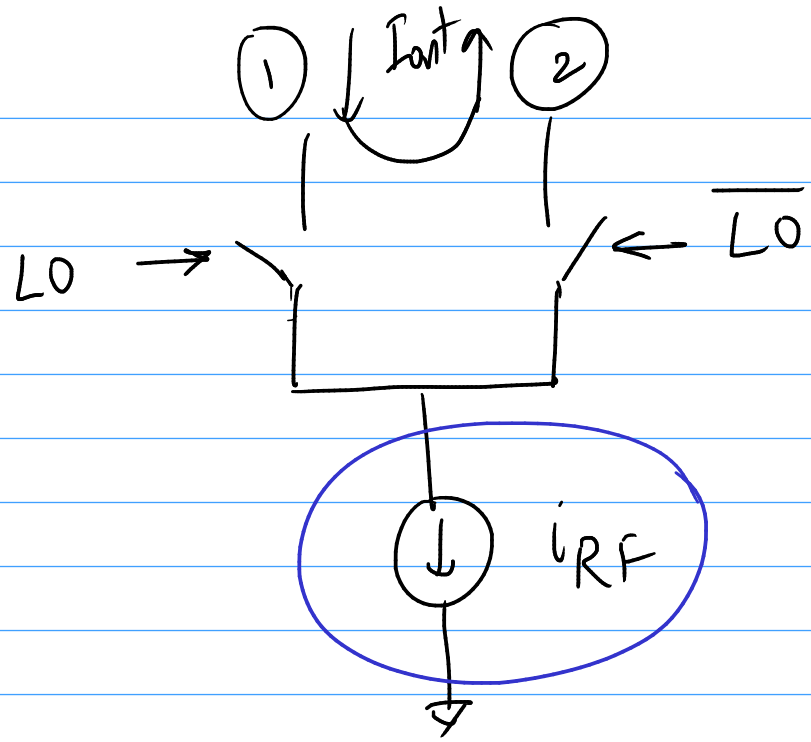
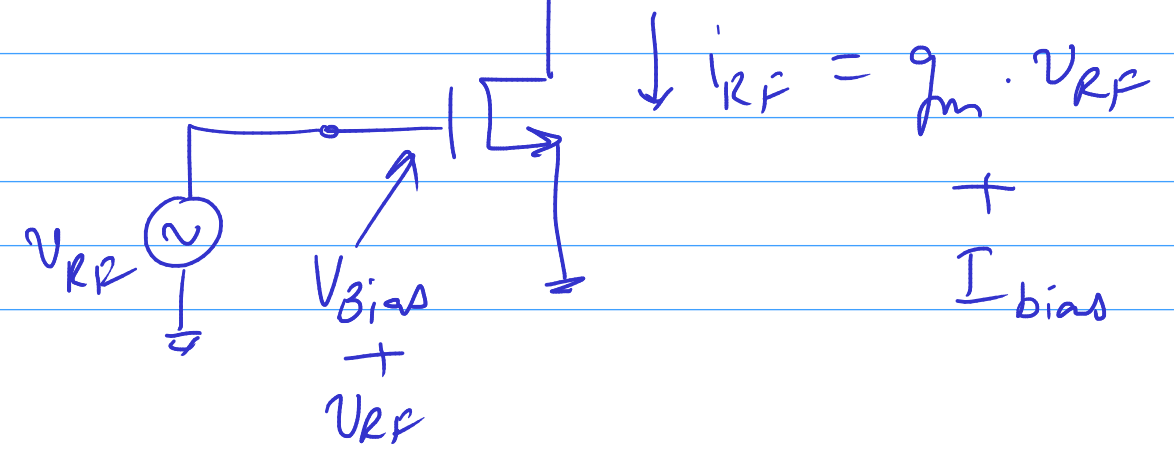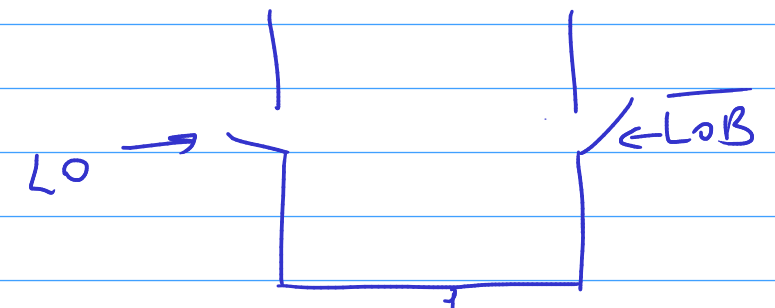
$$I_{out} = i_{RF} \times \text{sgn}(\sin \omega_{LO} t)$$



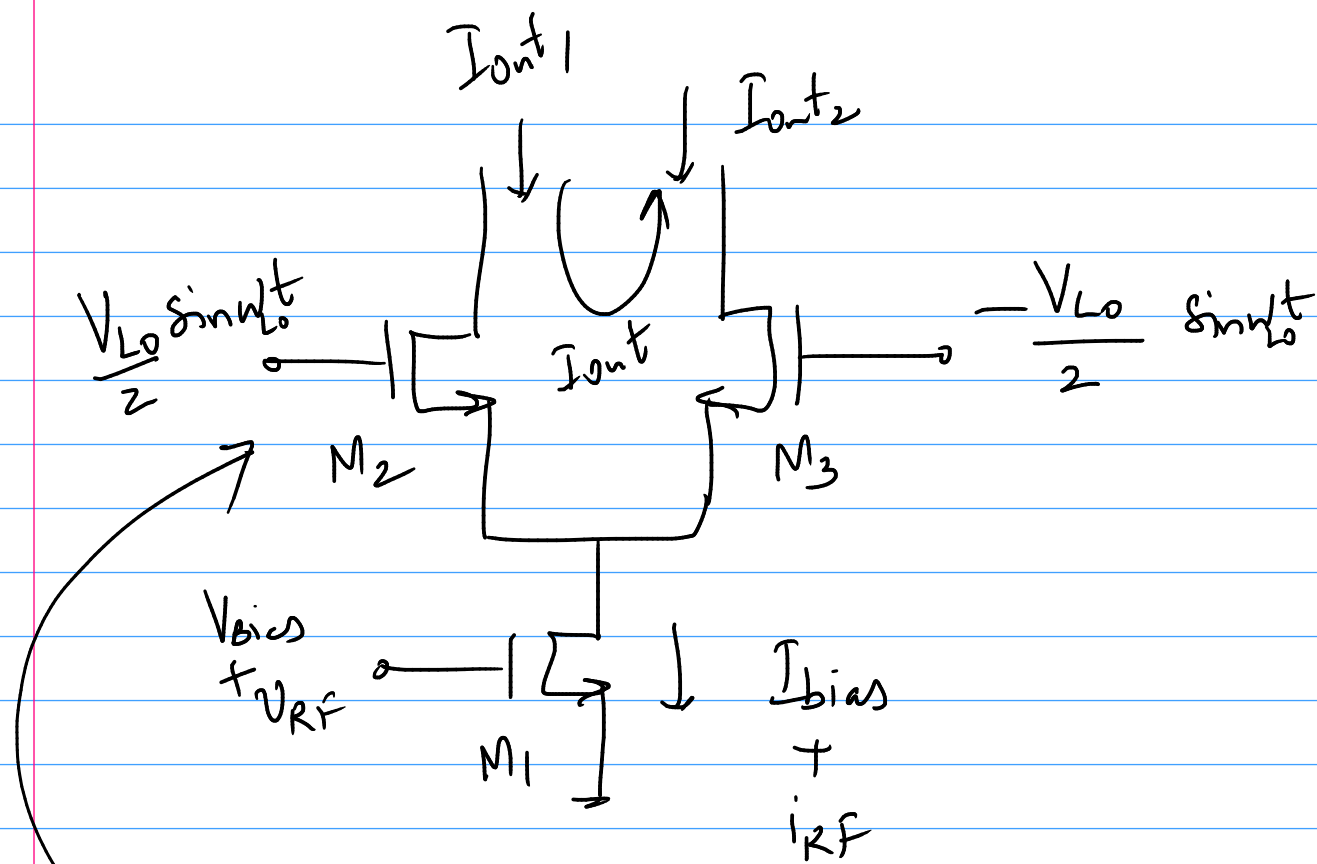


$$s_2(\omega) = \begin{array}{c} \uparrow \\ 0 \quad 1 \quad 0 \quad 1 \end{array}$$

$V_{LO}$  is large enough for

- 1) full switching
- 2) fast switching

$s_1(t) \Rightarrow$

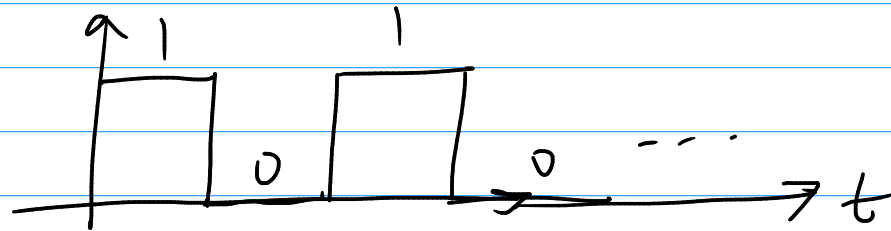

$$S_1(t) = 0.5 + 0.5 S(t)$$

$$I_{out,1} = \left( I_{bias} + I_{RF} \cdot \cos \omega_{RF} t \right) \times \left( 0.5 + 0.5 S(t) \right)$$

Fourier series

$$S(t) = \frac{a_0}{2} + \sum_{n=1}^{\infty} \left[ a_n \cos(n\omega_0 t) + b_n \sin(n\omega_0 t) \right]$$

$$\frac{a_0}{2} = 0 \quad ; \quad a_n = 0 \quad ; \quad b_n = \frac{2}{T_{Lo}} \int_0^{T_{Lo}} \text{sgn}(t) \sin(n\omega_0 t) dt$$

$$b_n = \frac{4}{T_{L_0}} \int_0^{T_{L_0}/2} \sin(n\omega_0 t) dt$$

$$= \frac{4}{T_{L_0}} \cdot \frac{1}{n\omega_0} \cdot \left[ -\cos(n\omega_0 t) \right]_0^{T_{L_0}/2}$$

$$= \frac{2}{n\pi} \cdot (1 - \cos n\pi)$$

$$b_n = \begin{cases} 0 & \text{for even } n \\ \frac{4}{n\pi} & \text{for odd } n \end{cases}$$

$I_{out}$

$$\underline{I_{bias} \text{ term}} : \frac{4 I_{bias}}{\pi} \left[ \sin \omega_{LO} t + \frac{1}{3} \sin(3\omega_{LO} t) + \frac{1}{5} \sin(5\omega_{LO} t) + \dots \right] \Rightarrow \text{LO feed-through}$$

$$s(t) = \frac{4}{\pi} \left[ \sin \omega_{LO} t + \frac{1}{3} \sin 3\omega_{LO} t + \dots \right]$$




$$I_{out}(t) = \left[ I_{bias} + I_{RF} \cos \omega_{RF} t \right] \cdot s(t)$$


$\rightarrow$  RF term

IRF term

$$\frac{4 I_{RF}}{\pi} \left[ \overbrace{\cos(\omega_{RF} t) \cdot \sin(\omega_{LO} t)}^{\omega_{LO} \pm \omega_{RF}} + \frac{1}{3} \overbrace{\cos(\omega_{RF} t) \cdot \sin(3\omega_{LO} t)}^{3\omega_{LO} \pm \omega_{RF}} + \dots \right]$$
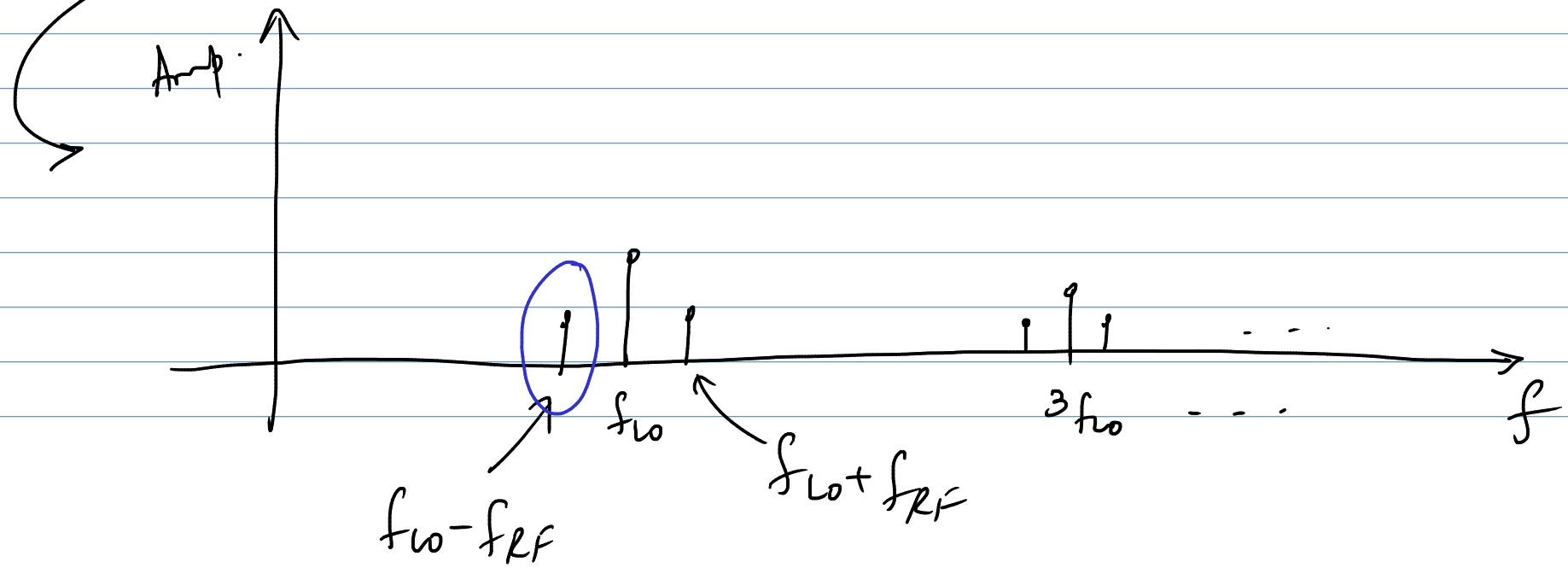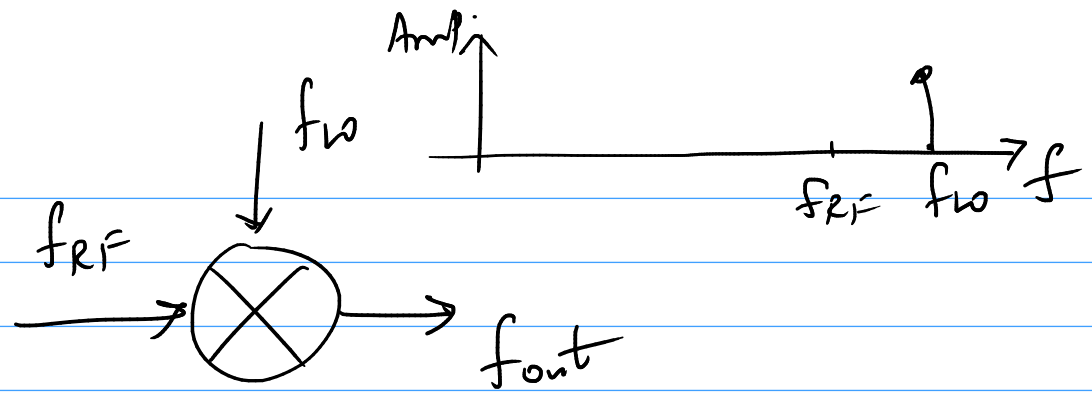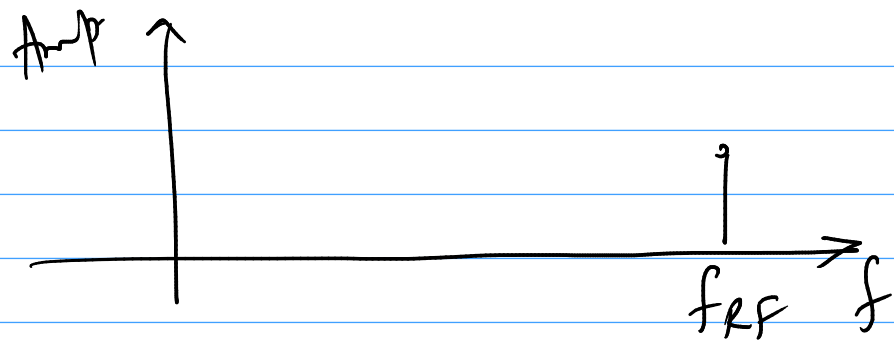
$$= \frac{2 I_{RF}}{\pi} \left[ \sin(\omega_{LO} - \omega_{RF}) + \sin(\omega_{LO} + \omega_{RF}) + \frac{1}{3} \sin(3\omega_{LO} - \omega_{RF}) + \sin(3\omega_{LO} + \omega_{RF}) + \dots \right]$$







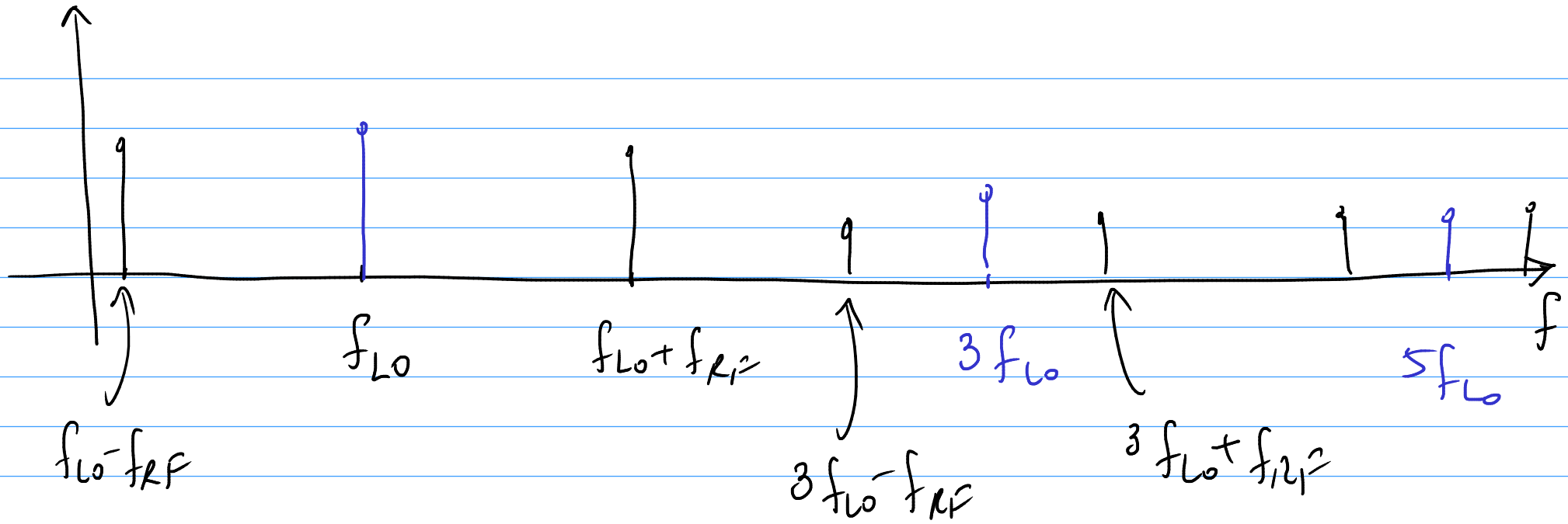



$$\text{current gain} = \frac{2}{\pi}$$

$$\left( \frac{I_{out}}{I_{RF}} \right)$$
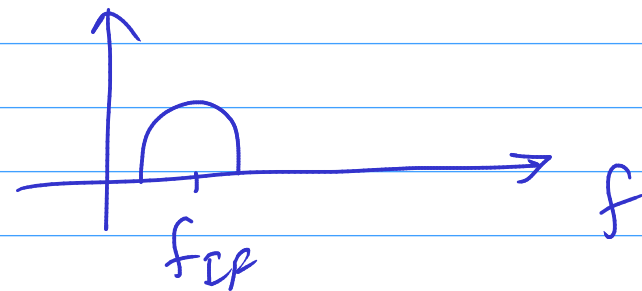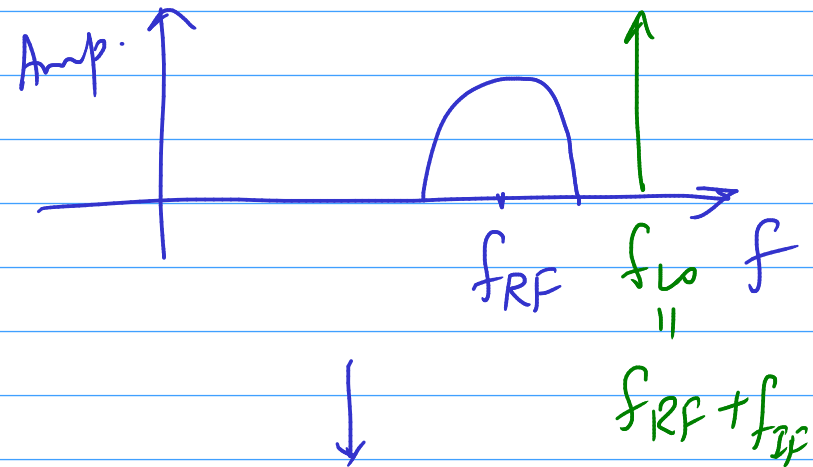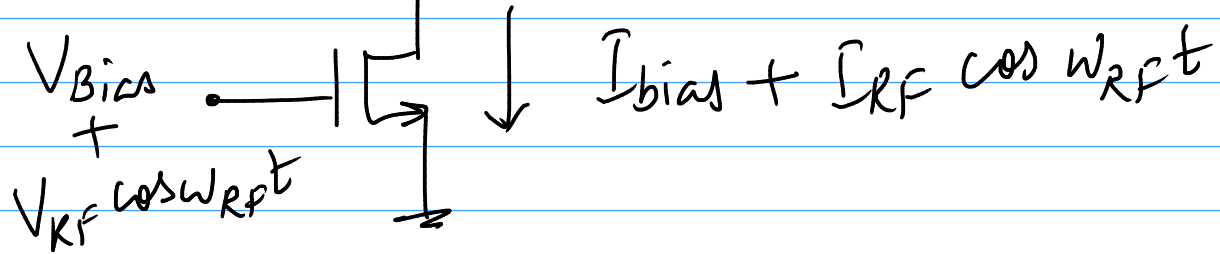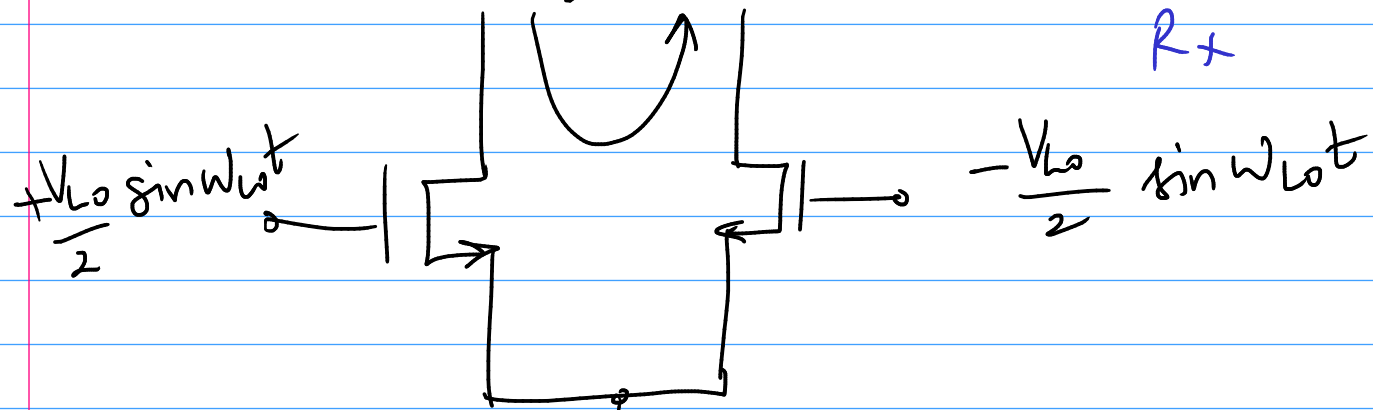
$$I_{out} = \frac{2}{\pi} I_{RF} \left[ \underbrace{\cos(\omega_L - \omega_{RF})t}_{R_x} + \underbrace{\cos(\omega_L + \omega_{RF})t}_{I_x} \right]$$



IF = Intermediate freq.

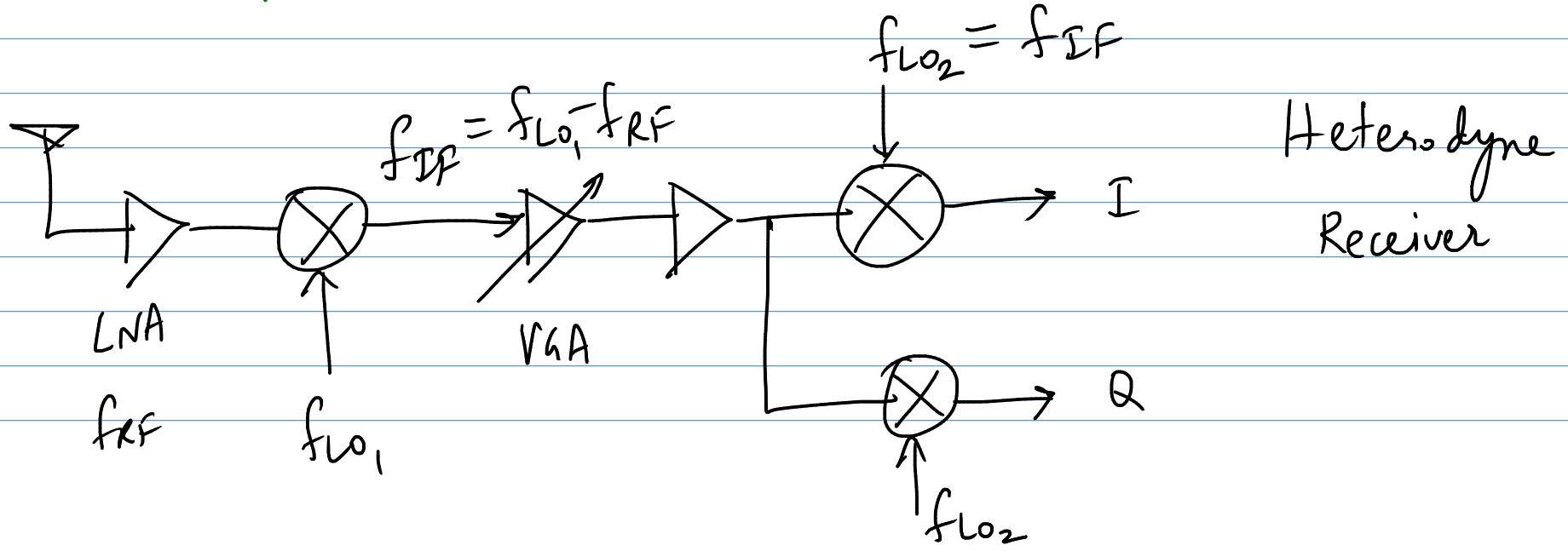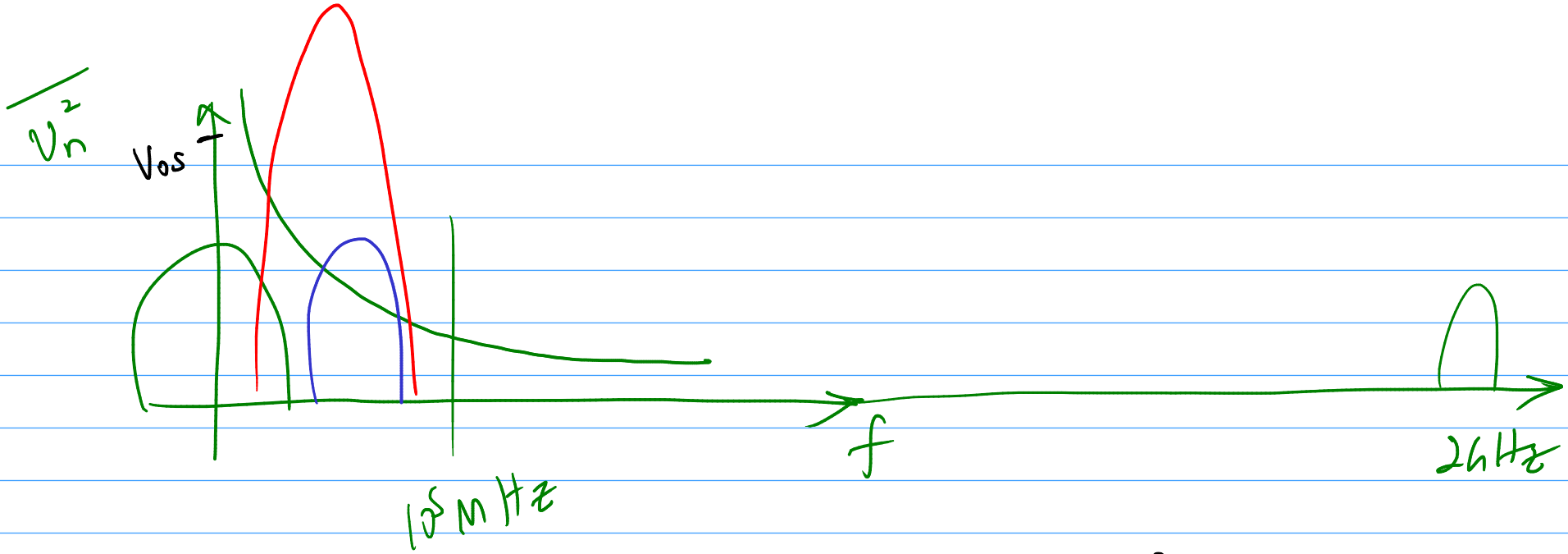

$$f_{RF} = 3.5 \text{ GHz}$$


$$f_{LO} = 3.6 \text{ GHz}$$

$$f_{IF} = 100 \text{ MHz}$$

$I_{out} \rightarrow$

100 MHz, 3.6 GHz, 7.1 GHz, ...



"Gilbert-cell"  
Mixer

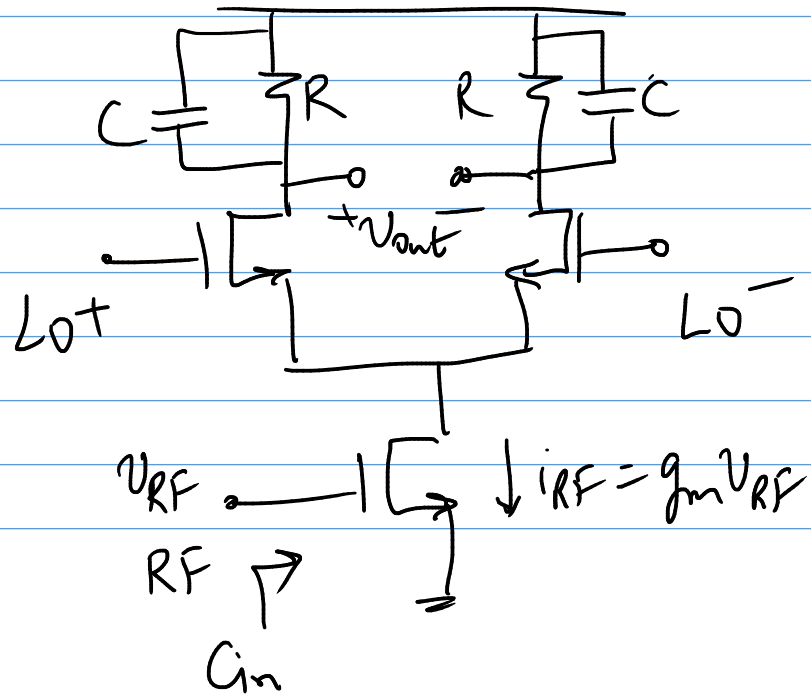


gain  $\rightarrow$  decides  $R$


filter  $\rightarrow$  decides  $C$

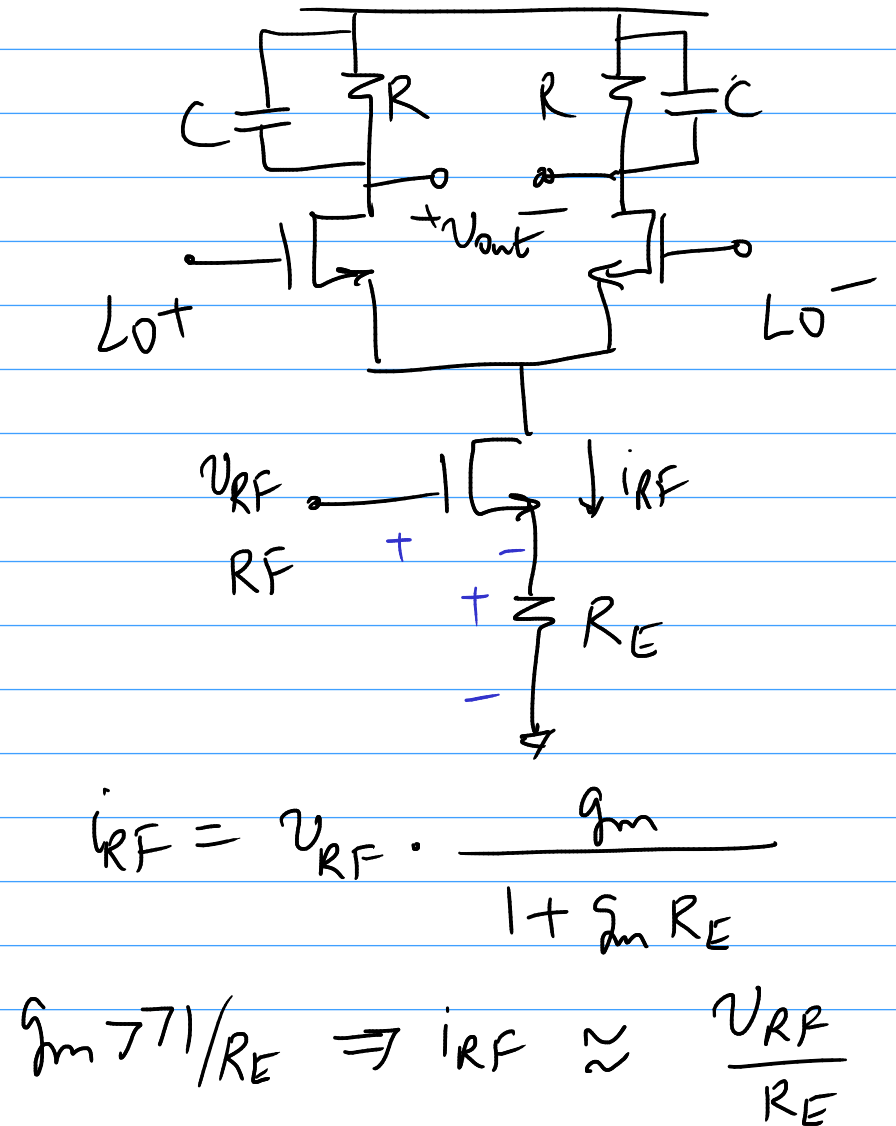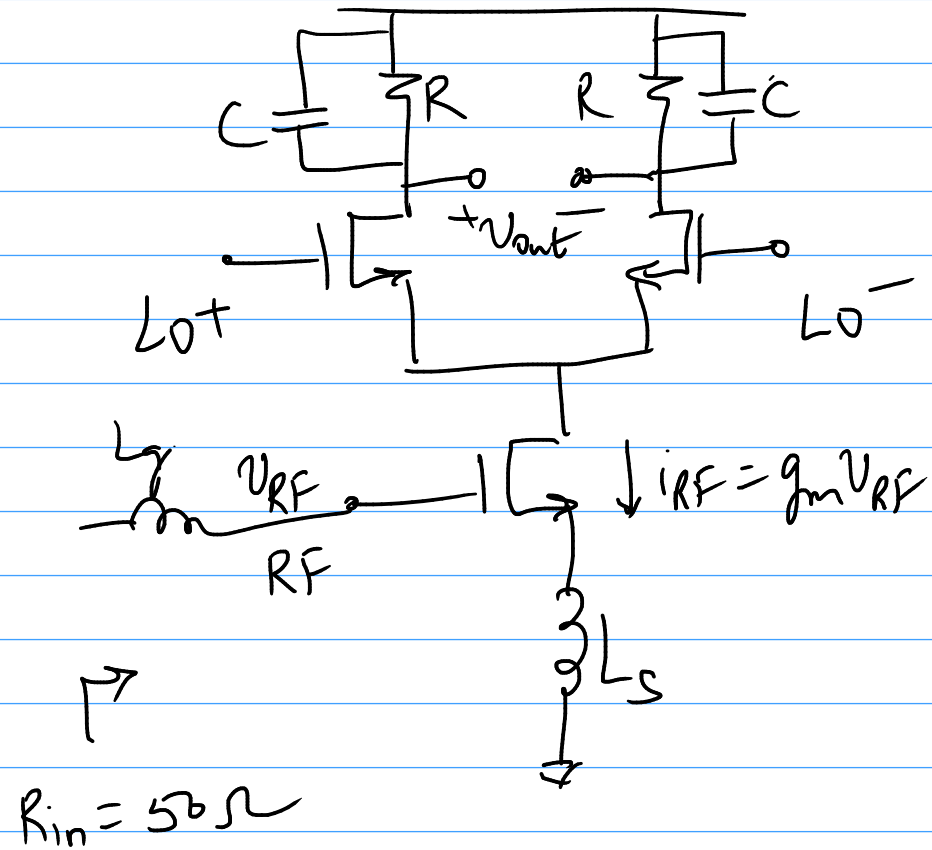
$$\text{gain } A_v = \frac{V_{out}}{V_{RF}} = \frac{2}{\pi} g_m R$$



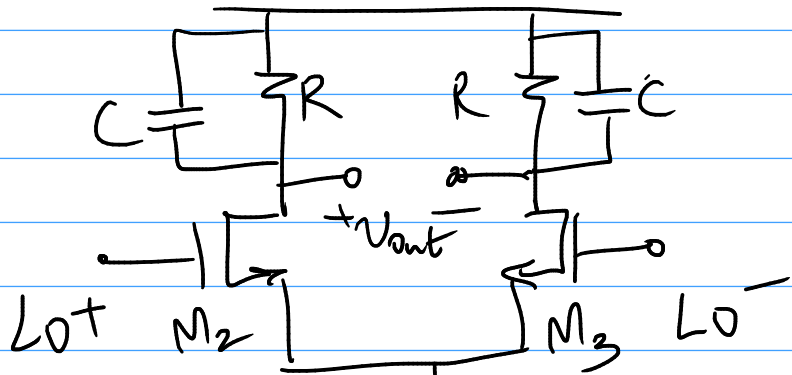

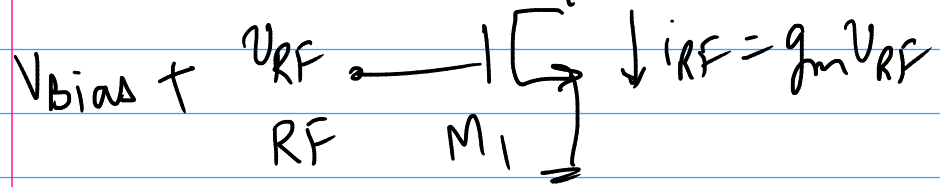choose  $V_{Bias}$  so that  $g_{m3}(m_1) \approx 0$



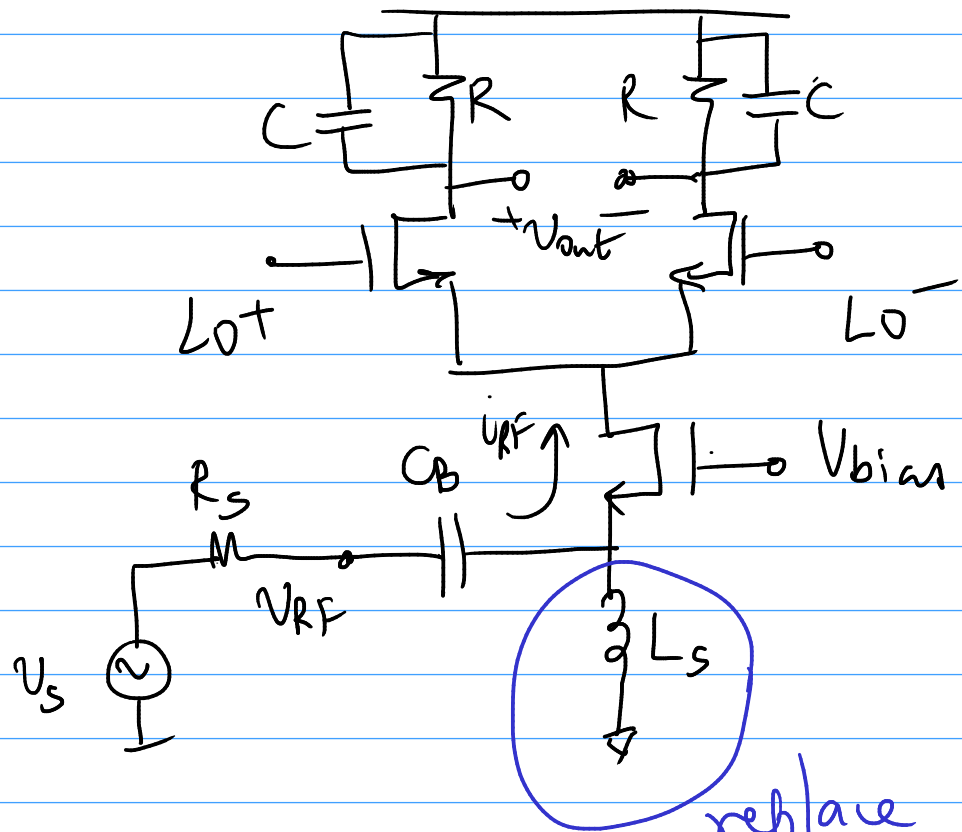


$$i_{RF} = \frac{V_s}{R_s + 1/g_m}$$

$$= \frac{g_m V_s}{1 + g_m R_s}$$

$$\approx \frac{V_s}{R_s} \text{ if } 1/g_m \ll R_s$$

replace with Ideal current source

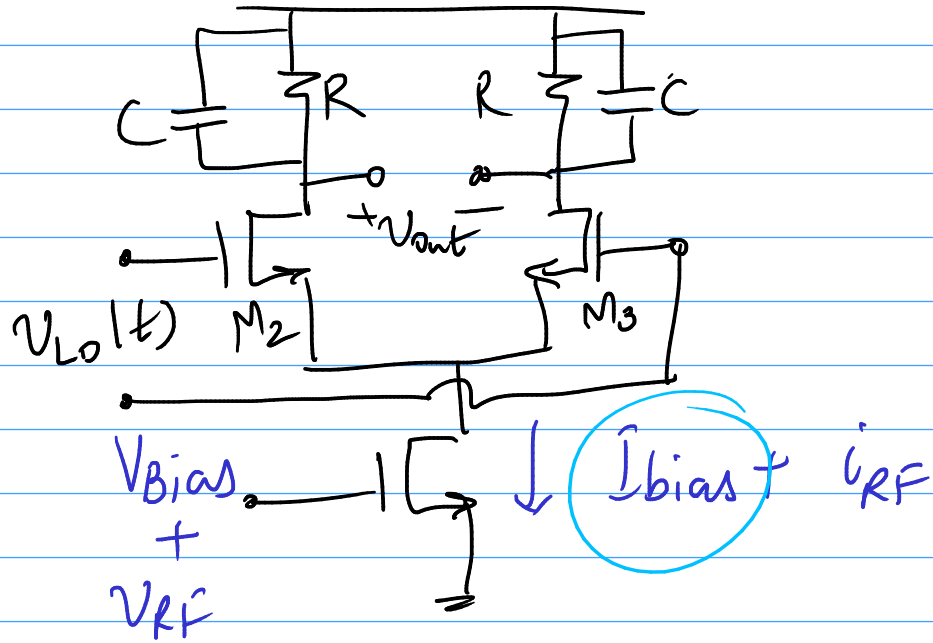


$$v_{Lo}(t) = V_{Lo} \sin \omega_{Lo} t \quad \checkmark$$


$(\omega)$

$V_{Lo}$

$$I_{D2} = I_{bias} + g_m \frac{V_{id}}{2}$$
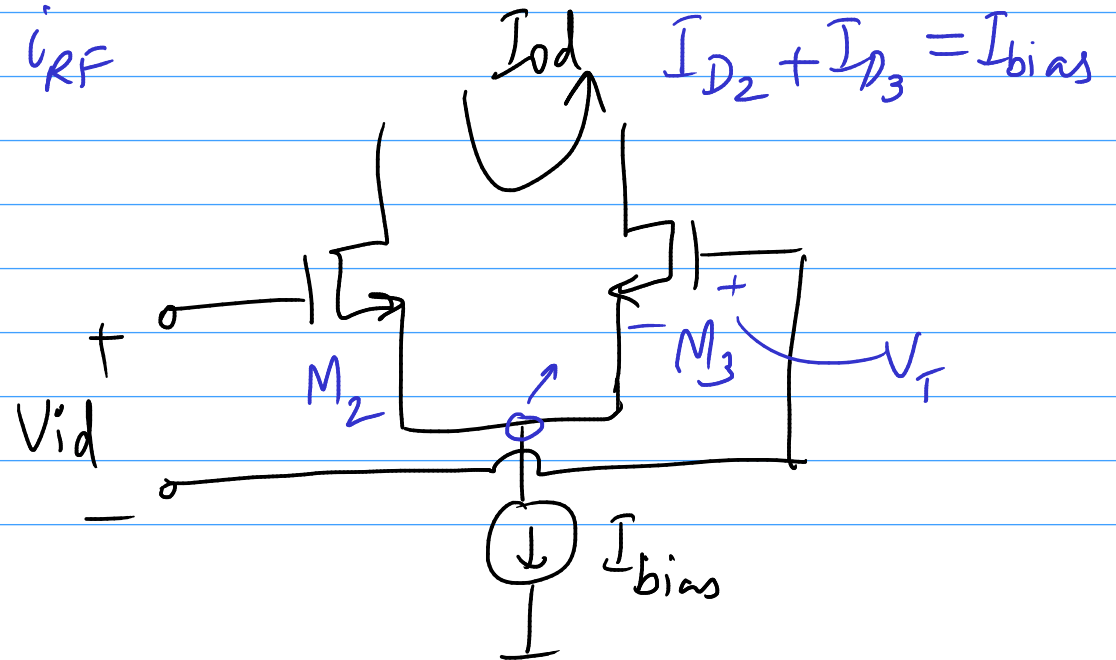
$$I_{D3} = I_{bias} - g_m \frac{V_{id}}{2}$$




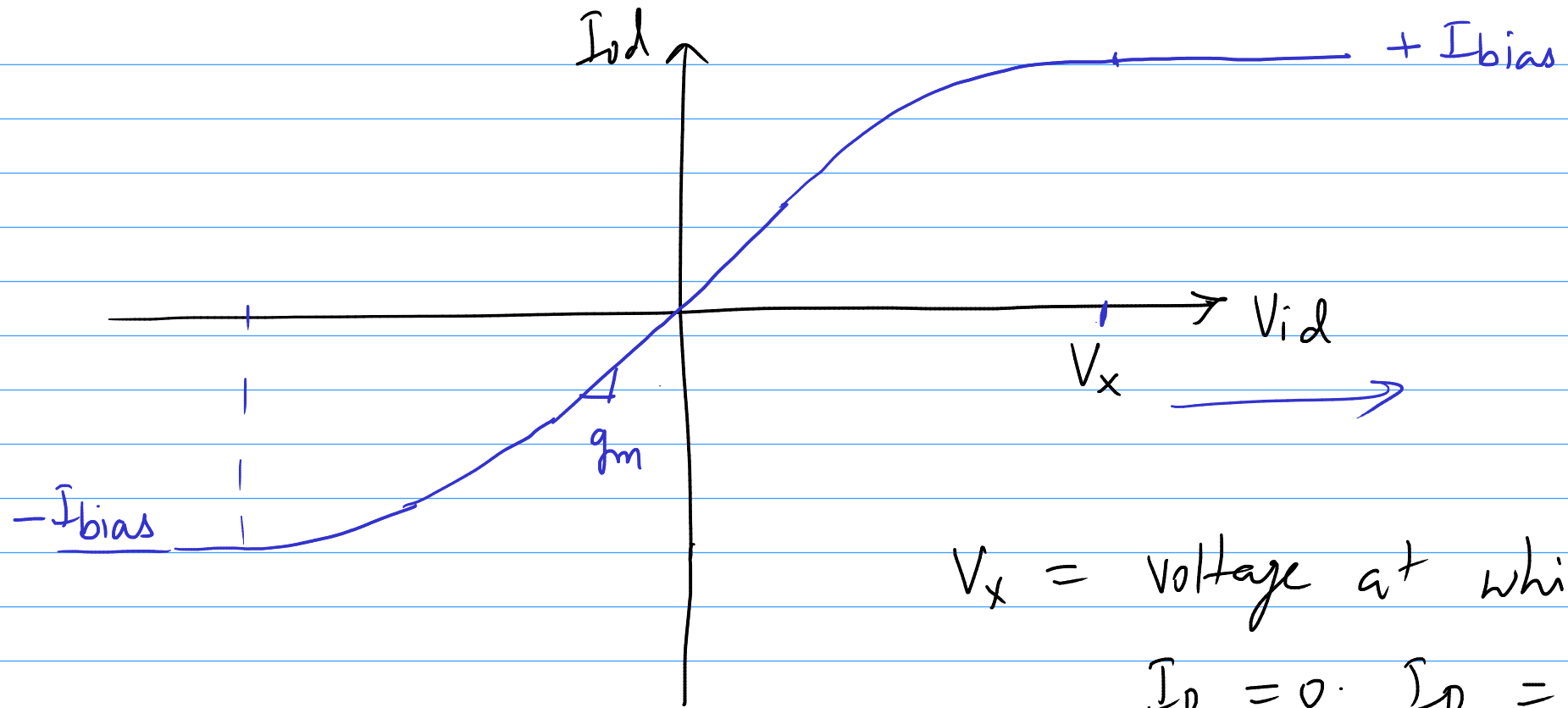

$V_x =$  voltage at which  
 $I_{D3} = 0; I_{D2} = I_{bias}$

$$= \sqrt{2} (V_{GS} - V_T)_{nom.}$$

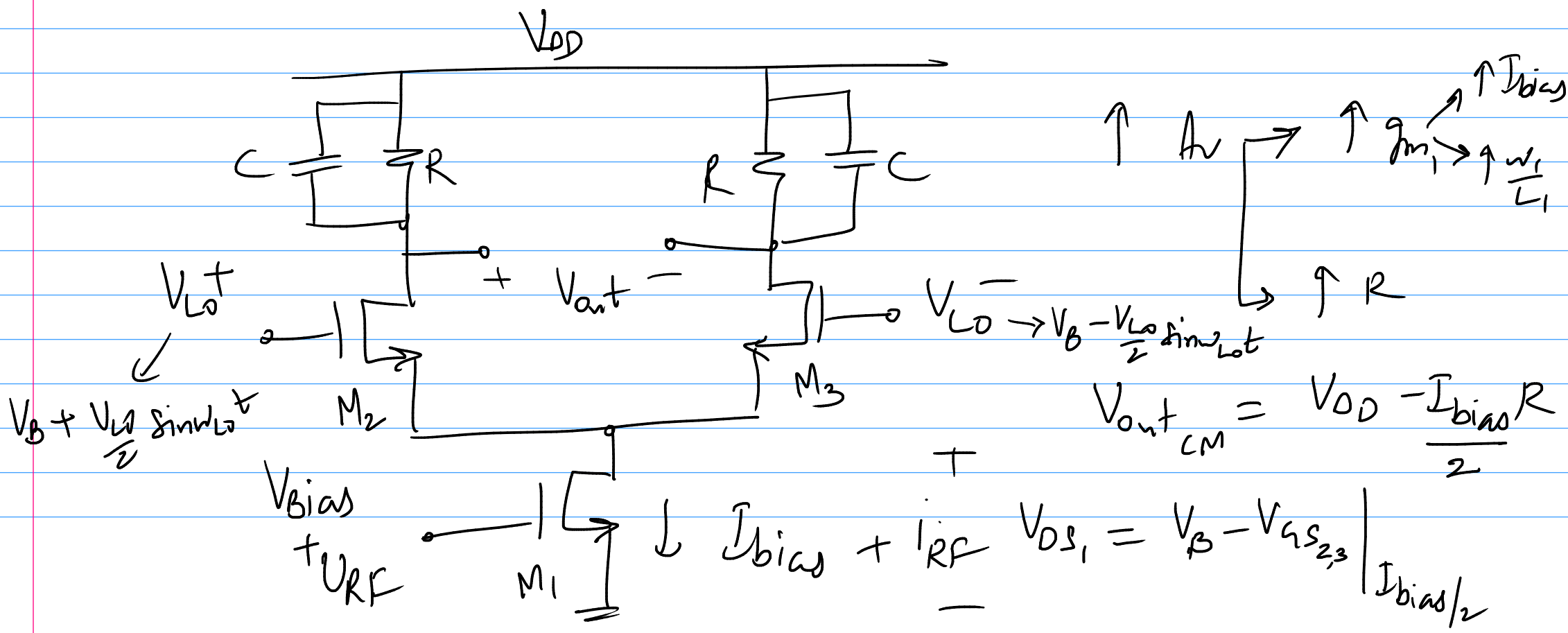$I_f$   $V_{LO} < \sqrt{2} V_{OV} \rightarrow$  lower Mixer gain



1) Choose  $V_B$  so that  $M_1$  is in Sat.  $\Rightarrow V_{DS1} = V_B - V_{DS2}$   
 $\geq V_{Bias} - V_{T1}$



2)  $V_{DD} - \frac{I_{Bias} R}{2} \geq V_B - V_{T23}$  so that  $M_2, M_3$   
are in sat. (bias)



3)  $I_f \frac{W_1}{L_1} \uparrow \Rightarrow C_{in} \uparrow \Rightarrow$  loads LNA

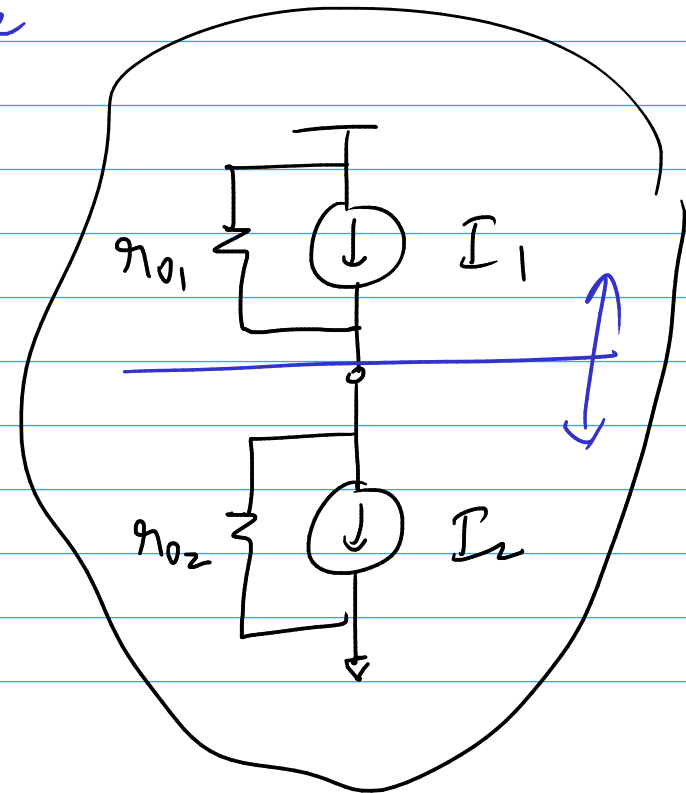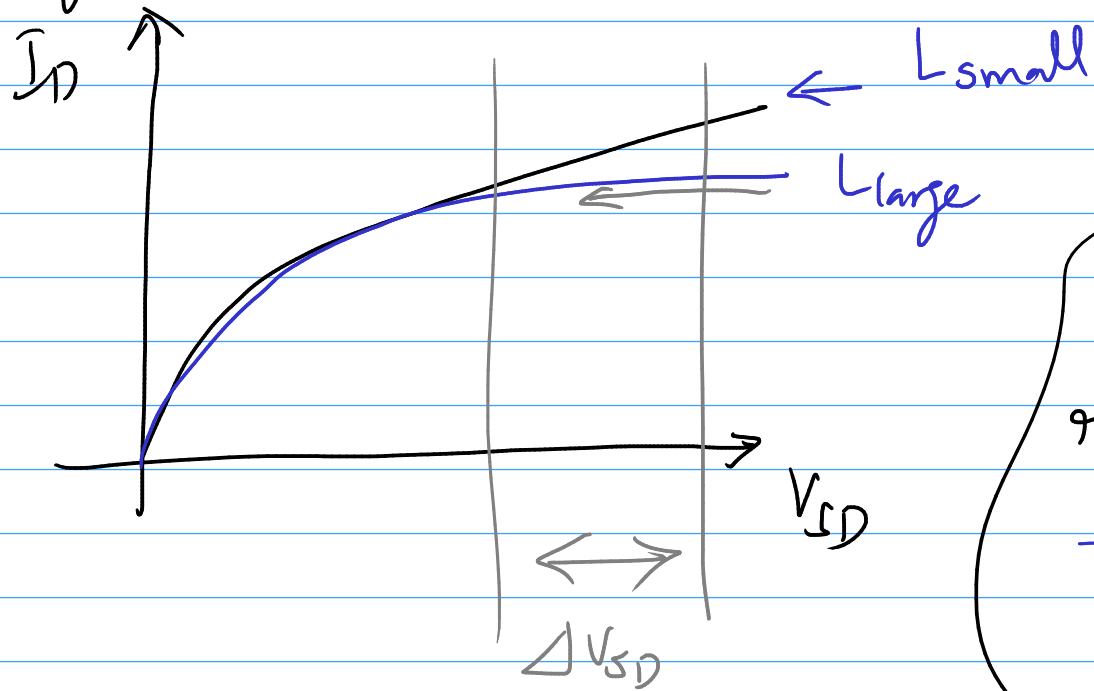
4)  $I_f$   $M_1$  goes to Moderate / Weak Inversion  
 $\hookrightarrow \uparrow \frac{W_1}{L_1}$  does not  $\uparrow g_m$   
 $\hookrightarrow$  device speed  $\downarrow (f_T)$



$\uparrow r_{ds4,5}$  by  $\uparrow L_{4,5} \Rightarrow \lambda \downarrow$



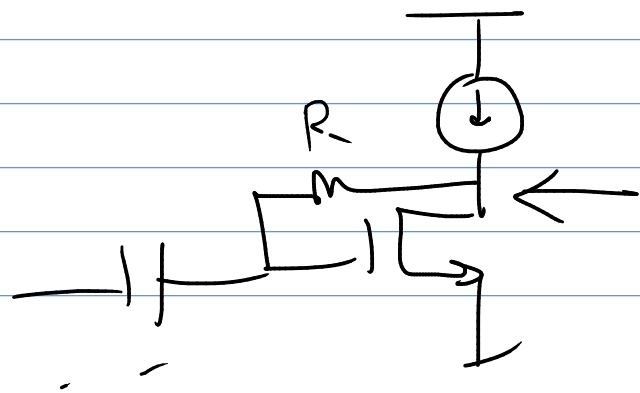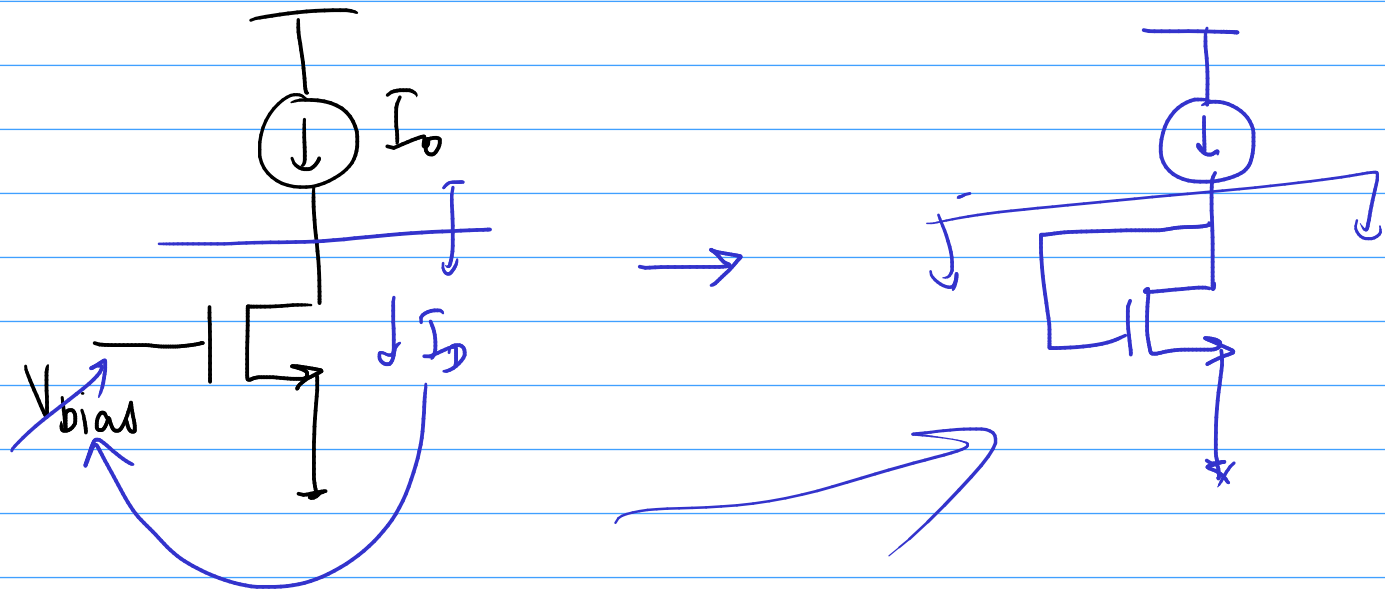

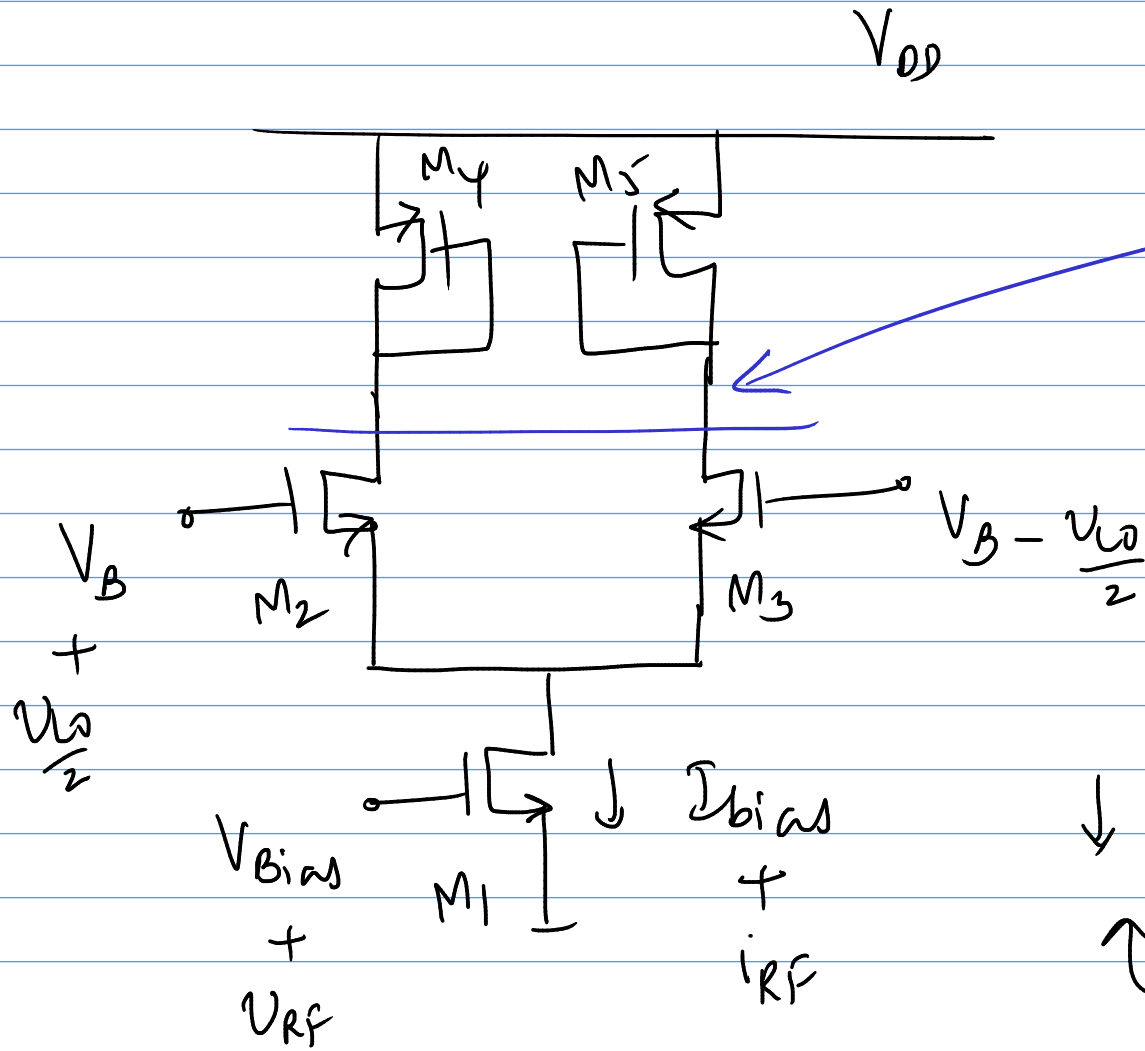

$$V_{O,DC} = V_{DD} - V_{DS_{4,5}} \left| \frac{I_{bias}}{2} \right.$$

$$V_{O,ac} = ( ? ) \cos \omega_{RF} t$$


$$A_v = \frac{2}{g_m} g_{m_1} \times \frac{1}{g_{m_{4,5}}}$$

↓  $V_{O,DC}$

↻ ↓  $\left(\frac{W}{L}\right)_{4,5}$

Make this small

Common-mode feedback  
(CMFB)


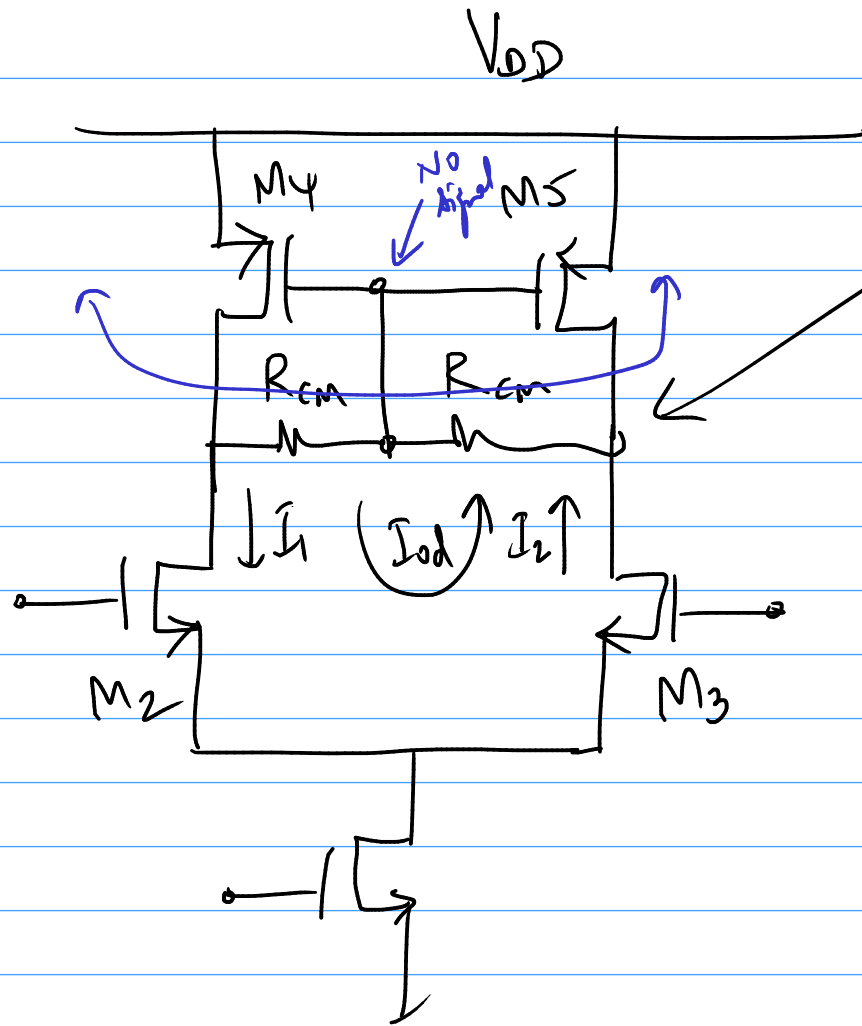



$$V_{o,DC} = V_{DD} - V_{S_{L_{4,5}}} \Big|_{\frac{I_{bias}}{2}}$$

$$A_v = \frac{2}{\pi} g_m (r_{ds_{4,5}} \parallel R_{cm})$$

Set  $V_{o,DC} \rightarrow$  set  $\left(\frac{W}{L}\right)_{4,5}$


set  $A_v \rightarrow$  set  $L_{4,5}$

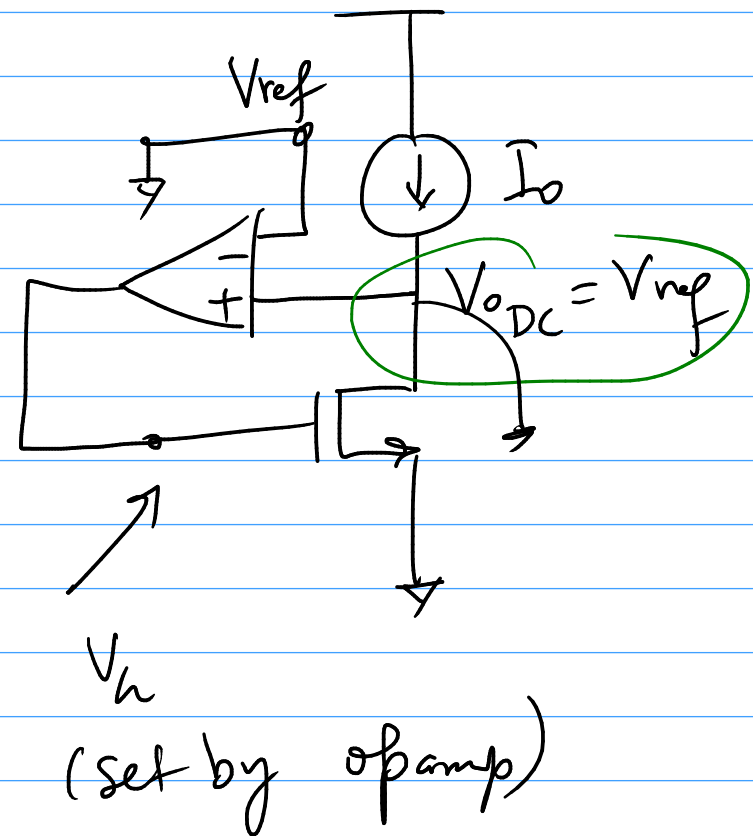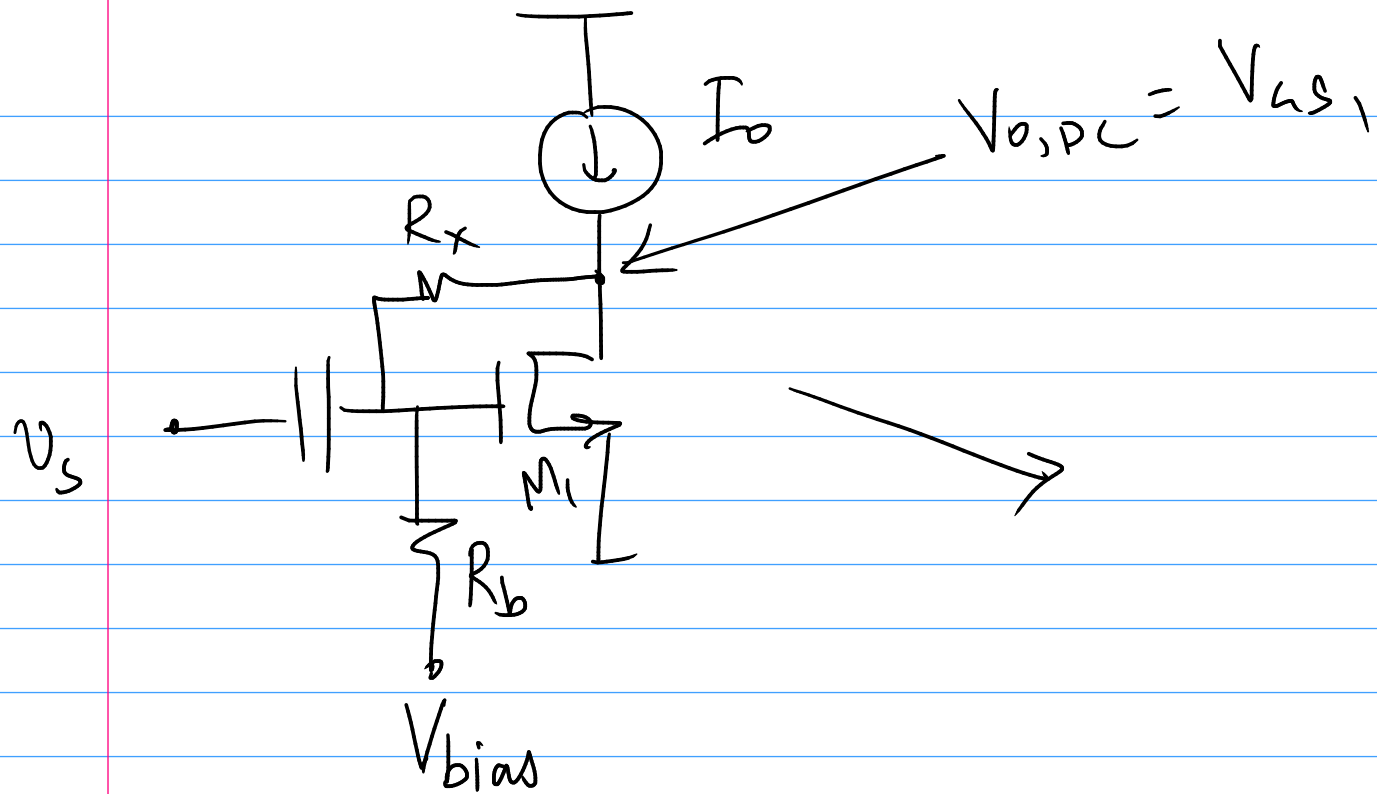


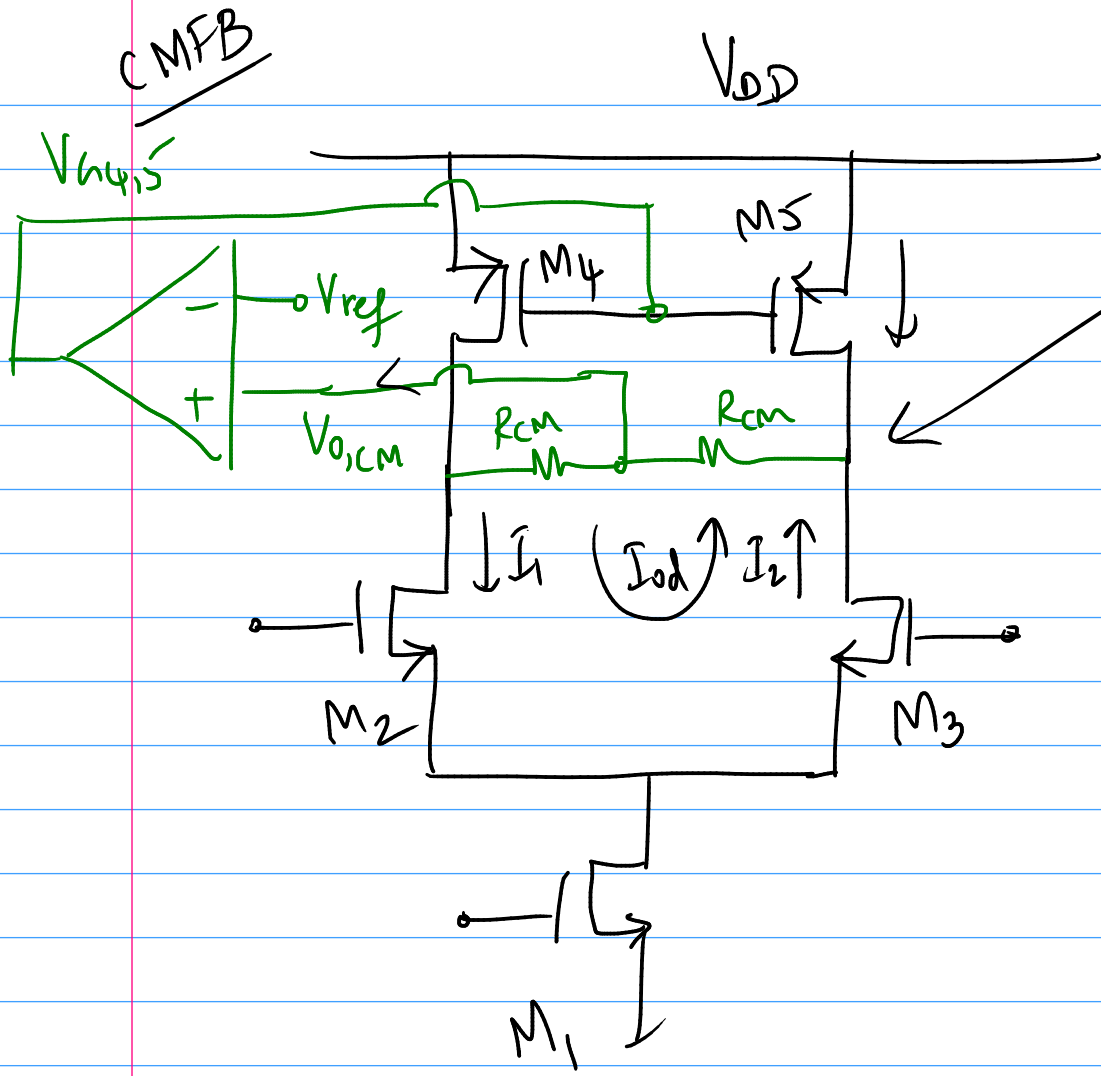


$V_{o,DC} = V_{ref}$  (set for max swing)

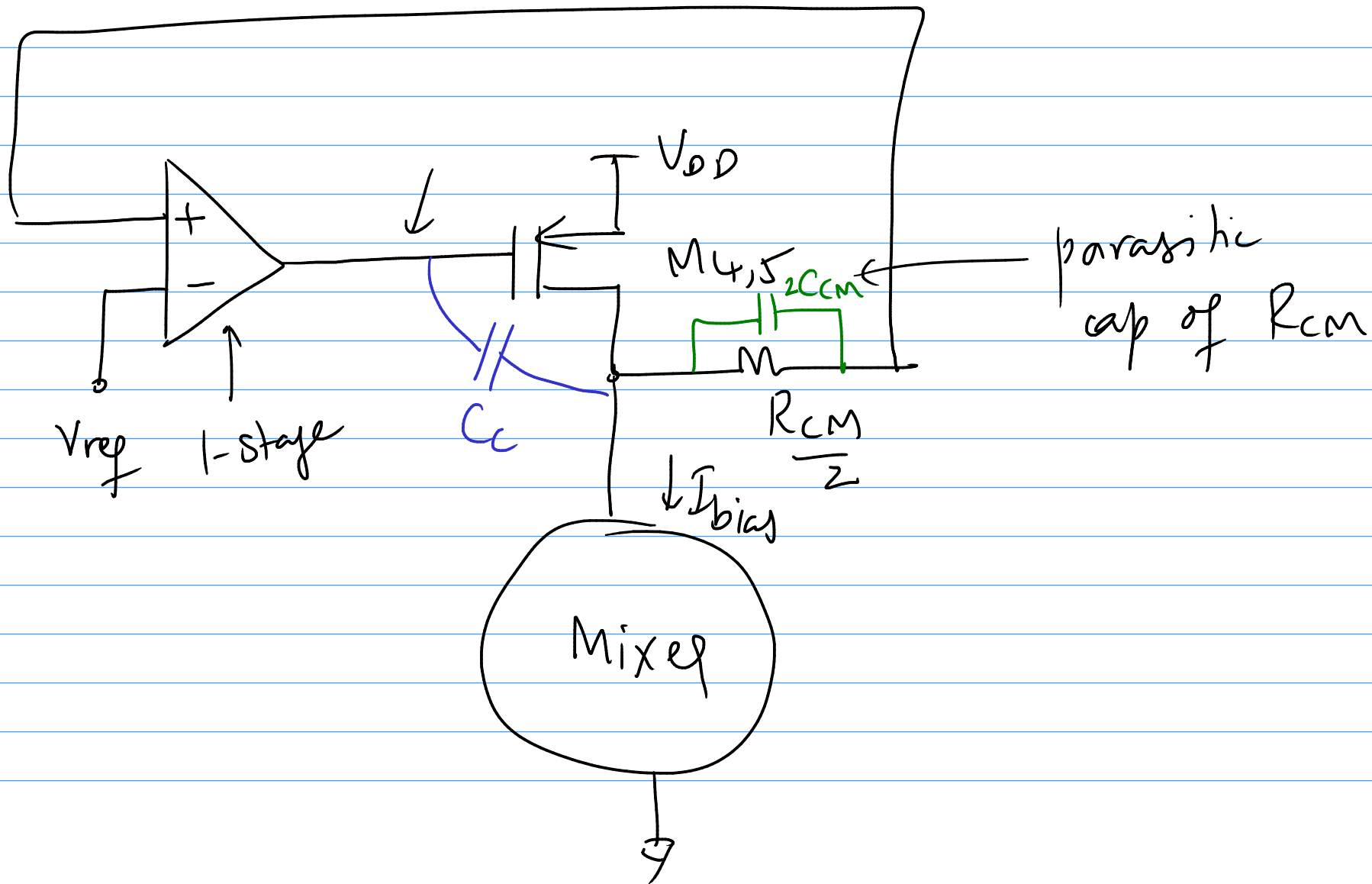
$$A_v = \frac{2}{\pi} g_m (g_{m4,5} \parallel R_{cm})$$



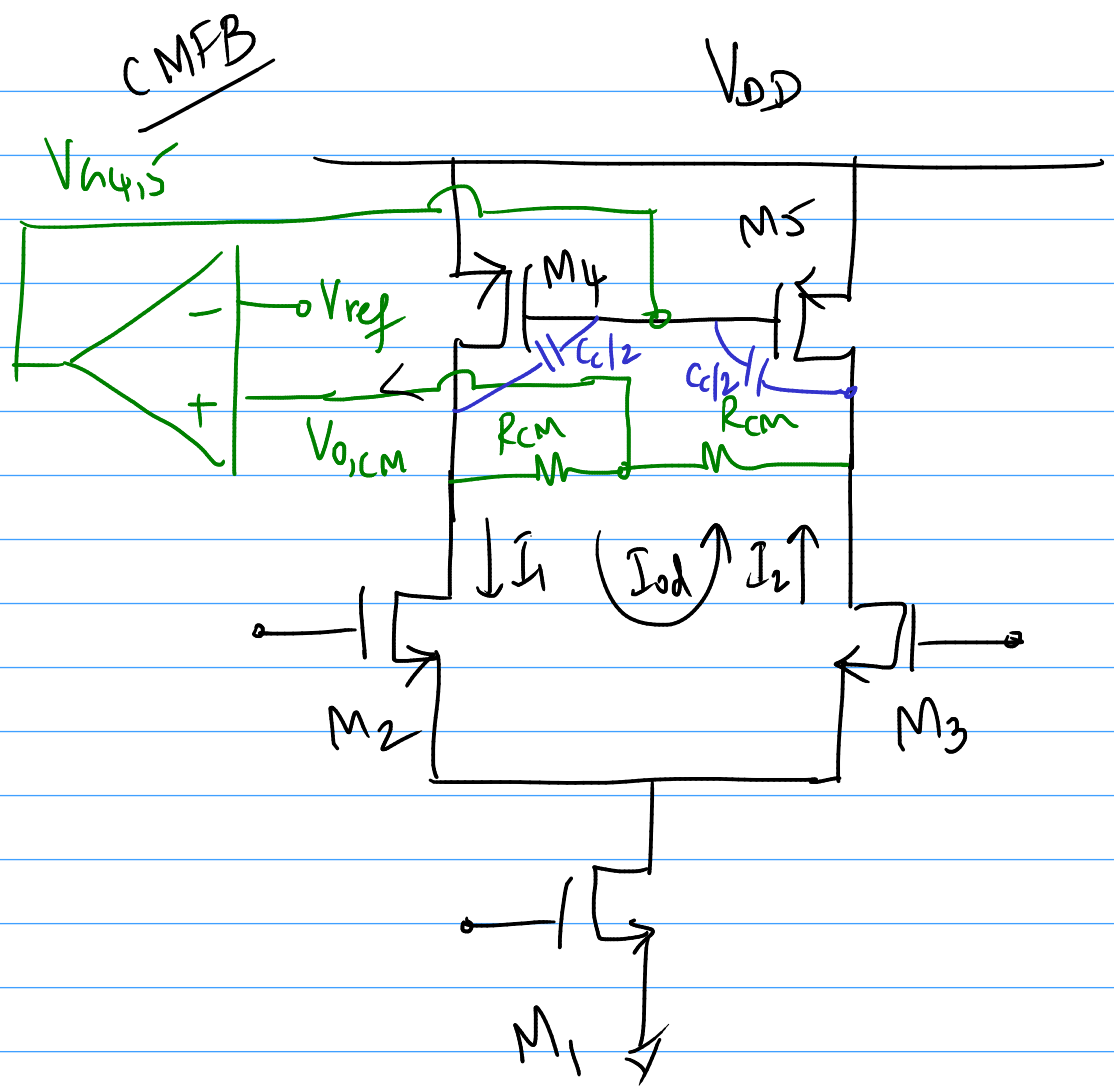


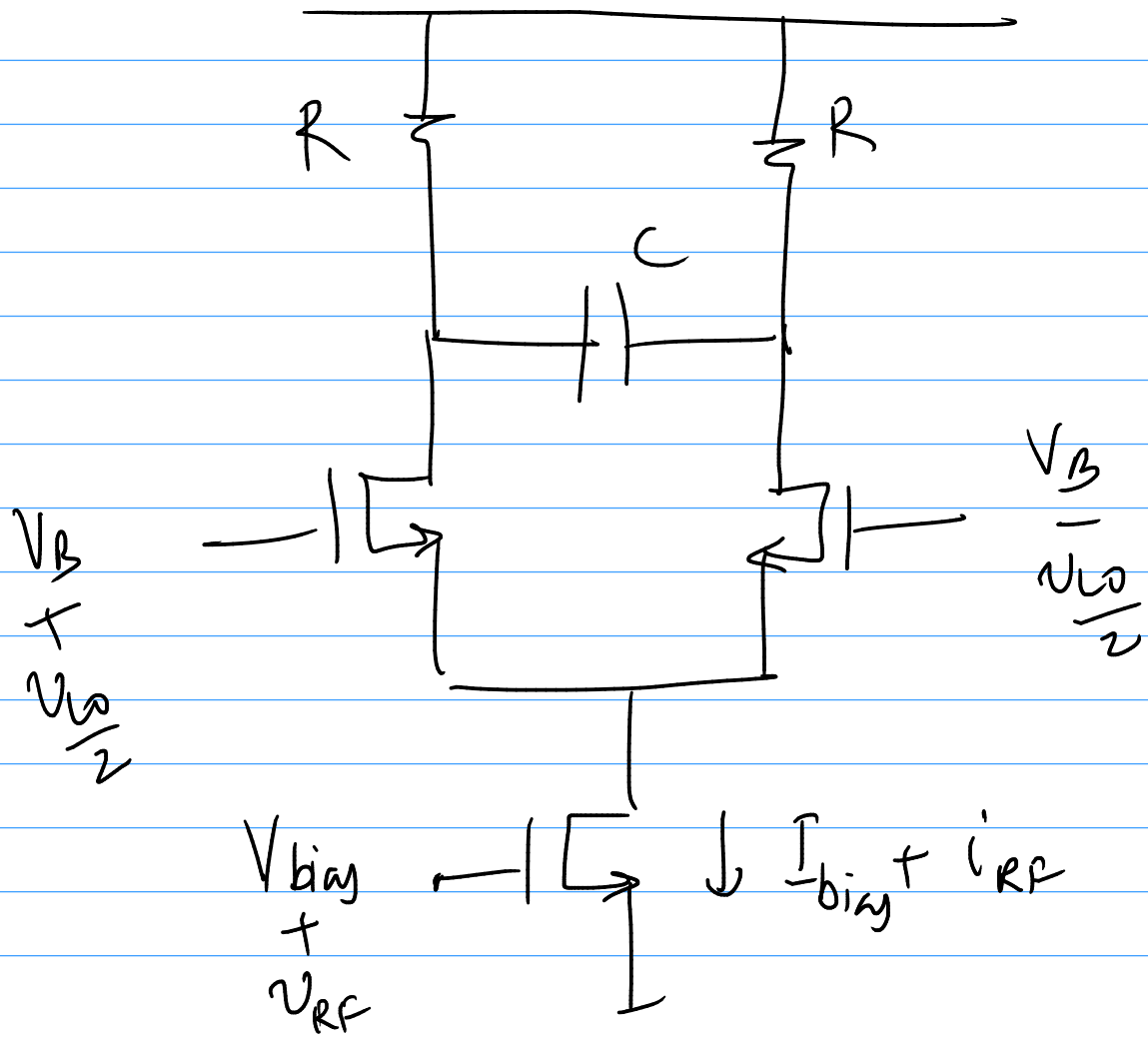


"Single-balanced"  
Mixer

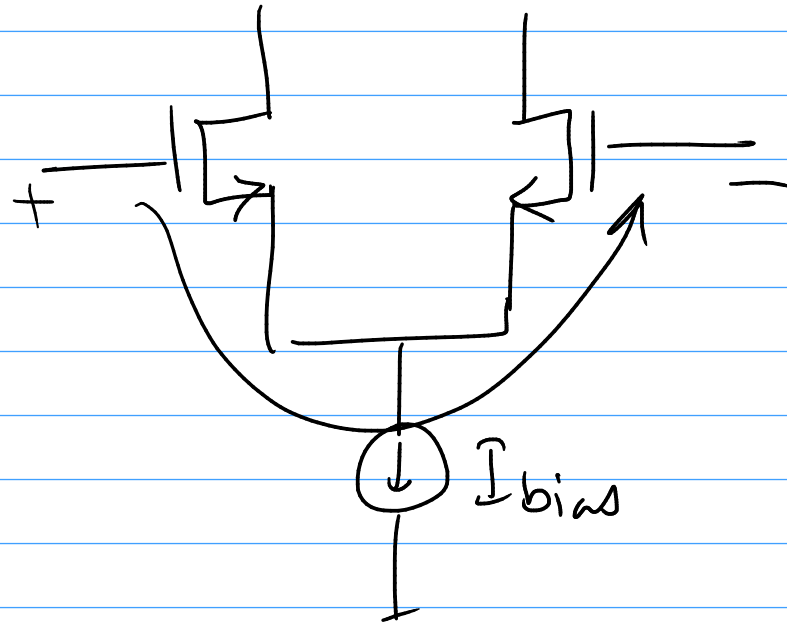


fully diff

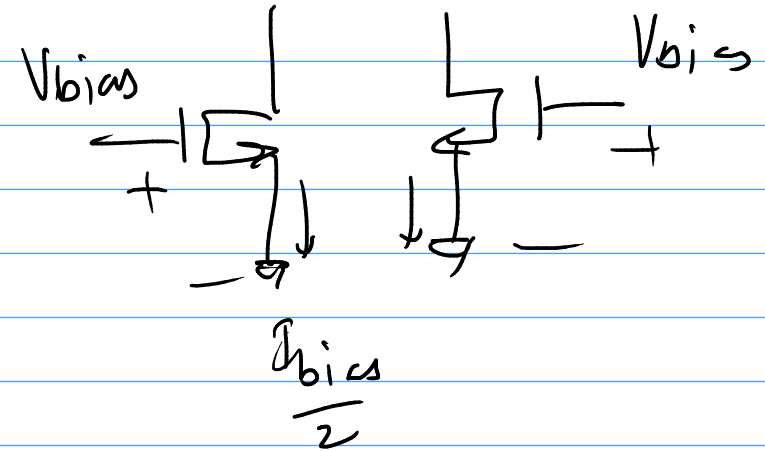

pseudo diff.

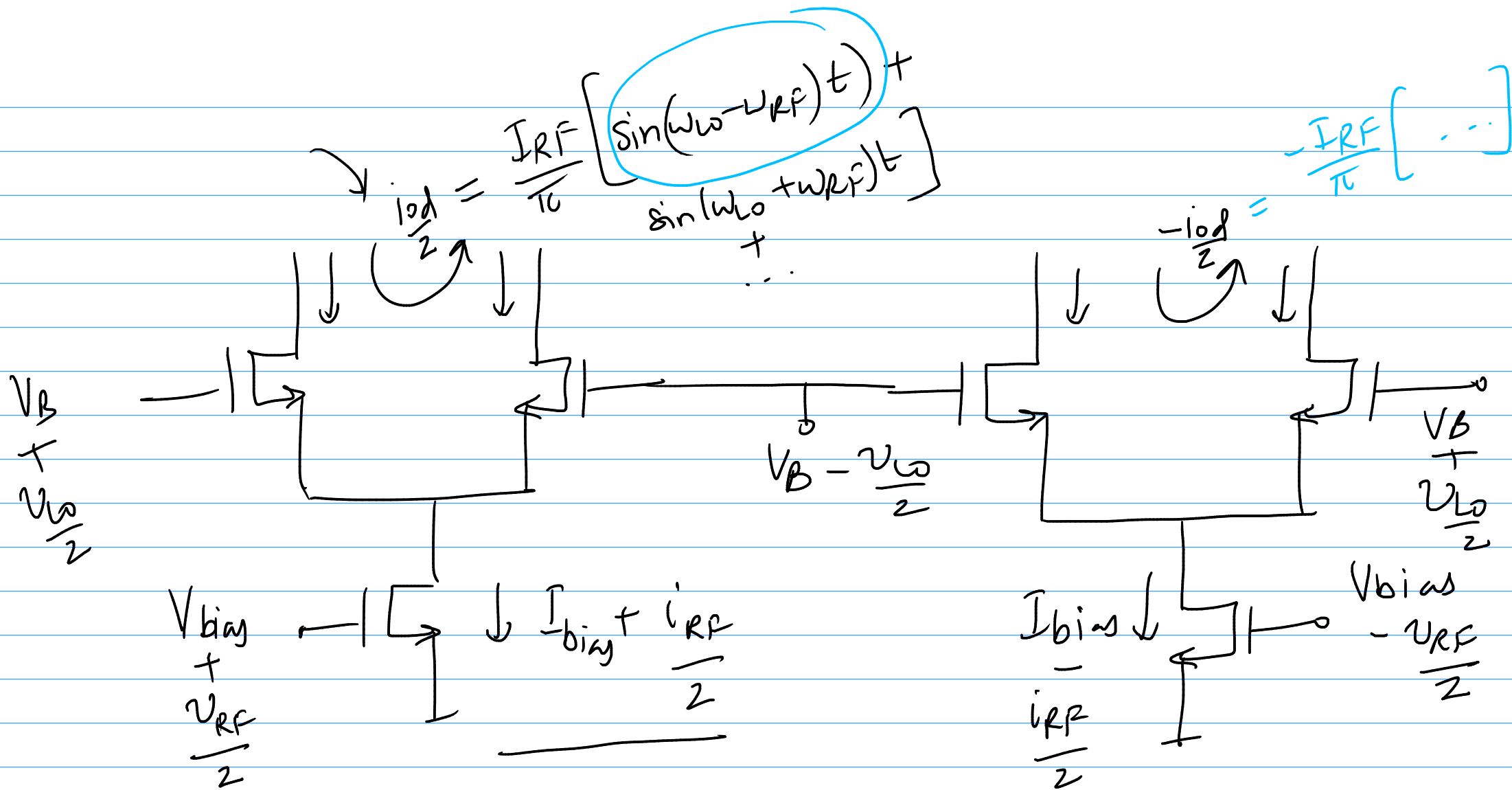


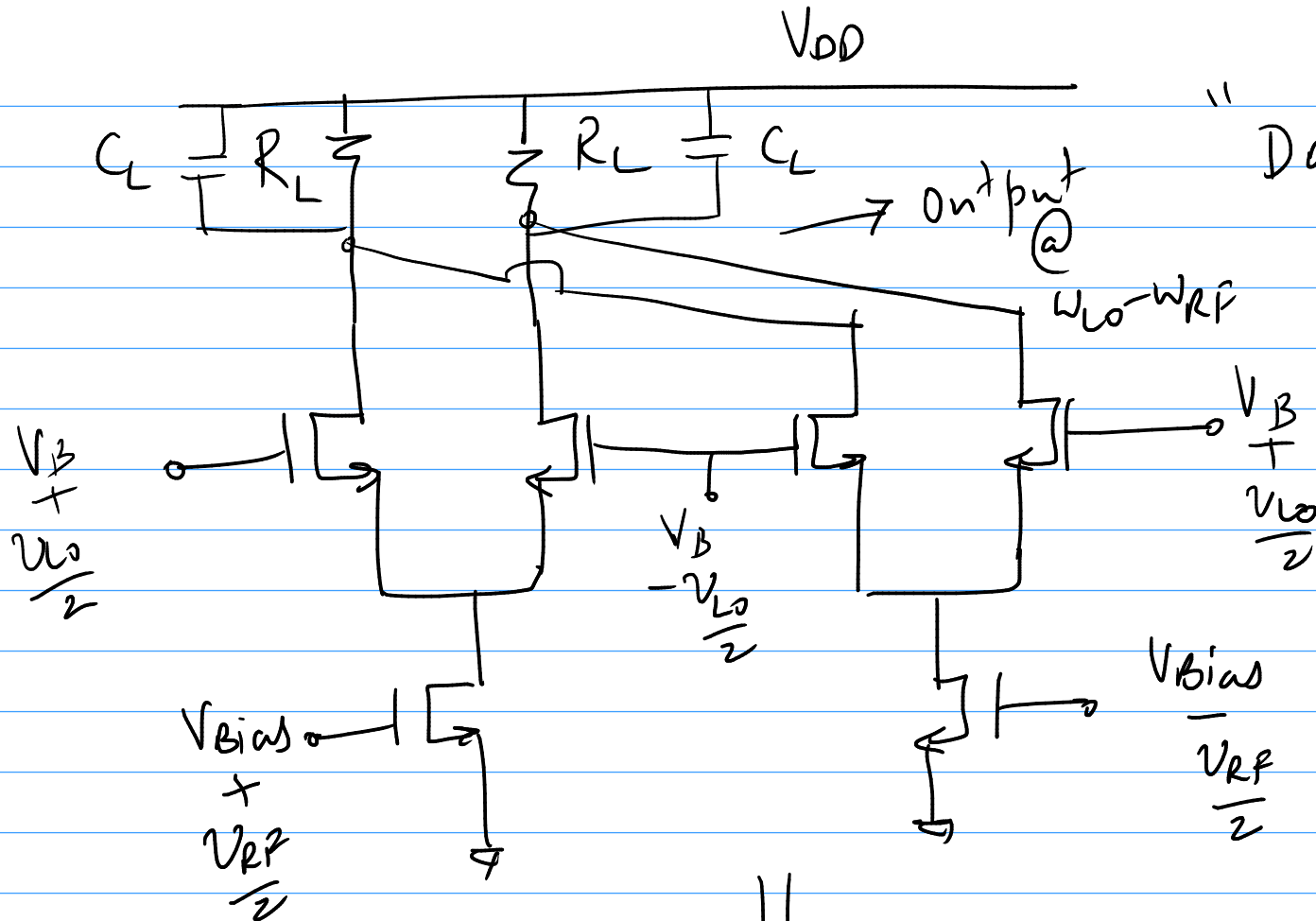


"Double-balanced" Mixer

(No LO feed-through)


Same gain

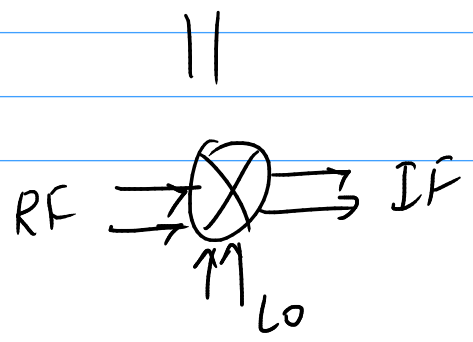


1)

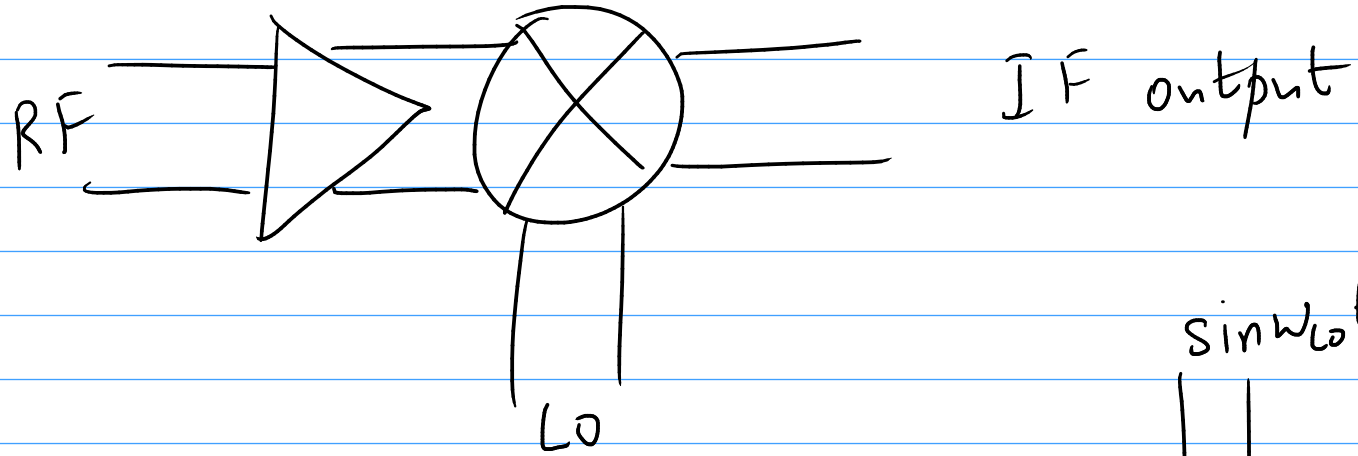


2)

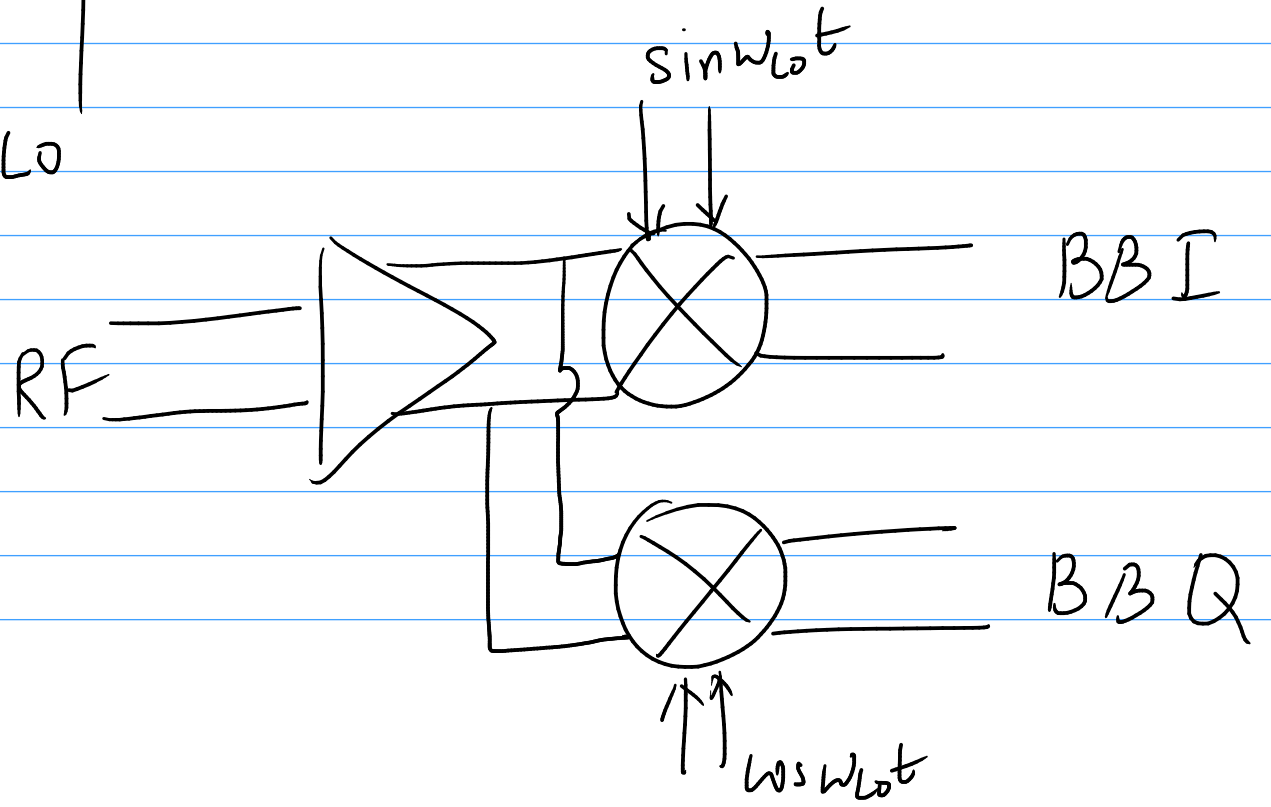


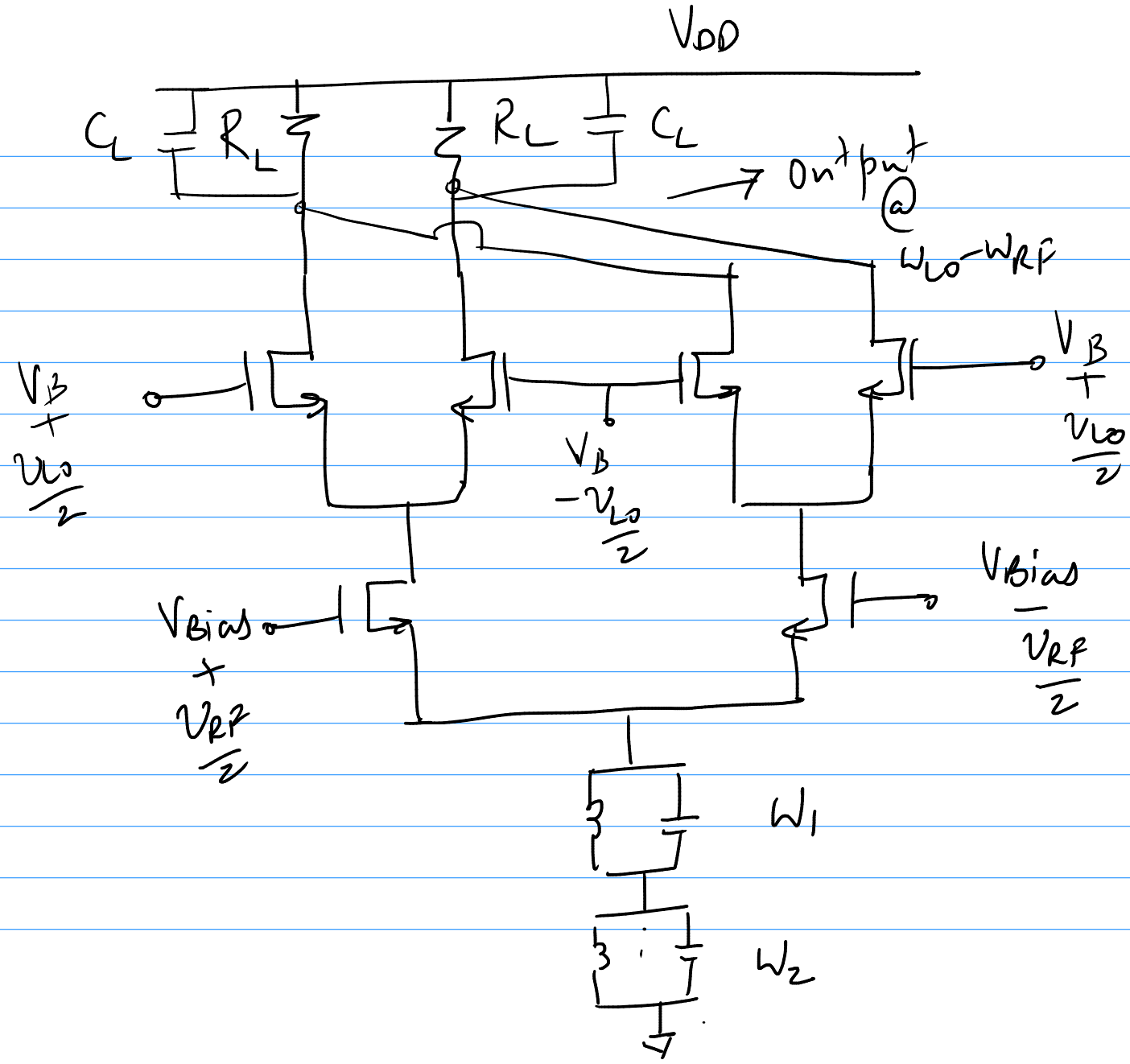


1)


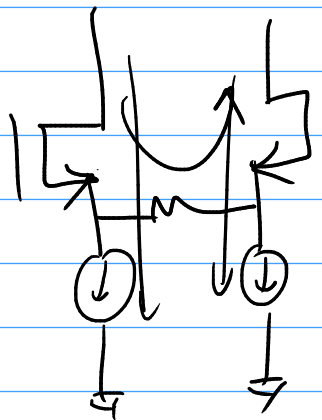



2)

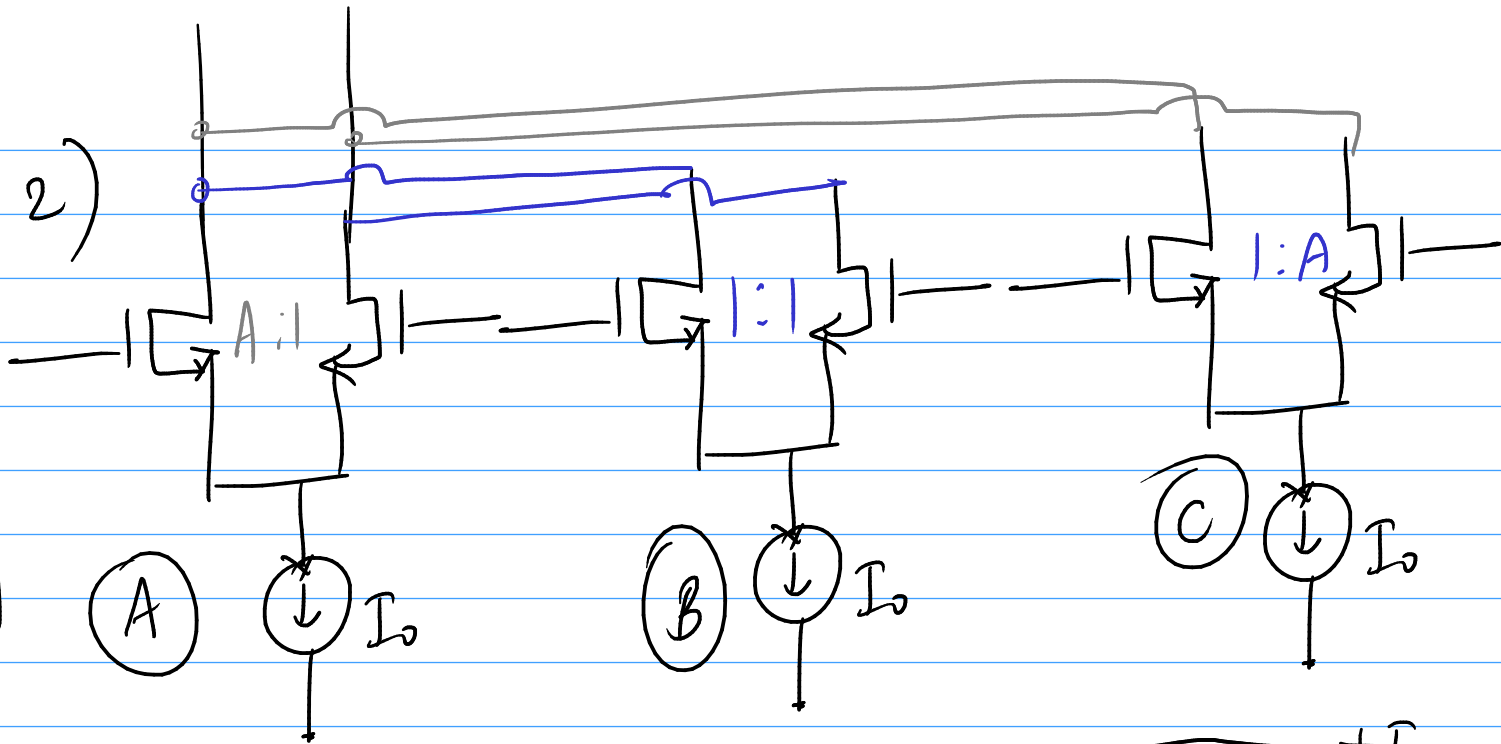

"Multi-tanh" transconductor

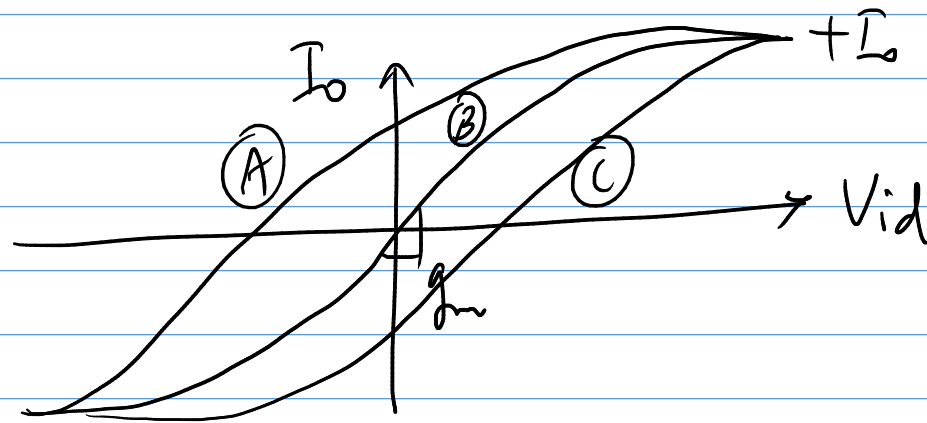


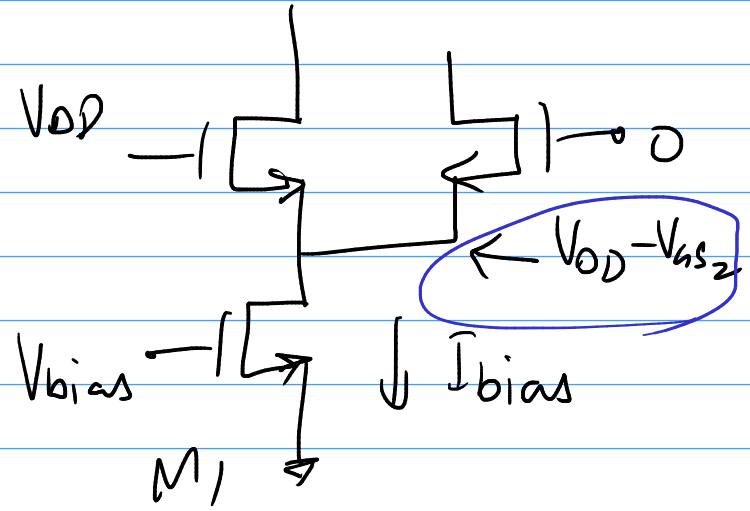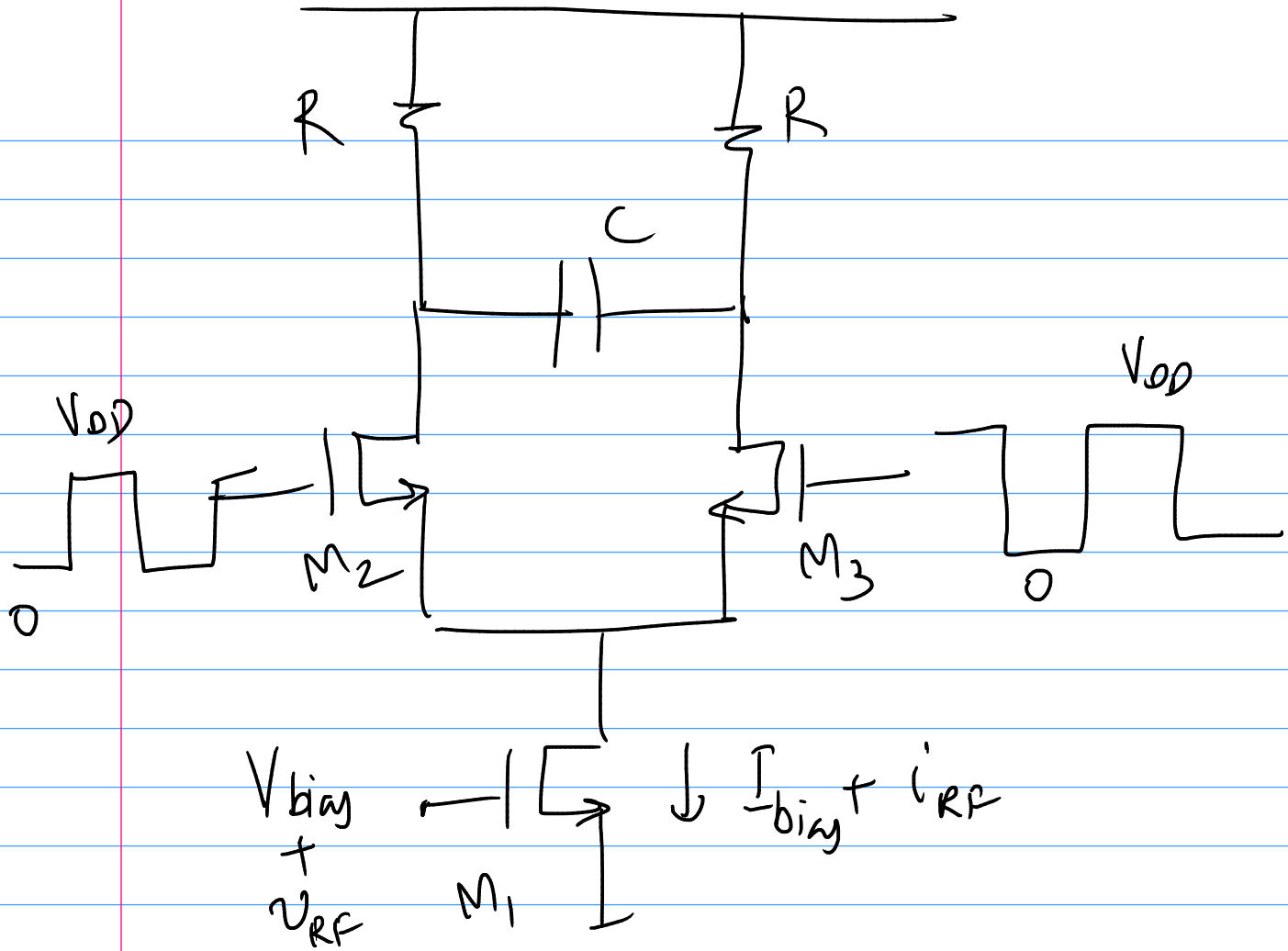

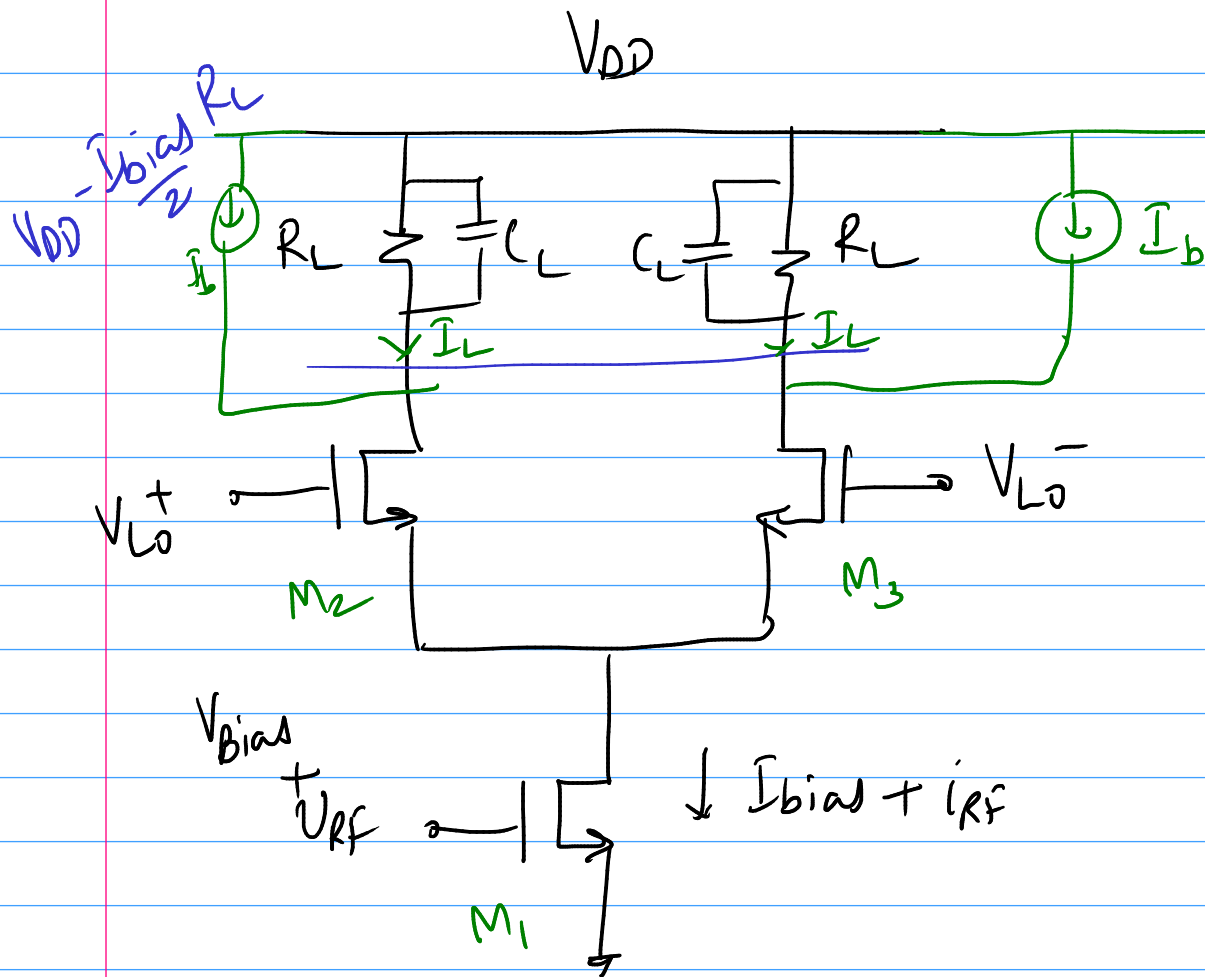


$$I_L = \frac{I_{bias}}{2} - I_b$$

We want small  $V_{sat_{2,3}}$

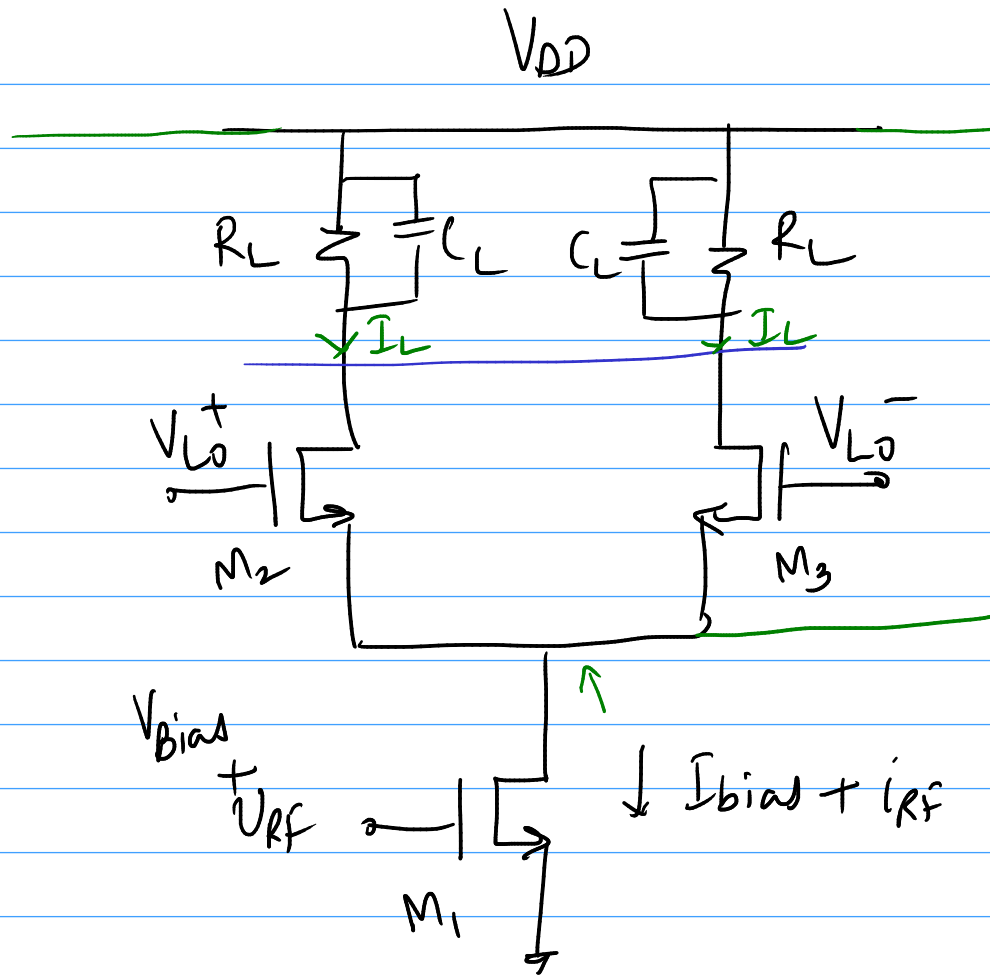

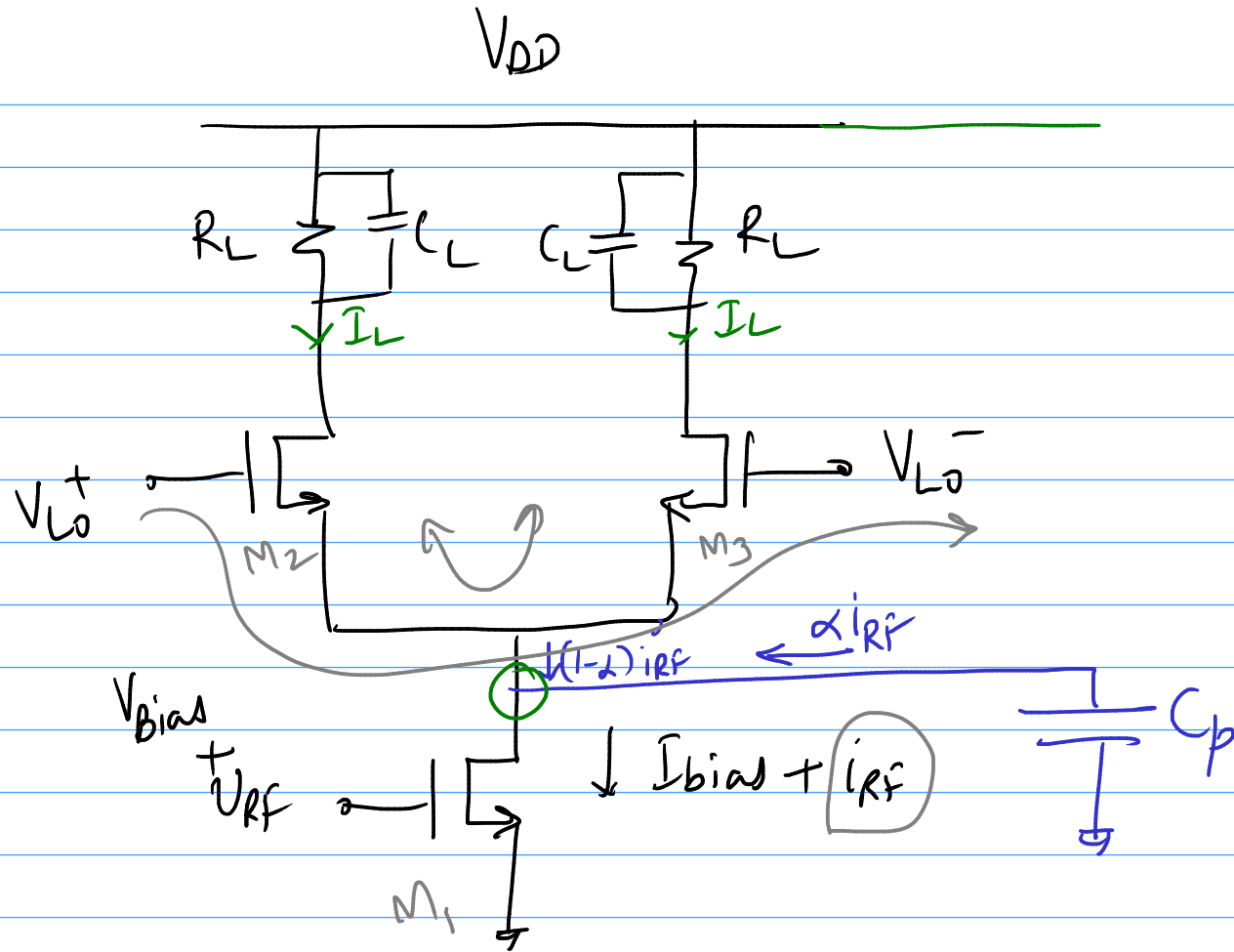$\rightarrow V_{b4}$  reduce  $V_{Dsat_{2,3}}$   
 $\downarrow$   
 $\uparrow \left(\frac{W}{L}\right)_{2,3}$  ,  $\downarrow I_{D_{2,3}}$   
 $\downarrow$   $\downarrow$   
 $\uparrow C_{gs_{2,3}}$   $I_{bias} - I_b$   
 $C_{db_{2,3}}$   $\frac{I_b}{2}$  ✓  
 $C_{sb_{2,3}}$   
 $\vdots$   
~~X~~



$$V_{LO}^+ - V_{LO}^- = V_{ds2} - V_{ds3} \quad \checkmark$$


$$I_{D_k} = \frac{1}{2} \mu C_{ox} \left(\frac{W}{L}\right)_k (V_{gs_k} - V_T)^2$$

$$I_{D_2} + I_{D_3} = I_{bias} + I_{Cp}$$


$$C_p \frac{dV_{cp}}{dt}$$

?

# Linearity of Mixer

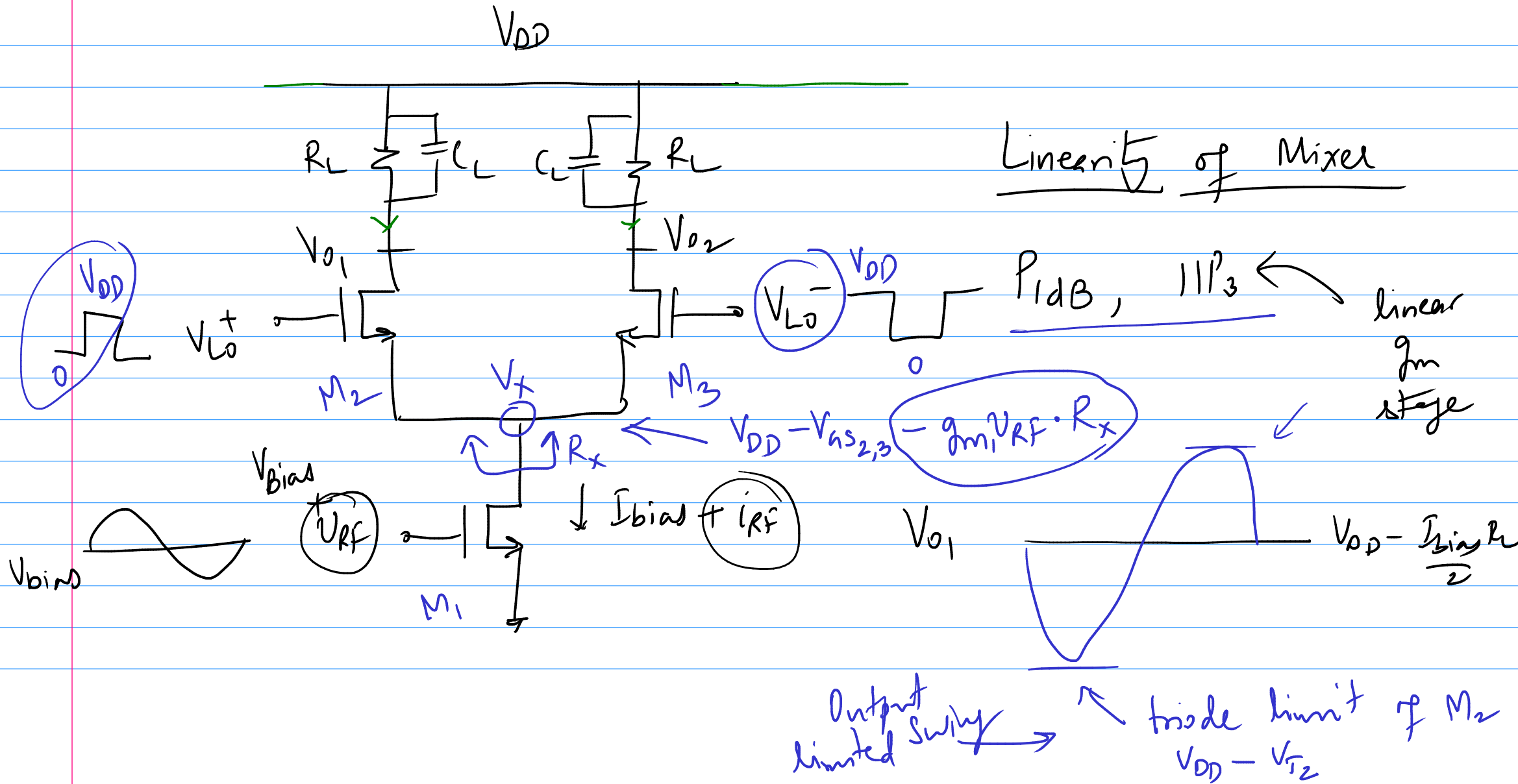

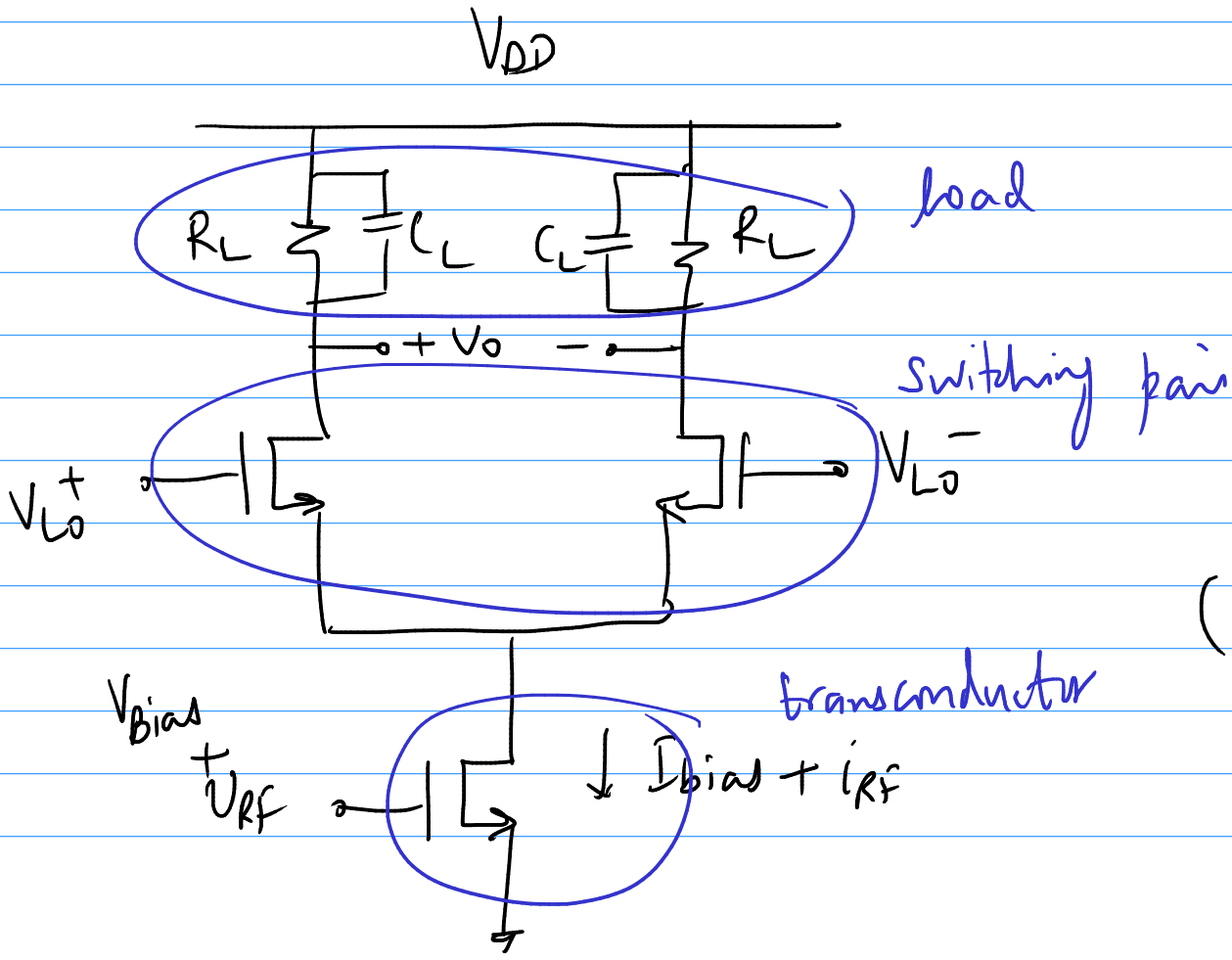Noise in active mixers  $\rightarrow$  NF, F




1) Load noise


(a)  $\frac{\overline{V_{onR_L}^2}}{\Delta f} = 8kTR_L$  ✓  
 or  $(\uparrow R_L \text{ for lower NF})$

(b) PMOS w/ CMFB

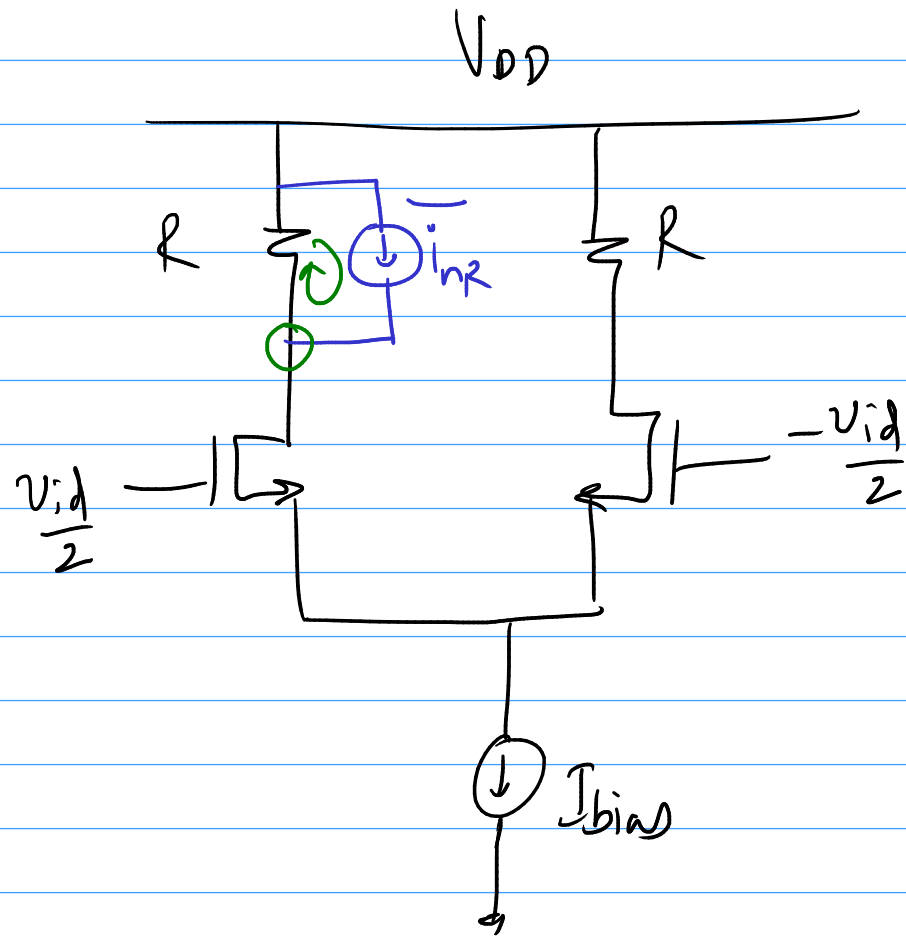(x)  $4kT \gamma^2 g_{m_{PMOS}}$   
 $\downarrow g_{m_{PMOS}} \rightarrow \downarrow \left(\frac{W}{L}\right)_{PMOS}$




HW


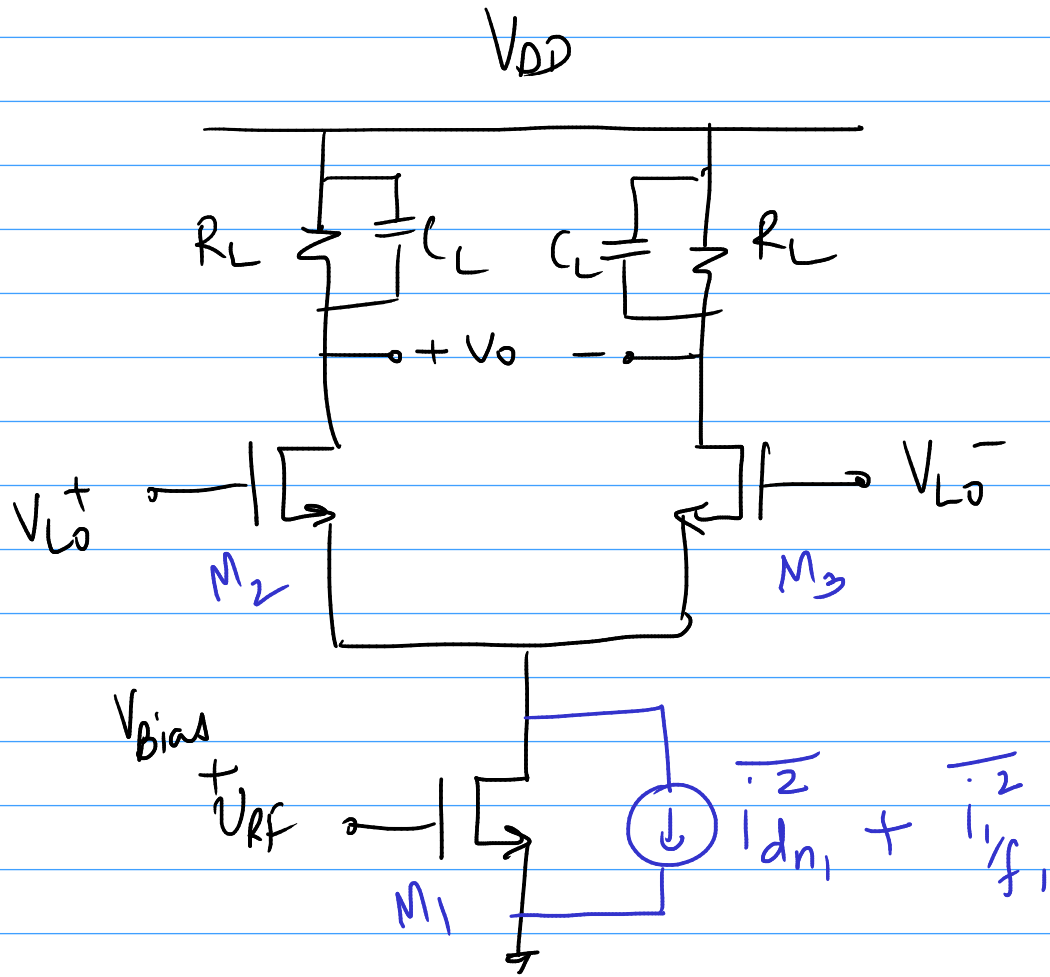


LPTV analysis

Effect on  $\overline{i_{n1}}$  is




Same as that for  $i_{RF}$

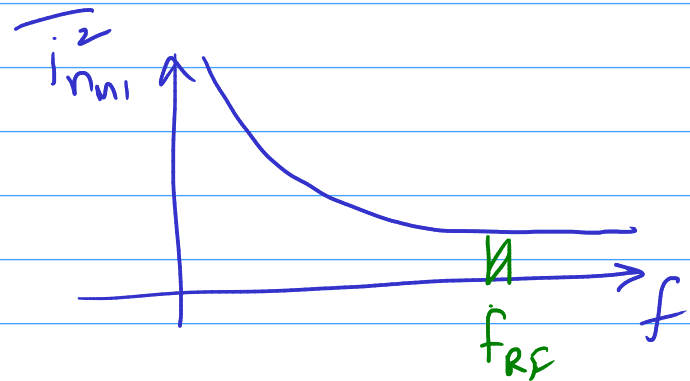

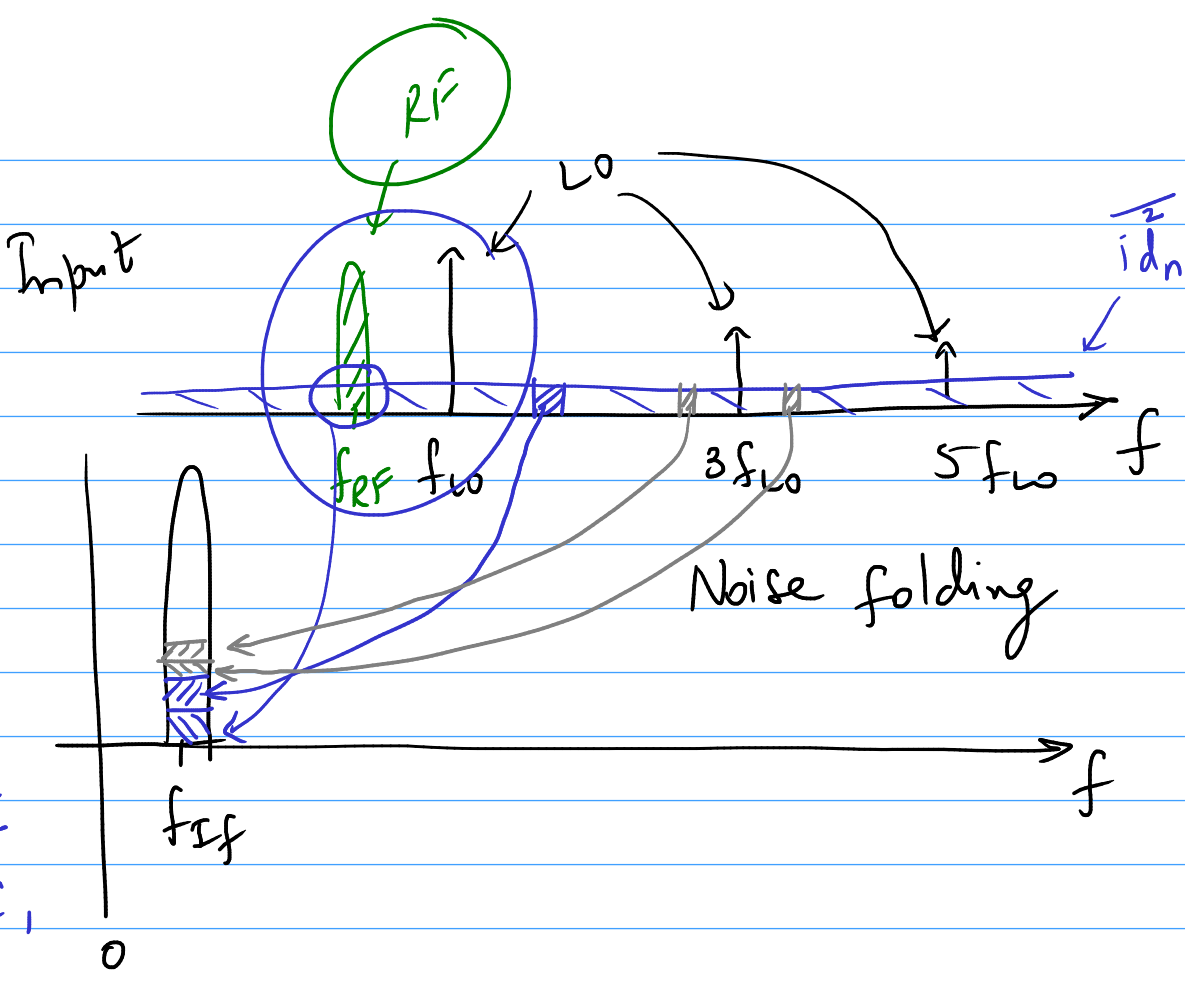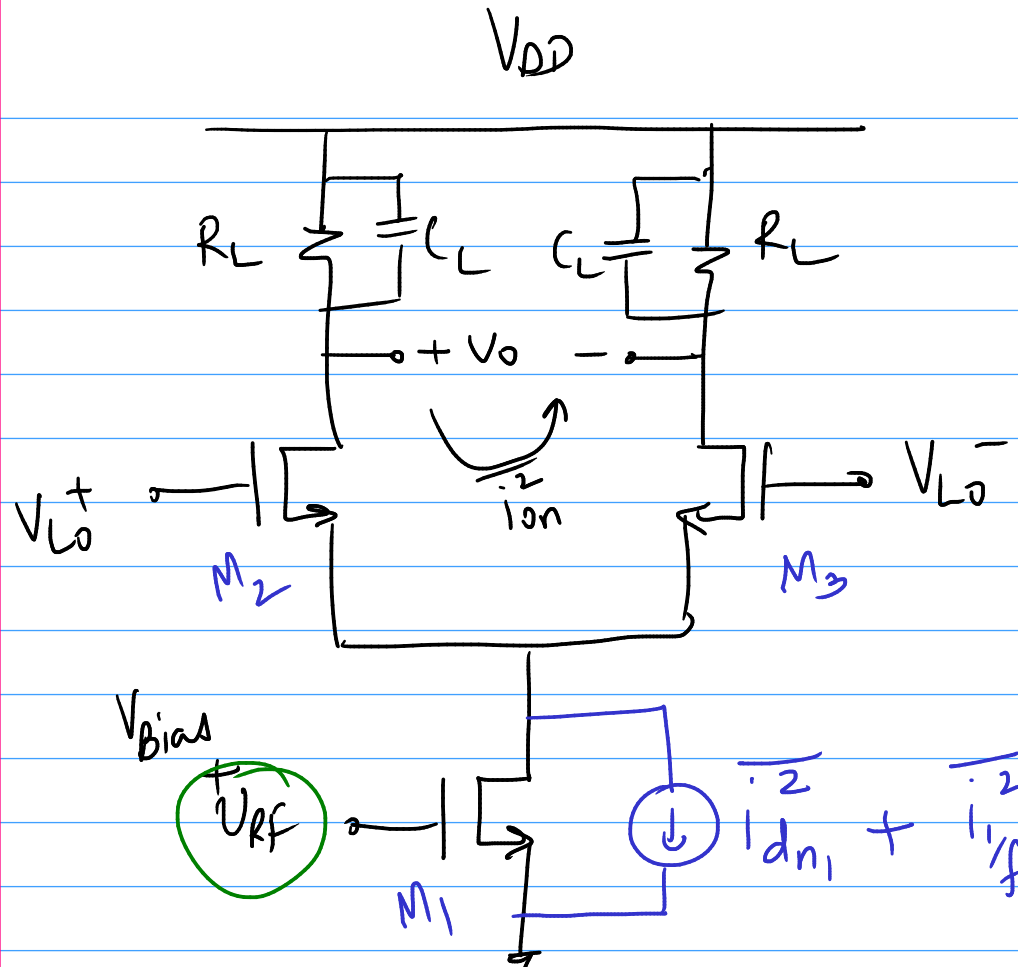


$$\frac{i_{on1}^2}{\Delta f} = 4kT \gamma^2 g_m \times \left(\frac{2}{\pi}\right)^2 \left[ 1 + \frac{1}{3^2} + \frac{1}{5^2} + \dots \right] \times 2$$

$\pi^2/8$

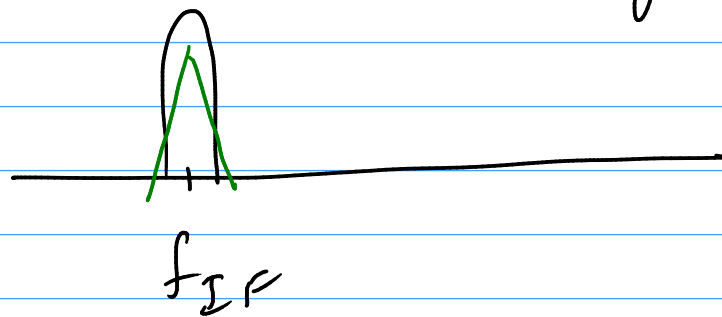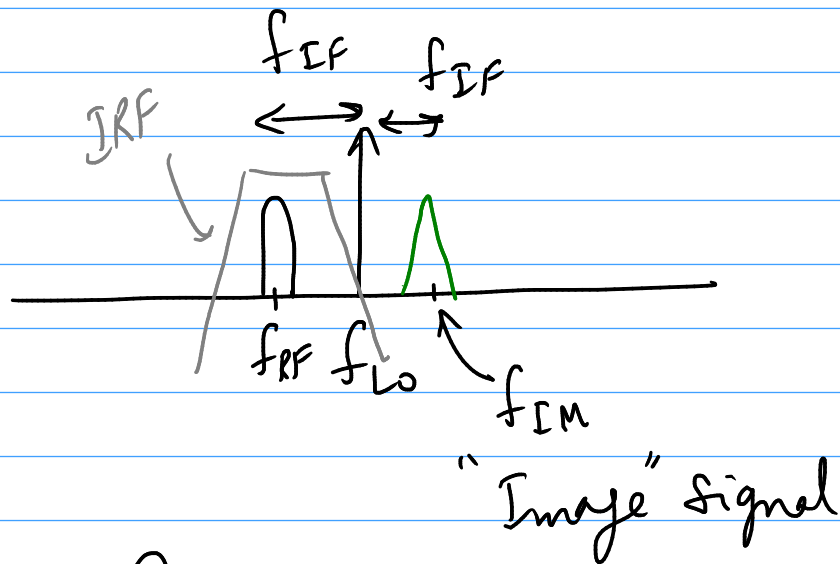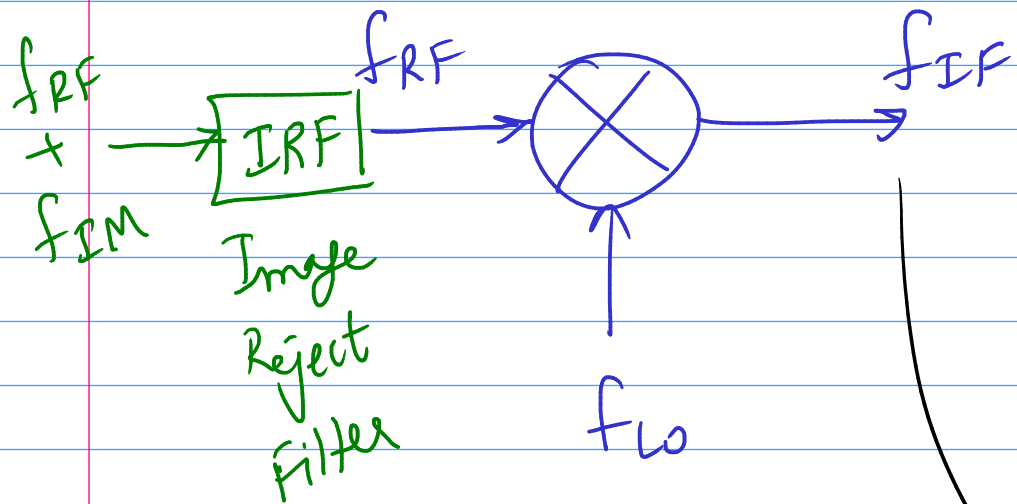

$$\frac{|i_{on}|^2}{\Delta f} = 4kT \gamma^2 g_m$$

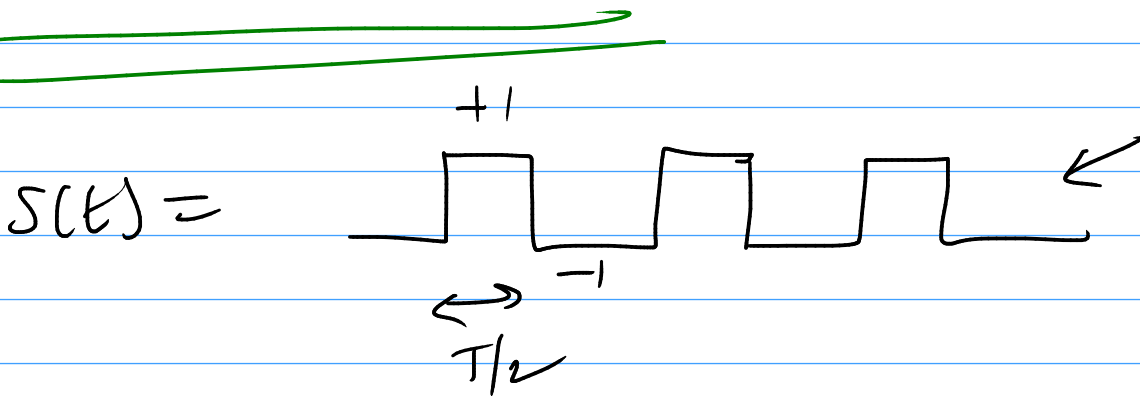


$$\sum |c_k|^2 = 1$$


$$S(t) = \sum_{k=-\infty}^{\infty} c_k e^{jk\omega_0 t}$$

drain thermal noise  
 $S_i(f - kf_{\omega}) = S_i$



$$S_o(f) = \sum_{-\infty}^{\infty} |c_k|^2 \cdot S_i(f - kf_{\omega}) = S_i \sum_{-\infty}^{\infty} |c_k|^2$$

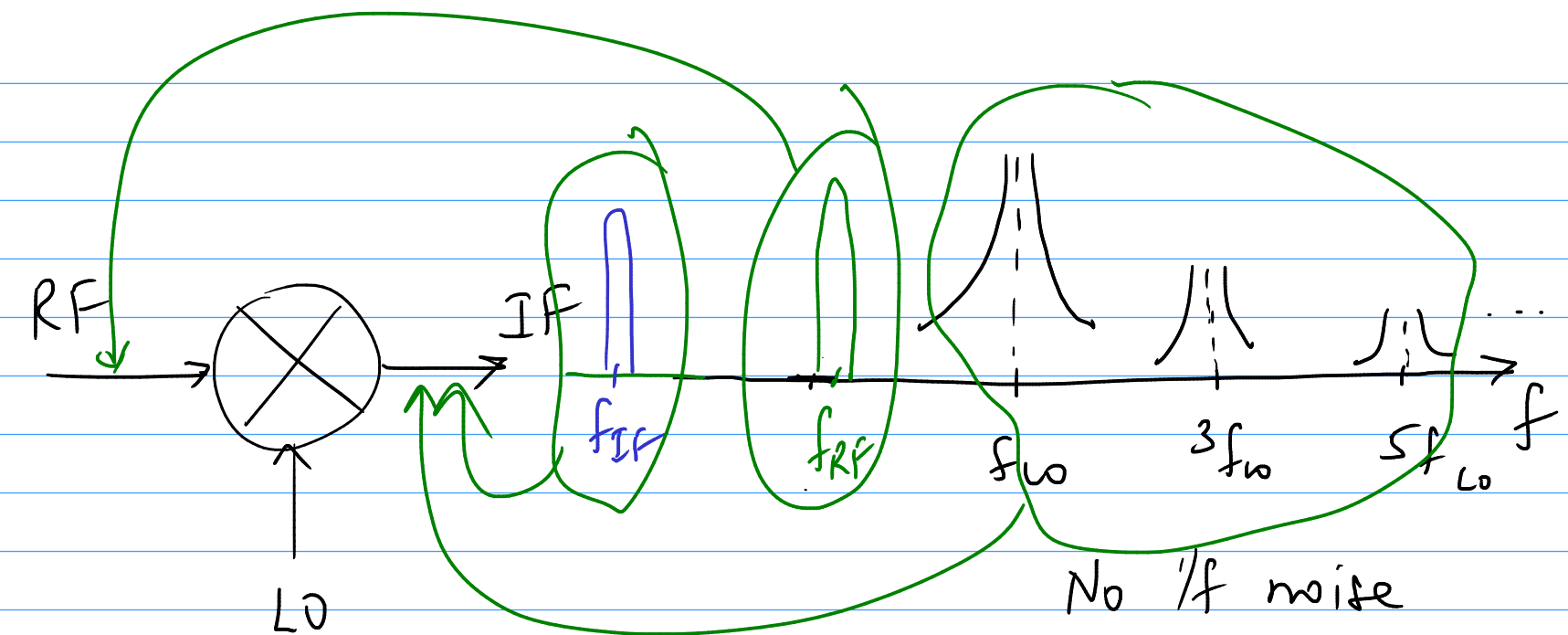

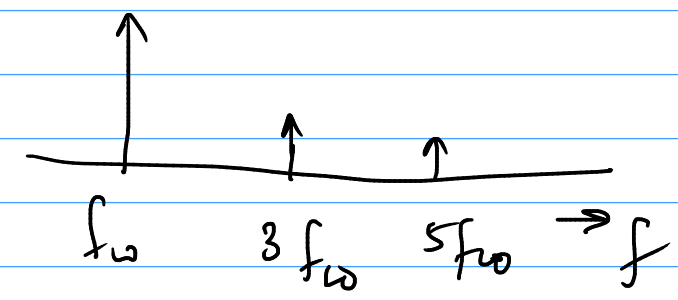
No  $1/f$  noise contribution @  $f_{IF}$  for  $R_x$  mixer



# Tx mixer

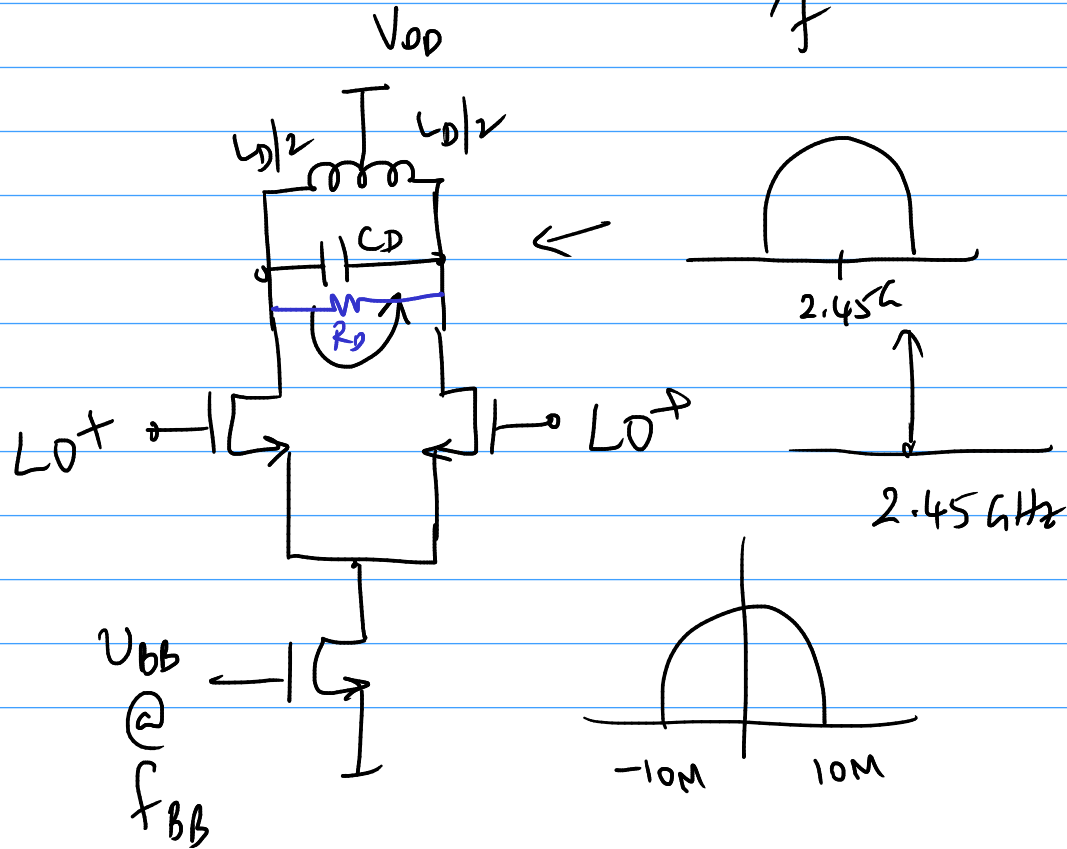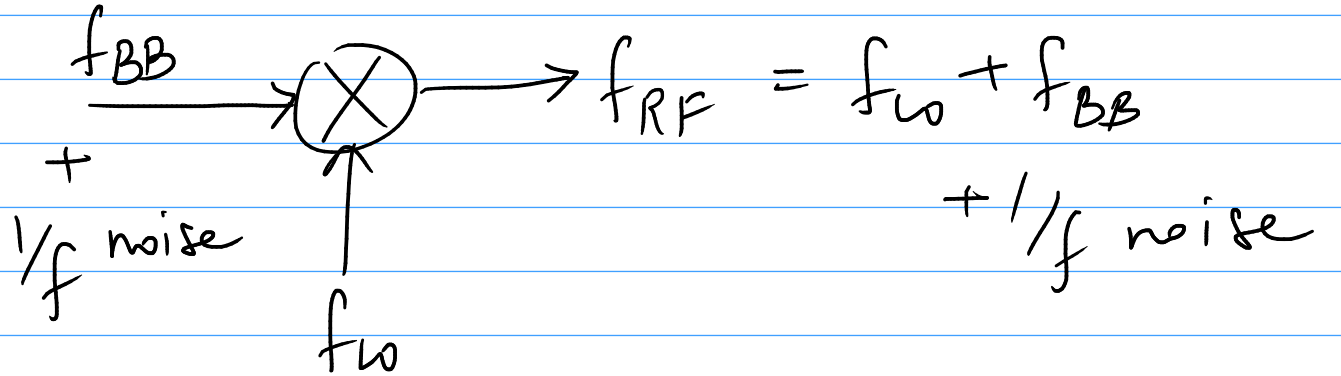

# Noise from Switches

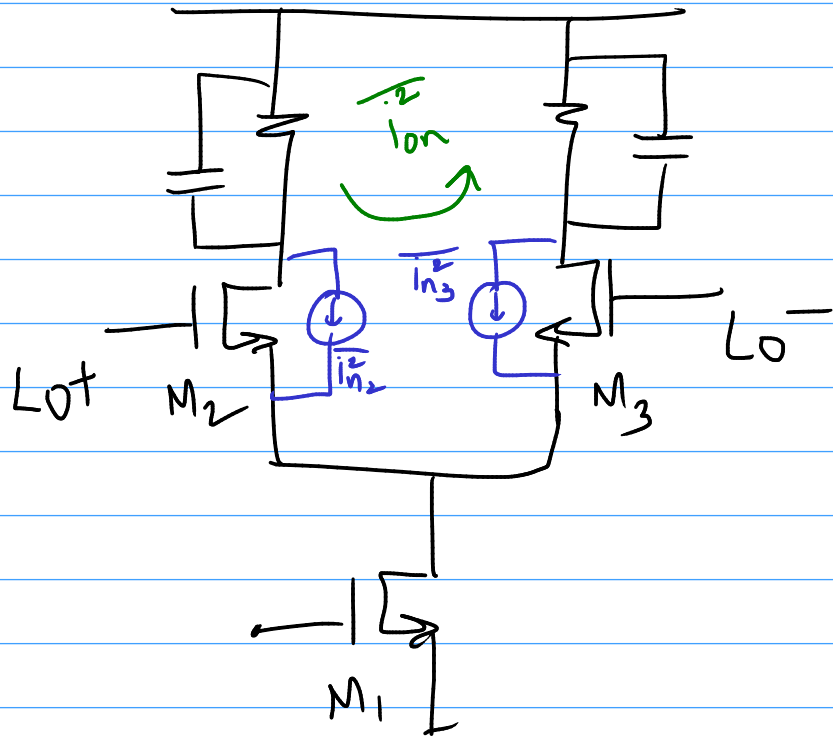

$$\overline{i_{o2}(t)} = \overline{i_{n2}(t)} \cdot a_2(t)$$

$$\overline{i_{o3}(t)} = \overline{i_{n3}(t)} \cdot a_3(t)$$

$$a_2(t) = a_2(t - kT_{Lo}) \quad \left. \vphantom{a_2(t)} \right\} \text{LP TV}$$

$$a_3(t) = a_3(t - kT_{Lo}) \quad \left. \vphantom{a_3(t)} \right\}$$

$$a_m(t) = \sum_{k=-\infty}^{\infty} a_{mk} \cdot e^{jk\omega_0 t}$$

$$i_{o_m}(t) = \overline{i_{n_m}(t)} \cdot a_m(t)$$

$$= \left[ \sum_{-\infty}^{\infty} a_{mk} e^{-jk\omega_0 t} \right] \cdot \overline{i_{n_m}(t)}$$

$$= \sum_{-\infty}^{\infty} a_{mk} \left( e^{-jk\omega_0 t} \cdot \overline{i_{n_m}(t)} \right)$$

$$S_{o_n}(f) = \sum_m \sum_{k=-\infty}^{\infty} |a_{mk}|^2 \cdot S_{n_m}(f - k f_{\omega_0})$$

$$S_{n_m}(f) = 4kT \gamma_{gm} S_W = S_{n_m}(f - k f_{\omega_0})$$

$$S_{on}^{tot}(f) = \sum_3 \sum_{k=-\infty}^{\infty} |a_{mk}|^2 (4kT \gamma g_{m,sw})$$

$$= \sum_3 4kT \gamma g_{m,sw} \cdot \underbrace{\sum_{k=-\infty}^{\infty} |a_{mk}|^2}$$


$$= \frac{1}{T_{Lo}} \int_0^{T_{Lo}} |a_m(t)|^2 dt$$

$$= A$$

$$S_{on}^{tot.}(f) = 2 \times 4kT \gamma g_{m,sw} \cdot A$$

$$a_m(t) = \left\{ \begin{array}{l} 0 \\ 1 \end{array} \right. \left. \begin{array}{l} \text{OFF} \\ \text{ON} \end{array} \right\} \quad A = \sum_{-\infty}^{\infty} |a_{mk}|^2 = \frac{1}{2}$$

In reality

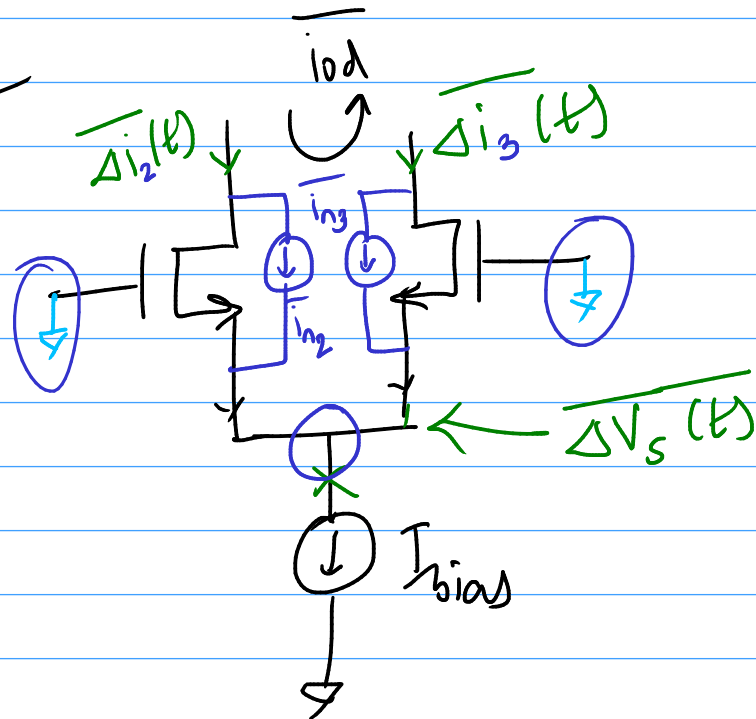

$$\overline{\Delta i_2(t)} + \overline{\Delta i_3(t)} = 0$$

$$\overline{\Delta i_2(t)} = \overline{i_{n2}(t)} - g_{m2}(t) \Delta V_s(t)$$


$$\overline{\Delta i_3(t)} = \overline{i_{n3}(t)} - g_{m3}(t) \Delta V_s(t)$$

$$\Delta V_s(t) = \frac{\overline{i_{n2}(t)} + \overline{i_{n3}(t)}}{g_{m2}(t) + g_{m3}(t)}$$

$$\begin{aligned} \overline{i_{od}} &= \Delta i_2(t) - \Delta i_3(t) \\ &= \left( \frac{2g_{m3}(t)}{g_{m2}(t) + g_{m3}(t)} \right) \overline{i_{n2}(t)} - \left( \frac{2g_{m2}(t)}{g_{m2}(t) + g_{m3}(t)} \right) \overline{i_{n3}(t)} \end{aligned}$$




$a_2(t)$   $a_3(t)$





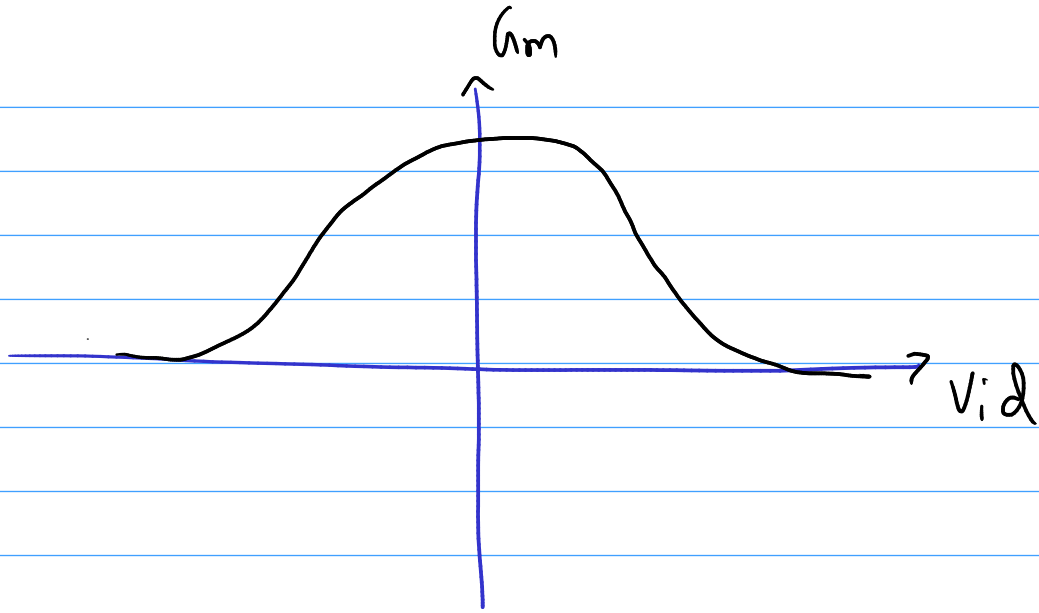

$F = ?$


HW

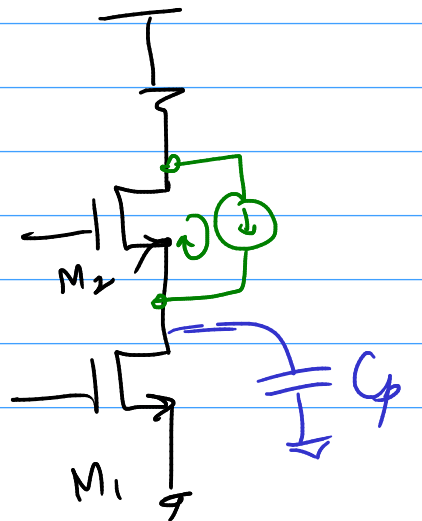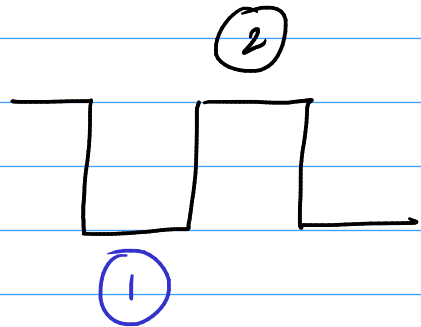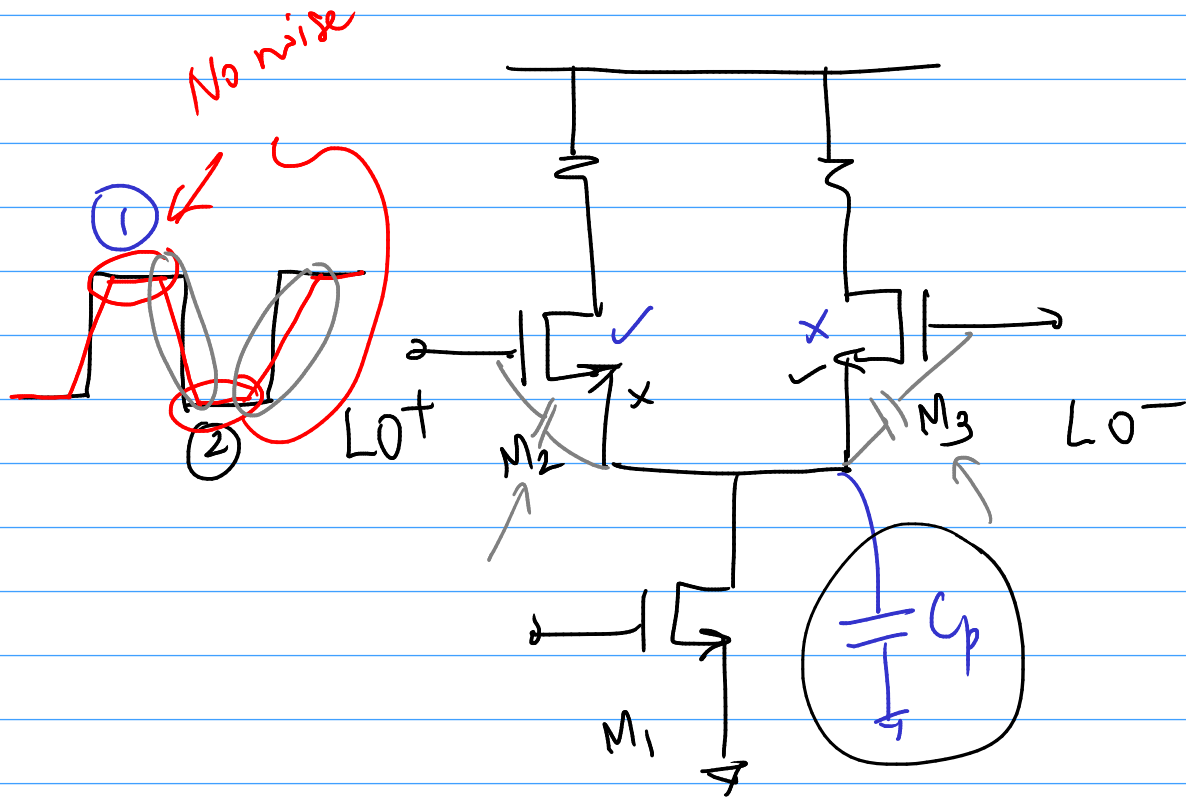

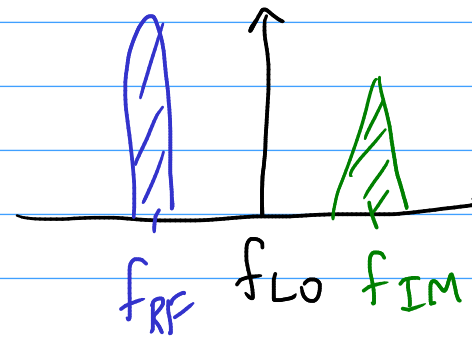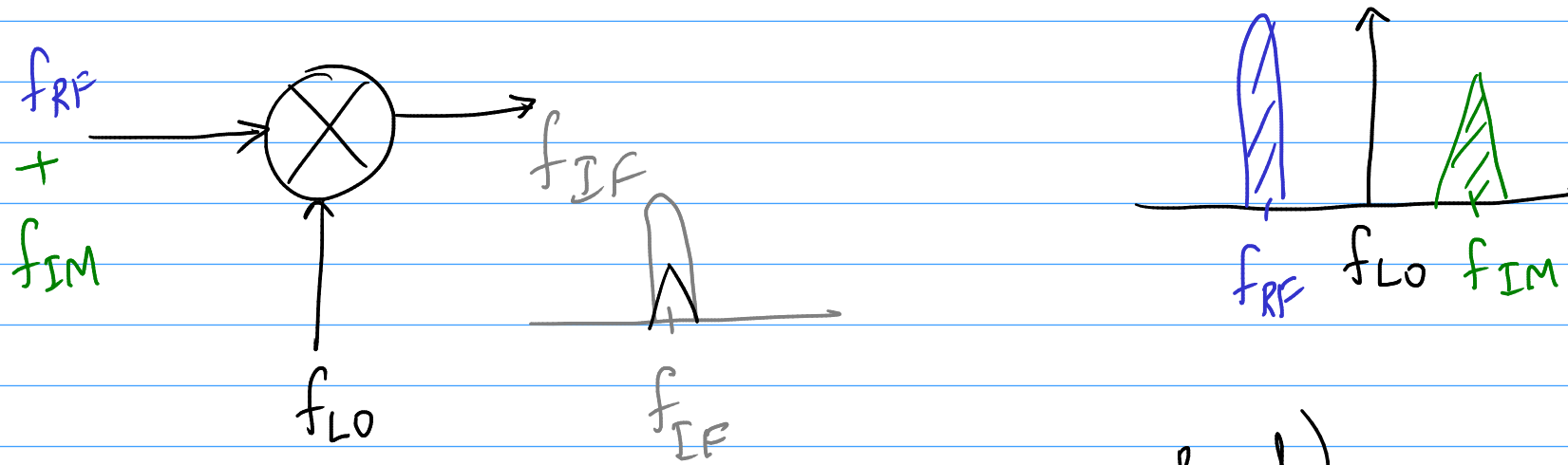


(Double Side Band)

DSB noise figure

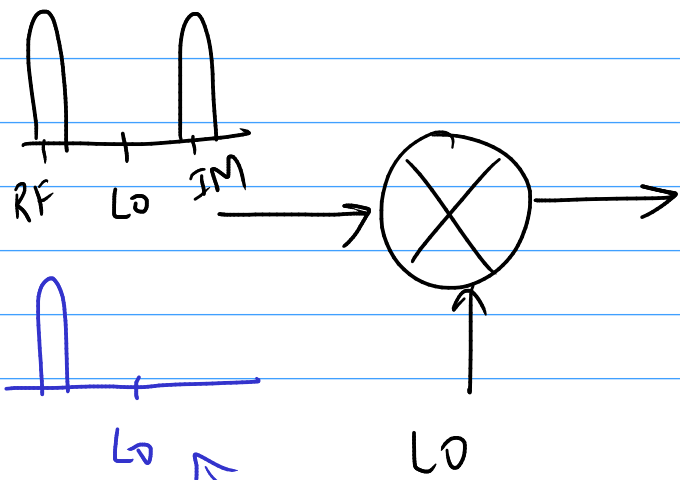

$$\frac{SNR_i}{SNR_o} = NF$$


SSB noise figure = DSB NF + 3 dB

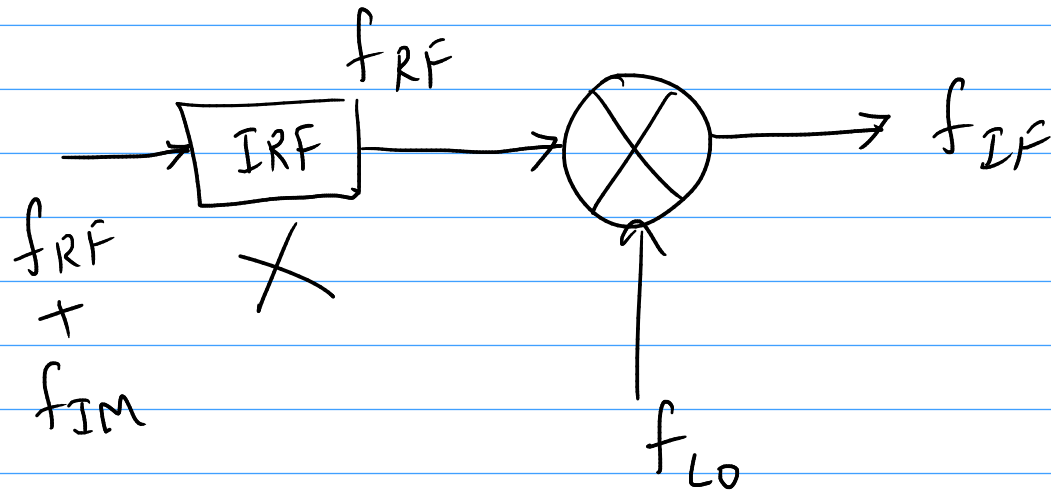


\* No IRF

\* Processes RF & IM differently

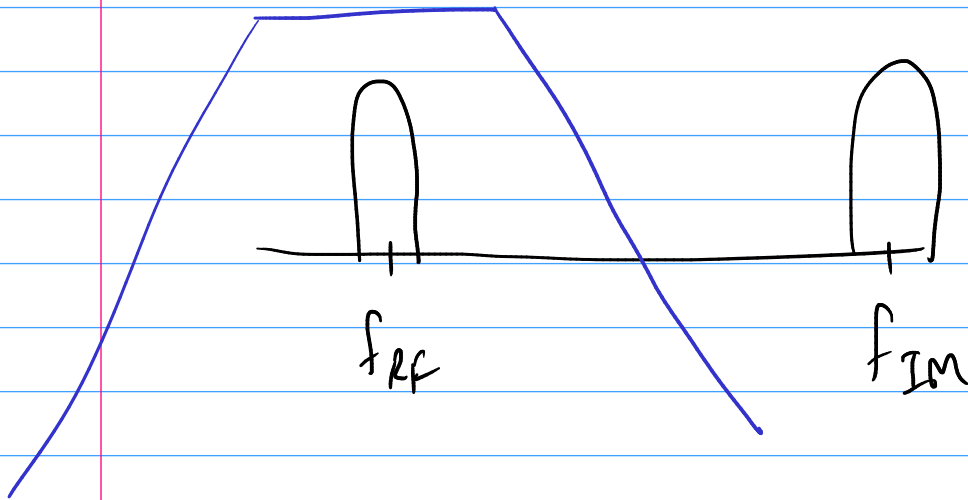\*  $f_{RF}$  &  $f_{IM}$  are on opposite sides of  $f_{LO}$



# Hartley Image Reject architecture

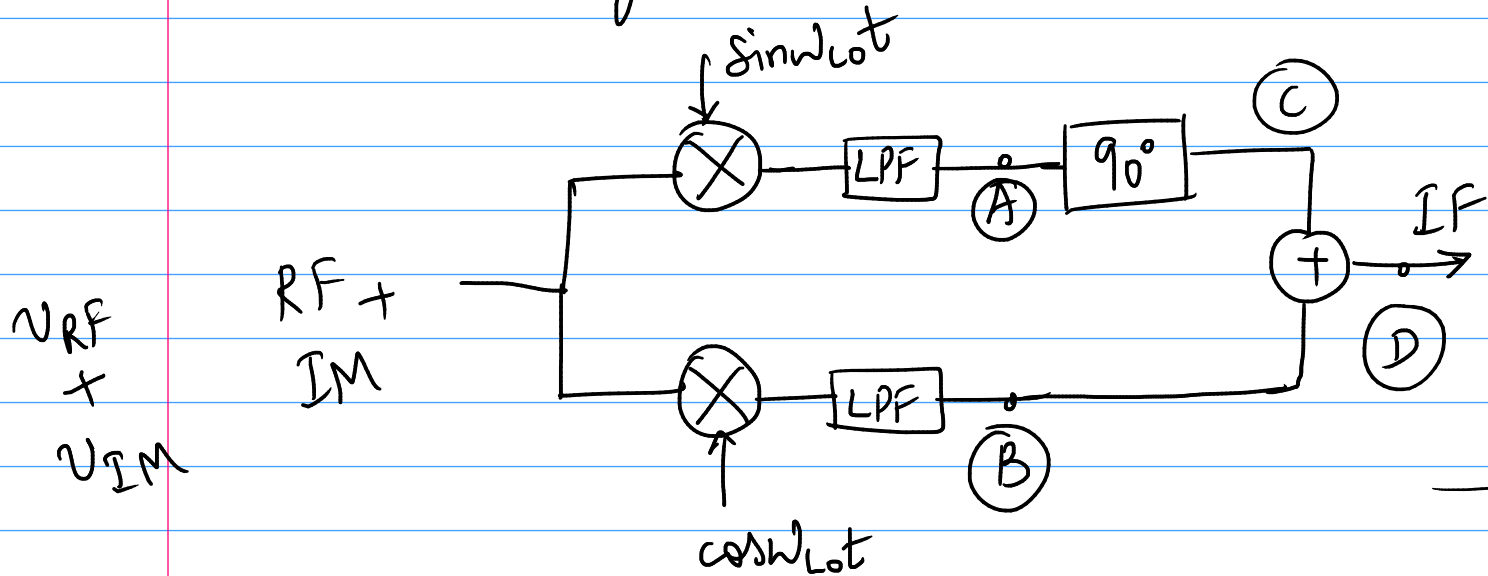

$$V_{RF} = A_{RF} \cos \omega_{RF} t$$

$$V_{IM} = A_{IM} \cos \omega_{IM} t$$

$$\omega_{IF} = \omega_{RF} - \omega_{Lo} = \omega_{Lo} - \omega_{IM}$$


$$x_A(t) = \frac{A_{RF}}{2} \cdot \sin(\omega_{Lo} - \omega_{RF})t + \frac{A_{IM}}{2} \sin(\omega_{Lo} - \omega_{IM})t$$



$$x_B(t) = \frac{A_{RF}}{2} \cdot \cos(\omega_{Lo} - \omega_{RF})t + \frac{A_{IM}}{2} \cos(\omega_{Lo} - \omega_{IM})t$$

$$x_A(t) = -\frac{A_{RF}}{2} \sin(\underbrace{\omega_{RF} - \omega_c}_{\omega_{IF}})t + \frac{A_{IM}}{2} \sin(\underbrace{\omega_c - \omega_{IM}})t$$

$$x_C(t) = +\frac{A_{RF}}{2} \cos(\omega_{RF} - \omega_c)t - \frac{A_{IM}}{2} \cos(\omega_c - \omega_{IM})t$$

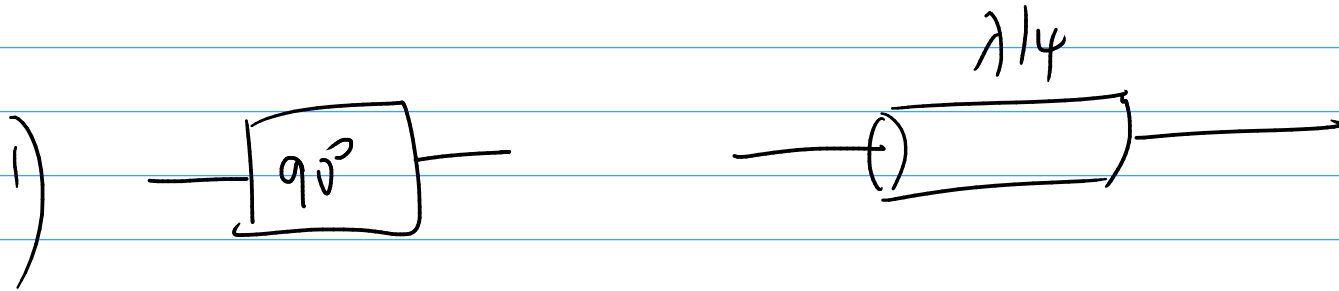
$$x_D = A_{RF} \cos(\omega_{RF} - \omega_c)t$$



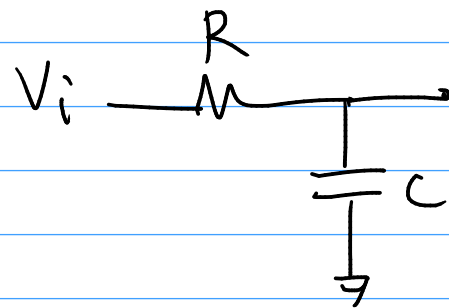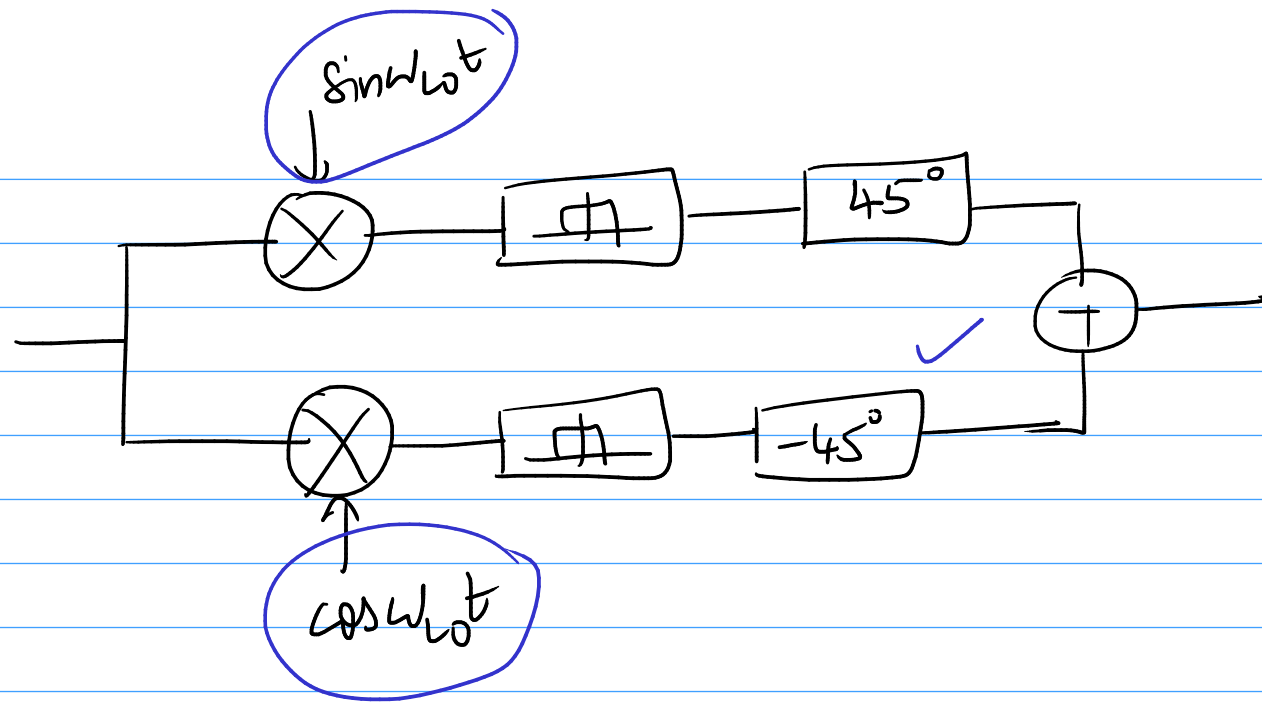

$$\frac{V_o}{V_i}(s) = \frac{1}{1 + sRC}$$

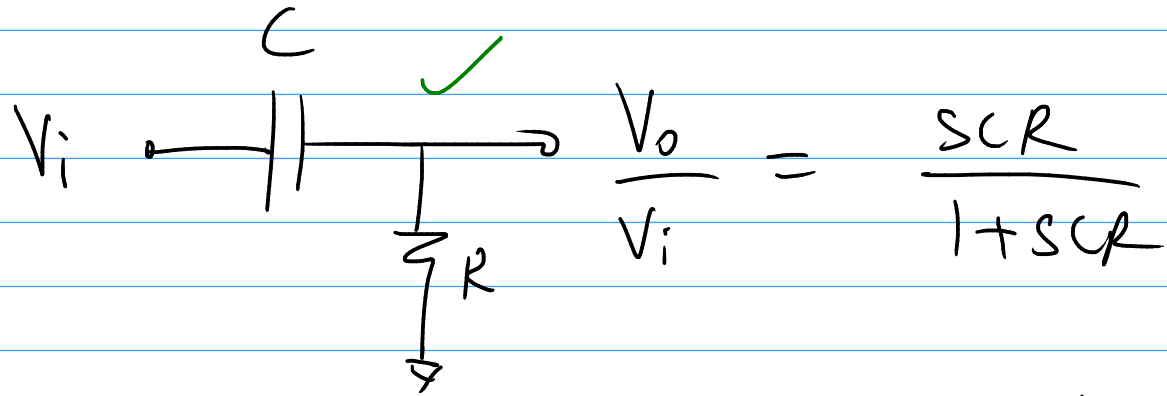(a)  $\omega = \frac{1}{RC} \rightarrow -45^\circ$  ✓




@  $\omega = \frac{1}{RC} \Rightarrow +45^\circ$  ✓

\* Amplitude mismatch


\*  $\phi$  mismatch

# Weaver IR architecture

$$W_{RF} \gg W_1 \gg W_{IM}$$

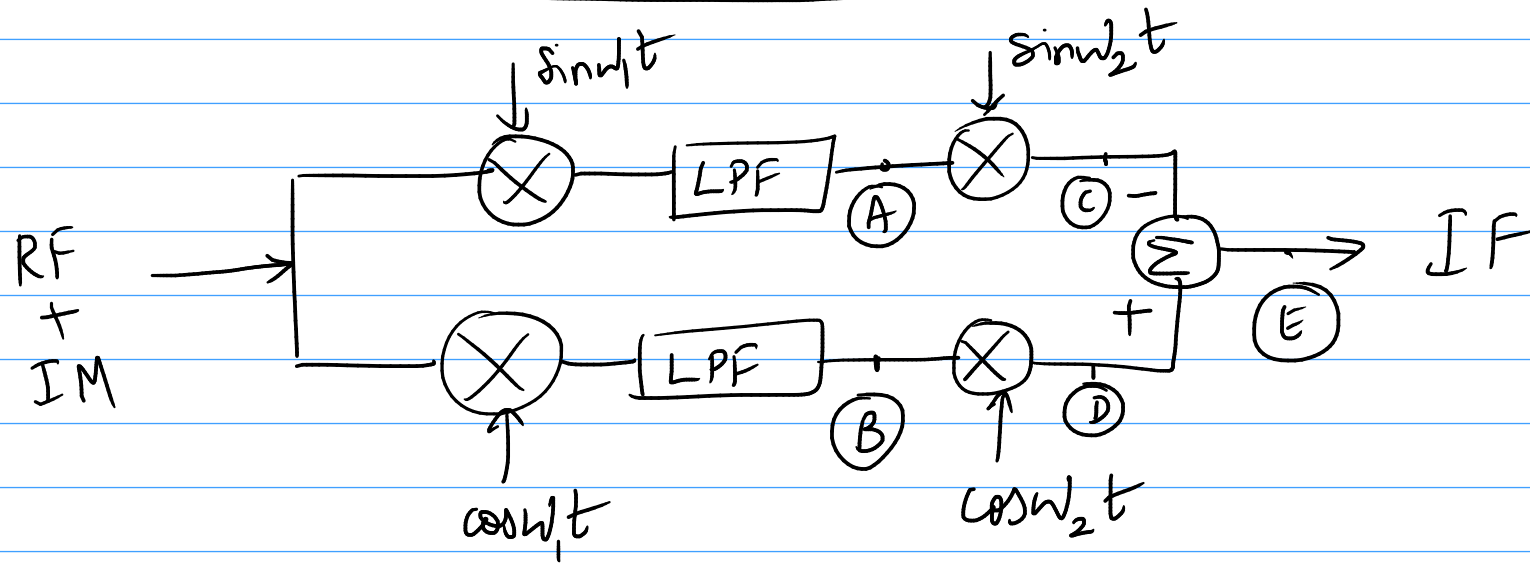


$x_A(t)$	}	same as before	$x_C(t) =$	}	HW
$x_B(t)$			$x_D(t) =$		
	$x_E(t) =$				

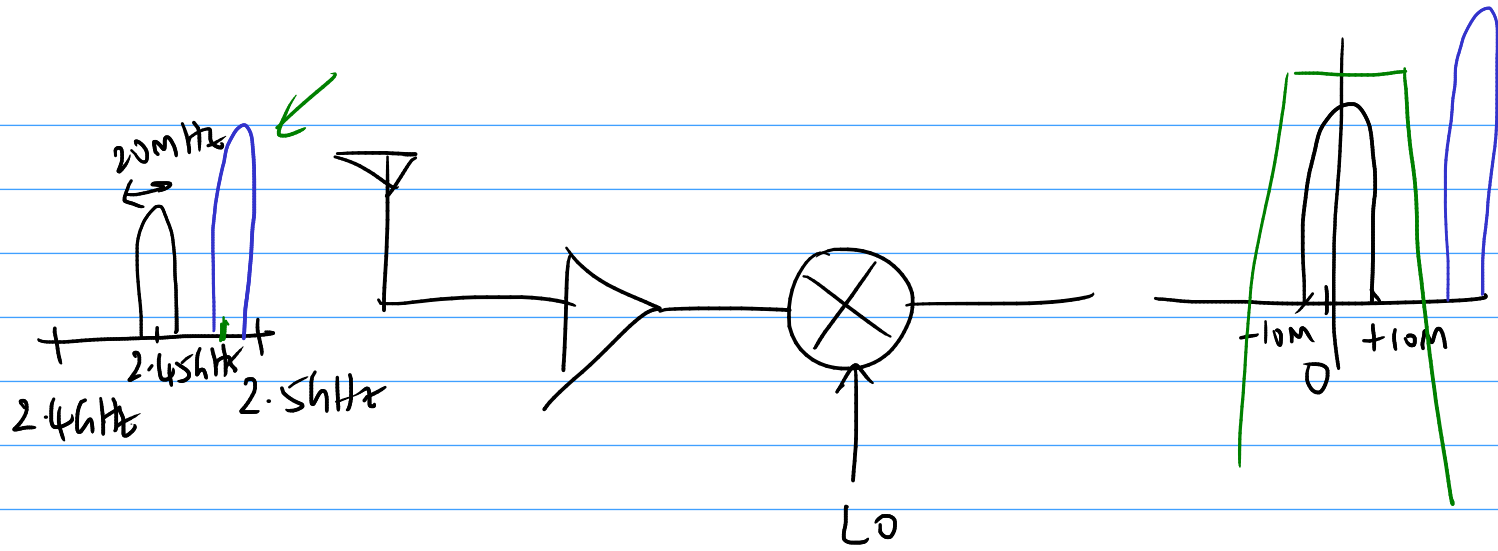


$2.45\text{ GHz}$   
X

Image Reject Ratio
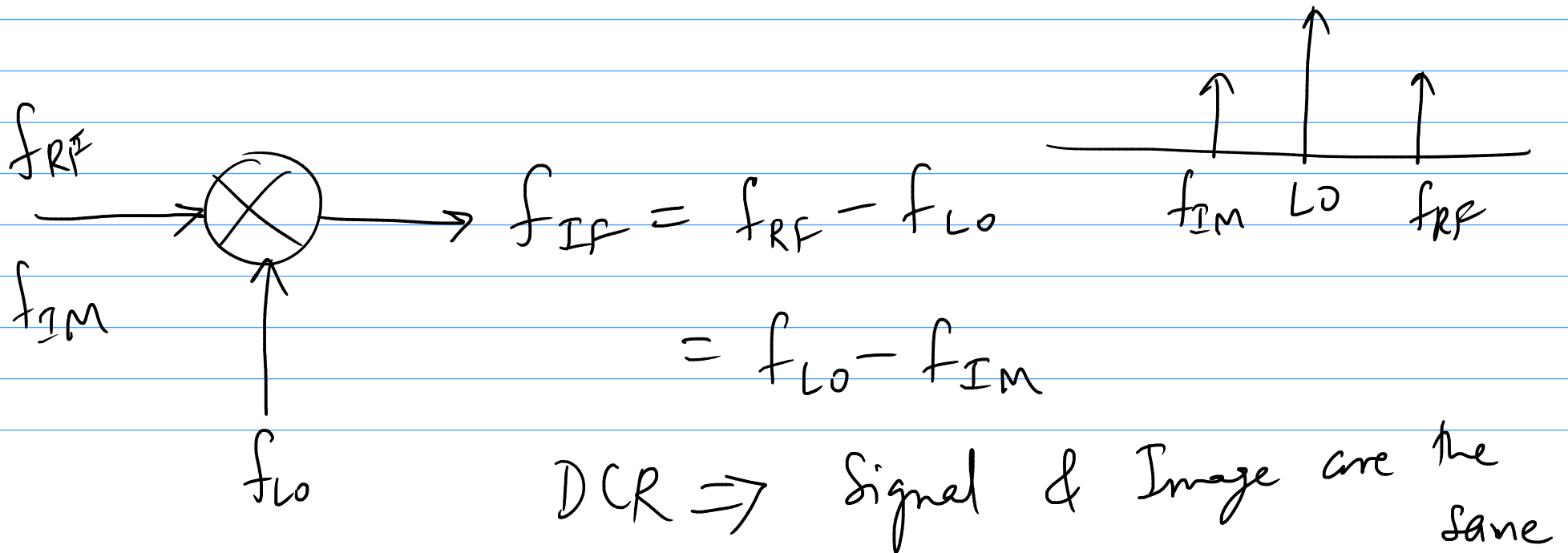
$$IRR = \frac{\text{Image to signal ratio @ output}}{\text{Image to signal ratio @ input}}$$



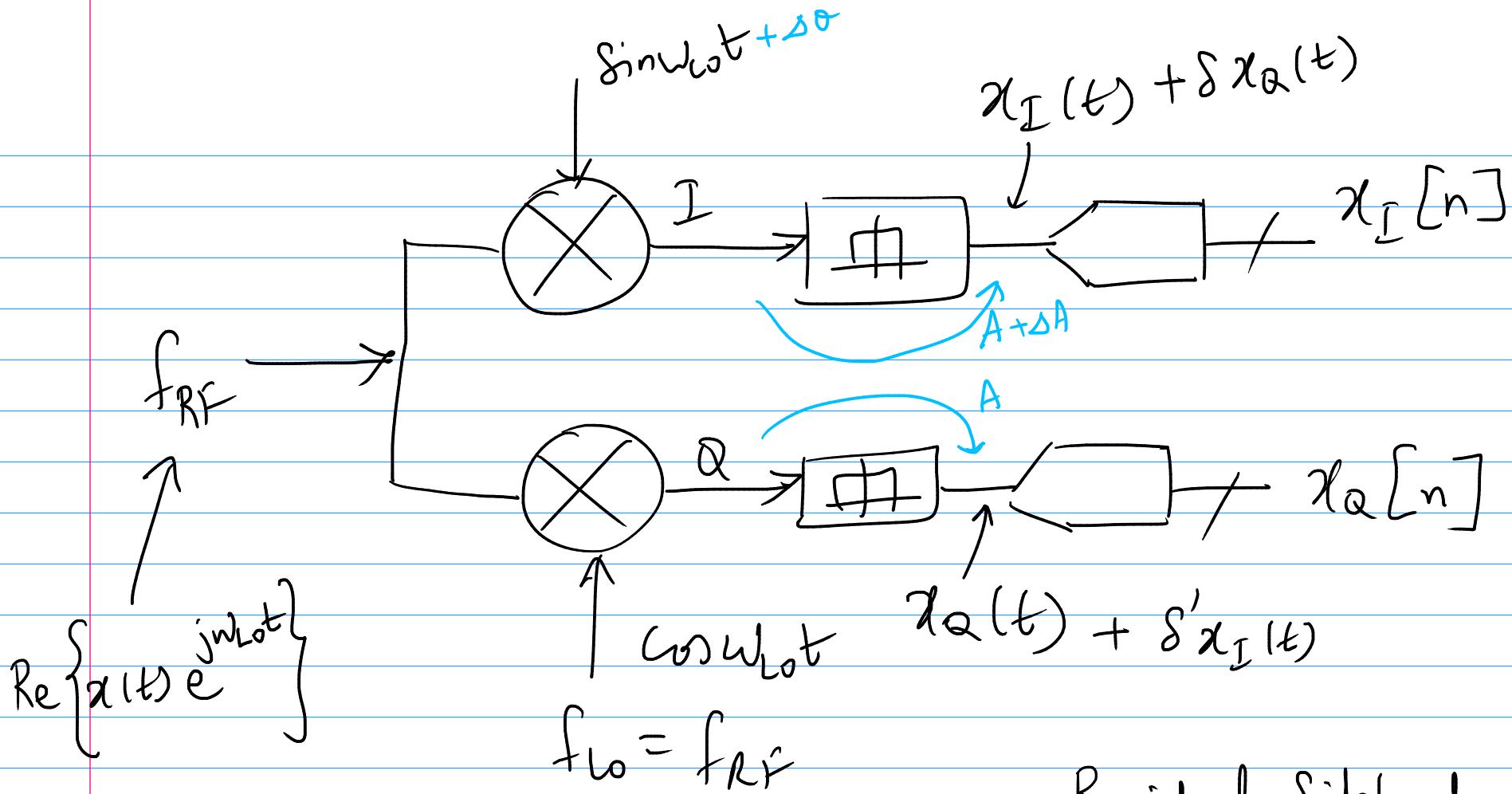
DCR  $\Rightarrow$  Signal & Image are the same



Residual Sideband (RSB)
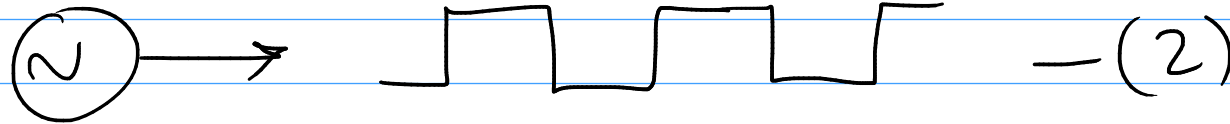
# Oscillators

② →  $V_o \cos(\omega_o t + \phi)$  — (1)



1) clock for digital

2) LO signal for mixer

3) clock for ADC, DAC

\* Hartley Osc.

\* Wien Bridge

\* Ring Osc.

\* Relaxation Osc.


\* Colpitts Osc.

\* RC phase shift Osc.

\* LC osc.

\* Schmitt Trigger Osc.

← Most common in RF Systems

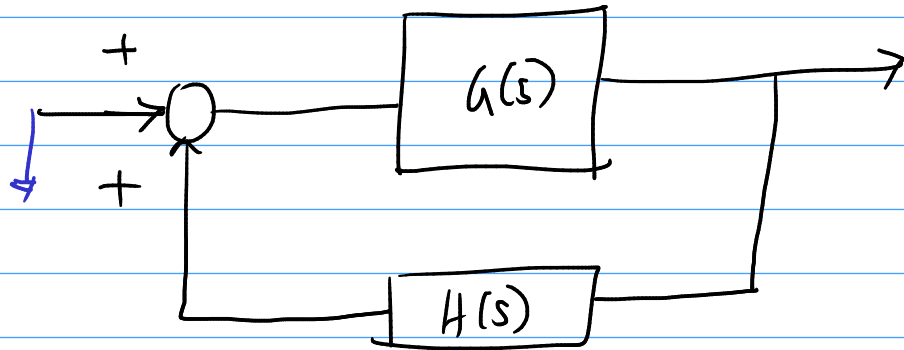

## Barkhausen Criteria

$$|G(j\omega) \cdot H(j\omega)| = 1$$

and



$$\angle G(j\omega) \cdot H(j\omega) = 360^\circ$$

Necessary but not sufficient  
conditions


$$A_0 = g_m R$$

$$\omega_p = \frac{1}{RC}$$

$$\frac{-A_0}{1 + s/\omega_p}$$


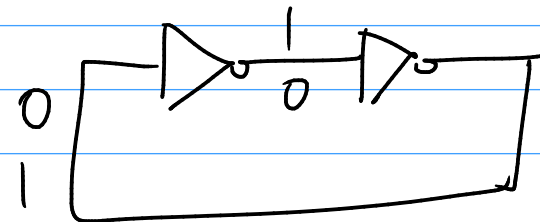
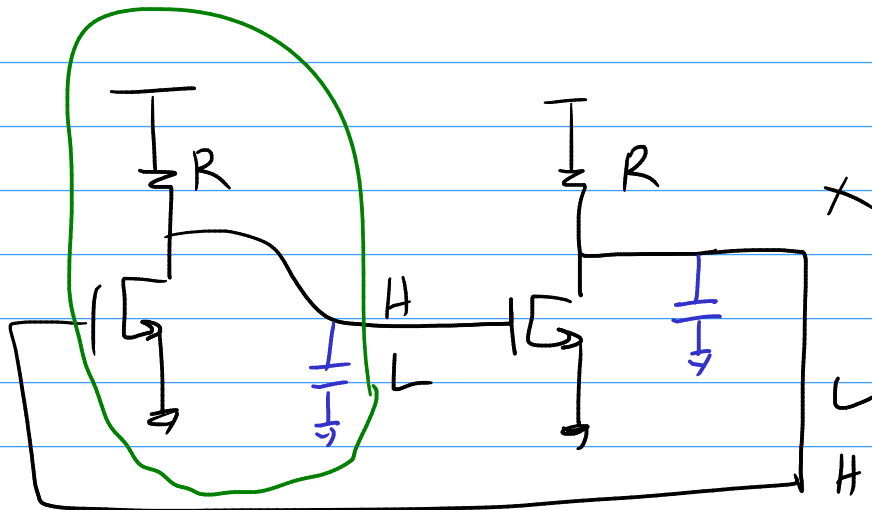


Latch

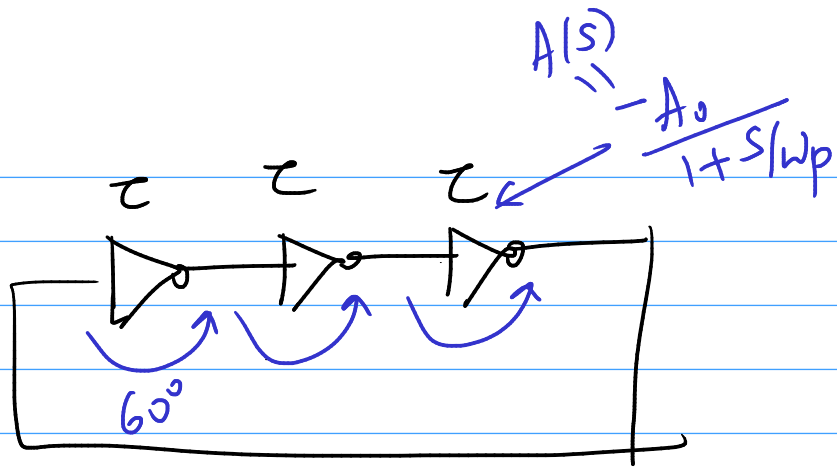




each inv gives  $60^\circ$  phase shift

@  $\omega_0$

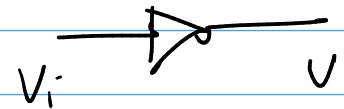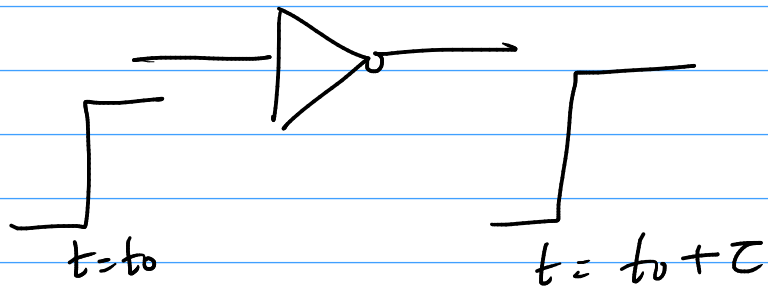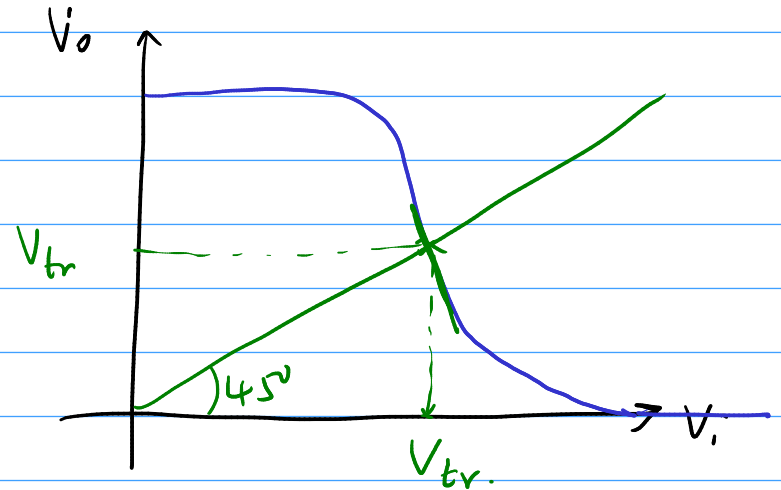
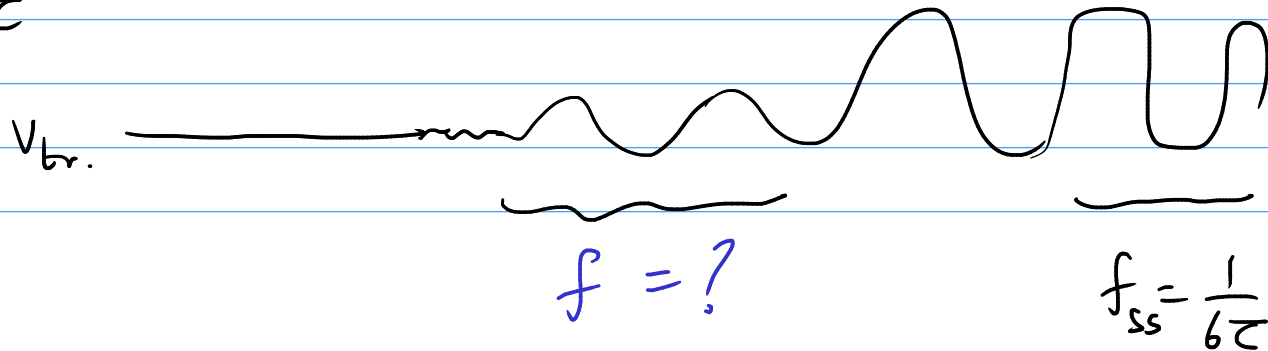
$$L_h(s) = \frac{-A_0^3}{(1 + s/w_p)^3}$$




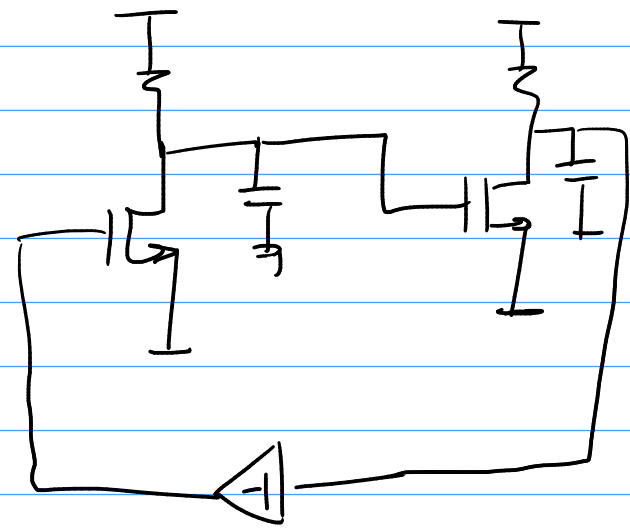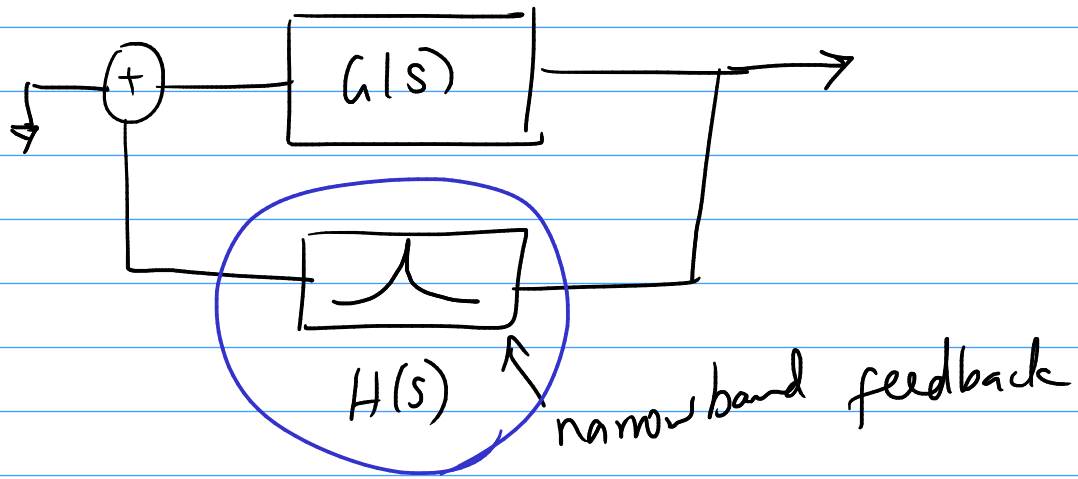


Ideal  
inv.

$$L_G = \frac{-A_0^2}{(1 + s/\omega_p)^2}$$
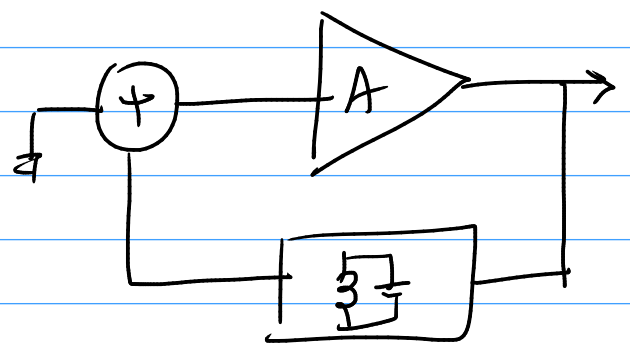
$$\phi = 360^\circ \text{ only @ } \omega = \infty$$




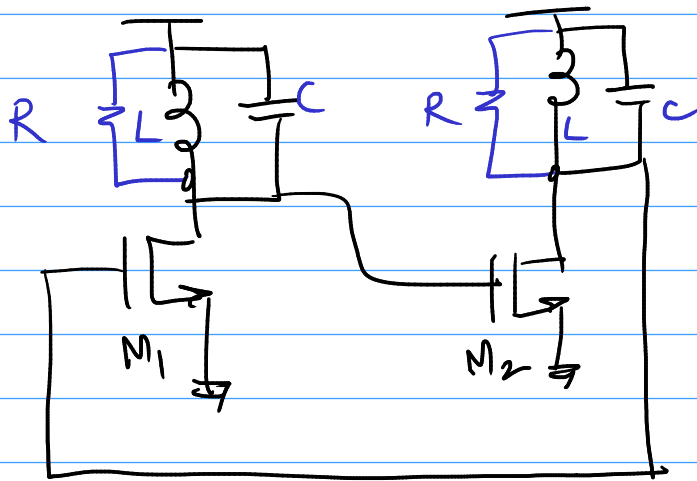


$$LG(s) = \frac{(g_m sL)^2}{\left[1 + \frac{sL}{R} + s^2LC\right]^2}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \leftarrow \text{phase} = -180^\circ \text{ per block}$$



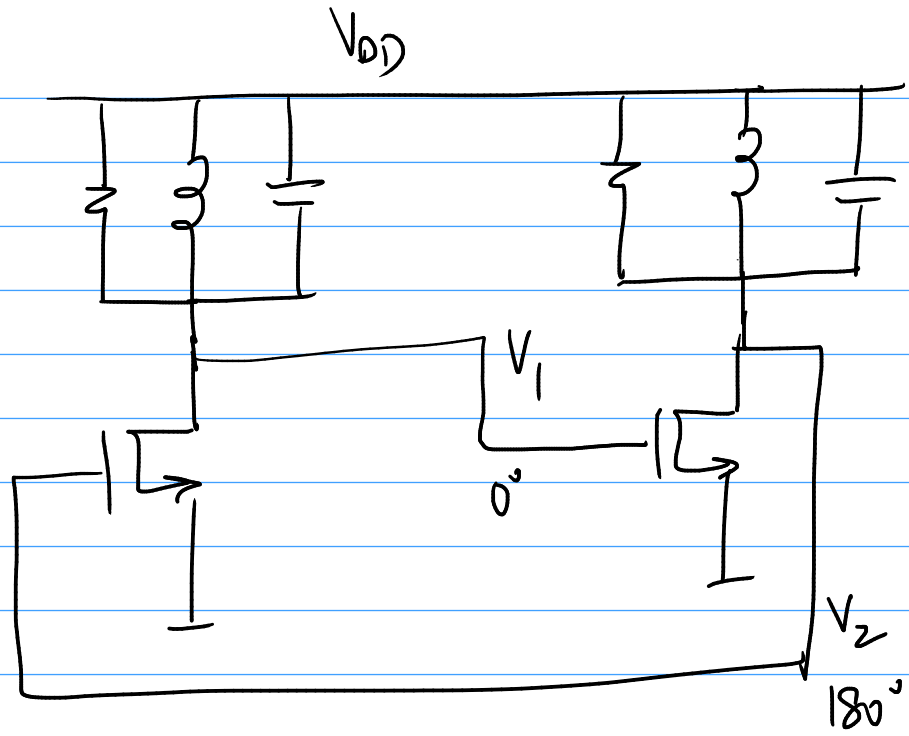
$$g_m R = 1 \Rightarrow \begin{array}{l} \text{Loop} \\ \text{gain} = 1 \\ \text{maj.} \end{array}$$






Cross-coupled  
LC oscillator

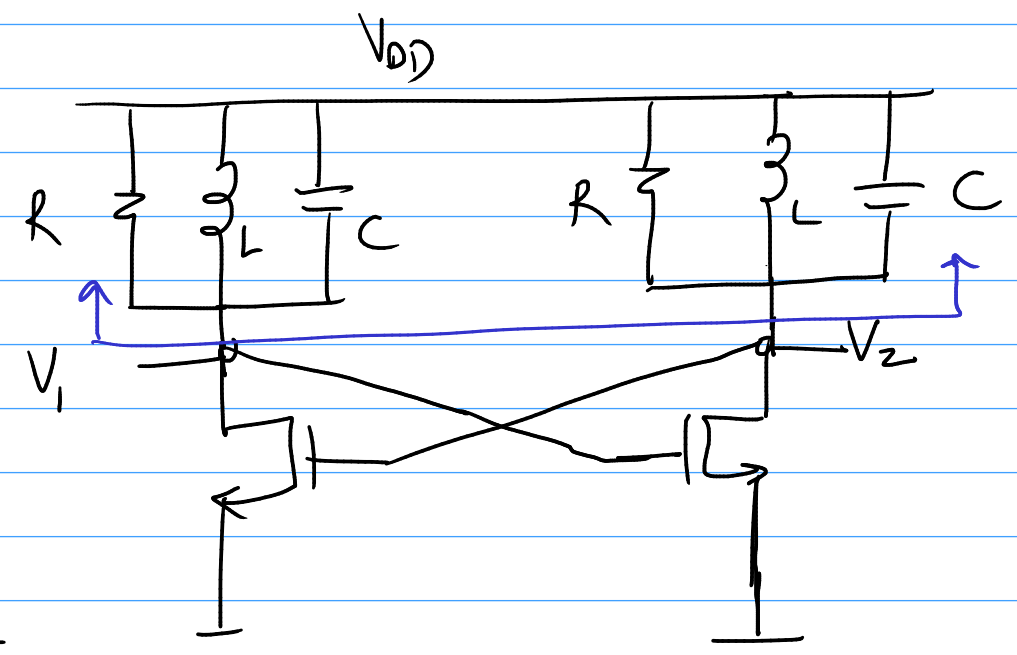



$$g_m = \frac{1}{R}$$

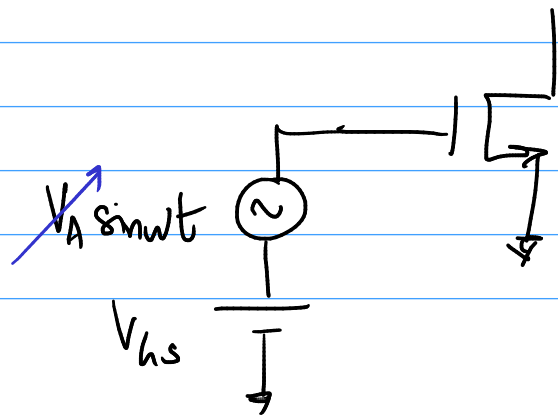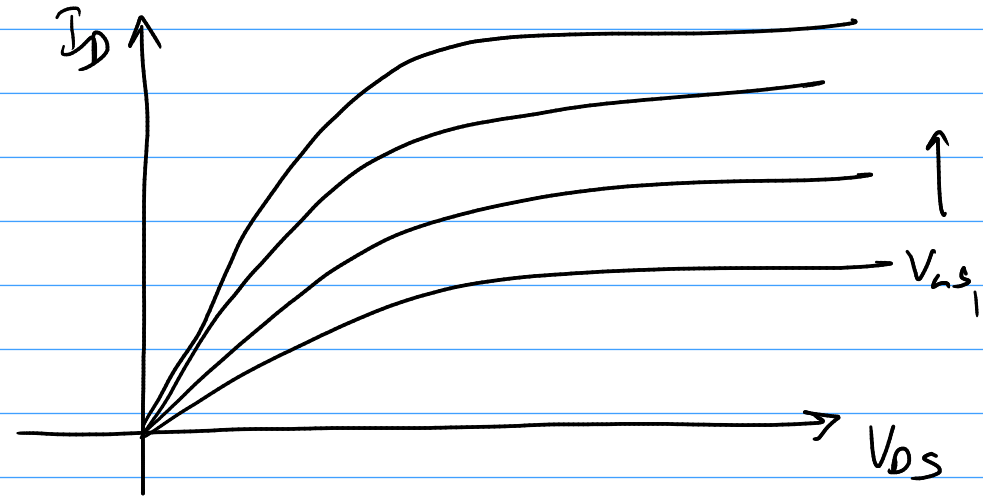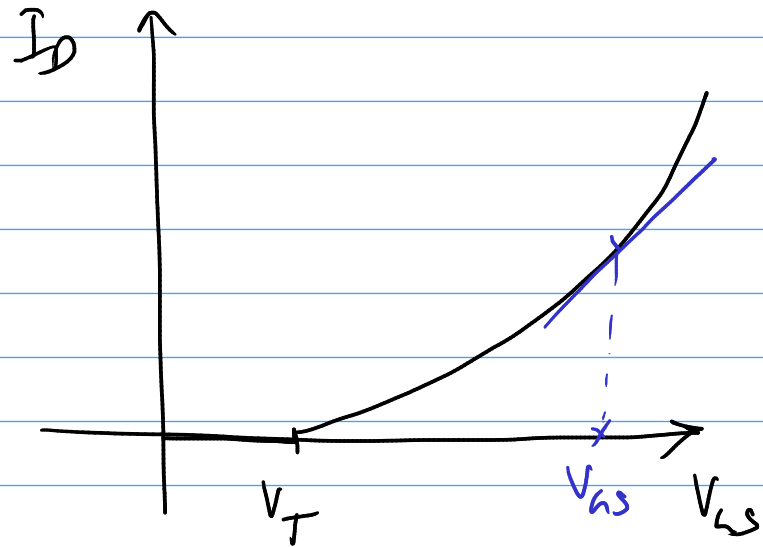

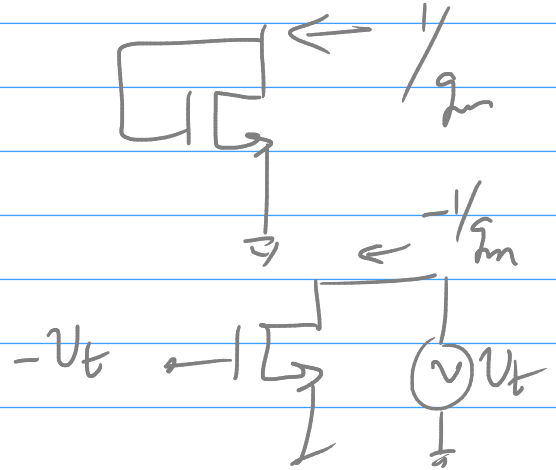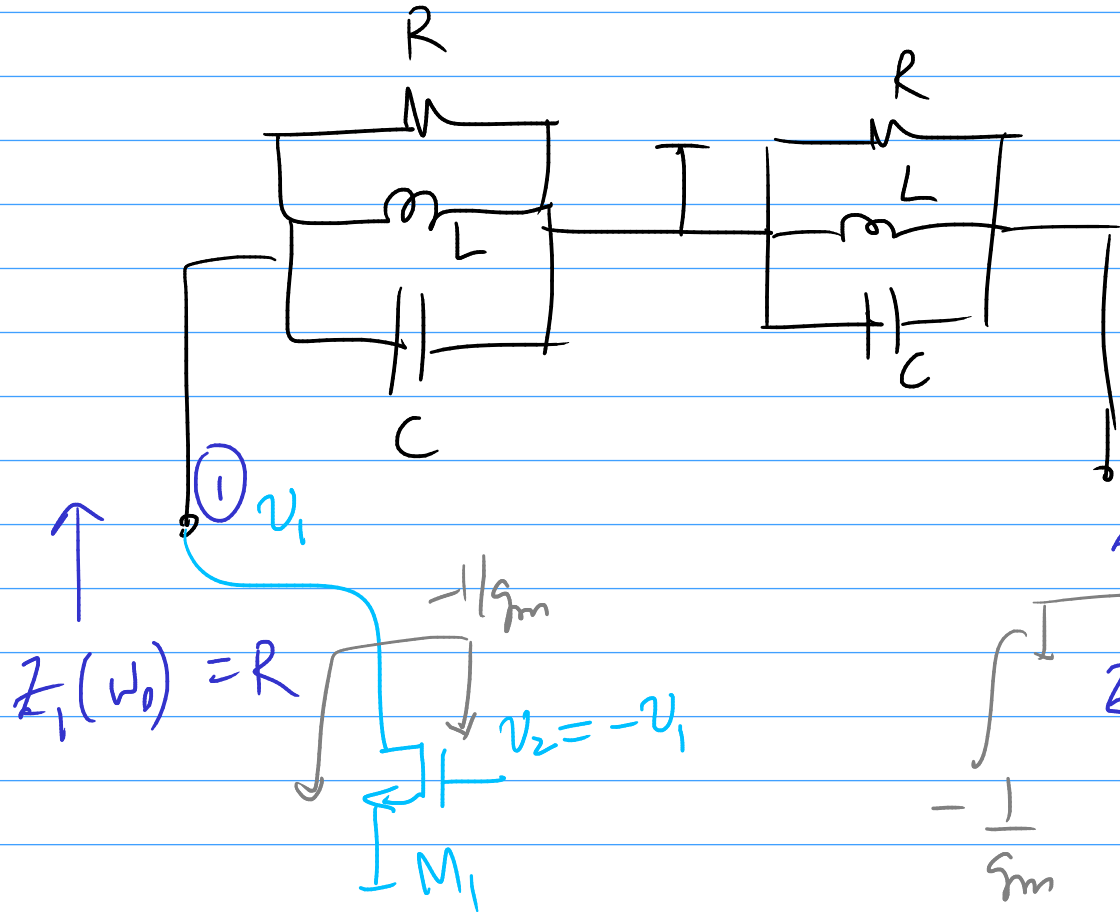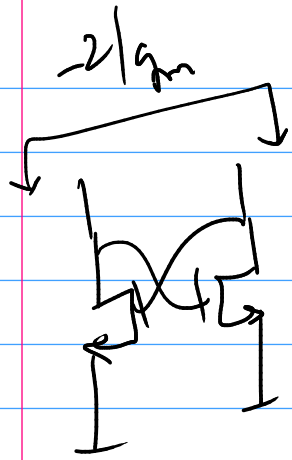- 1) In sat.  $\rightarrow$  does  $G_m$  stay constant?
- 2) If device goes to triode/cutoff  $\rightarrow G_m \rightarrow ?$




②  $v_2 = -v_1$

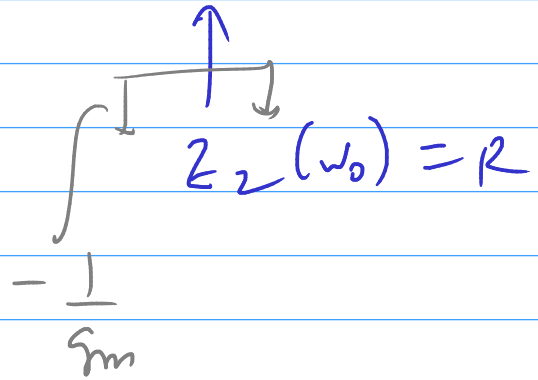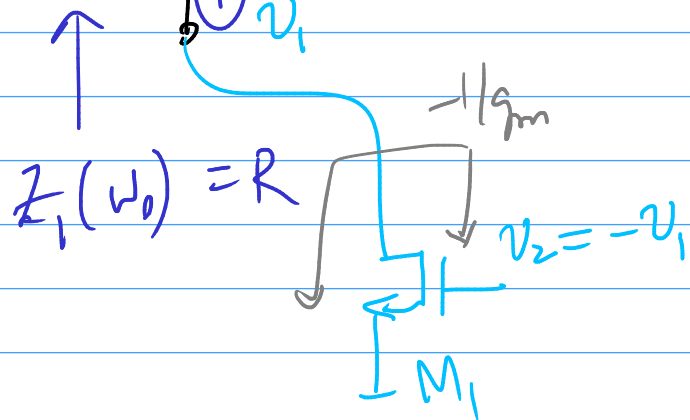

$Z_1(\omega_0) = R$

$Z_2(\omega_0) = R$

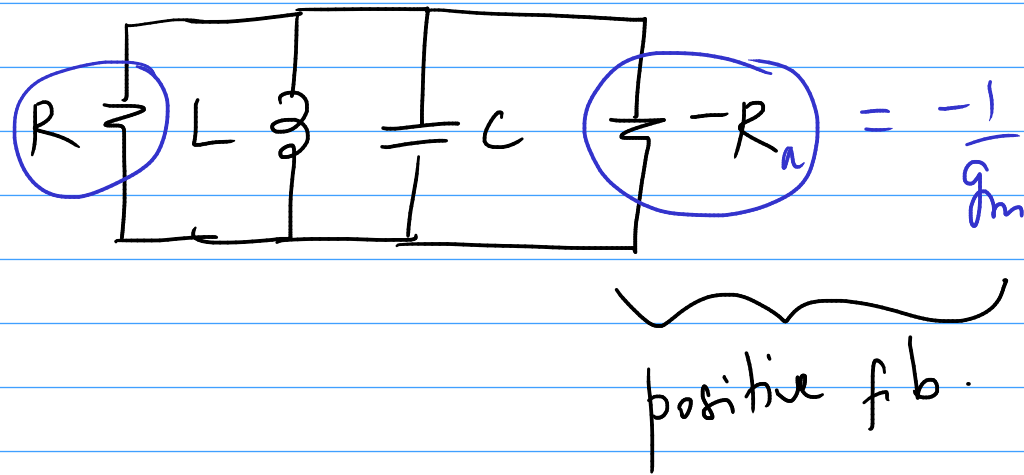

$$|R_a| < |R|$$

$\underbrace{\hspace{10em}}$   
 RHP poles


$$|R_a| = |R|$$

$\hookrightarrow$  poles on  
 $j\omega$  axis

$$|R_a| > |R|$$

$\hookrightarrow$  decaying osc.

# MOSFET $g_m$ and $g_m(t)$

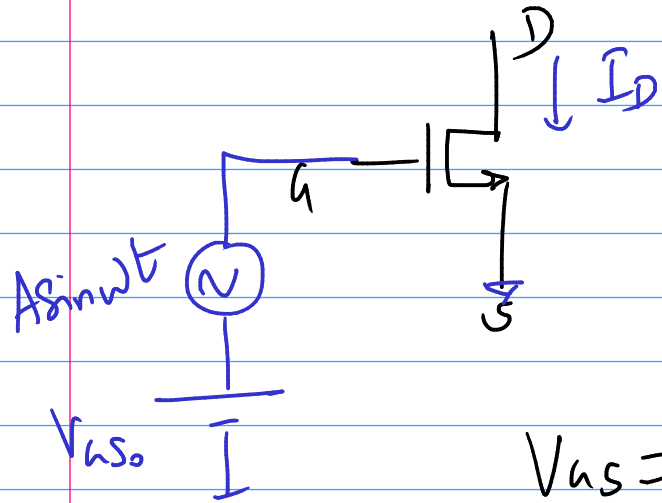

$$I_D = \frac{1}{2} \beta (V_{GS} - V_T)^2$$

$$\beta = \mu C_{ox} \left( \frac{W}{L} \right)$$


$$g_m = \beta (V_{GS0} - V_T)$$

$= g_m$   
only for  $\sim$   
square  
law  
device

$$V_{GS} = V_{GS0} + A \sin \omega t$$

$$I_D = \frac{1}{2} \beta (V_{GS0} + A \sin \omega t - V_T)^2$$
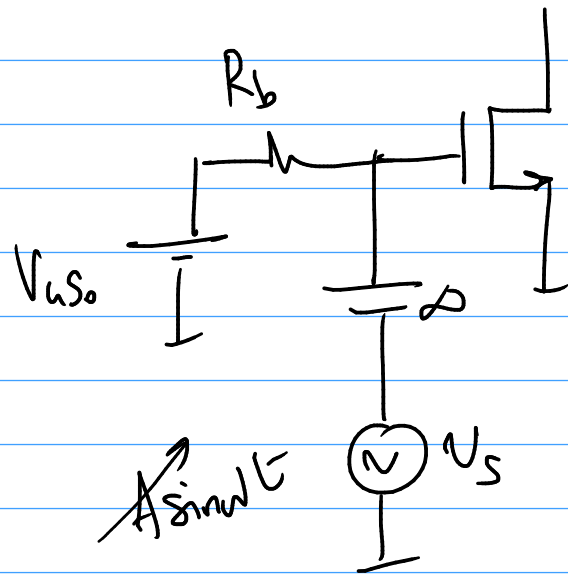
$$= \underbrace{\frac{1}{2} \beta (V_{GS0} - V_T)^2}_{I_{D0}} + \underbrace{\frac{1}{2} \beta A^2 \sin^2 \omega t}_{\text{circled}} + \underbrace{\beta (V_{GS0} - V_T) A \sin \omega t}_{g_m \cdot V_{GS}(t)}$$




$$\downarrow I_{DC} = \frac{1}{2} \beta (V_{as_0} - V_T)^2 \times$$

$$I_{DC} = I_{\text{average over 1 period}}$$

$$g_m(t) = \frac{\partial I_D(t)}{\partial V_{as}(t)} = \beta (V_{as_0} - V_T) + \beta A \sin \omega t$$




$$(g_m R) = 1$$


$R \ll \infty$   
 $|R_a| \ll |R|$

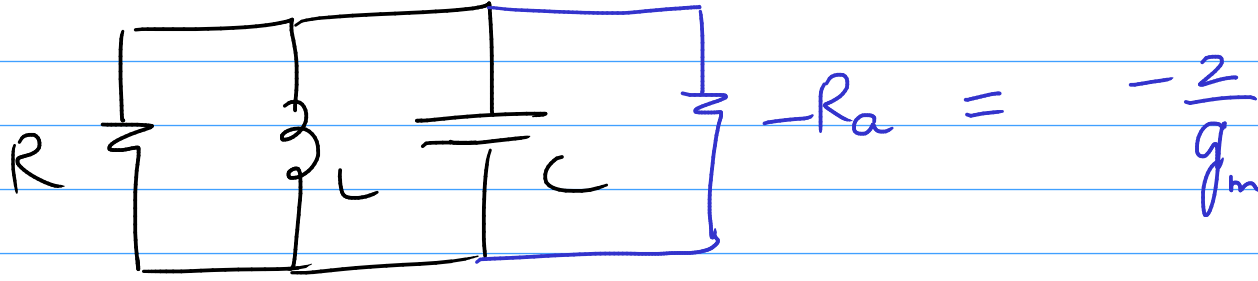

$$R_x = \frac{R_x - R_a}{R - R_a}$$

$$= \frac{R \cdot R_a}{R_a - R}$$

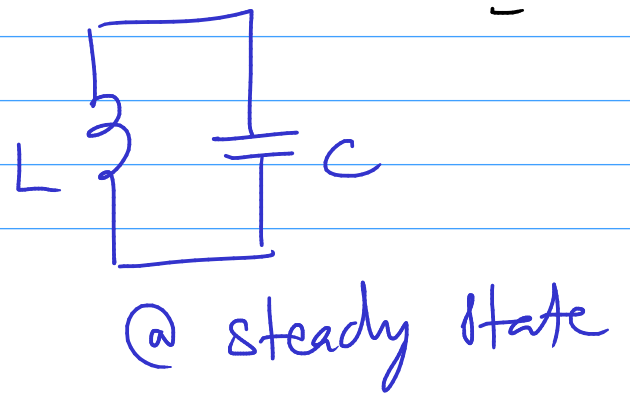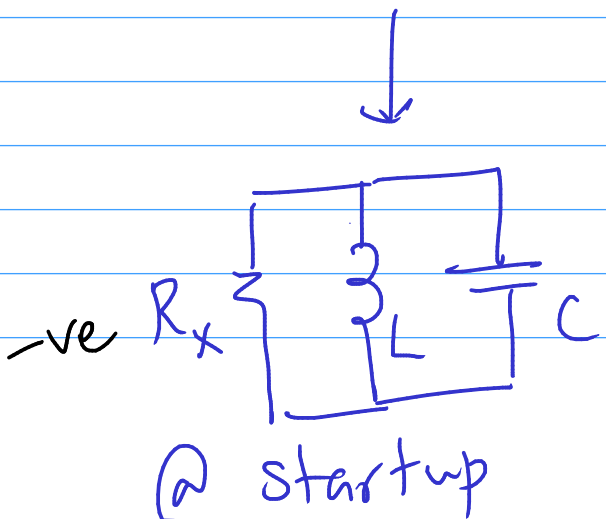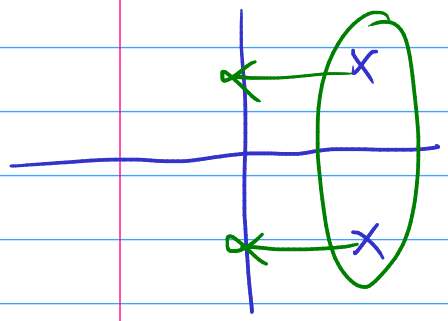

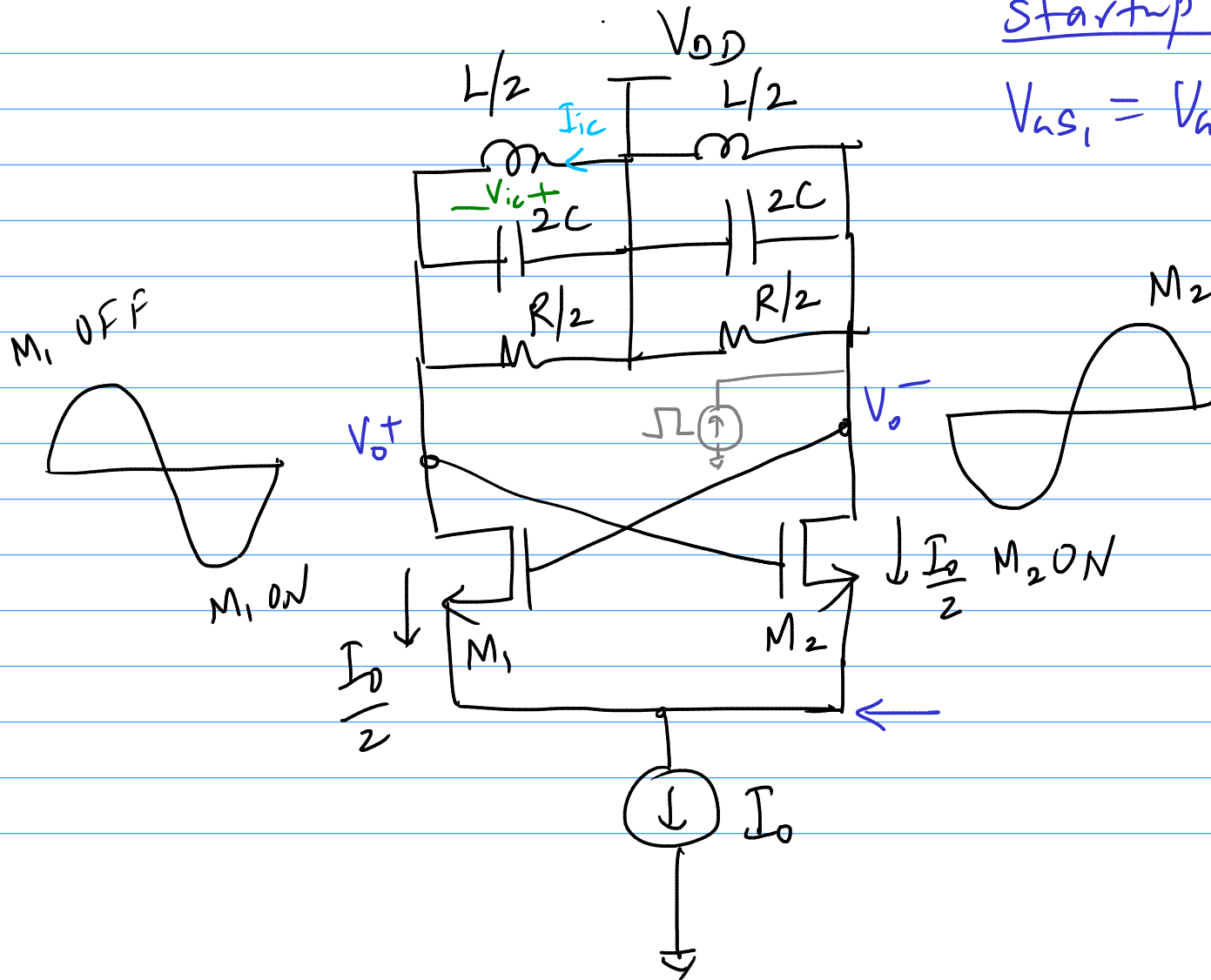

Startup:

$$V_{GS1} = V_{GS2} = V_T + \sqrt{\frac{I_0}{\beta}}$$

$$g_m = \sqrt{\beta I_0}$$

We want

$$g_m \gg \frac{2}{R}$$



$$g_{min} = \frac{2}{R}$$

$$g_m \gg g_{min}$$

e.g.  $g_m = 3 \times g_{min}$

20  $Q = \frac{R}{\omega_0 L}$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

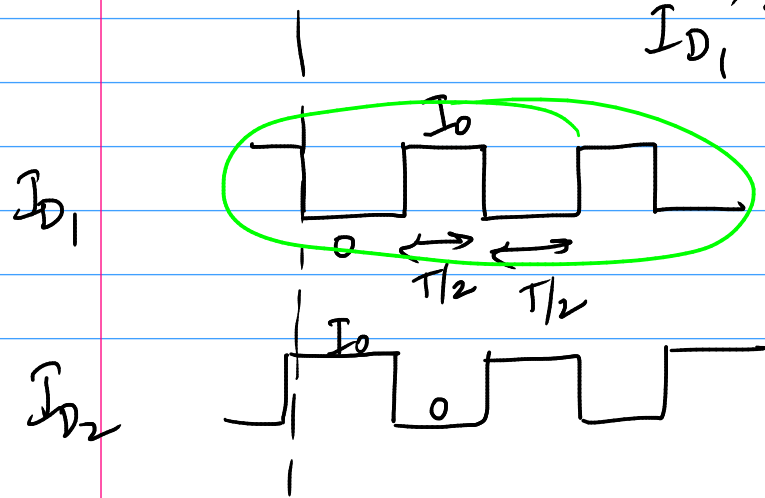
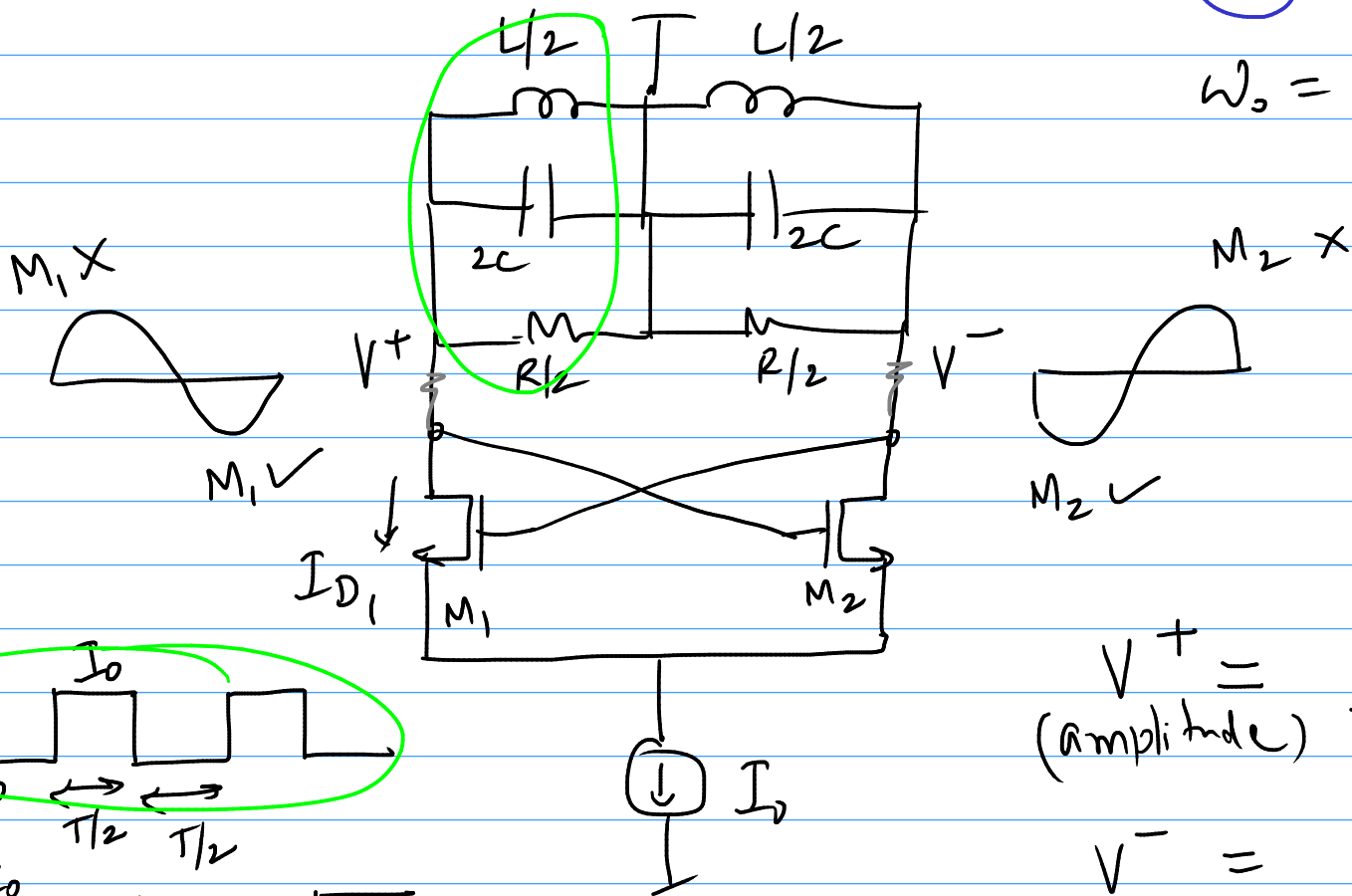




$$V^+ = \frac{R}{2} \times \frac{2}{\pi} \cdot I_0$$


(amplitude)

$$V^- = \frac{R}{2} \times \frac{2}{\pi} I_0$$
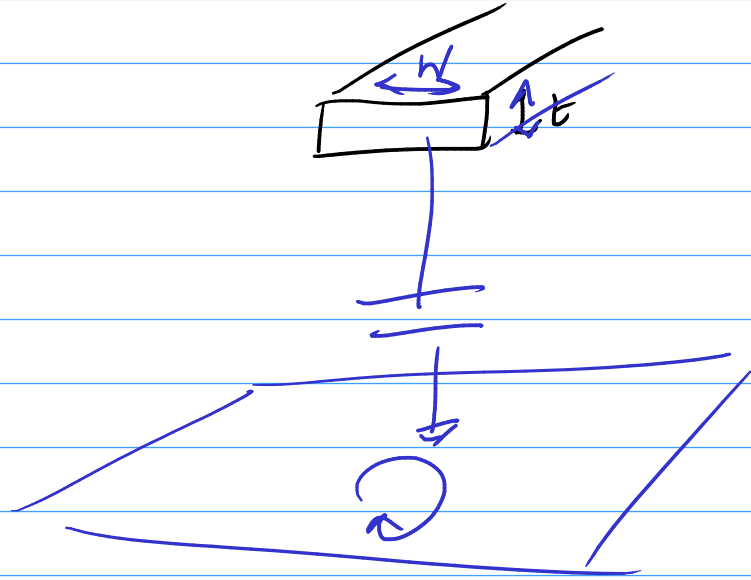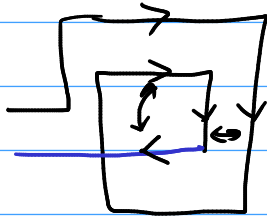
$$V_{od} = V^+ - V^- = \frac{2 I_0 R}{\pi} \checkmark$$



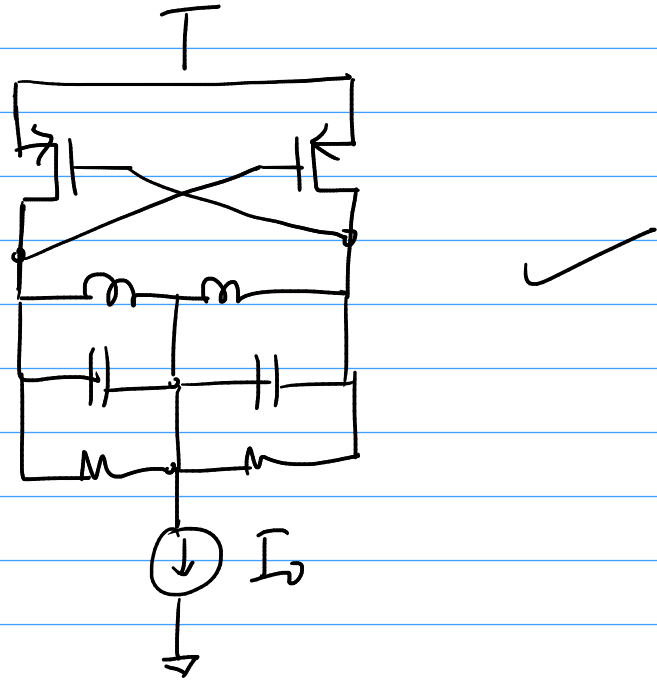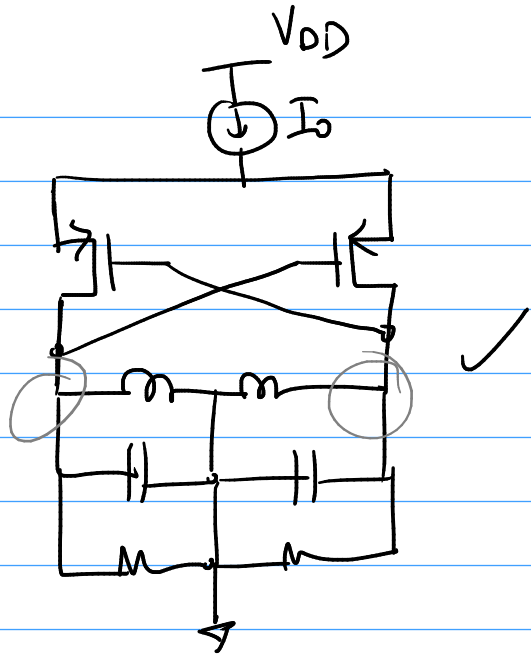


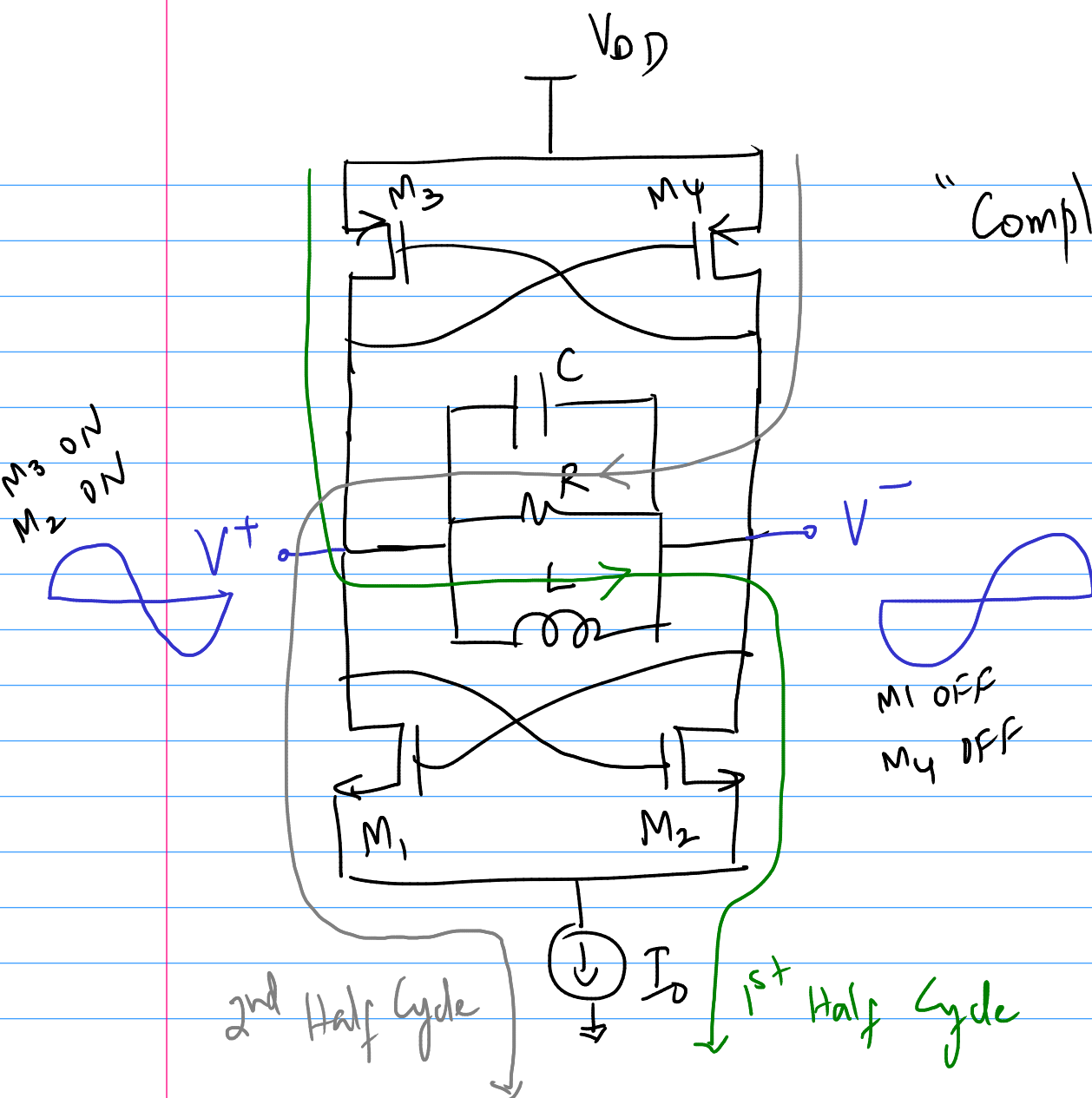

"Complementary" cross-coupled LC Oscillator

$$-R_a = \frac{-2}{g_{m_n} + g_{m_p}}$$

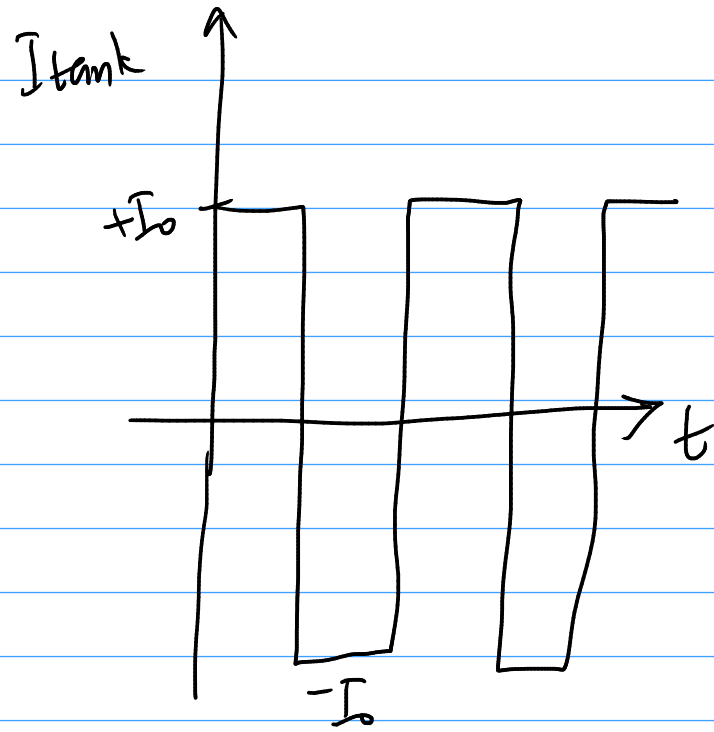
- \* Better startup
- \*  $V^+ / V^-$  "biased" at  $V_{DD} - V_{sat}$
- \* Current flows in LC tank in both half cycles




$$V_{od} = V^+ - V^-$$

$$= \frac{4}{\pi} I_0 \cdot R \cdot \sin \omega_0 t$$


$$\omega_0 = \frac{1}{\sqrt{LC}}$$

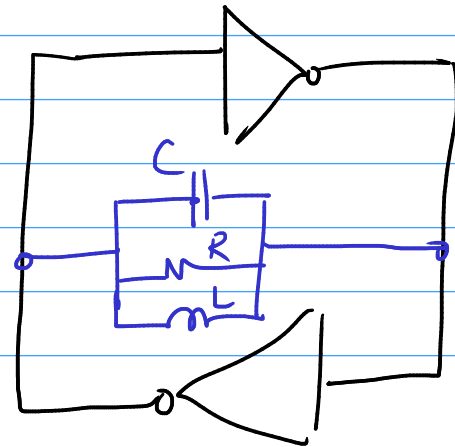

R, L, C,  $\mu$ ,  $t_{ox}$  ...

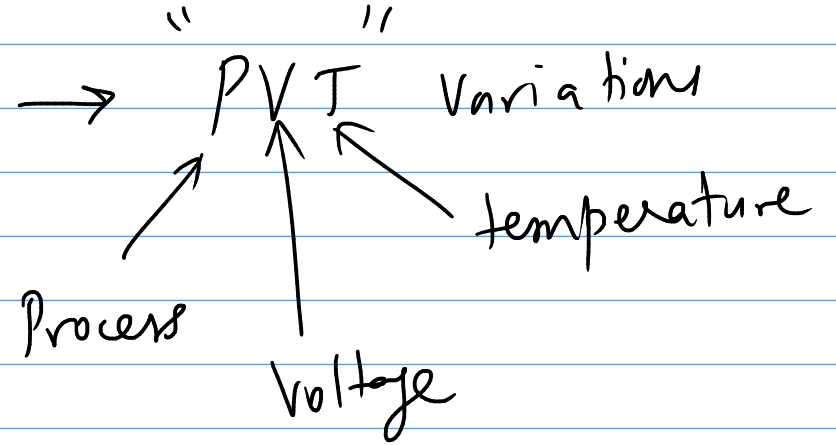

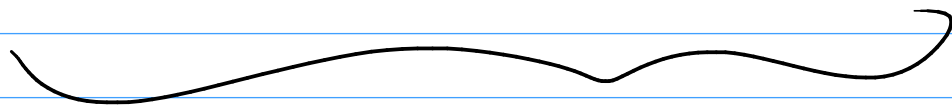$\omega_0 = \frac{1}{\sqrt{LC}}$  is not constant  
for every die  
& over temp.




Fix using Negative feedback

$C = f(V_c)$


↑

"Voltage Controlled Oscillator"  
VCO

# Voltage Amplifier


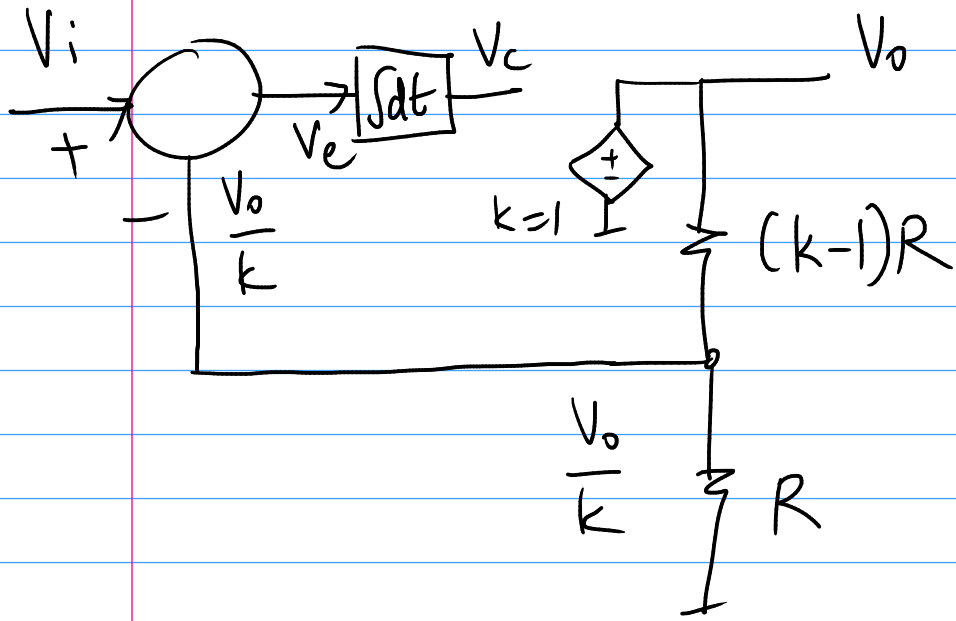


crystal  
osc.

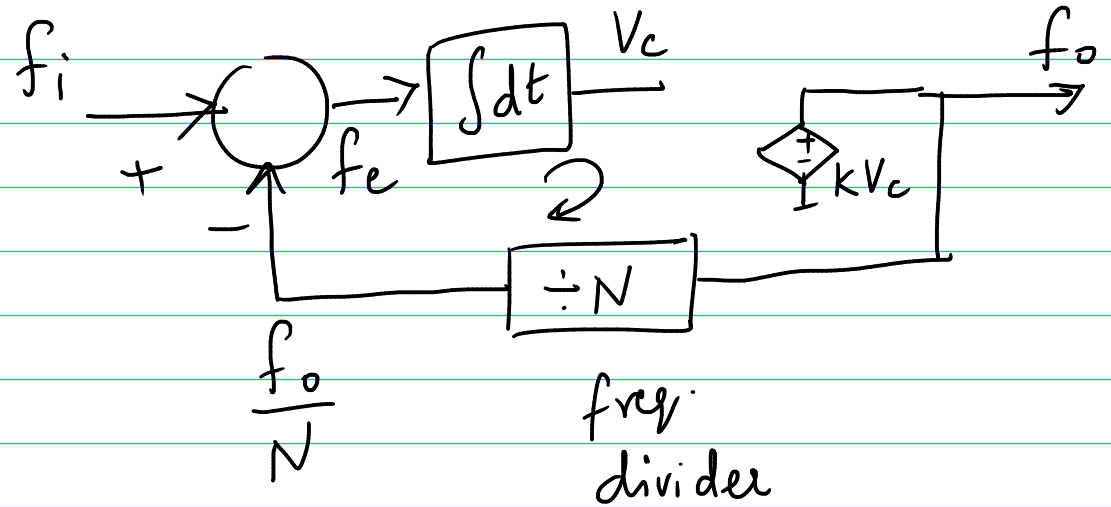


$$f_o = kV_c$$

~~~~~  
"VCO"

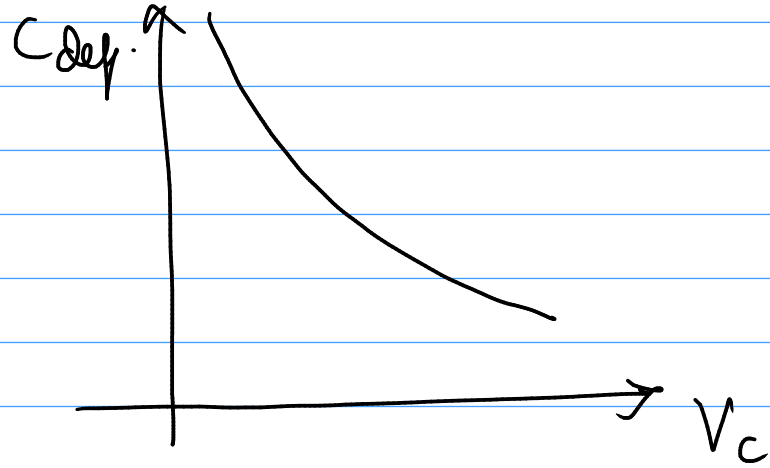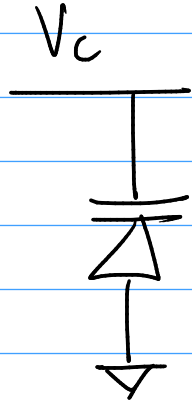




$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

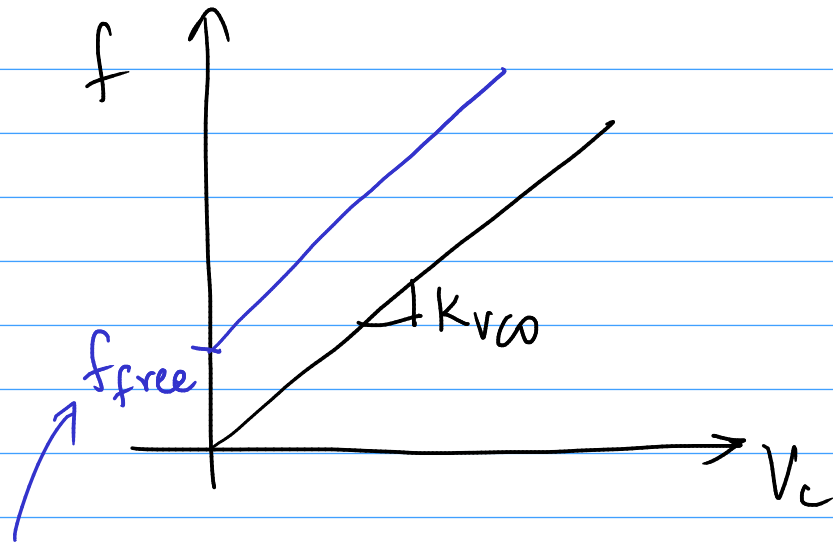




free running  
freq. of VCO



$$f_{VCO} = f_{free} + K_{VCO} \cdot V_c$$

$$K_{VCO} = \text{--- MHz}$$

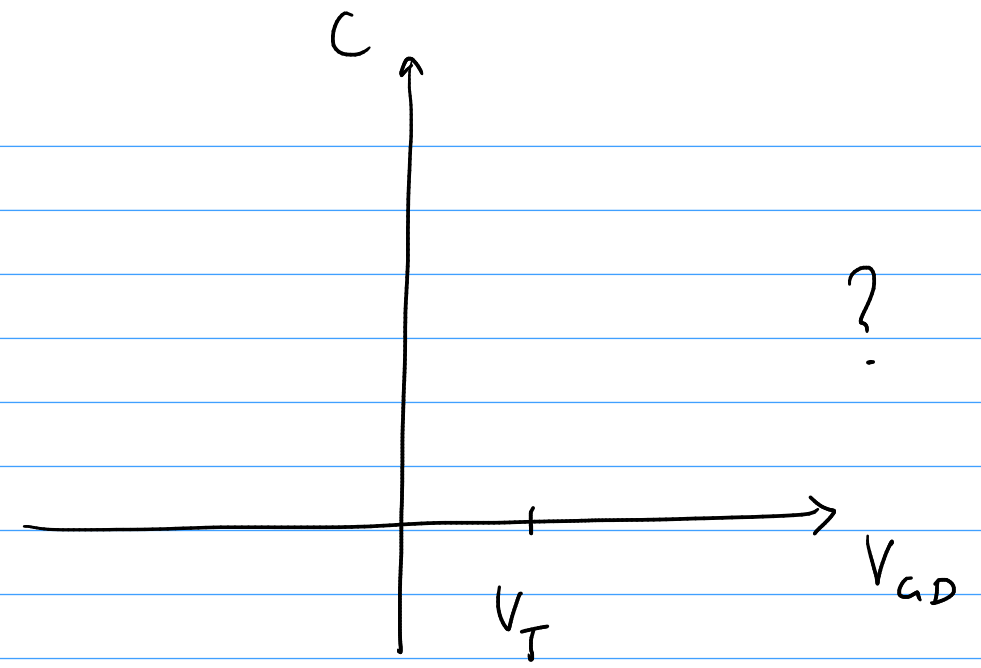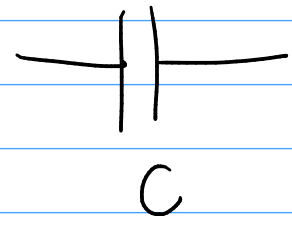
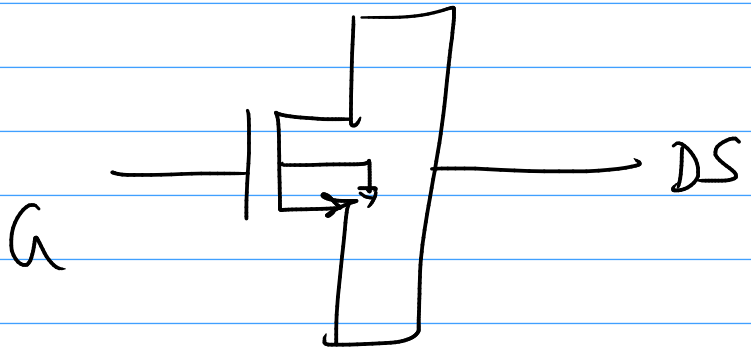


HW

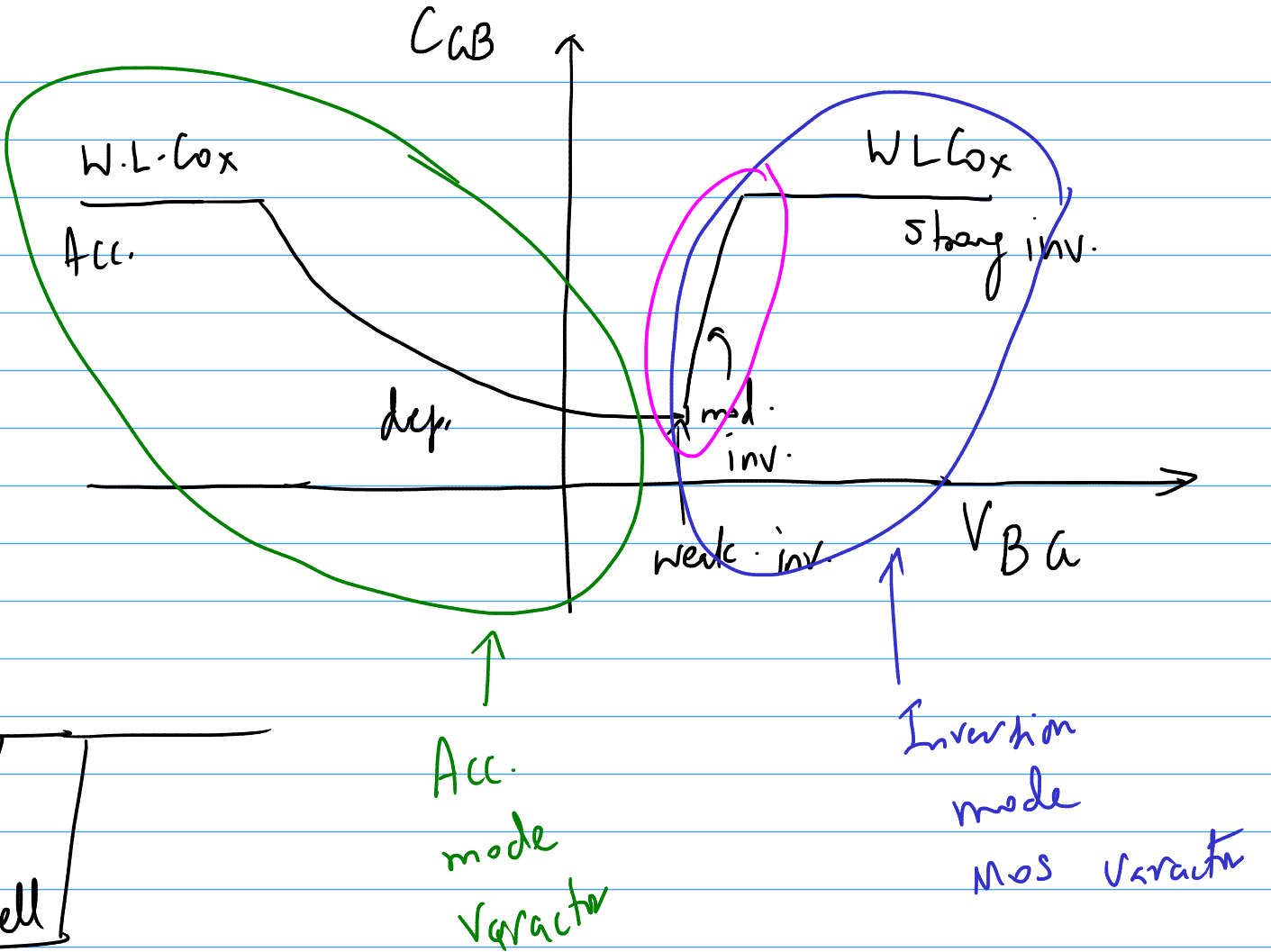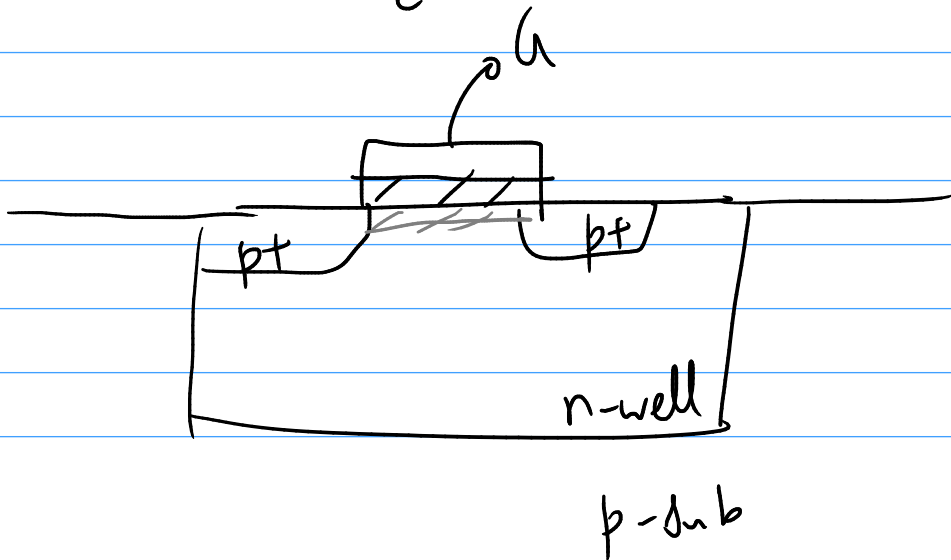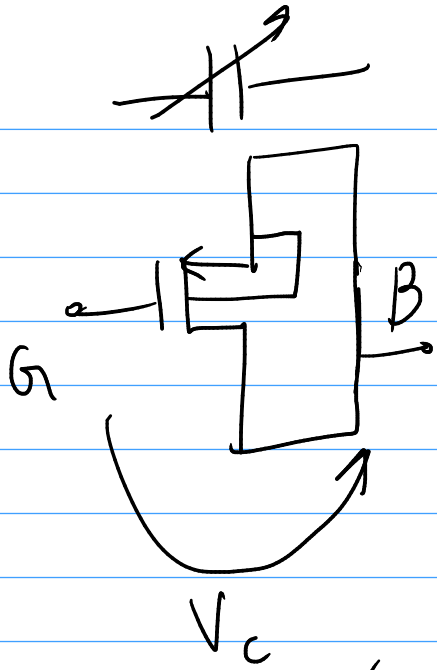


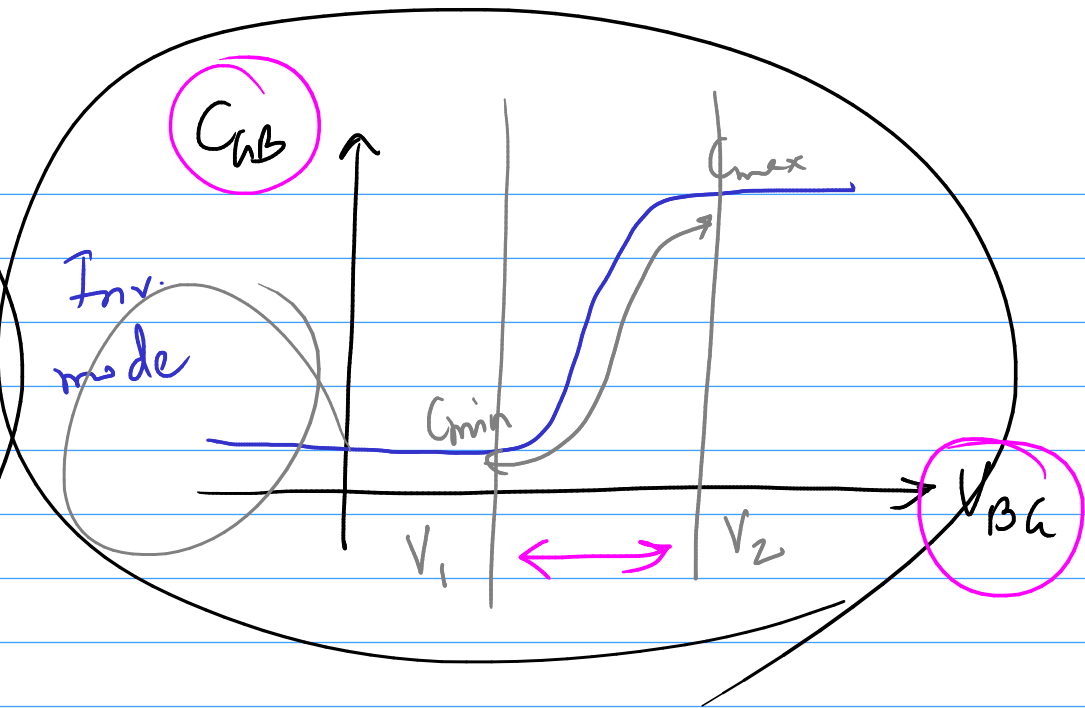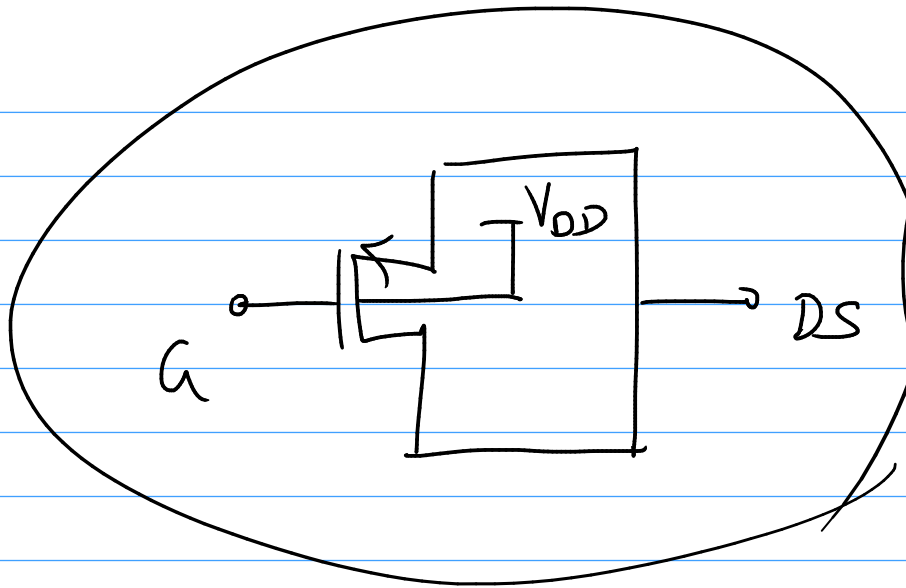


AC mode

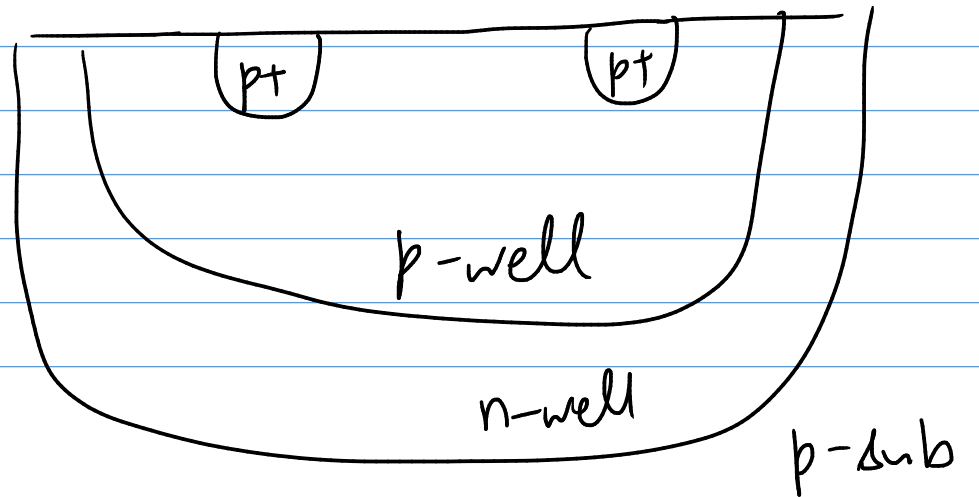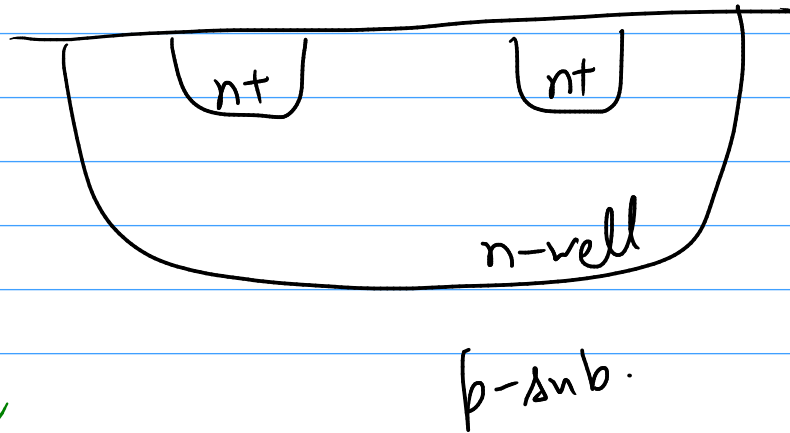


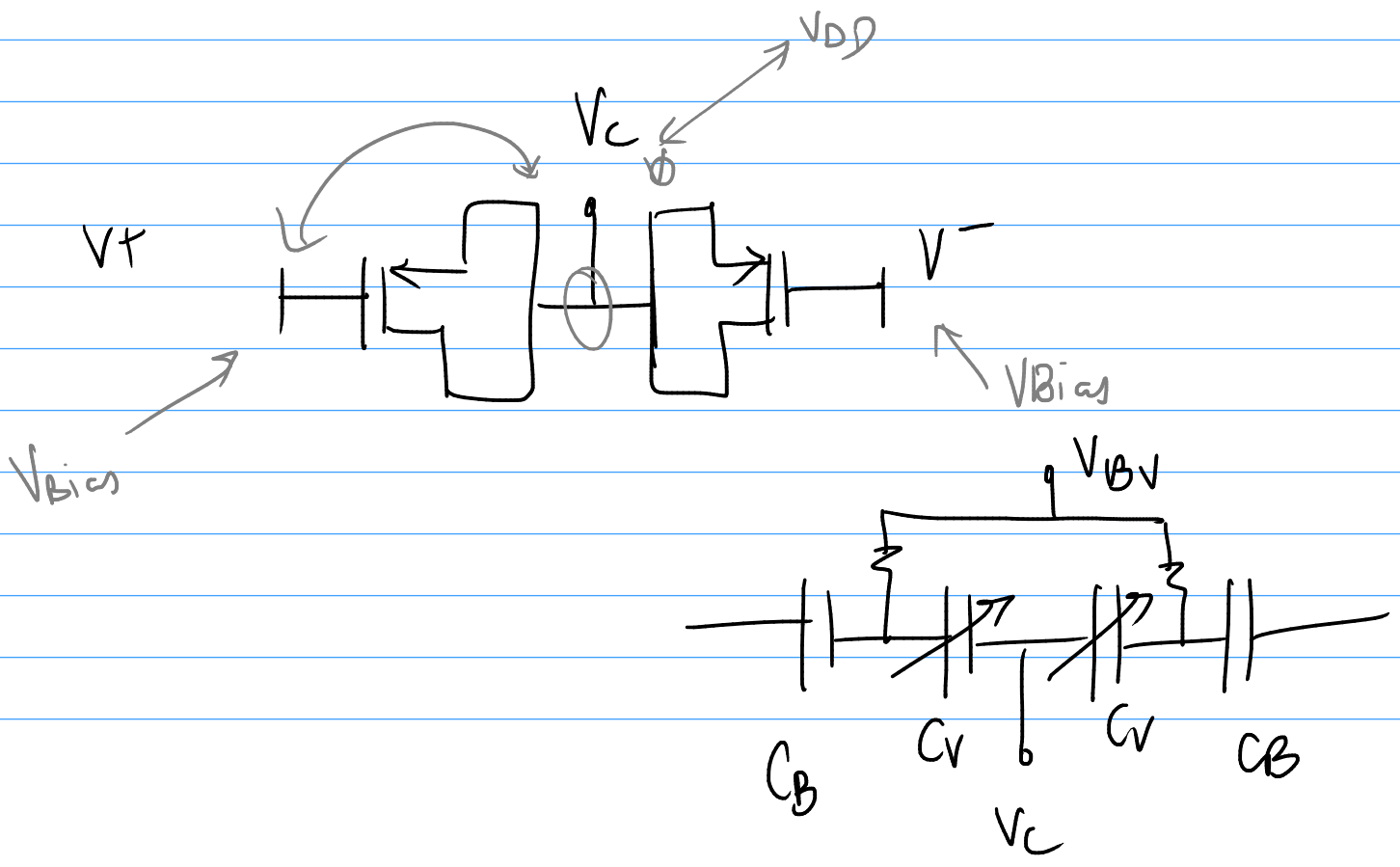
$$R_{\text{mosvar}} \approx \frac{1}{\mu C_{ox} \left(\frac{W}{L}\right) (V_{BL} - V_{Tp})}$$



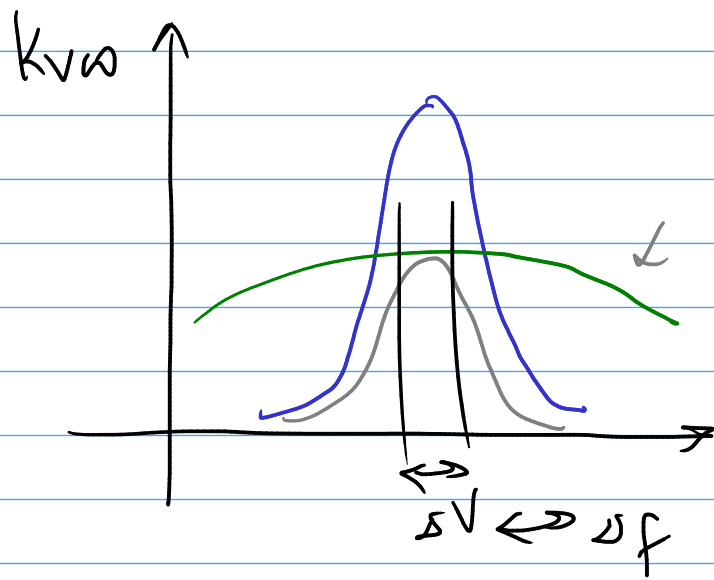




We want  $Kv\omega \sim 100 \frac{M}{Hz} \frac{1}{V}$

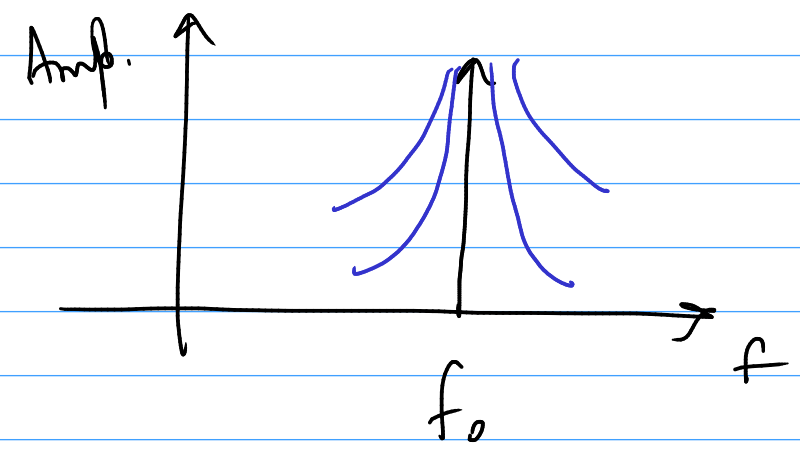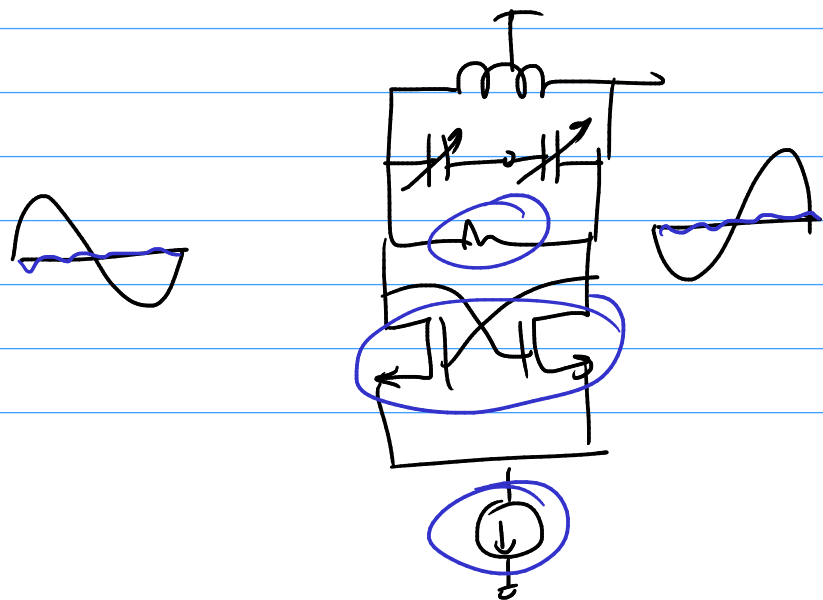large Varactor  
AM noise  $\rightarrow$  PM noise








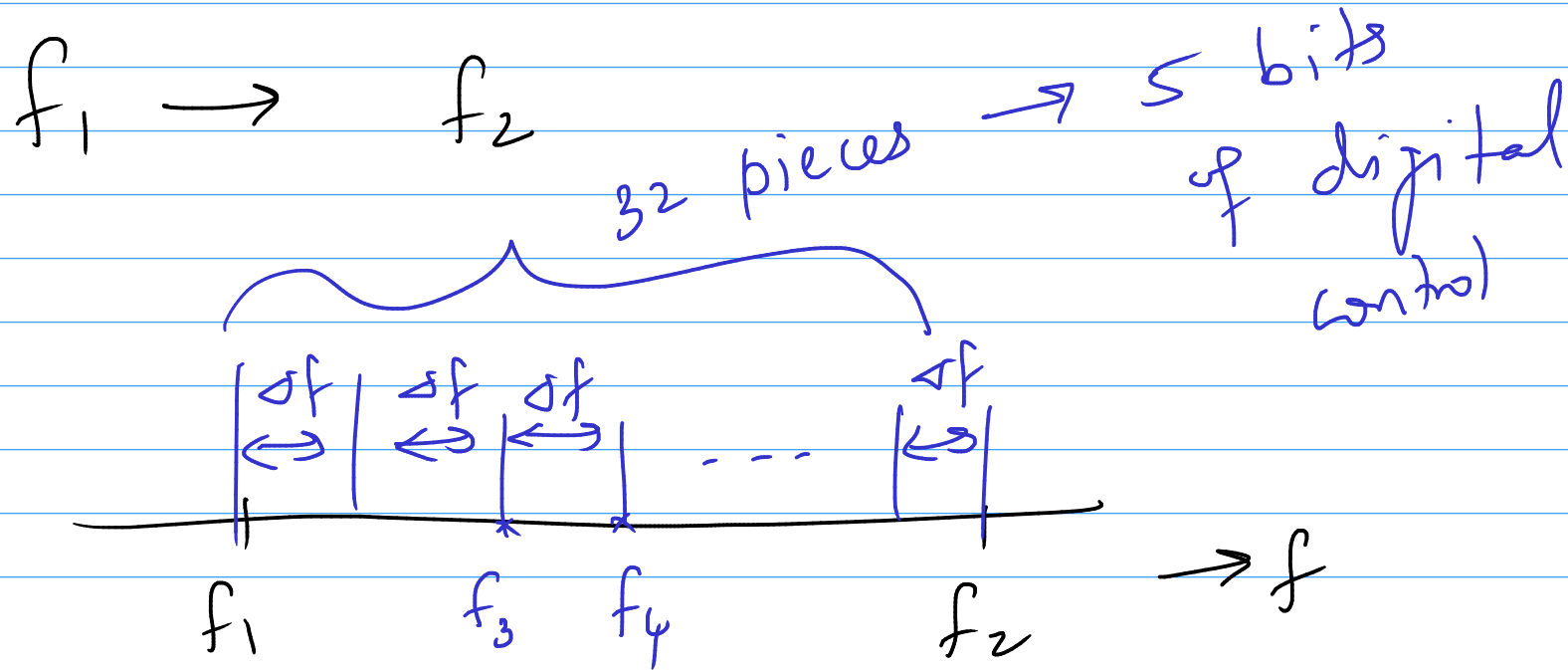
$$\textcircled{\sim} \rightarrow [A + a_n(t)] \cos(\omega_0 t)$$




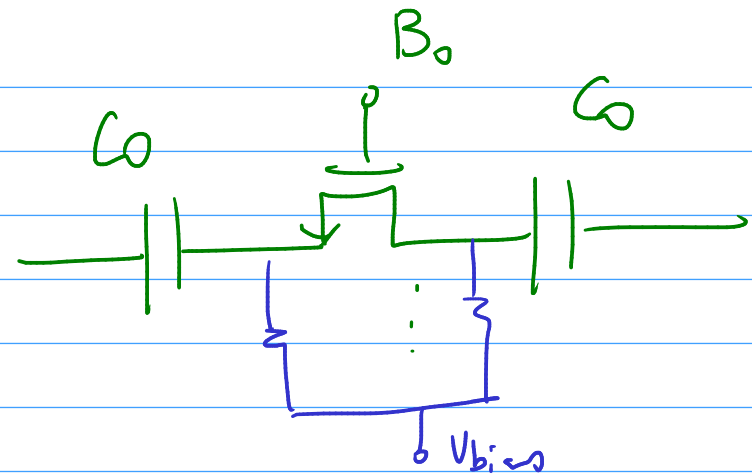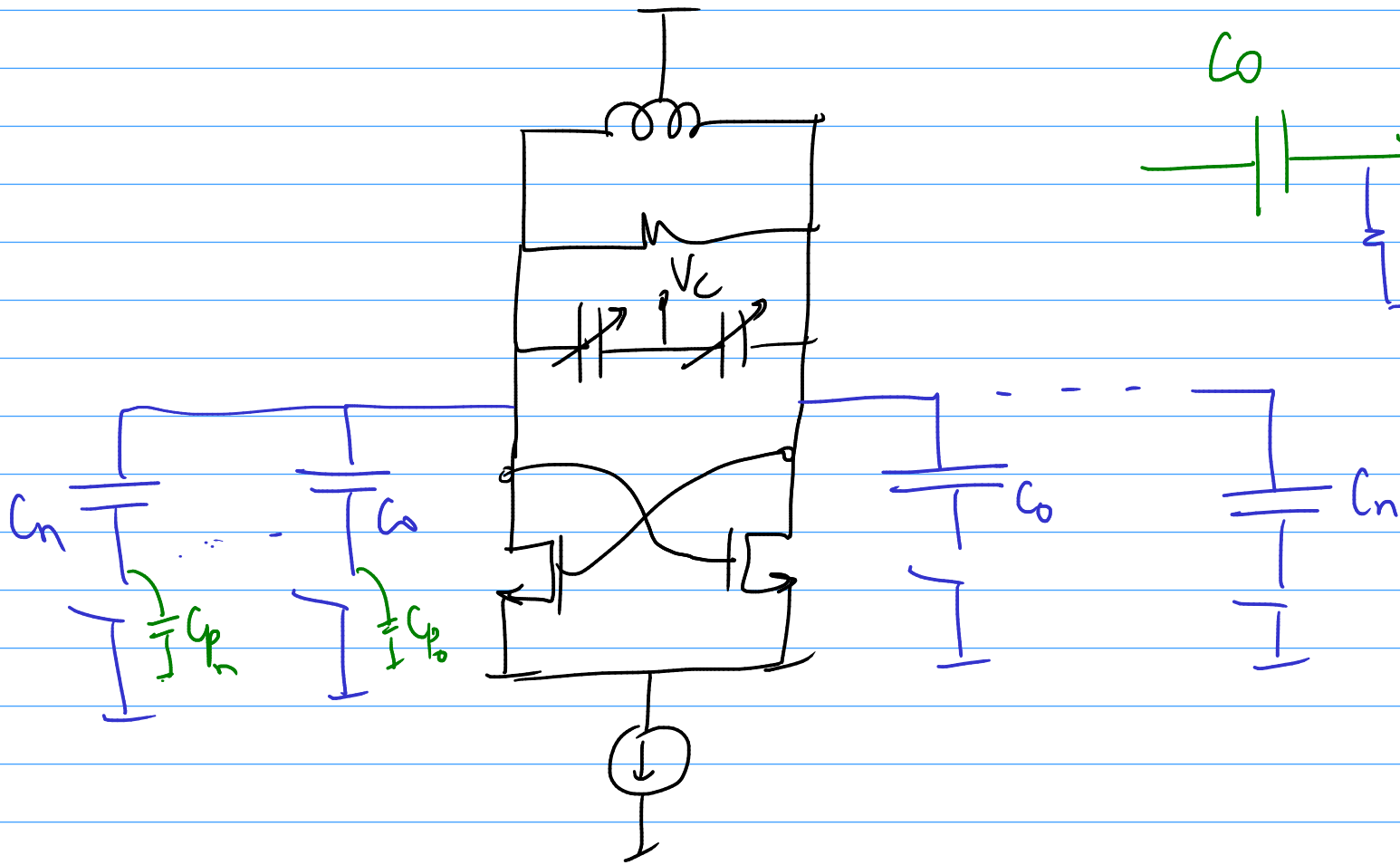

Size of  
switch



$\frac{C_{max}}{C_{min}}$  | cap bank  
 $Q$  | cap bank

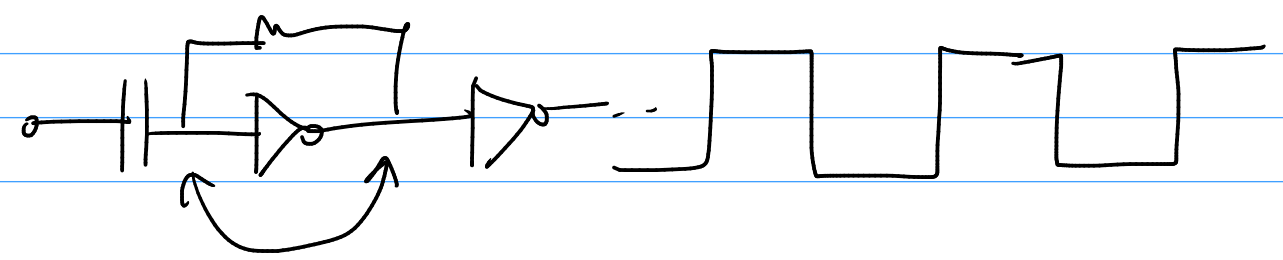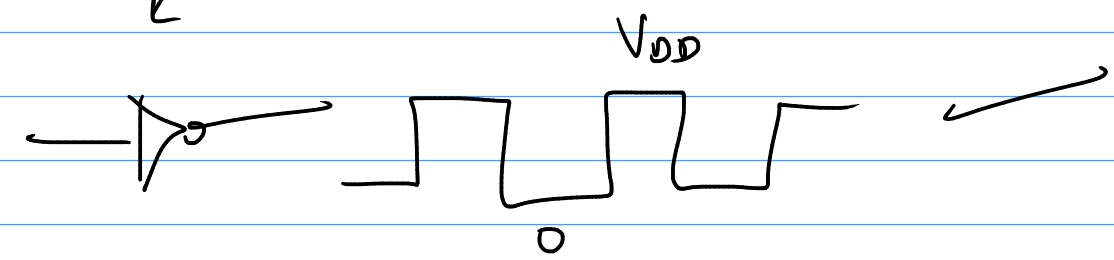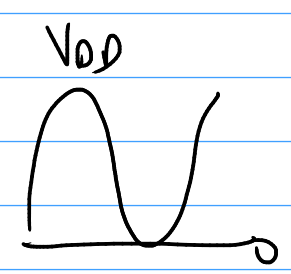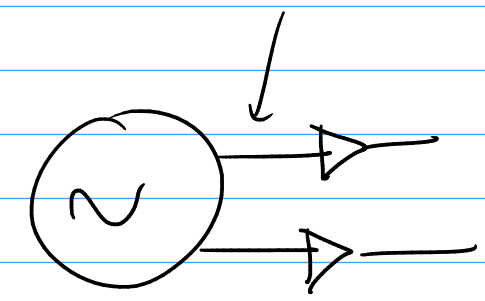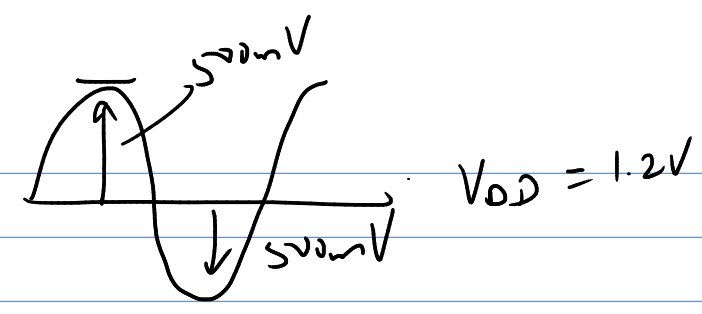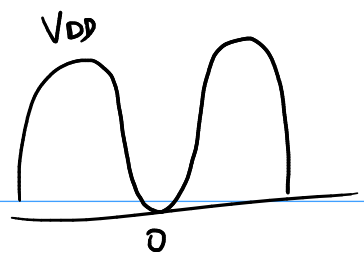





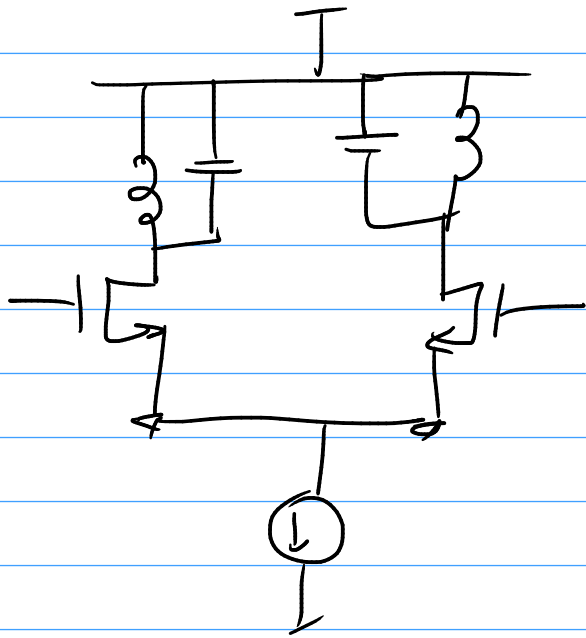





tuned buffer

fvst  
Polyphase filter

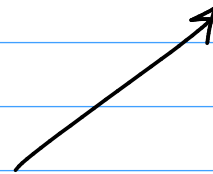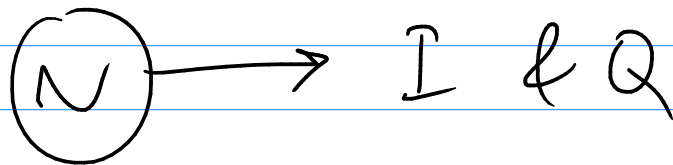


1) Polyphase

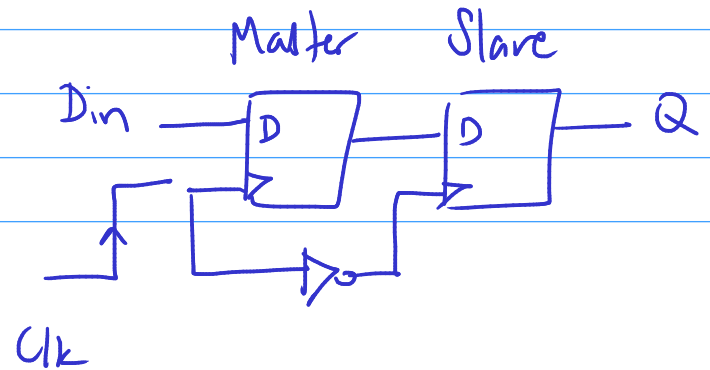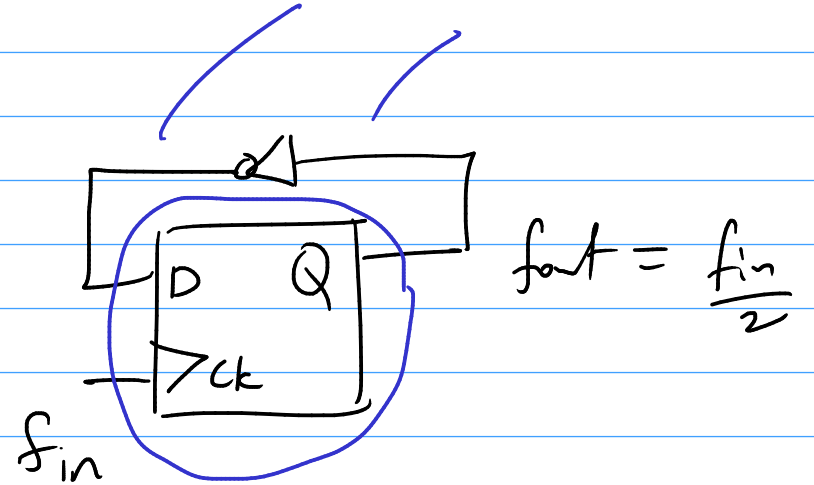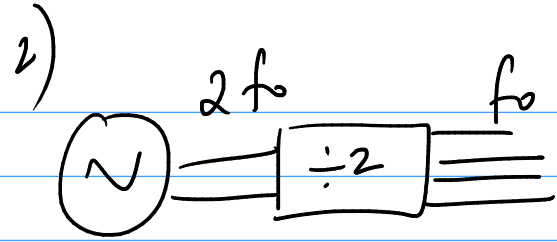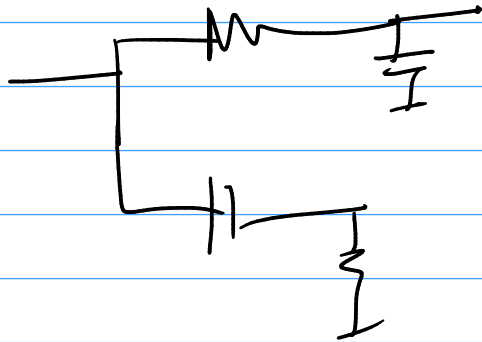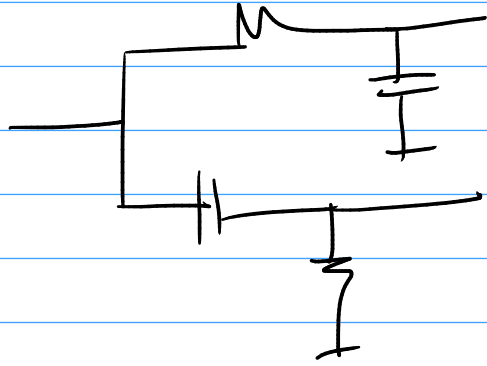

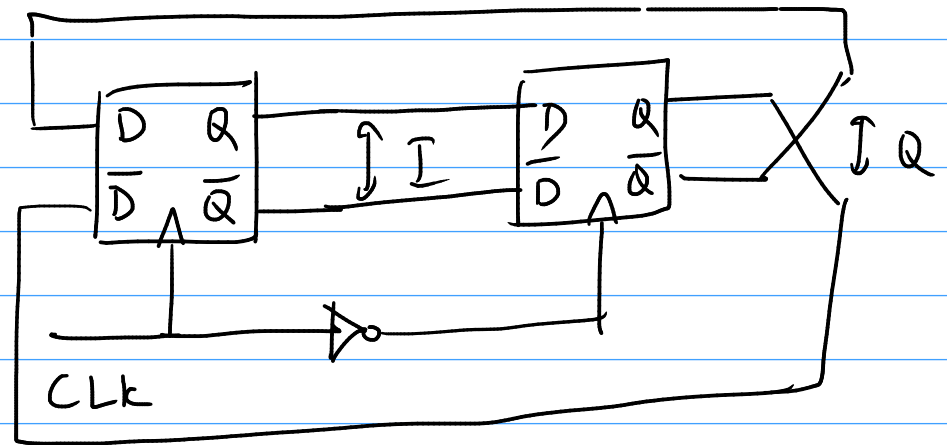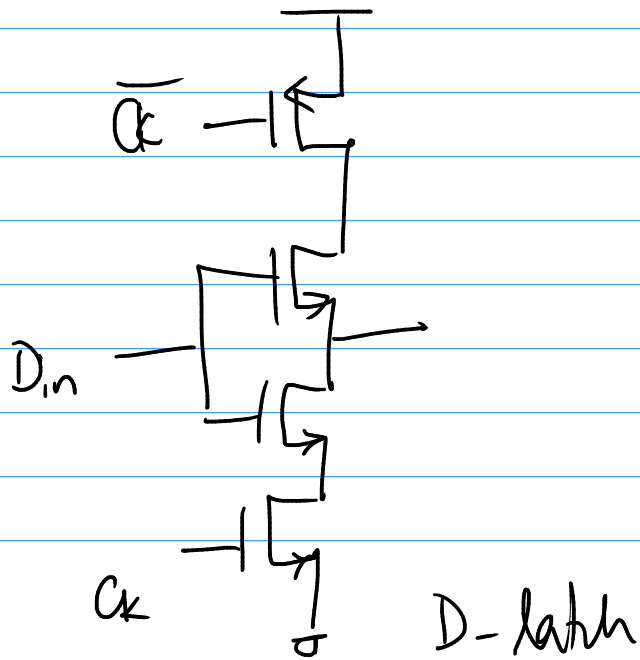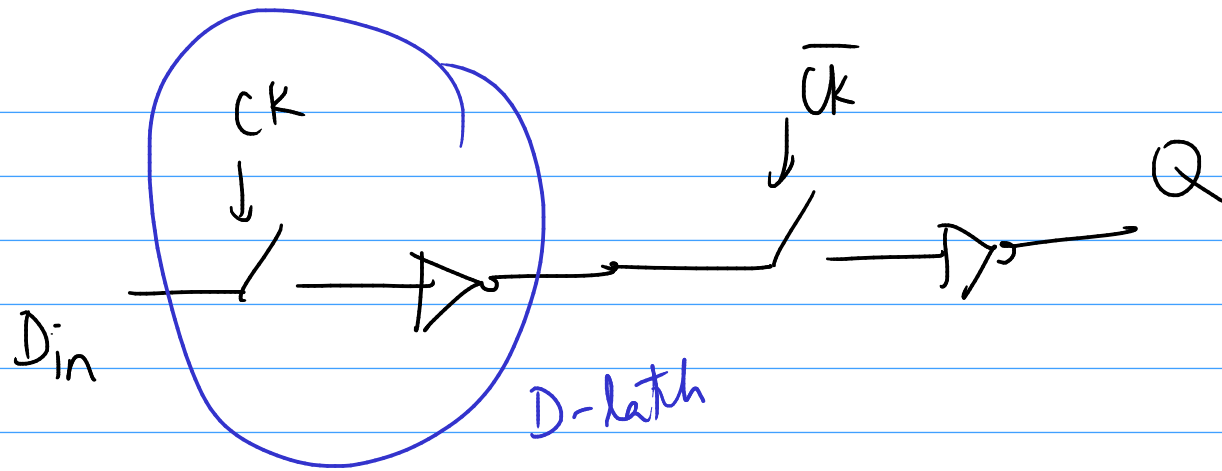


3)

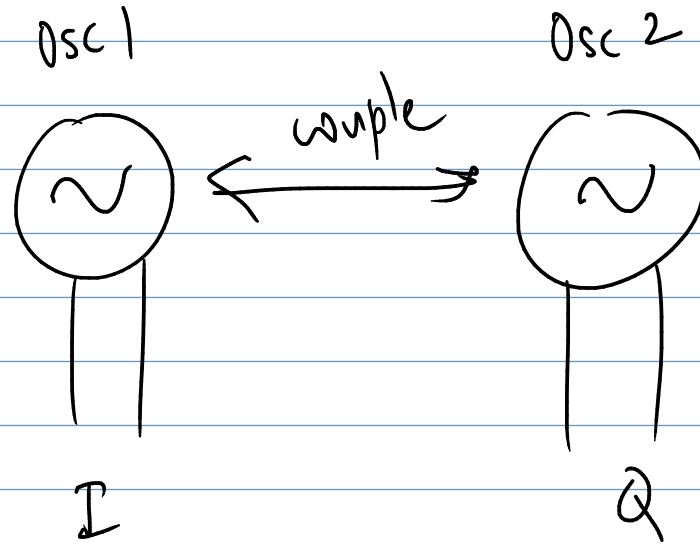


Quadrature VCO

Osc #1

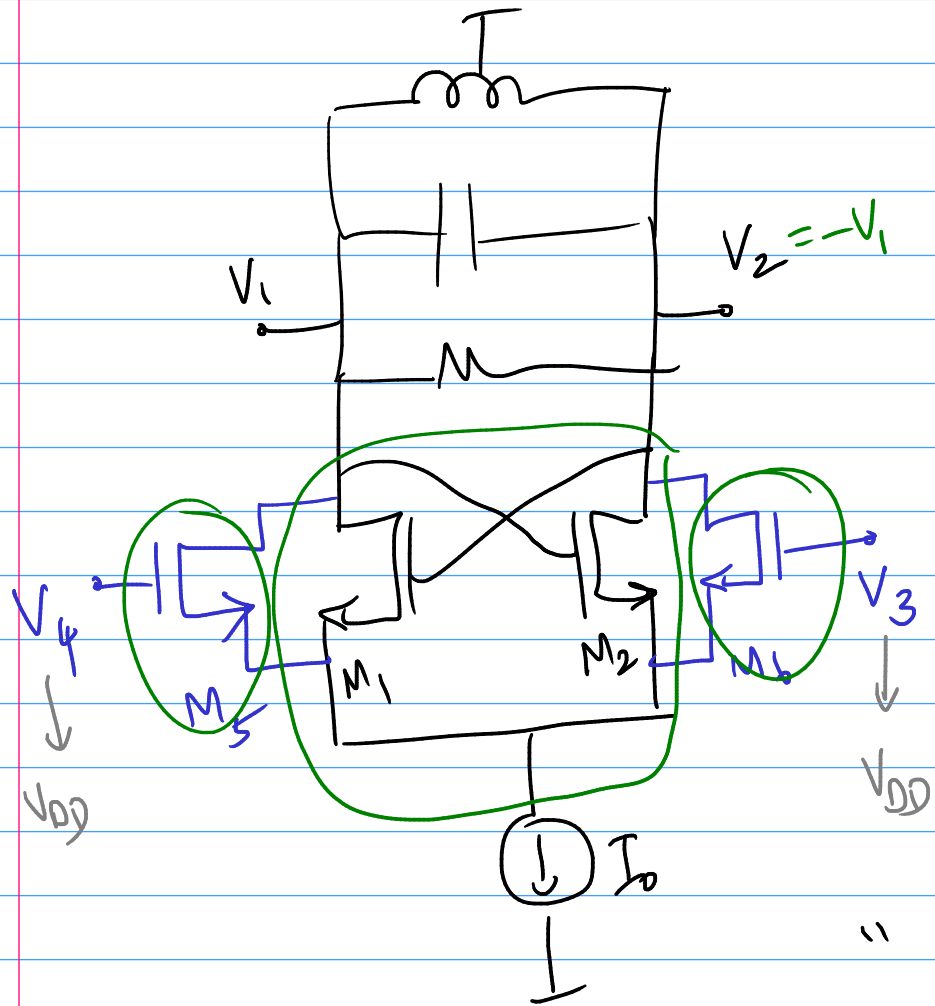

Osc #2

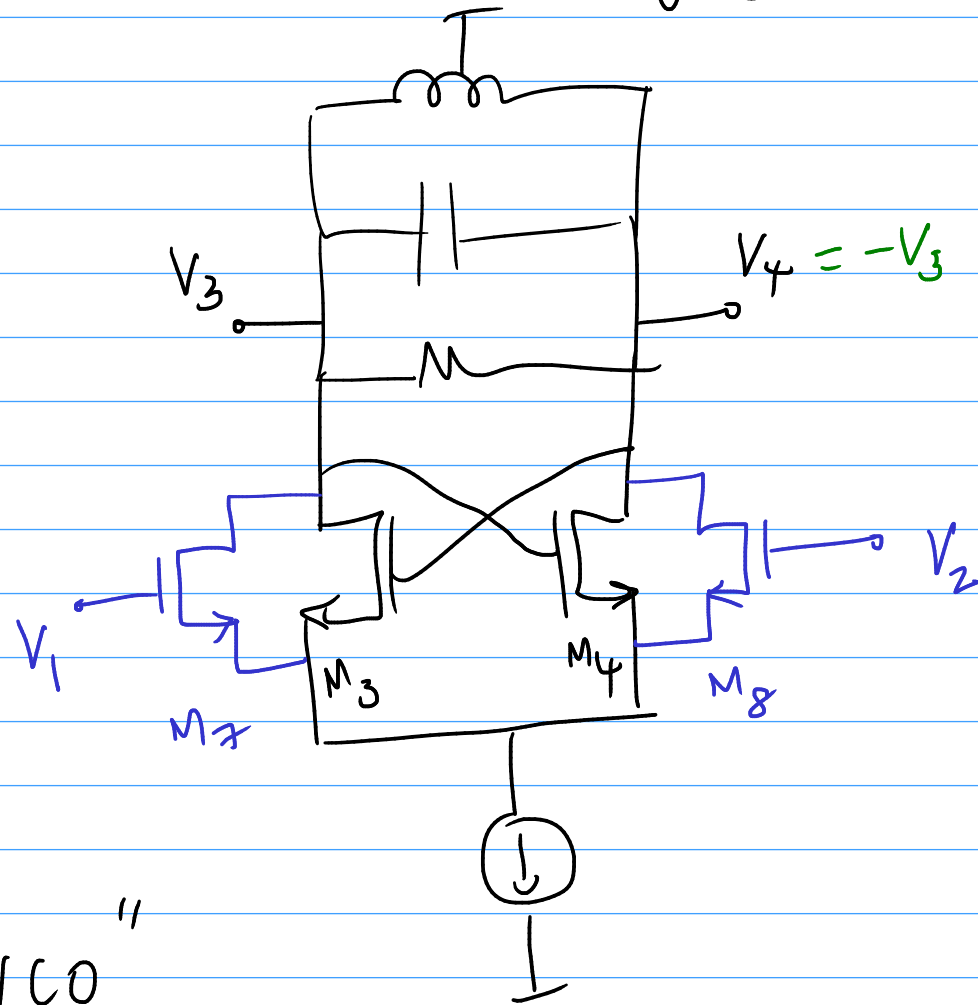

"QVCO"

case (i) :  $V_1 - V_2$  &  $V_3 - V_4$  are in phase

$$V_1 \equiv V_3, \quad V_2 \equiv V_4$$

$M_1 - M_8$  are all identical

\* Both osc. die down

case (ii)  $V_1 - V_2$  &  $V_3 - V_4$  are out of phase

$$V_1 \equiv V_4, \quad V_2 \equiv V_3$$

\* Both osc. die down

case (iii)

$V \angle 0$



$\odot$

$V \angle \theta$


$\odot$

\* Component of  $V \angle \theta$  in- or out-of-phase  
with  $V \angle 0$  will die out

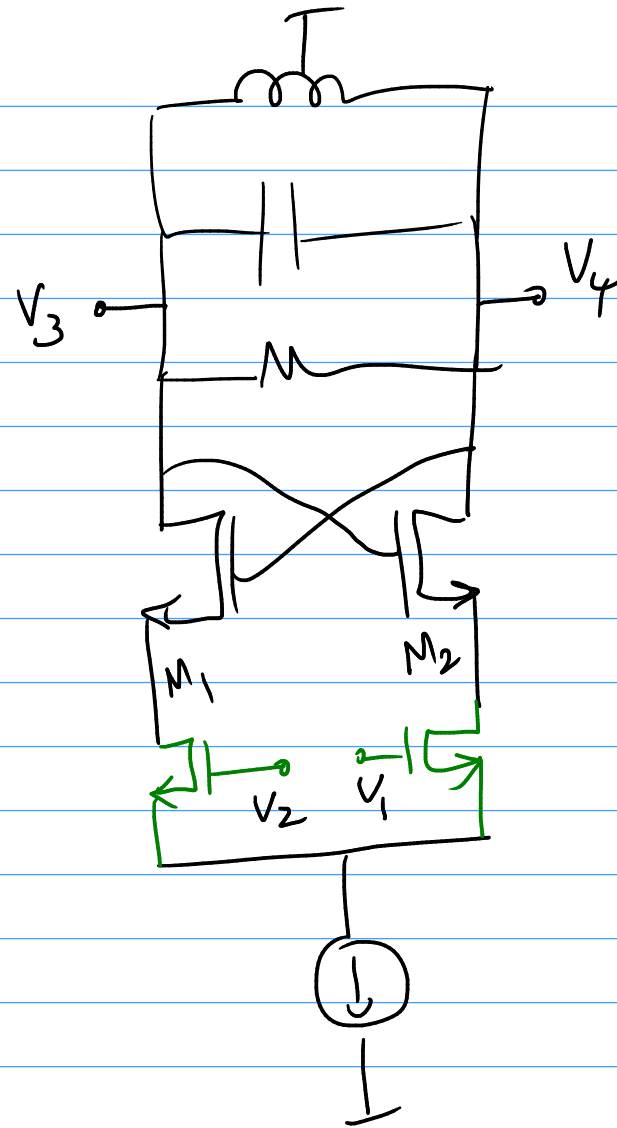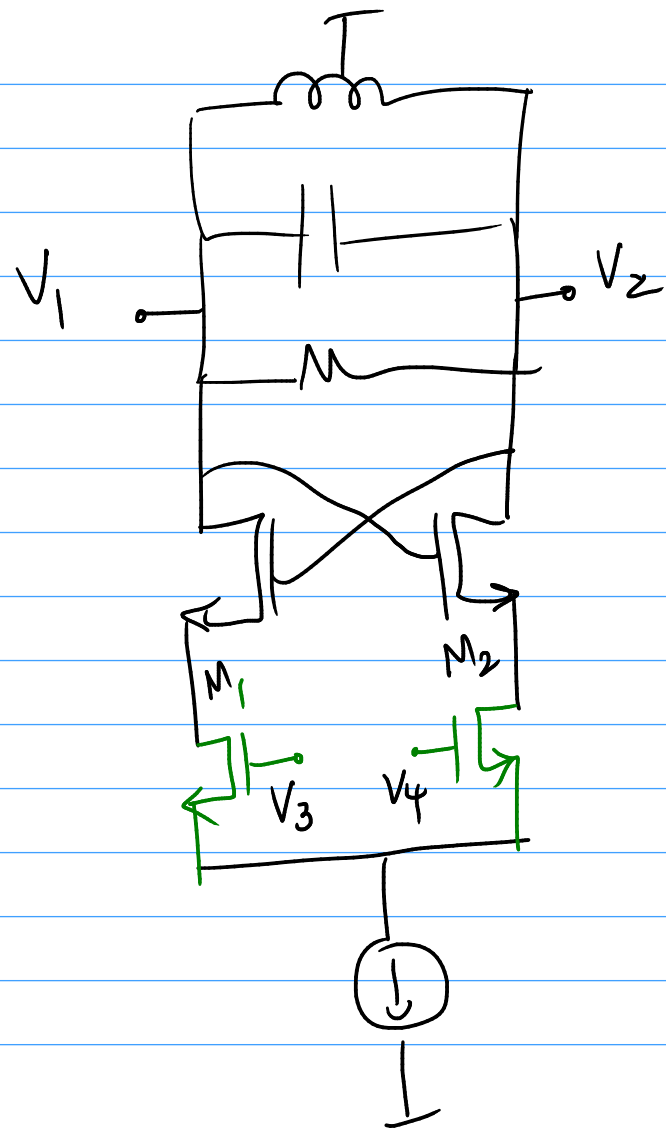\*  $V \angle 0$  &  $V \angle 90^\circ$  } steady state  
 $V \angle 0$  &  $V \angle -90^\circ$  }



Series  
Coupled  
QVCO

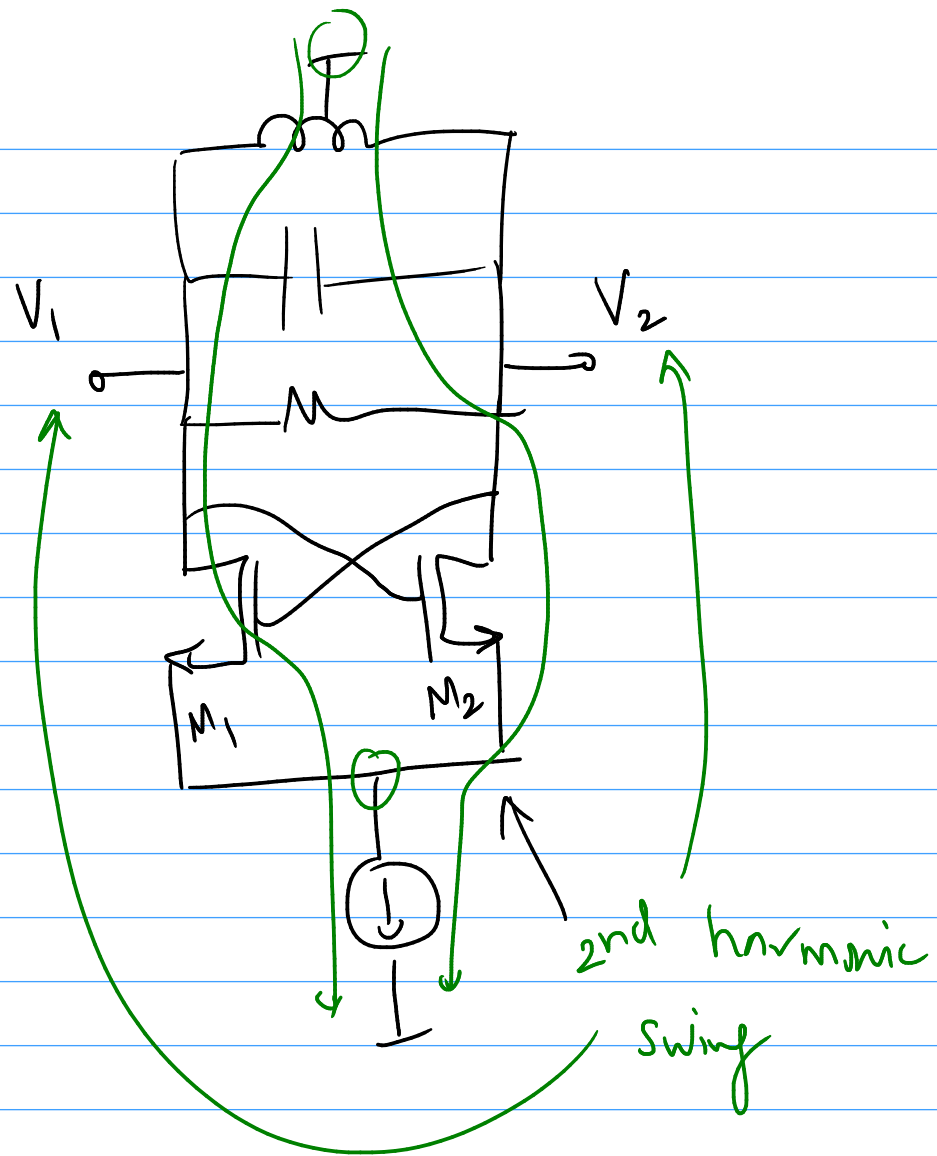

# Noise in Oscillators

Ideal  $\textcircled{\sim} \rightarrow V_a \cos(\omega_0 t)$




Real  $\textcircled{\sim} \rightarrow \curvearrowright$



$$\left[ V_a + \underbrace{u_n(t)}_{\text{Amplitude Noise}} \right] \cdot \cos(\omega_0 t + \underbrace{\phi_n(t)}_{\text{Phase Noise}})$$

Amplitude  
Noise

Phase  
Noise


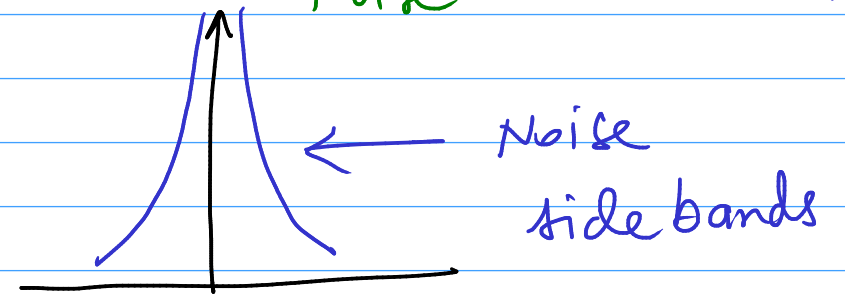

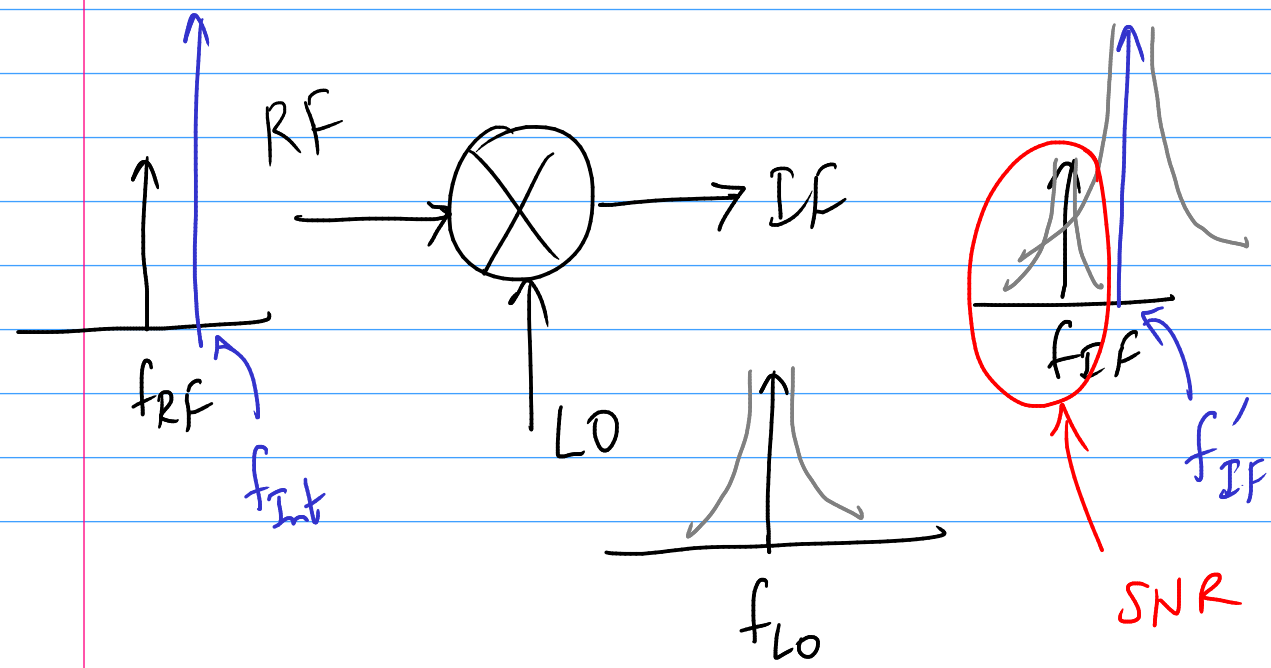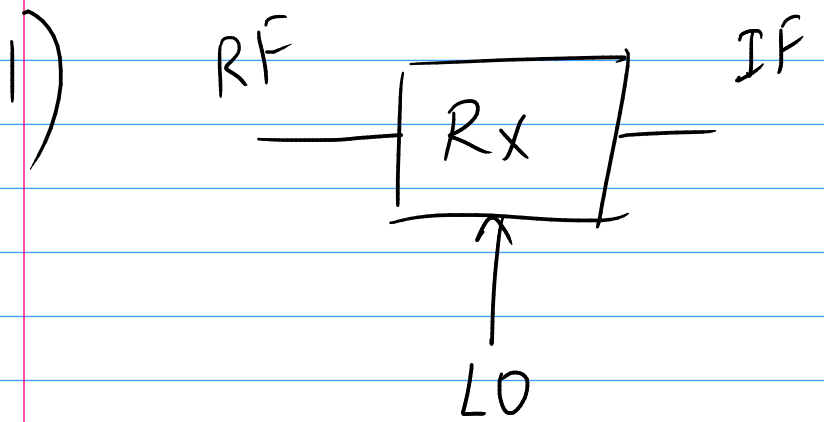
$$\omega(t) = \omega_0 + \frac{d}{dt} \phi_n(t)$$



"Reciprocal  
Mixing"


SNR degradation

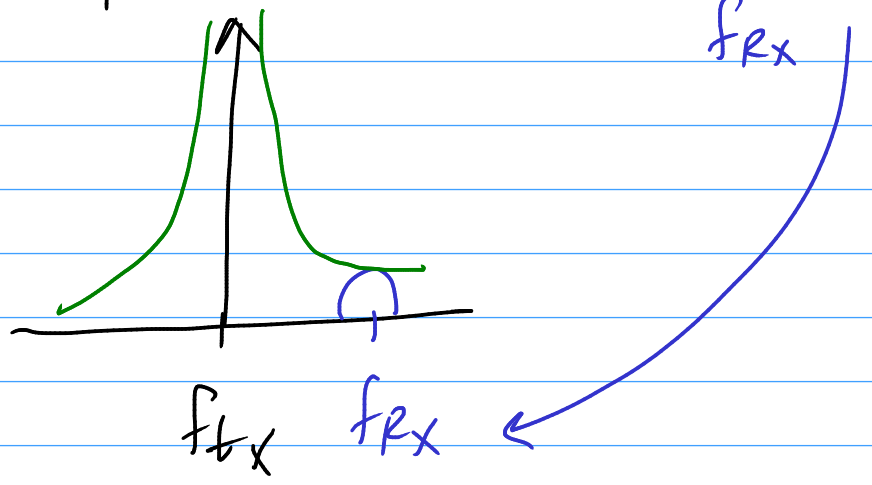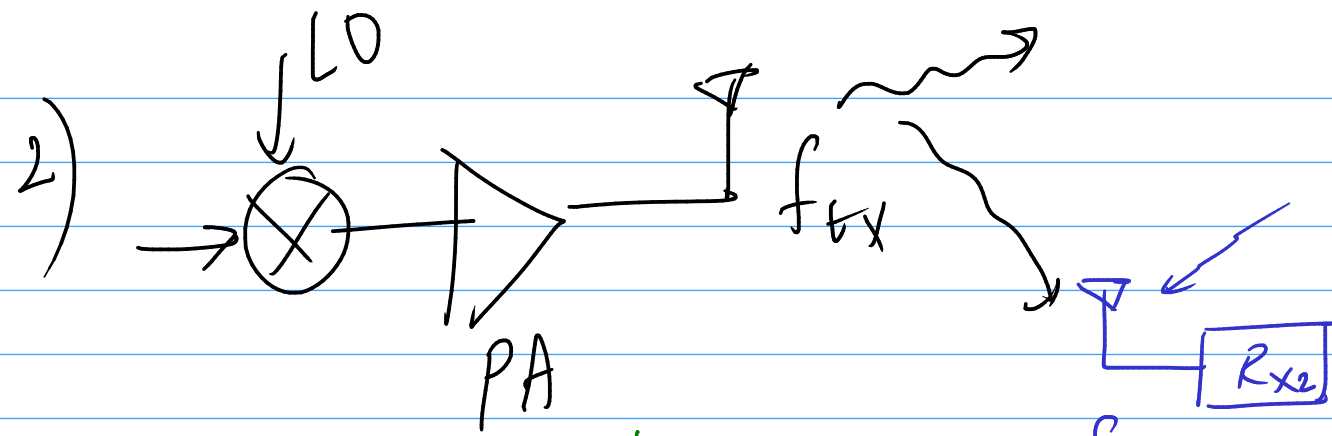


for  
any  
 $12 \times 1$

# Phase Noise

PN units = dBc/Hz

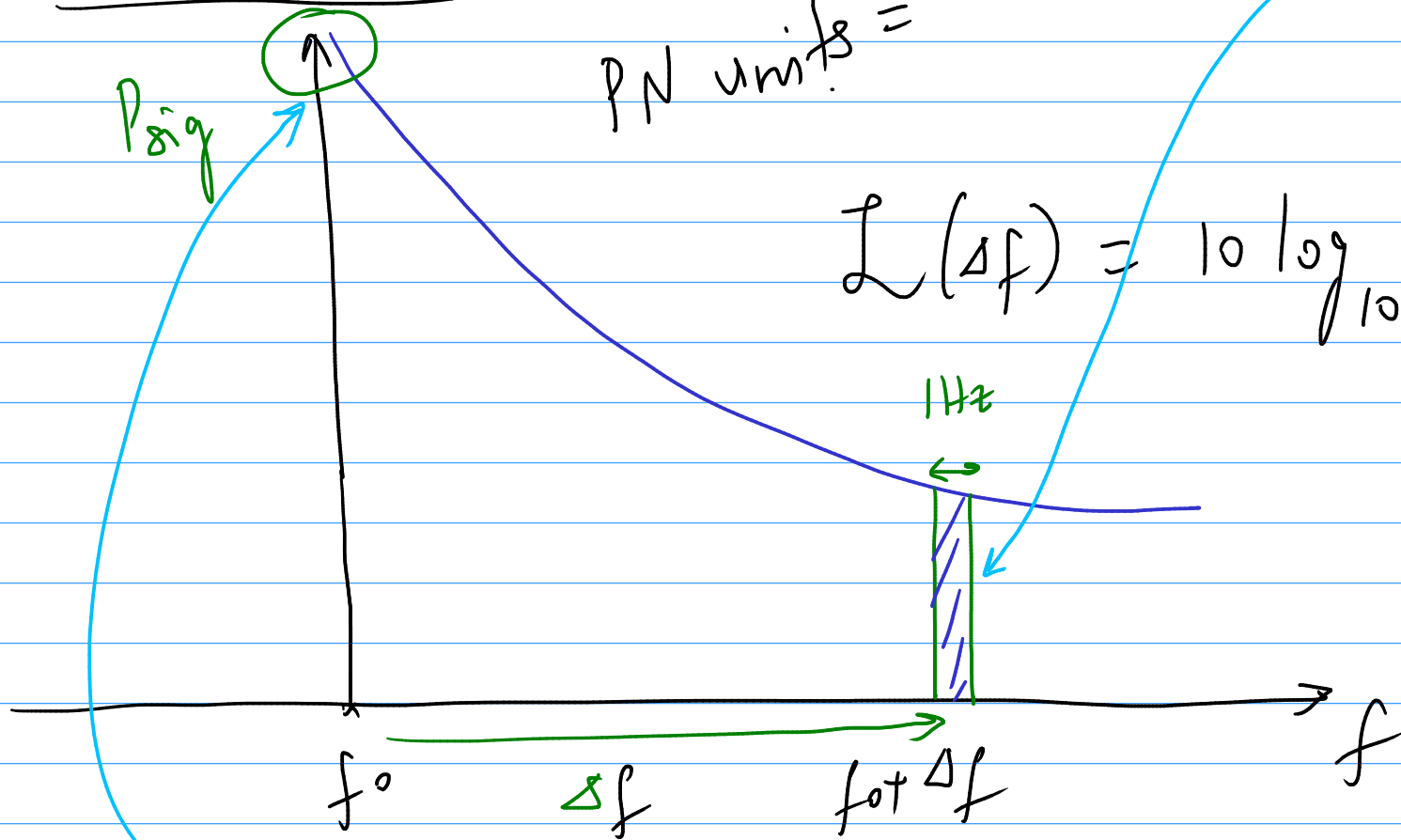
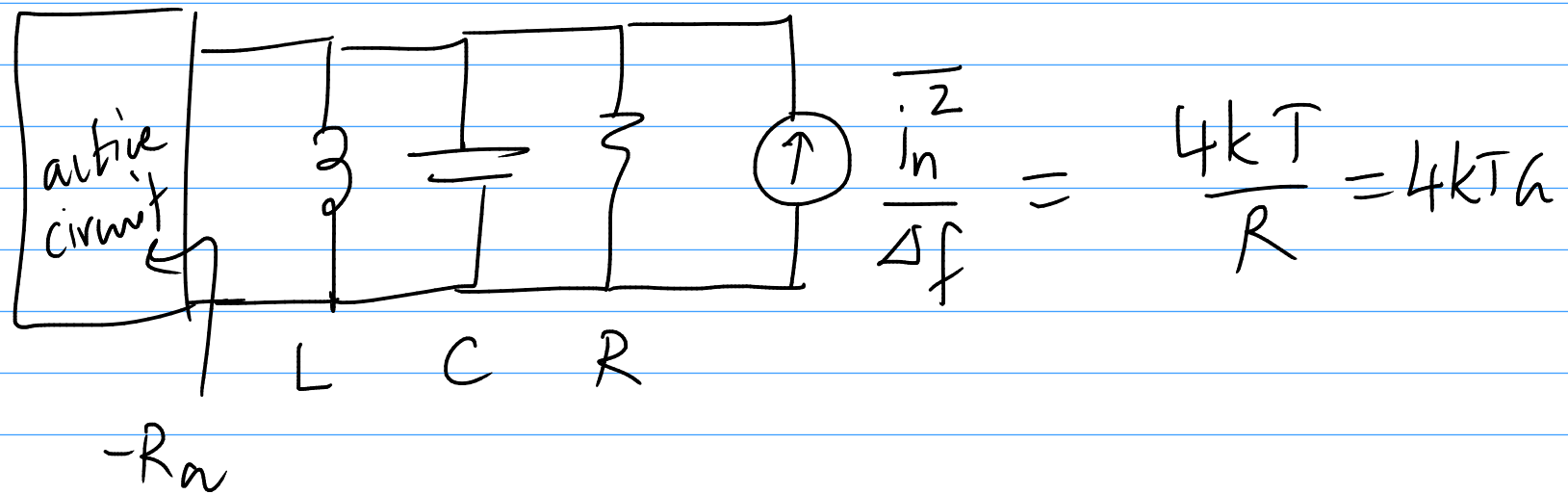
$$L(\Delta f) = 10 \log_{10} \left[ \frac{P_{1\text{Hz}}(f_0 + \Delta f)}{P_{\text{sig}}} \right]$$



(a)  $(\omega_0 + \Delta\omega)$

$$Y(\omega_0 + \Delta\omega) = G + j(\omega_0 + \Delta\omega) \cdot C + \frac{1}{j(\omega_0 + \Delta\omega)L}$$

$$= G + \frac{j^2 (\omega_0 + \Delta\omega)^2 LC + 1}{j (\omega_0 + \Delta\omega)L}$$

$$= G + \frac{\underbrace{1 - \omega_0^2 LC}_{\rightarrow 0} - 2\omega_0 \Delta\omega LC - \cancel{\Delta\omega^2 LC}_{\rightarrow 0}}{j (\omega_0 + \Delta\omega)L}$$

$$\approx G - \frac{2\omega_0 \Delta\omega LC}{j (\omega_0 + \Delta\omega)L} \approx G + j \frac{2\omega_0 \Delta\omega}{\omega_0 + \Delta\omega} C$$

$$Z(\omega_0 + \Delta\omega) = \frac{1}{G + j \cdot \frac{2\omega_0 \Delta\omega C}{\omega_0 + \Delta\omega}}$$

$$= \frac{1}{G} \cdot \frac{1}{1 + j \frac{2\omega_0 \Delta\omega RC}{\omega_0 + \Delta\omega}} \approx \omega_0$$

$$Q_0 = \omega_0 RC$$

$$Z(\omega_0 + \Delta\omega) = R \cdot \frac{1}{1 + j 2Q_0 \frac{\Delta\omega}{\omega_0}}$$

$$|Z(\omega_0 + \Delta\omega)| \approx \frac{R\omega_0}{2Q_{\text{eff}}\Delta\omega} \quad \text{if } Q \text{ is very high}$$

$$\frac{\overline{v_n^2}}{\Delta f} = \frac{\overline{i_n^2}}{\Delta f} \cdot |Z|^2$$

$$= \frac{4kT}{R} \times \frac{R^2 \cdot \omega_0^2}{4Q_{\text{eff}}^2 \Delta\omega^2}$$

$$= 4kTR \cdot \left( \frac{\omega_0}{2Q_{\text{eff}}\Delta\omega} \right)^2$$

1/2 as  
Ampl. Noise


1/2 as  
Phase Noise

$$P_N = \frac{1}{2} \frac{V_n^2}{\Delta f} = 2kTR \left( \frac{\omega_0}{2Q\Delta\omega} \right)^2$$


$$L(\Delta\omega) = 10 \log_{10} \left[ \frac{\frac{1}{2} \frac{V_n^2}{\Delta f}}{V_{sig}^2} \right]$$

$$= 10 \log_{10} \left[ \frac{2kTR \cdot \left( \frac{\omega_0}{2Q\Delta\omega} \right)^2}{V_{sig}^2} \right]$$
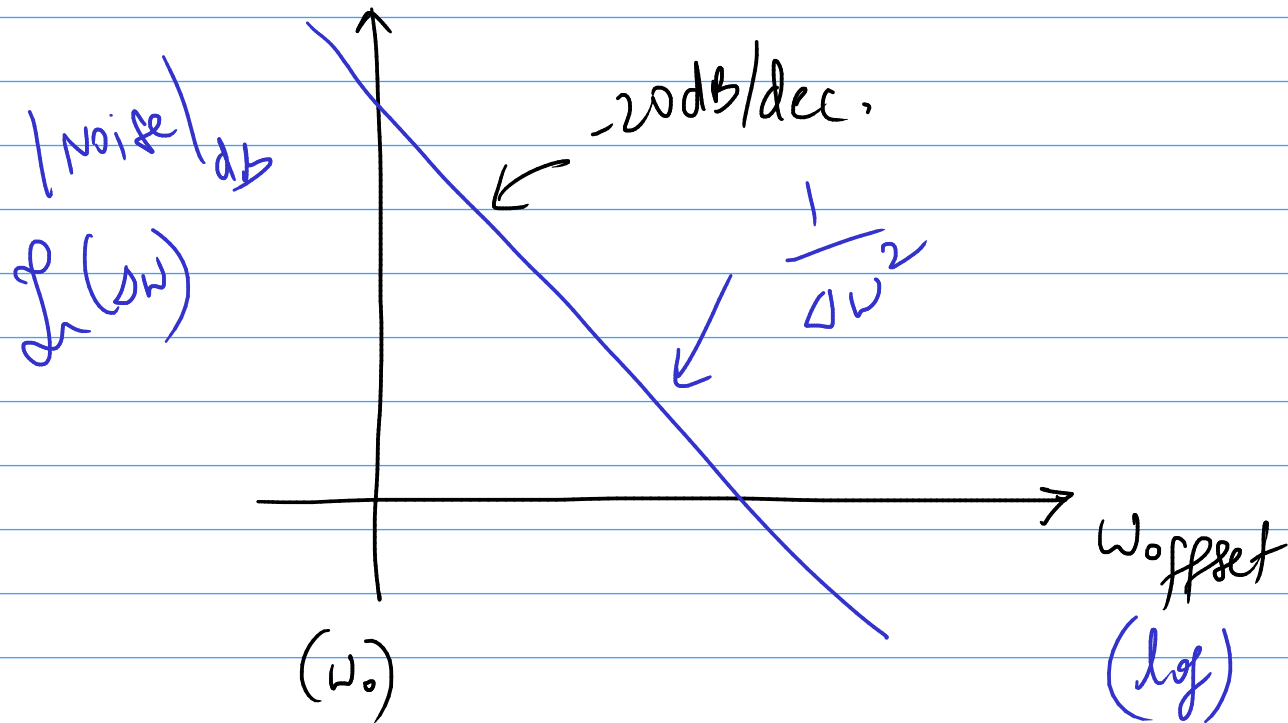
$$L(\Delta\omega) = 10 \log_{10} \left[ \frac{2kT}{P_{sig}} \left( \frac{\omega_0}{2Q\Delta\omega} \right)^2 \right]$$



# Real Osc. Spectrum:

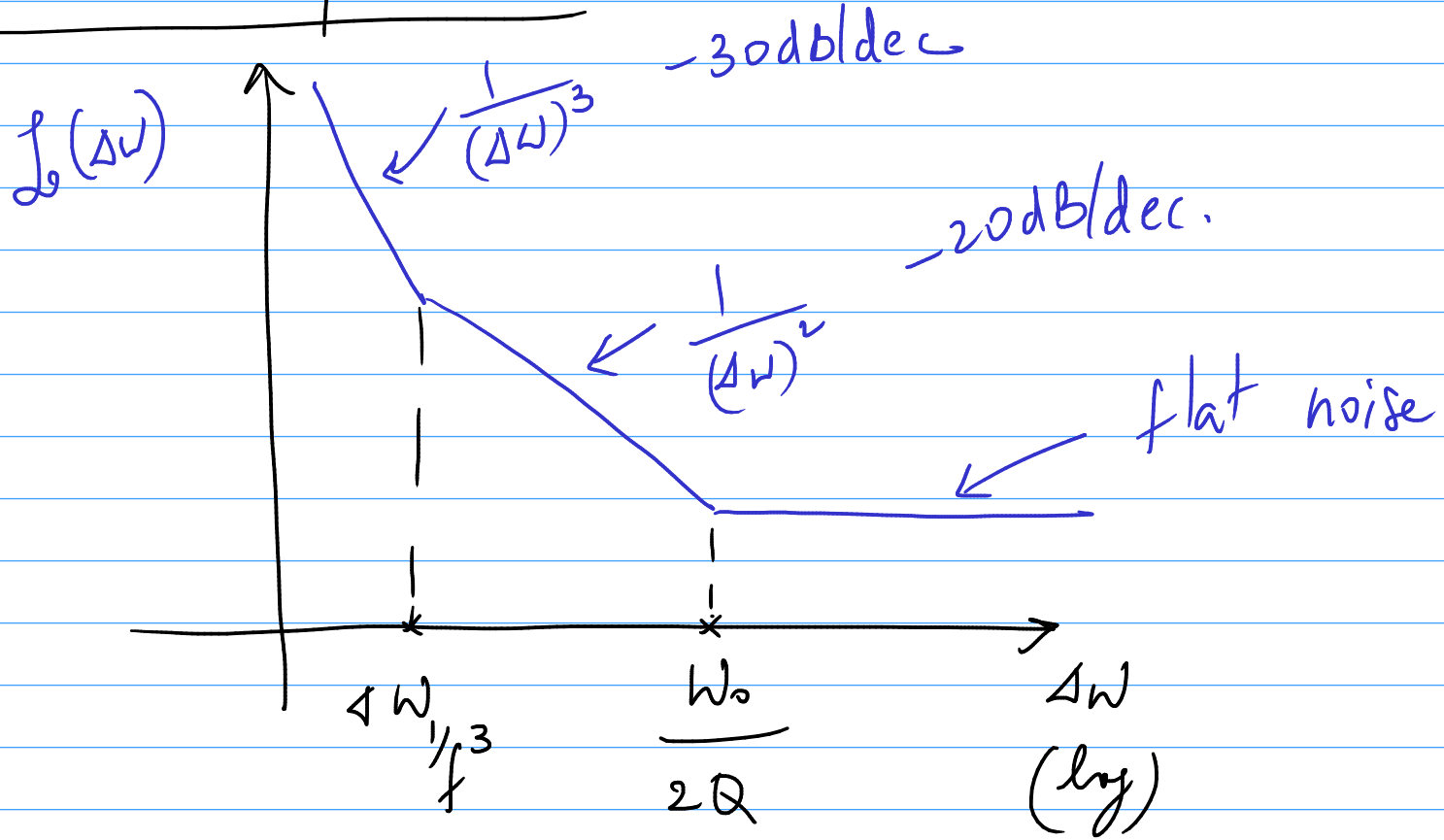

1) D.B. Leeson, "A simple model of feedback oscillator noise spectrum", Proceedings of the IEEE pp 320-330, Feb. 1966

$$L(\Delta\omega) = 10 \log_{10} \left[ \frac{2kTF}{P_{sig}} \left\{ 1 + \left( \frac{\omega_0}{2Q\Delta\omega} \right)^2 \right\} \left\{ 1 + \frac{\Delta\omega_{1/2}^3}{f} \right\} \right]$$

Maximise  
 $V_{sig}$

Maximise  
 $Q$

F - empirical term  
"excess noise number"

2) J. Rael & A. Abidi, "Physical processes of phase noise in differential LC oscillators", IEEE Custom Integrated Circuits Conference, 2000.

Osc. is Nonlinear


$$F = 2 + \frac{8\gamma^2 R I_T}{\pi V_0} + \gamma \cdot \frac{8}{9} g_m R$$

(CC LC osc.)



$$V_0 = \frac{2}{\pi} \cdot I_T R$$
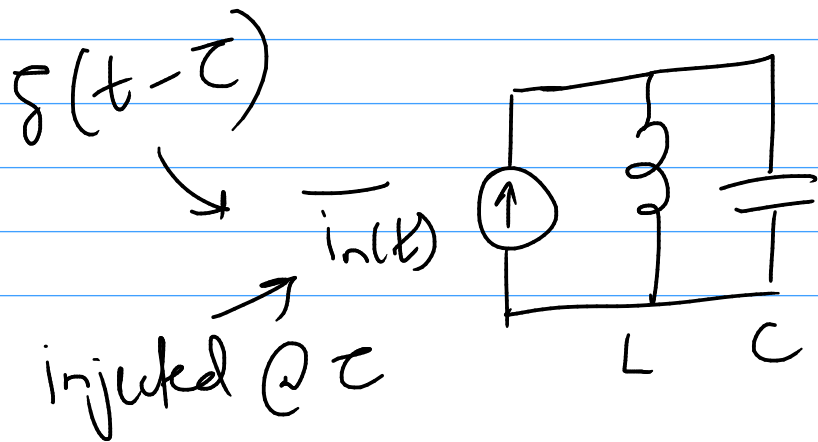
### 3) Hajimiri-Lee LTV model



Noise is small  $\rightarrow$  "Linear" approx is valid  
for small deviations around  
NL v operating point  
(but periodic)





1)

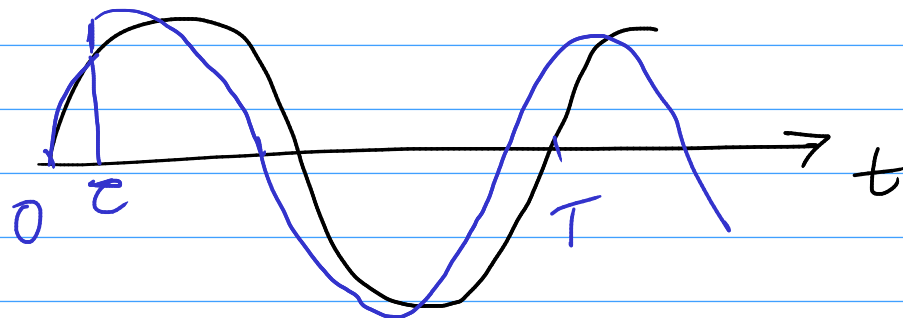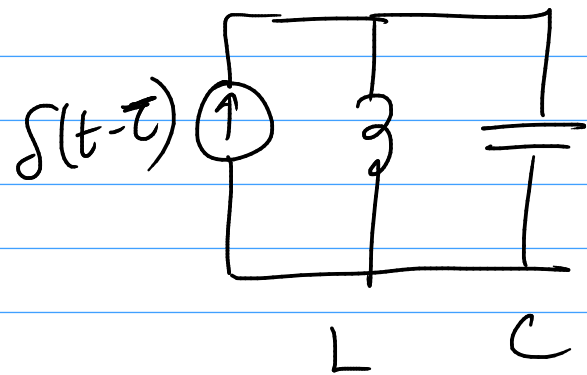

2)

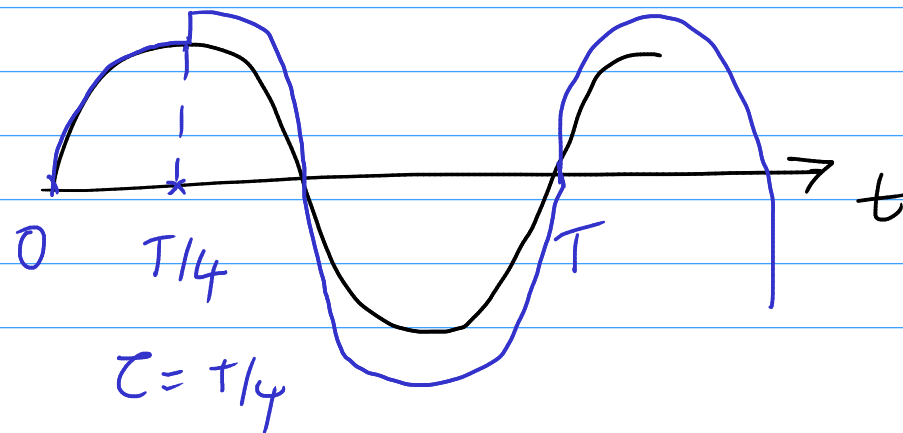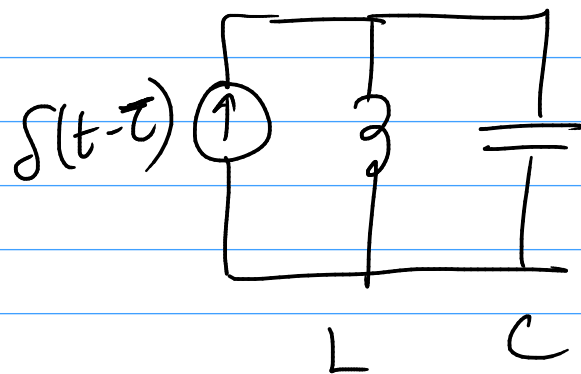


3)

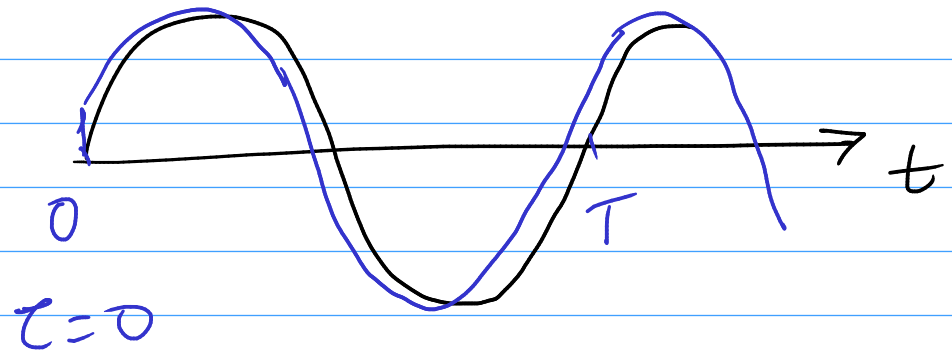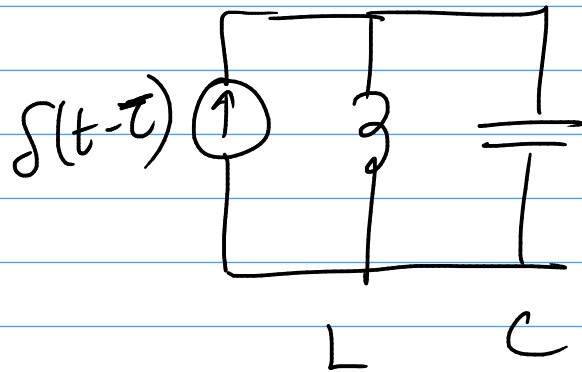

Osc. looks like an LTV system w.r.t. noise

$$v(t) = V_0 \cos(\omega_0 t)$$

$$i_n(t) = \Delta q \delta(t - \tau)$$

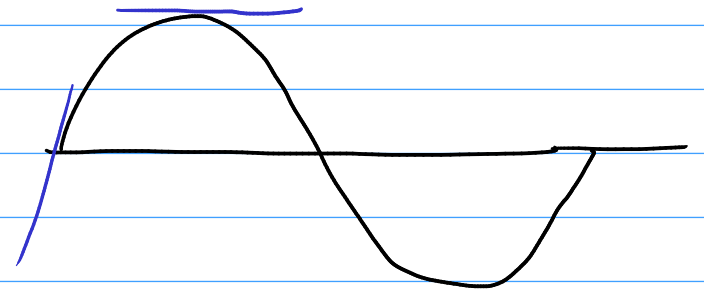

$$\Delta v = \frac{\Delta q}{C}$$

$$v(t + \Delta t) = v(t) + \frac{dv}{dt} \cdot \Delta t$$

$$\Delta v = \frac{dv}{dt} \cdot \Delta t \rightarrow \Delta t = \frac{\Delta v}{dv/dt}$$

$$\Delta t(\tau) = \frac{\Delta V}{- \omega_0 V_0 \sin(\omega_0 \tau)}$$

$$\Delta \varphi = \omega_0 \Delta t$$

$$\Delta \varphi(\tau) = \frac{\omega_0 \cdot \Delta q / C}{- \omega_0 V_0 \sin(\omega_0 \tau)} = - \frac{\Delta q}{\underbrace{C V_0}_{q_{\max}} \cdot \sin(\omega_0 \tau)}$$

$$\Delta \varphi(\tau) = - \frac{\Delta q}{q_{\max} \sin(\omega_0 \tau)}$$

Define  $\Gamma(\omega_0\tau) =$  Impulse Sensitivity Function (ISF)

$$\Delta\varphi = \frac{\Delta q}{q_{\max}} \cdot \underbrace{\Gamma(\omega_0\tau)}_{\text{dimensionless,}}$$

$$\Gamma(\omega_0\tau + 2\pi) = \Gamma(\omega_0\tau) \quad \text{periodic}$$

$i_n(t) \leftarrow$  noise current flowing into LC tank

$$dq = i_n(t) dt$$

$$d\varphi(t) = \frac{\Gamma(\omega_0 t)}{q_{\max}} \cdot i_n(t) dt$$

$$\frac{d\varphi}{dt} = \frac{\Gamma(\omega_0 t)}{q_{\max}} \cdot i_n(t)$$

$$\Gamma(\omega_0 t) = C_0 + \sum_{k=1}^{\infty} C_k \cos(k\omega_0 t + \theta_k)$$

$i_n(t) \leftarrow$  white noise  
 $S_i(\omega) = S_i$

$$\dot{\varphi} = \frac{d\varphi}{dt} = \frac{\Gamma(\omega_0 t)}{q_{\max}} \cdot i_n(t)$$

PSD

$$S_{\dot{\varphi}} = \frac{\Gamma_{\text{rms}}^2}{q_{\max}^2} S_i$$

$$\Gamma_{\text{rms}}^2 = \frac{1}{2\pi} \int_0^{2\pi} \Gamma^2(x) dx$$

$$\dot{\varphi} = \frac{d\varphi}{dt}$$

$$\dot{\Phi}(\omega) = j\omega \Phi(\omega)$$

$$\Phi(\omega) = \frac{1}{j\omega} \cdot \dot{\Phi}(\omega)$$

Phase  
PSD

$$S_{\varphi}(\omega) = \frac{1}{\omega^2} S_{\dot{\varphi}}(\omega)$$

$$= \frac{1}{\omega^2} \cdot \frac{\Gamma_{rms}^2}{q_{vmax}^2} \cdot S_i$$

$$L(\Delta\omega) \propto \frac{1}{(\Delta\omega)^2}$$

-20dB/dec  
region

Flicker noise

$$S_i(\omega) \propto \frac{1}{|\omega|} \quad \leftarrow \text{low-freq.}$$

$$S_\varphi(\omega) \propto \frac{1}{|\omega|^3},$$





depends on DC value of  $\int \rightarrow C_0$



$$S_{\dot{q}}(\omega) \propto \frac{C_0^2}{q_{\max}^2} \cdot \frac{1}{|\omega|}$$

$$S_q(\omega) \propto \frac{C_0^2}{q_{\max}^2} \cdot \frac{1}{|\omega|^3} \quad \left. \vphantom{\frac{C_0^2}{q_{\max}^2} \cdot \frac{1}{|\omega|^3}} \right\} -30 \text{ dB/dec.}$$

low  $C_0 \iff$  symmetric  $\Gamma$


choice of VCO topology matters

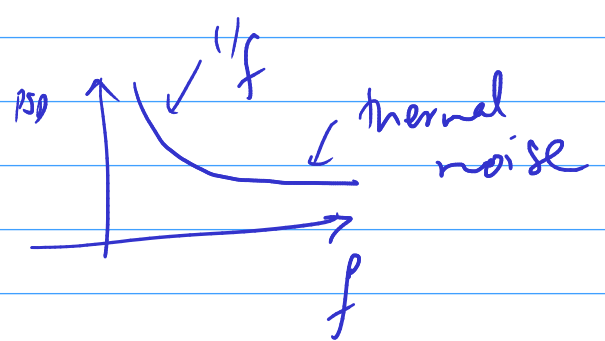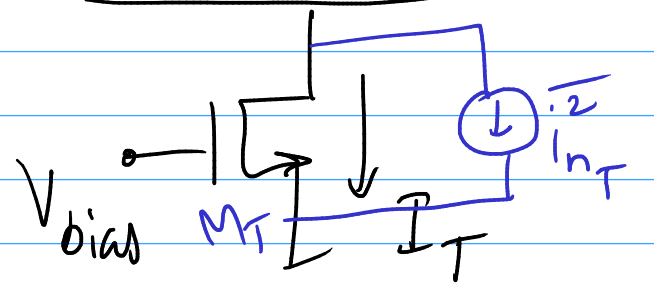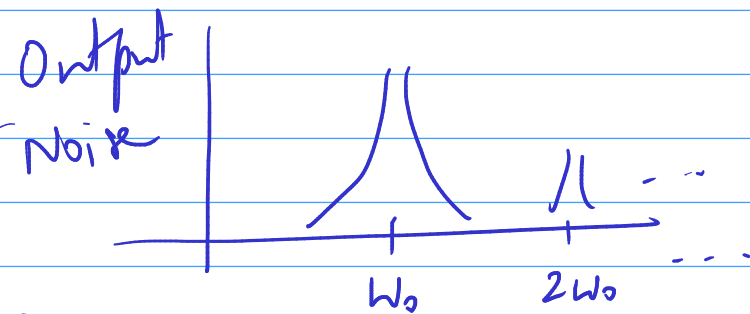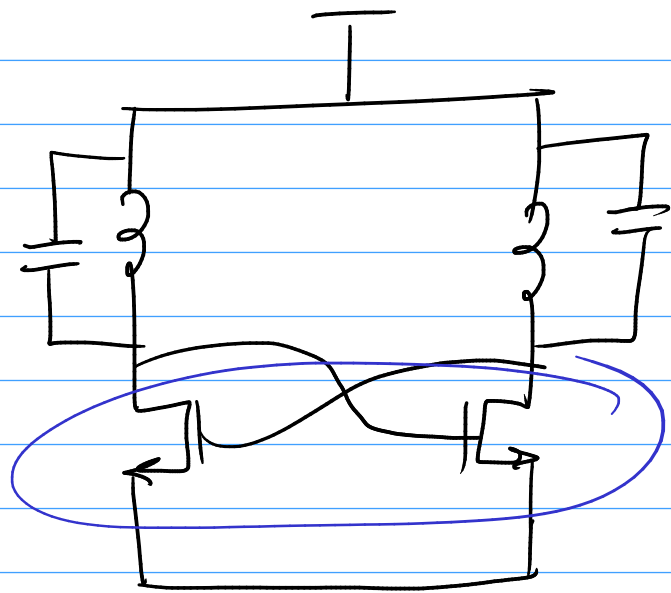

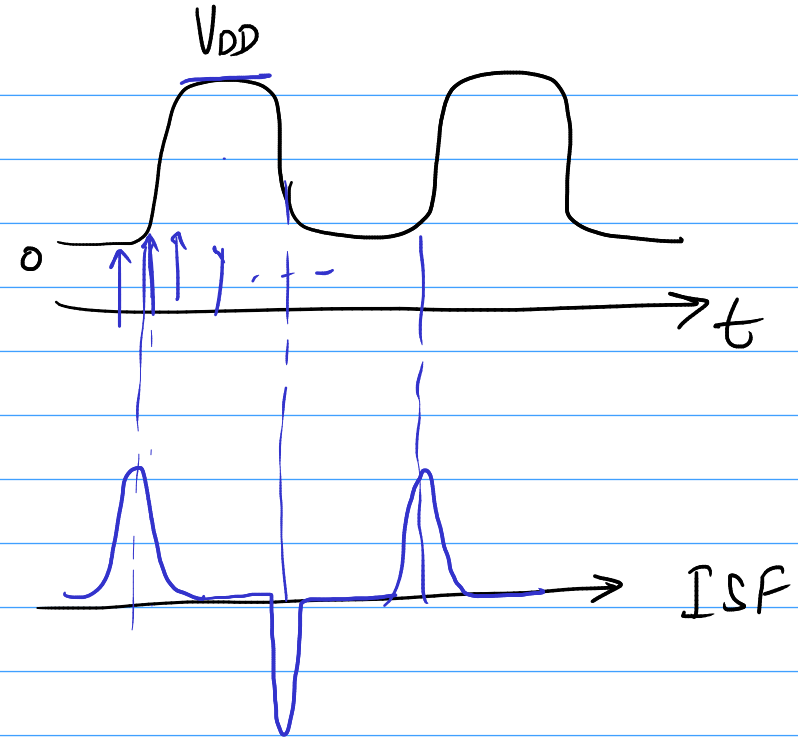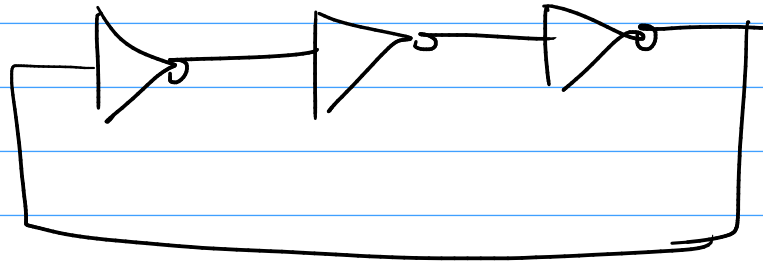

4) Demir - Roy Chowdhury Model


$ISF \leftrightarrow PPV$

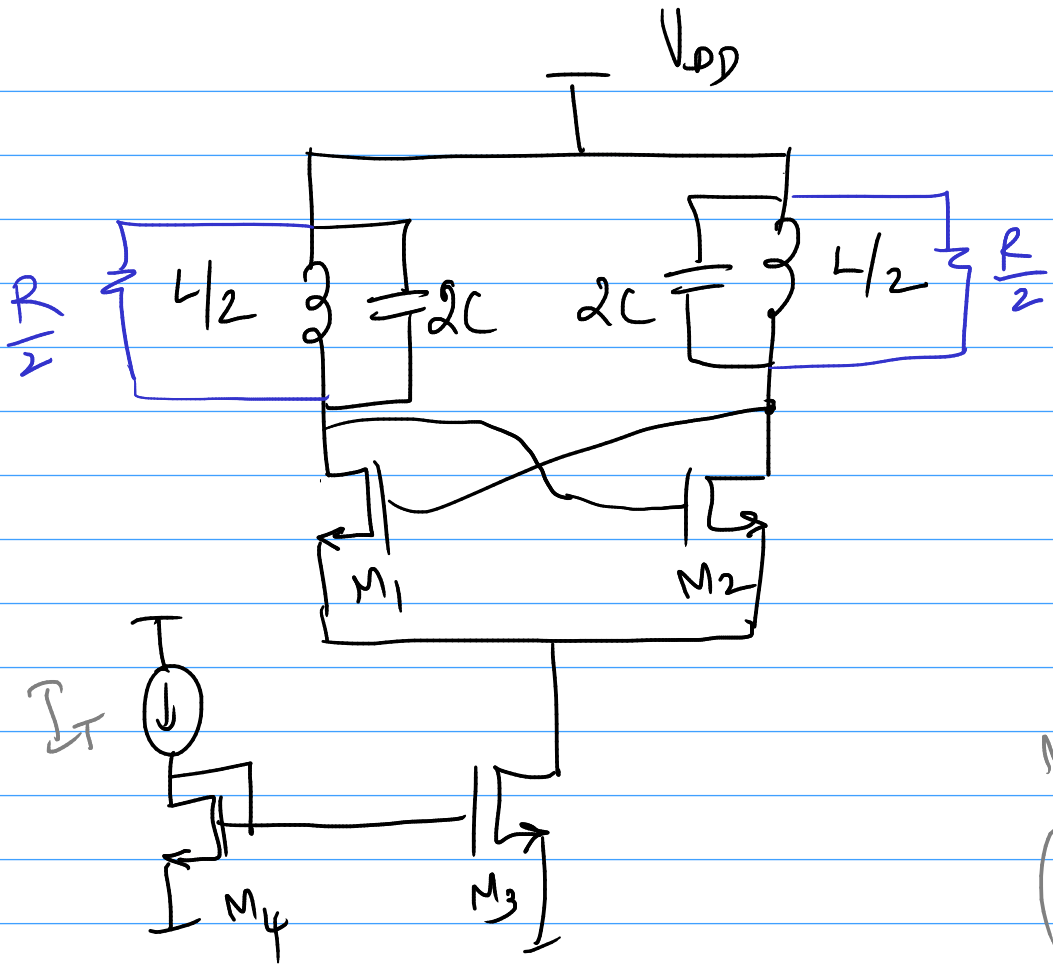


$$Q_L = \frac{R/2}{\omega_0 L/2} = \frac{R}{\omega_0 L}$$

$$R = \omega_0 L \cdot Q_L$$

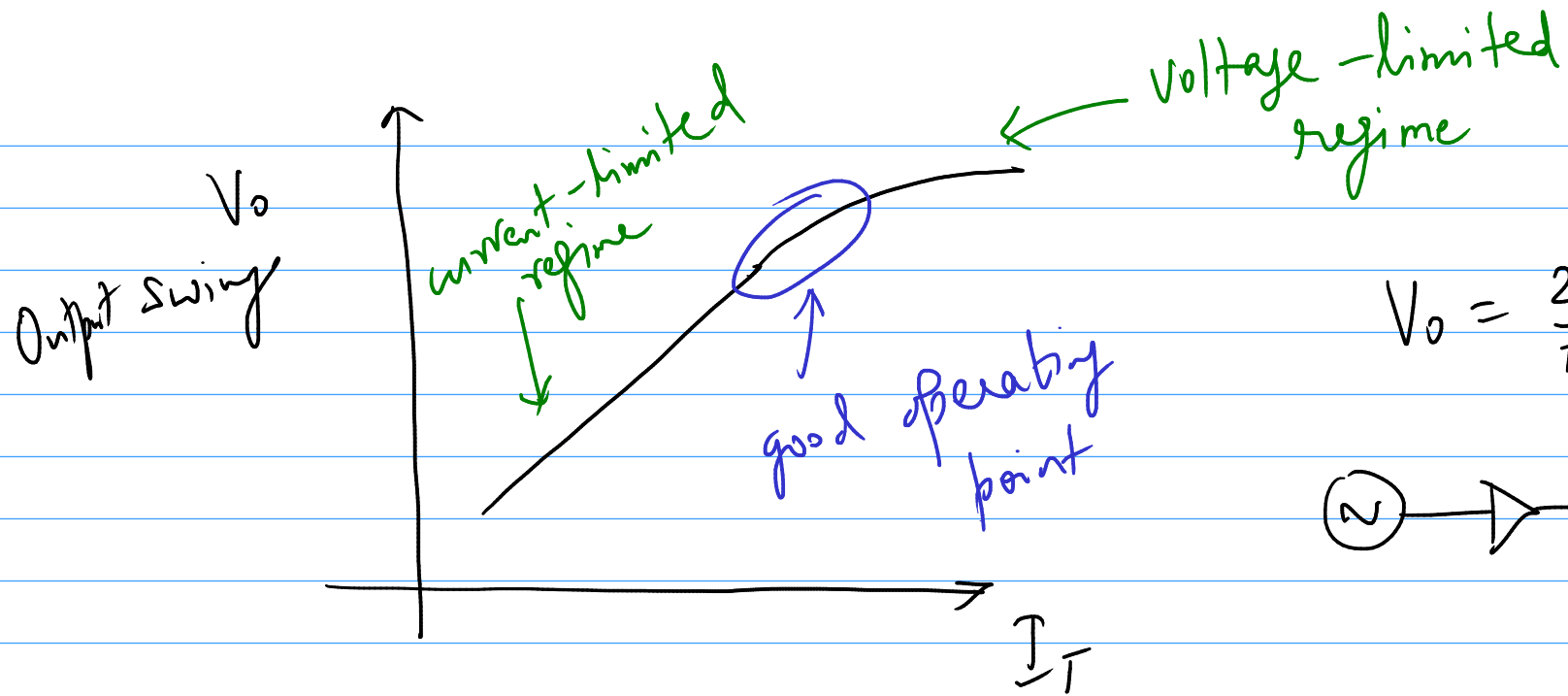maximise  $\rightarrow$  maximise  $Q_L$   
 maximise  $\rightarrow$  maximise  $L$   
 Max  $V_{sig}$  (P<sub>sig</sub>) for a given  $I_T$   
 Best PN



$$V_o = \frac{2}{\pi} I_T \cdot R$$

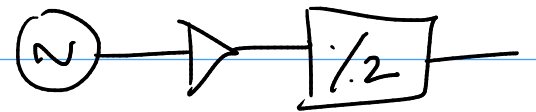


Max  $I_T \rightarrow \left(\frac{W}{L}\right)_{1/2}$  for startup gain of 2-3  
(P<sub>diss.</sub>)

choose  $C \leftarrow \omega_0 = \frac{1}{\sqrt{LC}} \leftarrow$  optimise for P<sub>N</sub>.

# CMOS Power Amplifiers

→ Driver Amplifiers

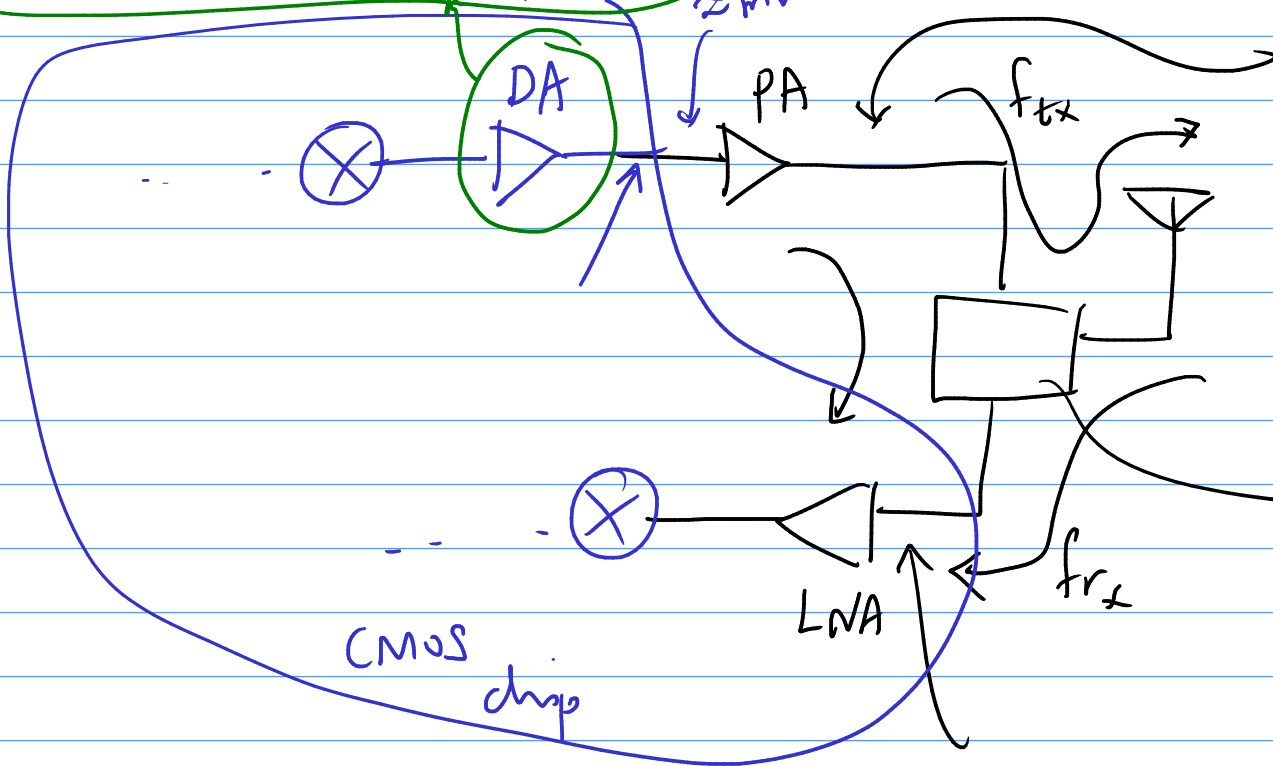



Cellular system > 1W


WiFi  $\approx$  100mW

Bluetooth < 10mW ✓


Diplexer / Switch / Duplexer



$\approx$  -100dBm

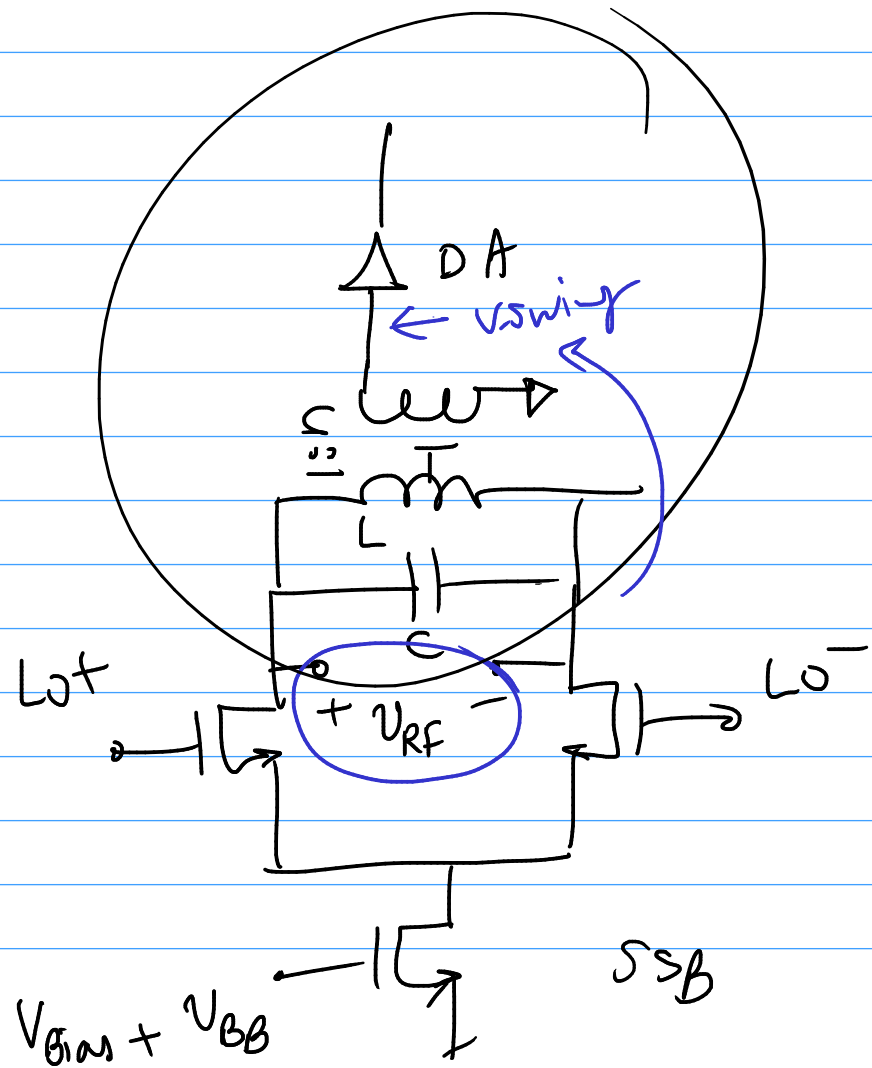
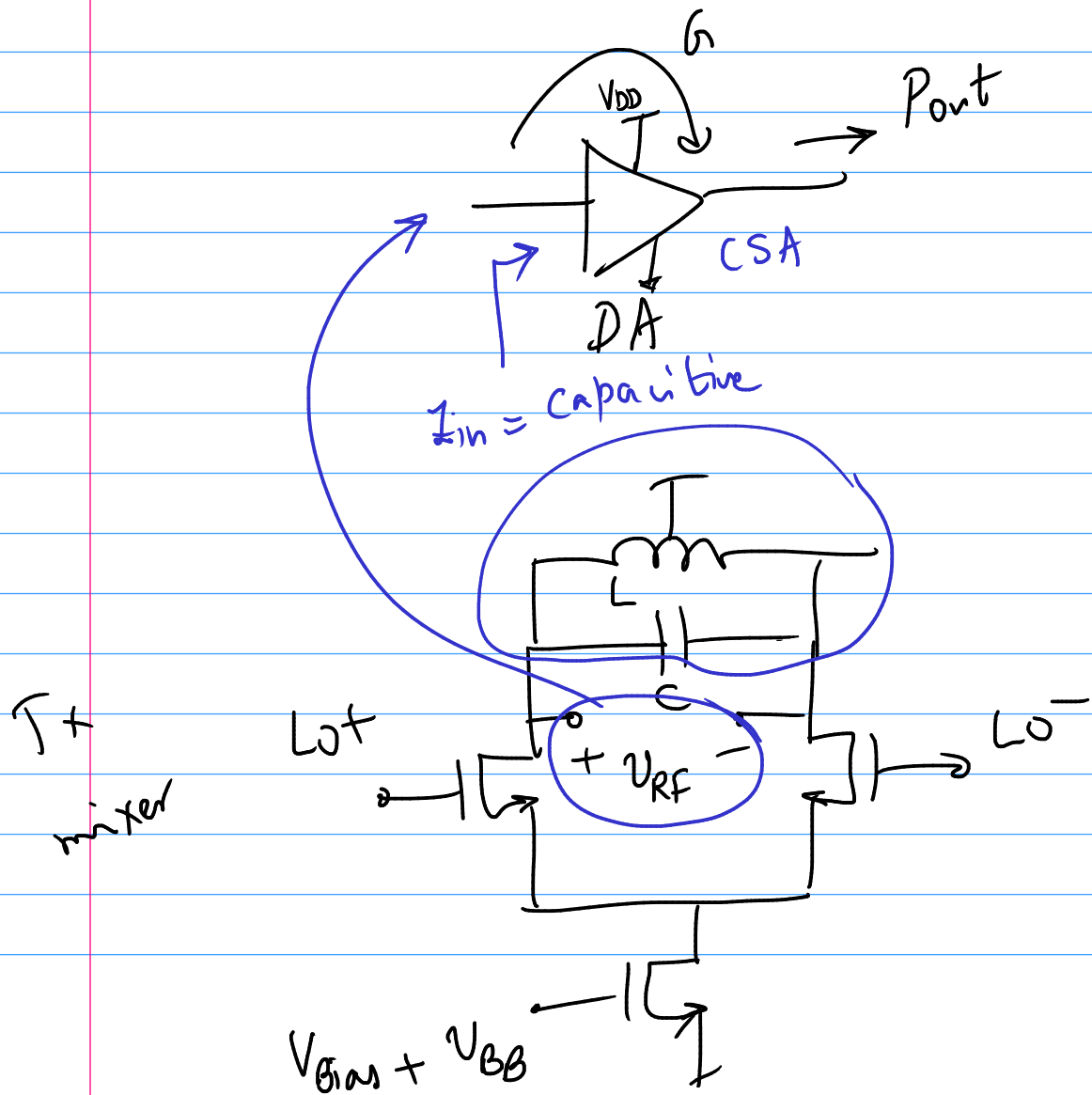



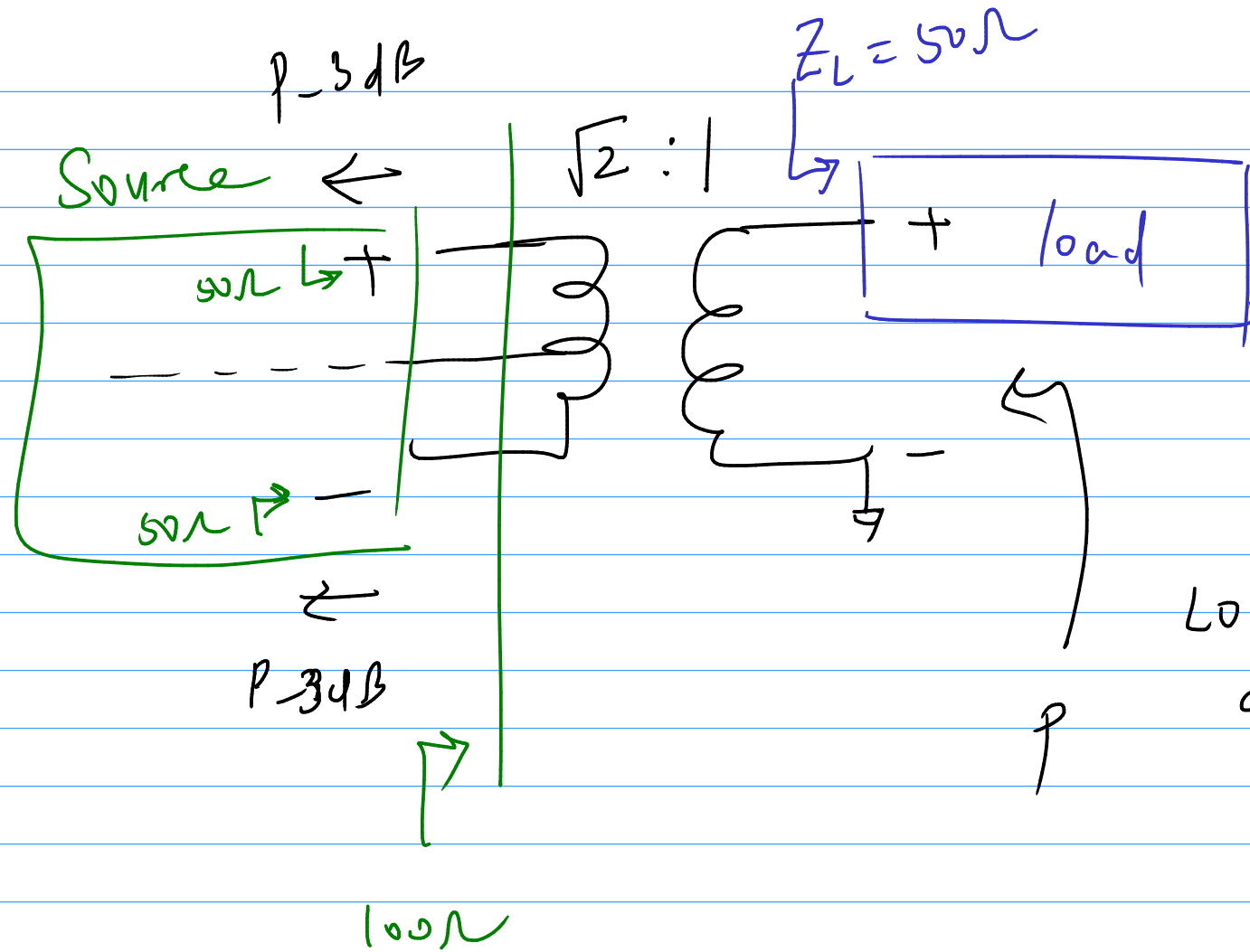



Balun unbalanced  
 Balanced

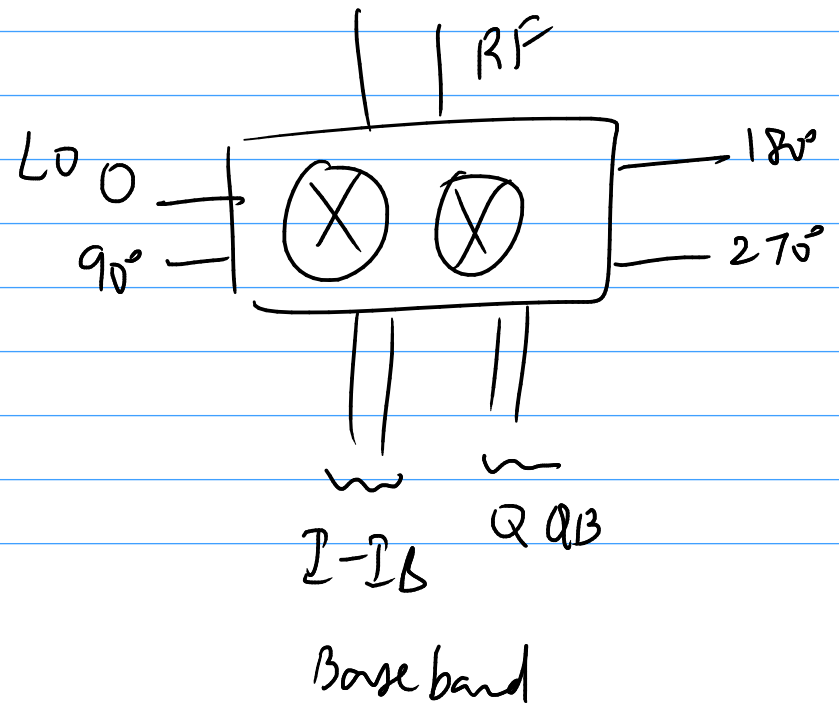


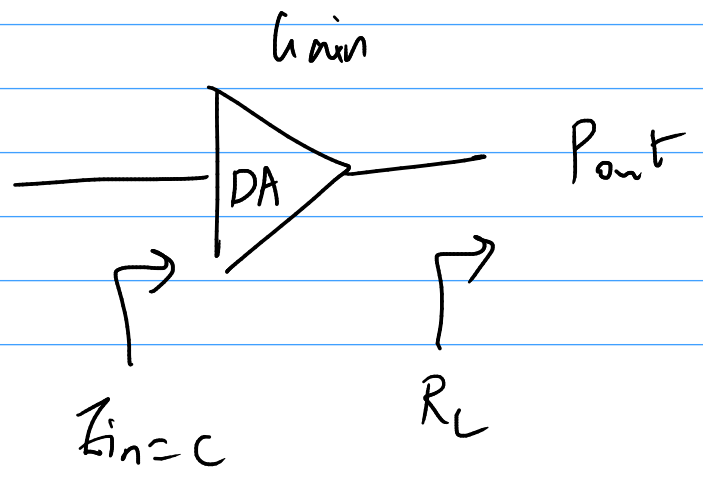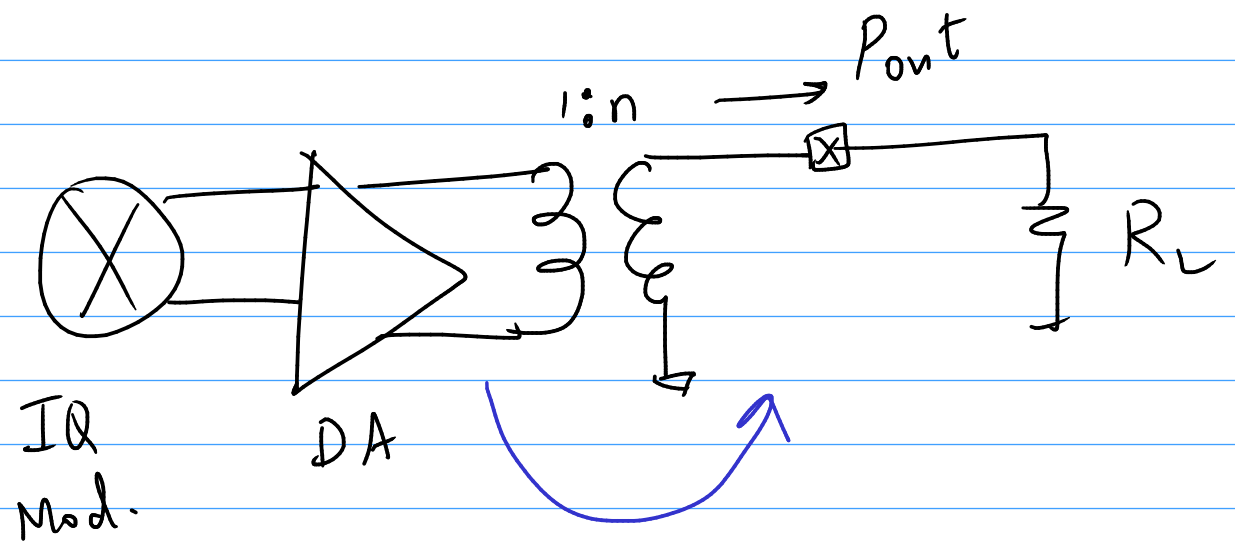

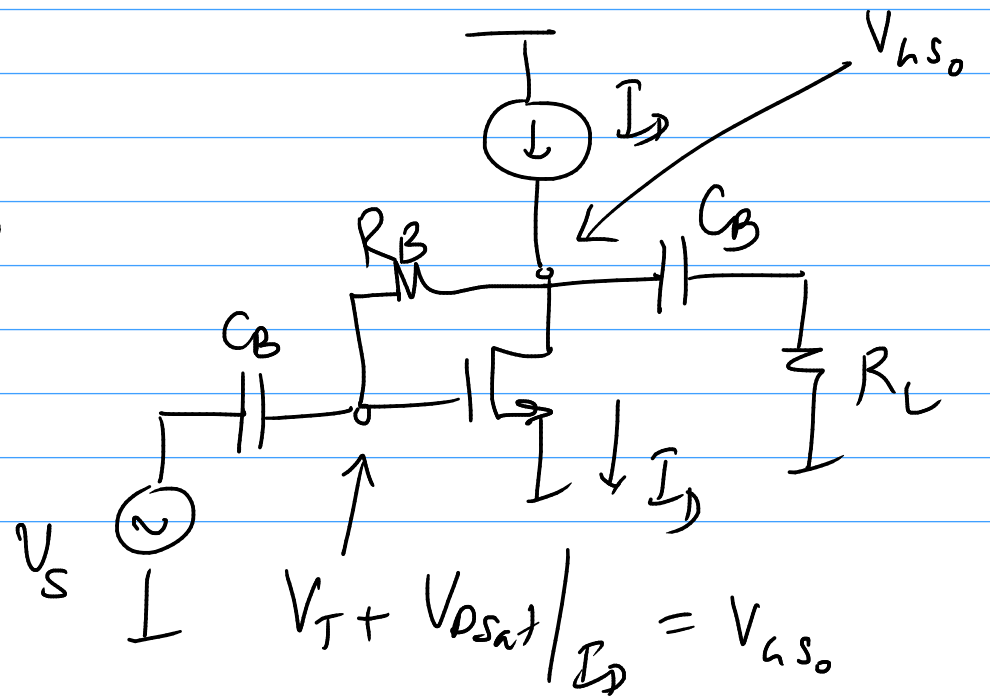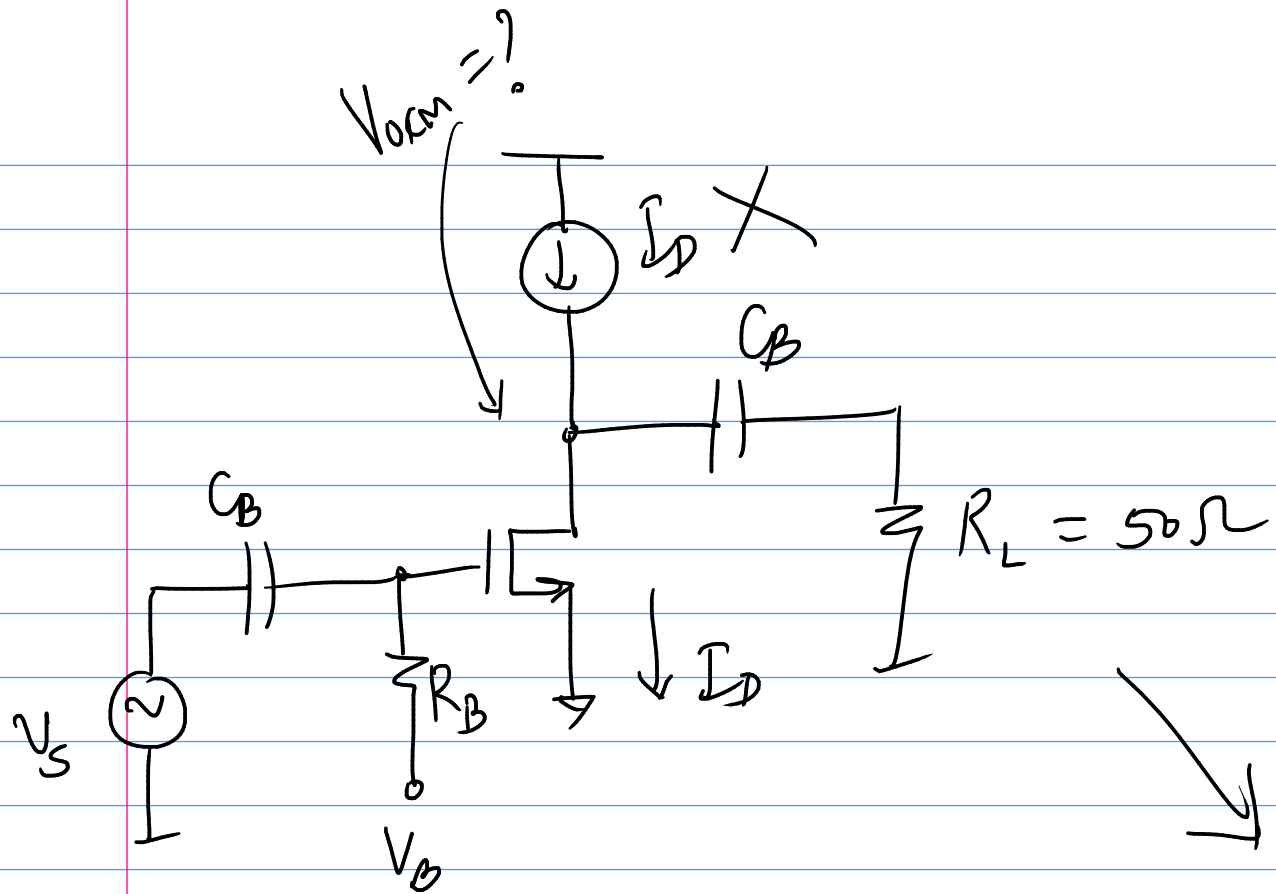

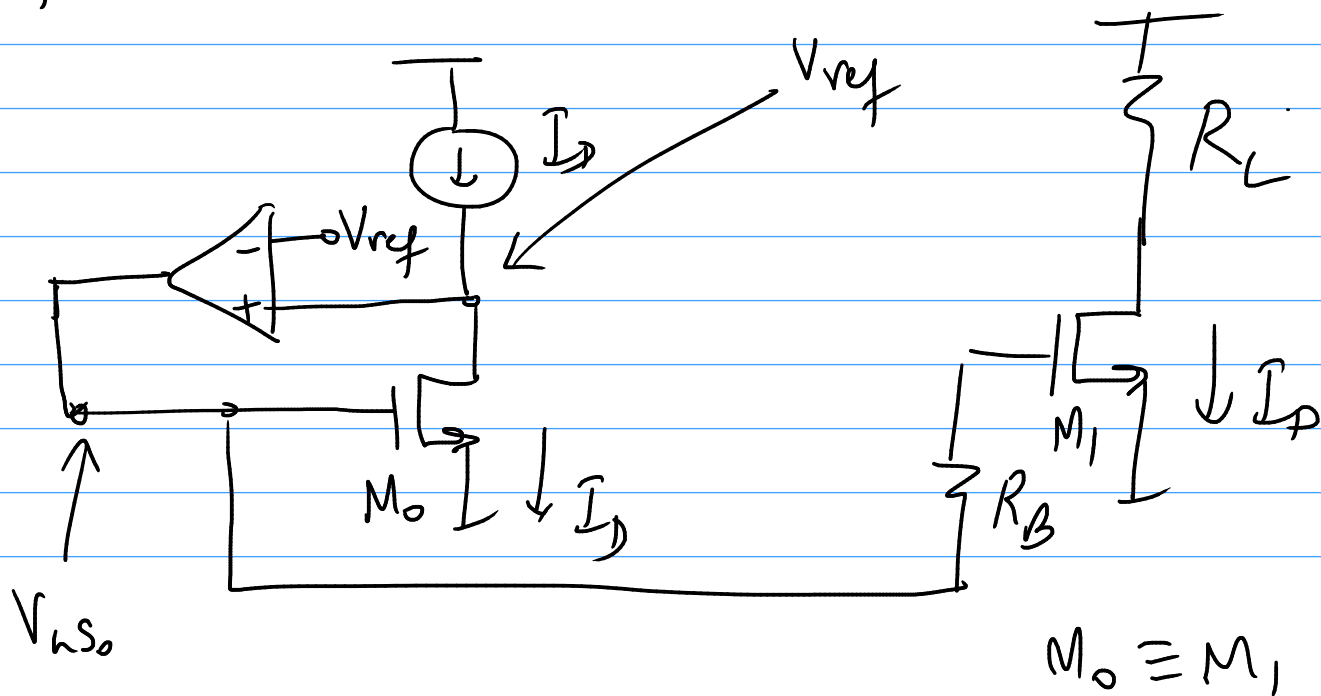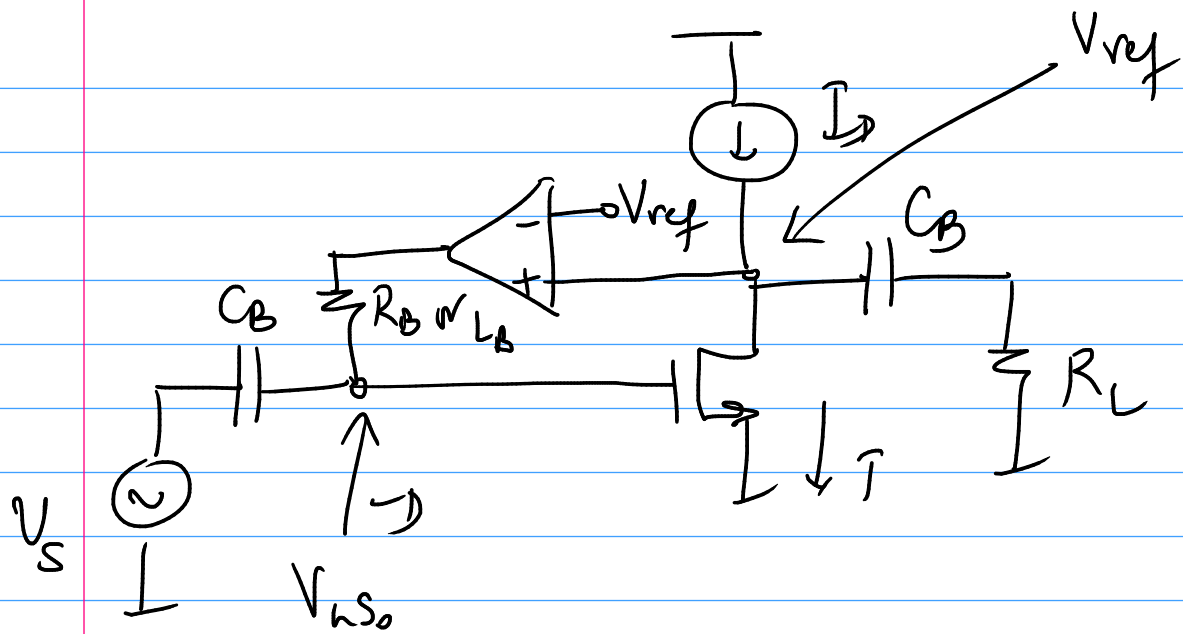

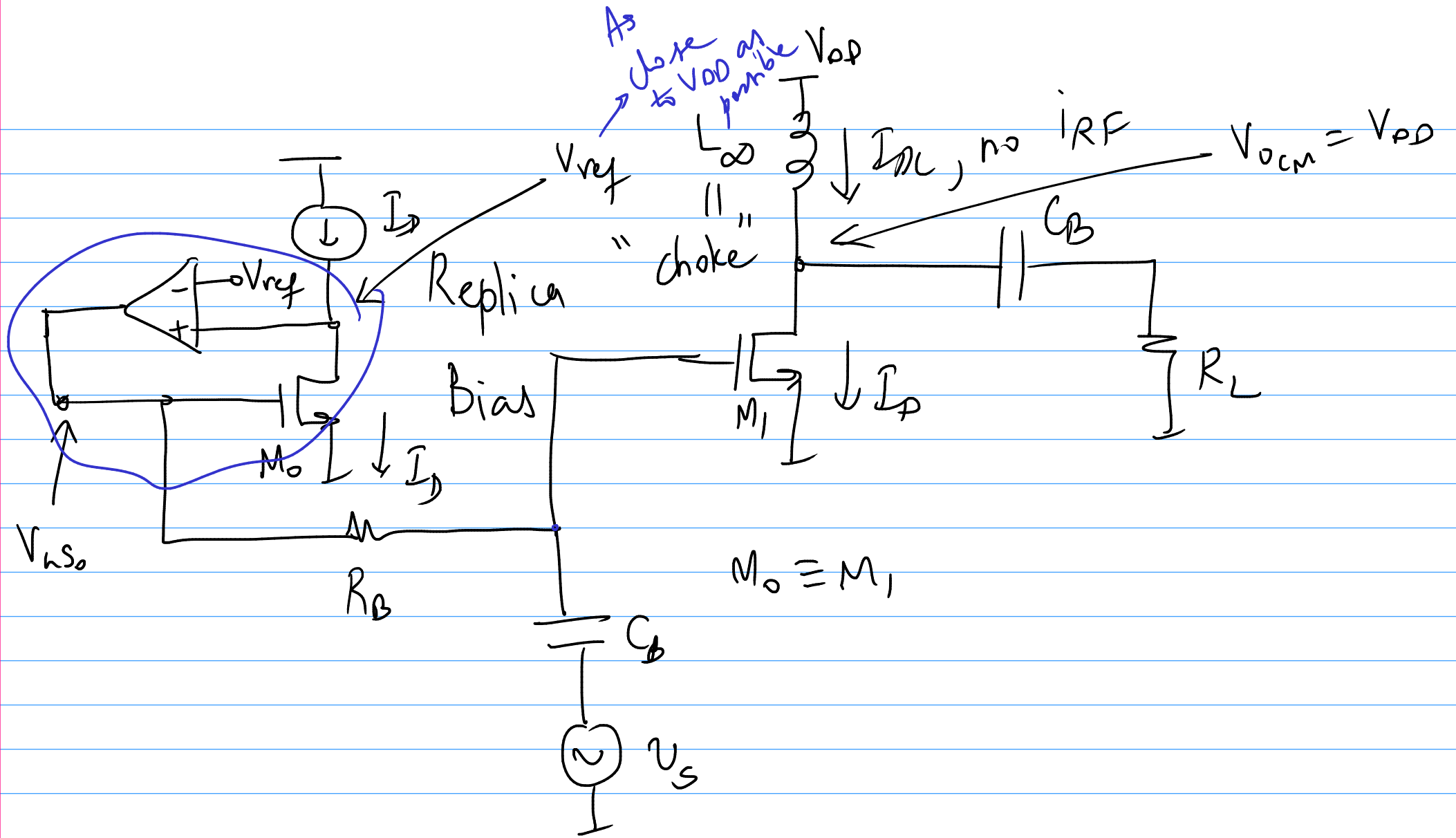

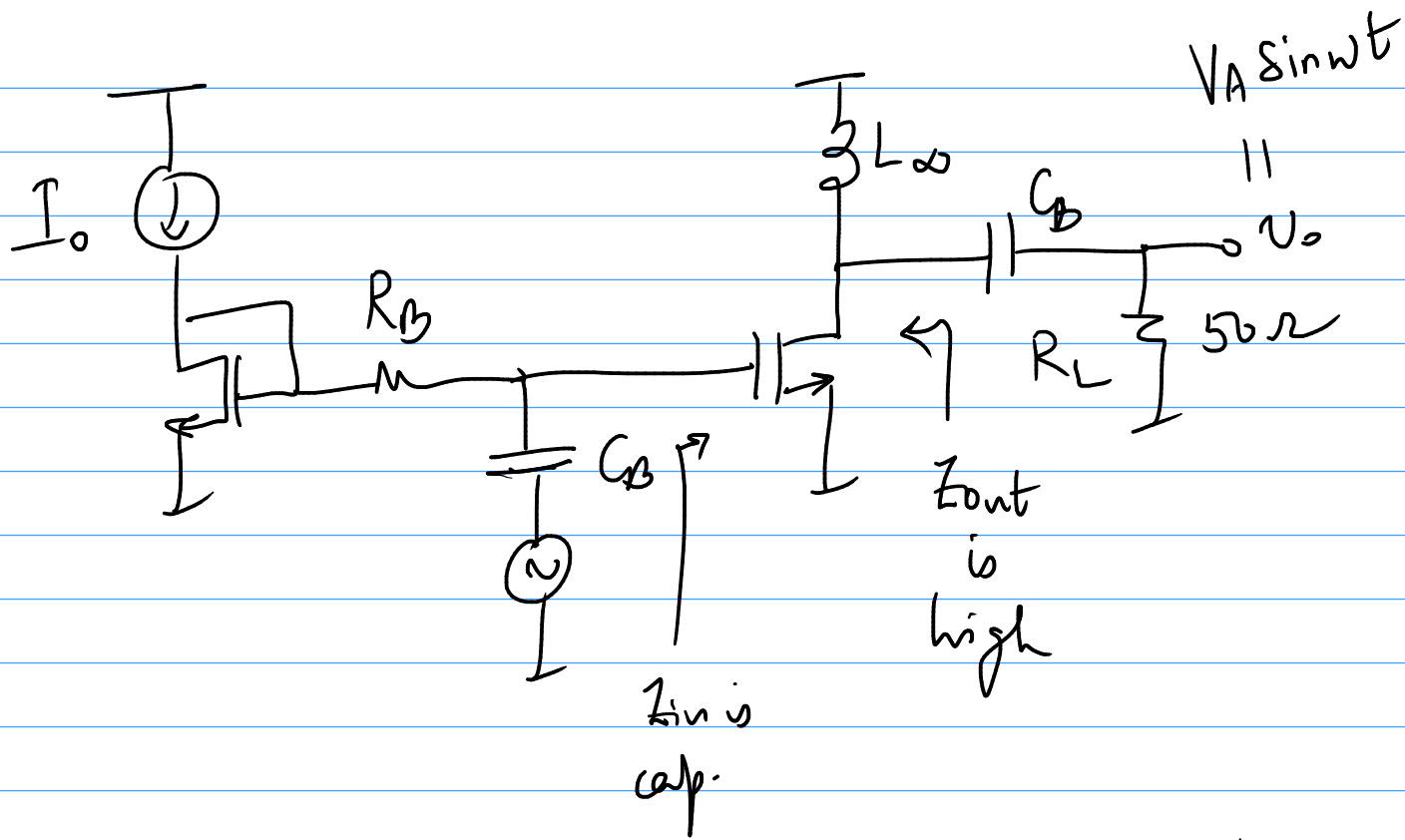

$$A_{gain} = -g_m \cdot R_L$$

$$P_{out} = \frac{(V_A / \sqrt{2})^2}{R_L}$$


$$= \frac{V_A^2}{2R_L}$$

$$= \frac{V_A^2}{100}$$

We want


|             |     |      |
|-------------|-----|------|
| $P_{out} =$ | 1W  | 10mV |
| $V_A =$     | 10V | 1V   |

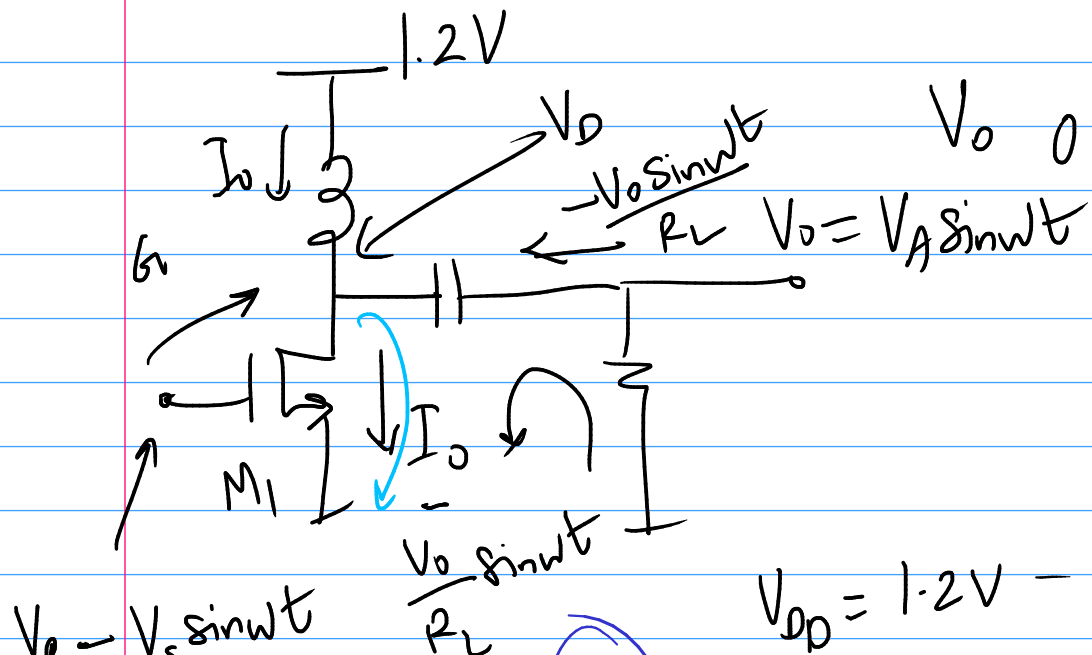
$$P_{out} = 10\text{mW} \Rightarrow V_A = 1\text{V}$$



$$V_A = V_B + V_S = V_B + \frac{V_A}{\beta}$$

$$V_D = V_{DD} - V_A$$

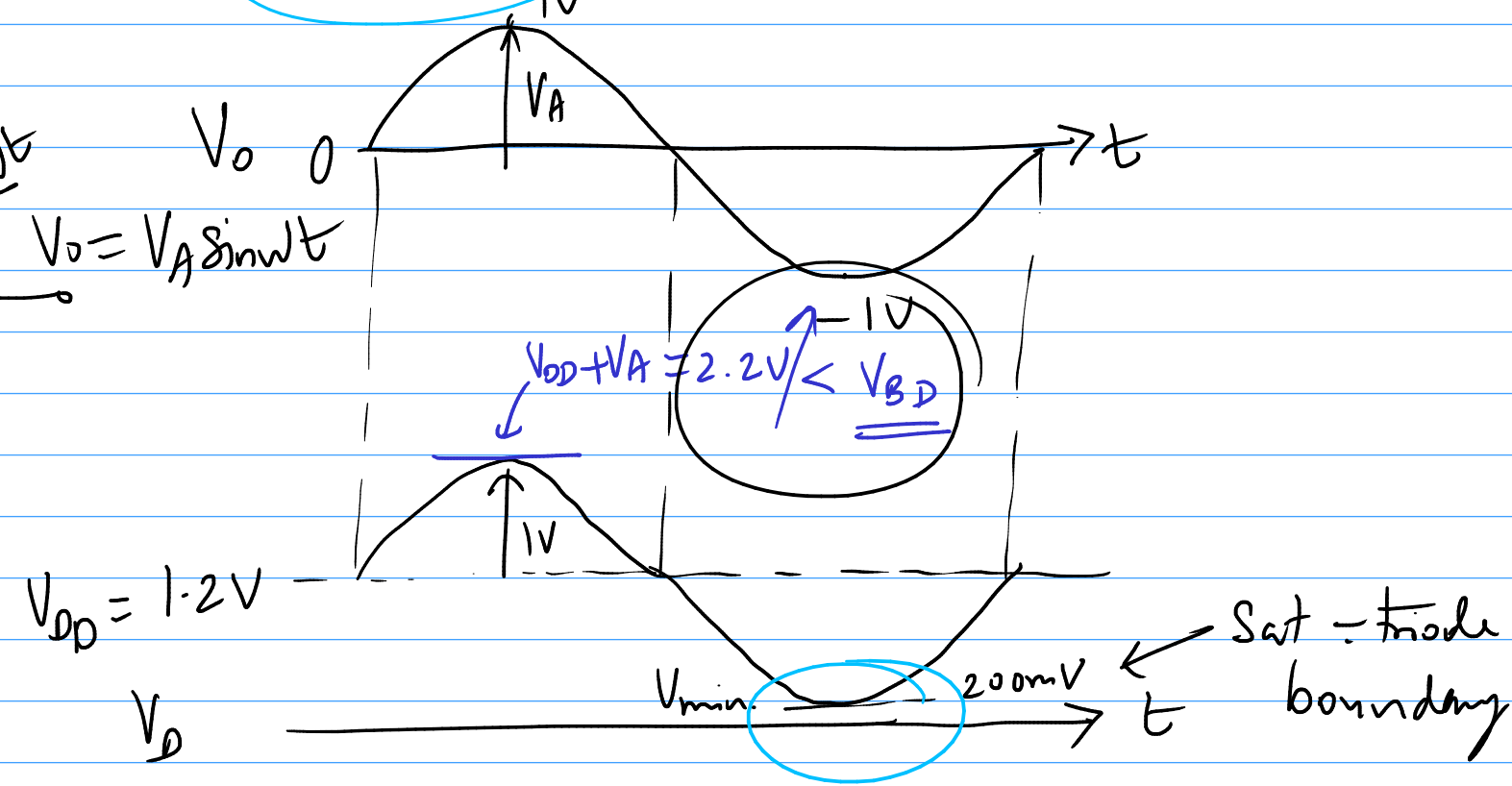

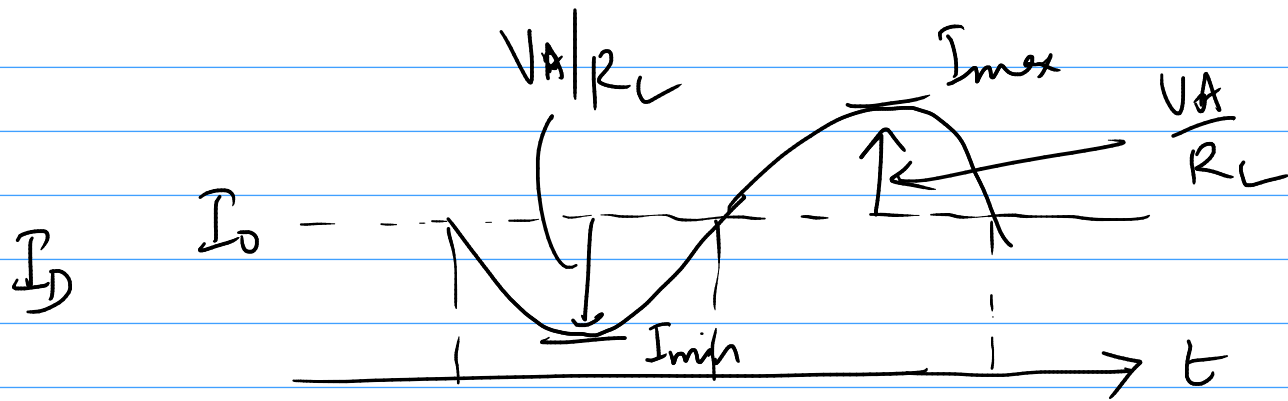

No  
Cut-off





$$\frac{V_A}{R_L} \leq I_0$$

large gain  $\rightarrow$   $V_{min} \approx V_{sat1}$   
 $V_A = I_0 R_L$

$$V_{sat} = \sqrt{\frac{2I_0}{\mu C_{ox} \left(\frac{W}{L}\right)}}$$

e.g.  $V_A = 1V \Rightarrow I_0 = 20\mu A$

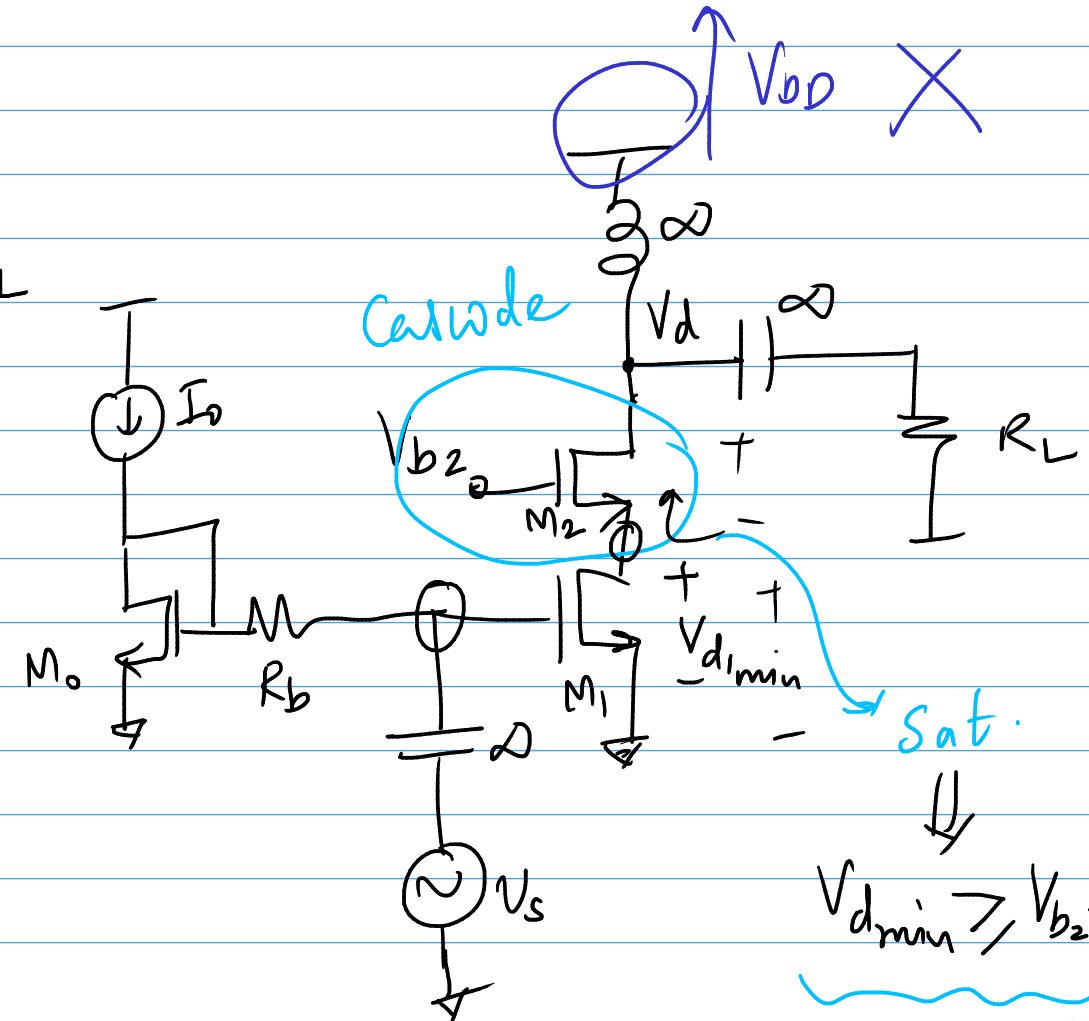
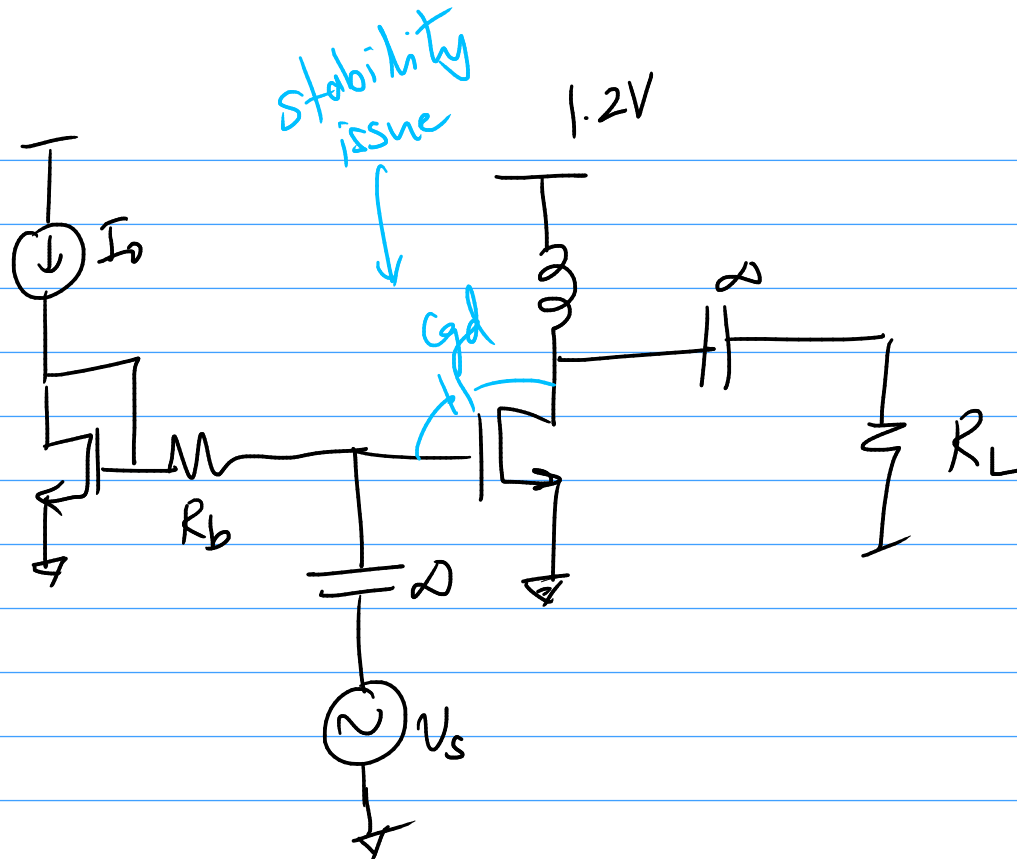
$$V_{sat} = 0.2V \Rightarrow \left(\frac{W}{L}\right) = \frac{2I_0}{\mu C_{ox} \cdot (V_{sat})^2}$$



min.  $V_{b2} = \underline{V_{d1, min}} + V_{GS2}$

$V_{d_{min}} \geq V_{b2} - V_{T2}$



may not meet  $V_o$  req.

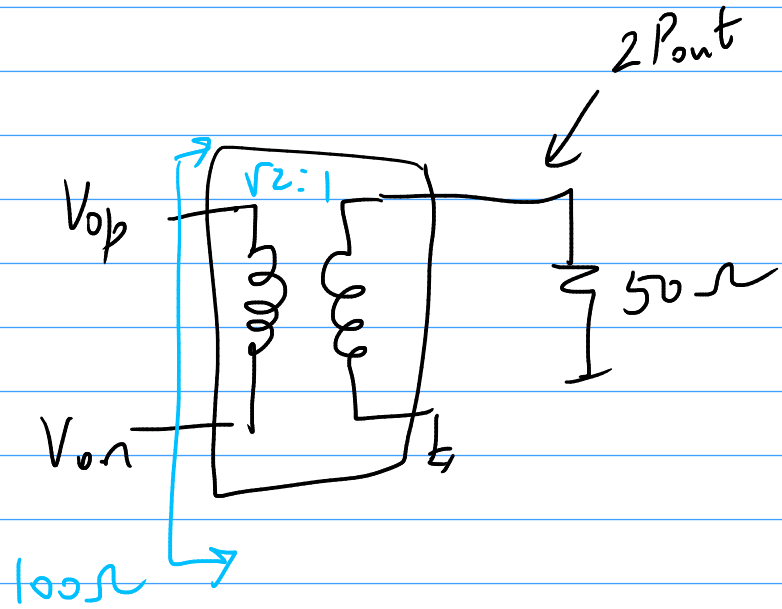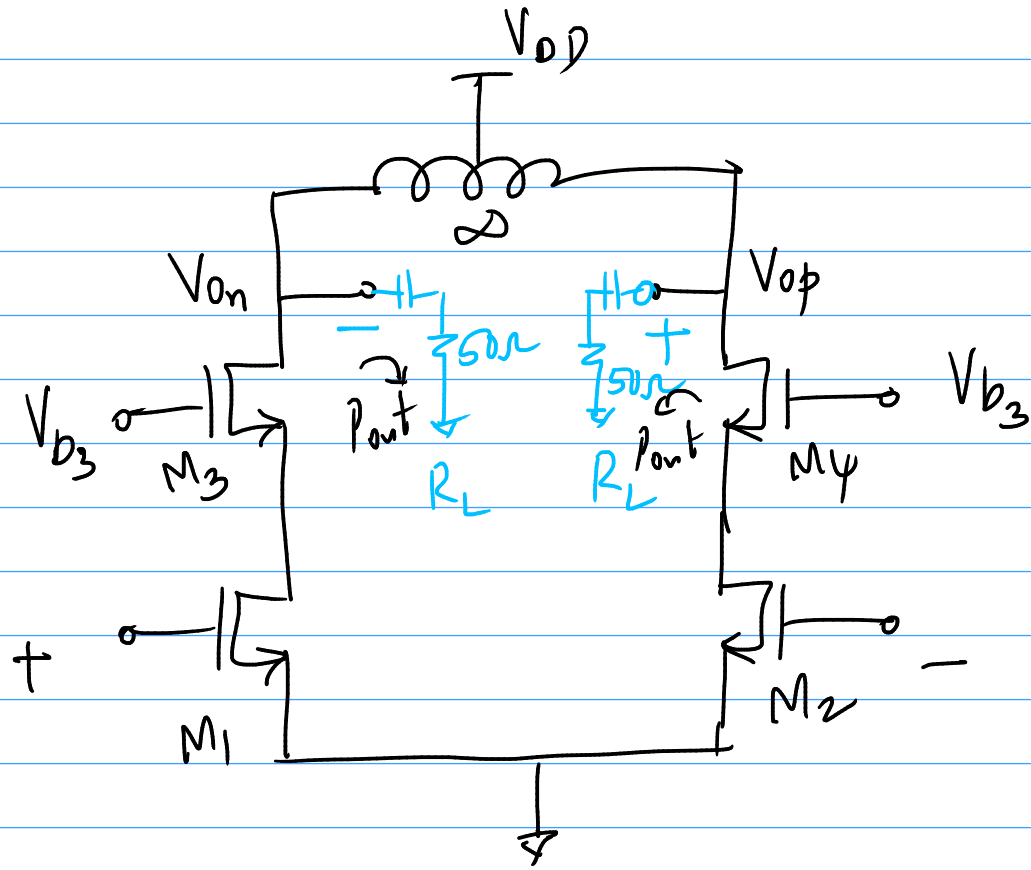

$$\begin{cases}
 P_{out} = 10\text{mW} \\
 P_{out} = \frac{(V_A \sqrt{2})^2}{50\Omega}
 \end{cases}$$

$\rightarrow V_A = 1\text{V}$


$\rightarrow R_L < 50\Omega$

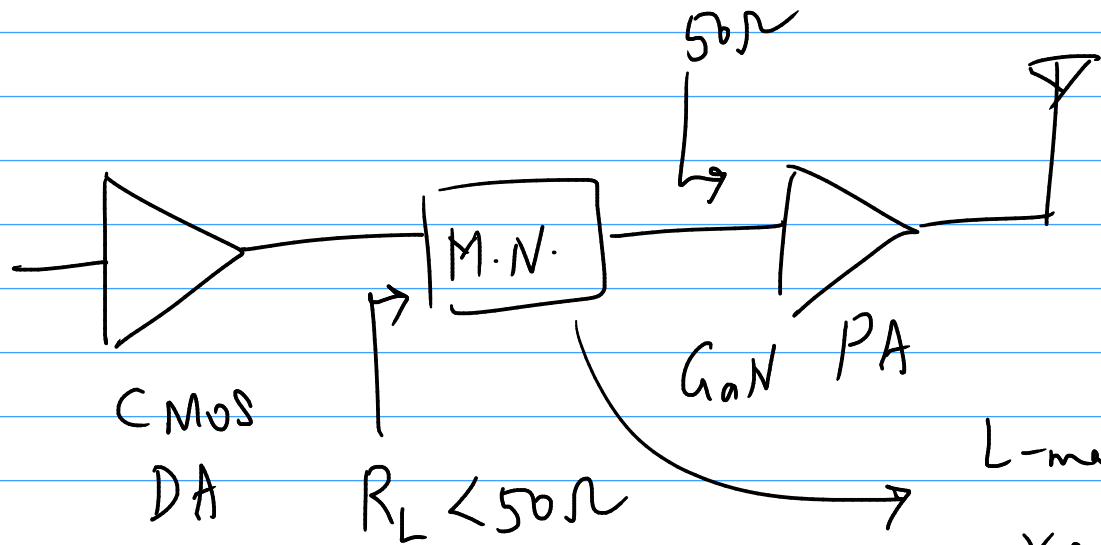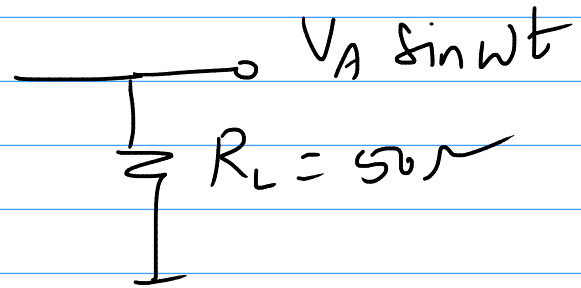



L-match,  $\Pi$ , T, Tapped  $\pi$ , -L  
 Xform ...




Say  $V_A = 0.5V$  allowed  $V_{DD} = 1.7V$



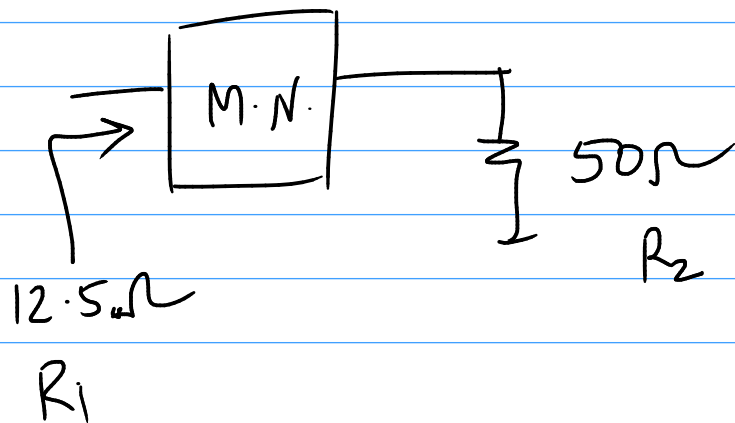
$$\frac{(0.5/\sqrt{2})^2}{R_L} = 10\text{mW} \Rightarrow R_L = 12.5\Omega$$




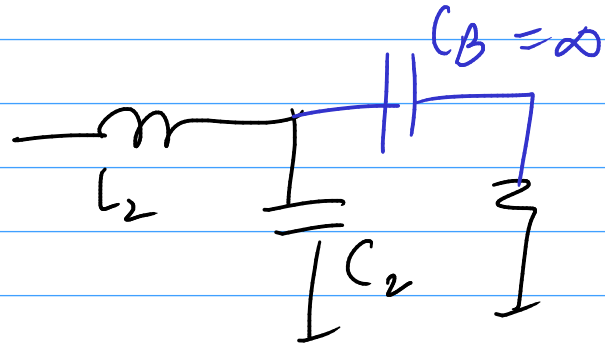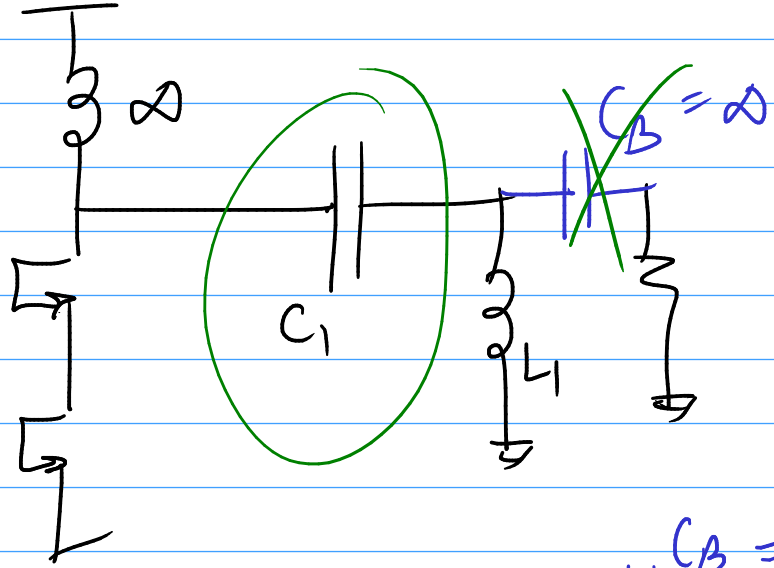$L \rightarrow$  match  $Q = \sqrt{\frac{R_2}{R_1} - 1} = \sqrt{3}$



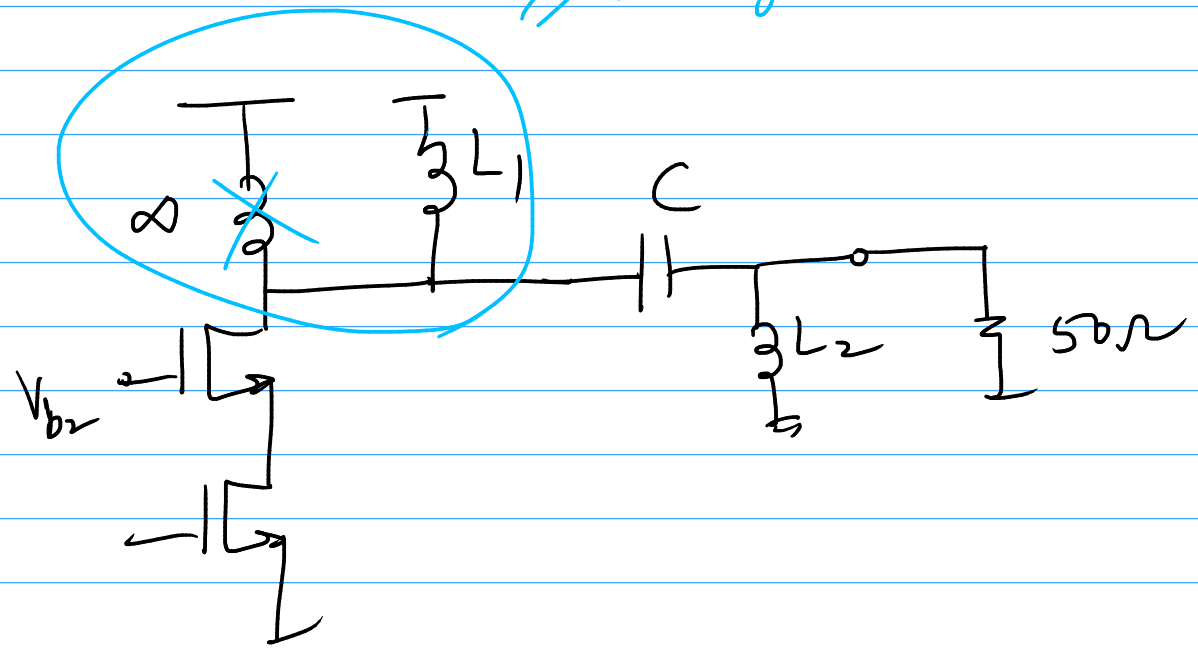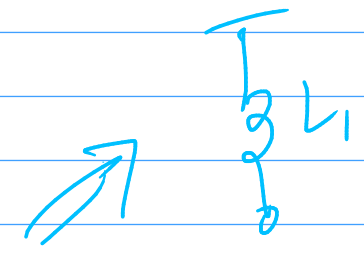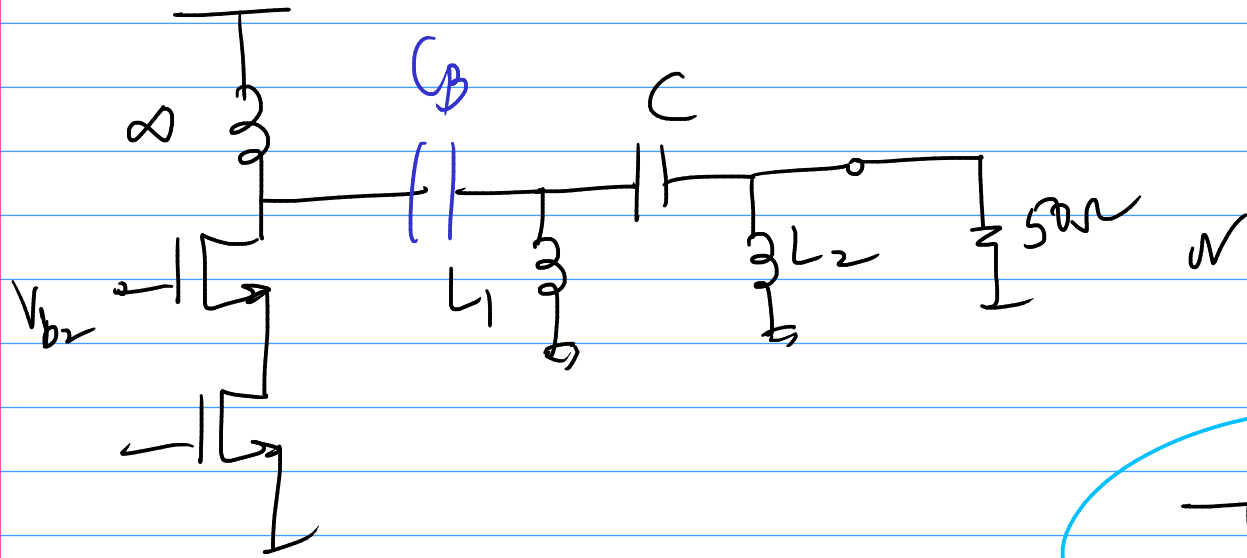


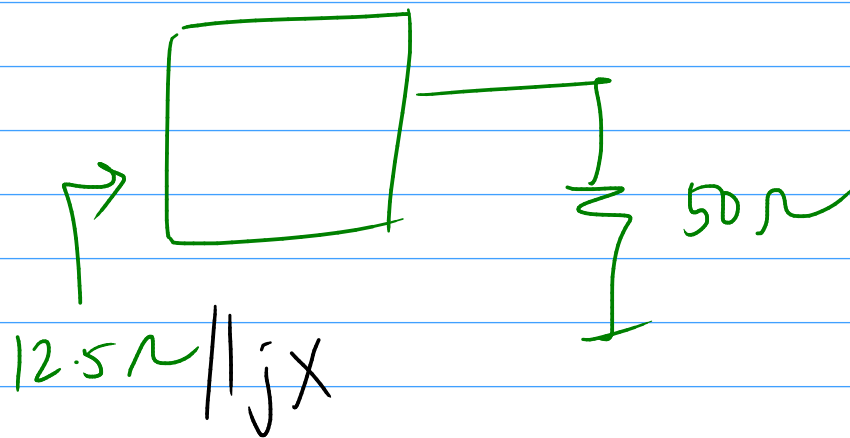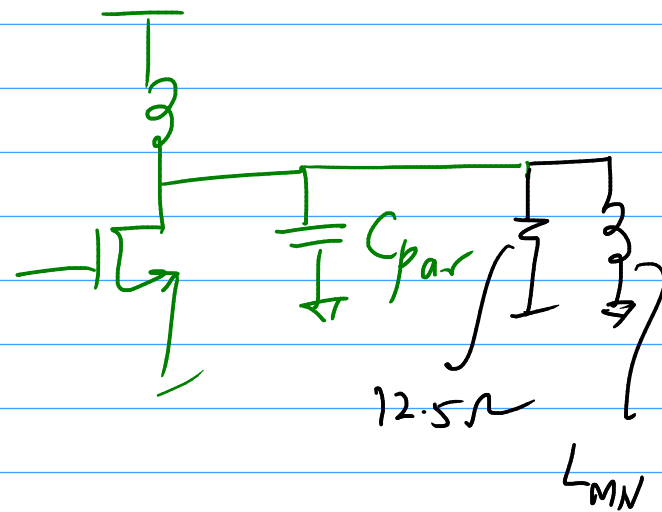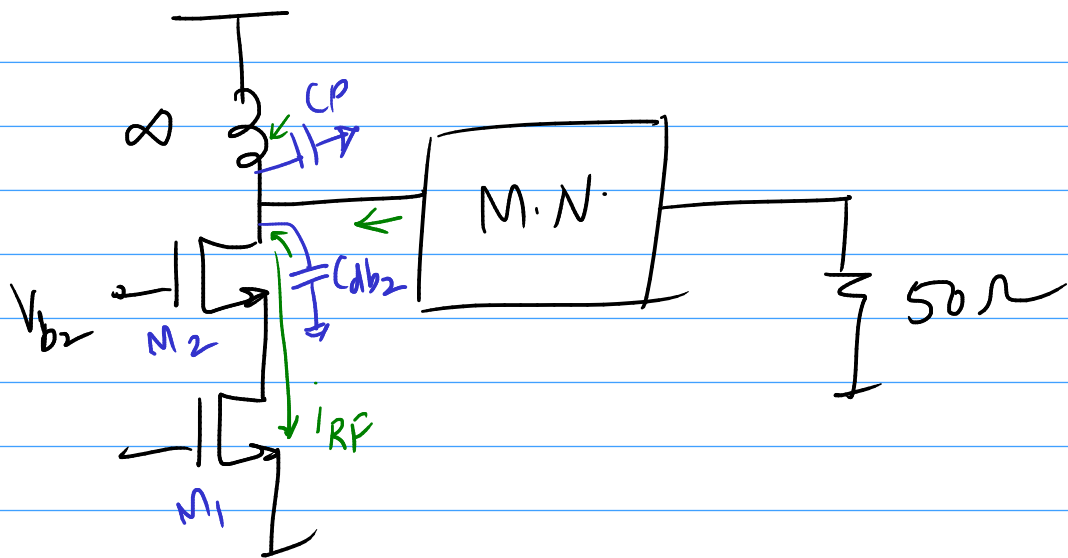

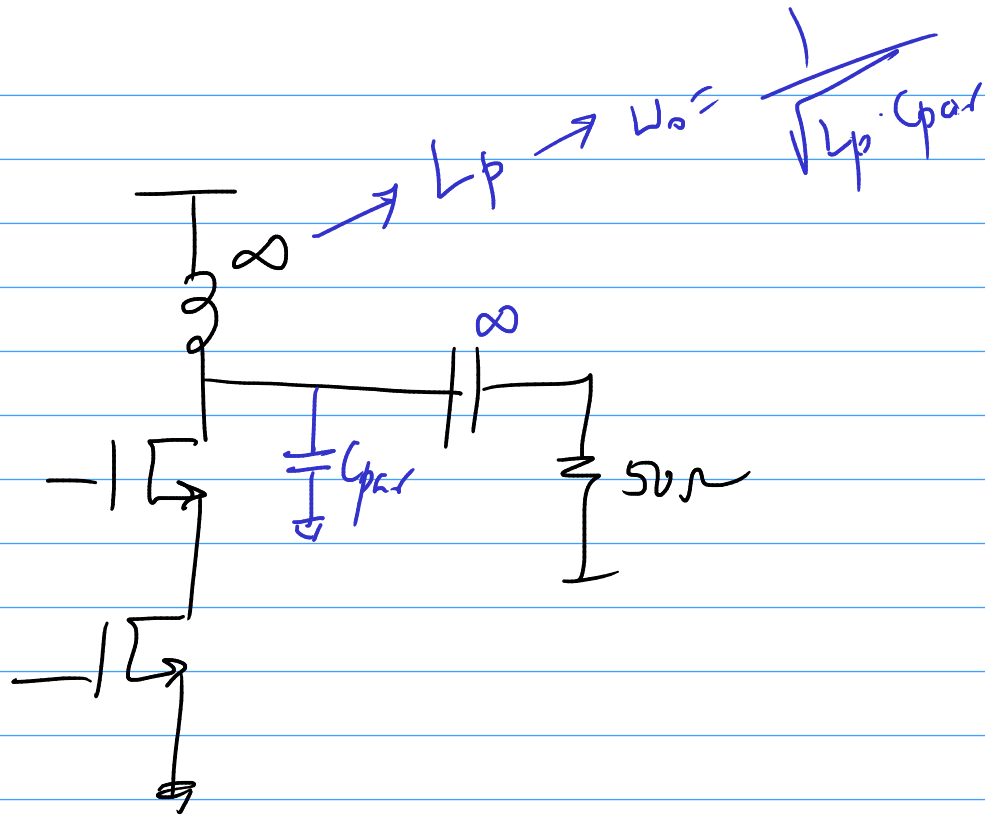


Linear (class-A)

PA

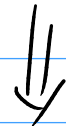

device is always  
in sat.


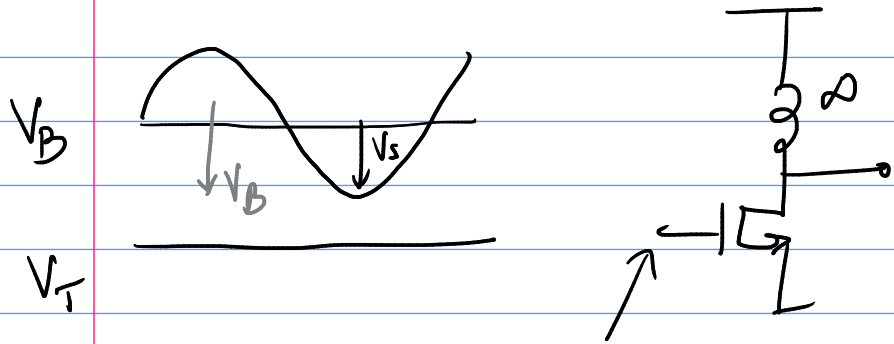


$$V_B + V_s \sin \omega t$$

$$V_B + V_s \sin \omega t \geq V_T$$




class-A



Conduction angle =  $360^\circ$

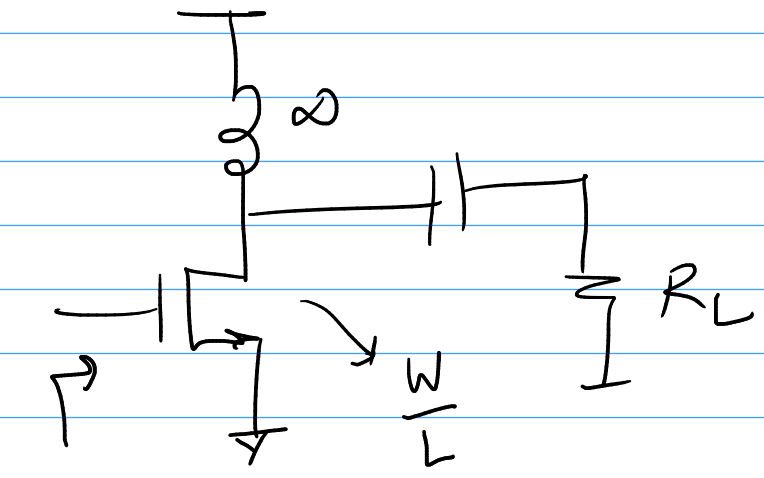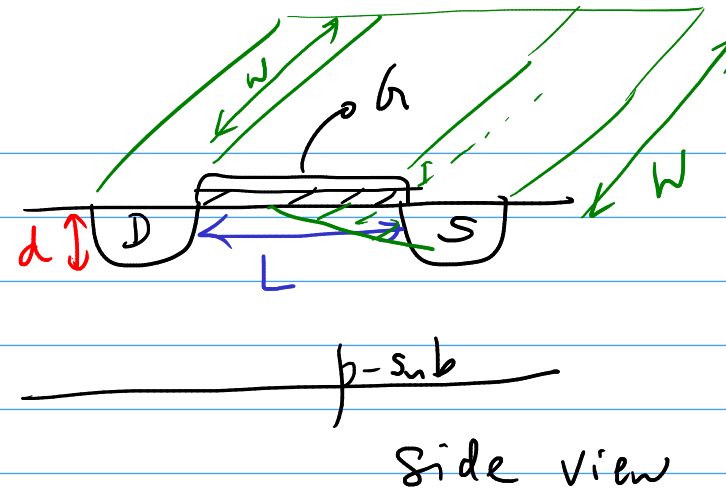

$$Z_{in} = \frac{1}{j\omega C_{gs}}$$

$\frac{W}{L} \times R_{sheet, poly}$

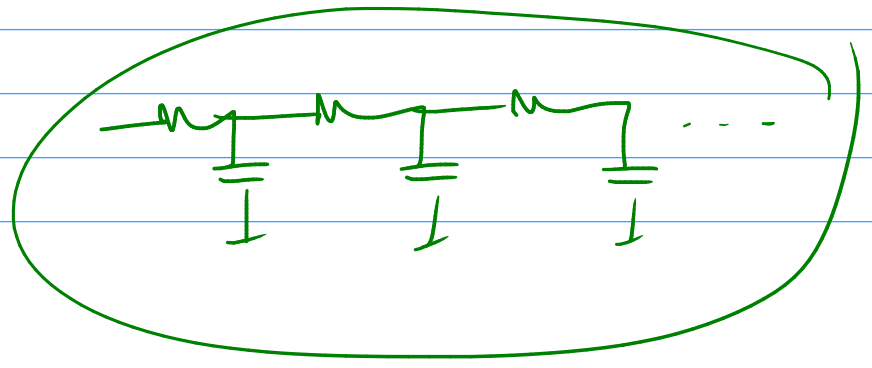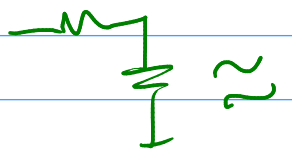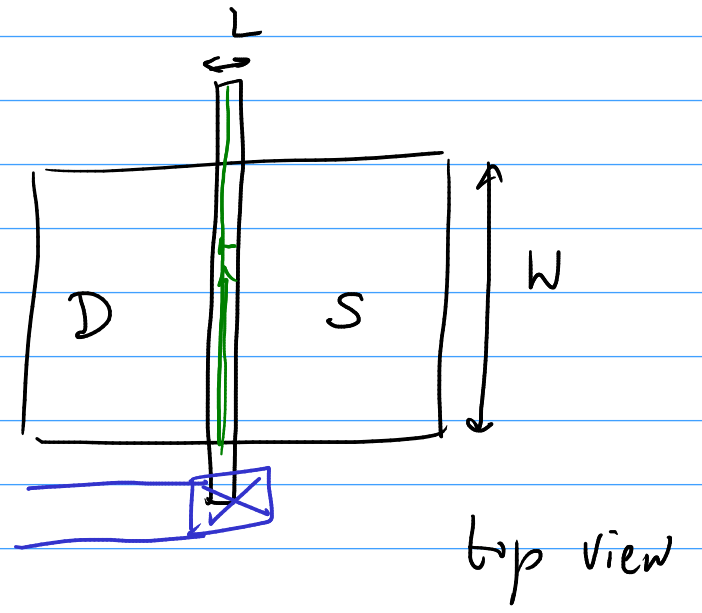

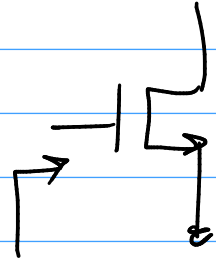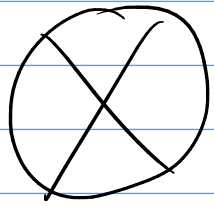



$$Z_{in} = R_g + \frac{1}{j\omega C_{gs}}$$

$$Y_{in} = G_g + j\omega C_{gs}$$

Voltage gain  $\leftrightarrow$


Power Gain  
 $G_{Av}$ ,  $G_{AN}$

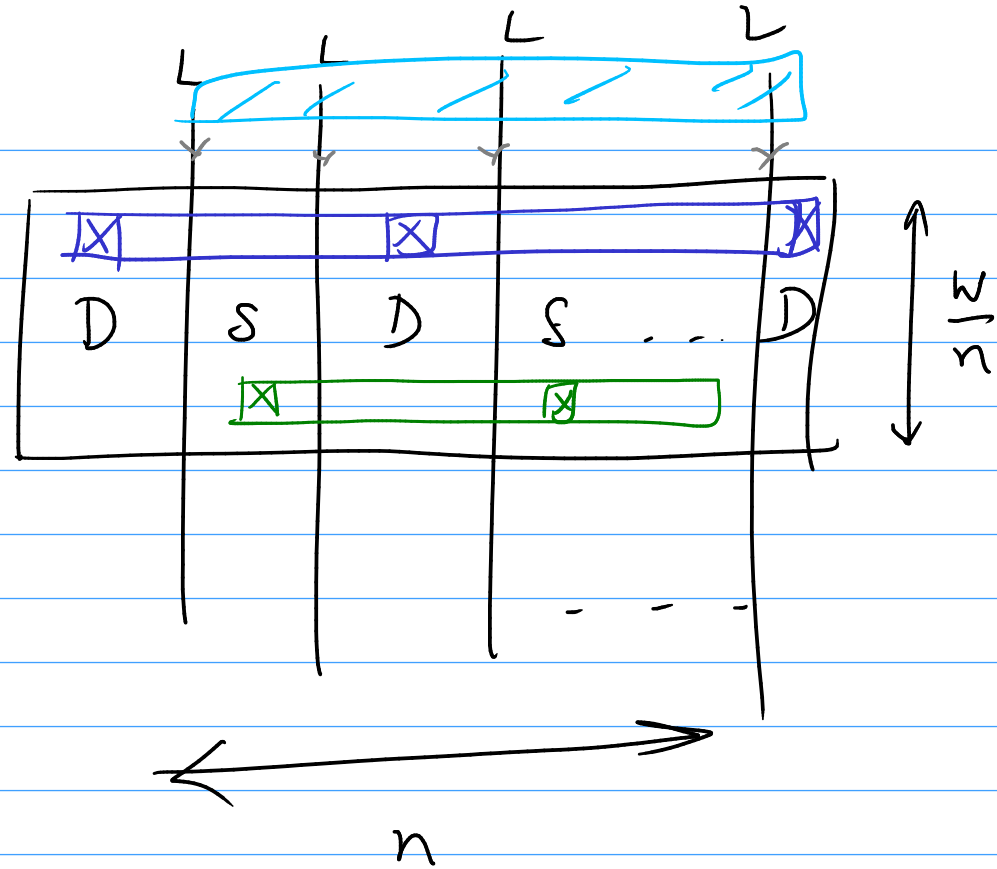

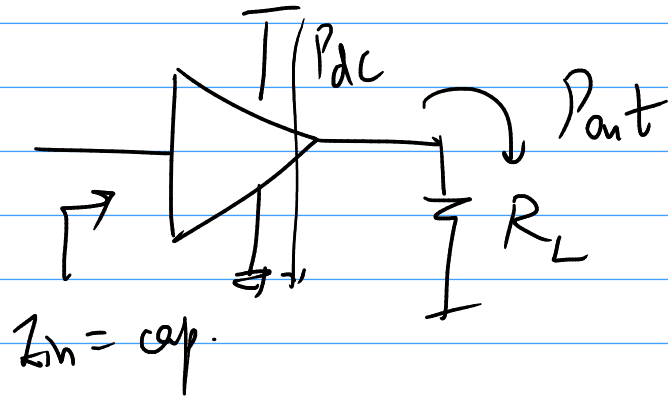




"Drain efficiency"




$$\eta_d = \frac{P_{out}}{P_{dc}}$$


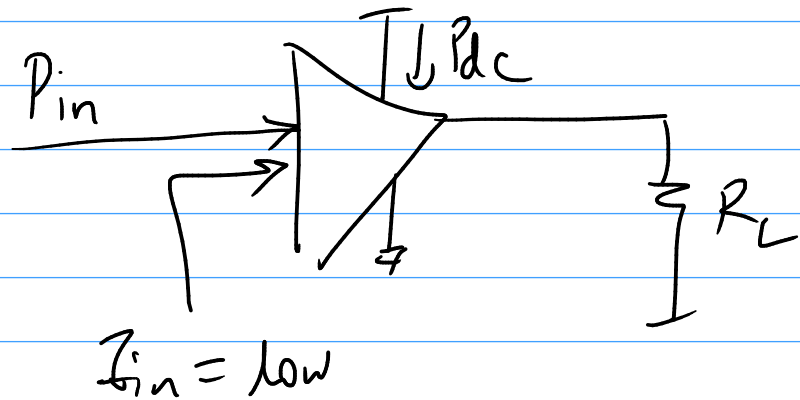


"power added efficiency"

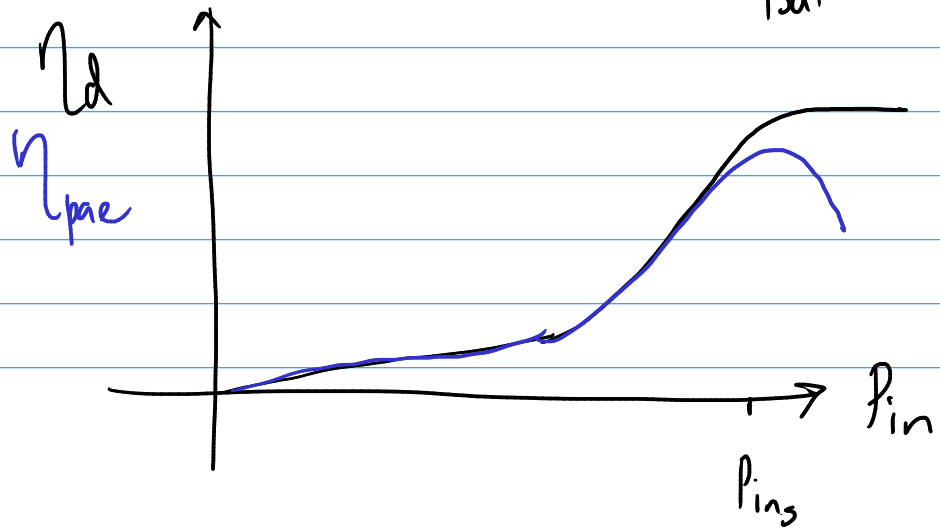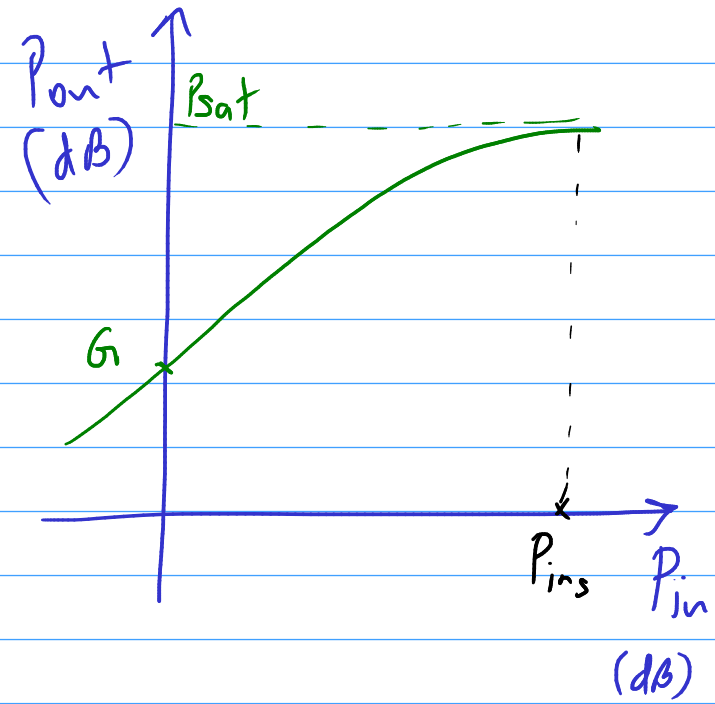
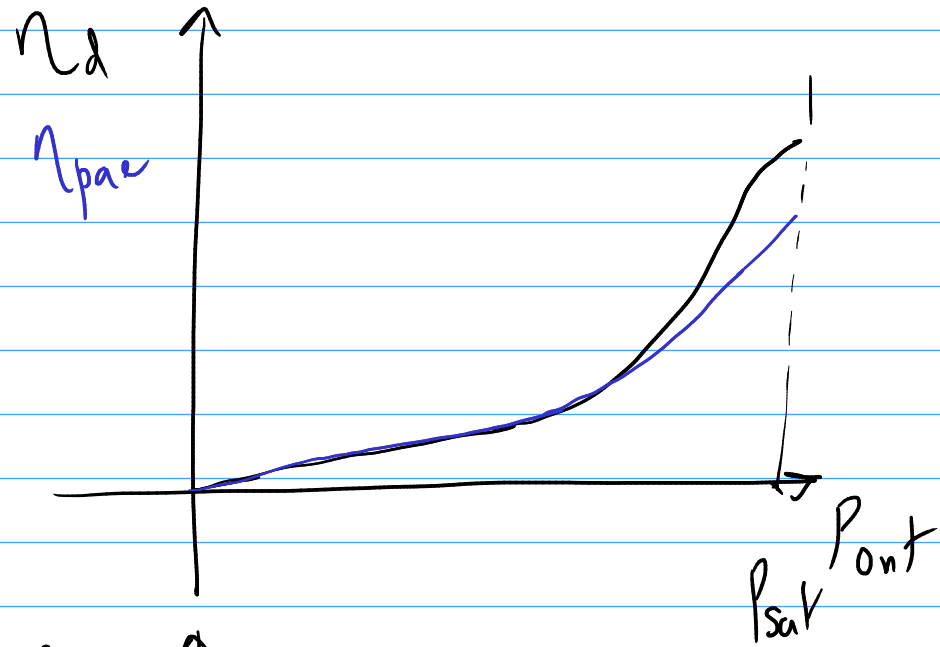
$$\eta_{pae} = \frac{P_{out}}{P_{in} + P_{dc}}$$



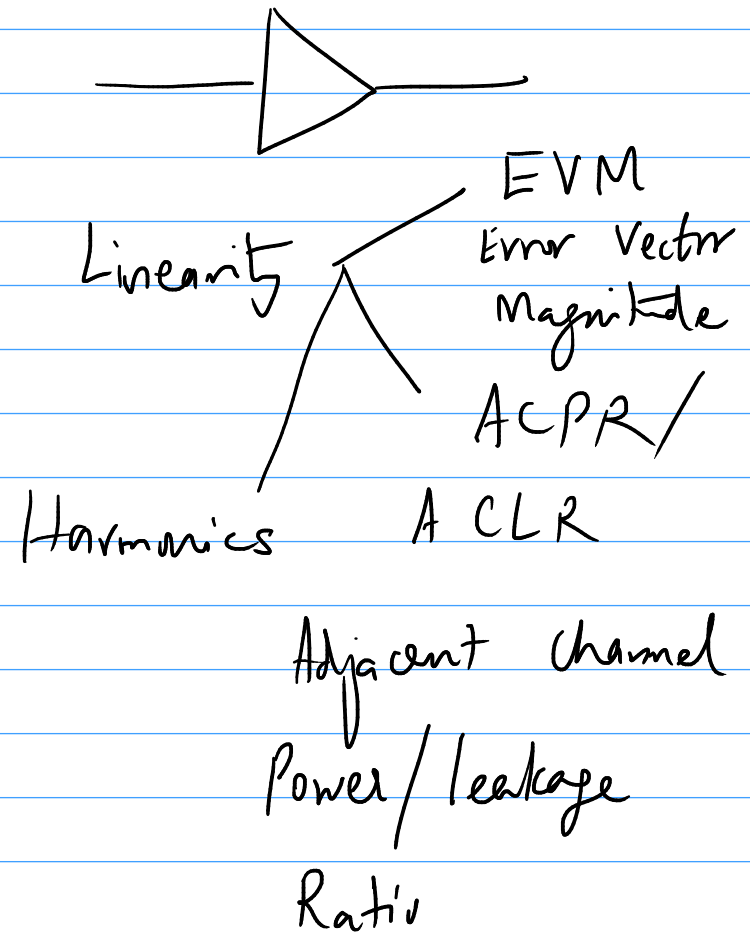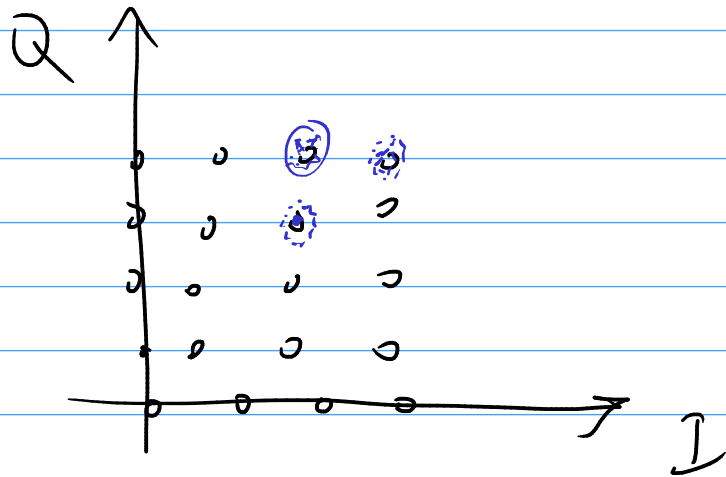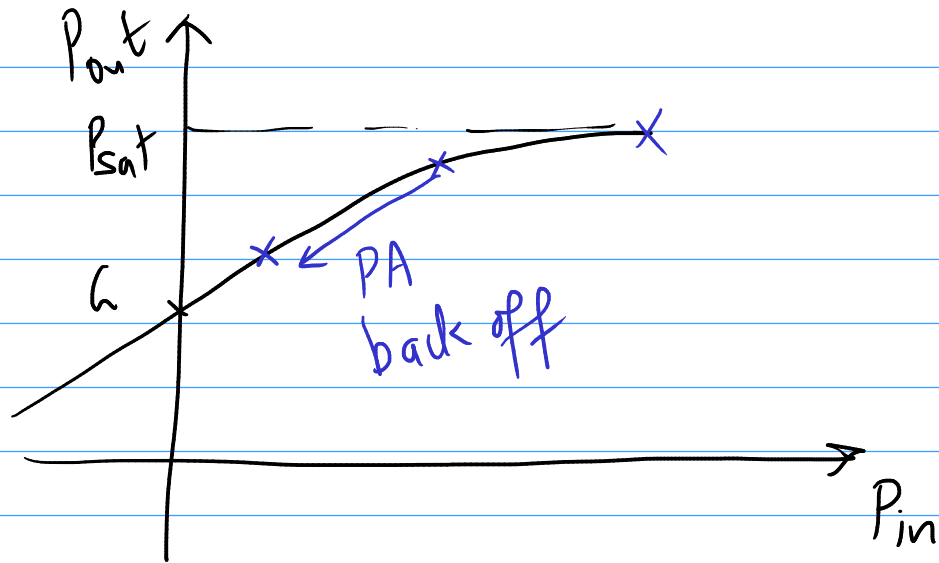


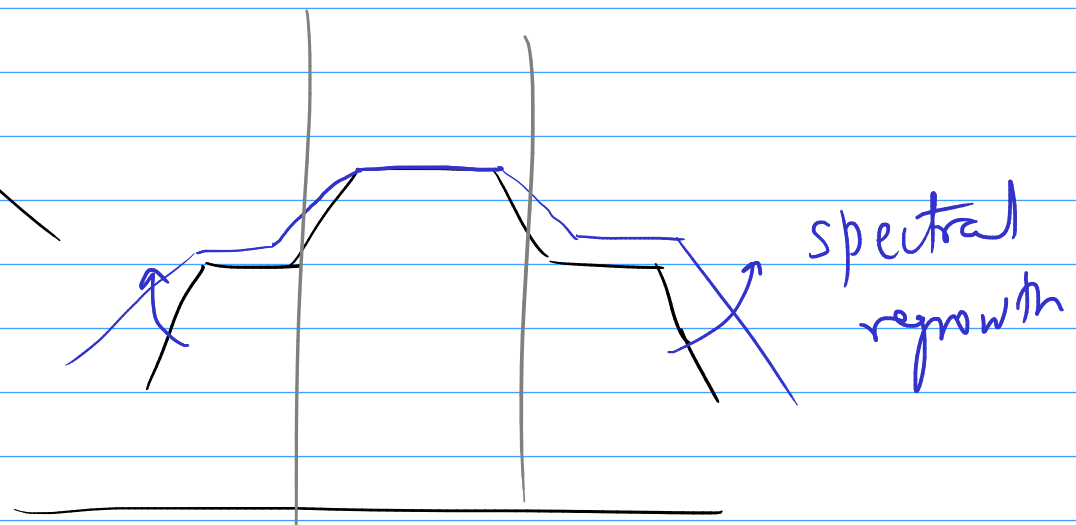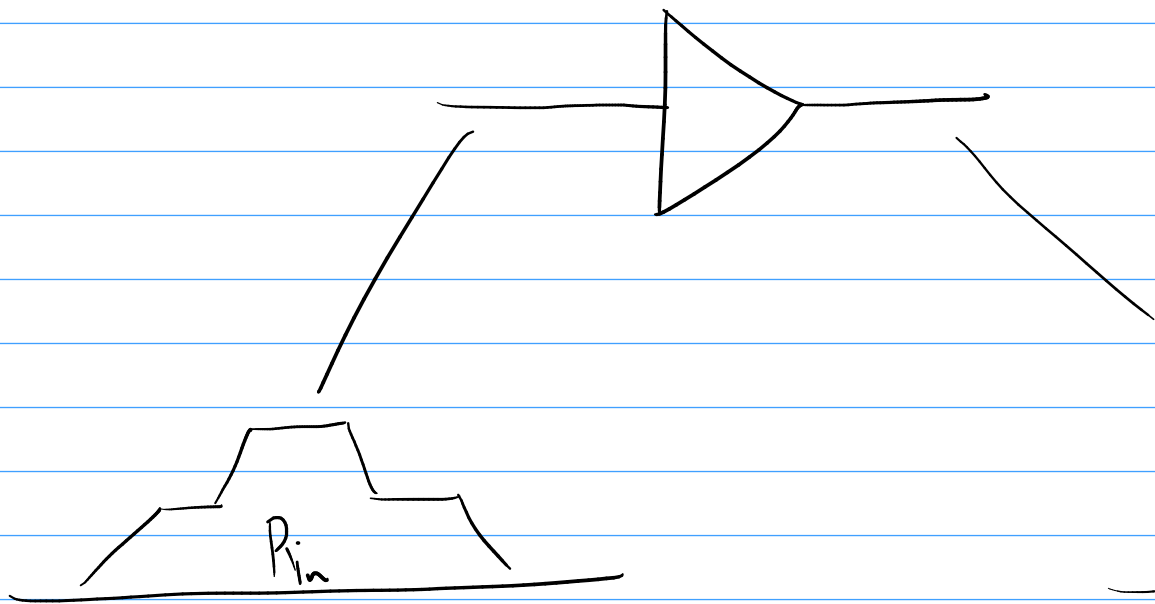

$V_{in} / P_{in}$

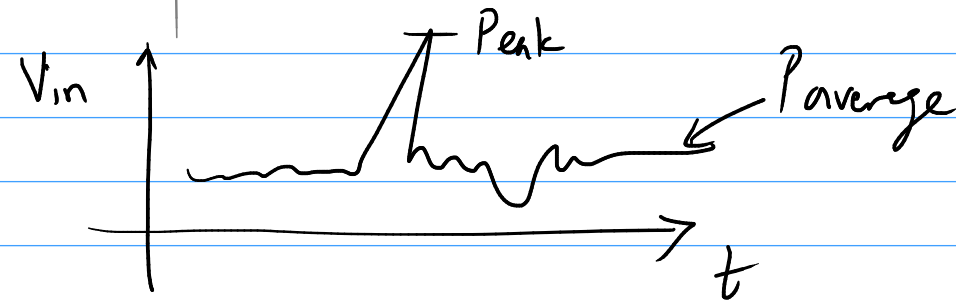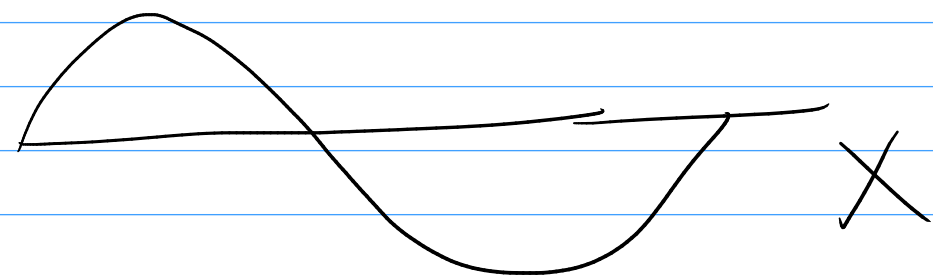

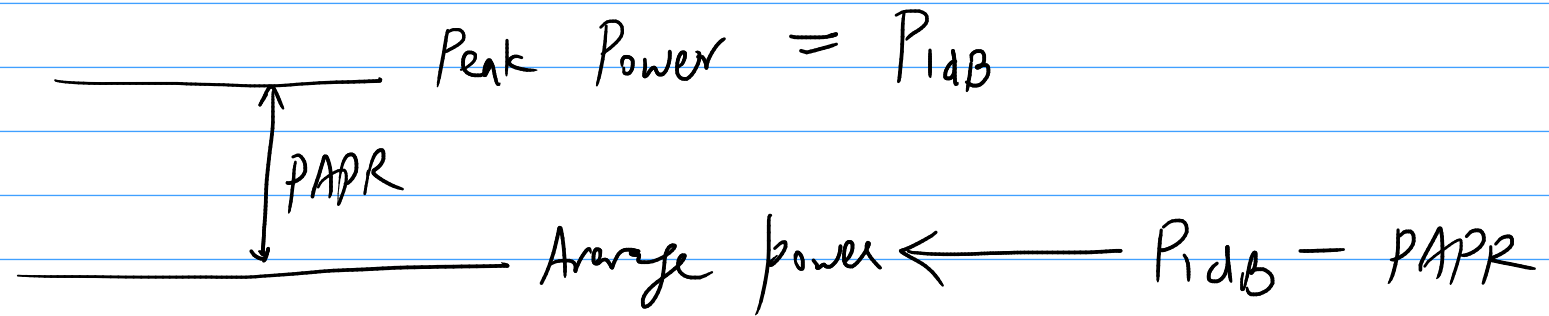
PAPR  $\equiv$  peak-to-average power ratio



Desired RF  $P_{out} = 10mW = 10dBm$


$PAPR = 10dB \leftarrow$  WiFi, 5G etc

PA  $P_{1dB_{out}} = 20dBm = 100mW!$

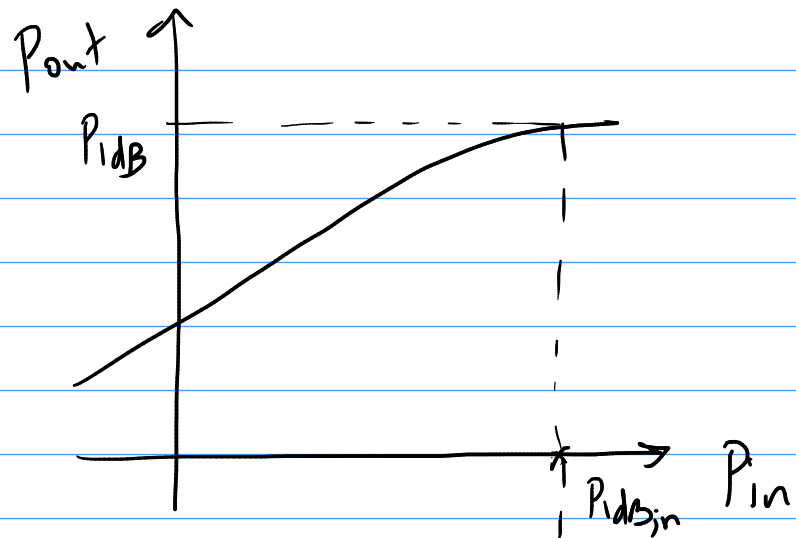




AM - AM

Normalise  
Phase Shift

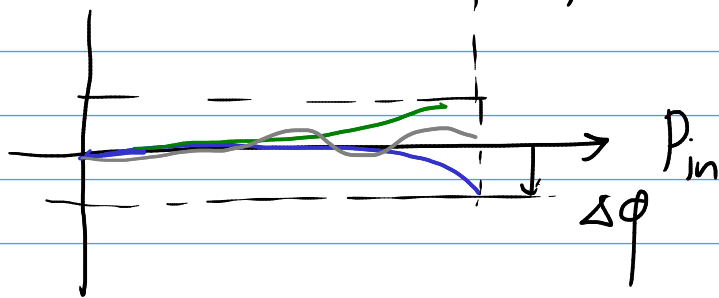

AM - PM


| $\theta_c$ ← conduction angle | class of PA |
|-------------------------------|-------------|
| $360^\circ$                   | Class - A   |
| $180^\circ - 360^\circ$       | class - AB  |
| $180^\circ$                   | class - B   |
| $< 180^\circ$                 | class - C   |
|                               | class - D   |
|                               | - E         |
|                               | F           |
|                               | ⋮           |

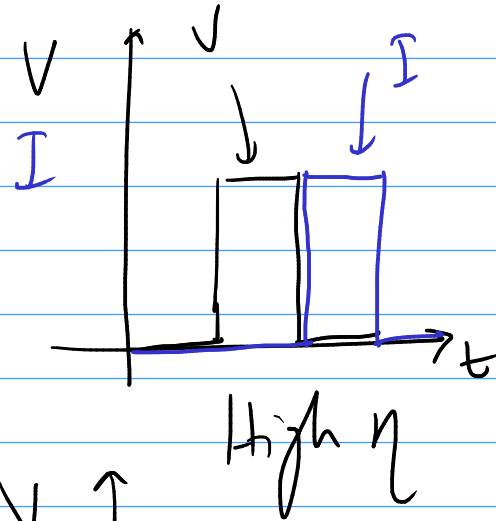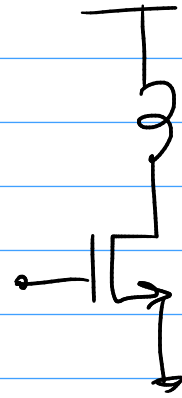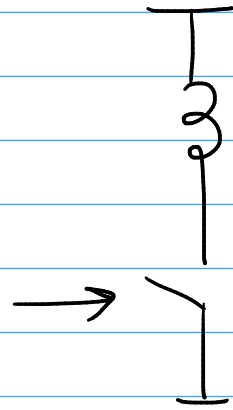


Class-E PA


Phase Modulated

signals

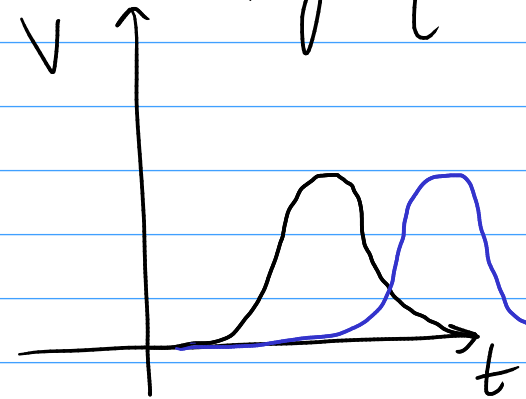


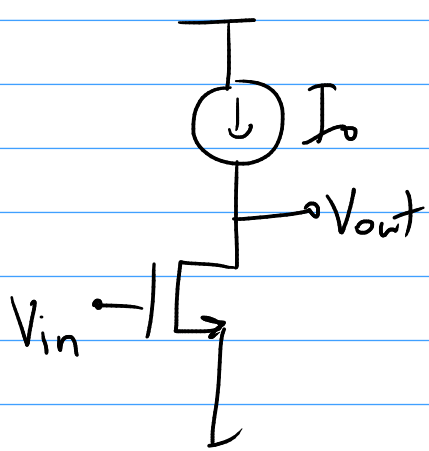


≡

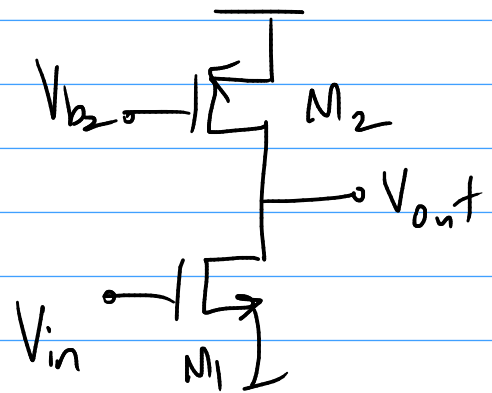


↓


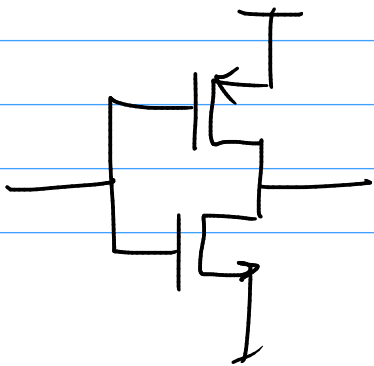

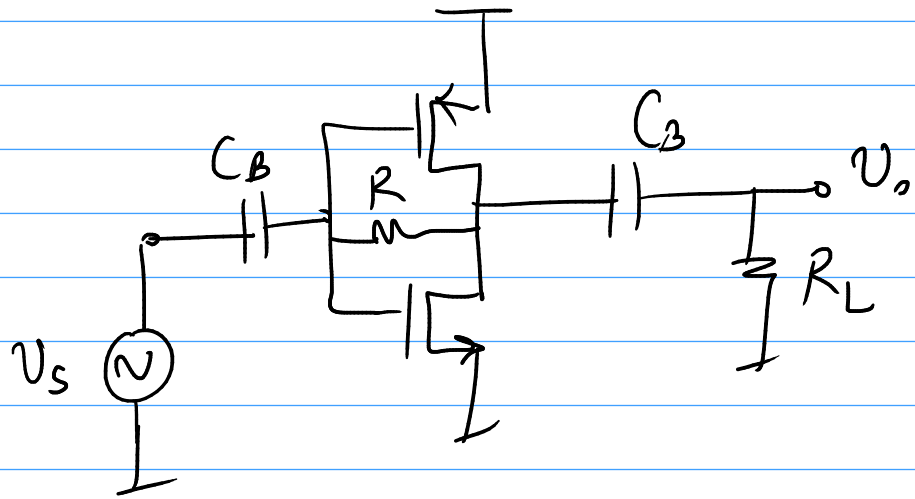
$$g_{m,n} = \frac{g_{m,n} + g_{m,p}}{g_{d,s,n} + g_{d,s,p}}$$



CMOS  
Inverter  
based  
DA

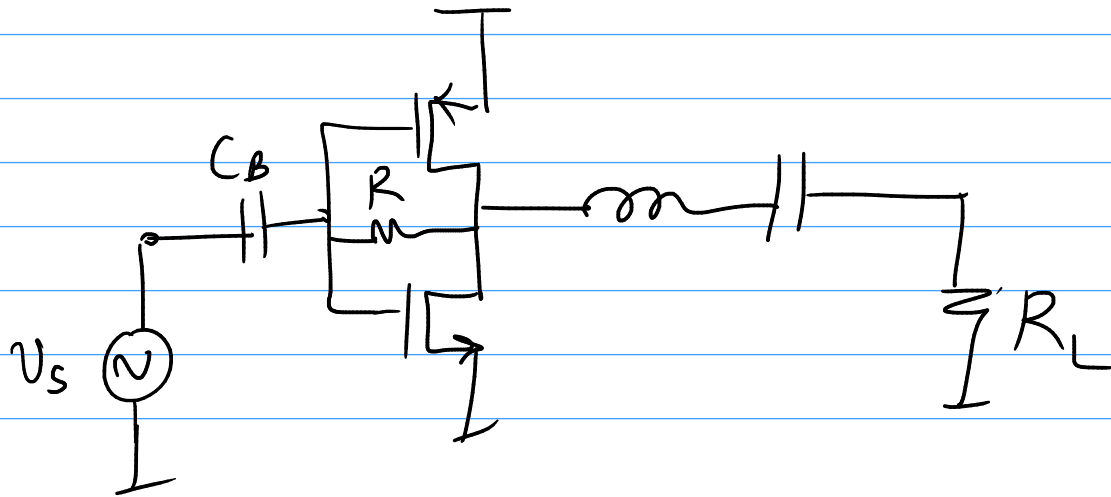

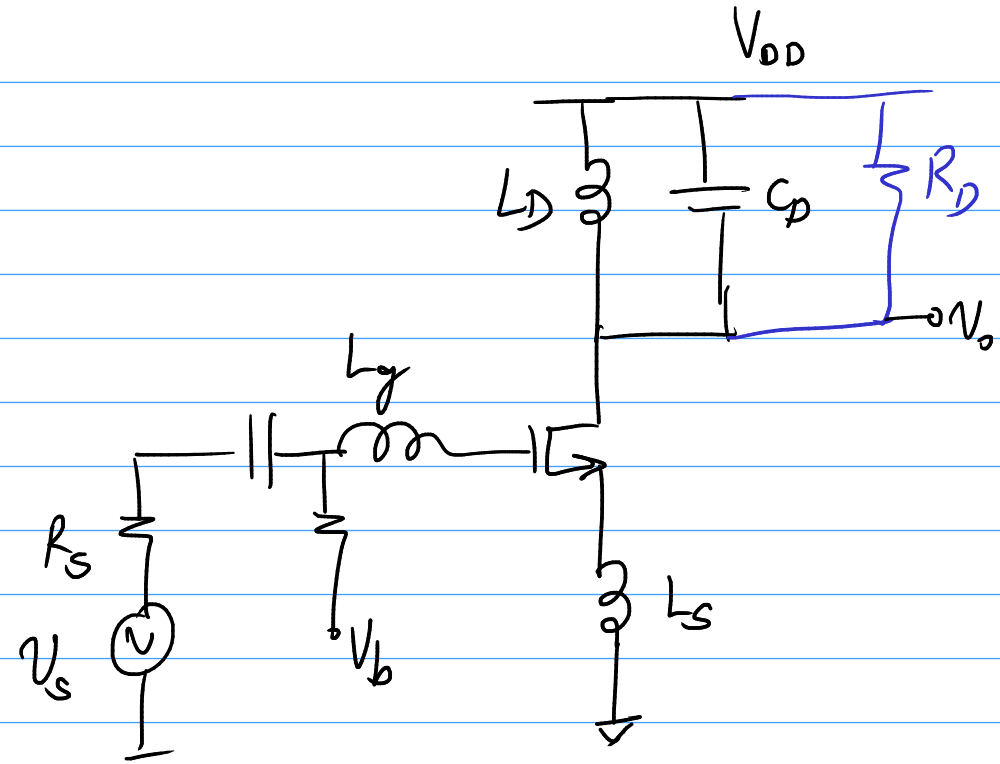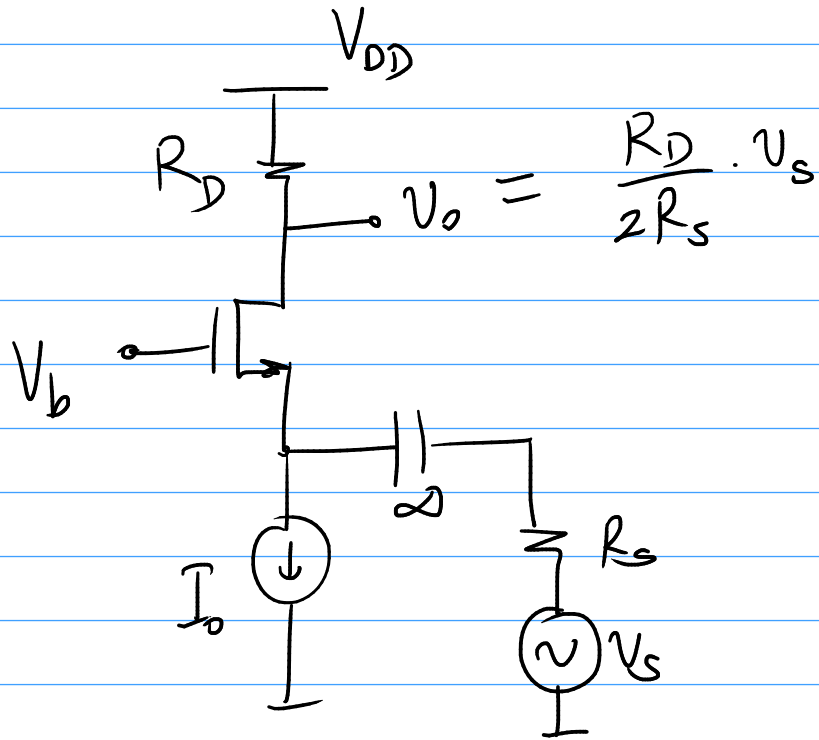


$$\frac{1}{g_m} = 50\Omega = R_s$$

CG LNA

- high NF
- Broadband
- low gain



CS LNA


- high gain
- low NF
- narrowband

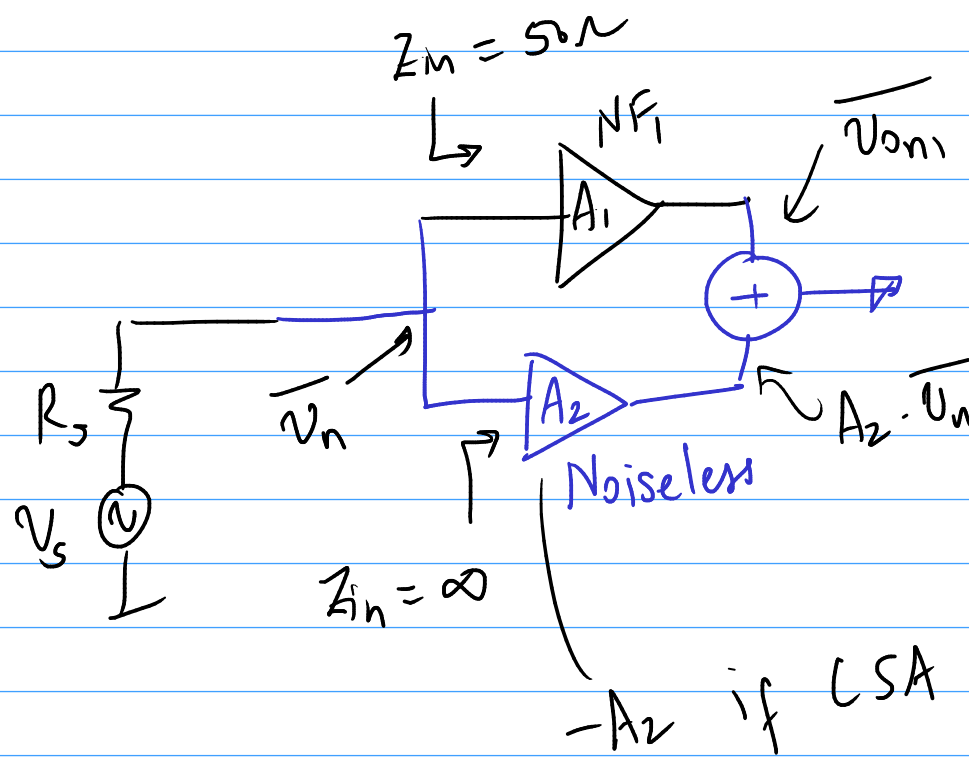

$A_2 \overline{V_n} + \overline{V_{n1}} \rightarrow$  lower NF  
 $NF < NF_1$

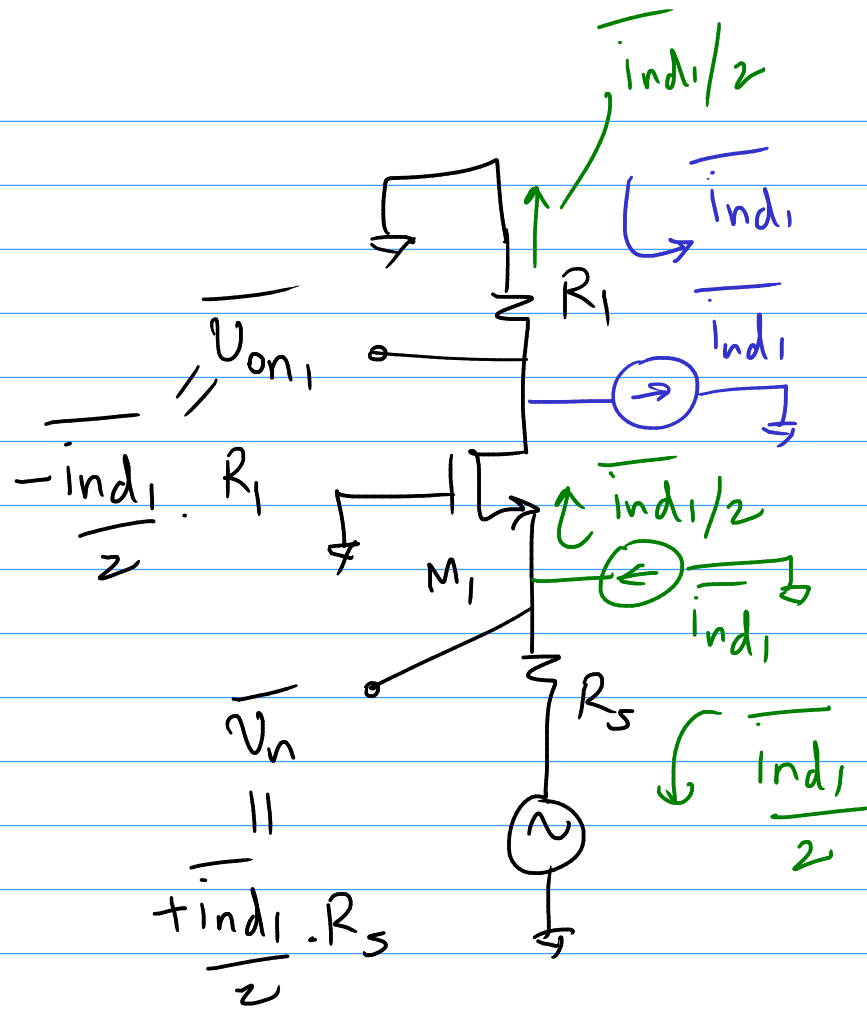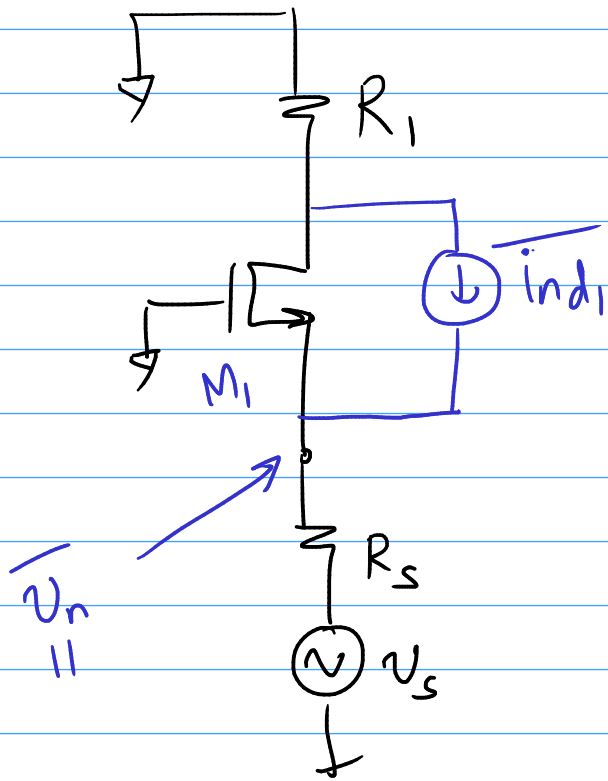$A_2 \cdot V_n + \overline{V_{n1}} < \overline{V_{n1}}$



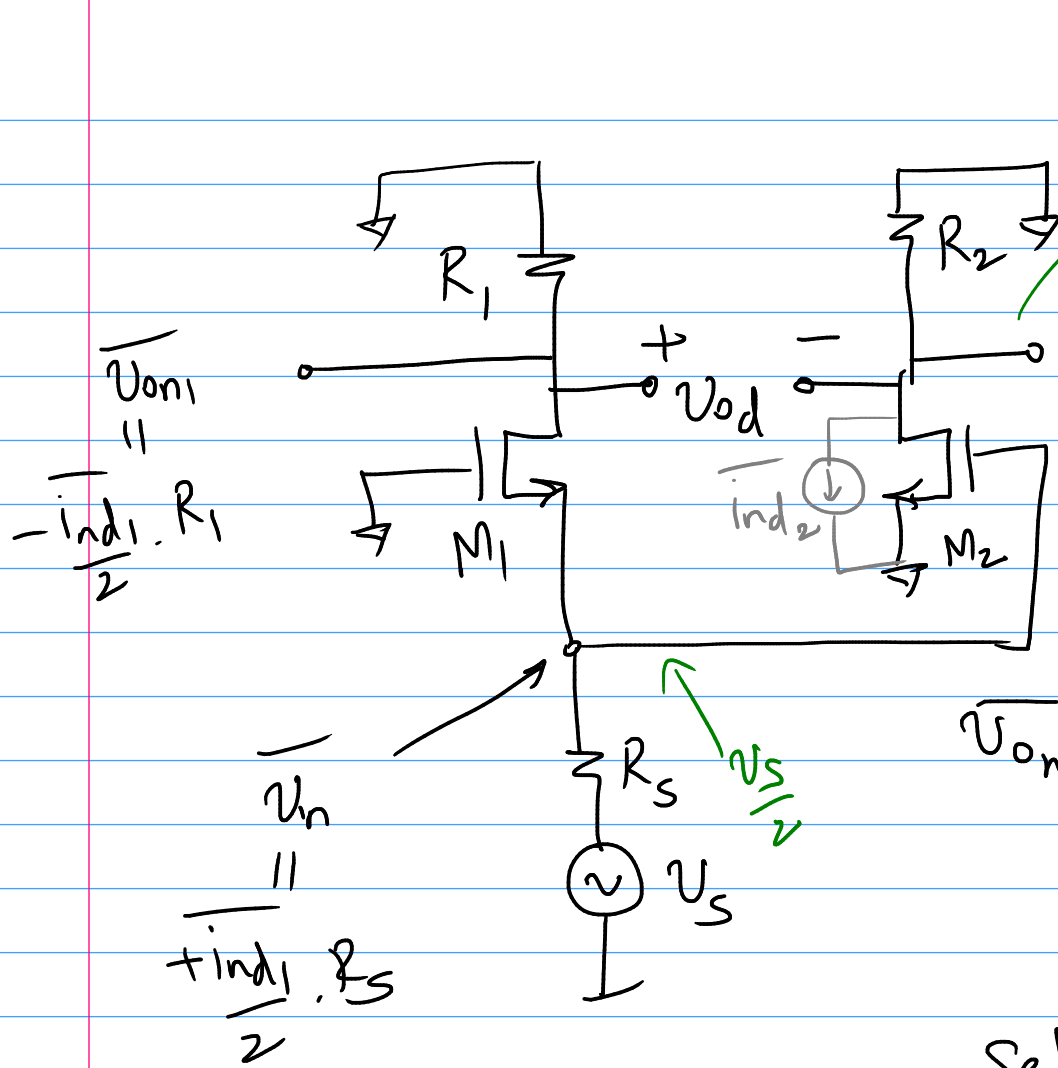

$$V_{o2} = -g_{m2} R_2 \cdot \frac{V_S}{2}$$

$$\begin{aligned} \overline{V_{on2}} &= -g_{m2} R_2 \cdot \overline{V_n} \\ &= -g_{m2} R_2 \cdot \frac{\overline{ind_1}}{2} \cdot R_S \end{aligned}$$

$$\overline{V_{ond_{M1}}} = \overline{V_{on1}} - \overline{V_{on2}}$$

$$= (g_{m2} R_2 R_S - R_1) \cdot \frac{\overline{ind_1}}{2}$$

Set  $\overline{V_{ond_{M1}}} = 0$

"Noise Cancelling"  
LNA

$$\boxed{g_{m2} R_2 = \frac{R_1}{R_S}}$$


for noise cancellation

$$\frac{V_{o1}}{V_S} = \frac{R_1}{2R_S}$$

$$\frac{V_{o2}}{V_S} = \frac{-g_{m2} R_2}{2}$$

$$\frac{V_{od}}{V_S} = \frac{R_1}{2R_S} + \frac{g_{m2} R_2}{2}$$
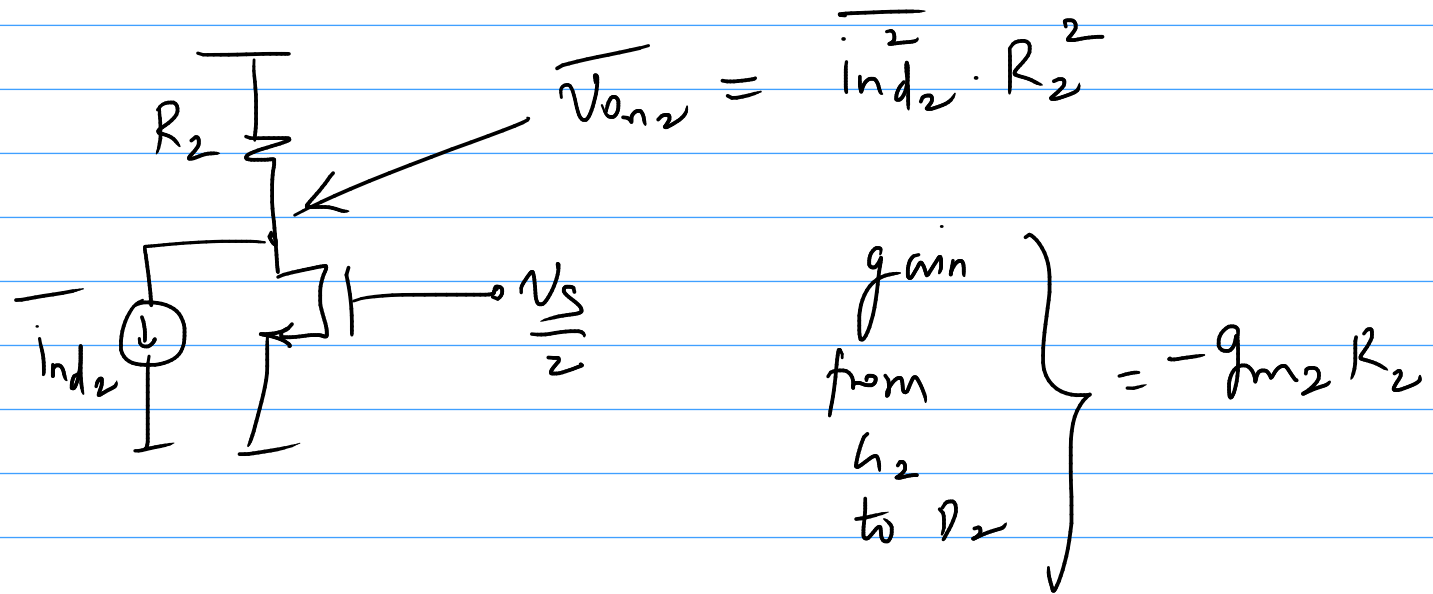
$$\boxed{\frac{V_{od}}{V_S} = \frac{R_1}{R_S}}$$



input referred noise

due to  $M_2 = \frac{\overline{i_{nd2}} R_2^2}{g_{m2}^2 R_2^2} = \frac{4kT\gamma}{g_{m2}} \Delta f$

large  $g_{m2} \rightarrow$  low NF contribution from  $M_2$

②  
output

\* Noise from  $M_1$  @ output = 0 (CG device)

\* Noise from  $M_2 = 4kT \gamma g_{m2} R_2^2$  (CS device)

\* Noise from  $R_1 = 4kTR_1$

\* " "  $R_2 = 4kTR_2$

\* Noise from  $R_S = \left(\frac{R_1}{R_S}\right)^2 \times 4kTR_S = \frac{4kTR_1^2}{R_S}$

$(\text{gain})^2 \times \overline{v_{nR_S}^2}$

$$F = 1 + \frac{4kT\gamma g_{m2} R_2^2 + 4kTR_1 + 4kTR_2}{4kTR_1^2/R_S}$$

$$= 1 + \gamma \cdot \left( g_{m2} \cdot R_S \cdot \frac{R_2^2}{R_1^2} \right) + \frac{R_S}{R_1} + \frac{R_S R_2}{R_1^2}$$


— apply  $g_{m2} R_2 = \frac{R_1}{R_S}$

$$= 1 + \gamma \cdot \frac{R_2}{R_1} + \frac{R_S}{R_1} + \frac{R_S R_2}{R_1^2}$$


min F   


 $\begin{array}{l} \rightarrow \text{min. } R_2 \\ \rightarrow \text{max } R_1 \end{array}$ 

 $\leftrightarrow \text{max. } g_{m2}$

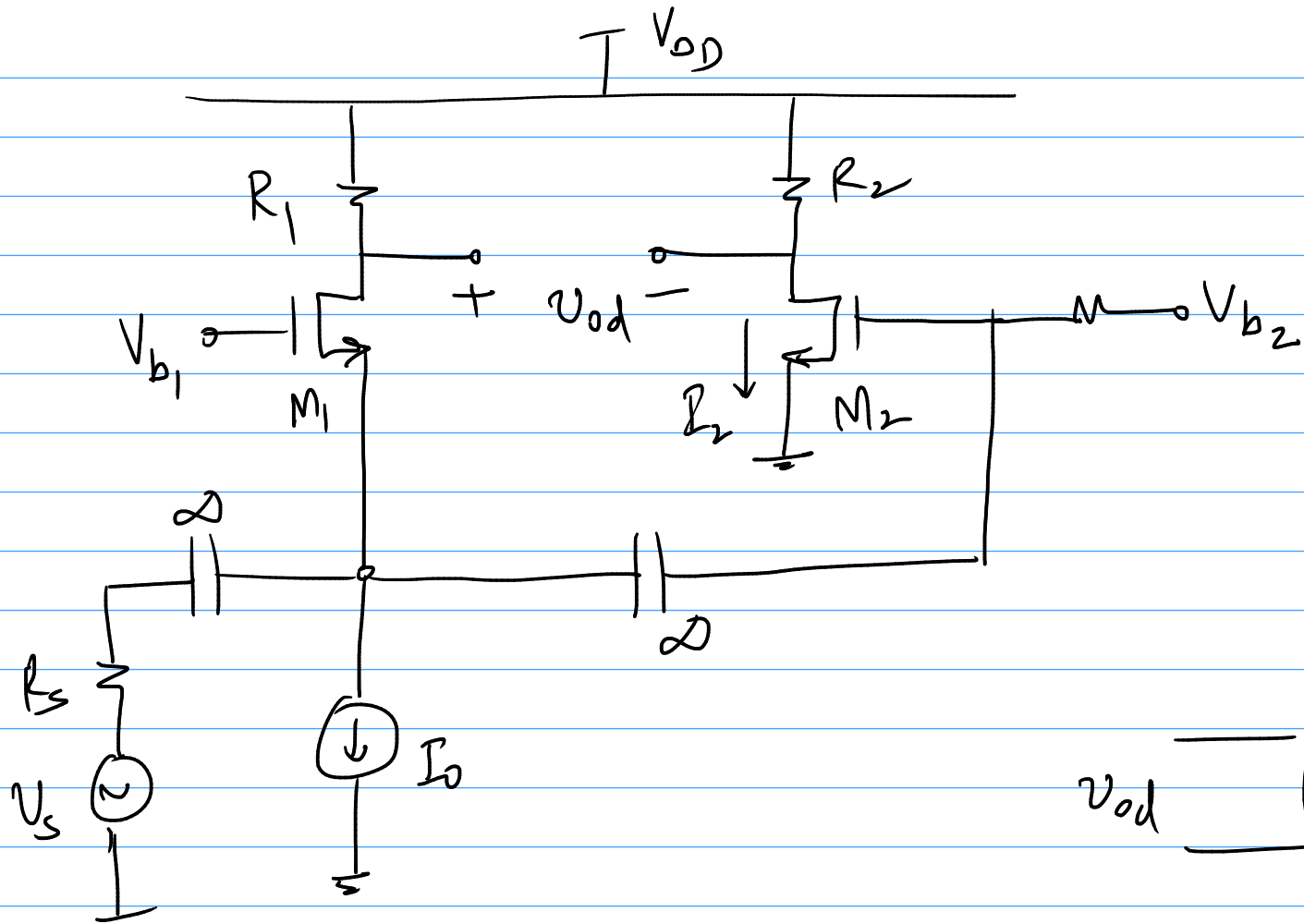


Noise Cancelling  
LNA

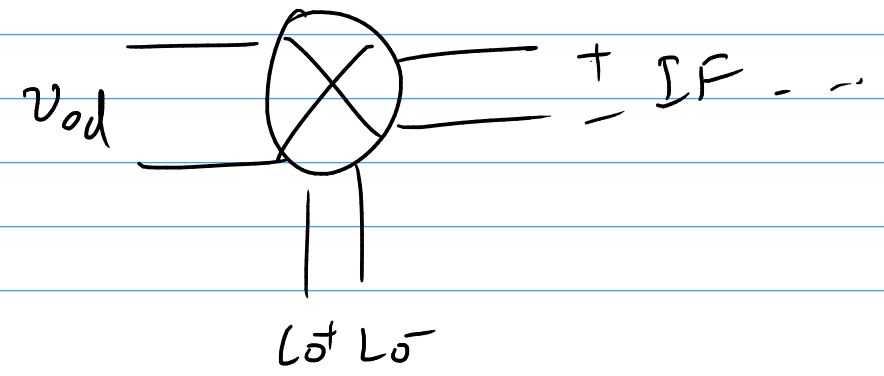

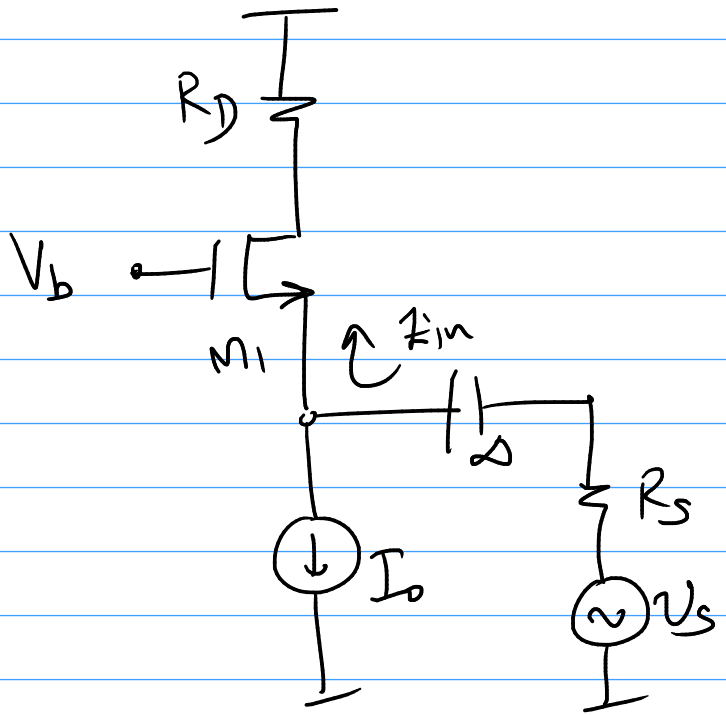

$$Z_{in} = \frac{1}{g_{m1}} = R_S$$

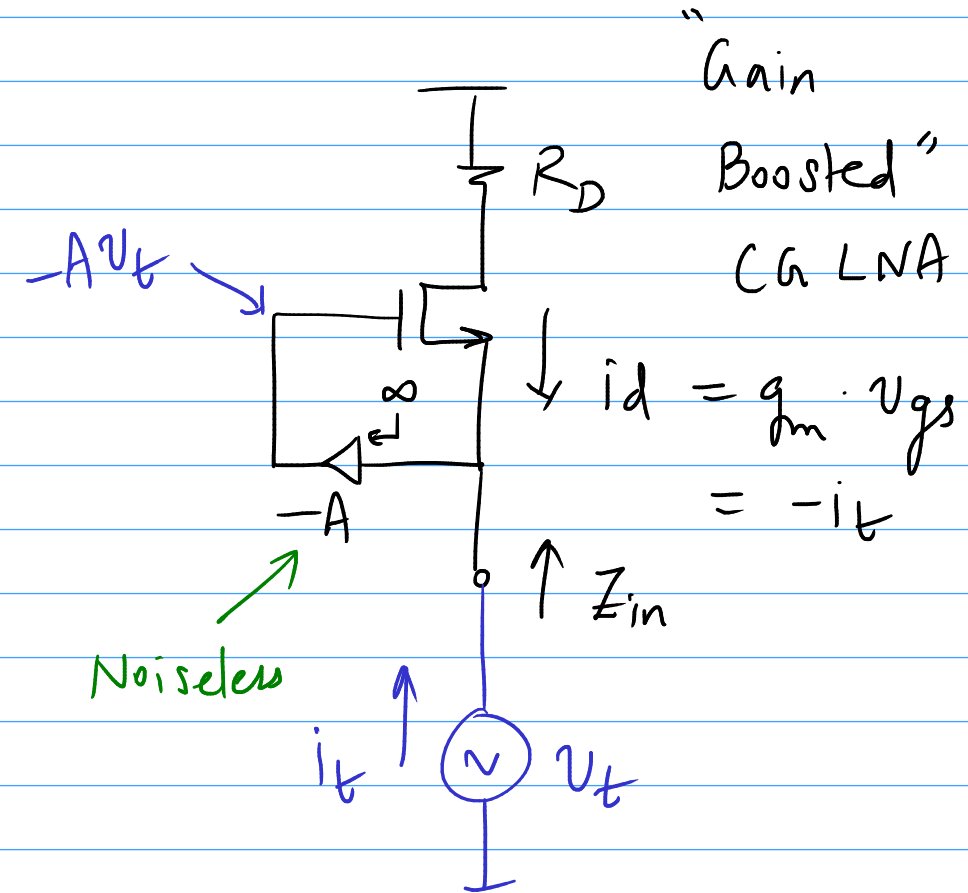

"Gain Boosted" CG LNA

$$i_d = g_{m1} \cdot v_{gs} = -i_t$$


$$-i_t = g_{m1} (-A v_t - v_t)$$

$$Z_{in} = \frac{v_t}{i_t} = \frac{1}{(1+A)g_m} = R_s$$

e.g. CGA  $\rightarrow g_m = \frac{1}{R_s} = 20\text{mS}$

Gain Boosted CGA  $\rightarrow g_m = \frac{1/R_s}{(1+A)} = \frac{20\text{mS}}{1+A}$

gain  $\frac{v_o}{v_s}$  is same

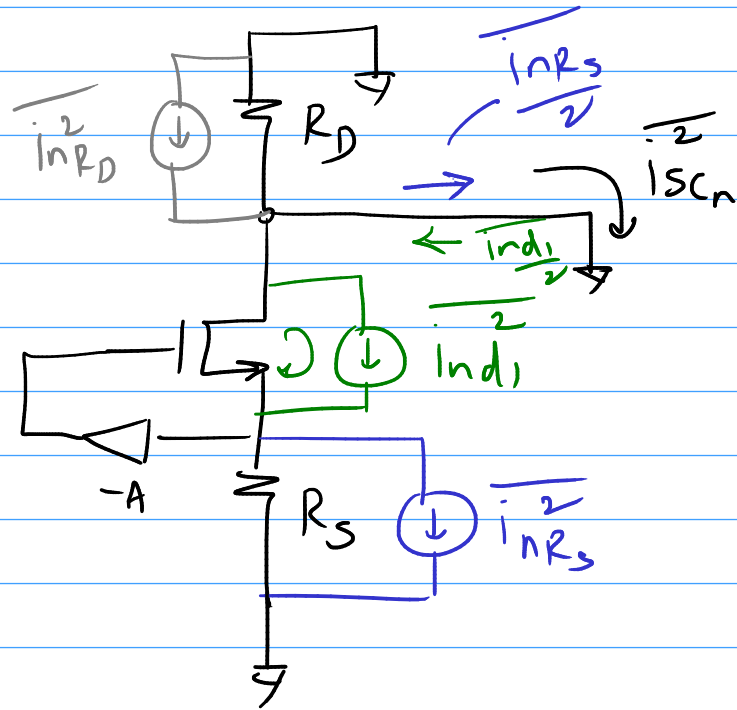

$$R_{in} = R_s = \frac{1}{g_m(1+A)}$$

$$\frac{kT}{R_s}$$

$$\frac{4kT}{R_L}$$


$$kT \gamma g_{m1}$$

$$F = 1 + \frac{kT \gamma g_{m1} + 4kT/R_L}{kT/R_s} = 1 + \gamma g_{m1} R_s + \frac{4R_s}{R_L}$$


$$g_{m1} R_s = \frac{1}{1+A}$$

$$F = 1 + \frac{\gamma}{1+A} + \frac{4R_s}{R_1}$$


A = Noiseless amp.

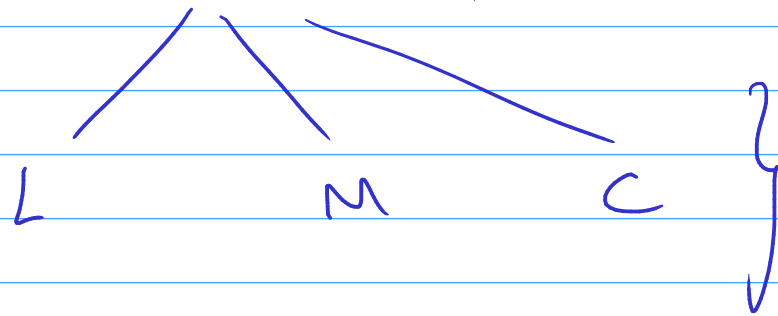


} give passive Noiseless  
Voltage gain

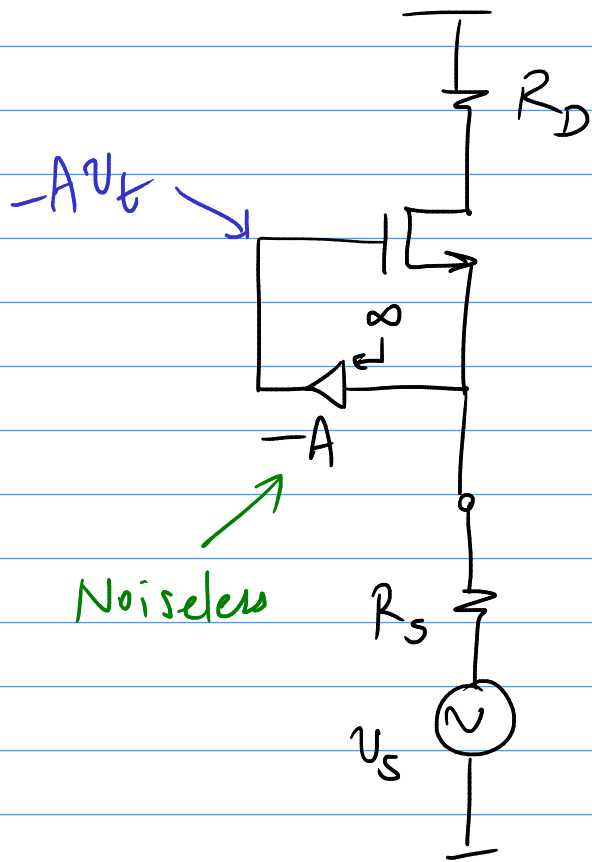

1)

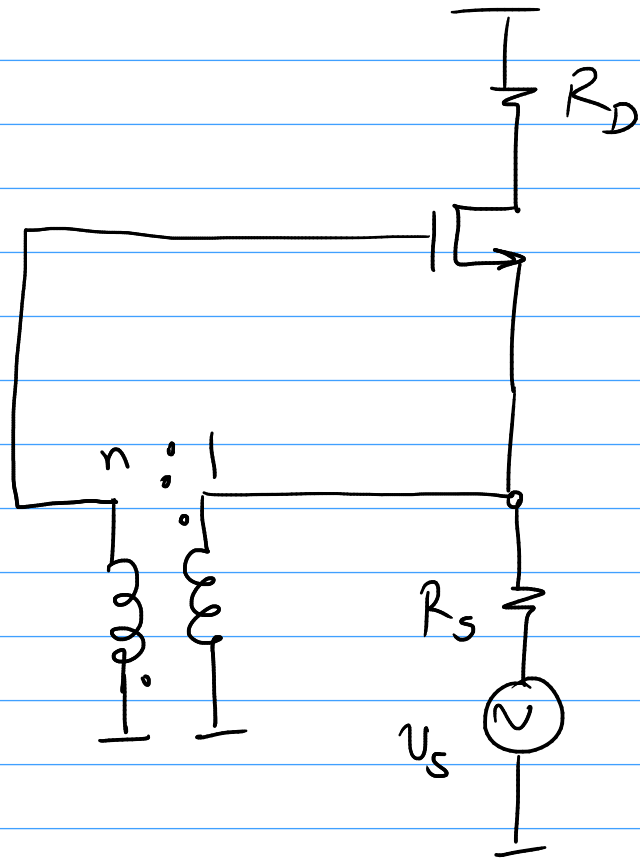

$A = n$   
 $n = 1$  is common





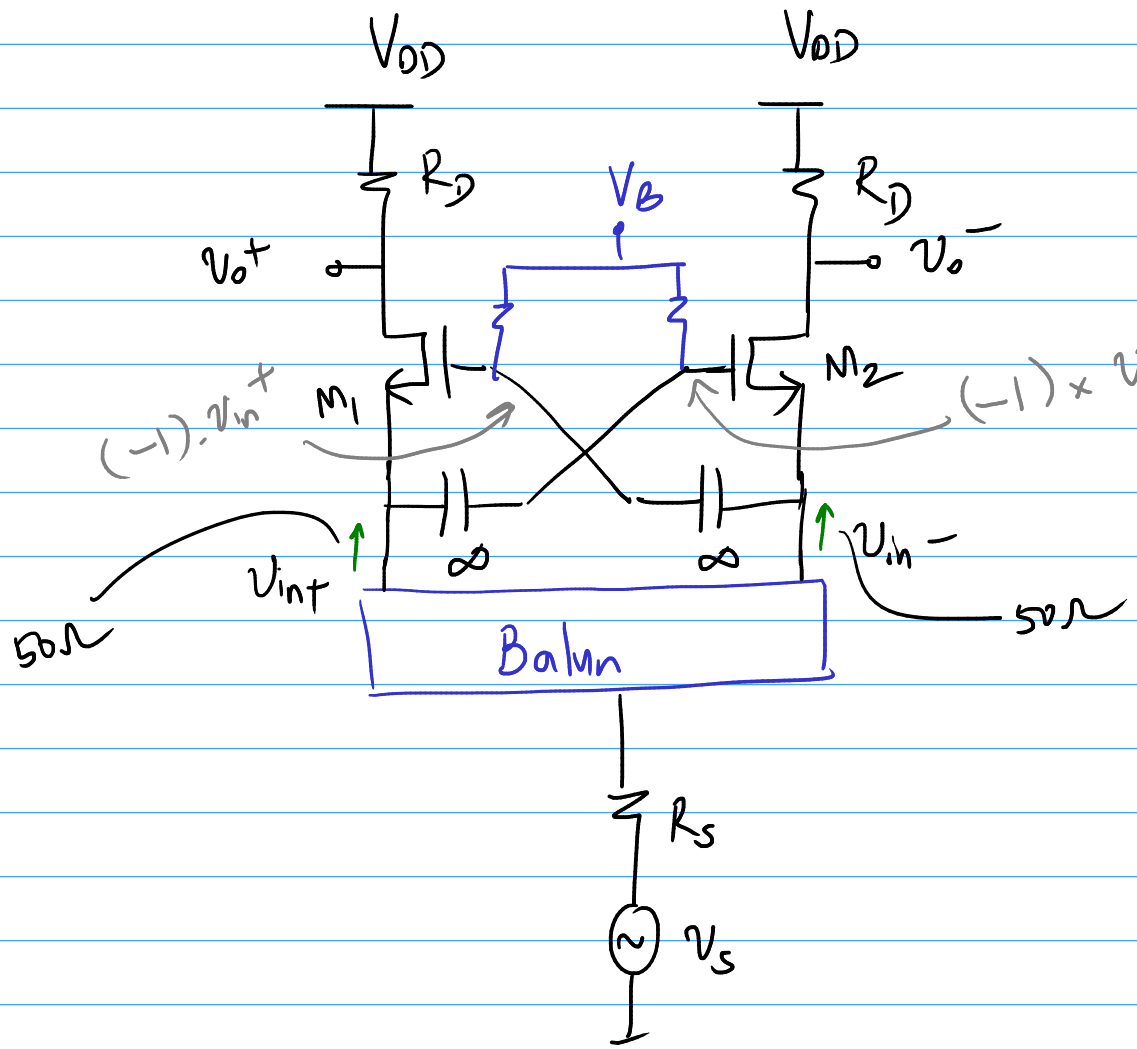





$$-A = -1$$

$$g_{m1} = g_{m2} = 10 \text{ mS}$$



Compact (No L, M)

Broadband

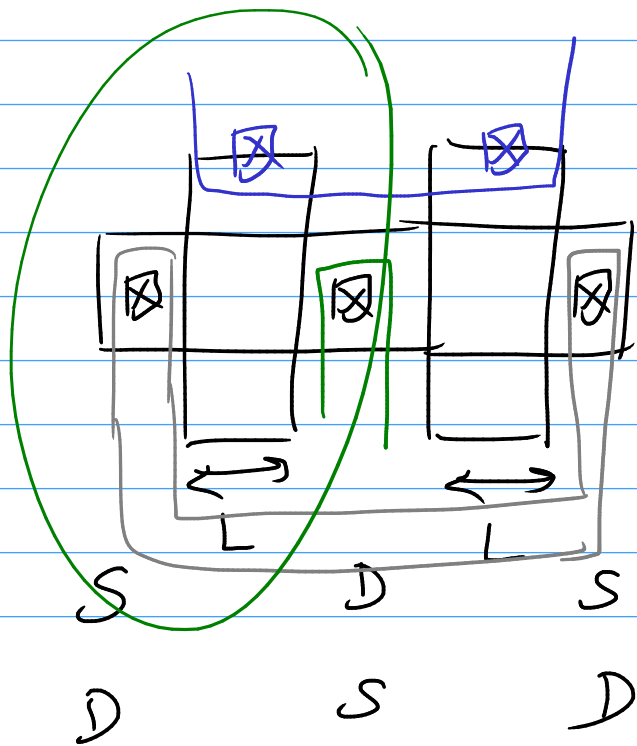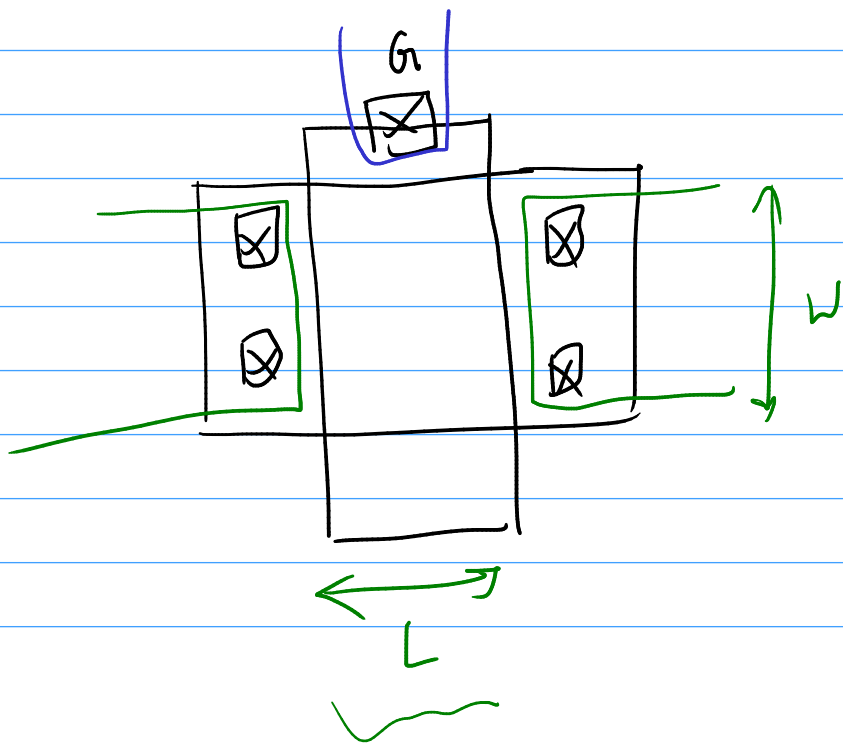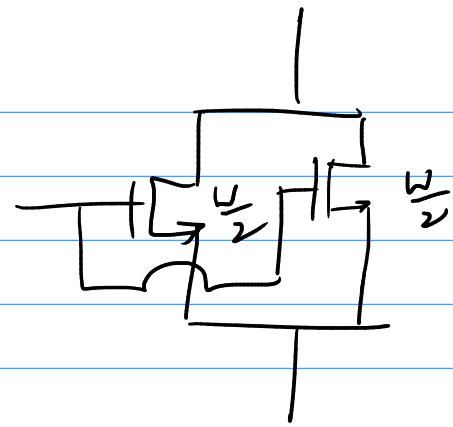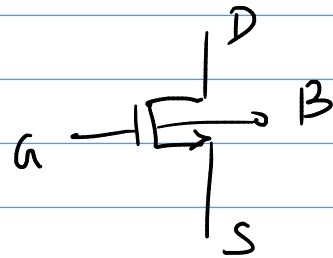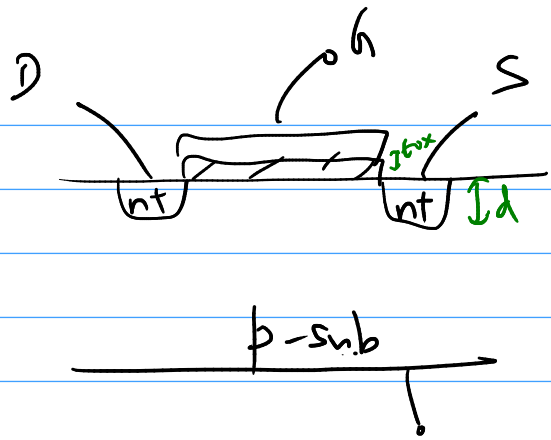

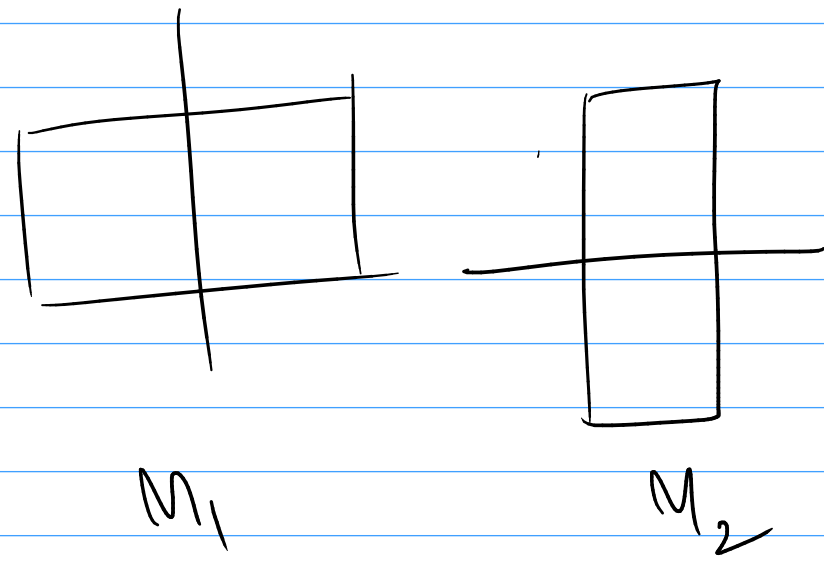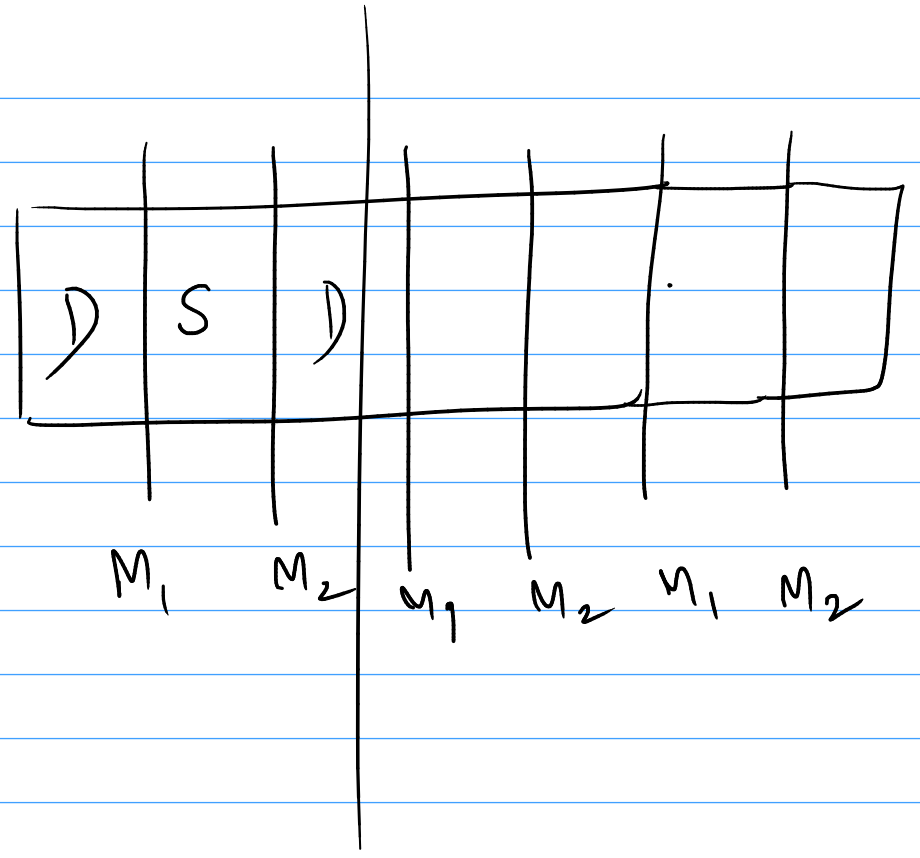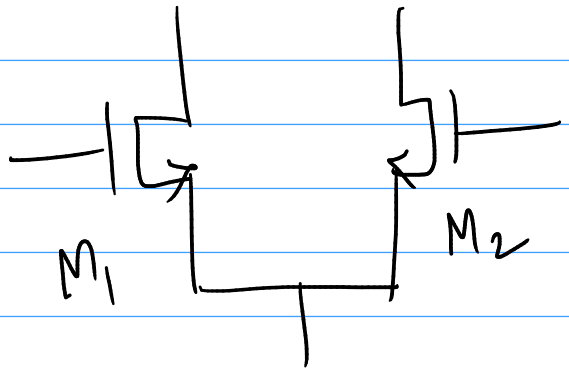


\_\_\_\_\_

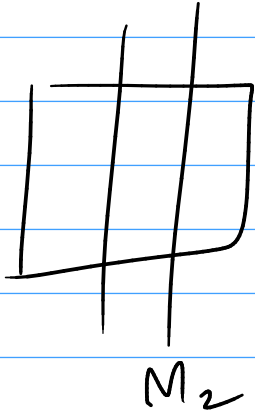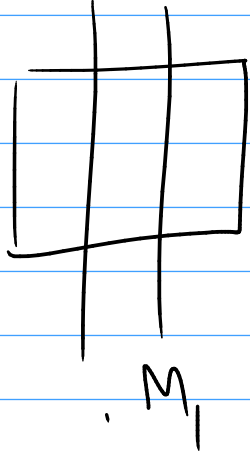


$M_1$




$M_2$

...

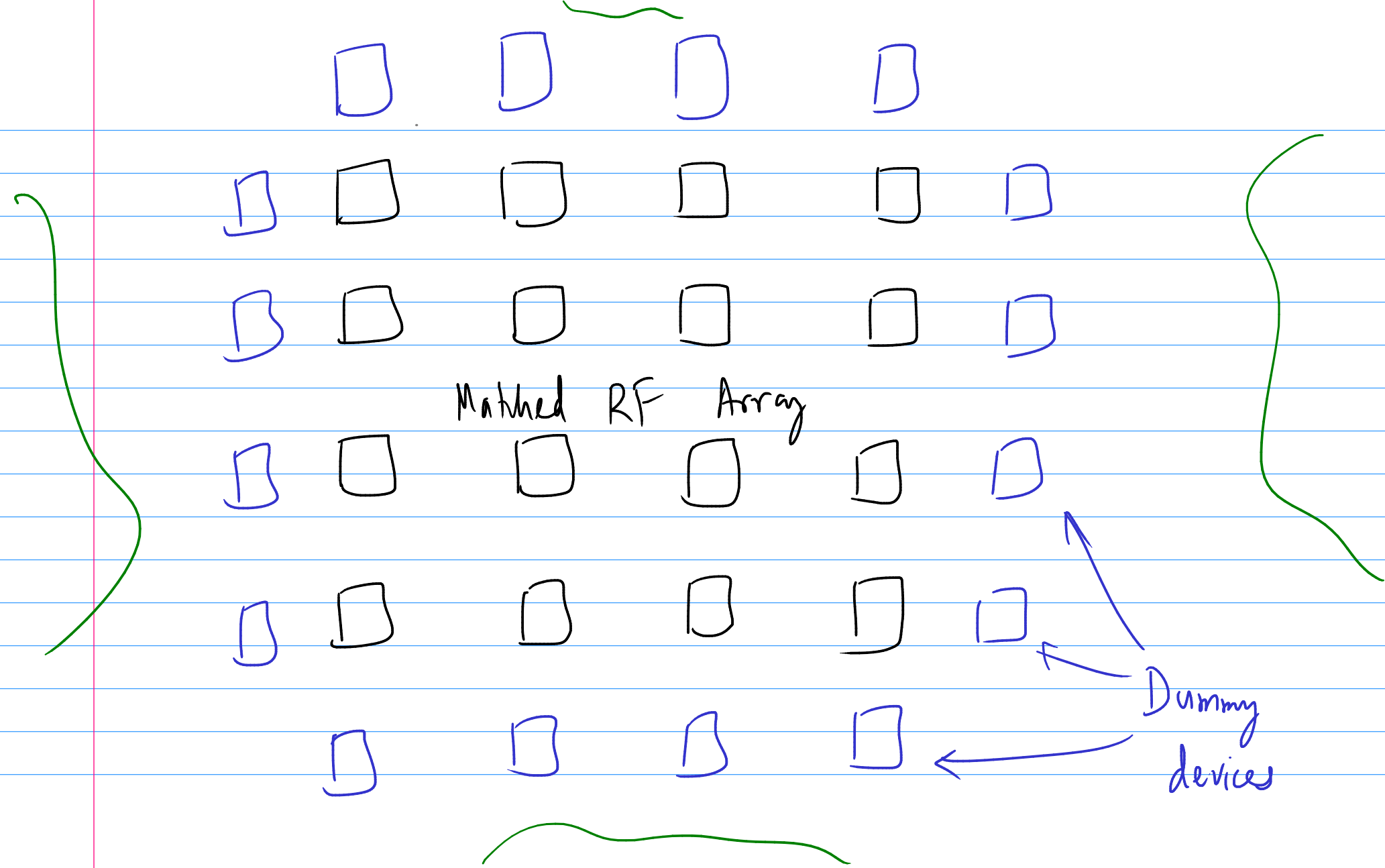


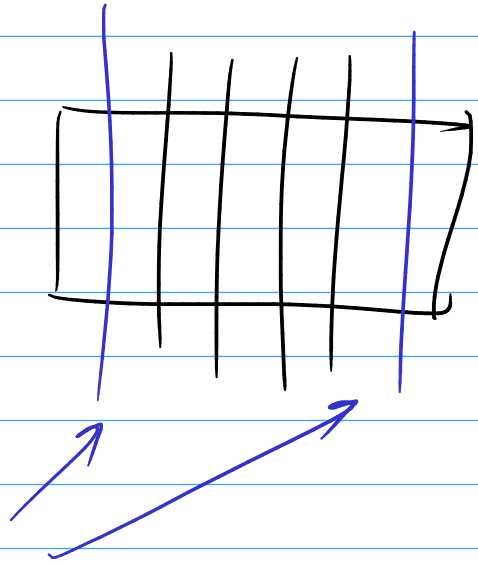



Dummy Finger

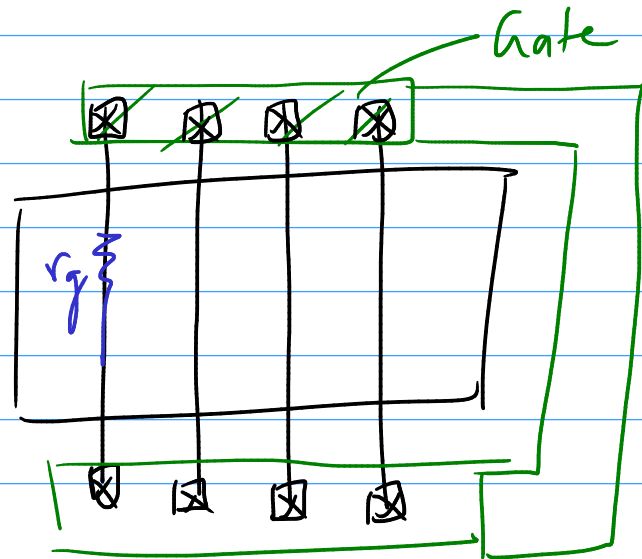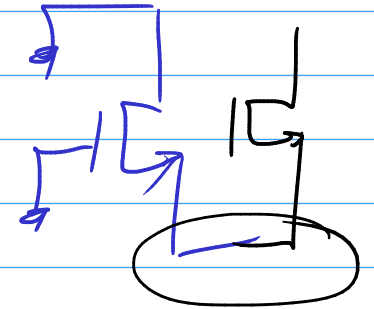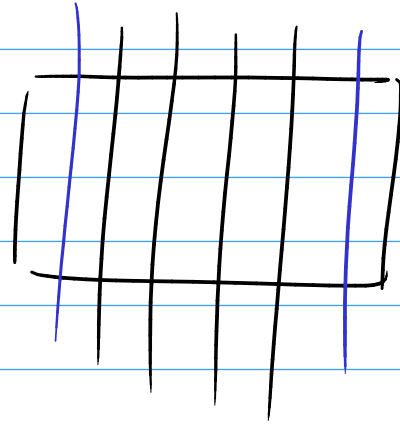


Dual-sided  
gate contacts




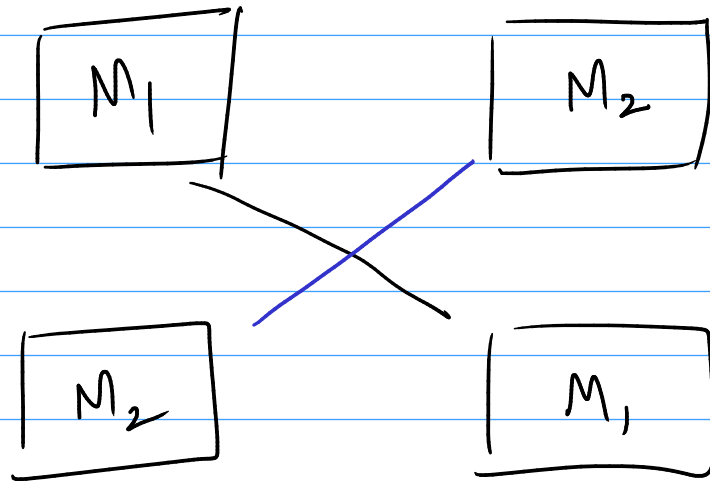



Common - centroid

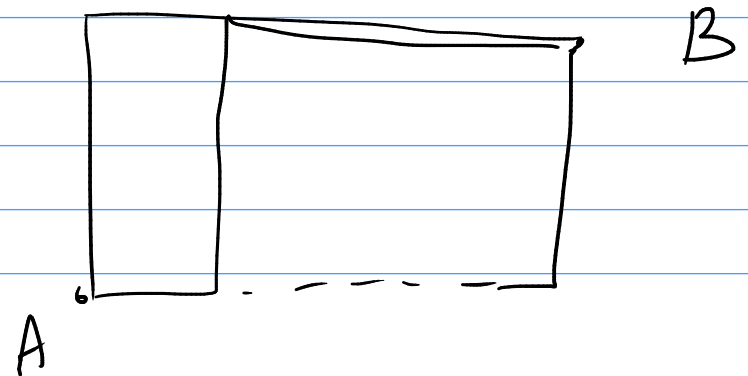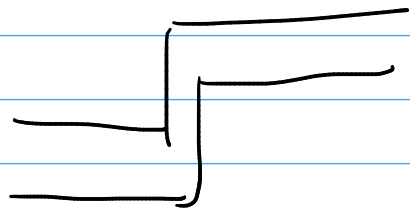


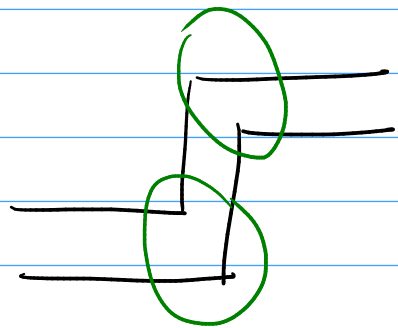


X

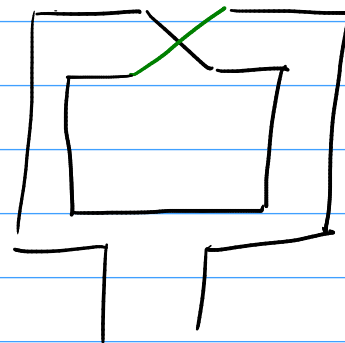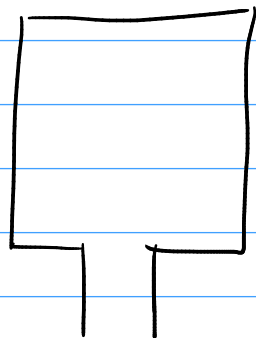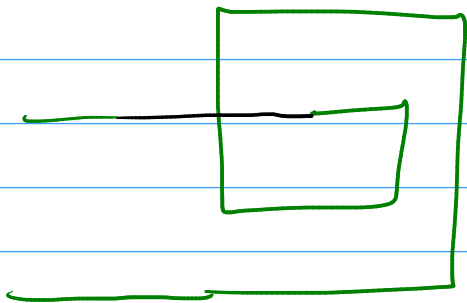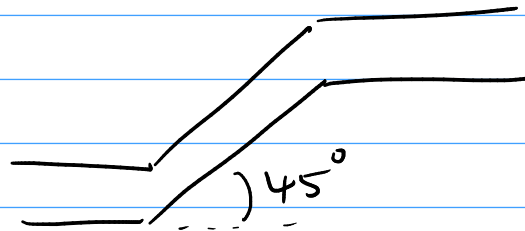

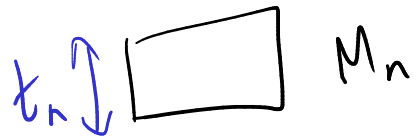


$\text{SiO}_2$

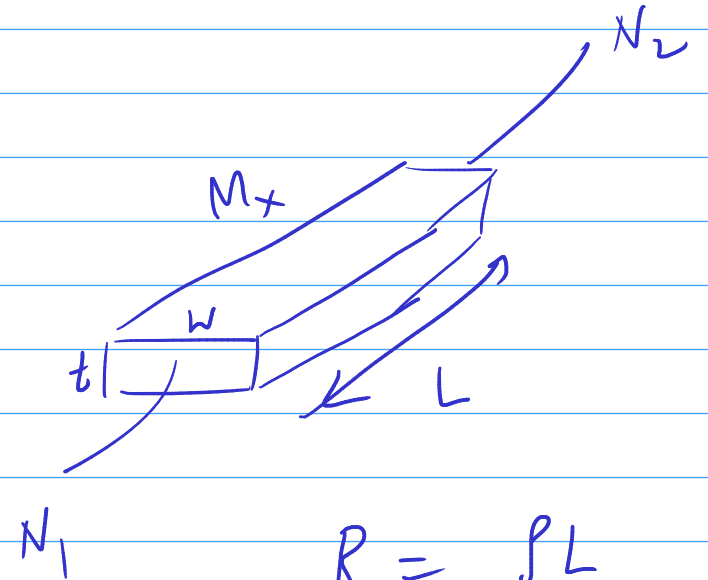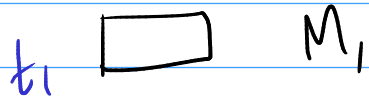


$$R = \frac{\rho L}{A} = \frac{\rho L}{N \cdot t}$$


$$= \underbrace{R_{\text{sheet}}}_{\rho/t} \cdot \underbrace{\# \text{ of squares}}_{L/w}$$

Skin Effect

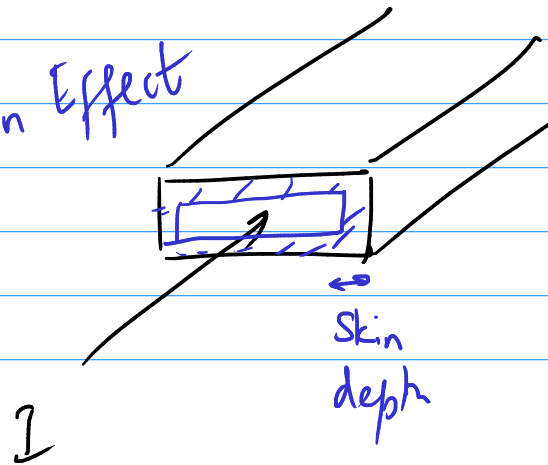


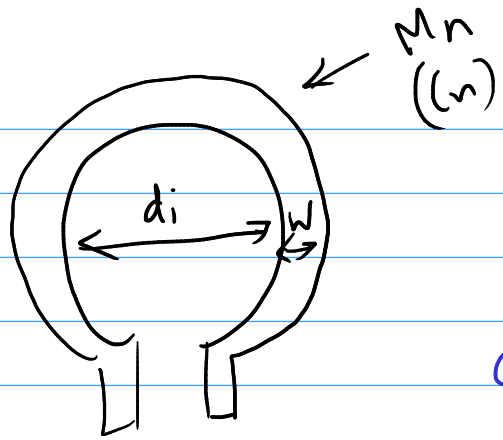


Circular

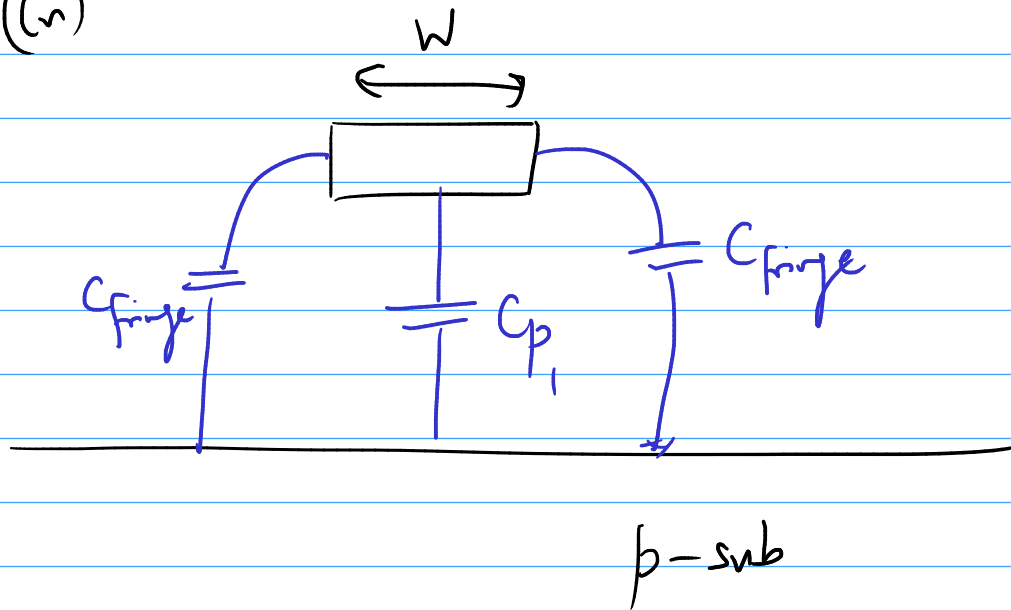


p-sub

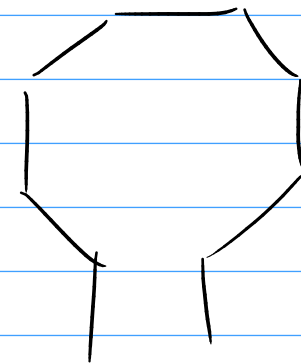


octagon

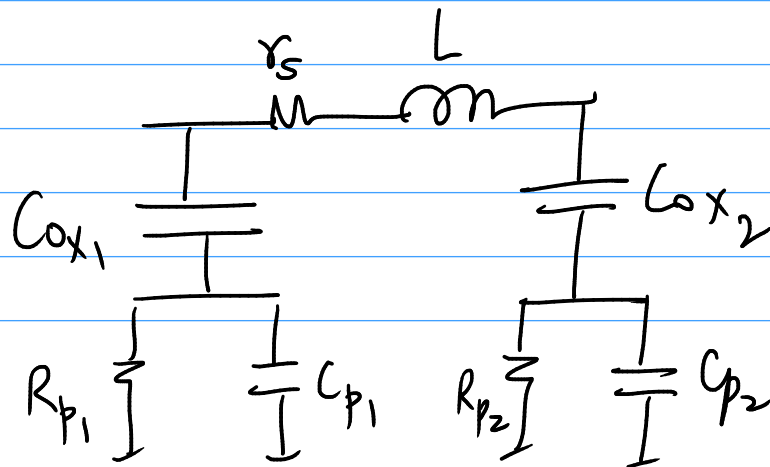

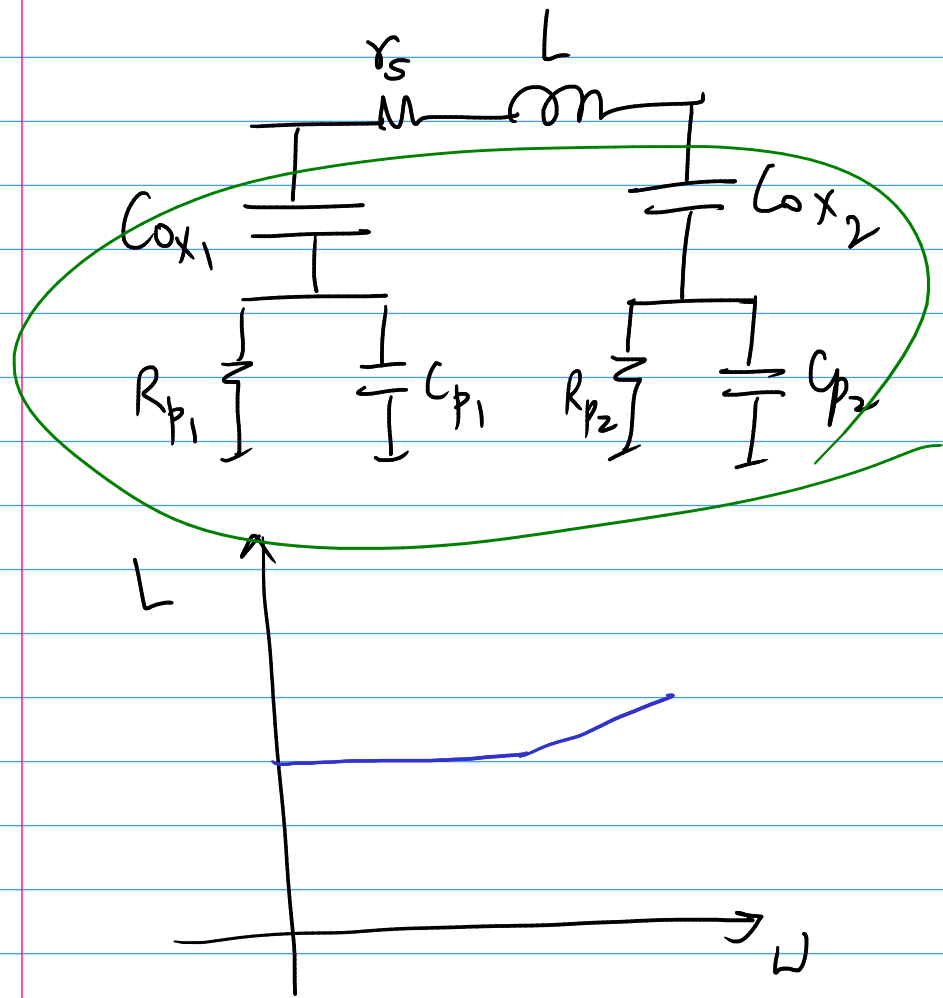Lumped Element  
Model of a spiral  
inductor (Narrowband)






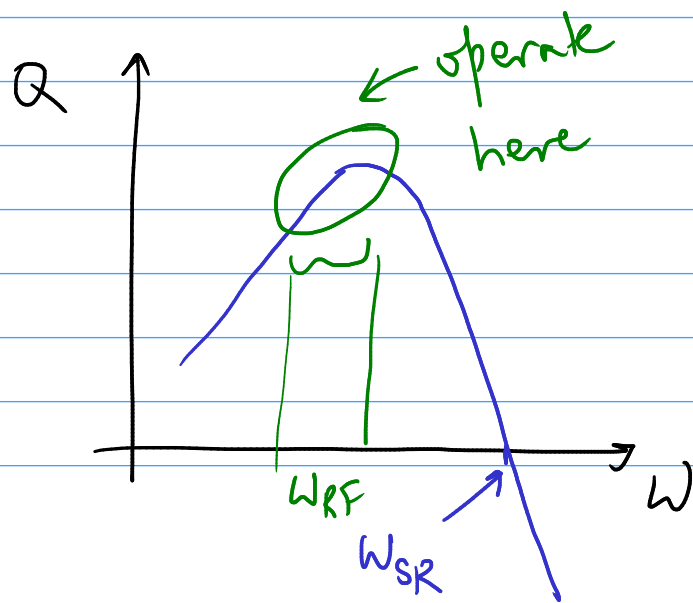Lumped Element  
Model of a spiral  
inductor (Narrowband)




$$Q = \frac{\text{Im}(Z)}{\text{Re}(Z)}$$

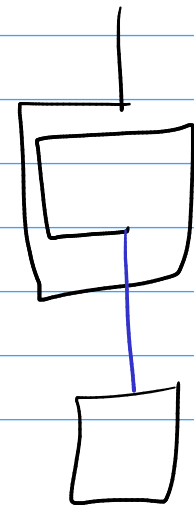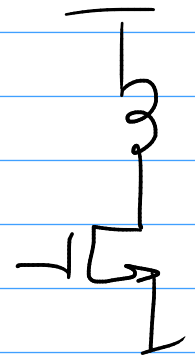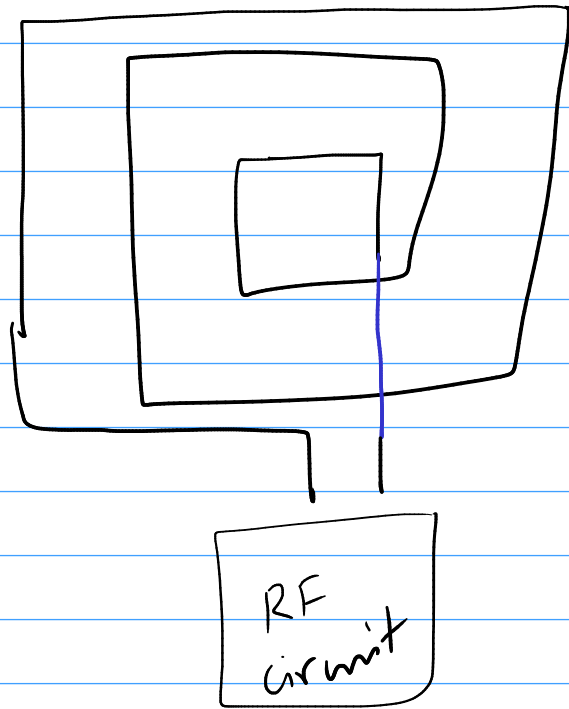$\omega_{SR}$  = self  
resonant  
frequency





1.5 turns

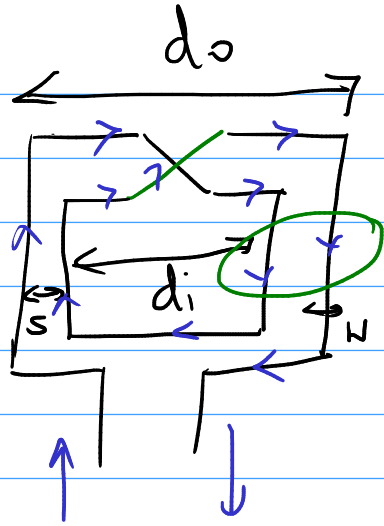

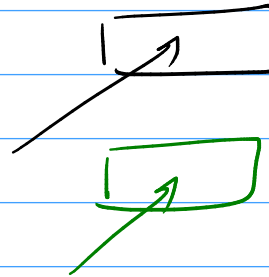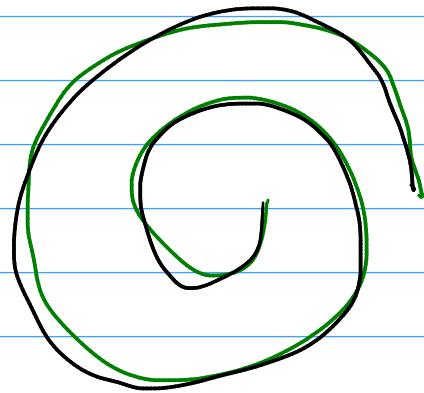
# turns  $n$   
 trace width  $w$   
 turn-to-turn spacing  $s$


inner diameter  $d_i$   
 outer diameter  $d_o$



# Passive Mixers

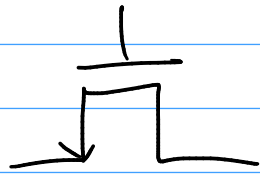

triode

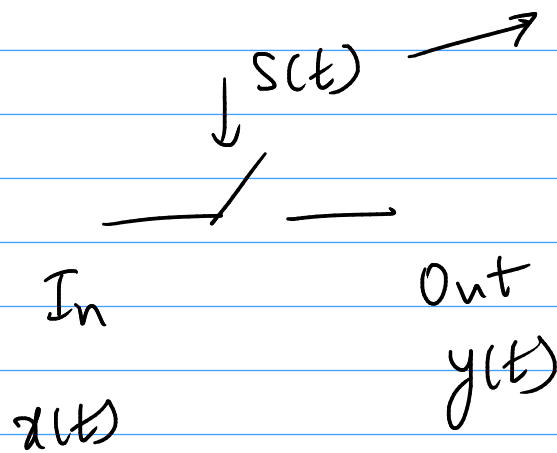

periodic signal  
switching @  $\omega_{LO}$

LPTV analysis


\*  $S(t + T_{LO}) = S(t)$

\* Linearity is valid

\*  $L_0$  is ideal

\*  $Z_s$  &  $Z_L$  connected

to LPTV mixer

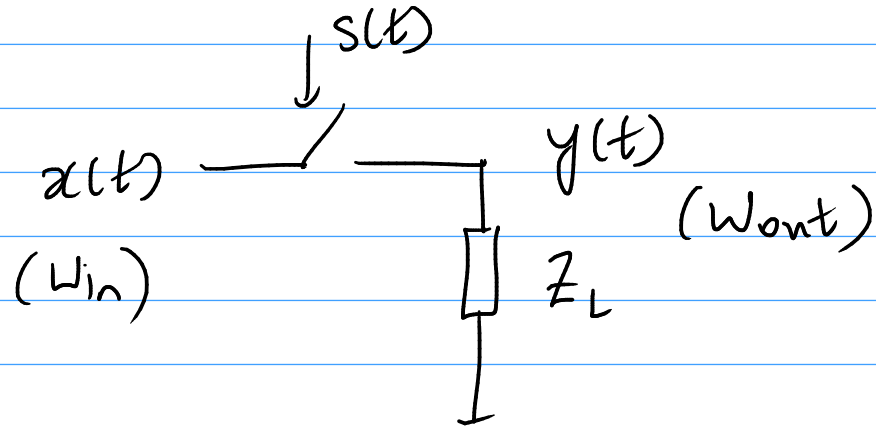

$$s(t) = \sum_{k=-\infty}^{\infty} s_k e^{jk\omega_0 t}$$

$$y(t) = x(t) \cdot s(t)$$


$$Y(\omega_{out}) = \sum_k s_k X(\omega_{in} - k\omega_0)$$

$$\omega_{out} = \omega_{in} + k\omega_0$$

$$R_x : k = -1$$

$$T_x : k = +1$$


Conversion gain =  $S_k$

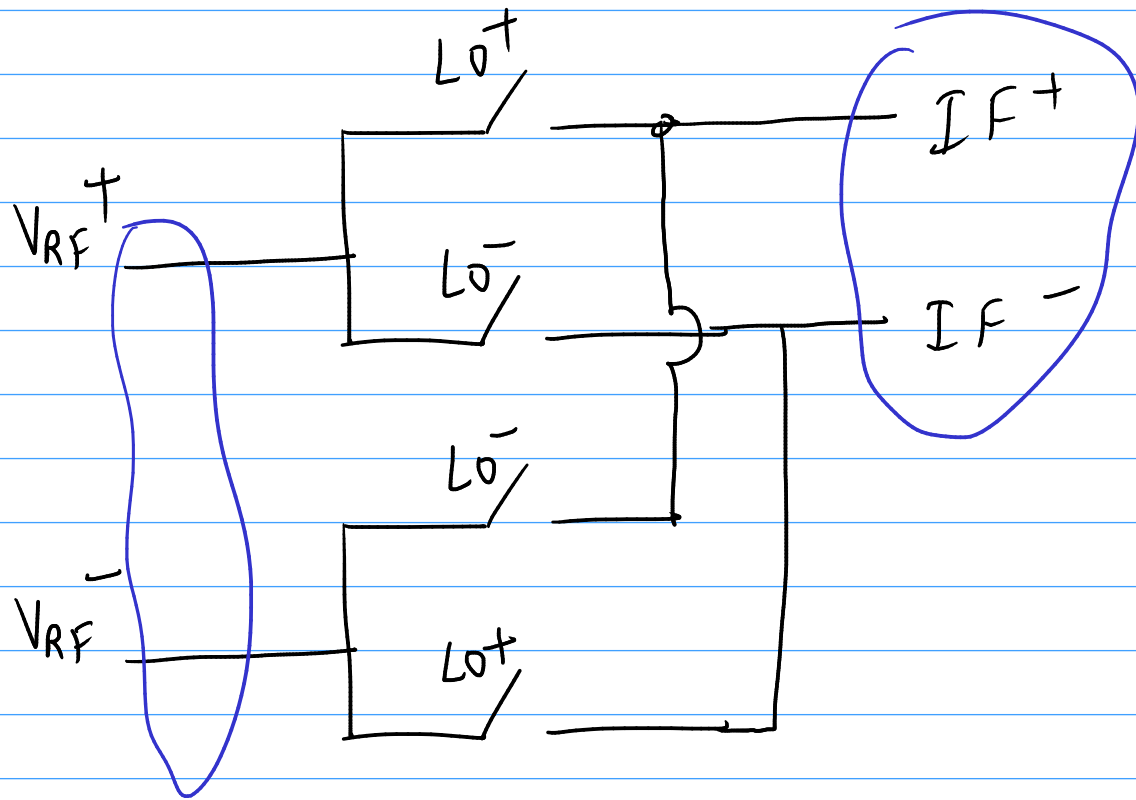

$$S(t) = \begin{cases} +1 \\ -1 \end{cases}$$

$$S_k = \begin{cases} \frac{2}{\pi k} & \text{odd } k \\ 0 & \text{even } k \end{cases}$$


Voltage mode Passive Mixer

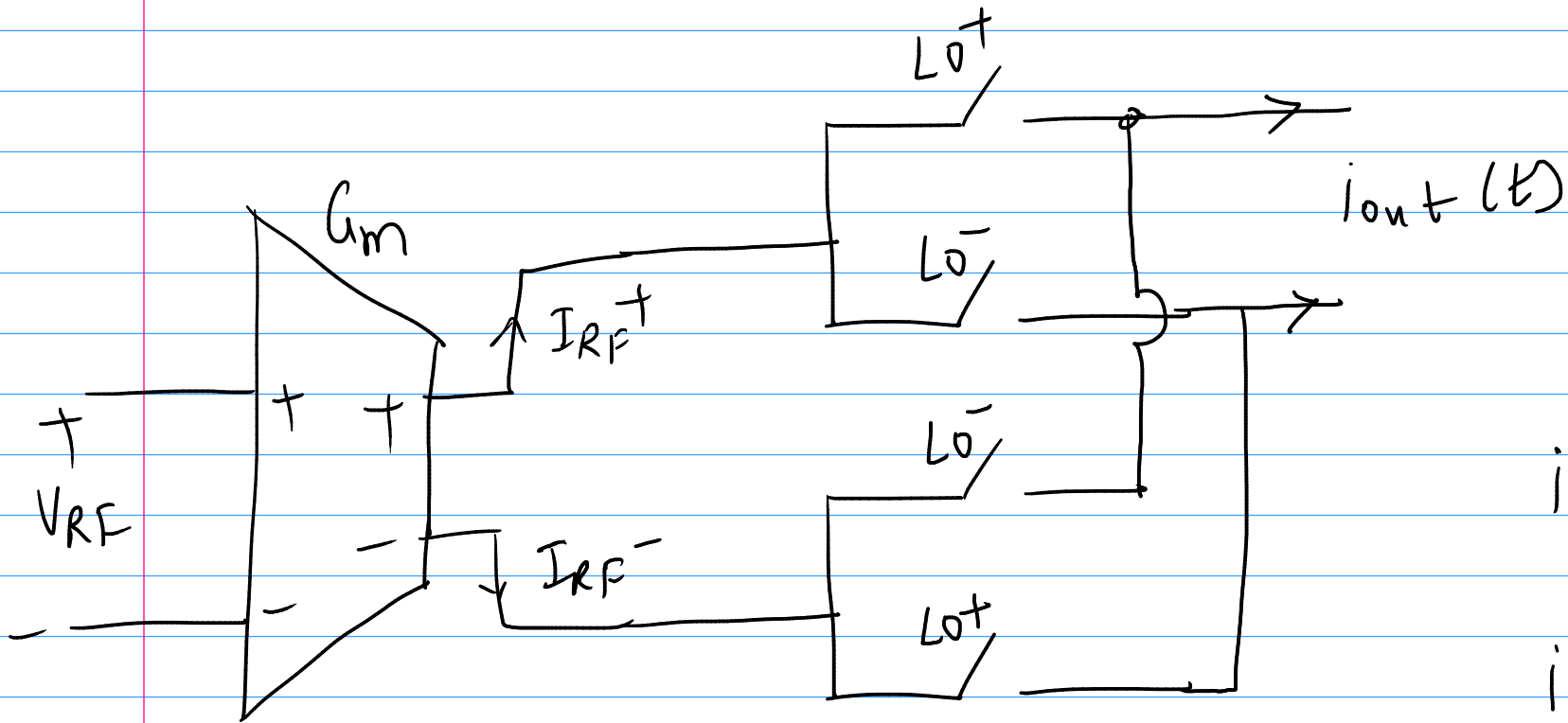

$$i_{RF}(t) = G_m V_{RF}(t)$$


$$i_{out}(t) = S(t) i_{RF}(t)$$

Current Mode Passive Mixer

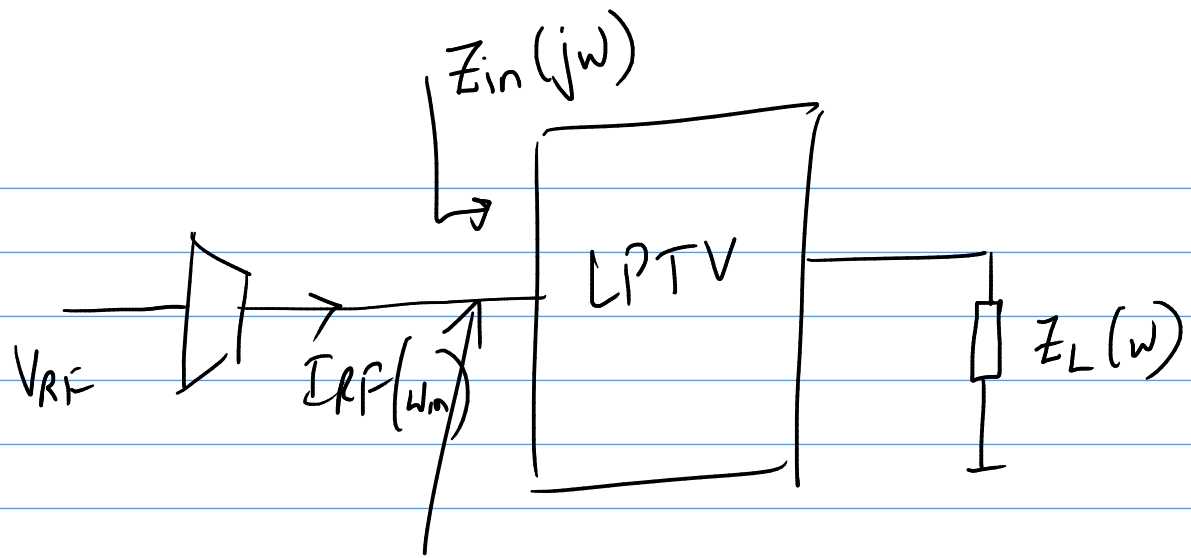


$$Y_{in}(\omega_{in}) = \frac{I_{RF}(\omega_{in})}{V_{RF}(\omega_{in})}$$
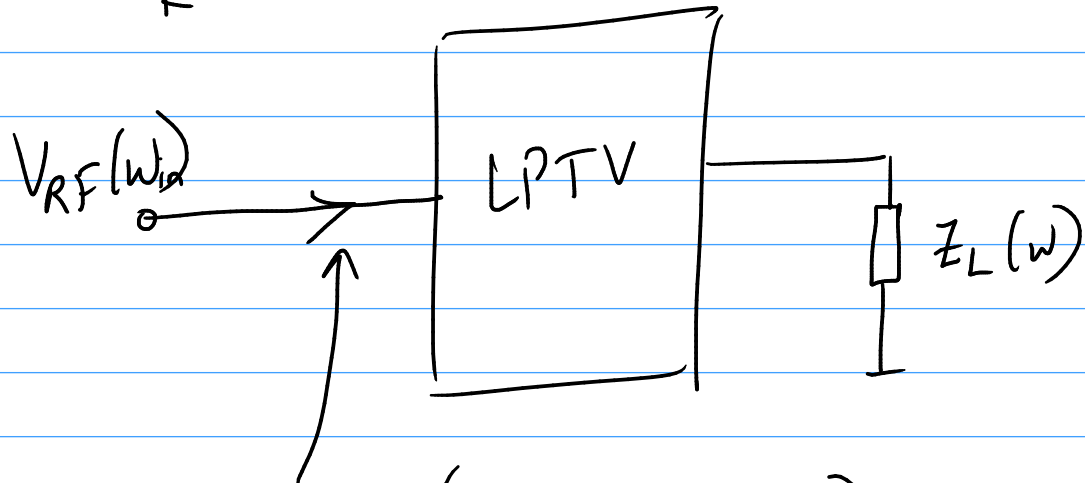
$$\sum_k V_{RF}(\omega_{in} - k\omega_{L0})$$



$$Z_{in}(\omega_{in}) = \frac{V_{RF}(\omega_{in})}{I_{RF}(\omega_{in})}$$
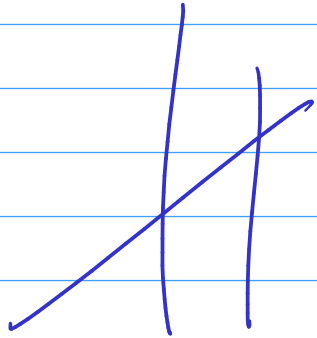
$$\sum_k I_{RF}(\omega_{in} - k\omega_{L0})$$




Noise

$$S_y (W_{out}) = \sum_k |S_k|^2 \cdot S_x (W_{in} - kW_0)$$

Noise Folding

$$F = \frac{\sum_k |S_k|^2}{|S_1|^2} = \frac{\pi^2}{4}$$

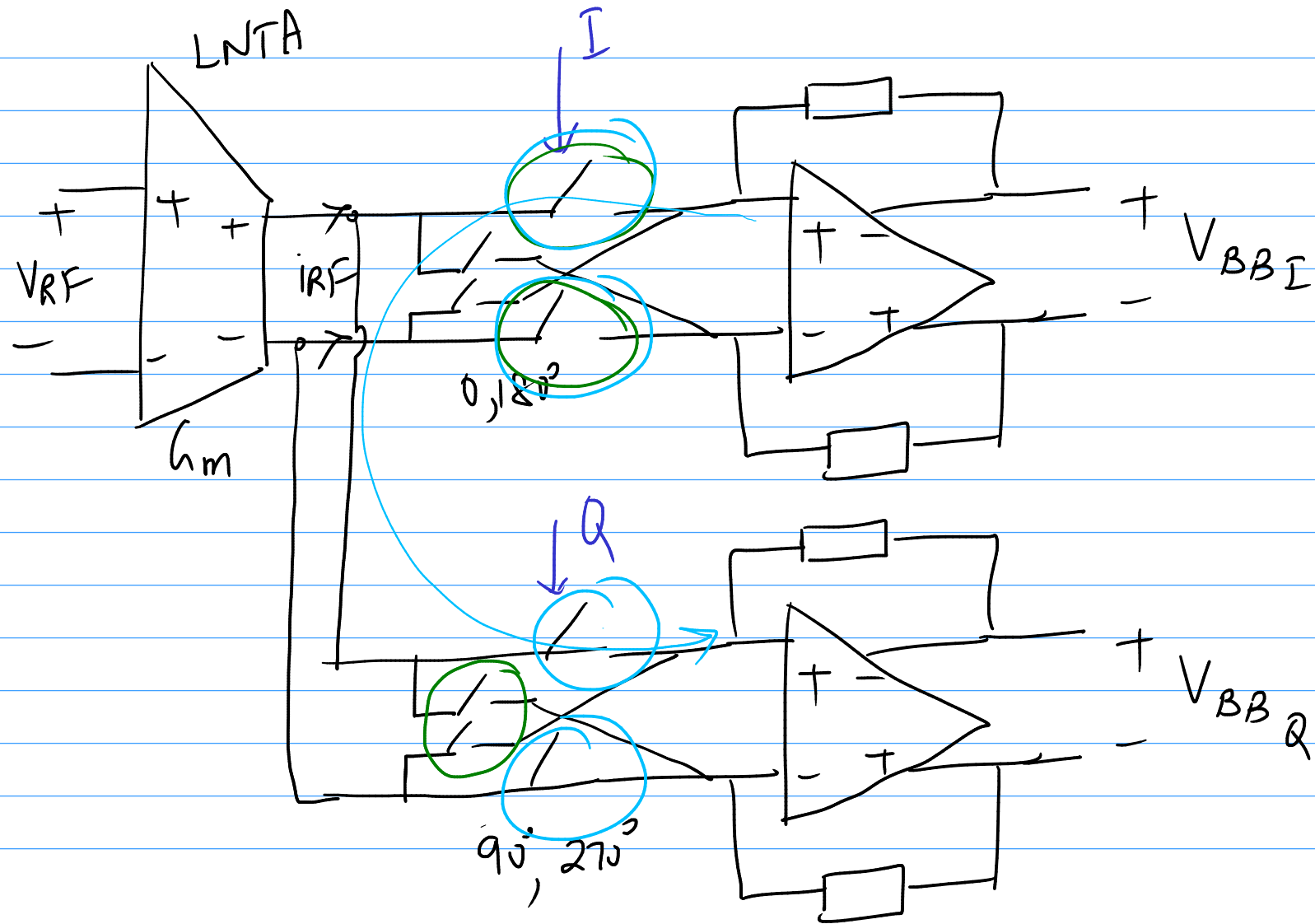

# RF Simulation


DC op pt  
AC Small-signal  
Noise     ")  
transient large signal


} Analog Sims

S-parameter     small signal

PSS ← periodic steady state

HB ← Harmonic Balance

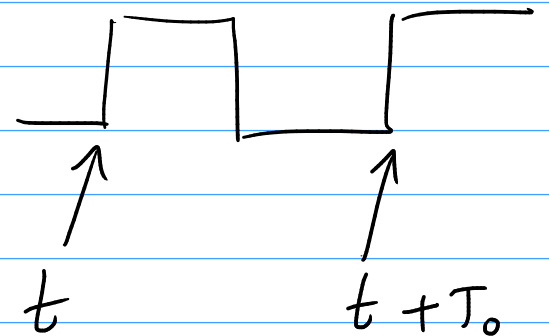

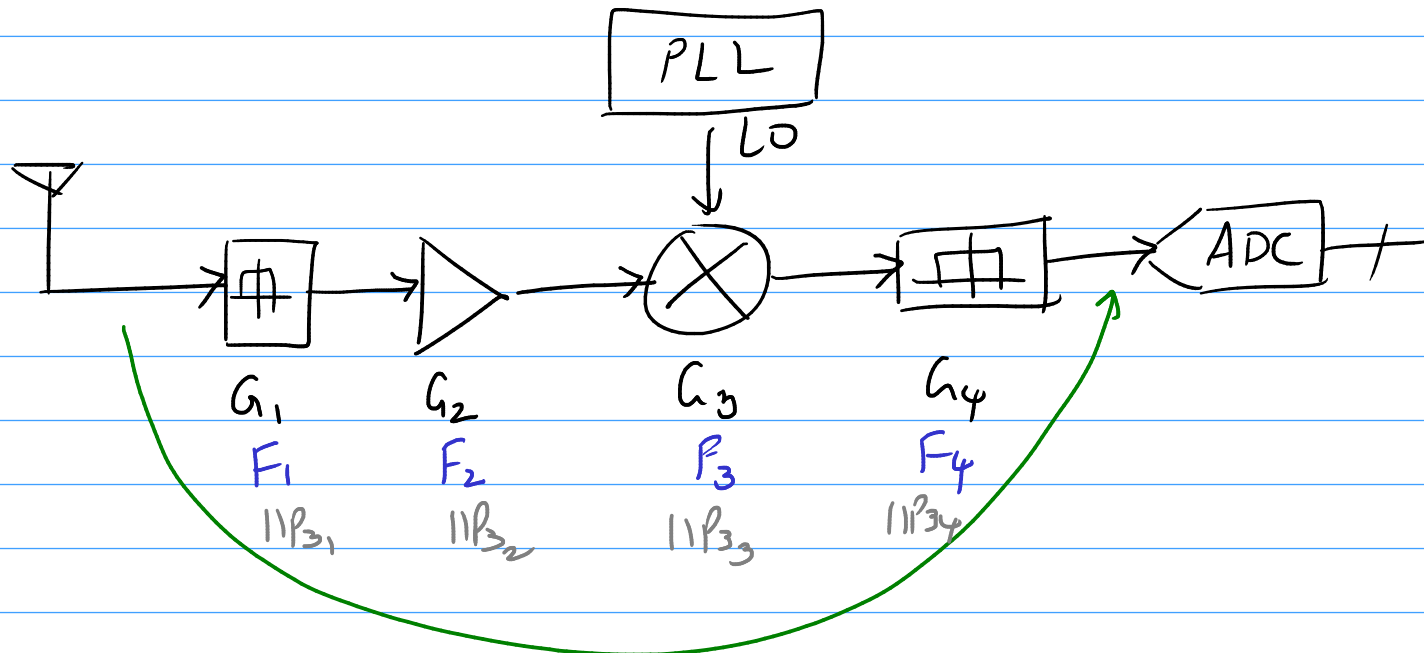


Overall gain =  $G_1 + G_2 + G_3 + G_4$  (all in dB)

$G = ?$

Overall NF = ?

Overall  $1IP_3$  or  $P_{1dB}$  = ?

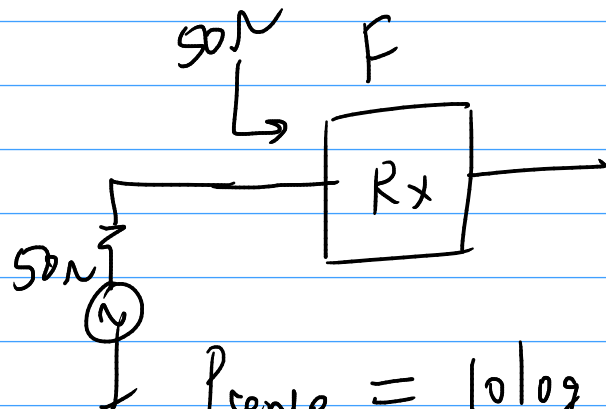
$P_{\text{sense}}$  = Sensitivity of  $R_x \equiv$  lowest  $P_{\text{in}}$  @  $R_x$  input  
 that can be demodulated  
 with a specific desired BER  
 (i.e.  $\text{SNR}_{\text{min}}$ )



available noise power  $\approx kTB$

$$P_{\text{sense.}} = 10 \log_{10}(kT) + 10 \log_{10}(B) + NF_{\text{dB}} + \text{SNR}_{\text{min}} (\text{dB})$$

in dBm

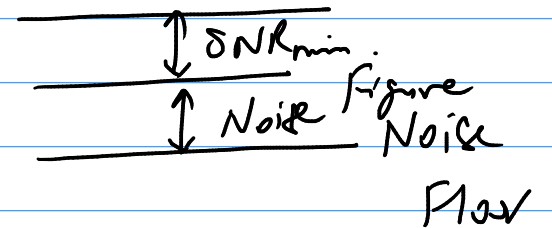

$$P_{\text{sens.}} = -174 \text{ dBm/Hz} + 10 \log(B) + NF + SNR_{\text{min.}}$$

## WiFi 802.11ag system design example

Ref: Chap 13 in RF Microelectronics by B. Razavi 2<sup>nd</sup> ed.

gain, NF, IIP3/P<sub>1dB</sub>

↓  
gain range (AGC)

1) NF 802.11ag std. specifies: Packet Error Rate = 10%.

↓  
BER =  $10^{-5}$

↓  
(64 QAM) SNR = 18.3 dB

Tx BB pulse shaping  $\rightarrow$  BW = 16.6 MHz

$$P_{\text{sens.}} = -174 \text{ dBm/Hz} + \text{NF} + 10 \log(16.6 \text{ MHz}) + 18.3 \text{ dB}$$

@ 52 Mbps  $\Rightarrow$   $P_{\text{sens.}} = -65 \text{ dBm}$  from standard

$$\text{NF} = 18.4 \text{ dB}$$

$\downarrow$  Non-idealities / Margins / Competitiveness

$$\text{NF} = 10 \text{ dB}$$

@ 6 Mbps  $\Rightarrow$   $P_{\text{sense}} = -82 \text{ dBm}$  from standard

$$\hookrightarrow \text{NF} = 10 \text{ dB}$$

2) Non linearity

(i) \* 52 sub channels  $\rightarrow$  PAPR = 9 dB


Standard specifies  $P_{in(max)} = -30\text{dBm}$

Peak input power =  $-21\text{dBm}$

Envelope variation due to pulse shaping  $\sim 2\text{dB}$

$P_{1dB} = -19\text{dBm} \Rightarrow 1P_3 \approx -9\text{dBm}$

(ii)  $1P_3$  due to intermodulation

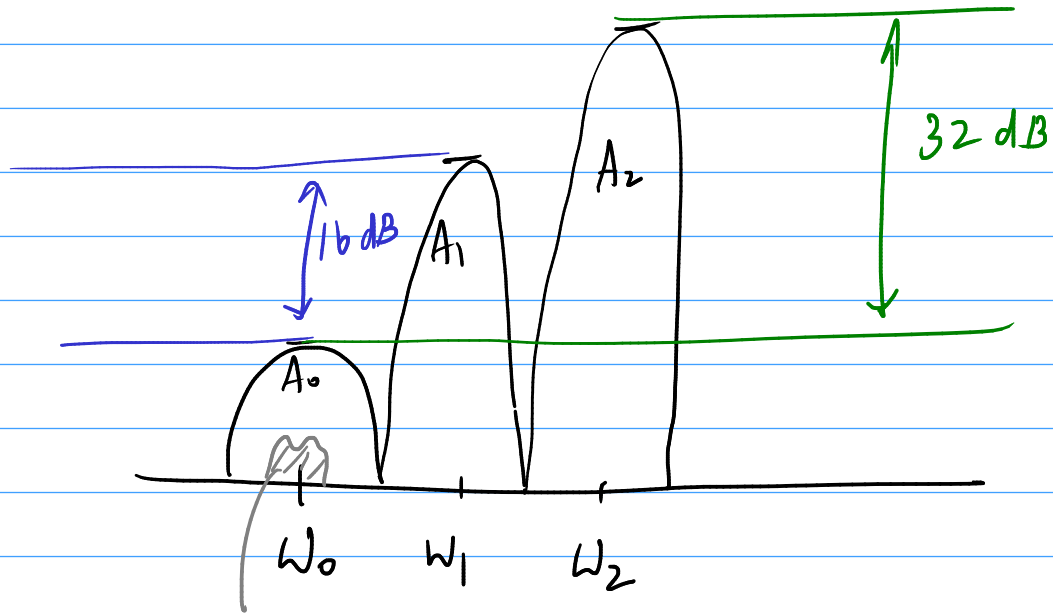

$IM_3$  of  $\omega_1$  &  $\omega_2$

$$y(t) = \alpha_1 x(t) + \alpha_2 x^2(t) + \alpha_3 x^3(t)$$

$$IM_3 = \frac{3 \alpha_3 A_1^2 A_2}{4}$$

Desired signal =  $\alpha_1 A_0$

Specified by  
standard

$$P_{in_{min}} = P_{sense} + 3dB$$

$$P_{\text{sense}} = -82 \text{ dBm} \quad (\text{BPSK})$$

$$\text{SNR} = 4-5 \text{ dB}$$

$I_{M_3}$  should lie 15dB below desired signal


$$20 \log \left( \frac{3 \alpha_3 A_1^2 A_2}{4 \alpha_1 A_0} \right) = -15 \text{ dB}$$

$$20 \log \left( \frac{3 \alpha_3}{4 \alpha_1} \right) = -15 \text{ dB} - 40 \log A_1 - 20 \log A_2 + 20 \log A_0$$

$$A \Leftrightarrow -79 \text{ dBm}, \quad A_1 \Leftrightarrow -63 \text{ dBm}, \quad A_2 \Leftrightarrow -47 \text{ dBm}$$

$$20 \log \left( \frac{3\alpha_3}{4\alpha_1} \right) = +79 \text{ dBm}$$

$$|IP_3|_{\text{dBm}} = 20 \log \sqrt{\left| \frac{4\alpha_1}{3\alpha_3} \right|} = -39.5 \text{ dBm}$$

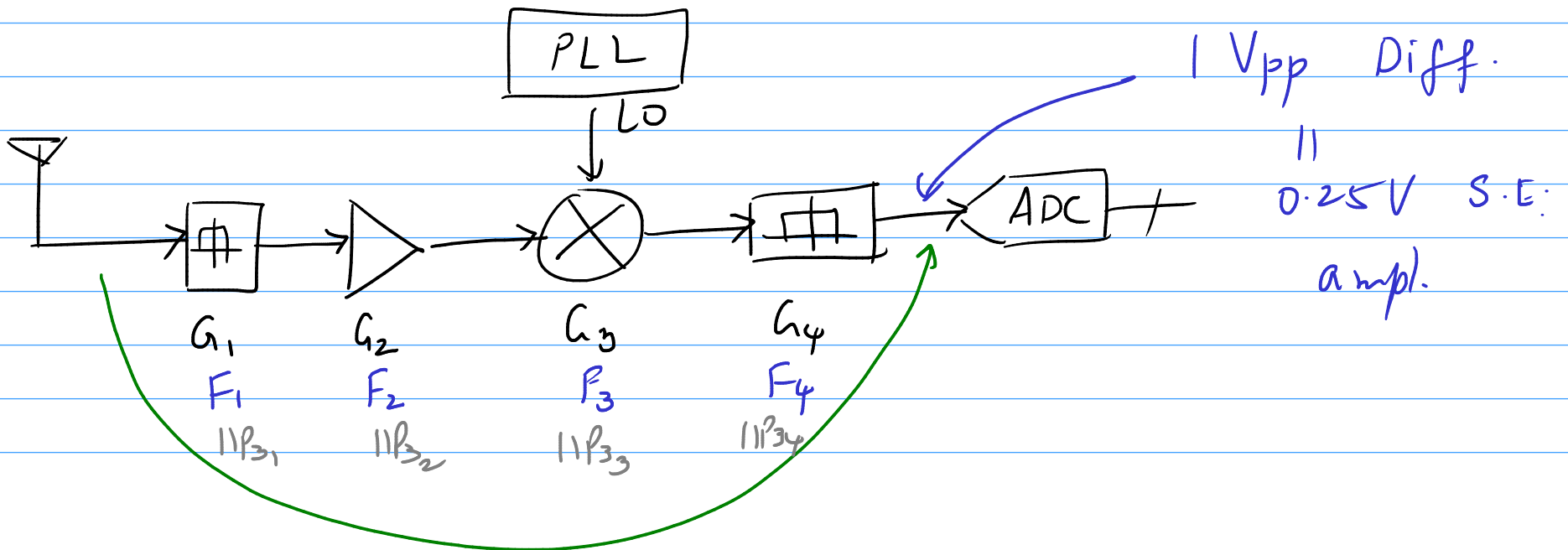

$$\left. \begin{array}{l} P_{in} = -82 \text{ dBm} \quad 6 \text{ Mbps} \\ P_{in} = -65 \text{ dBm} \quad 54 \text{ Mbps} \end{array} \right\}$$

$$NF = 10 \text{ dB}$$

$$V_{out} = \underbrace{1 V_{p-p}}_{+4 \text{ dBm @ } 50 \Omega}$$

|       |         | $P_{sens.}$ | PAPR | Env. Var. |
|-------|---------|-------------|------|-----------|
| 64QAM | 54 Mbps | -65         | 9    | 2         |
| BPSK  | 6 Mbps  | -82         | 2    | 0         |



$$\underline{P_{sens.} = -82 \text{ dBm}}$$

$$R_x \text{ gain} = +84 \text{ dB}$$

$$P_{sens.} = -65 \text{ dBm}$$

$$R_x \text{ gain} = +4 - (-65 + 9 + 2) = 58 \text{ dB}$$


Max Gain of Rx

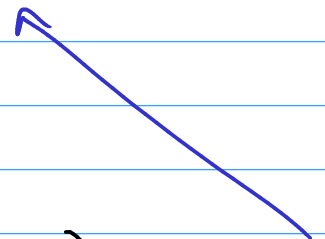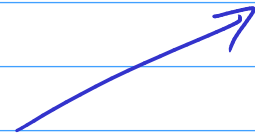

When  $P_{in\ max} = -30\text{ dBm}$

$R_x\ \text{gain} = 32\text{ dB}$  for BPSK

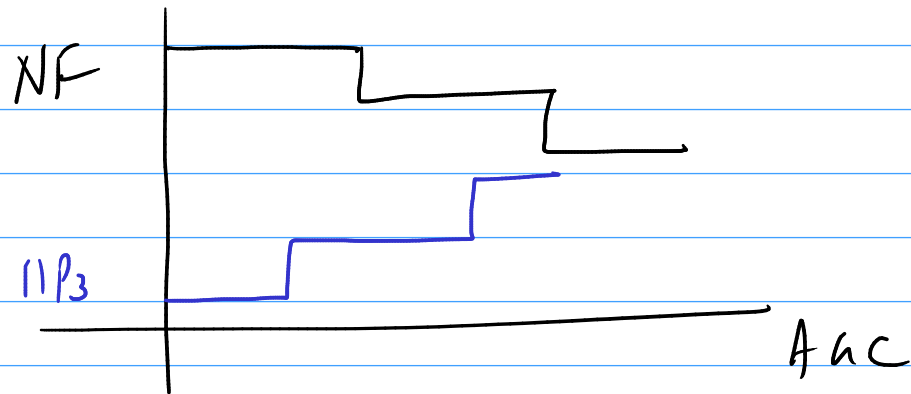$R_x\ \text{gain} = 23\text{ dB}$  for 64 QAM



Tx

