
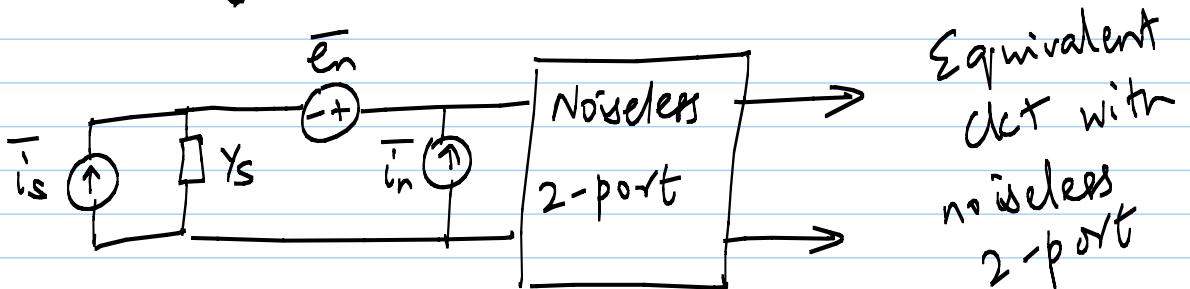

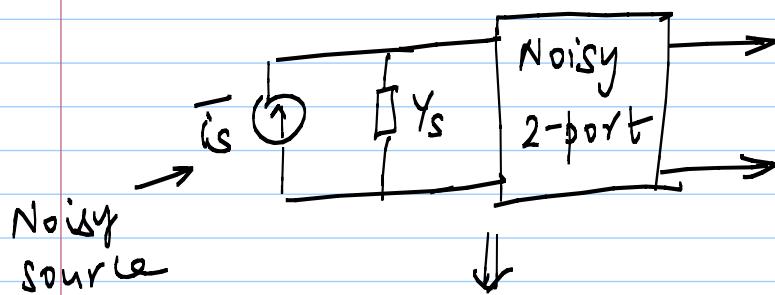
# Lecture 14 : Classical 2-port Noise Theory



\* OC & SC cases  $\rightarrow$  you need both  $e_n$  &  $i_n$

\* In general,  $e_n$  and  $i_n$  are correlated

\* actual ckt may have no physical input noise current

## Noise Factor


\*  $F = \frac{\text{total output noise power}}{\text{output noise due to input source only}}$

\* by convention, source is at a temp of 290K.

\*  $F$  is a measure of degradation in SNR

due to a system { degradation in SNR  $\uparrow \Rightarrow F \uparrow$ }

\* If system adds no noise,  $F = 1$

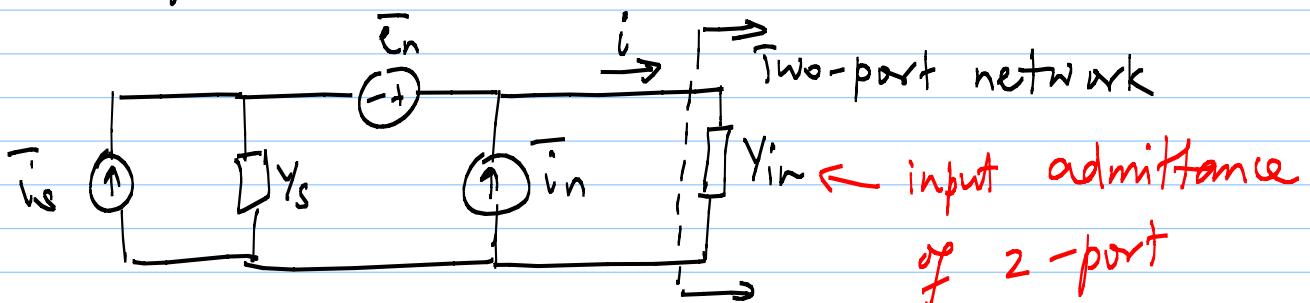

$$i_s = i_n \cdot \left( \frac{Y_{in}}{Y_s + Y_{in}} \right) + (i_n + e_n Y_s) \cdot \left( \frac{Y_{in}}{Y_{in} + Y_s} \right)$$

\*  $\bar{i}_s$  is assumed to be uncorrelated with  $\bar{e}_n$  &  $\bar{i}_n$

$$F = \frac{\bar{i}_s^2 \left( \frac{Y_{in}}{Y_s + Y_{in}} \right)^2 + |\bar{i}_n + \bar{e}_n Y_s|^2 \cdot \left( \frac{Y_{in}}{Y_s + Y_{in}} \right)^2}{\bar{i}_s^2 \cdot \left( \frac{Y_{in}}{Y_s + Y_{in}} \right)^2}$$

$$= 1 + \frac{|\bar{i}_n + \bar{e}_n Y_s|^2}{\bar{i}_s^2}$$

Let  $\bar{i}_{in} = \bar{i}_c + \bar{i}_n$

$\bar{i}_c$  is correlated with  $\bar{e}_n$

$$\Rightarrow \bar{i}_c = Y_c \cdot \bar{e}_n ; Y_c = \text{correlation admittance}$$

$i_n$  is uncorrelated with  $\bar{e}_n$

$$\Rightarrow F = 1 + \frac{|\bar{i}_{in} + (Y_c + Y_s) \bar{e}_n|^2}{\bar{i}_s^2}$$

$$= 1 + \frac{\bar{i}_{in}^2 + |Y_c + Y_s|^2 \bar{e}_n^2}{\bar{i}_s^2}$$

) because  $\bar{i}_n$  is un-correlated with  $\bar{e}_n$

\* Next, we define each of these 3 independent noise sources as an equivalent resistance or conductance and their associated thermal noise

Sources :

$$R_N = \frac{\bar{e}_n^2}{4kT\Delta f}$$

$$G_n = \frac{\bar{i}_n^2}{4kT\Delta f}$$

$$G_s = \frac{\bar{i}_s^2}{4kT\Delta f}$$

$$\Rightarrow F = 1 + \frac{G_u + [Y_c + Y_s]^2 \cdot R_N}{G_s}$$

Now, let  $Y_c = G_c + jB_c$  and  $Y_s = G_s + jB_s$

$$\Rightarrow F = 1 + \frac{G_u + [(G_c + G_s)^2 + (B_c + B_s)^2] \cdot R_N}{G_s}$$

\* Noise of any 2-port can be characterized by 4 parameters :  $\{R_N, G_u, G_c, B_c\}$

Conditions that minimize  $F$  (ie optimum source admittance) :

$$1) \frac{\partial F}{\partial B_s} = 0 \Rightarrow 2(B_c + B_s) \cdot R_N = 0$$

$$\Rightarrow B_s = -B_c = B_{opt.} \quad \leftarrow \text{Design condition for } F_{min.}$$

$$2) \frac{\partial F}{\partial G_s} = 0$$

$$\Rightarrow \frac{2(G_c + G_s)R_N}{G_s} - \frac{G_u + [(G_c + G_s)^2 + (B_c + B_s)^2] R_N}{G_s^2} = 0$$

$$\Rightarrow G_s^2 = \frac{G_u}{R_N} + G_c^2$$

$$\Rightarrow G_s = \sqrt{\frac{G_u}{R_N} + G_c^2} = G_{opt.} \quad \leftarrow \text{Design condition for } F_{min.}$$

$F_{min.}$  is given by :

$$F_{min.} = 1 + \frac{G_u + [(G_c + G_{opt.})^2 + (B_c + B_{opt.})^2] R_N}{G_{opt.}}$$

$$\text{also, } G_u = (G_{opt}^2 - G_c^2) \cdot R_N$$

$$\therefore F_{min} = 1 + \frac{G_{opt}^2 R_N - G_c^2 R_N + G_c^2 R_N + 2G_c G_{opt} R_N + G_{opt}^2 R_N}{G_{opt}}$$

$$F_{min} = 1 + 2 R_N (G_{opt} + G_c)$$


$$\text{or } F_{min} = 1 + 2 R_N \left[ \sqrt{\frac{G_u}{R_N}} + G_c + G_c \right]$$

### Noise Circles

Recall :

$$F = 1 + \frac{G_u + [(G_c + G_s)^2 + (B_c + B_s)^2] R_N}{G_s}$$
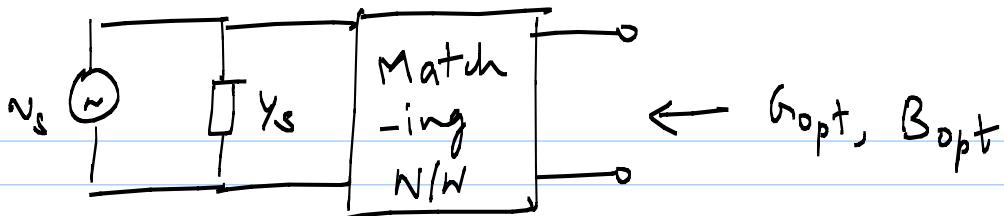
$$G_{opt}^2 = \frac{G_u}{R_N} + G_c^2 ; \quad B_c = -B_{opt}$$



$$G_u = R_N (G_{opt}^2 - G_c^2)$$

$$\Rightarrow F = 1 + \frac{[G_{opt}^2 - G_c^2 + (G_c + G_s)^2] R_N + (B_s - B_{opt})^2 R_N}{G_s}$$


$$= 1 + \frac{[G_{opt}^2 - G_c^2 + G_c^2 + 2G_c G_s + G_s^2] R_N + (B_s - B_{opt})^2 R_N}{G_s}$$

add & subtract  $2G_s G_{opt}$  to 1st term of numerator

$$\Rightarrow F = 1 + \frac{2(G_c + G_{opt}) \cdot G_s \cdot R_N + [(G_s - G_{opt})^2 + (B_s - B_{opt})^2] R_N}{G_s}$$

$$\Rightarrow F = F_{\min.} + \left[ (G_s - G_{\text{opt}})^2 + (B_s - B_{\text{opt}})^2 \right] \cdot \frac{R_N}{G_s}$$

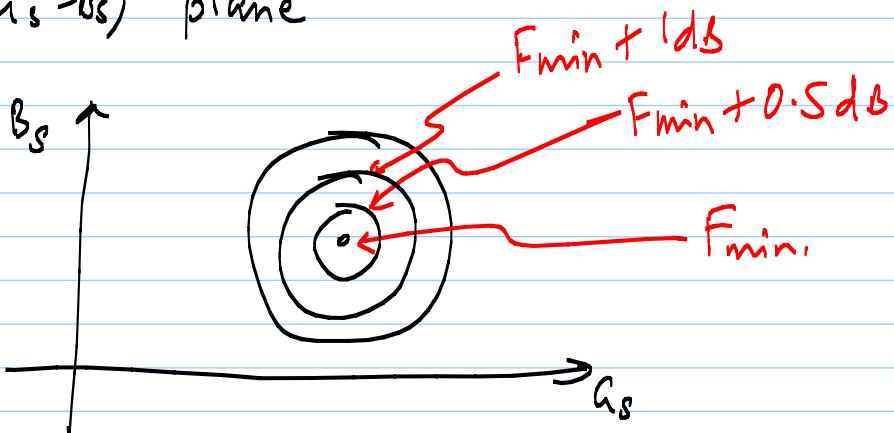- \* these are circles in the source admittance ( $G_s - B_s$ ) plane



- \* Circles of constant  $F$  in  $G_s - B_s$  plane
- \* Also circles on a Smith chart (mapping is a bilinear transformation)

- \* Conditions for  $F_{\min.}$  are slightly different from those for maximum power transfer!

→ Tradeoff between max gain & min. noise

- \* Noise Figure ≡ noise factor in dB

$$NF = 10 \log_{10} F$$

- \* Noise Temperature  $T_N$

≡ increase in temperature required of  $\gamma_s$  for it to account for all of the output noise at the ref. temp. ( $= 290\text{K}$ )

$$F = 1 + \frac{T_N}{T_{\text{ref}}} \Rightarrow T_N = T_{\text{ref}} \cdot (F - 1)$$

→ a 2-port that adds no noise has  $T_N = 0\text{K}$

- $T_N$  is useful for cascaded amplifiers and those whose  $F$  is close to 1 (ie  $NF \approx 0dB$ )
- $T_N$  offers a higher resolution description of noise performance