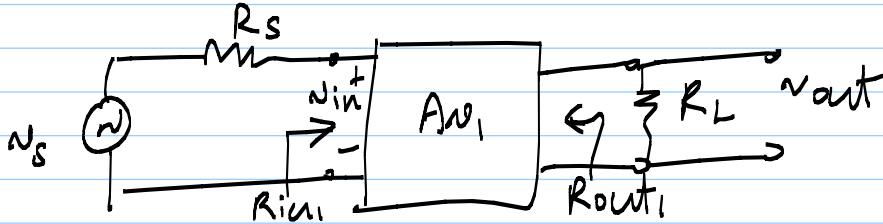


Lecture 15: NF (contd.)

Available power gain = A_p

$A_p \equiv \frac{\text{available Power (under matched condition)}}{\text{available source power (matched)}}$



$$R_s = R_{in1}; R_{out1} = R_L$$

$$v_{in} = v_s \cdot \frac{R_{in1}}{R_s + R_{in1}} = \frac{v_s}{2}$$


$$P_{av,s} = \frac{(v_s/2)^2}{R_s} = \frac{v_s^2}{4R_s}$$

$$v_{out} = v_{in} \cdot A_{v1} \cdot \left(\frac{R_L}{R_L + R_{out1}} \right) = v_s \left(\frac{R_{in1}}{R_s + R_{in1}} \right) \cdot A_{v1} \cdot \frac{1}{2}$$

$$\text{Power}_{av} = v_s^2 \left(\frac{R_{in1}}{R_s + R_{in1}} \right)^2 \cdot A_{v1}^2 \cdot \frac{1}{4R_{out1}}$$

$$\Rightarrow A_p = \left(\frac{R_{in1}}{R_s + R_{in1}} \right)^2 \cdot A_{v1}^2 \cdot \frac{R_s}{R_{out1}}$$

Noise Figure of Cascaded Systems

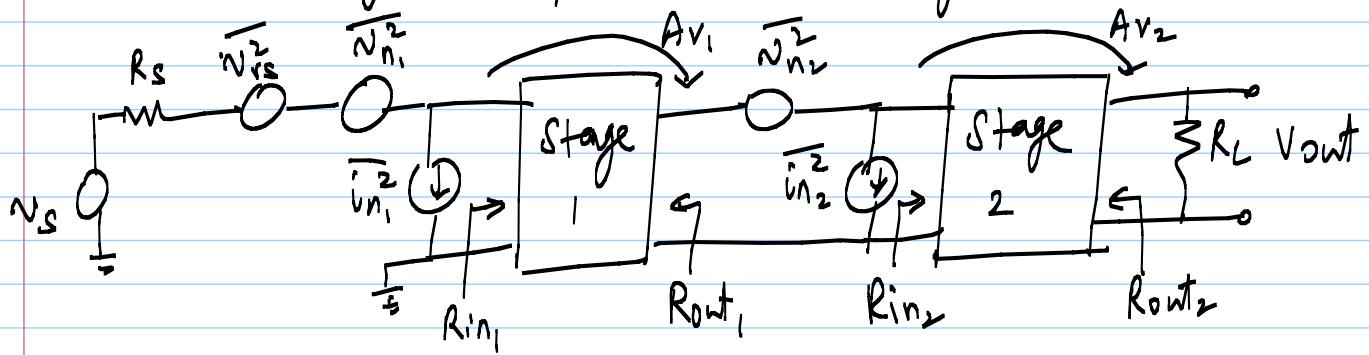

$A_{V1}, A_{V2} \rightarrow$ unloaded voltage gains of stage 1 & 2

* Noise power at input to stage 1 :

$$\overline{N_{n,in1}^2} = \left[\overline{i_{n1}} (R_s || R_{in1}) + \overline{N_{n1}} \left(\frac{R_{in1}}{R_s + R_{in1}} \right)^2 \right] + \overline{v_{Rs}^2} \left(\frac{R_{in1}}{R_s + R_{in1}} \right)^2$$

accounts for correlation between i_{n1} & $\overline{N_{n1}}$

* Noise power at input to stage 2 :

$$\overline{N_{n,in2}^2} = \overline{N_{n,in1}^2} \cdot A_{V1}^2 \cdot \left(\frac{R_{in2}}{R_{out1} + R_{in2}} \right)^2 + \left[\overline{i_{n2}} (R_{out1} || R_{in2}) + \overline{N_{n2}} \left(\frac{R_{in2}}{R_{in2} + R_{out1}} \right)^2 \right]$$

contribution from 1st stage

* Noise power at output of stage 2:

$$\overline{N_{\text{out}}^2} = A_{V2}^2 \cdot \left(\frac{R_L}{R_{\text{out}_2} + R_L} \right)^2 \cdot \overline{n_{n_2, \text{in}_2}^2}$$

* Total voltage gain:

$$A_{V,\text{tot.}} = \frac{R_{\text{in}_1}}{R_s + R_{\text{in}_1}} \cdot A_{V1} \cdot \frac{R_{\text{in}_2}}{R_{\text{out}_1} + R_{\text{in}_2}} \cdot A_{V2} \cdot \frac{R_L}{R_L + R_{\text{out}_2}}$$

* Overall noise factor:

$$F = \frac{\text{total noise power at output}}{\text{output noise due to } R_s \text{ only}} = \\ = \frac{\overline{N_{\text{out}}^2}}{A_{V,\text{tot.}}^2 \cdot 4kT R_s}$$

After a bunch of algebra:

$$F = 1 + \frac{|n_{n_1} + i_{n_1, R_s}|^2}{4kT R_s} \quad \leftarrow F_{1,R_s} = \text{noise factor of stage 1 w.r.t. } R_s$$

$$+ \frac{|n_{n_2} + i_{n_2, R_{\text{out}_1}}|^2}{A_{V1}^2} \cdot \frac{1}{\left(\frac{R_{\text{in}_1}}{R_s + R_{\text{in}_1}} \right)^2} \cdot \frac{1}{4kT R_s}$$

analyse further

* Noise factor of Stage 2 w.r.t. source impedance R_{out_1} is

$$F_{2, R_{\text{out}_1}} = 1 + \frac{|i_{n_2, R_{\text{out}_1}} + n_{n_2}|^2}{4kT R_{\text{out}_1}}$$

* the second term in expression for overall F is

$$\frac{\left|Nn_2 + i n_2 R_{out,1}\right|^2}{4kT R_s} \cdot \frac{1}{\left(\frac{R_{in,1}}{R_s + R_{in,1}}\right)^2} \cdot \frac{1}{A_{V1}^2} \cdot \frac{R_s / R_{out,1}}{R_s / R_{out,1}}$$

$\uparrow A_p$

$$= \frac{\left|Nn_2 + i n_2 R_{out,1}\right|^2}{4kT R_{out,1}} \cdot \frac{1}{A_p} = (F_{2,R_{out,1}} - 1) \cdot \frac{1}{A_p}$$

$\Rightarrow F = F_{1,R_s} + \frac{F_{2,R_{out,1}} - 1}{A_p}$

In general for m stages,

$$F_{tot.} = 1 + (F_1 - 1) + \frac{F_2 - 1}{A_{p1}} + \dots + \frac{F_m - 1}{A_{p1} \cdots A_{p(m-1)}}$$


where F_i = F of i^{th} stage w.r.t. source impedance driving that stage

FRIIS EQUATION

* Noise of front-end stages is most significant

Noise Factor of Lossy Circuits:

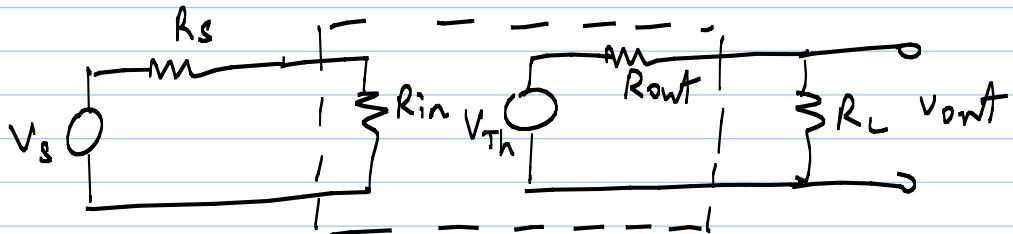
* off-chip passive filter \rightarrow finite in-band loss
 \rightarrow matched to 50Ω



$$\text{Available power loss } (L) = \frac{P_{in}}{P_{out}}$$

assume $R_{in} = R_s$ & $R_{out} = R_L$
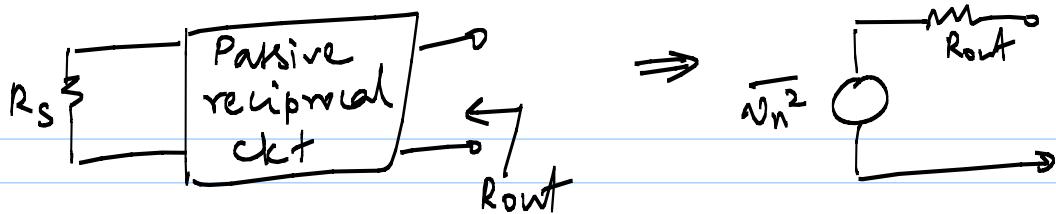
$$\Rightarrow L = \frac{(V_s^2 / 4R_s)}{(V_{th}^2 / 4R_{out})} = \frac{V_s^2}{V_{th}^2} \cdot \frac{R_{out}}{R_s}$$



It can be shown that $n_o^2 = 4kT R_{out}$ if
 Noise power at output:


$$\overline{n_o^2}_{out} = 4kT R_{out} \left(\frac{R_L}{R_L + R_{out}} \right)^2$$

$$A_V = \frac{V_{th}}{V_s} \cdot \frac{R_L}{R_L + R_{out}}$$

$$F = \frac{\overline{n_o^2}_{out}}{\overline{n_o^2}_{R_s} \cdot A_V^2} = \frac{4kT R_{out} \left(\frac{R_L}{R_L + R_{out}} \right)^2}{4kT R_s \cdot \frac{V_{th}^2}{V_s^2} \cdot \left(\frac{R_L}{R_L + R_{out}} \right)^2}$$

$$\Rightarrow F = \frac{V_s^2}{N_{th}^2} \cdot \frac{R_{out}}{R_s} = L$$

e.g.

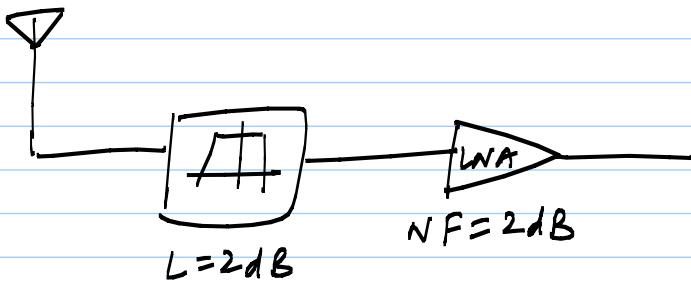


$$F_{tot.} = F_{filt.} + \frac{F_{LNA}-1}{L^{-1}} = L + L \cdot (F_{LNA}-1)$$

$$= L \cdot F_{LNA}$$

$$\Rightarrow NF_{tot.} = L_{dB} + NF_{LNA}$$

overall $NF @ \text{antenna} = NF(\text{LNA}) + L = 4 \text{dB}!$

* Alternative definition of F:

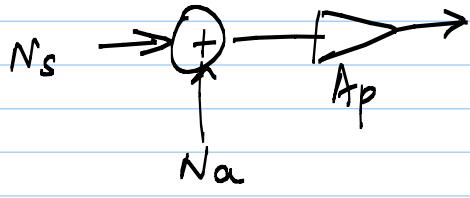

consider an amplifier of available power gain A_p , and input-referred noise power N_a

$$F = \frac{A_p(N_a + N_s)}{A_p \cdot N_s} = 1 + \frac{N_a}{N_s}$$

let signal power be S


$$SNR @ \text{input} = SNR_{in} = \frac{S}{N_s}$$

$$SNR @ \text{output} = SNR_{out} = \frac{A_p \cdot S}{A_p \cdot (N_a + N_s)}$$

$$\frac{SNR_{in}}{SNR_{out}} = \frac{S/N_s}{A_p S / A_p (N_a + N_s)} = \frac{N_a + N_s}{N_a} = F$$

$$\Rightarrow F = \frac{SNR_{in}}{SNR_{out}}$$

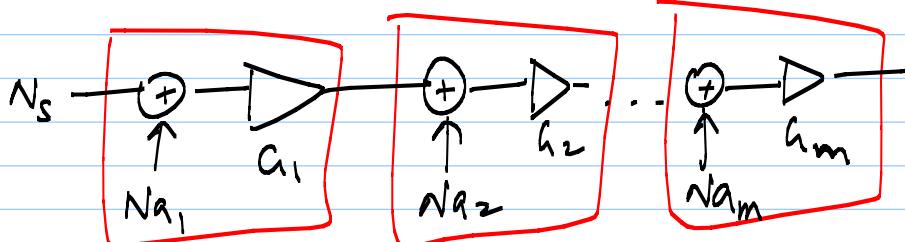* Alternative Derivation of Friis Equation:



* assume all impedances are equal (& matched)
+ $A_i = A_p$

$$\begin{aligned} \text{Total output noise power} &= (N_s + N_a) \cdot h_1 \cdot h_2 \cdots h_m \\ &\quad + (N_a) \cdot h_2 \cdots h_m \\ &\quad + \cdots + N_a \cdot h_m \end{aligned}$$

noise power due to source alone

$$= (N_s) \cdot h_1 \cdot h_2 \cdots h_m$$

$$\Rightarrow F = 1 + \frac{N_a}{N_s} + \frac{N_a}{N_s \cdot h_1} + \cdots + \frac{N_a}{N_s \cdot h_1 \cdot h_2 \cdots h_{m-1}}$$

$$F = 1 + (F_1 - 1) + \frac{F_2 - 1}{h_1} + \frac{F_3 - 1}{h_1 \cdot h_2} + \cdots + \frac{F_m - 1}{h_1 \cdot h_2 \cdots h_{m-1}}$$