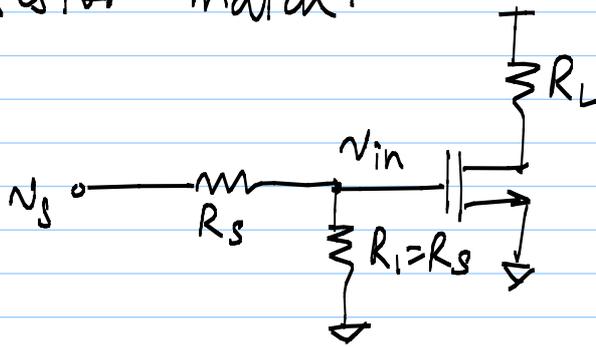


Lecture 17 : LNA design

Input Matching :

1) Resistor match:



* Broad band match

* Attenuates signal before amplifier ($v_{in} = \frac{v_s}{2}$)

* R_i adds its thermal noise

* F can be calculated to be


$$F = 2 + \frac{4\gamma}{\alpha} \cdot \frac{1}{g_m R_s}$$

derivation will be a HW problem

→ ignores gate noise

$$\rightarrow NF = 10 \log_{10} (2 + \alpha) > 3 \text{ dB} !$$

2) Shunt-series amplifier

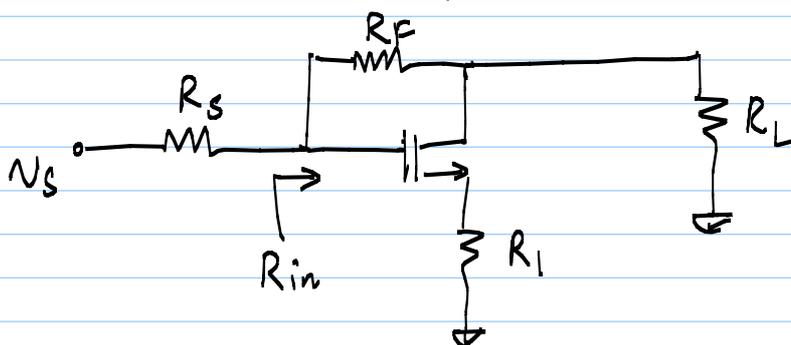


(biasing not shown)

* No attenuation before amplifier

* R_F generates thermal noise (degrades F)

* F still much larger than F_{min} .

3) Common-gate stage

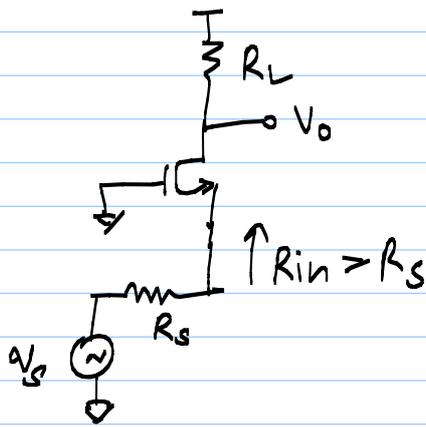


* Broadband match

* $R_{in} = \frac{1}{g_m}$ (neglecting r_{ds}) = 50Ω

→ device size & bias current

* No extra noise sources

Noise factor

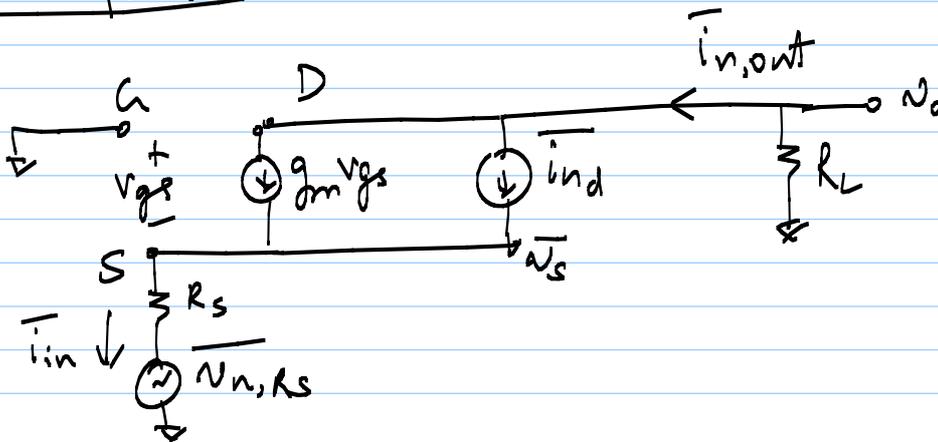

* $\overline{i_{ind}}$ and $\overline{v_{n,R_s}}$ are uncorrelated

→ analyse $\overline{i_{out}}$ for each separately
and add mean-square values

i) $\overline{v_{n,R_s}}$:

$$\overline{i_{out}} = g_m v_{gs} = -g_m \overline{v_s}$$

also, $\overline{v_s} = \overline{v_{n,R_s}} + \overline{i_{in} R_s}$

$$= \overline{v_{n,R_s}} + \overline{i_{in,out}} \cdot R_s$$

$$\frac{-\overline{i_{in,out}}}{g_m} = \overline{v_{n,R_s}} + \overline{i_{in,out}} R_s$$

$$\Rightarrow \overline{i_{in,out}} = \frac{-g_m \overline{v_{n,R_s}}}{1 + g_m R_s}$$

we know that

$$R_{in} = 1/g_m = R_s$$

$$\Rightarrow \overline{i_{n,out}} = \frac{-\overline{N_{n,R_s}}}{2R_s} \Rightarrow \overline{i_{n,out}^2} = \frac{\overline{N_{n,R_s}^2}}{4R_s^2}$$

2) $\overline{i_{n,d}}$:

$$\overline{V_s} = \overline{i_{n,out}} \cdot R_s$$

$$\overline{i_{n,out}} = -g_m \overline{V_s} + \overline{i_{n,d}}$$

$$= -g_m R_s \overline{i_{n,out}} + \overline{i_{n,d}}$$

$$\Rightarrow \overline{i_{n,out}} = \frac{\overline{i_{n,d}}}{1 + g_m R_s} = \frac{\overline{i_{n,d}}}{2}$$

$$\Rightarrow \overline{i_{n,out}^2} = \frac{\overline{i_{n,d}^2}}{4}$$

$$\Rightarrow \overline{i_{n,out,tot}^2} = \frac{\overline{N_{n,R_s}^2}}{4R_s^2} + \frac{\overline{i_{n,d}^2}}{4}$$

$$\therefore F = \frac{\frac{\overline{N_{n,R_s}^2}}{4R_s^2} + \frac{\overline{i_{n,d}^2}}{4}}{\frac{\overline{N_{n,R_s}^2}}{4R_s^2}} = 1 + R_s^2 \cdot \frac{\overline{i_{n,d}^2}}{\overline{N_{n,R_s}^2}}$$


$$= 1 + R_s^2 \cdot \frac{4kT \gamma g_{do} \Delta f}{4kTR_s \Delta f}$$

$$= 1 + \gamma g_{do} R_s = 1 + \gamma \frac{g_{do}}{g_m}$$


$$\Rightarrow \boxed{F = 1 + \frac{\gamma}{\alpha}}$$

for long-channel case, $F = 1.67 \Rightarrow NF_{min.} = 2.2 \text{ dB}$

4) Resistive input without resistors

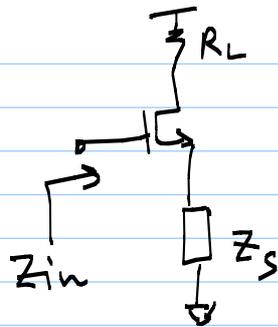

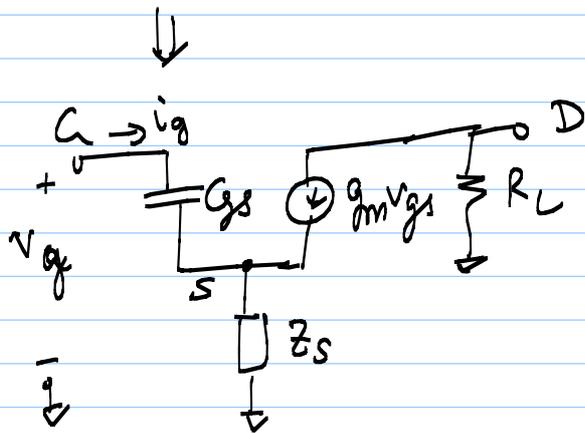* assume transistor model with only C_{gs} & g_m



$$\frac{v_g - v_{gs}}{Z_s} = g_m v_{gs} + i_g$$

$$\Rightarrow v_g = i_g Z_s + (1 + g_m Z_s) v_{gs}$$



also $v_{gs} = i_g / s C_{gs}$

$$\Rightarrow v_g = i_g Z_s + (1 + g_m Z_s) \frac{i_g}{s C_{gs}}$$

$$\Rightarrow Z_{in} = \frac{v_g}{i_g} = Z_s + \frac{1}{s C_{gs}} + \frac{g_m Z_s}{s C_{gs}}$$

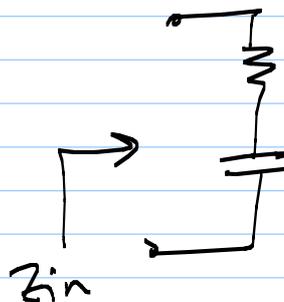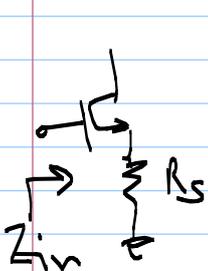a) $Z_s = R_s$

$$\Rightarrow Z_{in} = R_s + \frac{1 + g_m R_s}{s C_{gs}}$$




$$\frac{C_{gs}}{1 + g_m R_s} \approx \frac{1}{\omega_T R_s}$$

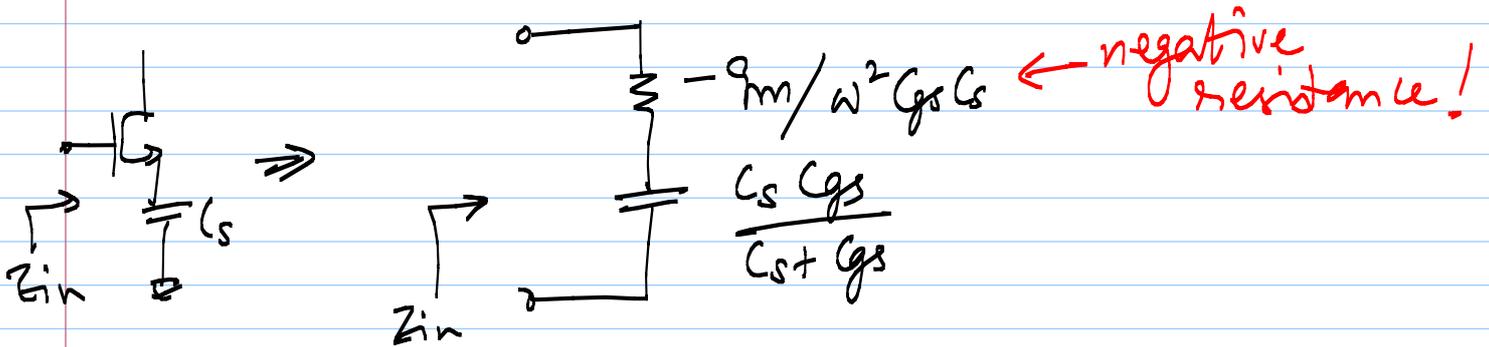b) $Z_s = \frac{1}{s C_s}$

$$\Rightarrow Z_{in} = \frac{1}{s C_s} + \frac{1}{s C_{gs}} + \frac{g_m}{s^2 C_{gs} C_s}$$


$$\Rightarrow Z_{in}(j\omega) = \frac{1}{j\omega} \left(\frac{C_s + C_{gs}}{C_s \cdot C_{gs}} \right) - \frac{g_m}{\omega^2 C_{gs} C_s}$$



- * -ve resistance useful in oscillators
- * beware of parasitic source cap. in amplifiers - can cause instability/oscillations

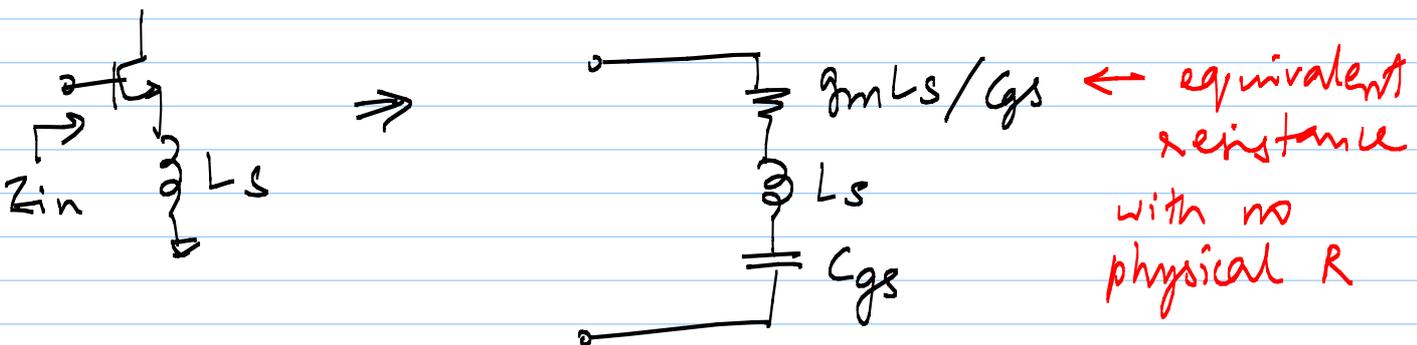
c) $Z_{in} = sL_s$

$$\Rightarrow Z_{in} = sL_s + \frac{1}{sC_{gs}} + \frac{g_m L_s}{C_{gs}}$$



- * Low-noise (no physical resistor)
- * power match: set $\frac{g_m L_s}{C_{gs}} = 50 \Omega$
- * $\frac{g_m L_s}{C_{gs}} = \omega_T L_s$


* Beware :

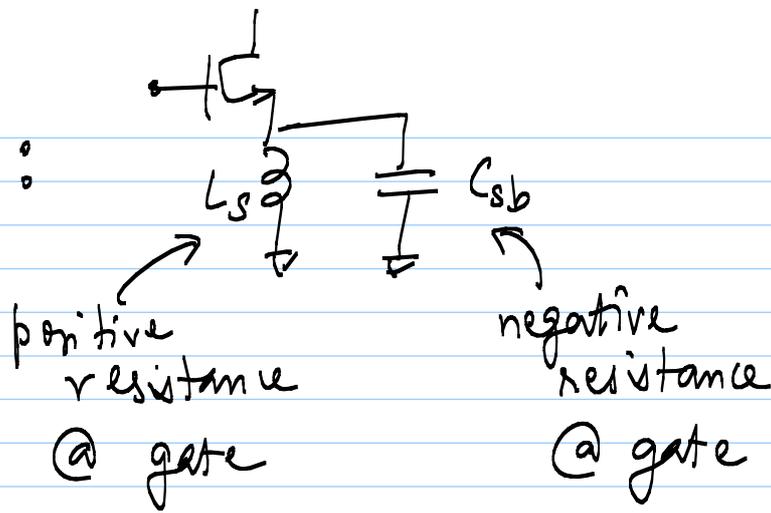

* Set $\omega_T L_S = 50 \Omega$

$$f_0 = \frac{1}{2\pi\sqrt{L_S C_S}} \quad \left\{ \begin{array}{l} Z_{in} \text{ is purely real around} \\ \text{resonant freq. } f_0 \end{array} \right.$$

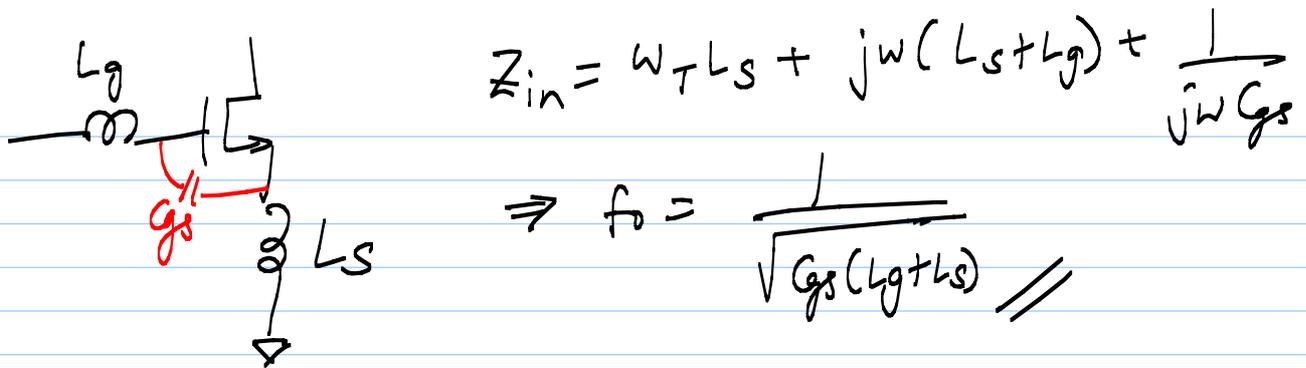* We want another degree of freedom - to set f_0 to be equal to operating freq. (lower)
 \rightarrow add a series inductor L_g at the gate




$$Z_{in} = \omega_T L_S + j\omega(L_S + L_g) + \frac{1}{j\omega C_{gs}}$$

$$\Rightarrow f_0 = \frac{1}{\sqrt{C_{gs}(L_g + L_S)}} //$$

* Q of resonant circuit:

recall: $Q = \frac{\omega_0 L}{R}$ for a series RLC
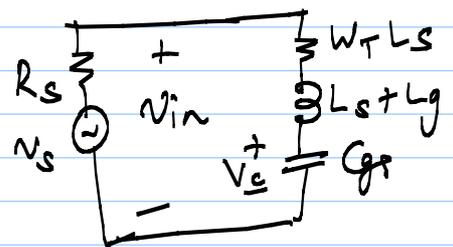
$$\Rightarrow Q_{in} = \frac{\omega_0(L_g + L_S)}{R_S + \omega_T L_S}$$



* effective g_m @ f_0 :

recall: $|V_{gs}| = |V_{in}| = Q |V_{in}|$ for a series RLC

$$\Rightarrow V_{gs} = V_c = Q_{in} \cdot v_s$$


$$\text{also, here } v_{in} = \frac{w_T L_s}{R_s + w_T L_s} \cdot v_s = \frac{v_s}{2} \quad \left\{ \begin{array}{l} \text{available} \\ \text{voltage} \\ \text{@ gate} \end{array} \right\}$$

$$\Rightarrow V_{gs} = 2 Q_{in} v_{in}$$

$$\Rightarrow i_d = g_m V_{gs} = (g_m - 2 Q_{in}) \cdot v_{in}$$

$$\Rightarrow \boxed{G_m = 2 Q_{in} \cdot g_m}$$

Output

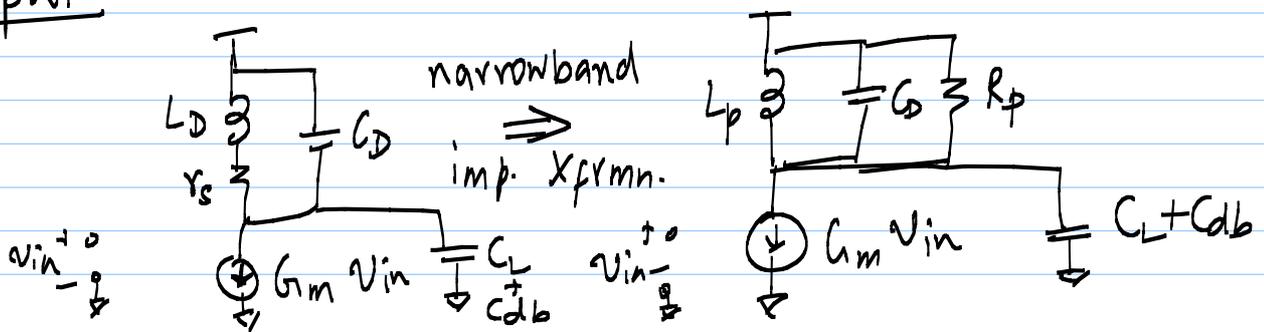

* series to parallel transformation

* tuned parallel RLC load

→ r_s = parasitic series resistance of inductor

→ $f_0 = \frac{1}{2\pi \sqrt{L_D (C_D + C_{db} + C_L)}} = \text{desired operating freq.}$

→ $C_D \gg C_{db}, C_L$ (input cap. of mixer)
so that f_0 does not vary with parasitics

* IC LNAs - output does not drive so r

→ input of mixer is capacitive





Stability: quantified using Stern Stability Factor

$$K = \frac{1 + |\Delta|^2 - |S_{11}|^2 - |S_{22}|^2}{2 |S_{21}| |S_{12}|}; \quad \Delta = S_{11} S_{22} - S_{21} S_{12}$$

* If $|k| > 1$ and $\Delta < 1$, circuit is unconditionally stable

* S_{12} is a measure of Reverse Isolation
 \rightarrow as reverse isolation increases (i.e. S_{12} decreases), circuit becomes more stable

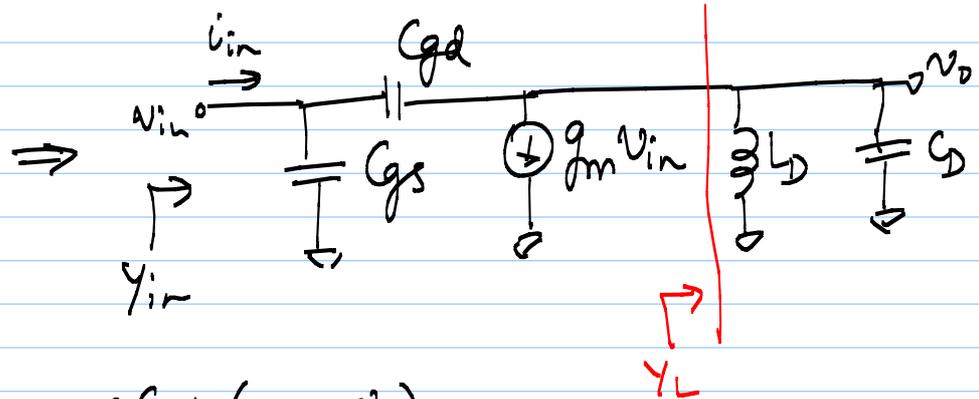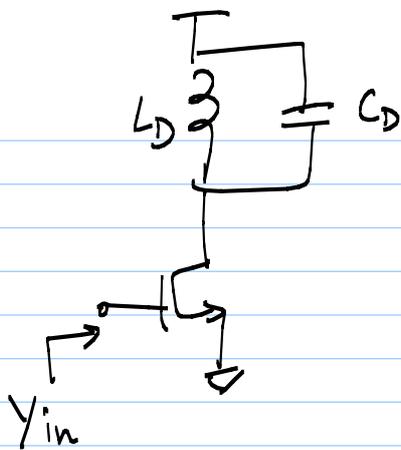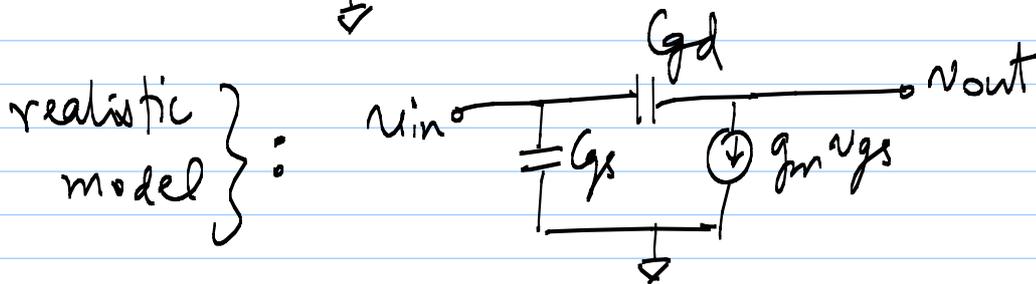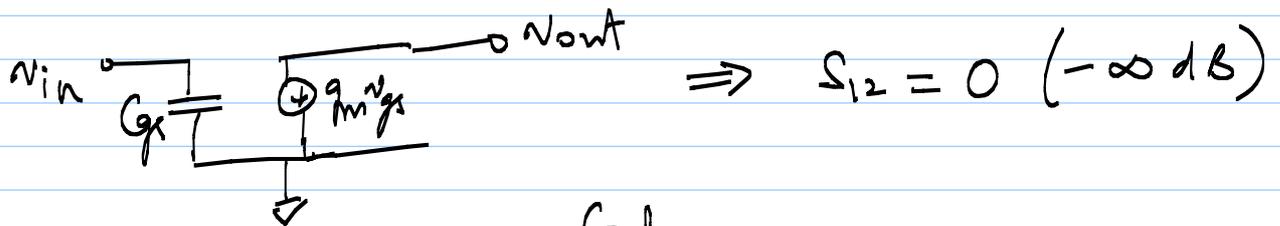* Simple MOS det model does not capture this



$$\begin{cases} i_{in} = sC_{gs}v_{in} + sC_{gd}(v_{in} - v_o) \\ sC_{gd}(v_{in} - v_o) = g_m v_{in} + v_o \cdot Y_L \end{cases}$$

$$\Rightarrow Y_{in} = \frac{i_{in}}{v_{in}} = sC_{gs} + sC_{gd} \frac{(Y_L + g_m)}{Y_L + sC_{gd}}$$

usually, $Y_L \gg sC_{gd}$,

$$\Rightarrow Y_{in} = sC_{gs} + sC_{gd} + \frac{g_m sC_{gd}}{Y_L}$$

at low frequencies, $Z_L(j\omega) \approx j\omega L_D$ {inductor dominates}

$$\Rightarrow Y_L(j\omega) = \frac{1}{Z_L} = -\frac{j}{\omega L_D}$$

$$\Rightarrow Y_{in}(j\omega) = j\omega(C_{gs} + C_{gd}) - g_m \omega^2 L_D C_{gd}$$

$$\text{Re}(Y_{in}(j\omega)) = \underbrace{-g_m \omega^2 L_D C_{gd}}_{\text{negative resistance!}}$$

→ can cause instability

→ neg. res. magnitude $\propto C_{gd}$

→ $C_{gd} = f(\text{device width, layout})$

→ simulate LNA over a wide frequency range to make sure it is stable at all freq.