

Lecture 18: LNA Design (contd.)

Note Title

7/26/2011

Last slide:

- 1) Input match
 - 2) Output match
- } may require iteration



* g_m & G_d will cause input & output matches to depend on each other - Iteration


* Input matching is quantified by S_{11} (also called 'return loss')

$$S_{11} = 20 \log \left| \frac{Z_{in} - R_s}{Z_{in} + R_s} \right|$$

* Similarly, output matching is quantified by S_{22}

3) stability: Circuit Techniques to improve stability
(ie. decrease G_d and increase S_{12})


A) Neutralisation:

 


- * L_f and G_d resonate at desired frequency
- * L_f & C_{block} parasitics load input mode
- * area intensive (L_f)

 B) Cascode: * reduces effect of G_d

- * reduces interaction between input & output tuned ckt's.



 - * parasitic cap can cause some loss of signal and degrade NF at high freq.
- * short-channel MOS - R_{out} is finite, so may want to use $L > L_{min}$.
→ This will increase C_{par}




4) Voltage gain A_v

$$A_v = \frac{v_{out}}{v_{in}} = g_m R_p$$

$$\Rightarrow [A_v = 2 Q_{in} g_m R_p]$$

* neglect r_{ds} (we will typically use a cascode)

5) Transducer Power gain G_T

 

$$G_T = \frac{\text{Power delivered to load}}{\text{Power available from source (max)}} = \frac{P_{\text{load}}}{P_{\text{available,source}}}$$

$$P_{\text{available,source}} = \frac{|v_{in}|^2}{2R_s} \quad \left\{ \begin{array}{l} \text{assume } v_{in}, v_{out} \text{ etc. are} \\ \text{peak values} \end{array} \right\}$$

$$\text{Let } Y_L = \frac{1}{Z_L} \Rightarrow h_L = \text{Re}(Y_L) = \text{Re}\left(\frac{1}{Z_L}\right)$$

$$\begin{aligned} P_{\text{load}} &= \frac{|v_{out}|^2}{2} \cdot g_L = \frac{|v_{out}|^2}{2} \cdot \text{Re}\left(\frac{1}{Z_L}\right) \\ &= \frac{1}{2} \text{Re}\left(\frac{1}{Z_L}\right) \cdot |G_m(R_p \parallel Z_L)|^2 \cdot |v_{in}|^2 \end{aligned}$$


$$\Rightarrow G_T = \left| G_m(R_p \parallel Z_L) \right|^2 \cdot R_s \cdot \text{Re}\left(\frac{1}{Z_L}\right)$$

a) LNA drives off-chip component (e.g. filter)

$\rightarrow Z_L$ is matched to R_p in that case


$$G_T = \left| G_m \frac{R_p}{Z_L} \right|^2 \cdot R_s \cdot \frac{1}{R_p} = \frac{G_m^2 R_s R_p}{4} //$$

 b) LNA drives mixer (or another amplifier)



series - parallel transformation :

input of M_2

 

$$R_L \approx Q_2^2 r_{g2}$$

$$C_L \approx C_{g2}$$

$$Q_2 = \frac{1}{\omega_0 r_{g2} C_{g2}}$$

- * MOSFET with good layout $\Rightarrow r_{g2}$ is very small
- * Ideally $r_{g2} \rightarrow 0 \Rightarrow Q_2 \rightarrow \infty \Rightarrow R_L \rightarrow \infty$

- * C_L is usually absorbed into C_p (output tuning network of LNA)

$$\Rightarrow Z_L \approx R_L = Q_2^2 r_{g2}$$

$$G_T = |G_m (R_p || R_L)|^2 \cdot \frac{R_s}{R_L}$$

$$G_T \rightarrow 0 \text{ as } R_L \rightarrow \infty$$

What does this mean?

- \rightarrow ideal MOSFET M_2 has purely capacitive gate
- \rightarrow no real power consumed @ input
- $\Rightarrow P_{load} \rightarrow 0 \Rightarrow A_T \rightarrow 0$

6) Available power gain A_p

$$A_p = \frac{\text{Power available from LNA output}}{\text{Power available from source}} = \frac{P_{av, LNA}}{P_{av, s}}$$

$P_{av, LNA}$ = power delivered to load under matched condition (same as 4(a))

$$A_p = \frac{G_m^2 R_s R_p}{4}$$

How about Power Dissipation?

Power-constrained noise optimization:

* Minimize F given a specific bound on P_{diss} .

* For full details, see Thomas Lee pp 380-384

From 2-port noise theory,

$$F = F_{min.} + \frac{R_n}{G_s} \left[(h_s - h_{opt})^2 + (B_s - B_{opt})^2 \right]$$

* define

$$\frac{h_{opt}}{w G_s} = \alpha \sqrt{\frac{s}{s\gamma} (1 - |c|^2)} = Q_{opt}.$$

$$Q_s = \frac{1}{w G_s R_s}$$

$$* \text{Rewrite } F = F_{min.} + \left[\frac{\gamma}{\alpha g_m R_s} \right] \left[1 - \frac{Q_{opt}^2}{Q_s^2} \right]$$

* optimum Q_{opt} turns out to be $\approx \underline{4.5}$

$$* W_{opt,p} = \frac{3}{2} \frac{1}{\omega L C_{ox} R_s Q_{sp}} \approx \frac{1}{3 \omega L C_{ox} R_s}$$

$$* F_{min,p} \approx 1 + 2 \cdot 4 \frac{\gamma^2}{2} \left[\frac{W}{W_T} \right]$$

$$* F_{min} \approx 1 + 2 \cdot 3 \left[\frac{W}{W_T} \right]$$

W_T/W	F_{min}	$F_{min,p}$	$\gamma=2, \delta=4, \alpha=0.85$
20	0.5	1.1	
15	0.6	1.4	
10	0.9	1.9	
5	1.6	3.3	

basic design procedure:

- 1) Determine $W_{opt,p}$ as above
- 2) Choose I_{bias} based on power constraint

- 3) Determine L_s (with R_{in}, W_T known)
- 4) Calculate $NF_{min,p}$
- 5) choose L_g for desired f_o
- 6) choose L_D to minimize R_p (highly dep. on process)
and \therefore gain

Note: you will probably need to iterate at each step and also between steps

* Noise vs. linearity trade off
as $I_{bias} \uparrow \Rightarrow (V_{AS} - V_T) \uparrow \Rightarrow IIP_3 \uparrow$

but \hookrightarrow increased short-channel effects
 $\Rightarrow \alpha \left(\text{i.e. } \frac{g_m}{g_{ds}} \right) \downarrow \Rightarrow f \uparrow$