
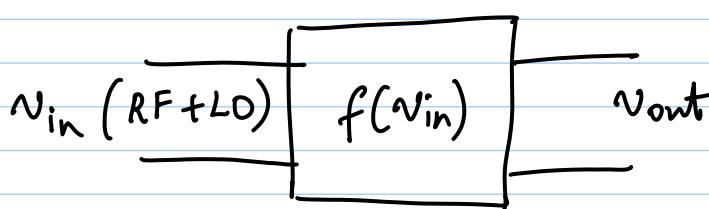


Lecture 20 : Two- & Three-port Mixers

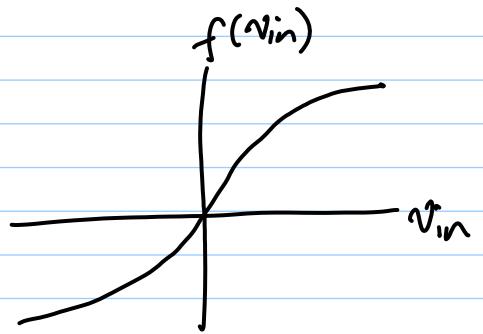

$$v_{\text{out}} = \sum_{n=0}^N c_n (v_{\text{in}})^n$$

Output contains:



"soft nonlinearity"

* DC terms - from even order terms

- use AC coupling to filter these

* harmonics of inputs - $m\omega_{\text{LO}}$ & $m\omega_{\text{RF}}$
($m = 1 \text{ to } N$)

- can be filtered as these are
 $\gg \omega_{\text{IF}}$ (Rx Mixer)

* IM terms - $p\omega_{\text{RF}} \pm q\omega_{\text{LO}}$

$$p, q > 0 \quad \& \quad p+q = 2, 3, \dots, N$$

M_2 : $\omega_{\text{RF}} \pm \omega_{\text{LO}}$ (i.e. $p=q=1$) = desired output
 \Rightarrow square-law (quadratic) behavior

$$\left. \begin{array}{l} M_3 : 2\omega_{\text{RF}} \pm \omega_{\text{LO}} \\ \omega_{\text{RF}} \pm 2\omega_{\text{LO}} \end{array} \right\} \begin{array}{l} p+q=3 \\ \text{undesired terms} \end{array}$$

Square-law mixer

let $C_i = 0$ for $i \neq 1, 2$

$$v_{\text{out}} = C_1 v_{\text{in}} + C_2 v_{\text{in}}^2$$

$$v_{\text{in}} = v_{\text{RF}} \cos \omega_{\text{RF}} t + v_{\text{LO}} \cos \omega_{\text{LO}} t$$

(A) fund. terms $\therefore C_1 [v_{\text{RF}} \cos \omega_{\text{RF}} t + v_{\text{LO}} \cos \omega_{\text{LO}} t]$

(B) square terms: $C_2 \{ [v_{RF} \cos \omega_{RF} t]^2 + [v_{LO} \cos \omega_{LO} t]^2 \}$

(C) cross terms: $2 C_2 v_{RF} v_{LO} [\cos \omega_{RF} t] \cdot [\cos \omega_{LO} t]$

{
 (A) - scaled versions of input
 (B) - rewrite $(\cos \omega t)^2$ as $\frac{1}{2} (1 + \cos 2\omega t)$
 \Rightarrow DC & 2nd harmonic terms

not useful, remove by filtering


rewrite (C): $C_2 v_{RF} v_{LO} [\cos(\omega_{RF} - \omega_{LO})t + \cos(\omega_{RF} + \omega_{LO})t]$

* If v_{LO} is fixed,
 $A_{IF} \propto A_{RF} \Rightarrow$ linear mixing

$$G_c = \frac{C_2 v_{RF} v_{LO}}{v_{RF}} = C_2 \cdot v_{LO}$$

* Long-channel MOSFETs can serve as good square-law mixers


example 1

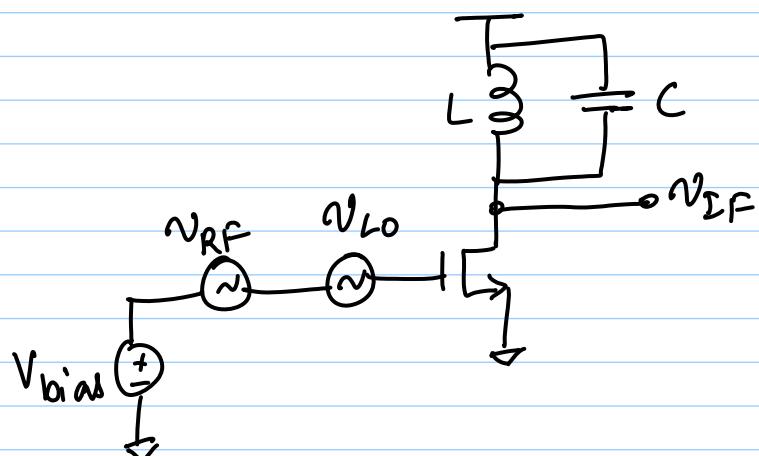

* summation thru' resistive/reactive networks

* poor isolation between LO & RF

example 2

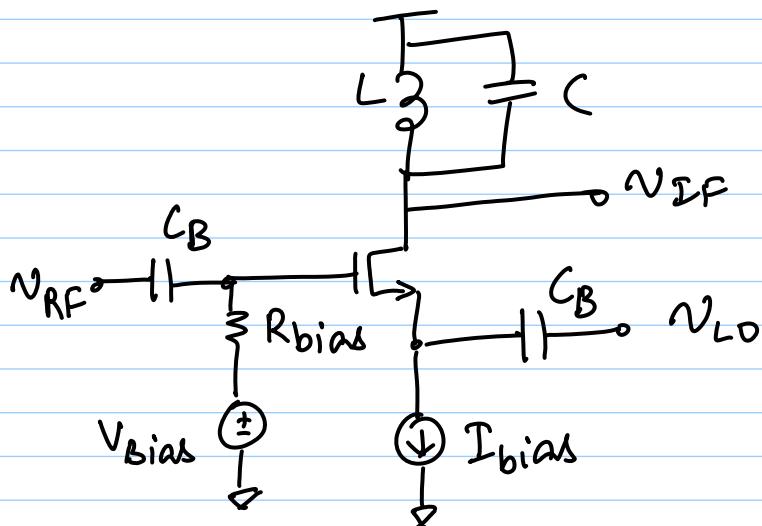

* $V_{GS} = V_{RF} - V_{LO}$

* $R_{Bias} = \text{large enough}$

so that a) min. loading

b) min. noise

* Assume V_{Bias}, I_{bias} & L are chosen

such that :

$$I_D = \frac{1}{2} \mu C_{ox} \frac{W}{L} (V_{GS} - V_T)^2 \text{ is valid}$$

* short-channel devices are inferior

* V_{Bias}, I_{bias} chosen to avoid sub-threshold operation (exponential)

$$I_D = \frac{1}{2} \mu C_{ox} \frac{W}{L} \left[(V_{Bias} - V_T) + (V_{RF} \cos \omega_{RF} t - V_{LO} \cos \omega_{LO} t) \right]^2$$

Expand into 3 terms:

$$(i) : \frac{1}{2} \mu C_{ox} \frac{W}{L} [V_{Bias} - V_T]^2 \Rightarrow \text{DC bias term}$$

$$(ii) : \underbrace{\frac{1}{2} \mu C_{ox} \frac{W}{L}}_{g_m} \cdot \cancel{(V_{Bias} - V_T)} \cdot \cancel{(V_{RF} \cos \omega_{RF} t - V_{LO} \cos \omega_{LO} t)}$$

$$= g_m (V_{RF} \cos \omega_{RF} t - V_{LO} \cos \omega_{LO} t)$$

\Rightarrow fundamental gain terms

$$(iii) : \frac{1}{2} \mu C_{ox} \frac{W}{L} [V_{RF} \cos \omega_{RF} t - V_{LO} \cos \omega_{LO} t]^2$$

$$= \frac{1}{2} \mu C_{ox} \frac{W}{L} \left[V_{RF}^2 \cos^2 \omega_{RF} t + V_{LO}^2 \cos^2 \omega_{LO} t \right.$$

Ⓐ Ⓛ Ⓜ

$$\left. - 2 V_{RF} V_{LO} \cos \omega_{RF} t \cdot \cos \omega_{LO} t \right]$$

Ⓒ

$$(A) : \frac{V_{RF}^2}{2} (1 + \cos 2\omega_{RF} t)$$

DC term 2nd harmonic term

$$(B) : \frac{V_{LO}^2}{2} (1 + \cos 2\omega_{LO} t)$$

$$(C) : \frac{1}{2} \mu C_0 \times \frac{W}{L} \cdot V_{RF} V_{LO} \cdot [\cos(\omega_{RF} - \omega_{LO}) t + \cos(\omega_{RF} + \omega_{LO}) t]$$

mixing terms

conversion gain

$$G_C = \frac{\frac{1}{2} \mu C_0 \times \frac{W}{L} \cdot V_{RF} V_{LO}}{V_{RF}}$$

$$= \frac{1}{2} \mu C_0 \times \frac{W}{L} \cdot V_{LO} = C_2 \cdot V_{LO}$$

G_C is

- * independent of bias
- * temp. dependent (through μ)
- * dependent on V_{LO}

Bipolar mixer (perfect square-law is not necessary)

$$i_C = I_S \exp(V_{BE}/V_T)$$

can be expanded as:

$$i_C = I_C \left[1 + \frac{V_{in}}{V_T} + \frac{1}{2} \left(\frac{V_{in}}{V_T} \right)^2 + \dots \right]$$

$$C_2 = \frac{1}{2} \frac{I_C}{(V_T)^2} = \frac{g_m}{2V_T}$$

$$\Rightarrow G_C = C_2 V_{LO} = g_m \cdot \frac{V_{LO}}{2V_T}$$

* Rewrite G_{CMOS} as :

$$G_{CMOS} = \frac{1}{2} \mu_C \cdot \underbrace{\frac{W}{L}}_{g_m} (V_{BIAS} - V_T) \cdot \frac{V_{LO}}{(V_{BIAS} - V_T)}$$

$$= g_m \frac{V_{LO}}{2V_{DSAT}}$$

$$\frac{G_{CBJT}}{G_{CMOS}} = g_m (BJT) \cdot \frac{V_{LO}}{2V_T} \cdot \frac{2V_{DSAT}}{g_m (MOS) \cdot V_{LO}}$$

$$= \frac{g_m (BJT)}{g_m (MOS)} \cdot \frac{V_{DSAT}}{V_T} \Rightarrow \text{For same } g_m, BJT \text{ has higher } G_c$$

Issues with 2-port mixers :

- No isolation between LO & RF (2-port)
- generation of undesired spurs (multiplication is side-effect)


Multiplexer-based mixers

- * ideally generate only desired IM product
- * 3-port mixers \Rightarrow good isolation between RF, LO & IF


* CMOS - excellent switches

Single-balanced mixer

Based on "Gilbert multiplier" topology

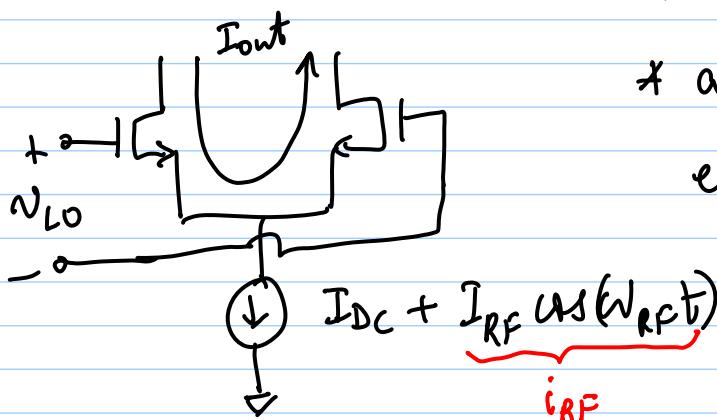


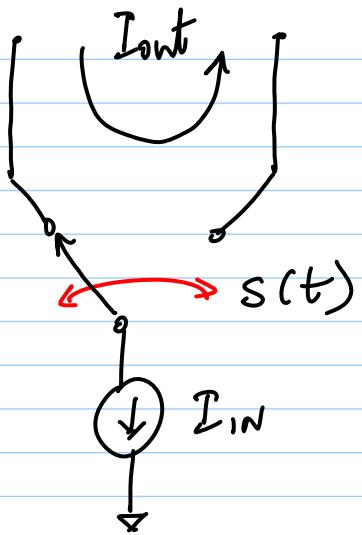* assume V_{LO} is large enough to switch currents completely between two sides.



$$I_{out} = I_{IN} \times s(t)$$
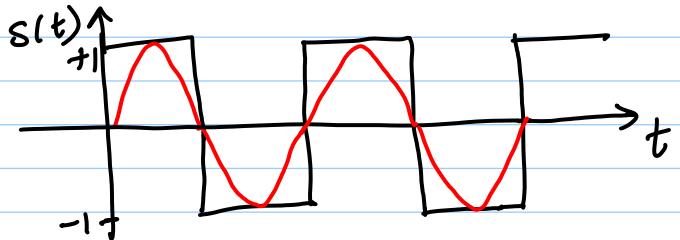
$$s(t) = \text{sgn}(\sin \omega_{LO} t)$$




$\text{sgn}(x) \equiv \text{"signum" or sign function}$

$$= \begin{cases} -1 & \forall x < 0 \\ 0 & x = 0 \\ +1 & \forall x > 0 \end{cases}$$

Note: Single-ended o/p current $\{I_{out}^+ \text{ or } I_{out}^-\}$ is given by $I_{IN} \times S_i(t)$ where

$$S_i(t) = 0.5 + 0.5s(t)$$

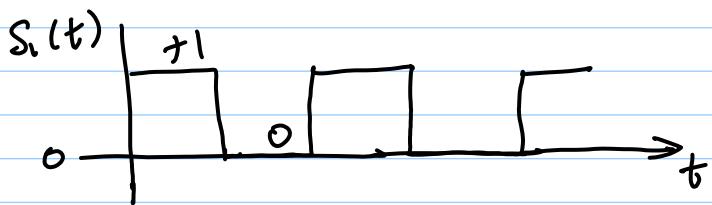


$$I_{out}^+ = (I_{DC} + i_{RF}) \times \{0.5 + 0.5s(t)\}$$

direct feedthrough

Differential current $I_{out}(t)$
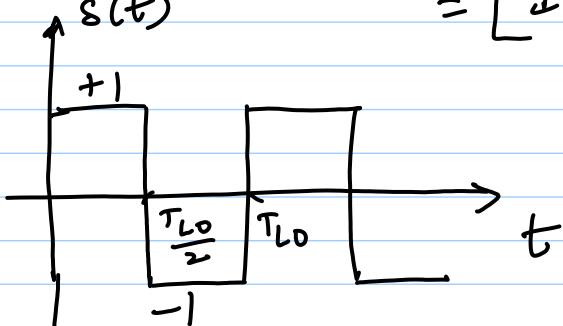
$$= [I_{DC} + I_{RF} \cos \omega_{RF} t] \cdot \text{sgn}[\sin \omega_{LO} t]$$



$$\omega_{LO} = \frac{2\pi}{T_{LO}} = 2\pi f_{LO}$$

Fourier Series of $s(t)$:

$$s(t) = \frac{a_0}{2} + \sum_{n=1}^{\infty} [a_n \cos(n\omega_{L0}t) + b_n \sin(n\omega_{L0}t)]$$

$$\frac{a_0}{2} = 0 \quad (\text{DC average})$$

$$a_n = \frac{2}{T_{L0}} \int_0^{T_{L0}} \operatorname{sgn}(t) \cos(n\omega_{L0}t) dt = 0 \quad \forall n \left\{ \begin{array}{l} \operatorname{sgn}(t) \\ \text{is odd} \end{array} \right\}$$

$$b_n = \frac{2}{T_{L0}} \int_0^{T_{L0}} \operatorname{sgn}(t) \sin(n\omega_{L0}t) dt$$

$$= 2 \cdot \frac{2}{T_{L0}} \int_0^{T_{L0}/2} \sin(n\omega_{L0}t) dt$$

$$b_n = \frac{4}{T_{L0}} \cdot \frac{1}{n\omega_{L0}} [-\cos(n\omega_{L0}t)] \Big|_0^{T_{L0}/2}$$
$$= \frac{2}{n\pi} [1 - \cos(n\pi)] //$$

$$\therefore b_n = \begin{cases} 0 & \forall \text{ even } n \\ \frac{4}{n\pi} & \text{for odd } n \end{cases}$$

$$\therefore s(t) = \frac{4}{\pi} \left[\sin \omega_{L0}t + \frac{1}{3} \sin 3\omega_{L0}t + \frac{1}{5} \sin 5\omega_{L0}t + \dots \right]$$

$$\begin{aligned} i_{out}(t) &= [I_{DC} + I_{RF} \cos \omega_{RF}t] \cdot s(t) \\ &= I_{DC} \cdot s(t) + I_{RF} \cos \omega_{RF}t \cdot s(t) \end{aligned}$$

(I)

(II)

$$\textcircled{I} \Rightarrow \frac{4 I_{DC}}{\pi} \cdot \left[\sin \omega_{LO} t + \frac{1}{3} \sin 3\omega_{LO} t + \dots \right]$$

↑ ↑
 "LO feedthrough" feedthrough of
 LO harmonics

$$\begin{aligned}\textcircled{II} \Rightarrow & \frac{4 I_{RF}}{\pi} \cdot \left[\cos \omega_{RF} t \sin \omega_{LO} t + \frac{1}{3} \cos \omega_{RF} t \sin 3\omega_{LO} t + \dots \right] \\ = & \frac{4 I_{RF}}{\pi} \cdot \frac{1}{2} \left[\sin(\omega_{LO} - \omega_{RF})t + \sin(\omega_{LO} + \omega_{RF})t \right. \\ & \left. + \frac{1}{3} \sin(3\omega_{LO} - \omega_{RF})t + \frac{1}{3} \sin(3\omega_{LO} + \omega_{RF})t + \dots \right] \\ = & \frac{2}{\pi} I_{RF} \left[\begin{array}{l} \sin(\omega_{LO} - \omega_{RF})t + \sin(\omega_{LO} + \omega_{RF})t \\ \text{lower sideband} \qquad \qquad \qquad \text{upper sideband} \\ + \text{higher order terms} \end{array} \right]\end{aligned}$$


$$\therefore i_{out}(t) = \frac{2}{\pi} I_{RF} \left[\begin{array}{l} \text{desired term} \\ \sin(\omega_{LO} - \omega_{RF})t + \sin(\omega_{LO} + \omega_{RF})t \\ + [\text{higher order mixing terms}] \\ + [\text{LO & LO harmonic feedthrough terms}] \end{array} \right]$$

close to desired

can be filtered out

term in case of Tx
 - cannot be filtered out

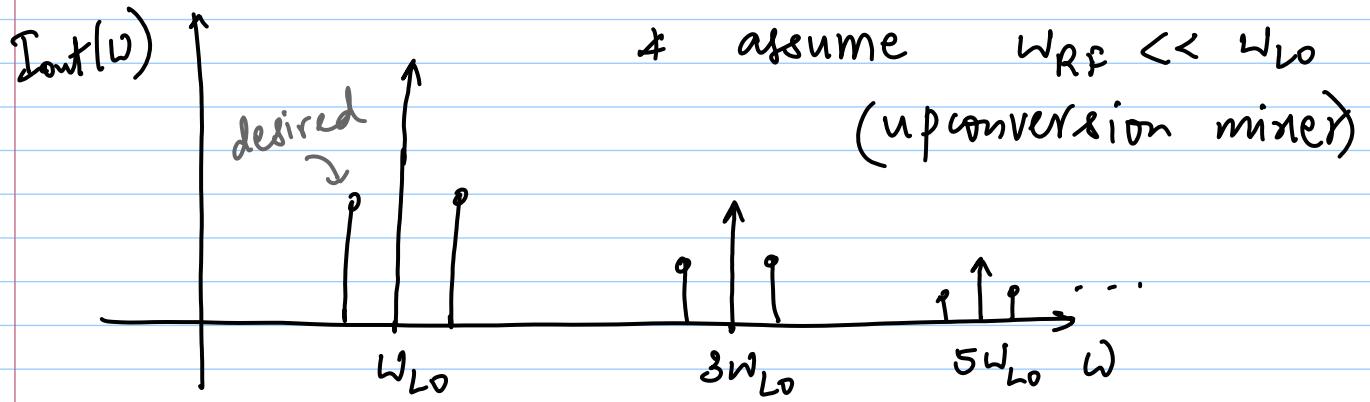- * square wave has only odd harmonics of fundamental [ω_{LO} , $3\omega_{LO}$, $5\omega_{LO} \dots$]



* assume $\omega_{RF} \ll \omega_{LO}$
(upconversion mixer)

- * poor isolation between LO & output ports
- * input RF is required to be a current
 - V-I converters are usually imperfect
 - more of a problem for down-converters

- * no RF feedthrough assumes perfect M_2 - M_3 matching
- * Immediate switching requires ω_{LO} waveform zero crossings to coincide, otherwise
 - LO diff. pair simultaneously ON
 - RF current is "wasted" as common-mode signal ($G_c \downarrow, NFT \uparrow$)