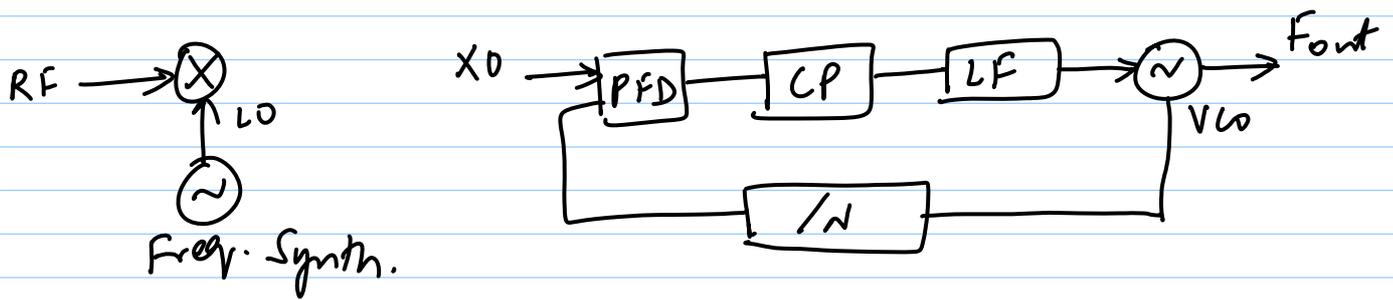


Lecture 27 : VCOs - I



* Autonomous ckt (i.e. needs to be locked with a PLL)

* Applications: → Freq. Synthesis
→ Clock & Data Recovery ckt
(also optical comm.)
→ μ -processor clk gen.

Types of Oscillators (RF)

* Relaxation oscillators (typically C-based)

→ poor spectral purity

→ high phase noise


* Harmonic oscillators

→ LC VCOs, Crystal oscillators

→ good phase noise & spectral purity

In this course, we will study these

Feed back model (2-port)

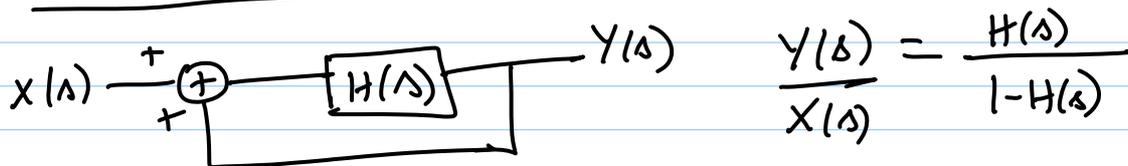

$H(s_0) = 1 \Rightarrow$ self-sustaining oscillations

Amplitude is constant if $H(s_0 = j\omega_0) = 1$


Barkhausen Criterion

(1) $|H(j\omega_0)| = 1$

(2) $\angle H(j\omega_0) = 360^\circ$ (loop phase shift is +ve)

\rightarrow if there is DC negative feedback, only 180° excess phase shift is required


i.e. $\angle H(j\omega_0) = 180^\circ$

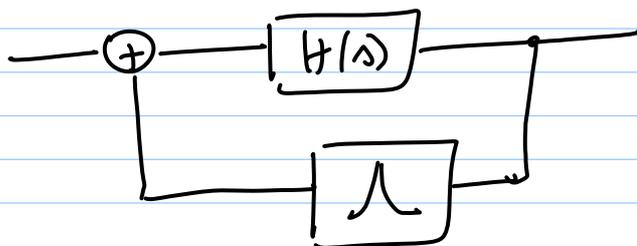

RLC tank = sets frequency ω_0


* Barkhausen criteria are necessary but not sufficient conditions

e.g. #1

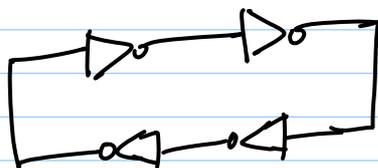

\leftarrow does not oscillate

①

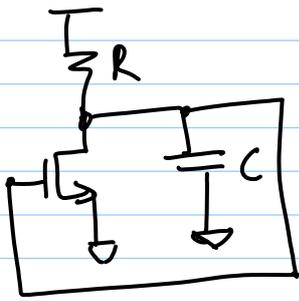


* Does not oscillate

only 1 pole; 270° phase shift

@ $\omega = \infty$

②

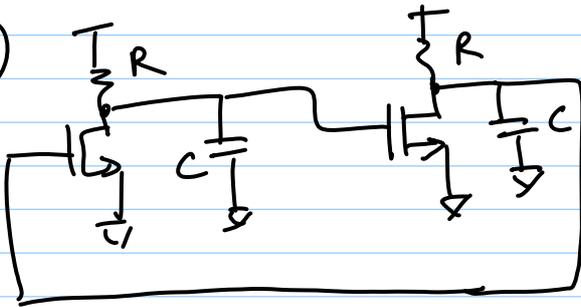


* Does not oscillate

2-poles = 180° @ $\omega = \infty$

but, DC f.b. = 360°

\Rightarrow latch-up

③

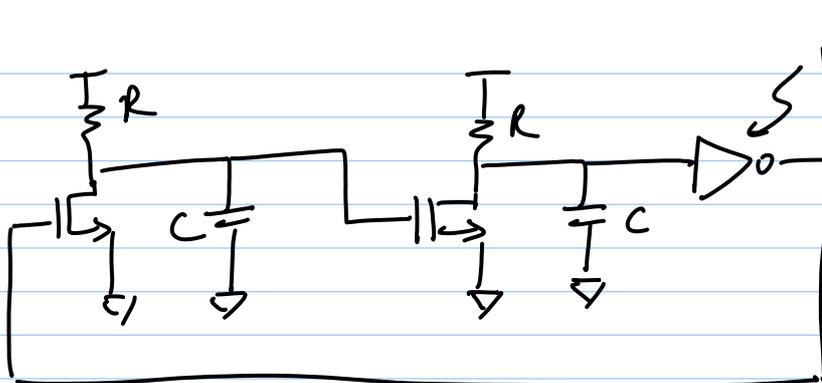

ideal inv.


* Does NOT oscillate

DC f.b. = -ve (180°)

excess phase required = 180°

2-poles $\Rightarrow 180^\circ$ reached only @ $\omega = \infty$

④


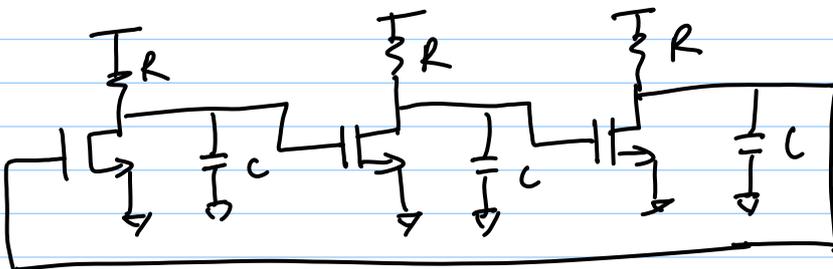


Does oscillate

at DC $\Rightarrow 180^\circ$ phase shift
for each stage,

$$\frac{out}{in} = \frac{-A_0}{1 + s/\omega_p}$$
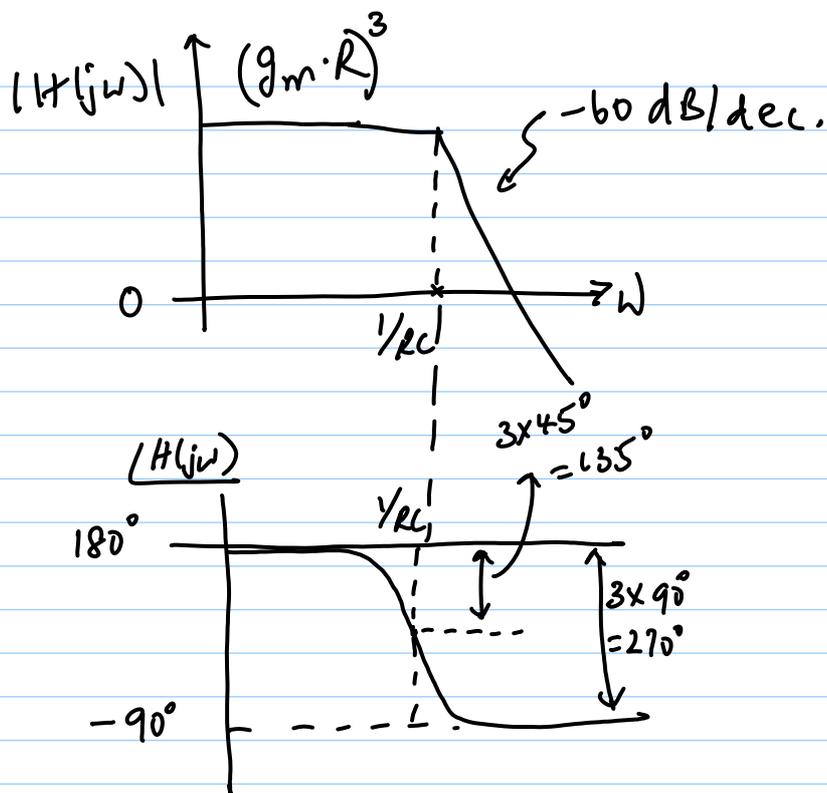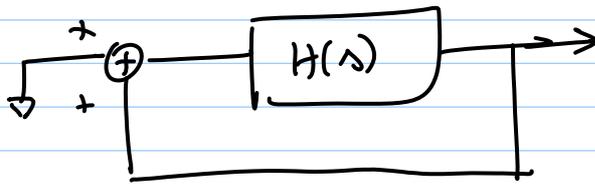
$$\Rightarrow H(s) = - \left(\frac{A_0}{1 + s/\omega_p} \right)^3 ; \omega_p = \frac{1}{RC}$$



say oscillation happens @ ω_0

$|H(j\omega)| = 360^\circ/0^\circ$ has to be satisfied

$$\Rightarrow \pi - 3 \tan^{-1} \left(\frac{\omega_0}{\omega_p} \right) = 0^\circ$$



$$\tan^{-1} \left(\frac{\omega_0}{\omega_p} \right) = \frac{\pi}{3}$$

$$\Rightarrow \boxed{\omega_0 = \sqrt{3} \omega_p}$$

$$|H(j\omega_0)| = \frac{A_0^3}{\left[1 + \left(\frac{\omega_0}{\omega_p} \right)^2 \right]^{3/2}} = \frac{A_0^3}{8}$$

$|H(j\omega_0)| = 1$ has to be satisfied $\Rightarrow \boxed{A_0 = 2}$

* What happens if $A_0 \neq 2$?

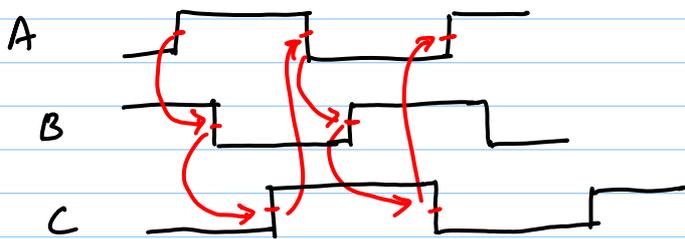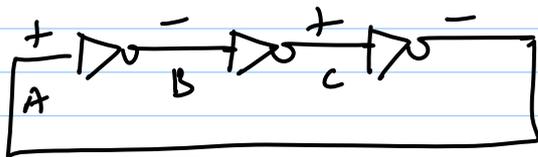


$$T = 6 \tau$$

$$\tau = \frac{t_r + t_f}{2}$$

In general $T = 2n\tau$ for n inv.

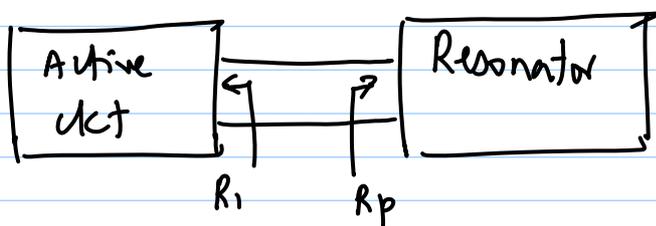One-port View (useful for LC oscillators)




we want

$$R_i = -R_p$$


* Energy is lost in R_p every cycle

* This is replenished by active ckt

Remember

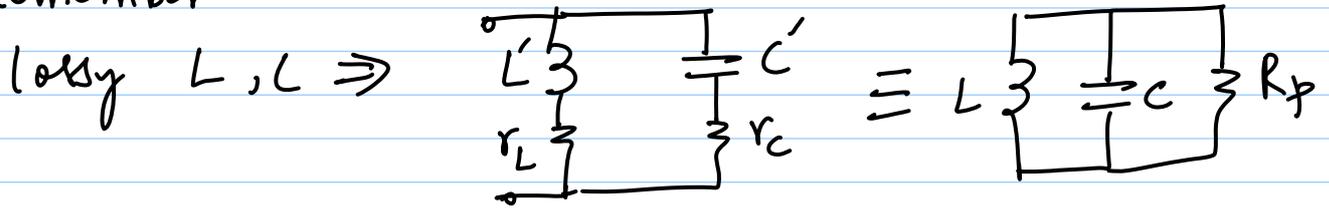

* Freq. determined by L, C

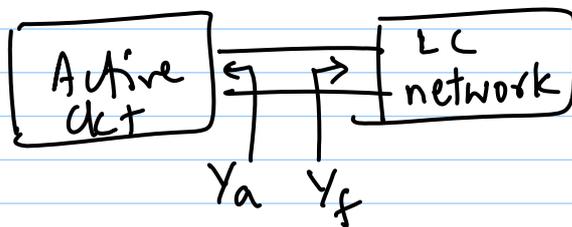

$$Y_a = G_a + jB_a$$

$$Y_f = G_f + jB_f$$




$$\Rightarrow G_a = -G_f \quad \text{and} \quad B_a = -B_f$$


* How about amplitude?

\rightarrow usually require "startup" loop gain > 1 (e.g. 3)

\rightarrow at steady state, amp inside active block saturates with low gain @ peaks so that average $Lh = 1$

choose $G_a + G_f < 0$ for startup

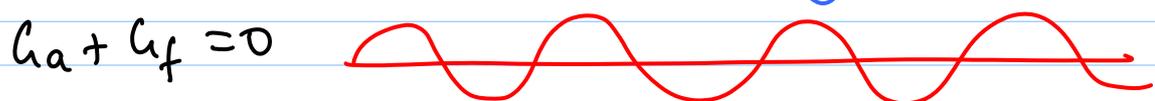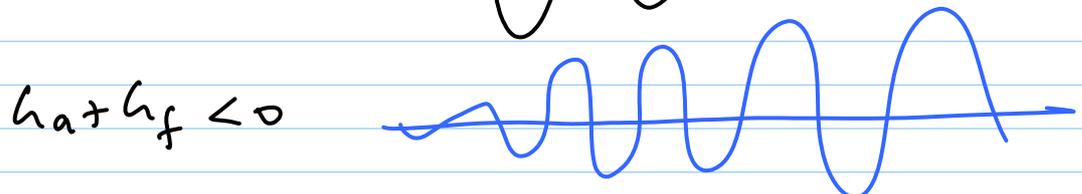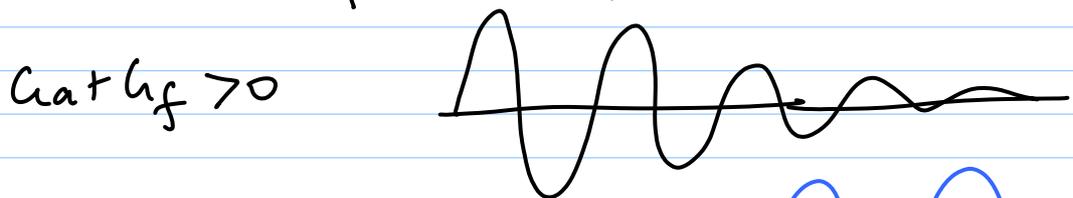

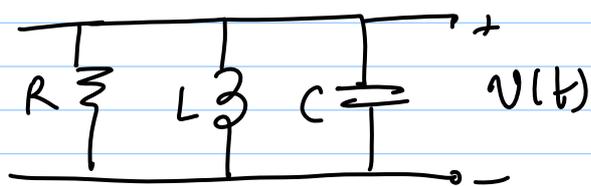


$v(0) = V_0 = \text{initial voltage across cap.}$

If $Q = \frac{R}{\omega_0 L} = \omega_0 RC = \sqrt{\frac{L}{C}} > \frac{1}{2}$,

the 2nd-order system will have imaginary roots


⇒ exponentially decaying sinusoid

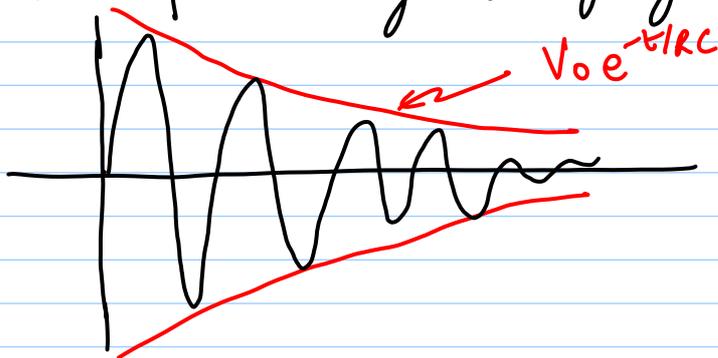

$\tau = 1/RC$

as $R \rightarrow \infty$, $\tau \rightarrow \infty$

⇒ amplitude does not decay (ideal LC)

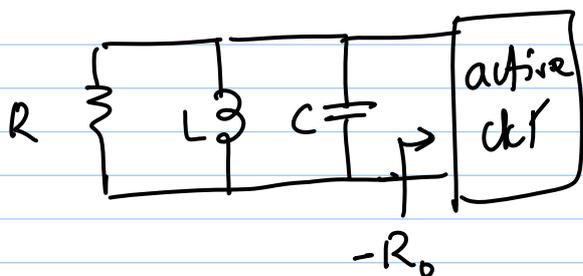

$R_{eq} = \frac{R R_0}{R_0 - R}$


decaying exponential envelope = $V_0 \exp\left[-\frac{t}{R_{eq} C}\right]$

$R = R_0 \Rightarrow$ amplitude never decays

$R < R_0 \Rightarrow$ decaying exp.


$R > R_0 \Rightarrow$ growing exp.

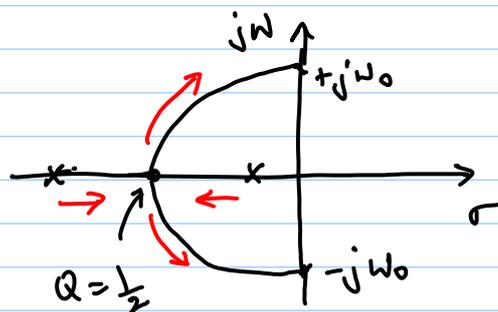@ $Q = \frac{1}{2}$, poles split into complex conjugate pair




Linear oscillators

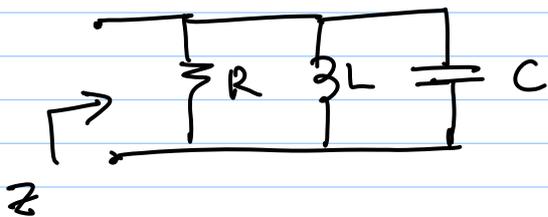
- 1) $G_{in} + G_p = 0 \Rightarrow$ oscillations are sustained, but startup is compromised
- 2) $G_{in} + G_p < 0 \Rightarrow$ startup possible, but amplitude not stable (\uparrow)
 \Rightarrow oscillator needs to be fundamentally non-linear


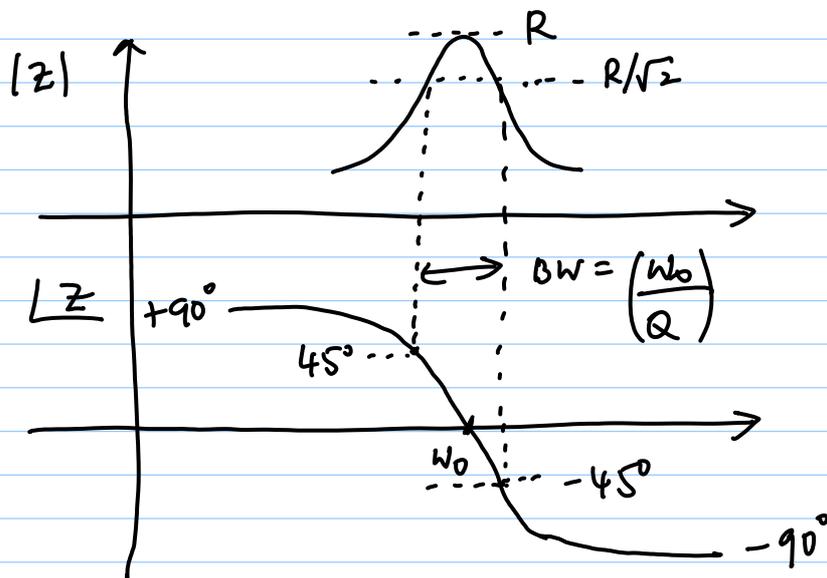
$$Z(j\omega) = \frac{sL}{LCs^2 + \frac{L}{R}s + 1}$$



$$\omega_0 = \frac{1}{\sqrt{LC}}$$

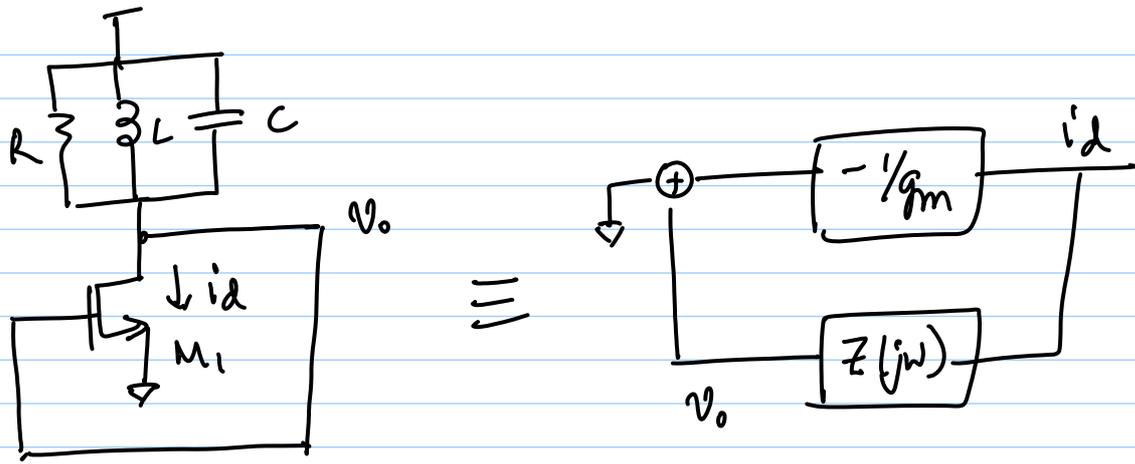


(a) resonance, RLC tank phase shift = 0

M_1 phase shift = 180°

$\Rightarrow |H(s)| = 180^\circ \Rightarrow$ no oscillations

Let us cascade two of these stages.

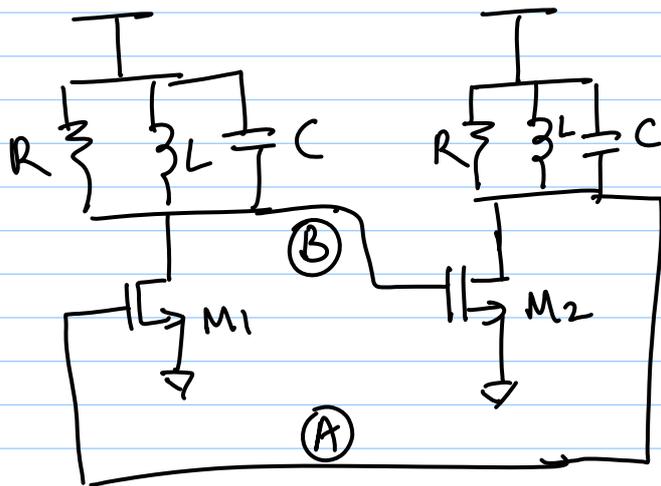

* at $\omega_0 = \frac{1}{\sqrt{LC}}$,
each stage contributes
 180° phase shift


* $|H(s)| = 360^\circ$

* oscillations are possible if $|H(j\omega_0)| \geq 1$

$$\Rightarrow (g_m R)^2 \geq 1$$

$\left. \begin{array}{l} > \Rightarrow \text{startup} \\ = \Rightarrow \text{steady-state} \end{array} \right\}$

Redraw :

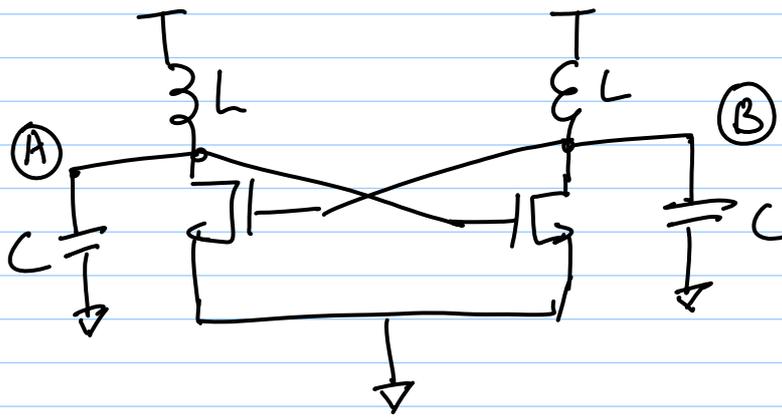

Modern on-chip
LC oscillator

(A) & (B) are 180° out of phase
 \Rightarrow differential outputs