
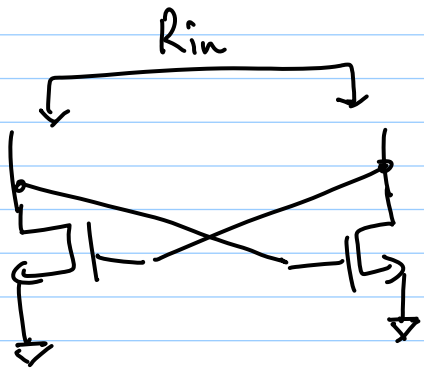


Lecture 28: VCOs - II

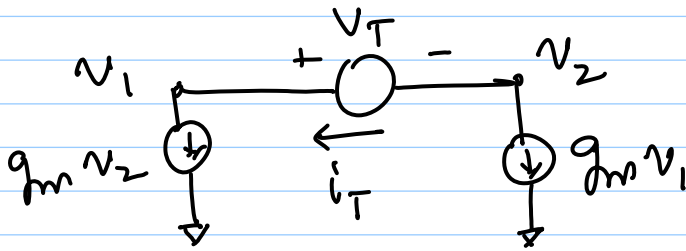

$R_{in} = ?$




$$i_T = g_m v_2 = -g_m v_1$$

$$2i_T = g_m (v_2 - v_1)$$

$$= -g_m v_T$$

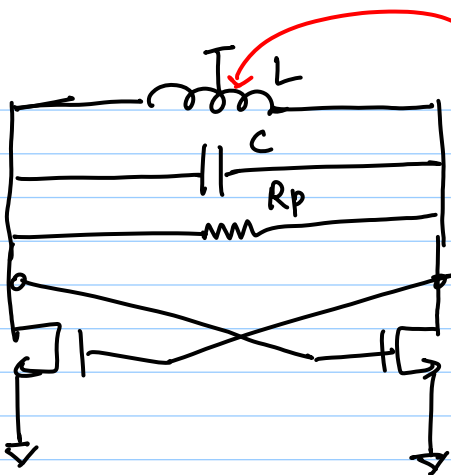
$$\Rightarrow R_{in} = \frac{V_T}{i_T} = -\frac{2}{g_m}$$




centre-tap to V_{DD}

for oscillations,

$$|R_p| = \left| -\frac{2}{g_m} \right| \Rightarrow \underline{\underline{g_m R_p = 2}}$$

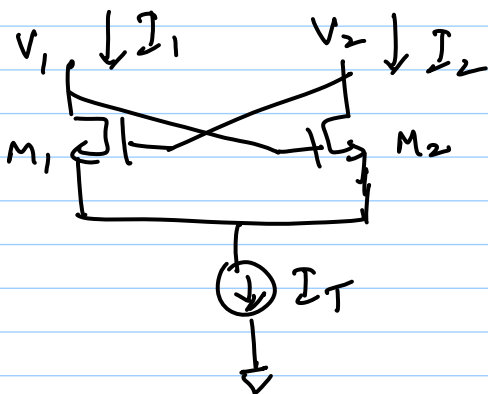

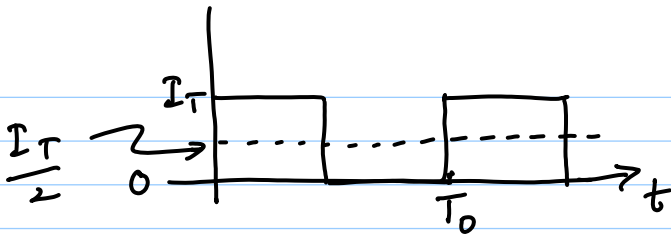positive feedback; assume M_1 & M_2 switch quickly
 $I_1 - I_2 = I_d$



$$I_1 = I_T \left[\frac{1}{2} + \frac{2}{\pi} \left\{ \sin(\omega_0 t) + \frac{1}{3} \sin(3\omega_0 t) + \dots \right\} \right]$$

LC tank filters out DC & harmonics of I





$$\Rightarrow V_1 \{ = -V_2 \} = I_1(\omega_0) \cdot Z(j\omega_0) = \frac{2}{\pi} \cdot I_T \cdot \frac{R_p}{2}$$

$$= \frac{1}{\pi} I_T \sin(\omega_0 t) \cdot R_p$$


$$|V_{od}| = \frac{2}{\pi} I_T R_p \leftarrow \text{output amplitude}$$

* to a first order, oscillation ampl. is independent of device size!

Other flavours of CC VCO:

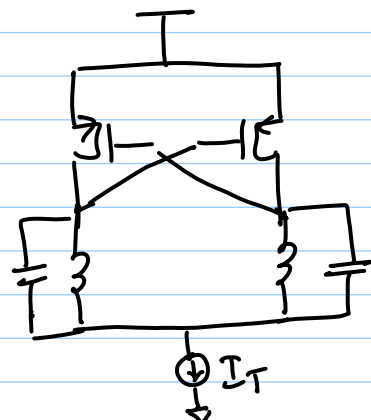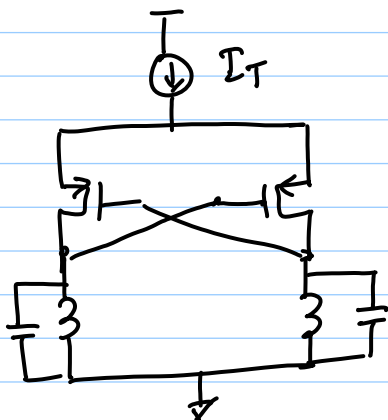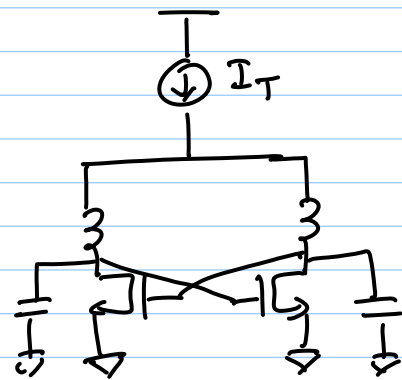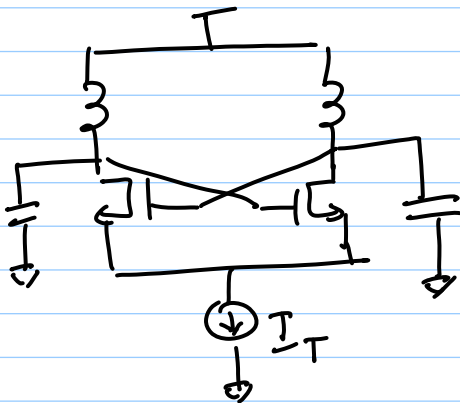


Another popular topology?

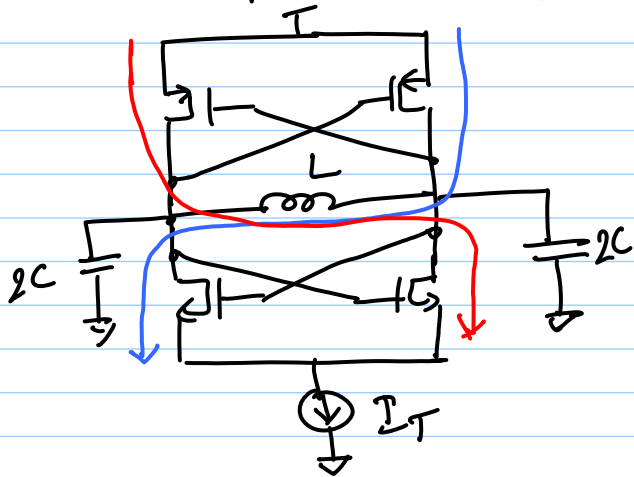

* current sense
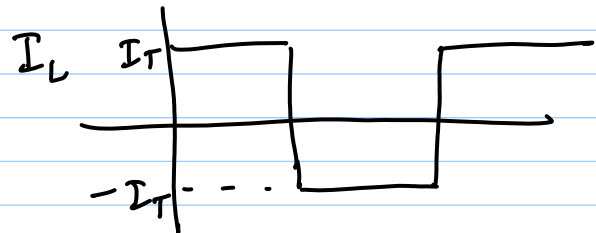
$$\Rightarrow R_{in} = \frac{-2}{g_{m_n} + g_{m_p}}$$





$$\Rightarrow I_L = \frac{4I_T}{\pi} \left[\sin \omega t + \frac{1}{3} \sin 3\omega t + \dots \right]$$

$$\Rightarrow \boxed{\text{Amplitude} = \frac{4}{\pi} I_T R_p}$$

← double the amplitude compared to nmos-c-c. VCO

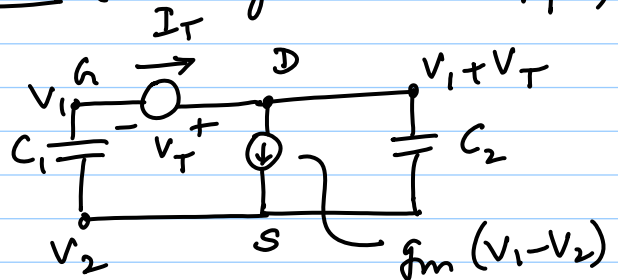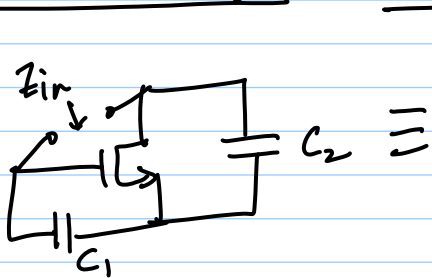Single-transistor oscillators (usually discrete apps)



$$V_1 = V_2 - I_T \cdot \frac{1}{sC_1}$$

$$\Rightarrow (V_1 - V_2) = -\frac{I_T}{sC_1}$$

KCL @ D:



$$\begin{aligned} I_T &= g_m (V_1 - V_2) + \left\{ (V_1 - V_2) + V_T \right\} \cdot sC_2 \\ &= (g_m + sC_2) \cdot (V_1 - V_2) + V_T \cdot sC_2 \\ &= -\frac{(g_m + sC_2)}{sC_1} \cdot I_T + V_T \cdot sC_2 \end{aligned}$$

$$\Rightarrow Z_{in} = \frac{V_T}{I_T} = \frac{g_m + s(C_1 + C_2)}{s^2 C_1 C_2}$$

$$= \frac{g_m}{s^2 C_1 C_2} + \frac{1}{s C_{eq}} \quad \text{where } C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$

$$Z_{in}(j\omega) = -\frac{g_m}{\omega^2 C_1 C_2} + \frac{1}{j\omega C_{eq}}$$


i.e. equivalent circuit is

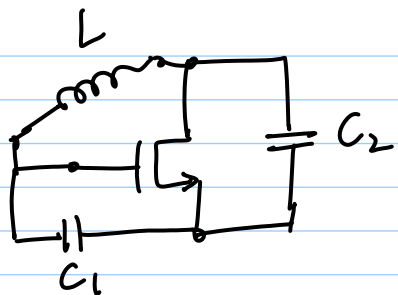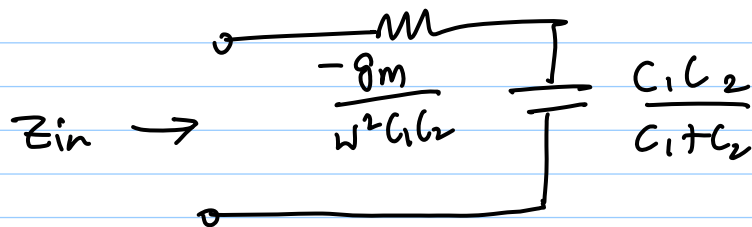


* For oscillations, we require

$$\frac{g_m}{\omega^2 C_1 C_2} \leq R_p$$

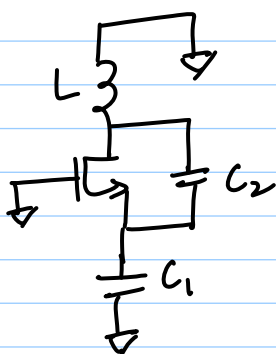
* Note that we can get 3 oscillator topologies by defining an AC ground
Ground gate \Rightarrow Colpitts oscillator




\Rightarrow
with
biasing

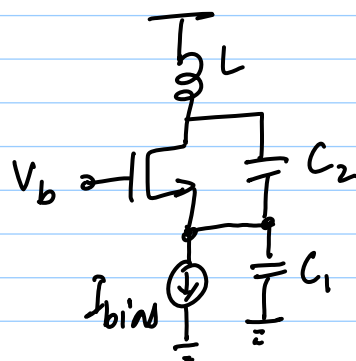


Ground source

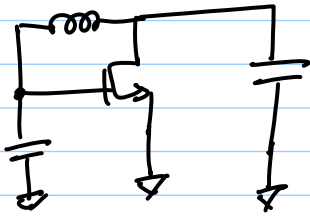


\Rightarrow
with
biasing

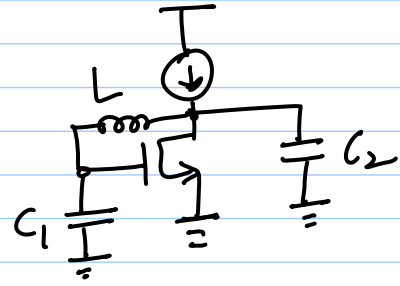


Ground drain

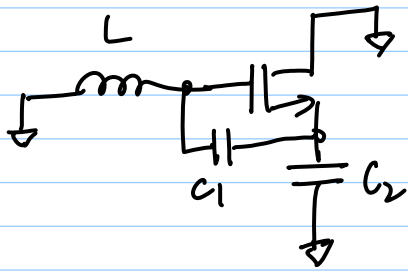


\Rightarrow
with
biasing

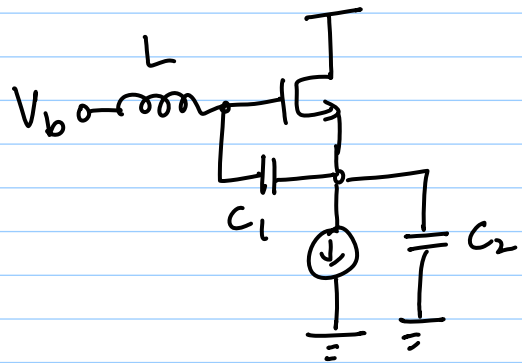

* back to FB model :

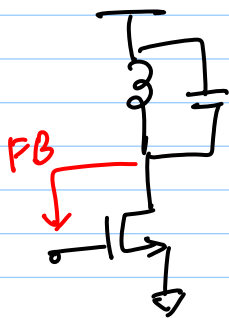

X

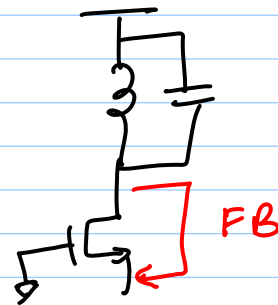


✓

\rightarrow (a) resonance, $z(\text{tank}) = R_p$

$\Rightarrow V$ & I are in-phase

total phase = 0 \Rightarrow f.b. signal goes to emitter

(without any additional phase in f.b.)

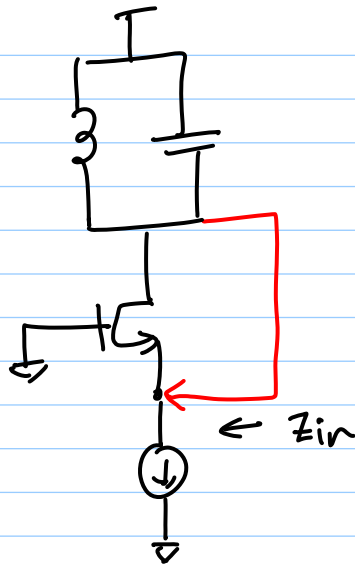


$$Z_{in} = \frac{1}{g_m + g_{mb}} + \frac{R_p}{(g_m + g_{mb})r_o}$$


neglect this

= low impedance

original tank

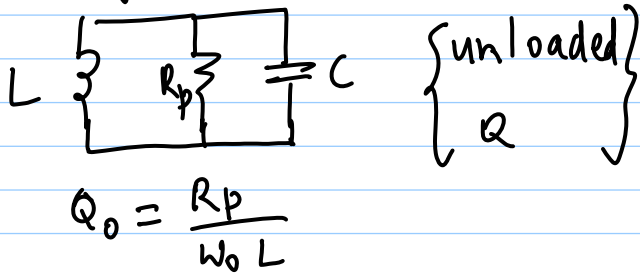



after f.b.

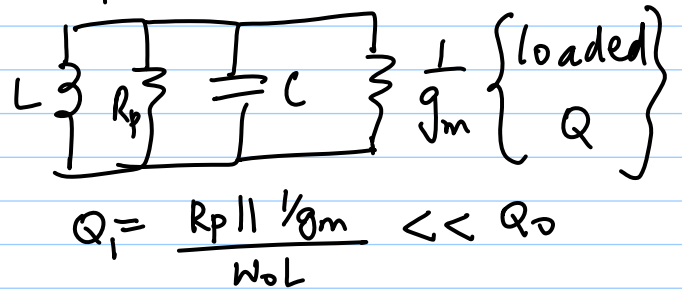

$\Rightarrow LQ$ can become $< 1 \Rightarrow$ no oscillations


\rightarrow Use an Impedance Xfmr

Explicit Xfmr

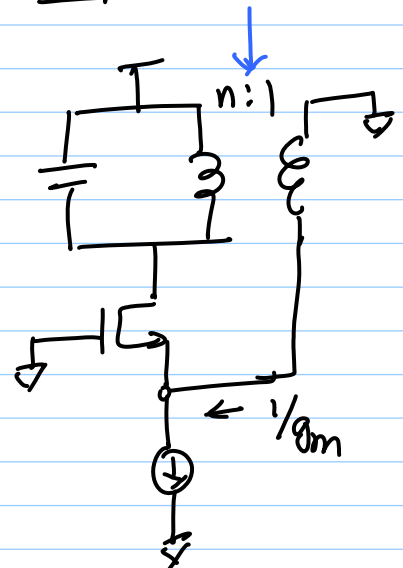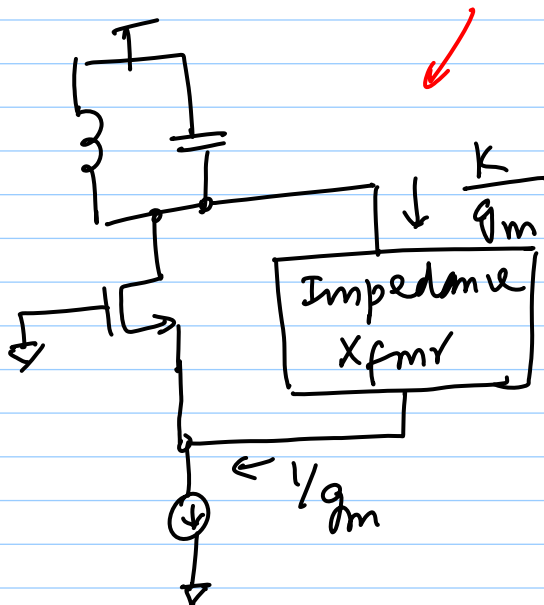


$\frac{n^2}{g_m}$ is seen by tank

Remember from impedance matching:

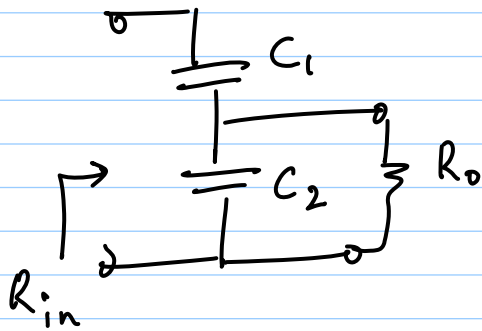
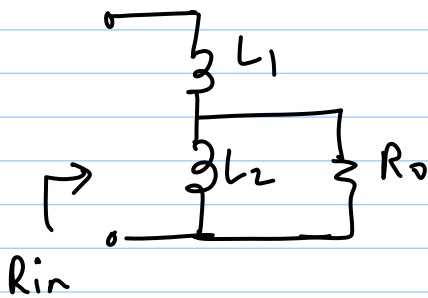
$$R_{in} = \left(1 + \frac{C_2}{C_1} \right)^2 R_0$$
$$= n^2 R_0$$



$$R_{in} = \left(1 + \frac{L_1}{L_2} \right)^2 R_0$$
$$= n^2 R_0$$