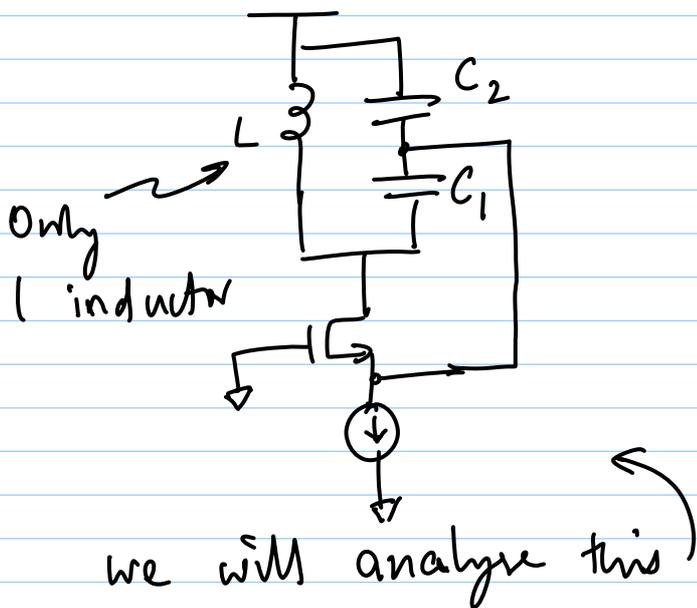



Lecture 29 : Colpitts Oscillator ; Quadratic Signal Generation

Colpitts oscillator




$$\omega_0 = \frac{1}{\sqrt{L - \frac{C_1 C_2}{C_1 + C_2}}}$$


Hartley oscillator

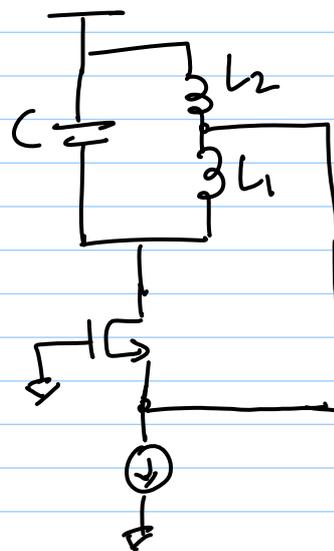

Colpitts oscillator

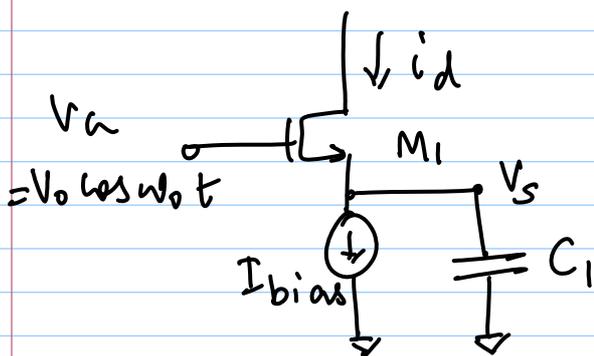

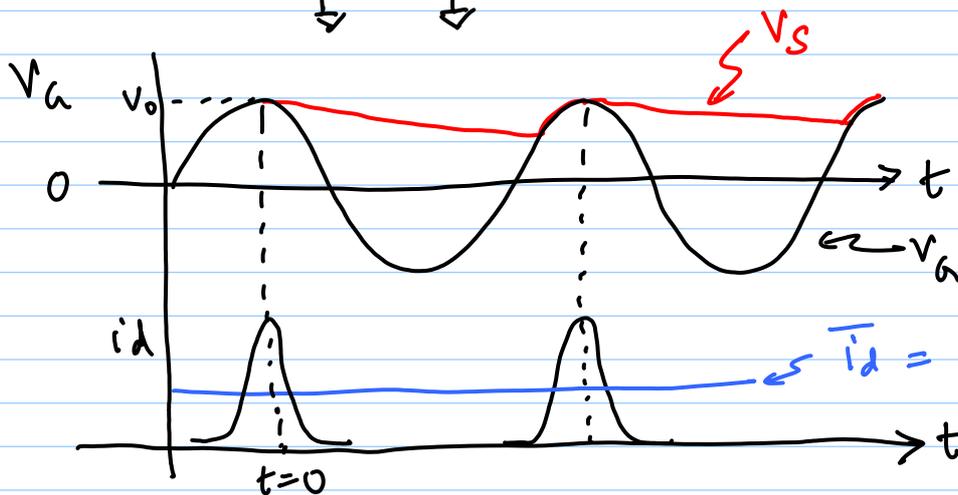- * Assume large amplitude
- * Assume $\omega_0 =$ high freq.
- * Assume C_1 is short @ ω_0



* M_1 conducts only when V_a is large ($\sim V_0$)
 \rightarrow when $V_a \ll V_0$, M_1 cuts off, I_{bias} discharges C_1

* $i_d =$ periodic pulses of current @ ω_0

Fourier series:

$$i_d(t) = I_0 + \sum_{n=1}^{\infty} \hat{I}_n \cos n\omega_0 t$$

$\rightarrow t=0$ reference = peak of $V_0 \cos \omega_0 t$

$$I_{DC}(C_1) = 0 \Rightarrow I_0 = I_{bias}$$

\rightarrow fundamental component of i_d is

$$\hat{I}_1 = \frac{2}{T} \int_0^T i_d(t) \cos \omega_0 t dt$$

$$\approx \frac{2}{T} \int_0^T i_d(t) dt \quad \left\{ \begin{array}{l} \text{current exists} \\ \text{only @ peak } V_a \end{array} \right.$$

$$\hat{I}_1 = 2I_{bias}$$

* If i_d flows through a tank tuned to ω_0 ,
 only \hat{I}_1 creates a voltage

$$G_m \approx \frac{\hat{I}_1}{V_0} = \frac{2I_{bias}}{V_0}$$

\leftarrow applicable to
any device

\leftarrow assume V_S is

Recall that

$$g_m (\text{long channel}) = \frac{2I_{bias}}{V_{DSAT}}$$

constant (due
to C_1)

short-channel!



$$I_D = \mu_n \frac{C_{ox}}{2} \left(\frac{W}{L}\right) (V_{GS} - V_T) \cdot L E_c \quad (\text{vel. sat.})$$


$$\Rightarrow g_m = \frac{\partial I_D}{\partial V_{GS}} = \frac{I_{bias}}{V_{DSAT}}$$

\Rightarrow in general,

$$\frac{I_{bias}}{V_{DSAT}} \leq g_m \leq \frac{2 I_{bias}}{V_{DSAT}}$$
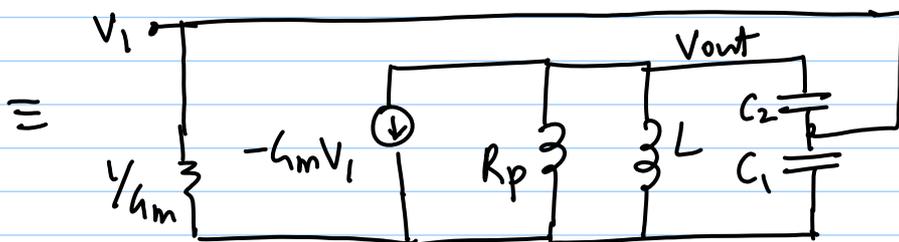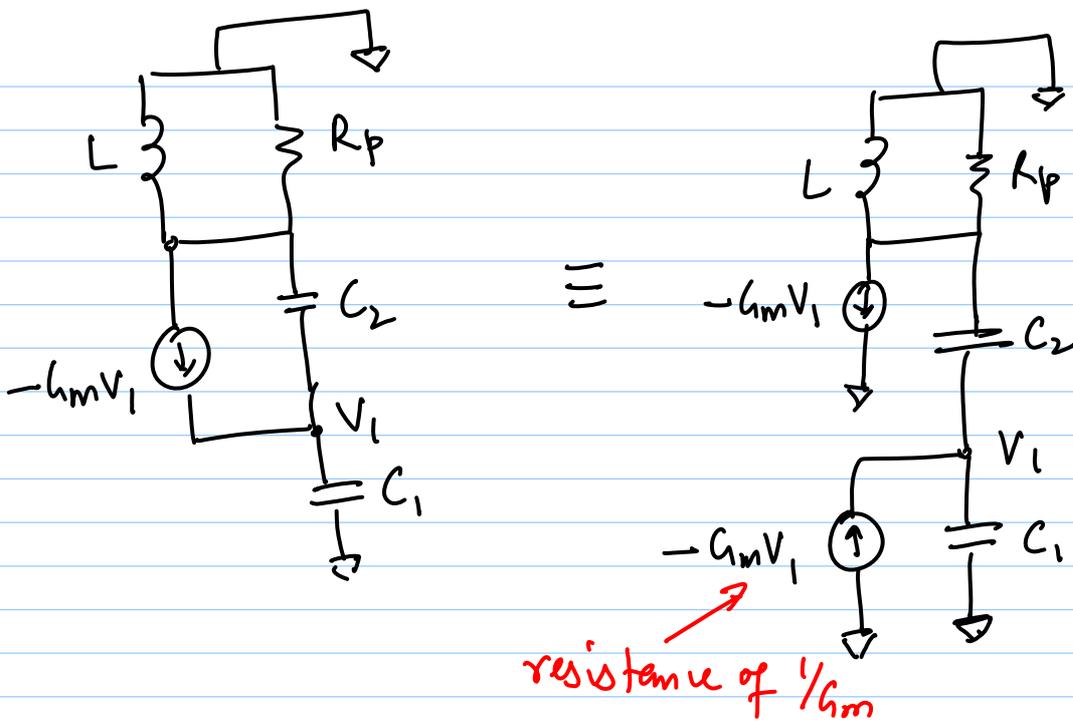
$$\Rightarrow \boxed{\frac{V_{DSAT}}{V_0} \leq \frac{G_m}{g_m} \leq \frac{2 V_{DSAT}}{V_0}}$$



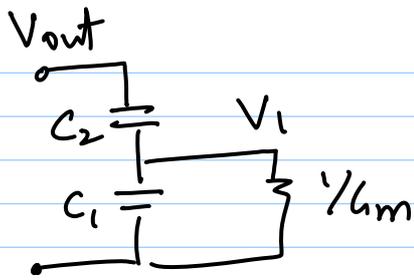


assume $1/g_m$ does not load
the cap divider
(i.e. $Q \gg 1$)


$$V_1 = \frac{C_2}{C_1 + C_2} \cdot V_{out} = \frac{1}{n} \cdot V_{out}$$

$$n = \frac{C_1 + C_2}{C_2} = 1 + \frac{C_1}{C_2} \leftarrow \text{equivalent trans ratio}$$

equivalent ckt:

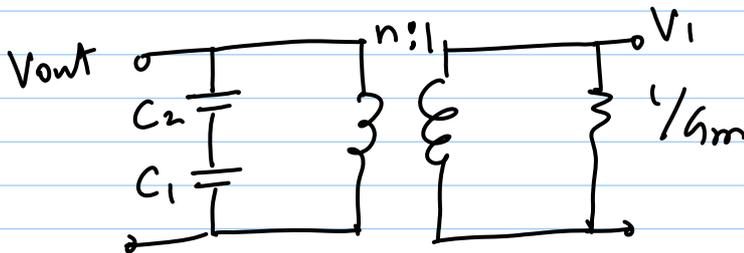

overall oscillator ckt becomes:

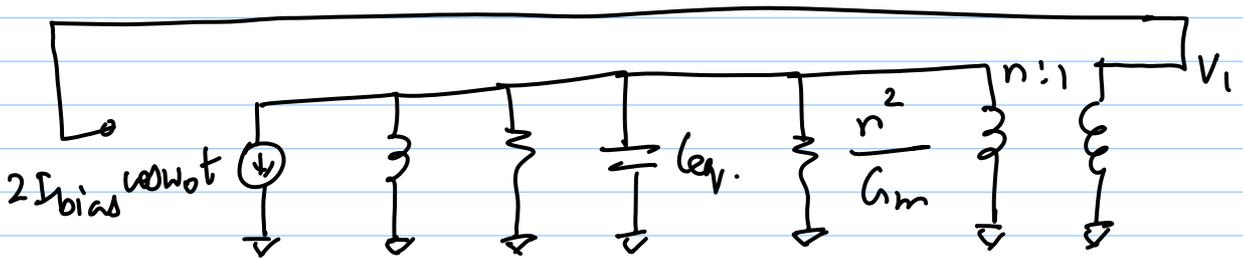

$$C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$

resonance: set $\omega_0 = \frac{1}{\sqrt{L \cdot C_{eq}}}$

$$V_{out} = 2 I_{bias} \cdot R_p \parallel \frac{n^2}{G_m}$$

$$= 2 I_{bias} \cdot \frac{R_p \cdot n^2 / G_m}{R_p + n^2 / G_m}$$

$$= \frac{2 I_{bias} R_p}{1 + \frac{R_p G_m}{n^2}}$$

$$\Rightarrow V_{out} \left[1 + \frac{R_p G_m}{n^2} \right] = 2 I_{bias} R_p$$


$$V_{out} \left[1 + \frac{R_p}{n^2} \cdot \frac{2 I_{bias}}{V_{out}/n} \right] = 2 I_{bias} R_p$$

$$\Rightarrow V_{out} + \frac{2 I_{bias} R_p}{n} = 2 I_{bias} R_p$$

$$V_{out} = 2 I_{bias} R_p \left(1 - \frac{1}{n} \right)$$


* For startup, use small-signal g_m

Quadrature Signal Generation

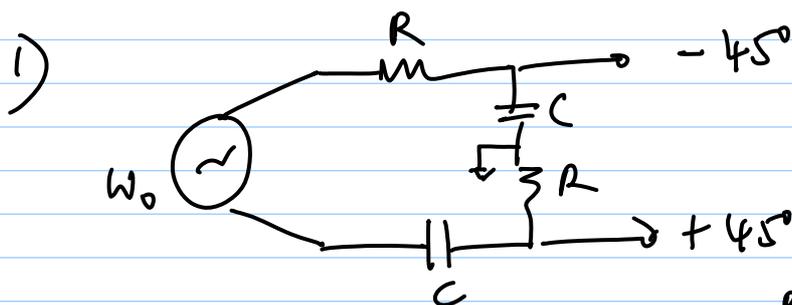

← we discussed this before


Polyphase Filter

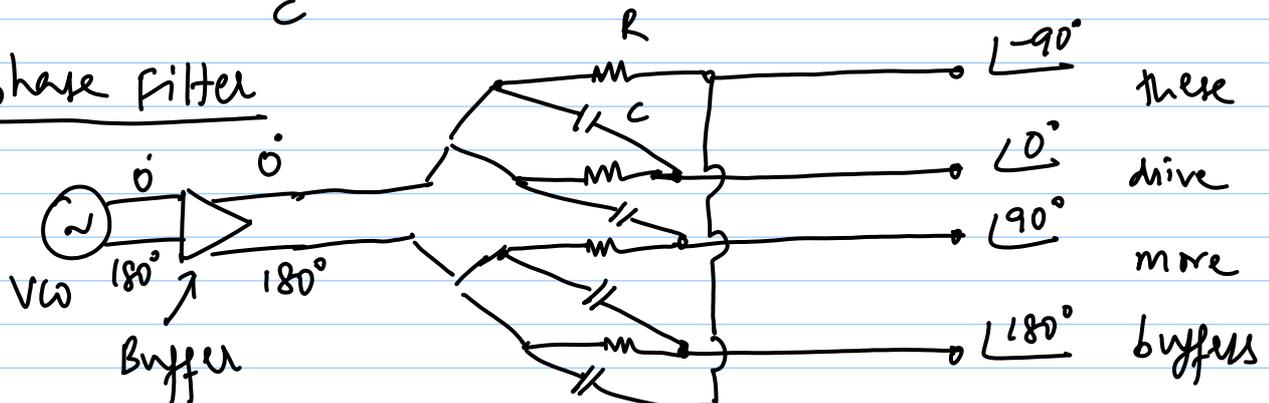

* Buffers consume extra power

* R, C mismatches affect phase error


2)

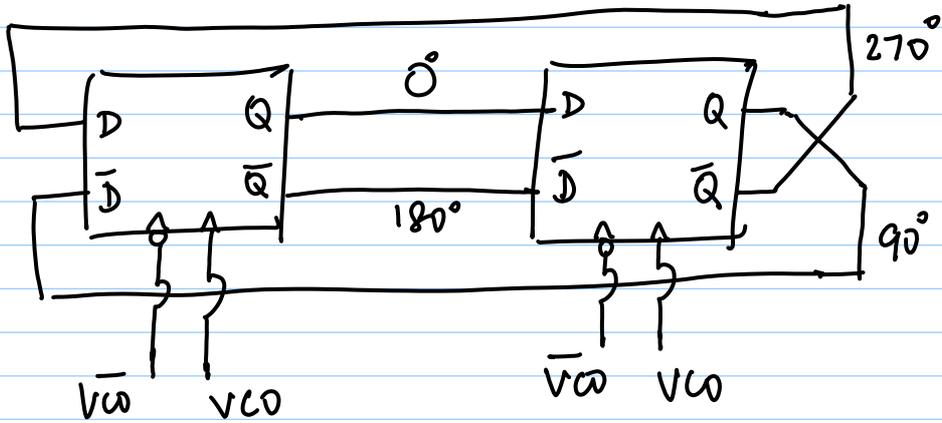

- * Basically a synchronous counter (that counts to 2)
- * power consumption @ high frequencies \uparrow

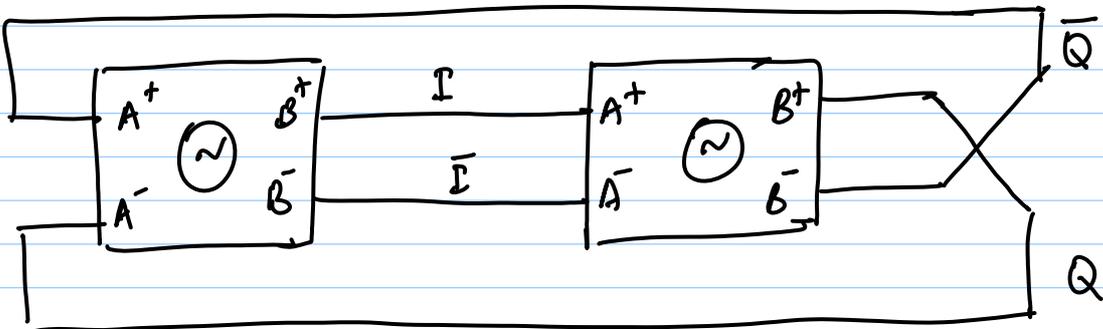
3) Quadrature VCOs

- * Couple 2 identical oscillators in quadrature



- * A - inputs (coupling)
- * B - oscillator output


a) parallel coupling

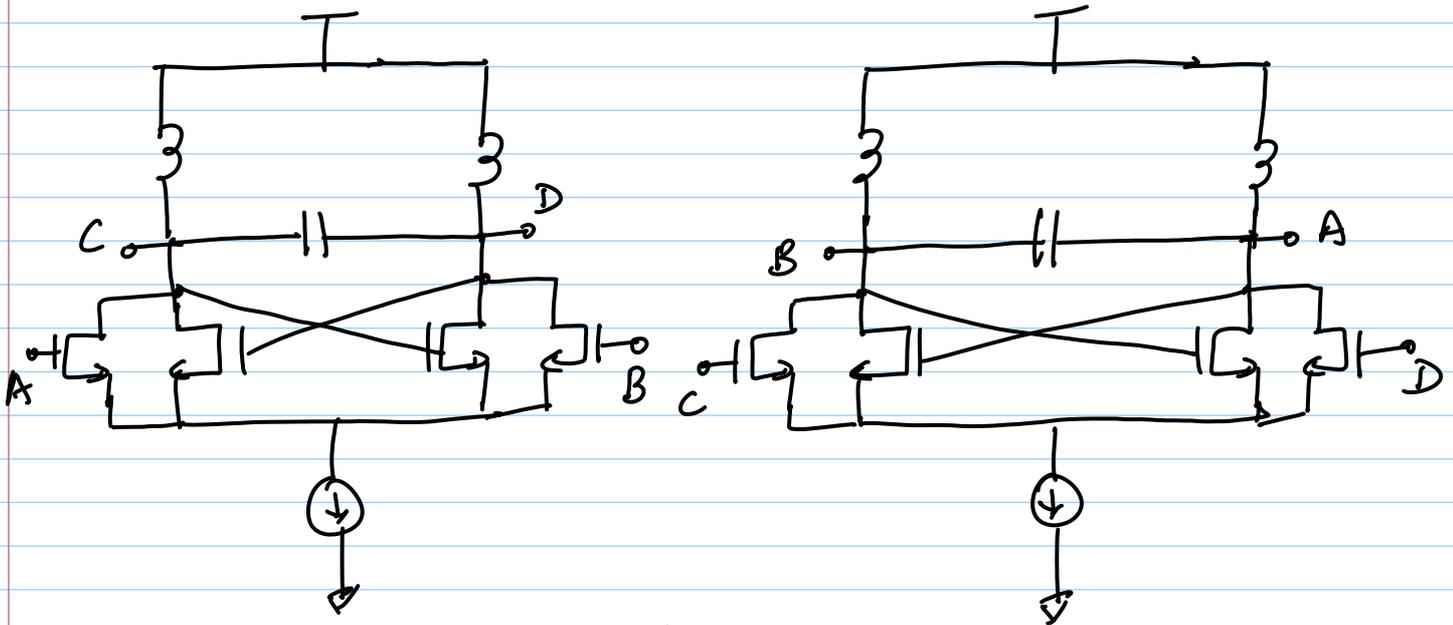

* Exercise: Analyse the det with waveforms
→ assume outputs @ 0° & 180° phases and

see what happens (both cases will result in no oscillations - i.e. any $0^\circ/180^\circ$ components will die out)

b) Series coupling

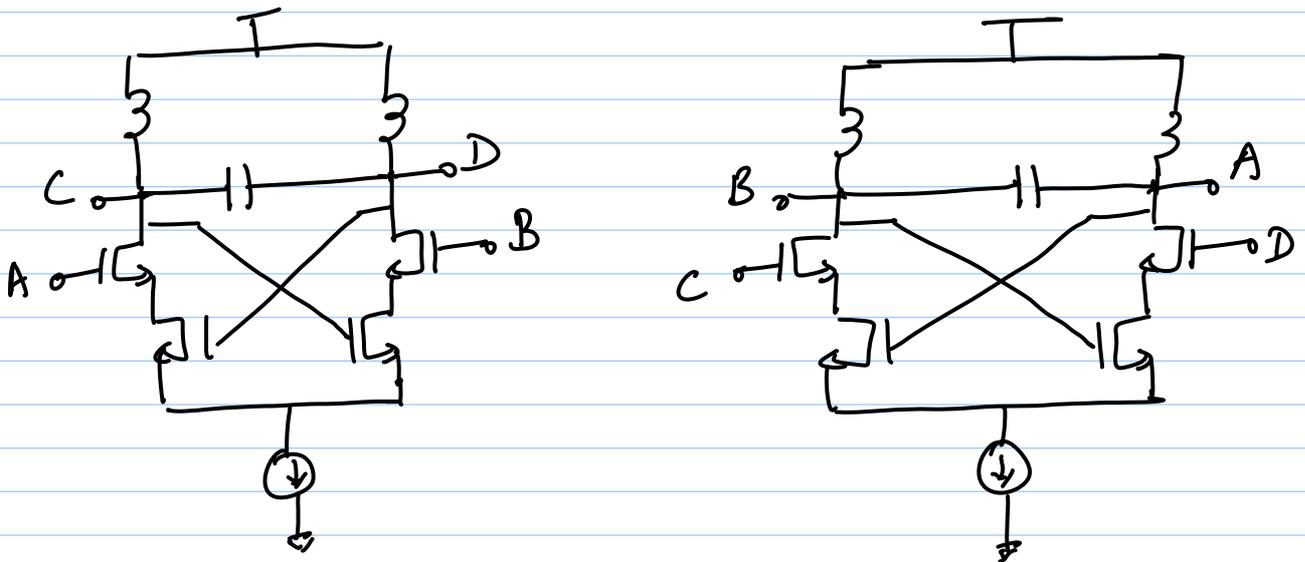


* (a) & (b) : extra parasitic cap on tank (\downarrow tuning range)

* (b) : quadrature coupling devices have to be much larger than uncoupled devices (to increase headroom for CC devices)

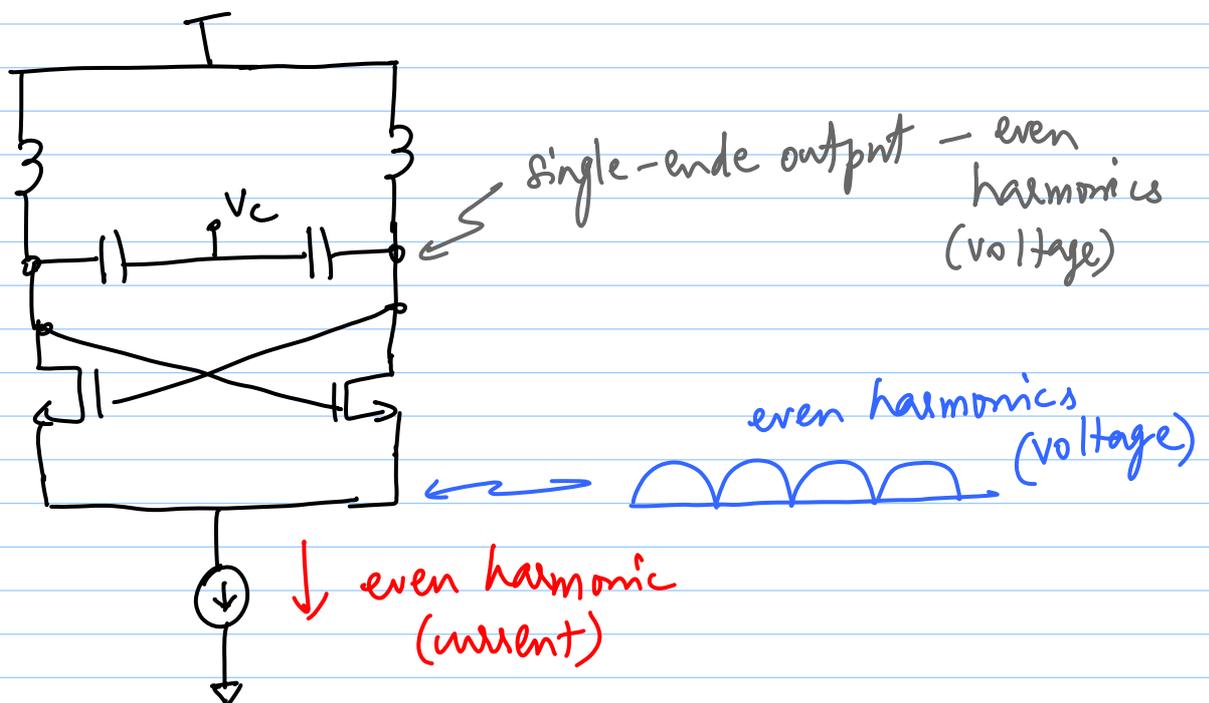
(c) Harmonic injection

* Single-ended outputs
Common-mode nodes
Common-mode paths } even harmonics exist in voltages and/or currents


* Harmonics have specific phase relationship with fundamental freq.




(i) C-S. coupling

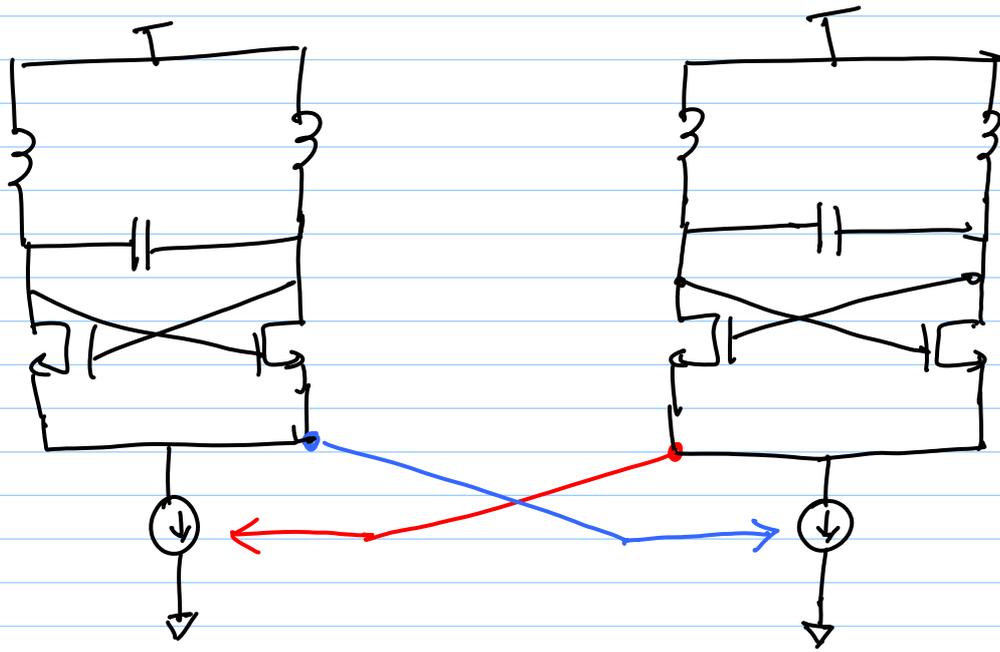


(ii) Capacitive coupling

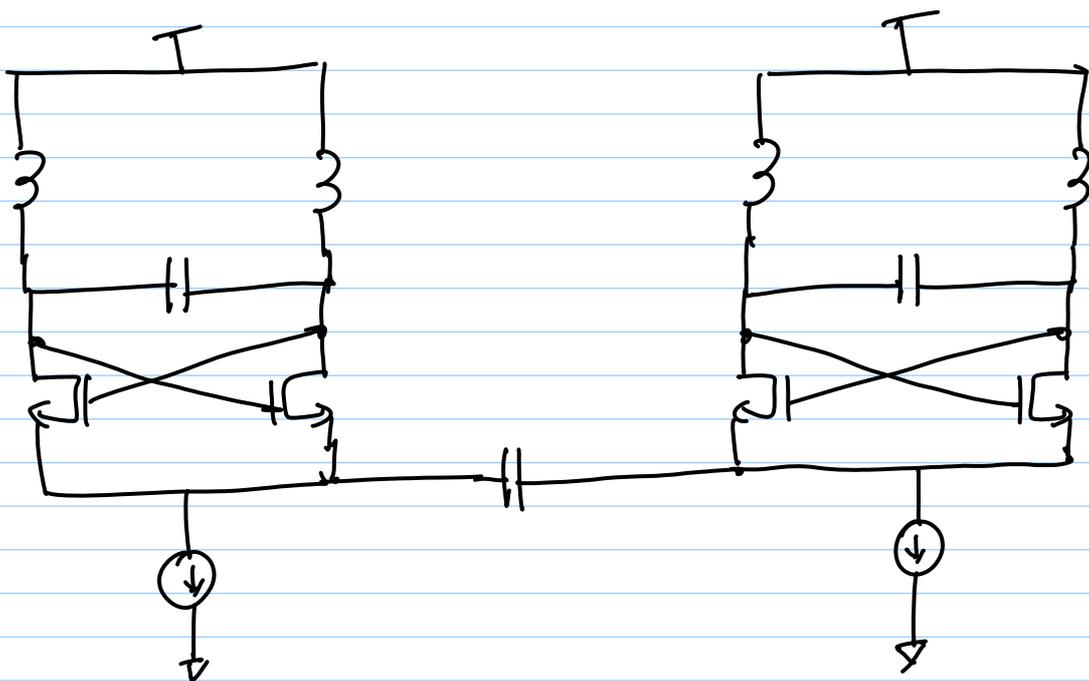

(iii) Transformer coupling

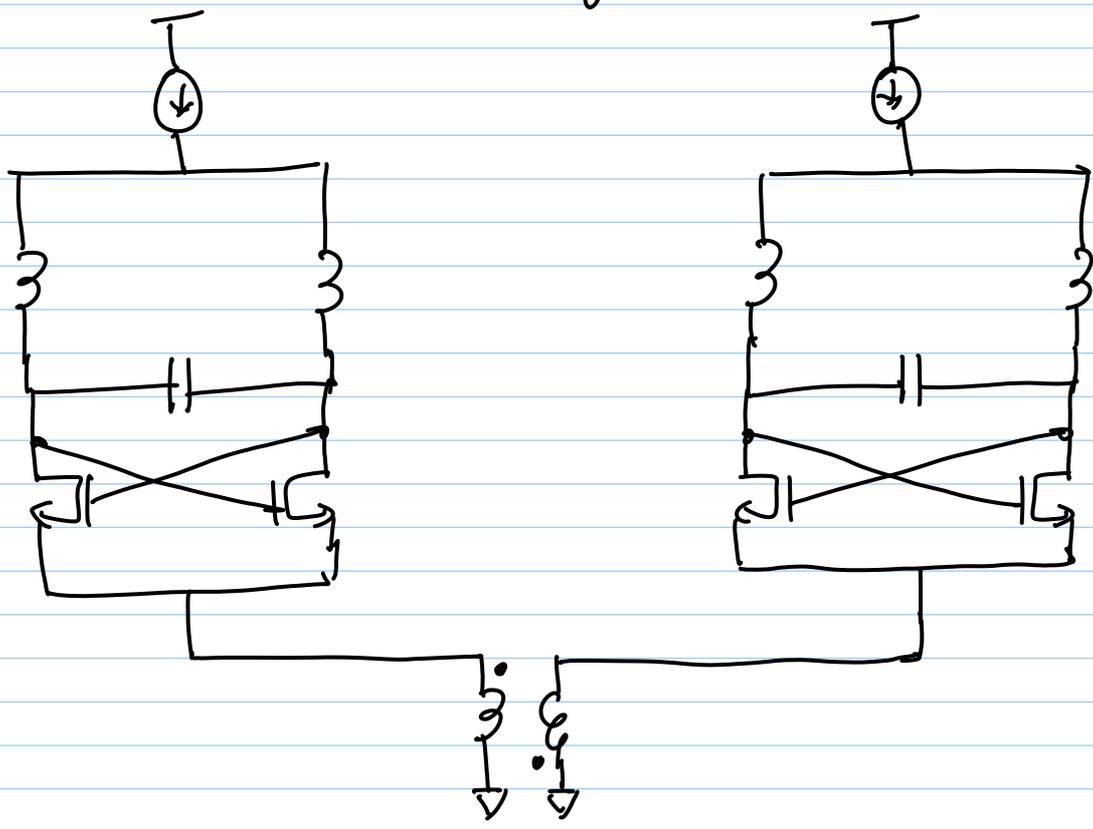






(iv) Backgate coupling

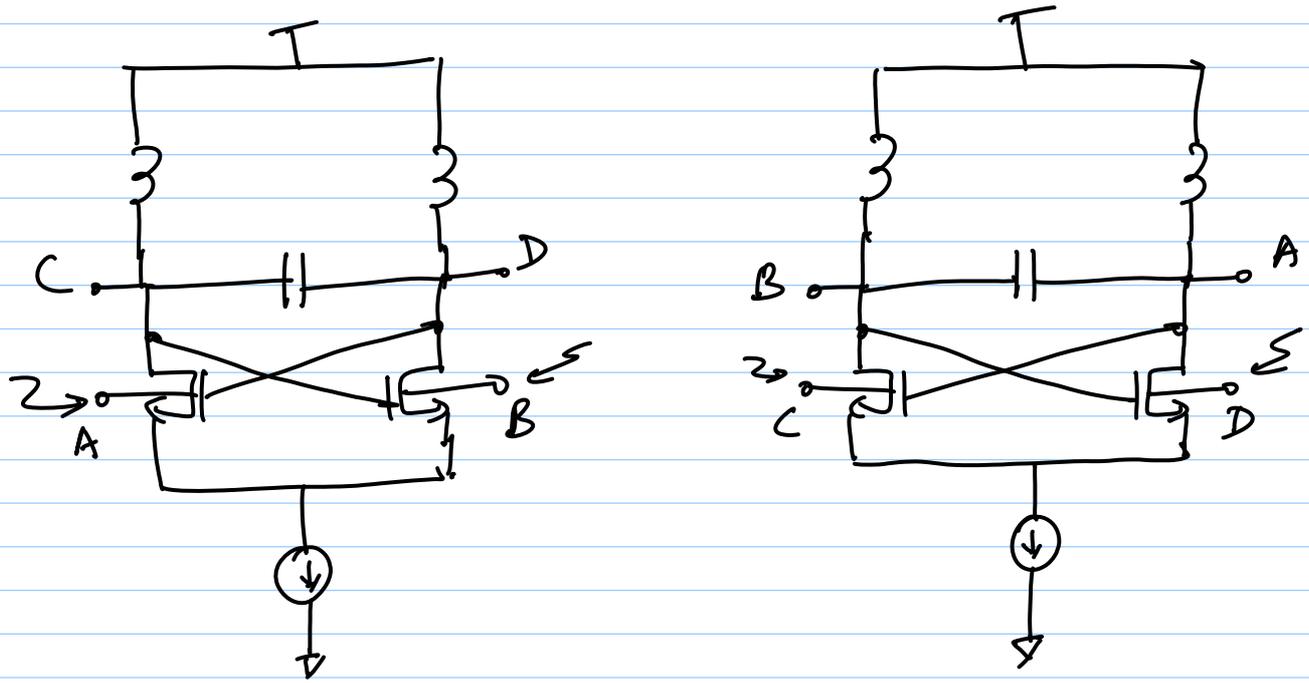

Other features of the VCO

1) tuning & tuning range

varactor is a 2-terminal device
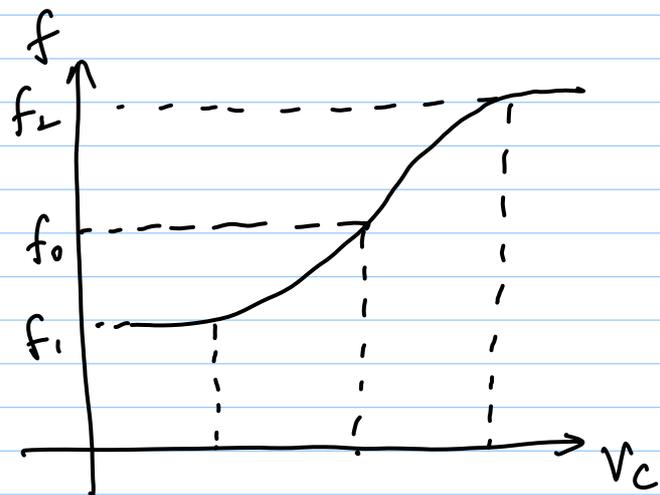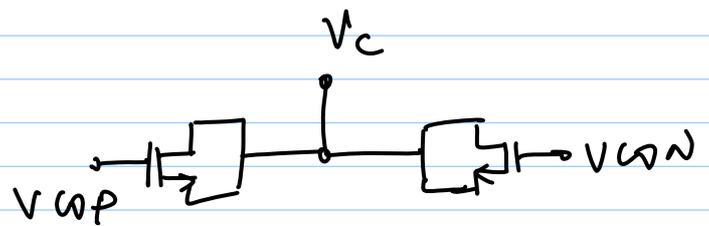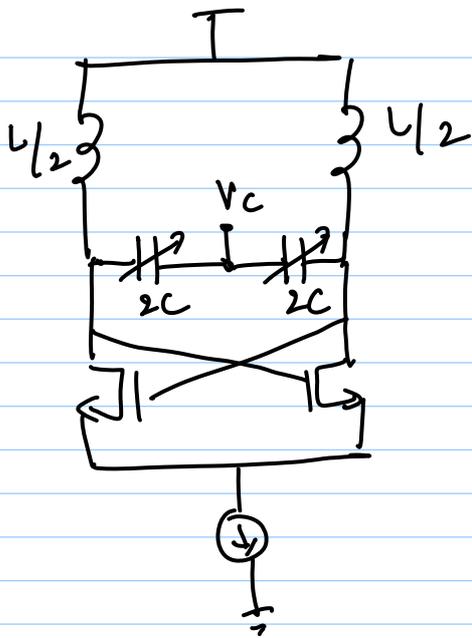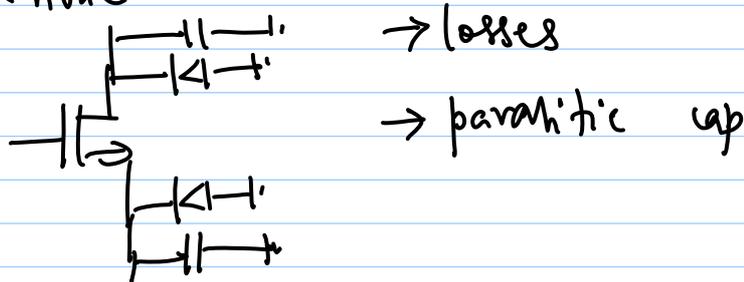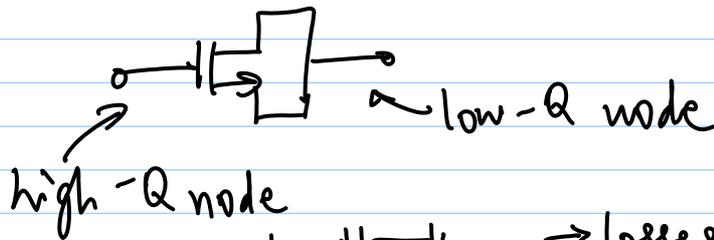
$$\left. \begin{array}{l} \text{tuning} \\ \text{range} \end{array} \right\} = \frac{f_2 - f_1}{f_0}$$


2) centre frequency $f_0 = \frac{f_1 + f_2}{2}$

3) VCO gain

$$K_{VCO} = \frac{f_2 - f_1}{\Delta V_c} \quad \left\{ \text{typically MHz/V} \right\}$$

4) Power consumption

5) Supply pushing/rejection

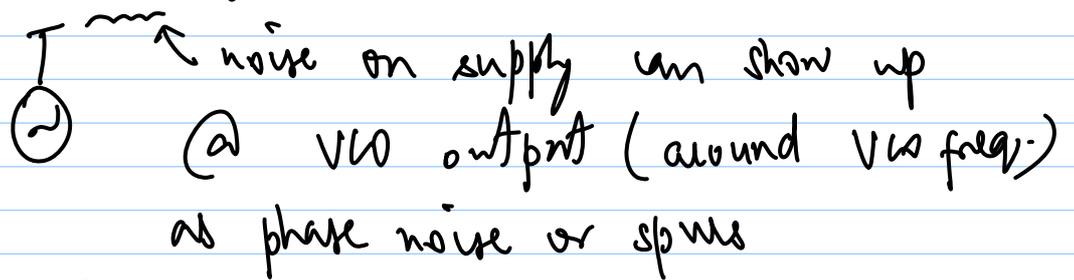

6) Phase noise