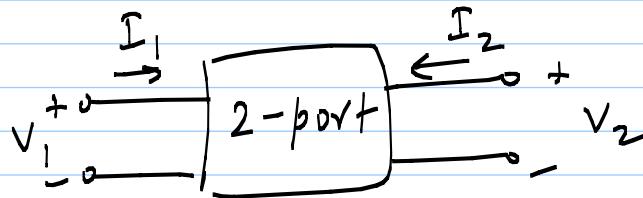


Lecture #3 - S-parameters, ABCD parameters, Resonance

Recall :



$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

In general, $[V] = [Z] \cdot [I]$


By $[Y]$, $[H]$, $[A]$ can also be defined

All of these relate voltages and currents of the network

For a distributed network, we talk of incident & reflected waves.

⇒ Scattering (S-) parameters

$$[V_r] = [S] \cdot [V_i]$$

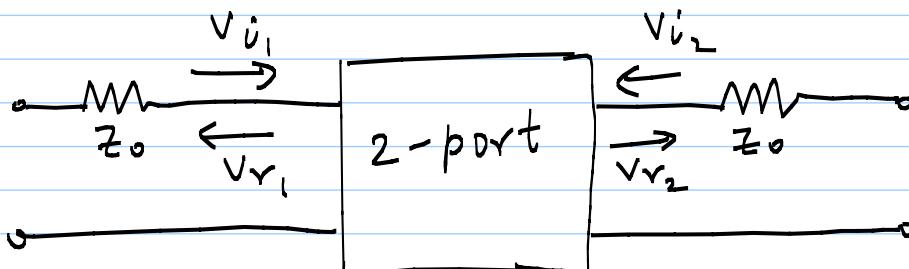

$$\begin{bmatrix} V_{r1} \\ V_{r2} \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \begin{bmatrix} V_{i1} \\ V_{i2} \end{bmatrix}$$

Usually normalized w.r.t. Z_0 :

$$a_1 = \frac{V_{i_1}}{\sqrt{Z_0}} ; \quad a_2 = \frac{V_{i_2}}{\sqrt{Z_0}}$$

$$b_1 = \frac{V_{r_1}}{\sqrt{Z_0}} ; \quad b_2 = \frac{V_{r_2}}{\sqrt{Z_0}}$$

$$\begin{bmatrix} b_1 \\ b_2 \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix}$$

$a_1^2, a_2^2, b_1^2, b_2^2 \Rightarrow$ powers of incident & reflected waves

S_{ij} are usually represented in dB
i.e. $20 \log(\text{value})$

$$S_{11} = \left. \frac{b_1}{a_1} \right|_{a_2=0} = \frac{V_{r_1}}{V_{i_1}} = \Gamma_1 \quad (\text{input reflection coefficient})$$

$$S_{21} = \left. \frac{b_2}{a_1} \right|_{a_2=0} = \frac{V_{r_2}}{V_{i_1}} \quad (\text{gain})$$

$$S_{21}^2 = \frac{V_{r_2}^2}{V_{i_1}^2} = \frac{V_{r_2}^2 / Z_0}{V_{i_1}^2 / Z_0} = \text{power gain}$$

$$S_{22} = \left. \frac{b_2}{a_2} \right|_{a_1=0} = \frac{V_{r_2}}{V_{i_2}} = \Gamma_2 \quad (\text{output port reflection coefficient})$$

$$S_{12} = \left. \frac{b_1}{a_2} \right|_{a_1=0} = \frac{V_{r_1}}{V_{i_2}} \quad (\text{reverse transmission gain})$$

Short note on units etc :

let x be any linear electrical value (e.g.

$$x \text{ (in dB)} = 20 \log(x) \quad \begin{matrix} V, I \\ \text{etc.} \end{matrix}$$

power $P \propto V^2$ or I^2

$$\therefore P \text{ (in dB)} = 10 \log(P)$$

$$P \text{ (in dBm)} = 10 \log\left(\frac{P}{1mW}\right)$$

i.e. 0dB reference value is 1mW

$$1mW \text{ in dBm} = 10 \log\left(\frac{1mW}{1mW}\right) = 0 \text{ dBm}$$

$$10mW \text{ in dBm} = 10 \log(10) = 10 \text{ dBm}$$

If $Z_0 = 50\Omega$, 0dBm corresponds to $\approx 223mV_{rms}$

We can also talk about dBV etc.

$$1V \longleftrightarrow 0 \text{ dBV}$$


$$dB_C \equiv \text{power w.r.t. carrier}$$

"C" \rightarrow 0dB reference is power of carrier
 \Rightarrow used for noise, distortion etc.

ABCD parameters (Transmission matrix)

very useful for cascaded 2-ports
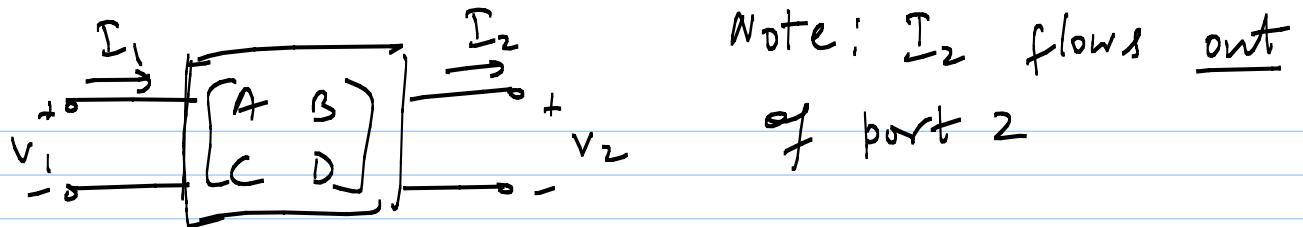
$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$



Consider a cascade of two 2-port networks

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$

$$\begin{bmatrix} V_2 \\ I_2 \end{bmatrix} = \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix} \begin{bmatrix} V_3 \\ I_3 \end{bmatrix}$$

$$\Rightarrow \begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix} \begin{bmatrix} V_3 \\ I_3 \end{bmatrix}$$

can easily relate input & output of cascade.

LHW 1 will include the following:

1) Derive $[S]$ in terms of $[Z]$

2) Derive $[ABCD]$ in terms of $[Z]$

Resonance:

All (narrowband) RF systems employ resonance


- * tuned bandpass amplifiers

- * impedance transformations and matching


- * RF oscillators

Series and Parallel RLC categories


Parallel RLC

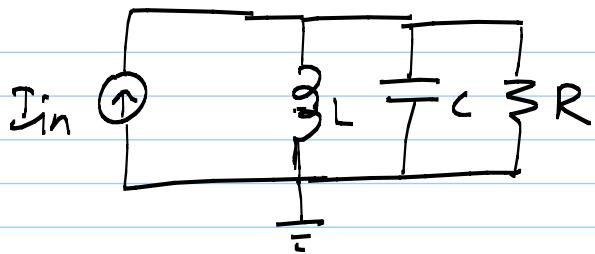


Intuitively:

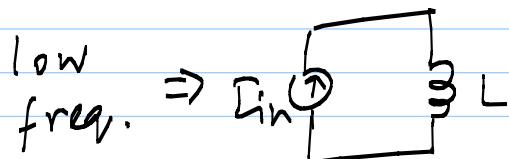

inductive

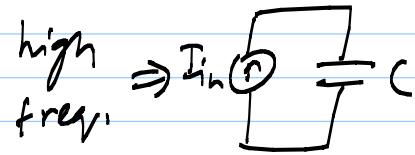

capacitive

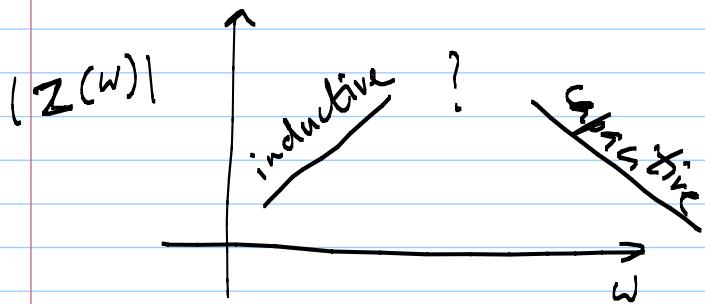

what happens
in-between?

$$\text{Admittance } Y(w) = \frac{1}{R} + jwC + \frac{1}{jwL}$$


$$= \frac{1}{R} + j\left(wC - \frac{1}{wL}\right)$$


$$\text{At resonance, } w_0 C = \frac{1}{w_0 L} \Rightarrow w_0^2 = \frac{1}{LC}, \quad w_0 = \frac{1}{\sqrt{LC}}$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

Do not confuse
 ω (rad/s) & f (Hz)

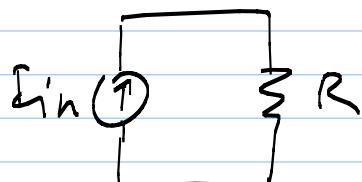
$$Y(w_0) = \frac{1}{R} \Rightarrow \text{purely resistive}$$



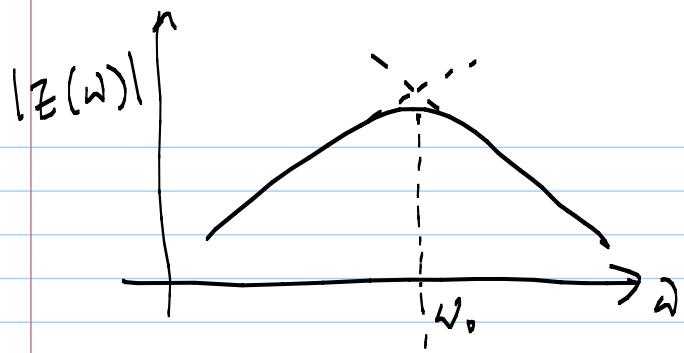

convenient on-chip values:
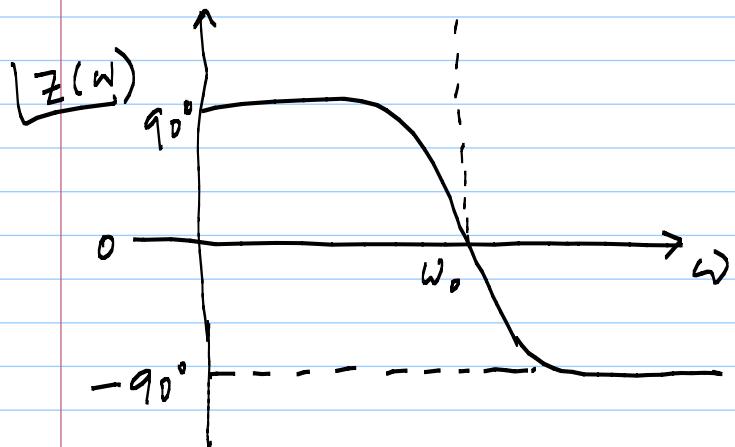
$$1\text{ pF} \parallel \text{Int} \approx 5\text{ GHz}$$




Quality Factor (physical definition)

$$Q \equiv \omega \cdot \frac{\text{Energy stored}}{\text{Average Power dissipated}}$$

$$\text{at } \omega = \omega_0, V_{\text{out}} = I_{\text{in}} \cdot R$$

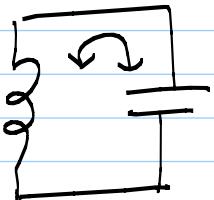stored energy moves back and forth between $L \leftrightarrow C$



$$V_{\text{out}, \text{pk}} = I_{\text{pk}} \cdot R \Rightarrow E_{\text{tot.}} = \frac{1}{2} C (I_{\text{pk}} \cdot R)^2$$

$$P_{\text{ave}} = (I_{\text{RMS}})^2 \cdot R = \left(\frac{I_{\text{pk}}}{\sqrt{2}}\right)^2 \cdot R = \frac{1}{2} I_{\text{pk}}^2 R$$

$$\Rightarrow Q = \omega_0 \cdot \frac{E_{\text{tot.}}}{P_{\text{ave}}} = \frac{1}{\sqrt{L/C}} \cdot \frac{\frac{1}{2} C I_{\text{pk}}^2 R^2}{\frac{1}{2} I_{\text{pk}}^2 R}$$

$$Q = \frac{R}{\sqrt{L/C}}$$

Intuitive check: at $R \rightarrow \infty, Q \rightarrow \infty$

seems correct \Rightarrow no average power dissipated

$$\sqrt{\frac{L}{C}} = \underline{\text{characteristic impedance of network}}$$

At resonance,

$$|Z_L| = \omega_0 L = \frac{L}{\sqrt{L/C}} = \sqrt{\frac{L}{C}}$$


$$|Z_C| = \frac{1}{\omega_0 C} = \frac{\sqrt{L/C}}{C} = \sqrt{\frac{L}{C}}$$

Basic forms of Q for parallel RLC:

$$Q = \frac{R}{\sqrt{L/C}}$$

$$Q = \frac{R}{|Z_L|} = \frac{R}{\omega_0 L}$$

$$Q = \frac{R}{|Z_C|} = \omega_0 R C$$

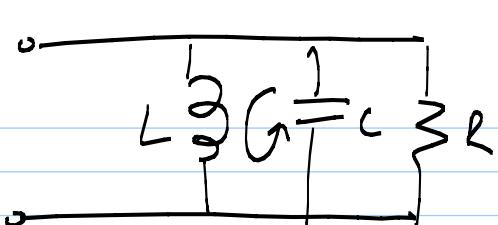

Beware! Branch currents
at resonance

$$|I_L| = |I_C| = \frac{|V_{0\text{out}}|}{\omega_0 L} = \frac{|I_{in}|R}{\omega_0 L} = Q \cdot |I_{in}|$$

- * very large currents can flow through L & C at resonance
- * careful layout is required to ensure current carrying capability (esp. for C)
- * It is dangerous to think of resonance as L & C "canceling" each other out!

BW & Q relationship:

Calculate impedance close to resonance
at a frequency $\omega = \omega_0 + \Delta\omega$

$$Y(\omega) = \frac{1}{R} + j \left(\omega C - \frac{1}{\omega L} \right)$$

$$= \frac{1}{R} + \frac{j}{\omega L} \left(\omega^2 LC - 1 \right)$$

$$Y(\omega_0 + \Delta\omega) = \frac{1}{R} + \frac{j}{(\omega_0 + \Delta\omega)L} \left[(\omega_0 + \Delta\omega)^2 LC - 1 \right]$$


$$= \frac{1}{R} + \frac{j}{\omega_0 L \left(1 + \frac{\Delta\omega}{\omega_0} \right)} \cdot \left[\cancel{\omega_0^2 LC + 2\omega_0 \Delta\omega LC} + \cancel{\Delta\omega^2 LC - 1} \right]$$


$$Y(\omega_0 + \Delta\omega) = \frac{1}{R} + \frac{j}{\cancel{\omega_0 L \left(1 + \frac{\Delta\omega}{\omega_0} \right)}} \cdot \cancel{\omega_0 \Delta\omega C} \left[2 + \frac{\Delta\omega}{\omega_0} \right]$$

$$\approx \frac{1}{R} + j \Delta\omega C \left(2 + \frac{\Delta\omega}{\omega_0} \right) \left(1 - \frac{\Delta\omega}{\omega_0} \right)$$

$$= \frac{1}{R} + j \Delta\omega C \left[2 - \frac{2\Delta\omega}{\omega_0} + \frac{\Delta\omega}{\omega_0} - \left(\frac{\Delta\omega}{\omega_0} \right)^2 \right]$$

$$\approx \frac{1}{R} + j 2 \Delta\omega C \quad \left\{ \text{neglecting } \Delta\omega^2, \Delta\omega^3 \right\}$$

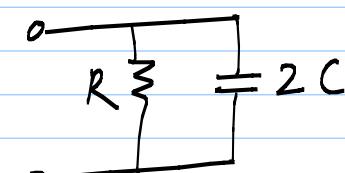equivalent circuit \Rightarrow 

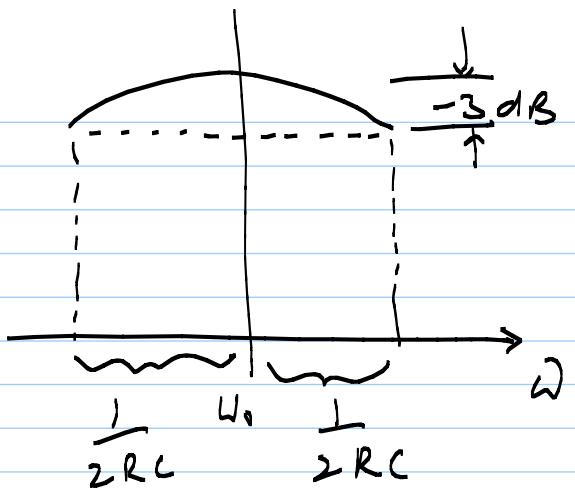

by symmetry,

$$\text{total } BW = \frac{1}{RC}$$

$$\frac{\omega_0}{BW} = \frac{RC}{\sqrt{LC}} = \frac{R}{\sqrt{L/C}} = Q$$

Different definitions of Q:

1) Fundamental physical definition:

$$Q \equiv \omega_0 \frac{E_{tot.}}{P_{ave}}$$


also applicable to distributed systems and non-resonant systems (e.g. Q of an RC network)

$$2) Q = \frac{\text{Im}(Z(\omega))}{\text{Re}(Z(\omega))}$$

$$3) Q = \frac{\omega_0}{BW}$$


$$4) Q = \frac{\omega_0}{2} \left| \frac{d\phi}{d\omega} \right| \quad \text{where } \phi(\omega) = \text{phase of open loop TF.}$$

Series RLC networks

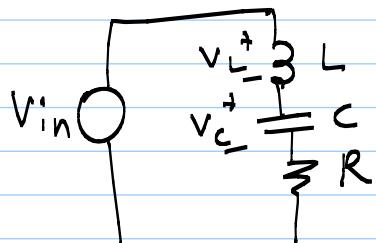


intuitively:

low-freq.

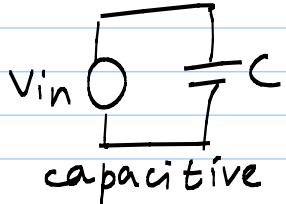

capacitive

high freq

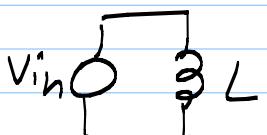


inductive

At resonance, reactive impedances are equal and opposite $\Rightarrow V_L + V_C = 0$


$$Z(\omega) = R + j\omega L + \frac{1}{j\omega C} = R + j(\omega L - \frac{1}{\omega C})$$

$$\omega_0 = \frac{1}{\sqrt{LC}} ; f_0 = \frac{1}{2\pi\sqrt{LC}}$$

network behaves as if purely resistive

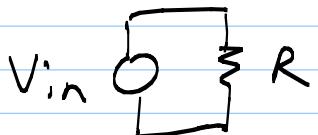

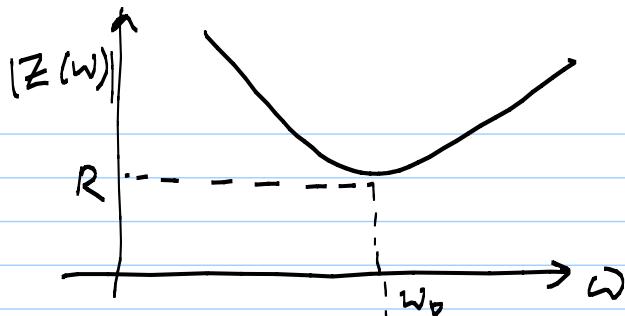Note! HW1 will have a problem on deriving $Z(\omega)$ & Q expressions for series RLC networks



Prove for yourself:

$$|V_L| = |V_C| = |V_{in}| \cdot Q$$

\Rightarrow Useful for passive

Voltage amplification
in LNAs

Series LC is not just
a short!

