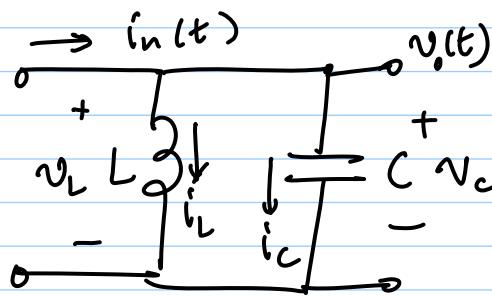


## Lecture 32 : VCO Design

ISF




initially,  $v_o(t)$  is

$$v_o(t) = V_0 \cos \omega_0 t$$

current pulse @  $t = \tau$   
 $\Rightarrow i_{in}(t) = \Delta q / \delta(t - \tau)$

\* Use superposition

because the system  
is linear

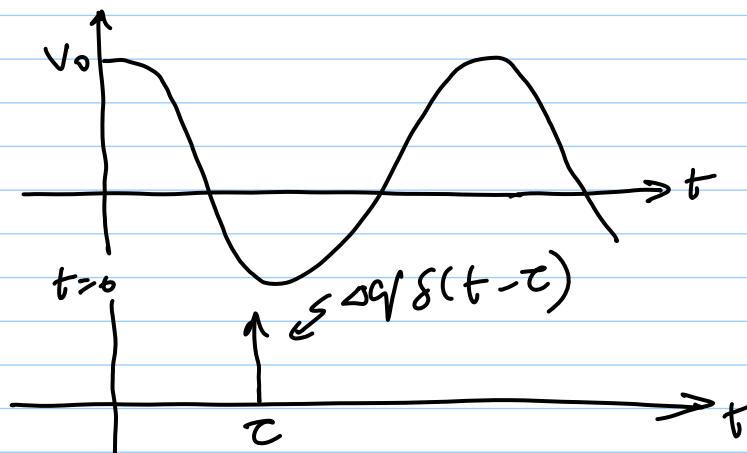

\* Current pulse of  
 $\Delta q / \delta(t - \tau) \Rightarrow$  charge  
of  $\Delta q$  is injected into  
LC tank


how does current pulse split between L & C?

→ if any portion of  $i_{in}(t)$  pulse flows through  
L  $\Rightarrow v_L = \infty$

→ all of  $i_{in}(t)$  flows through cap. C

$$i_C = C \frac{d v_C}{dt}$$

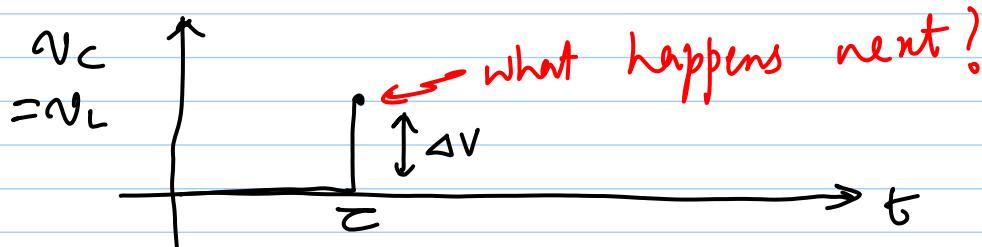→  $v_C$  experiences a voltage step due  
to  $i_{in}(t)$




$$\text{charge } q = \int i_n(t) dt = Q_n$$

$$\Rightarrow \Delta q = C \Delta V \Rightarrow \boxed{\Delta V = \frac{\Delta q}{C}}$$

If this initial charge sets up oscillations in the LC system

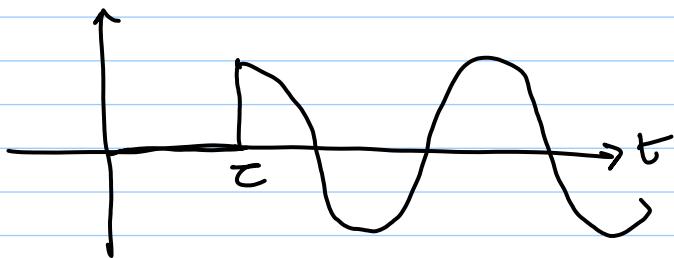$\rightarrow$  energy switches back & forth between  $L$  &  $C$



$$v_2(t) = \Delta V \cos [\omega_0(t - \tau)]$$

$$v_o(t) = v_1(t) + v_2(t) \quad \{ \text{superposition} \}$$

$$= V_0 \cos \omega_0 t + \Delta V \cos \omega_0 (t - \tau)$$

$$v_o(t) = V_0 \cos \omega_0 t + \Delta V \cos \omega_0 (t - \tau)$$

$$= V_0 \cos \omega_0 t + (\Delta V \cos \omega_0 \tau) \cdot \cos \omega_0 t$$

$$+ (\Delta V \sin \omega_0 \tau) \cdot \sin \omega_0 t$$

$$= (V_0 + \Delta V \cos \omega_0 \tau) \cos \omega_0 t$$

$$+ (\Delta V \sin \omega_0 \tau) \cdot \sin \omega_0 t$$

$$= V \cos(\omega_0 t + \phi)$$

$$V = \sqrt{(V_0 + \Delta V \cos \omega_0 \tau)^2 + (\Delta V \sin \omega_0 \tau)^2}$$

$$\varphi = \tan^{-1} \left( \frac{\Delta V \sin \omega_0 \tau}{V_0 + \Delta V \cos \omega_0 \tau} \right)$$

(i) If  $\tau = 0 \Rightarrow$  pulse injected @ peak of cosine

$$\sin \omega_0 \tau = 0, \cos \omega_0 \tau = 1$$

$$\Rightarrow V = (V_0 + \Delta V); \varphi = 0$$

$$v_0(t) = (V_0 + \Delta V) \cos \omega_0 t$$

$\Rightarrow$  amplitude change, no phase change

(ii) If  $\tau = T/4 \Rightarrow$  pulse injected @ zero crossing

$$\sin \omega_0 \tau = 1, \cos \omega_0 \tau = 0$$

$$V = \sqrt{V_0^2 + \Delta V^2} \quad \leftarrow \text{ampl. change}$$

$$\varphi = \tan^{-1} \left( \frac{\Delta V}{V_0} \right) \quad \leftarrow \text{phase change}$$

(iii) When is  $\varphi$  (phase change) maximum?

$$\varphi = \text{max. when } \begin{cases} \sin \omega_0 \tau = 1 \\ \cos \omega_0 \tau = 0 \end{cases} \Rightarrow \tau = T/4$$

i.e. pulse injected @ zero-crossing causes max. phase-shift

## negative-gm oscillator (cross-coupled)

\*  $f_0 = \frac{1}{2\pi\sqrt{LC}}$  ✓

\*  $V_o = \frac{2}{\pi} I_T R_p$   
 $\approx 0.64 I_T R_p$  ✗

\* Startup condition  
 $g_m R_p > 2$  (easier) ✓

## Colpitts Osc.

\*  $f_0 = \frac{1}{2\pi\sqrt{L\left(\frac{C_1 C_2}{C_1 + C_2}\right)}}$  ✓

\*  $V_o = 2 I_T \left(1 - \frac{1}{n}\right) R_p$

$\frac{1}{n} = \frac{C_2}{C_1 + C_2} \sim 0.2$  for best PN  
 $\Rightarrow V_o \approx 1.6 I_T R_p$  ✓

\* Startup condition

$$g_m R_p \left( \frac{1}{n} - \frac{1}{n^2} \right) > 1$$

$$\Rightarrow g_m R_p (0.2 - 0.04) > 1$$

$$\Rightarrow g_m R_p > 6.25$$
 ✗

## -ve gm Osc.

\* Tuning range ✓  
 NMOS - good  
 PMOS - ok

Compl. - ok

\* Good phase noise ✓  
 (but noise inj. @ zero cross)  
 \* differential ✓

## Colpitts Osc.




\* Tuning Range poor ✗  
 → part of cap used to  
 create  $C_1, C_2$  feedback

\* Better PN (noise inj. @  
 voltage peaks) ✓  
 \* diff. form possible ✓


## VCO biasing

\*  $\gamma_f$  noise up conversion  
 → tail CS to output

⇒ looks like a mixer

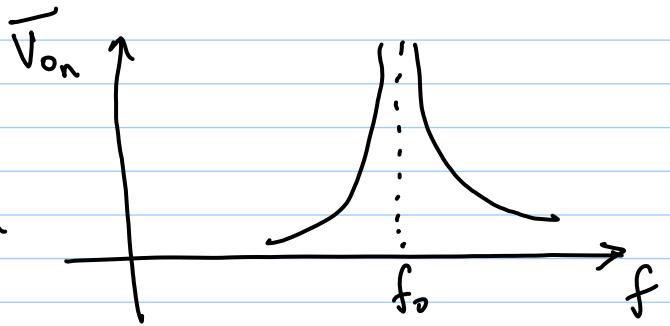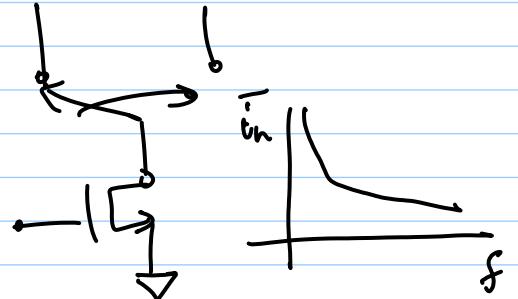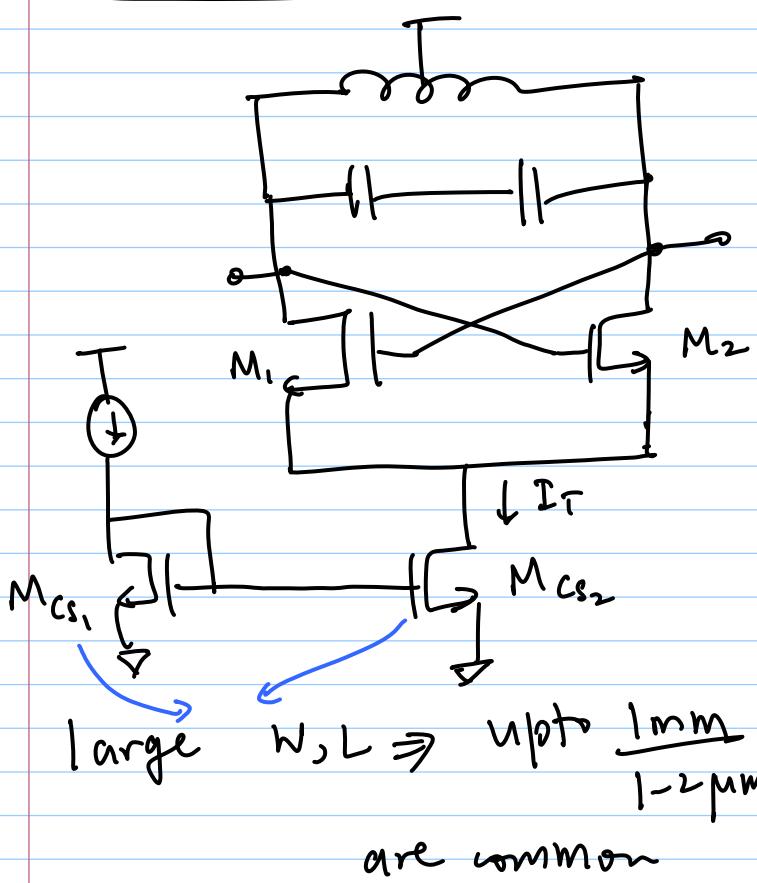

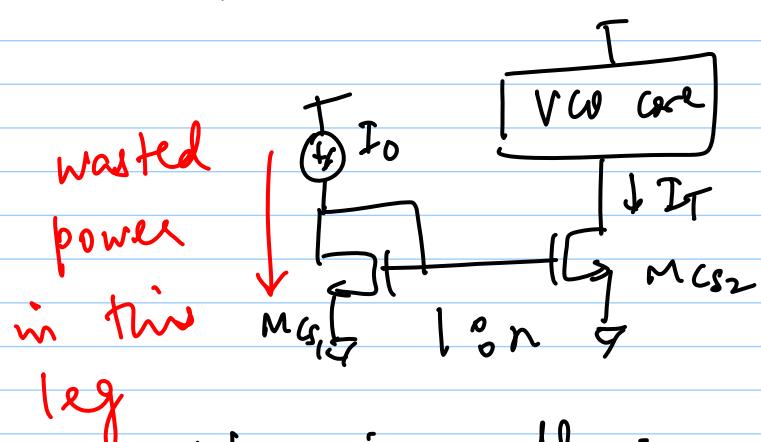- \*  $\gamma_f$  noise from both  $M_{CS1}$  &  $M_{CS2}$
- \* You may be tempted to have a large CM ratio



$$\text{e.g. } I_T = 2 \text{ mA}$$

$$I_0 = 20 \mu\text{A} \left( \frac{1}{n} \right) \frac{\gamma_f}{I_T}$$

$$n = 100$$


$$\frac{W_{CS1}}{W_{CS2}} = \frac{1}{100}$$

- \*  $W_{CS1}$  is small ⇒ more  $\gamma_f$  noise

- \*  $1:n$  CM ratio ⇒  $\gamma_f$  noise gets multiplied

⇒  $\gamma_f$  noise is dominated by  $M_{CS1}$ !

You may be tempted to do this:

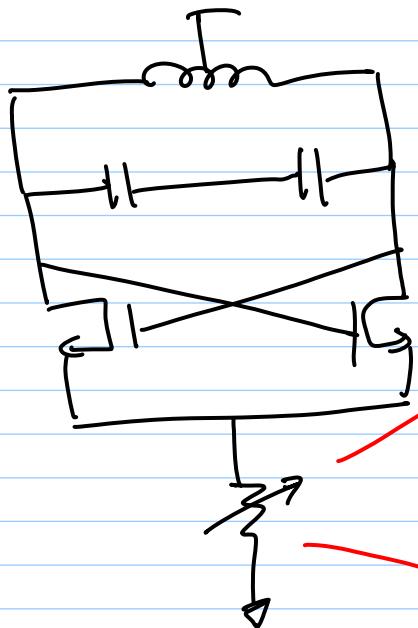


- \* Bias can still be tuned
- \*  $1/f$  noise from CS absent

Problem: Bias current varies a lot over process

Problem: no rejection of common-mode noise from ground node

typical solution:

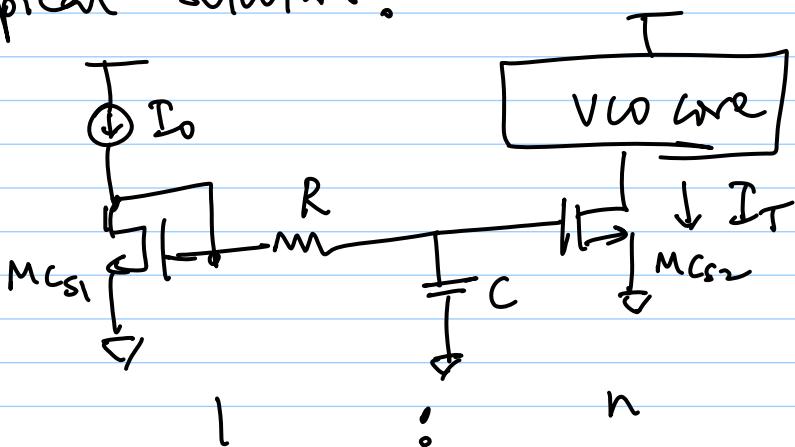

$$\begin{aligned} * & n = 100 \\ \Rightarrow & I_0 = 0.01 I_T \\ (\text{no wastage of } & \text{current}) \end{aligned}$$

\*  $1/f$  noise filtered by RC filter!

$$\left. \begin{array}{l} R = 2 \text{ M}\Omega \\ C = 400 \text{ pF} \end{array} \right\} f_{BW} = \frac{1}{2\pi RC} = 199 \text{ Hz}$$

$\rightarrow$  low enough so  $1/f$  noise does not matter

\* Why not choose

$$R = 20\text{ M}\Omega, C = 40\text{ pF}?$$


$$f_{BW} = 199 \text{ Hz} \text{ again}$$

→ remember  $\frac{kT}{C}$  noise!

→ you will see a noise hump which may end up at an inconvenient freq.


→ R area starts competing with C area

\* Implement R with MOSFET (PMOS!)

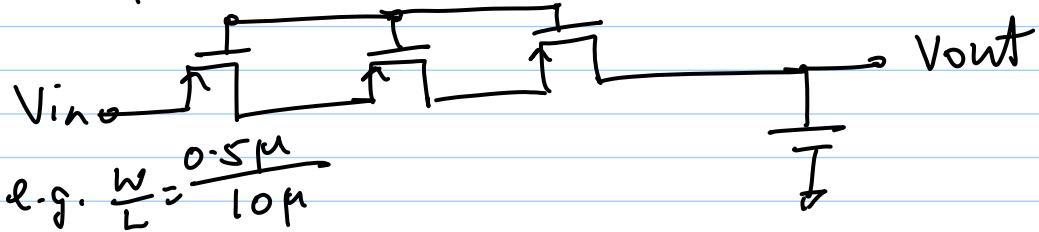



\* leads to start-up problem!
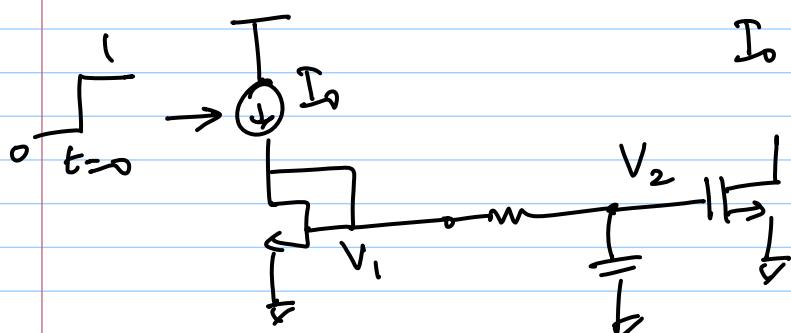
$$\tau = RC = 800\text{ }\mu\text{s}! \leftarrow \text{very large time constant}$$



I0 turned on @  $t=0$

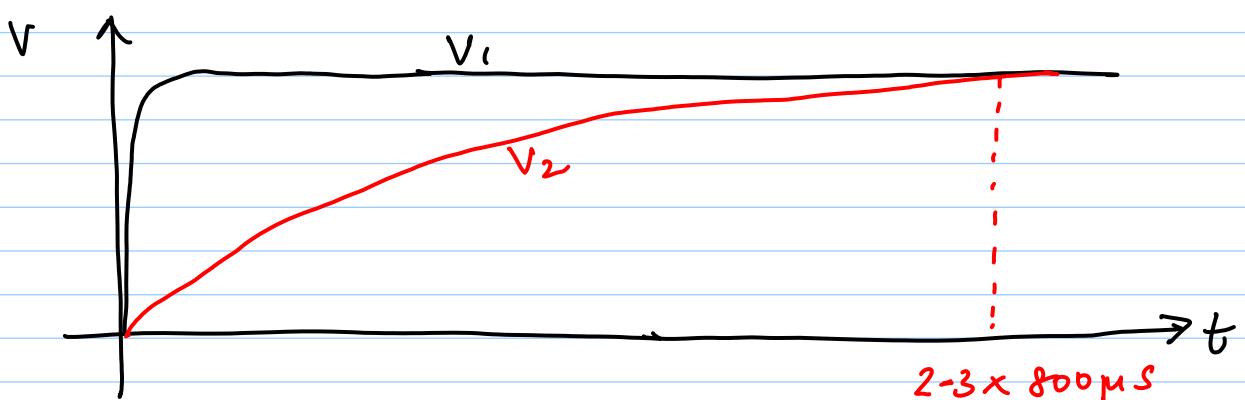

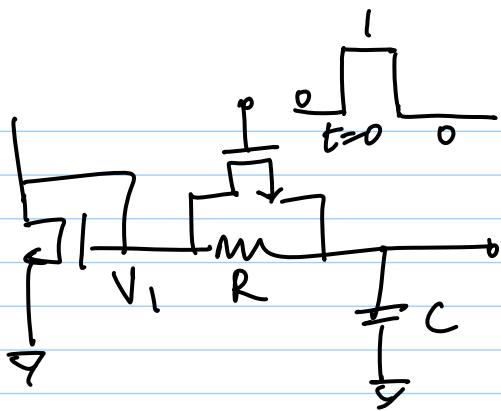


\* bypass  $R$  till  $C$  is charged up (typically in  $10 - 15 \mu s$ )

\* NMOS switch  $R$  matters!

\* No need for PMOS here

$(V_1 \sim 0.5 - 0.6 \text{ V})$


PMOS C-S.

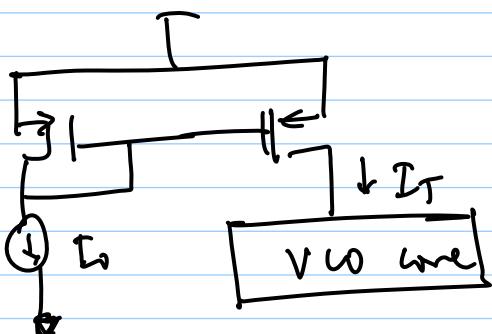



\* PMOS may have lower  $V_f$  noise

\* But 3x as large for same headroom

$V_{CO}$  - regions of operation

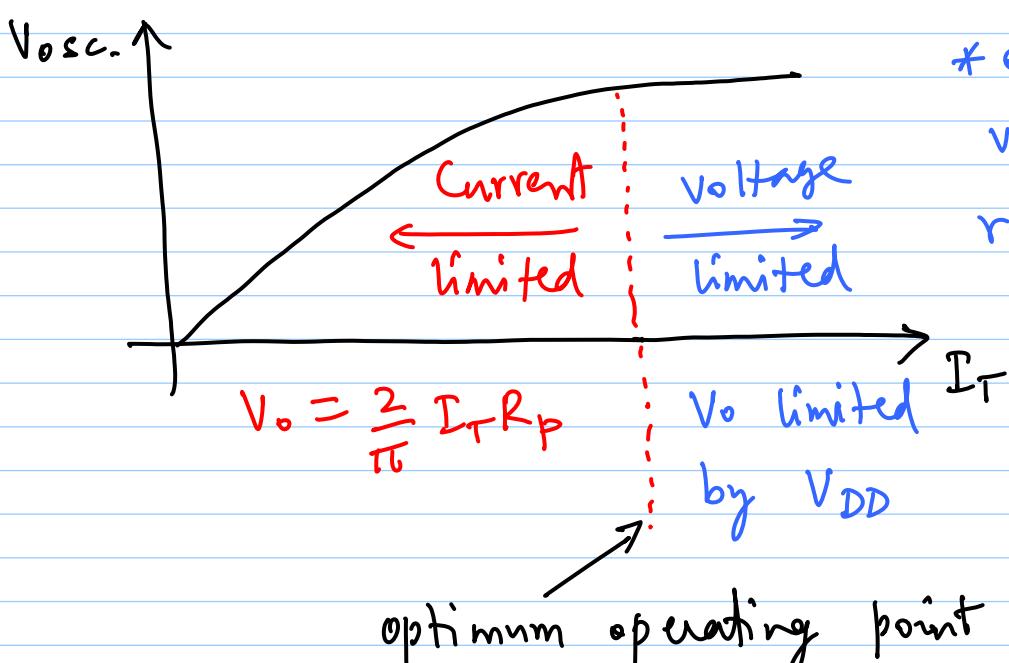

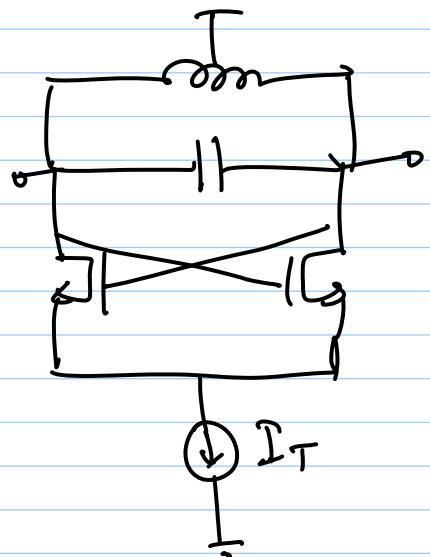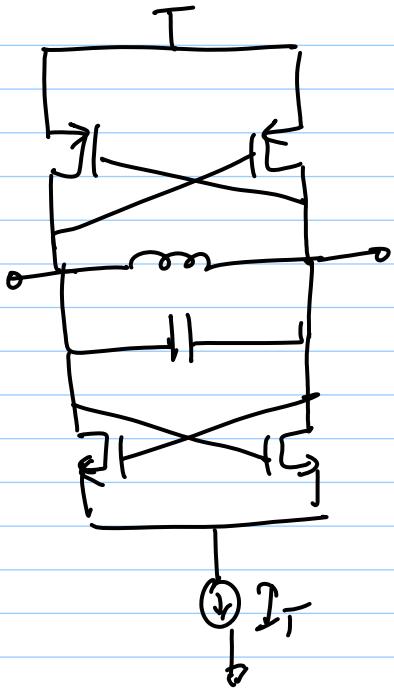\* extra power in voltage limited regime goes into  
a) harmonics  
b) noise




$$\rightarrow V_0 = \frac{4}{\pi} I_T R_p$$

$$\rightarrow V_{0\min} \sim V_{DD}$$

$$\rightarrow V_0 = \frac{2}{\pi} I_T R_p$$

$\rightarrow V_0$  can swing above  $V_{DD}$

$$\rightarrow V_0(\max) \sim 2V_{DD}$$

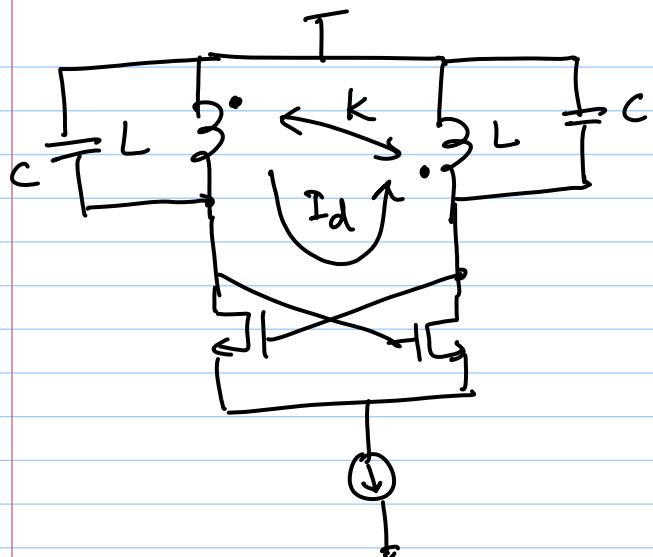

$I_d$  = differential current

$$k = \frac{M}{\sqrt{L_1 L_2}} \quad \left\{ \begin{array}{l} \text{coupling factor} \\ \text{factor} \end{array} \right\}$$

$$= \frac{M}{L} \text{ here}$$

we want max  $k$  ( $0 \leq k \leq 1$ )





$$L_{eff.} = (L + M) = L(1+k)$$

$$Q_{eff.} = \frac{\omega_0 L_{eff.}}{r} = \frac{\omega_0 L}{r} (1+k) = Q(1+k)$$


series  
res. of  
inductor

If  $Q = 10$ , you can almost double it to 20!

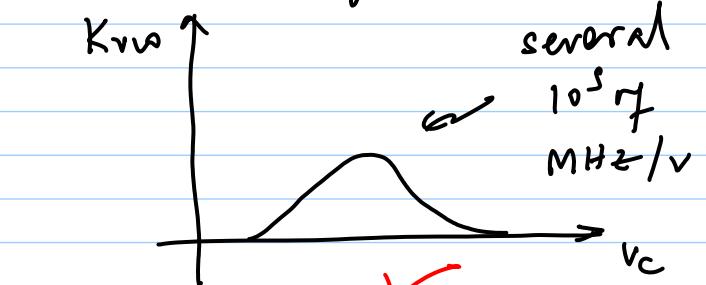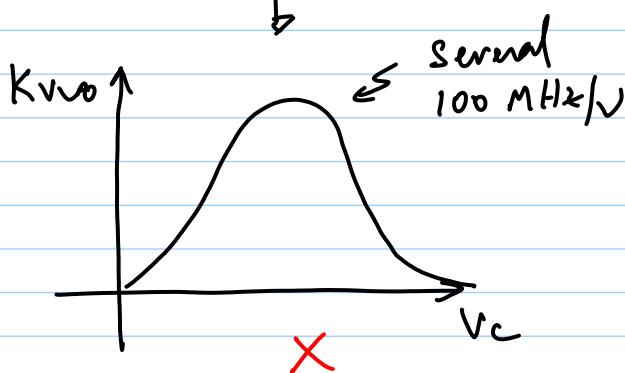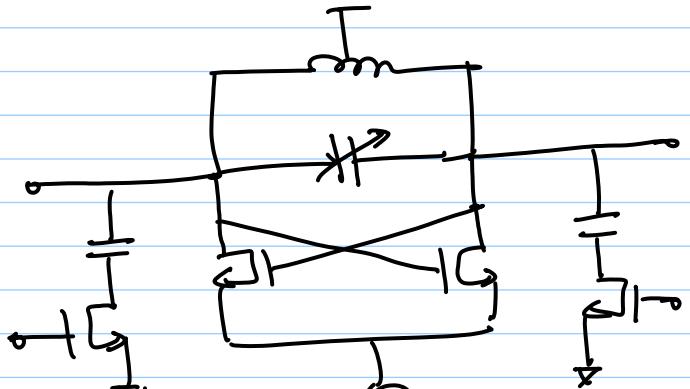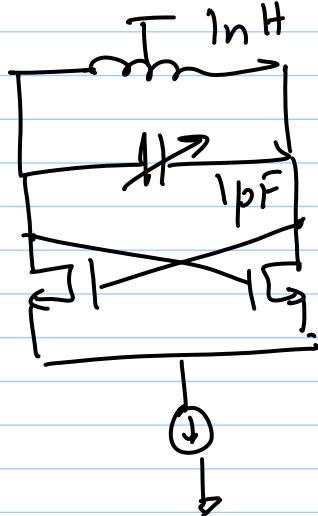Tuning → continuous (varactor) → discrete (cap. bank)




\* low  $K_{vo}$  is good

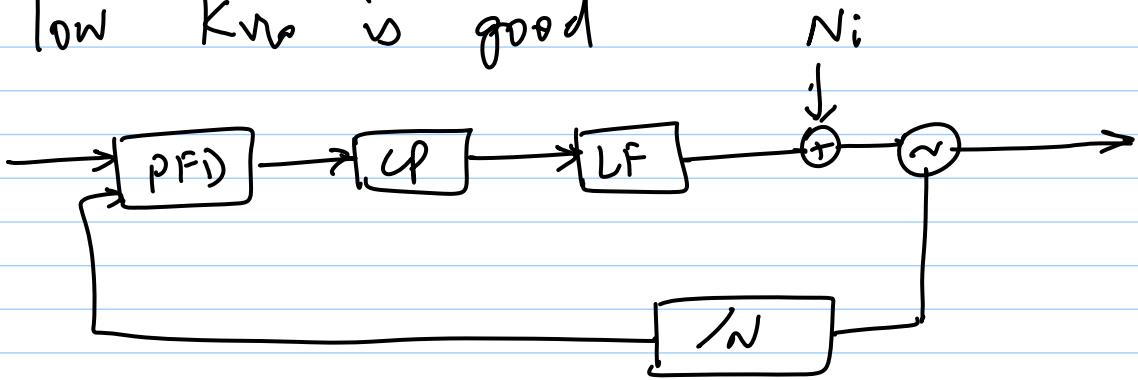



→ noise or spurs coupling @ VCO input  
do not have a large gain to output

\* Effects of noise coupling to A, B

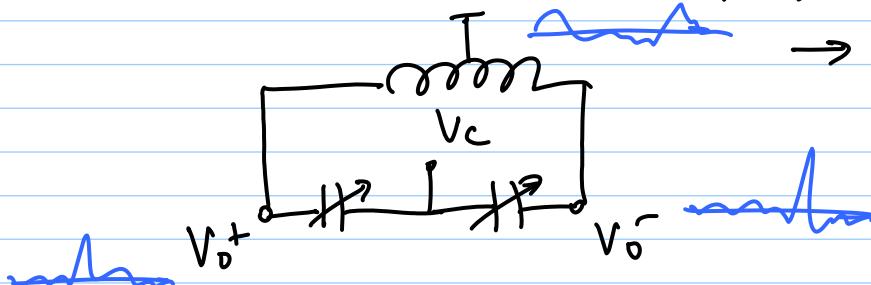

→ Varactor performs AM - PM conversion

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

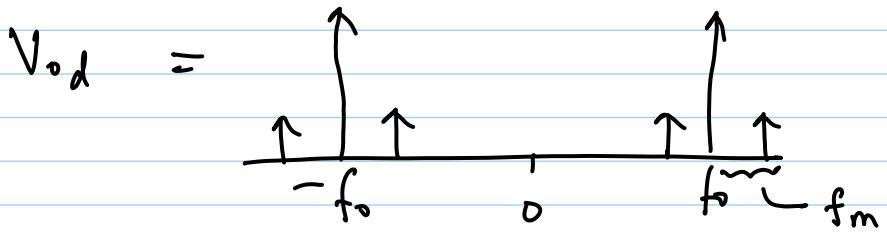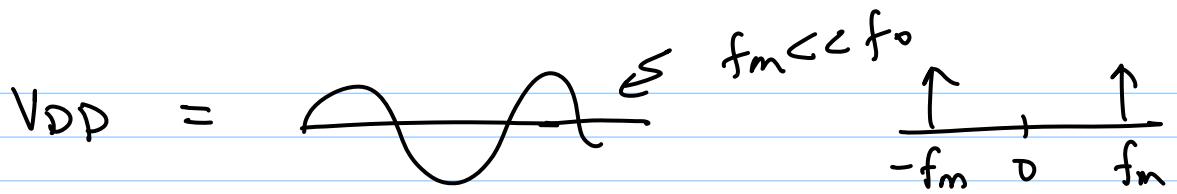

\* Need overlap in discrete tuning (PVT variations)

