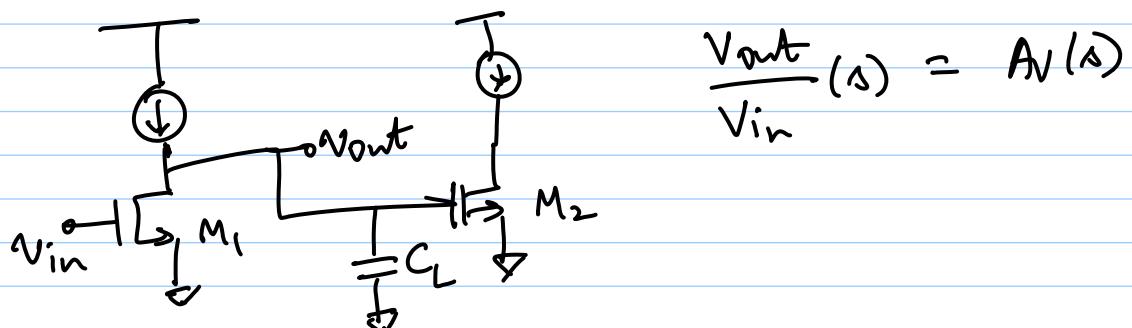


## Lecture 34 : Wideband Amplifiers - I

- Applications :
- PCB chip-to-chip links
  - Optical fibre communications
  - wideband wireline comm. (e.g. TV)
  - measurement instrument front-ends  
(e.g. Oscilloscopes)
  - Wireless : UWB radio & multiband radios

ABW product

- \* C.S. amplifier driving identical stage




$$A_V(\omega) = \frac{g_m r_{ds}}{1 + s C_L r_{ds}}$$


$$\text{DC gain } A_0 = g_m r_{ds}$$

$$\omega_{-3dB} = \omega_0 = \frac{1}{C_L r_{ds}}$$

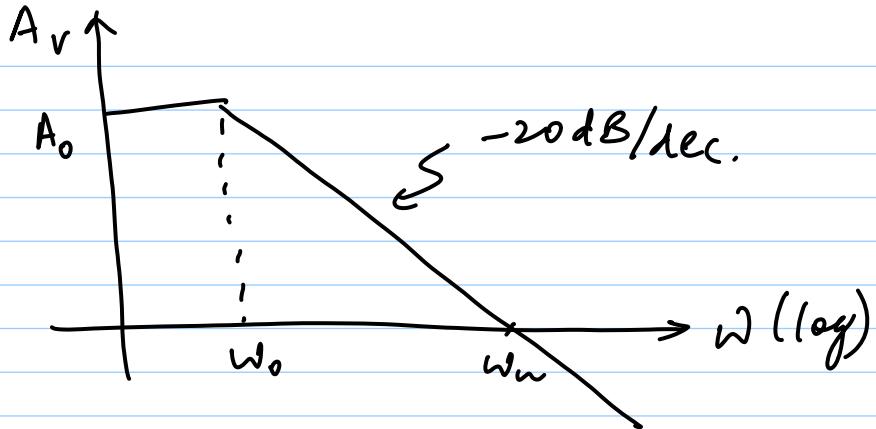
$$\text{Unity gain freq. } \omega_u = A_0 \omega_0 = \frac{g_m}{C_L}$$



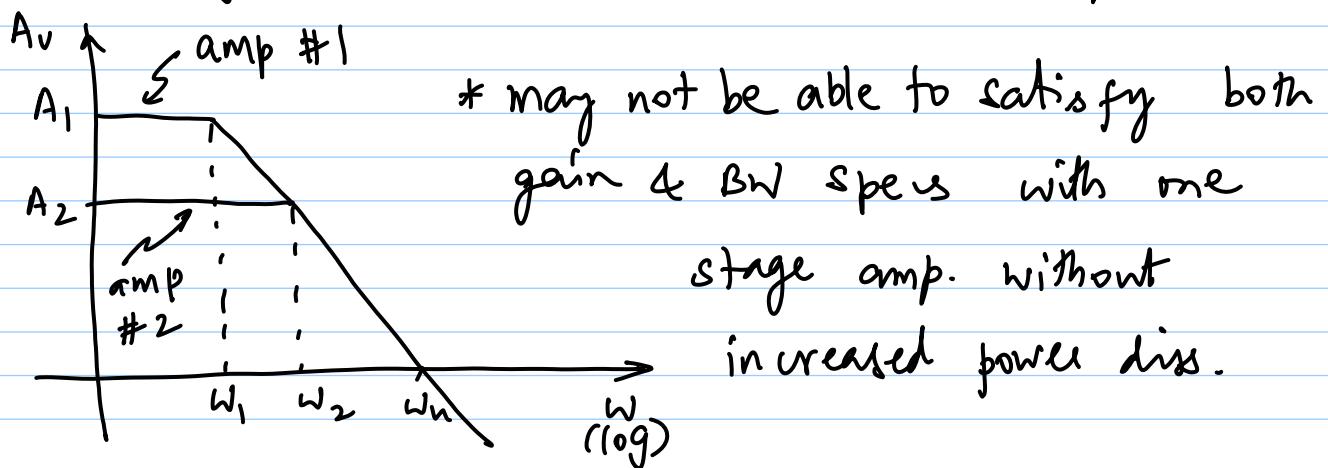$\omega_n = f(\text{device size, bias point, load cap})$



\* increasing power cannot take us far:

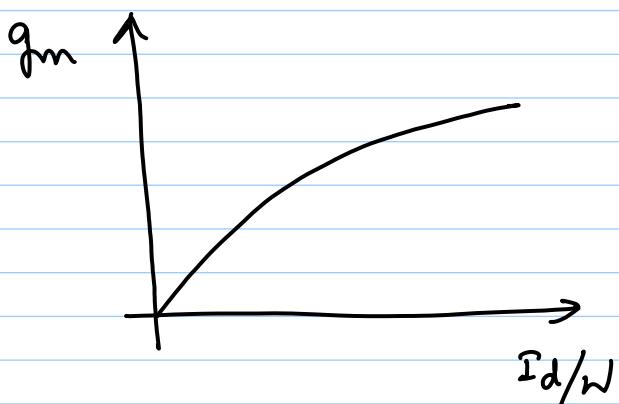


\* If  $\omega \uparrow \Rightarrow g_m \uparrow$   
but so does  $C_L$   
 $\Rightarrow \frac{g_m}{C_L} = \text{constant}$

\* Cascade a number of single-pole amps can accomplish this, but  $\Rightarrow$  more delay

$\Rightarrow$  Gain - BW - Delay tradeoff is fundamental

## BW Enhancement Techniques

### i) Shunt-Peaking:

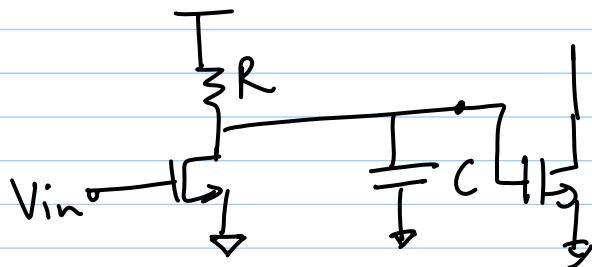

gain ↑

$g_{mL}$

$$\omega_0 = \frac{1}{RC}$$

\*  $L$  introduces a zero

( $Z \uparrow$  with freq.)

$\Rightarrow$  broader freq. range  
than  $\omega_0$  is possible

\* In the time domain: assume an input voltage step

$\rightarrow$  inductor delays current flow in branch containing  $R, L$

$\rightarrow$  more current available for charging  $C$

$\Rightarrow$  rise time is reduced

i.e. BW is increased

$$Z(s) = (\Delta L + R) \parallel \frac{1}{sC}$$

$$= \frac{R \left( s \cdot \frac{L}{R} + 1 \right)}{\Delta^2 LC + \Delta RC + 1}$$

$$\left. \begin{cases} A_r(\Delta) = g_m |Z(j\omega)| \\ \Rightarrow \text{study } |Z(j\omega)| \end{cases} \right\}$$

$\Rightarrow$  2 poles (complex conjugate is possible)

$$L \text{ zero } \omega_z = -R/L$$

Define :

(i) original 3dB BW  $\omega_0 = \frac{1}{RC}$

(ii) time constant corresponding  
to zero  $\tau = L/R$

(iii)  $m = \frac{\text{original time constant}}{\text{new time constant}} = \frac{RC}{L/R}$

$$= \frac{1}{\omega_0 \tau}$$

$$\Rightarrow \frac{Z(s)}{R} = \frac{s\tau + 1}{s^2\tau^2m + s\tau m + 1}$$

$$\frac{|Z(j\omega)|}{R} = \sqrt{\frac{(s\tau)^2 + 1}{(1 - s\tau^2m)^2 + (s\tau m)^2}}$$

@  $\omega = \omega_{3dB}$ ,  $\frac{|Z(j\omega)|}{R} = \frac{1}{\sqrt{2}}$

$$\Rightarrow \frac{1 + \omega^2\tau^2}{(1 - \omega^2\tau^2m)^2 + (\omega^2\tau^2m)^2} = \frac{1}{2}$$

$$\text{Let } x = \omega^2\tau^2$$

$$\Rightarrow \frac{1 + x}{(1 - mx)^2 + m^2x} = \frac{1}{2}$$

$$\Rightarrow 2 + 2x = m^2x^2 - 2mx + 1 + m^2x$$

$$m^2x^2 + (m^2 - 2m - 2)x - 1 = 0$$

$$\Rightarrow x = \frac{(2m+2-m^2) + \sqrt{(2m+2-m^2)^2 + 4m^2}}{2m^2}$$

only +ve root because  $x = \omega^2 \tau^2 > 0$

$$x = \frac{1}{m^2} \left\{ \left( m+1 - \frac{m^2}{2} \right) + \sqrt{\left( m+1 - \frac{m^2}{2} \right)^2 + m^2} \right\}$$

$$\begin{aligned} x &= (\omega_{3dB} \cdot \tau)^2 = \left( \frac{\omega_{3dB}}{\omega_0} \right)^2 \cdot (\omega_0 \tau)^2 \\ &= \left( \frac{\omega_{3dB}}{\omega_0} \right)^2 \cdot \frac{1}{m^2} \end{aligned}$$

$$\Rightarrow \frac{\omega_{3dB}}{\omega_0} = \sqrt{\left( -\frac{m^2}{2} + m + 1 \right) + \sqrt{\left( -\frac{m^2}{2} + m + 1 \right)^2 + m^2}}$$

\* You can plot  $\frac{\omega_{3dB}}{\omega_0}$  as a function of  $m$




\* Also plot  $\frac{Z(j\omega)}{R}$  as a function of  $m$

i) For max BW extension,

$$m = \sqrt{2} = 1.41$$

$$\begin{aligned} \Rightarrow \frac{\omega_{3dB}}{\omega_0} &= 1.85 \quad \text{at no increase in power!} \\ &= \text{BW extension factor (BWEF)} \end{aligned}$$

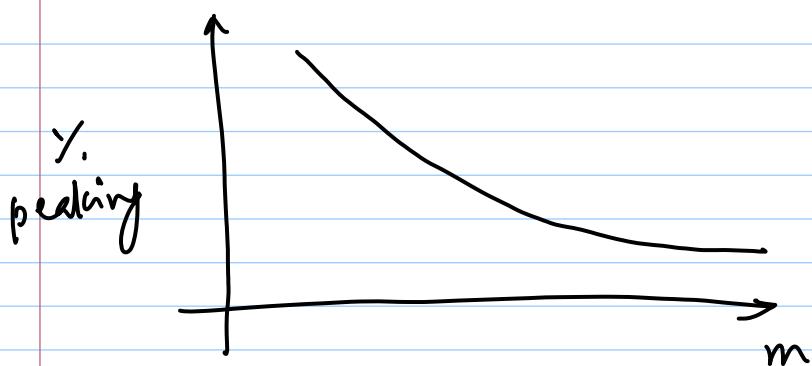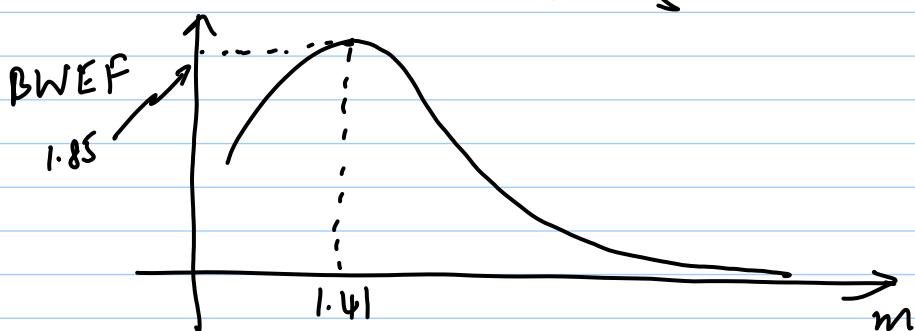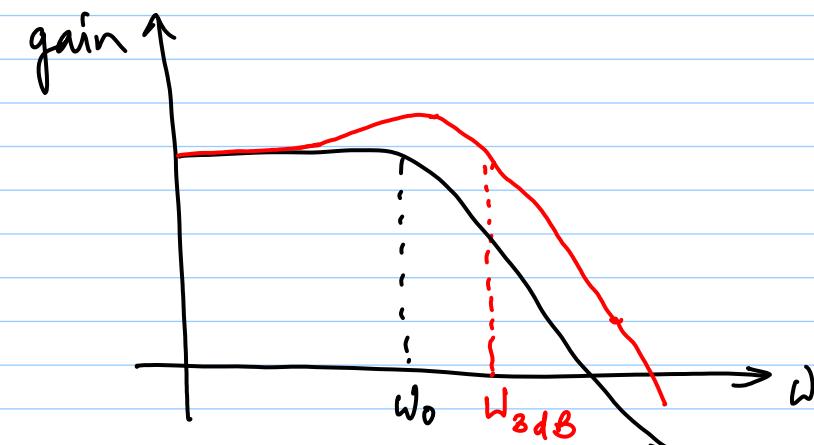\* Problem : almost 20% peaking in freq. response



\* set  $|z| = R$  @  $\omega_0$  to moderate peaking  
 $\Rightarrow$  solving for  $m$  gives

$$m = 2$$

BWEF

$$\omega_{3dB} = \omega_0 \sqrt{1 + \sqrt{5}} \approx 1.8\omega_0$$

$\rightarrow$  BW extension almost the same

$\rightarrow$  peaking  $\sim 3\%$  {often-used optimum}

2) Maximally flat response (Butterworth)

→ no peaking

\*  $|Z(j\omega)|^2 \Rightarrow$  maximize # of derivatives where value is zero @ DC

$$\Rightarrow m = 1 + \sqrt{2} = 2.41$$

$$\Rightarrow \omega_{3\text{dB}} = 1.72 \omega_0$$

↖ BWEF

3) Even with maximally flat response, phase distortion may occur. (ISI)  
⇒ optimise for group-delay response  
e.g. optical commun. applications, UWB

\* ideal wide band amp ⇒ phase ↑ linearly with freq. (i.e. same delay for all freq.)  $\Rightarrow \frac{d\phi}{d\omega} = \text{constant over freq.}$

\* Non-linear phase response ⇒ unequal delay of freq. components  
 $\Rightarrow$  group-delay distortion

\* Maximally flat group delay:

$$T_D(\omega) = - \frac{d\phi}{d\omega}$$

⇒ maximise # of derivatives of  $T_D(\omega)$  where value is zero at DC.

after lots of algebra:

$$\Rightarrow m \approx 3.1$$

$$\Rightarrow \omega_1 \approx 1.1 \omega_0$$

BWEF

\* conditions for maximally flat gain and delay do not coincide, so tradeoff is involved.

### Design

Given: DC gain, load cap C,  $\omega_{3dB}$ , constraint on max BW/mag. response  
phase response

$$\omega_0 = \frac{\omega_{3dB}}{BW \times F} = \frac{1}{RC} \Rightarrow \textcircled{R}$$

$$Av_{AC} = g_m R \Rightarrow \textcircled{g_m}$$

$$m = \frac{RC}{L/R} \Rightarrow L = \frac{R^2 C}{m} \Rightarrow \textcircled{L}$$

\* R is in series with L


$\Rightarrow$  low-Q L is ok, absorb series  $r_s$  into R

\* Emphasis more on area  $\Rightarrow$  max L in minimum area

$\rightarrow$  series stacked structures are popular

condition	$m = R^2 C / L$	$BW \times F$	Normalised peak freq. response
max BW	1.41	1.85	1.19
$ z  = R @ \omega_0$	2	1.8	1.03
minimally flat	2.41	1.72	1
group delay	3.01	1.6	1
No shunt peaking	$\infty$	1	1


### Series Peaking

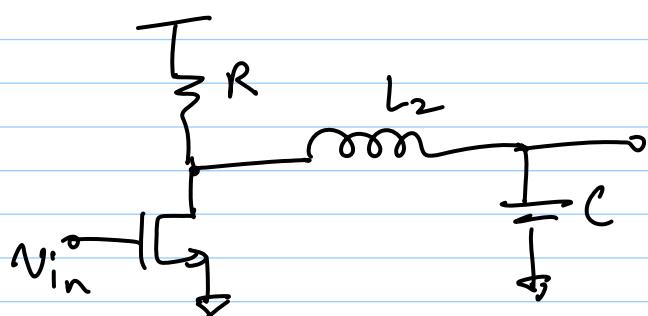

again  $L_2 = \frac{R^2 C}{m}$

- \* max BW  $\Rightarrow m = 2 ; BW \times F = \sqrt{2}$
- minimally flat amplitude also
- \* max flat group delay  $\Rightarrow m = 3 ; BW \times F = 1.36$
- \* Shunt peaking  $BW \times F >$  series peaking  $BW \times F$
- \* Why not use both?


## Shunt-series peaking

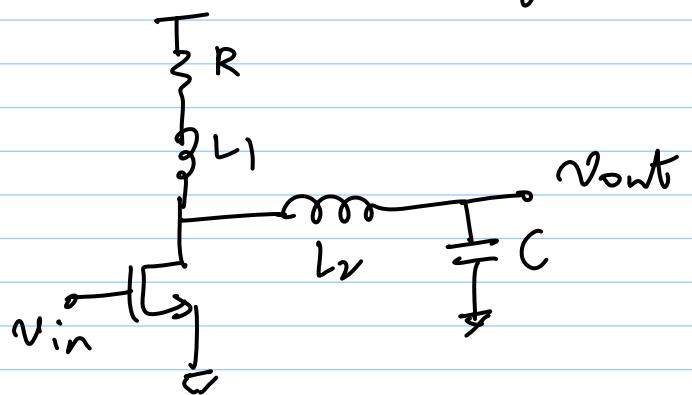


+ BW - delay  
tradeoff

\*  $C_{db}$  &  $C_L$  are charged serially in time

## Shunt-double series peaking

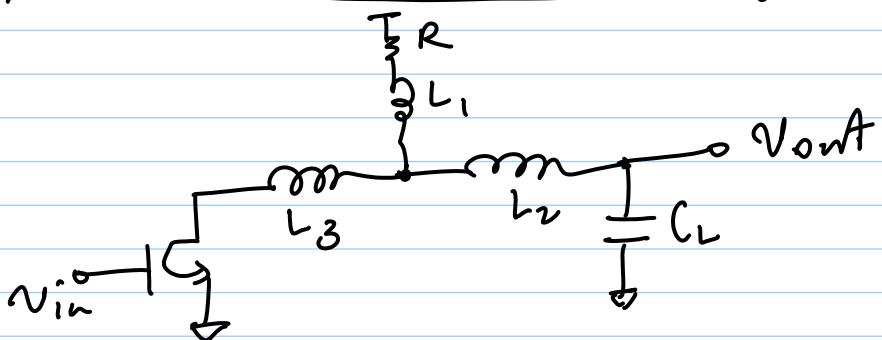

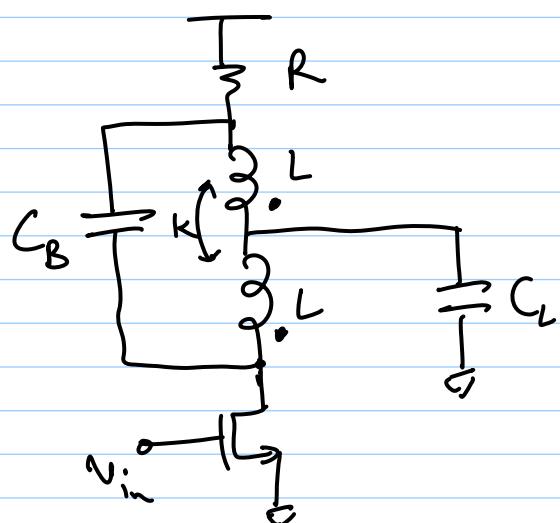- \*  $L_1, L_2, L_3$  can be replaced by a single Xfmr to save area
- \* Add bridging cap to create parallel resonance (this helps with BW too)



Bridged  
T-Coil

\* You can show that

$$L = \frac{R^2 C}{2(1+k)}$$

$$C_B = \frac{C}{4} \cdot \frac{(1-k)}{(1+k)}$$

\*  $k = 1/3 \Rightarrow$  Butterworth mag. response

$k = 1/2 \Rightarrow$  max. flat group delay

\* Used in oscilloscopes for a long time

$$\omega_{3dB} (\text{max}) = 2\sqrt{2} \omega_0$$

$$\approx 2.83 \omega_0$$

↑  
BWF