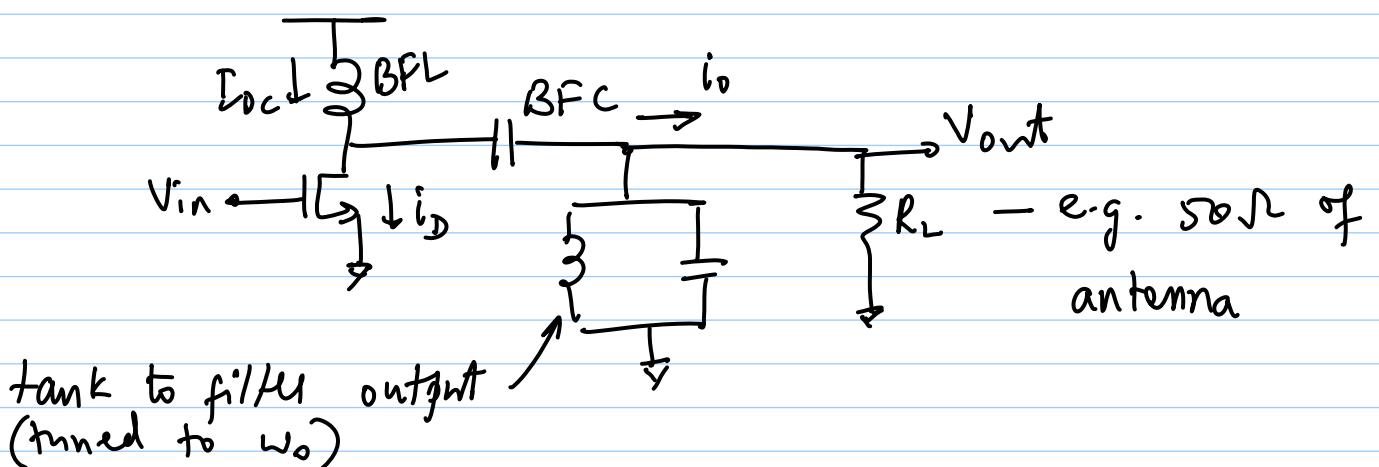


Lecture 36 : Power Amplifiers

- * Narrowband vs. Broadband
- * Linear vs. Constant Envelope operations
 - AM etc.
 - ↓
 - PM, FM etc.
- * Tradeoffs
 - Power gain
 - Linearity
 - Output Power
 - Efficiency (drain eff. & power added eff.)

Classical PAs (linear)

- class A, AB, B, C
- classified based on bias conditions



* BFC prevents DC power diss. in R_L



* BPL provides approximated constant current

* tank ckt with high Q provides linear output

I Class A

* 360° conduction angle

* $V_{in\ min.} = V_T$

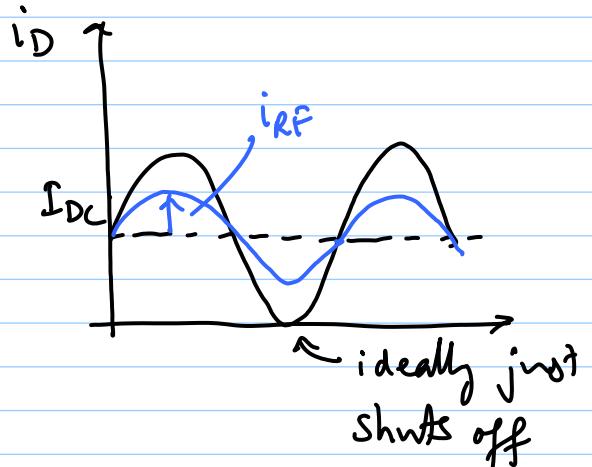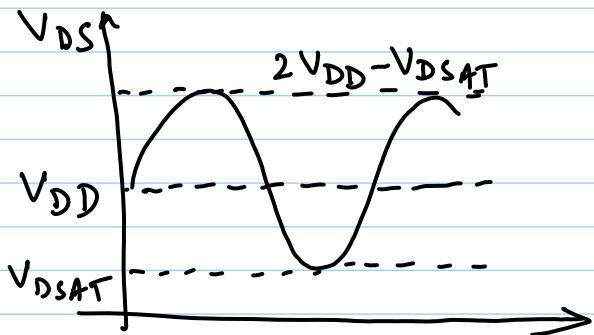

- * high linearity
- * poor efficiency


$$i_D = I_{DC} + i_{RF} \sin \omega_0 t$$

$$i_o = I_{DC} - i_D = -i_{RF} \sin \omega_0 t$$

$$V_{out} = i_o \cdot R_L = -i_{RF} R_L \sin \omega_0 t$$

$$V_{DS} = V_{DD} + i_o \cdot R_L = V_{DD} - i_{RF} \cdot R_L \sin \omega_0 t$$
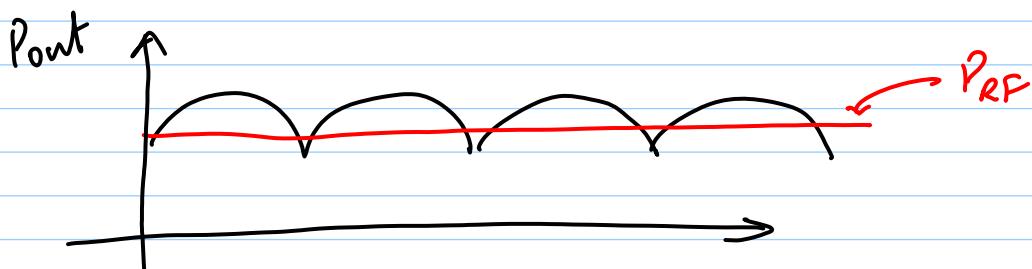
$$P_{out} = i_{out} \cdot V_{out} = i_{RF}^2 R_L \sin^2 \omega_0 t$$



$$P_{RF} = (i_{RF, rms})^2 \cdot R_L = \frac{i_{RF}^2 R_L}{2}$$

$$P_{DC} = DC \text{ power from } V_{DD}$$

$$= V_{DD} \cdot I_{DC} = V_{DD} \cdot i_{RF} \text{ (assume } M_1 \text{ just turns off at low current)}$$

η = drain current efficiency

$$\eta = \frac{P_{out}}{P_{DC}} = \frac{\frac{1}{2} i_{RF}^2 R_L}{i_{RF} \cdot V_{DD}} = \frac{\frac{1}{2} i_{RF} \cdot R_L}{V_{DD}}$$

max. value of $i_{RF} \cdot R_L = V_{DD}$ (max. swing neglecting V_{DSAT})

$$\Rightarrow \eta_{\max} = \frac{1}{2} \text{ or } 50\%$$


practical $\eta \sim 30 - 35\%$

Normalized Power output capability $\equiv P_N$

$$P_N = \frac{P_{rf}}{V_{DSpk} \cdot i_{Dpk}} = \frac{V_{DD}^2 / 2 R_L}{(2V_{DD}) \cdot \left(\frac{2V_{DD}}{R_L}\right)}$$

$= \frac{1}{8}$ // High device stress

II Class B PA

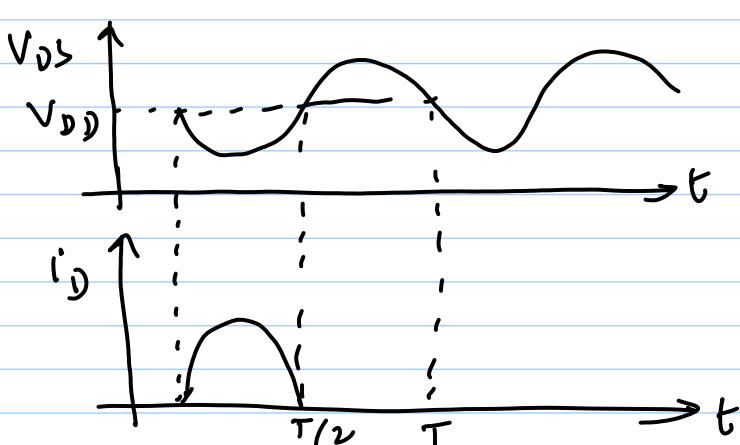

* 180° conduction angle

* Current flows only

when V_{DS} is small


\rightarrow low $P_{diss.}$

$$i_D = i_{RF} \sin \omega_0 t \text{ for } 0 - T/2$$

* Tank filters out harmonics of i_D , leaving a sinusoidal voltage across R_L

* fundamental current:
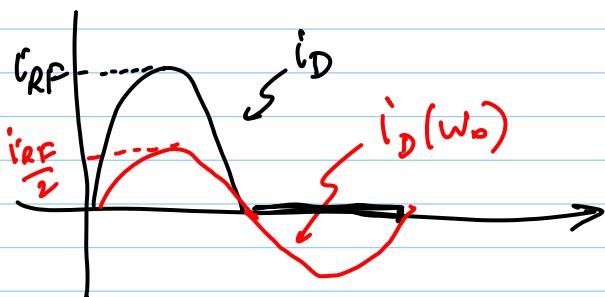
$$\begin{aligned} i_D(\omega_0) &= \frac{2}{T} \int_0^{T/2} i_{RF} \sin \omega_0 t \cdot \sin \omega_0 t dt \\ &= \frac{i_{RF}}{2} \end{aligned}$$



$$V_o = \frac{i_{RF}}{2} R_L \sin \omega_0 t$$

$$V_o (\text{max}) \approx V_{DD} \Rightarrow i_{RF} (\text{max.}) = \frac{2V_{DD}}{R_L}$$

$$P_o (\text{max.}) = \frac{V_{DD}^2}{2R_L}$$

$$i_{DC} = \frac{1}{T} \int_0^{T/2} \frac{2V_{DD}}{R_L} \sin \omega_0 t dt = \frac{2V_{DD}}{\pi R_L}$$


$$\begin{aligned} \therefore P_{DC} &= i_{DC} \cdot V_{DD} \\ &= \frac{2V_{DD}^2}{\pi R_L} \end{aligned}$$

$$\eta = \frac{P_{o,AT}}{P_{DC}} = \frac{\frac{V_{DD}^2}{2R_L}}{\frac{2V_{DD}^2}{\pi R_L}} = \frac{\frac{\pi}{4}}{\frac{2}{\pi}} = 78.5\%$$

$$P_N = \frac{P_{RF}}{V_{DS(\text{max.})} i_D(\text{max.})}$$

$$= \frac{V_{DD}^2 / 2R_L}{2V_{DD} \cdot \frac{2V_{DD}}{R_L}} = \frac{1}{8} \quad \text{High stress}$$

With biasing:

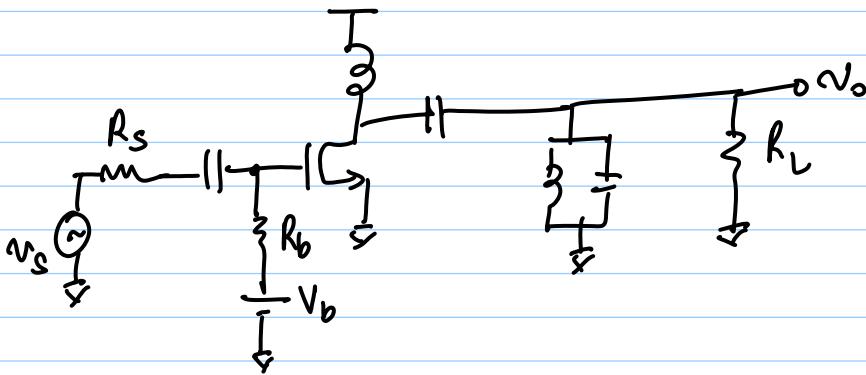

$$V_o = V_{RF} \sin \omega t$$


Class-A

$$V_b > (V_T + V_{RF})$$

Class-B

$$V_b = V_T$$

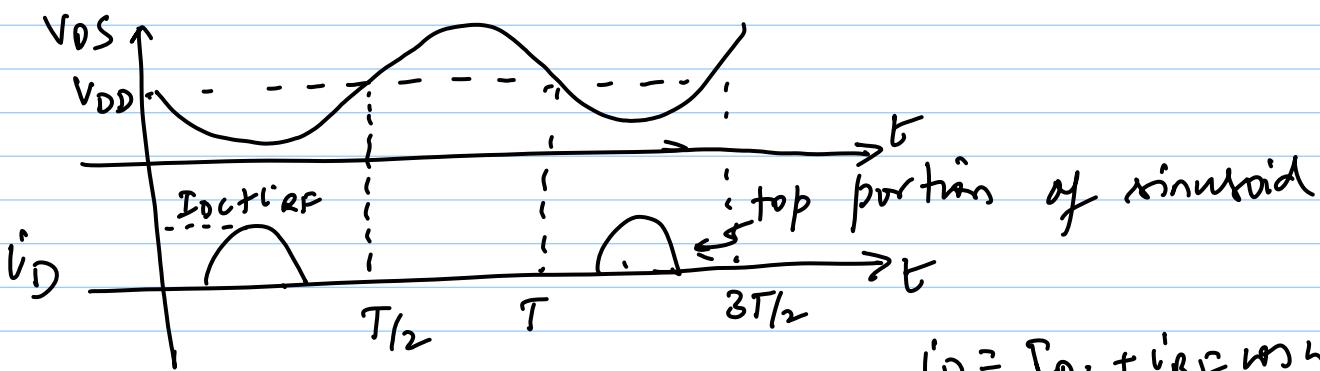III class-C PA $\Rightarrow V_b < V_T$
conducts for $< 180^\circ$



$$i_D = I_{DC} + i_{RF} \sin \omega t$$

$2\Phi \equiv \text{conduction angle}$

$$\Phi = \cos^{-1} \left(-\frac{I_{DC}}{i_{RF}} \right)$$

"Bias unbalance"

$$I_{DC} = -i_{RF} \cos \Phi \quad \begin{cases} \text{offset current } i \\ \text{negative} \end{cases}$$

average current

$$\bar{i}_D = \frac{1}{2\pi} \int_{-\Phi}^{\Phi} (I_{DC} + i_{RF} \cos \varphi) d\varphi$$

$$= \frac{1}{2\pi} \left[2\Phi I_{DC} + \frac{1}{2\pi} (i_{RF} \sin \varphi) \right]_{-\Phi}^{\Phi}$$

$$= \frac{i_{RF}}{\pi} \left[\sin \Phi - \Phi \cos \Phi \right]$$

fundamental:

$$i_{fund} = \frac{2}{T} \int_0^T i_D \cos \omega_0 t dt$$

$$= \frac{1}{2\pi} \left(4 I_{DC} \sin \Phi + 2 i_{RF} \Phi + i_{RF} \sin 2\Phi \right)$$

$$= \frac{i_{RF}}{2\pi} \left(2\Phi - \sin 2\Phi \right)$$

max. swing $\leq V_{DD}$

$$\Rightarrow V_{DD} = i_{RF} \frac{R_L}{2\pi} \left(2\Phi - \sin 2\Phi \right)$$

$$\Rightarrow i_{RF_{max.}} = \frac{2\pi V_{DD}}{R_L [2\Phi - \sin 2\Phi]}$$

$$\Rightarrow i_{D_{pk.}} = i_{RF_{max.}} + I_{DC}$$

$$\Rightarrow \frac{2\pi V_{DD}}{R_L (2\Phi - \sin 2\Phi)} \left[1 + \frac{\sin \Phi - \Phi \cos \Phi}{\pi} \right]$$

$$\Rightarrow \eta_{max.} = \frac{2\Phi - \sin 2\Phi}{4 (\sin \Phi - \Phi \cos \Phi)}$$

as $\Phi \rightarrow 0$, $\eta \rightarrow 100\%$

but gain & Pout $\rightarrow 0$

* We can obtain high efficiency at the expense of linearity, gain & Pout






Switching PA

Basic Principle: Use MOSFET as a switch rather than as a controlled current source in the case of linear PAs

ideal switch ON $\Rightarrow V=0$, $I > 0$ Power ≈ 0
OFF $\Rightarrow V > 0$, $I = 0$ Power $= 0$

no loss in switch $\Rightarrow 100\%$ efficiency

D Class-D PA

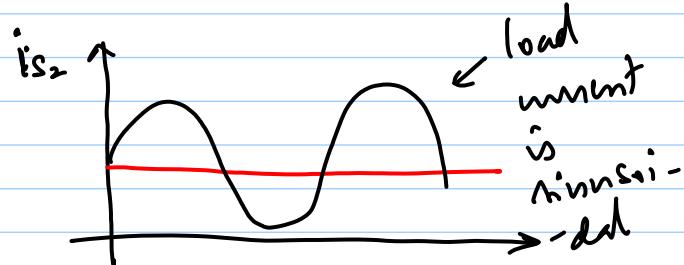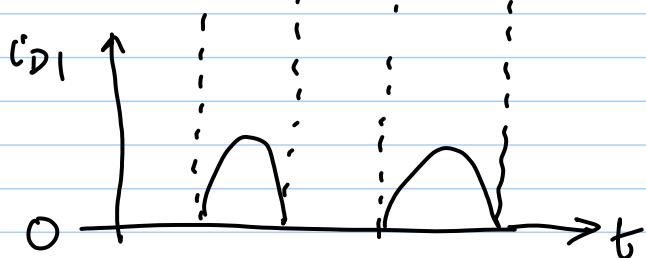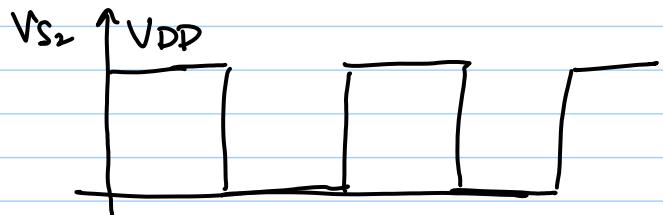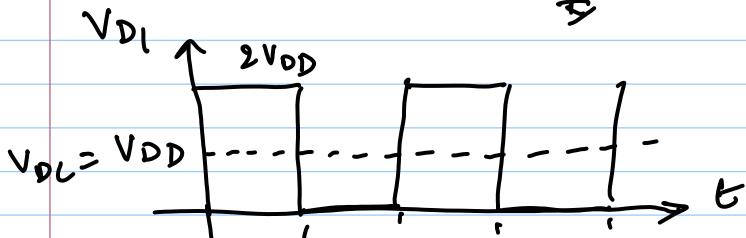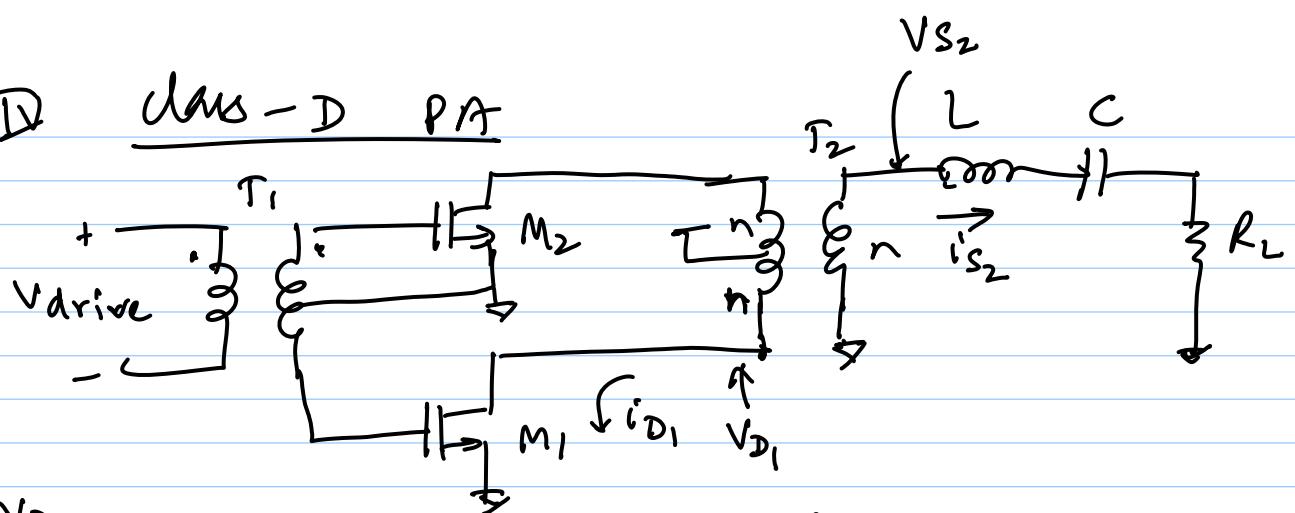

You can show that:

normalised power handling capability




$$P_N = \frac{P_{\text{out}}}{V_{DS\text{pk}} \cdot i_{D\text{pk}}} = \frac{1}{\pi b} \quad \leftarrow \text{much lower stress than linear PAs}$$

ideal $\eta = 100\%$

Practical: switches must be very fast relative to ω_0 , otherwise $\eta < 100\%$.

IV Class-E PAs

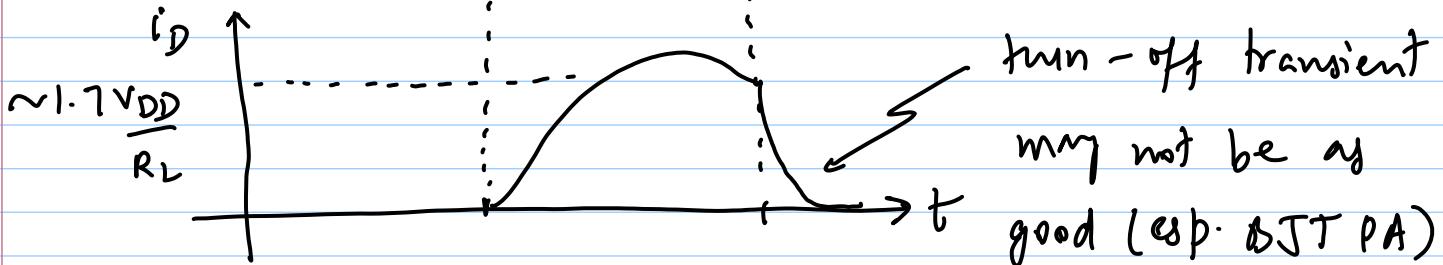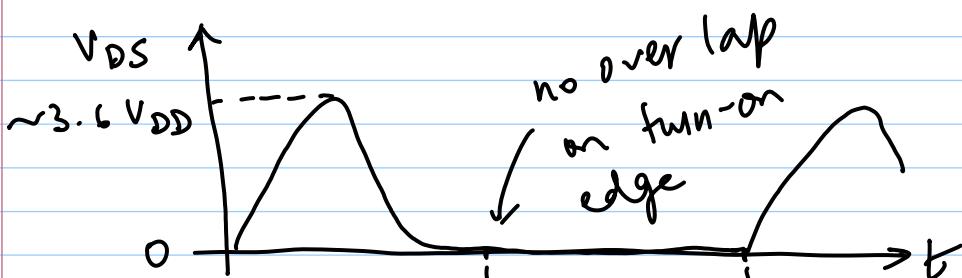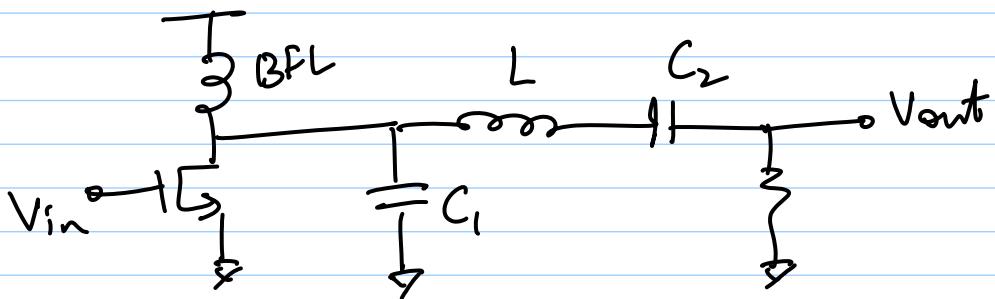key ideas & switch voltage \approx before current flows
& use higher order filter to shape the pulses



Ref: Sorkal & Sorkal, JSSC June 1975
Design Equations

$$L = \frac{Q R_L}{\omega}$$

$$C_1 = \frac{1}{\omega R_L \left(\frac{\pi^2}{4} + 1 \right) \left(\frac{\pi^2}{2} \right)} \approx \frac{1}{5.447 \omega R_L}$$


$$C_2 \approx C_1 \left(\frac{5.447}{Q} \right) \left(1 + \frac{1.42}{Q - 2.08} \right)$$

$$\text{Power (max.)} = \frac{2}{1 + \pi^2/4} \cdot \frac{V_{DD}^2}{R_L} \approx 0.577 \frac{V_{DD}^2}{R_L}$$


$$P_N = \frac{P_0}{V_{DSpk} \cdot I_{Dpk}} \approx 0.098 \leftarrow \text{high stress}$$

note that $V_{DSpk} = 3.6 V_{DD}$
 $I_{Dpk} = 1.7 \frac{V_{DD}}{R_L}$) very high values

VI Class-F PA's

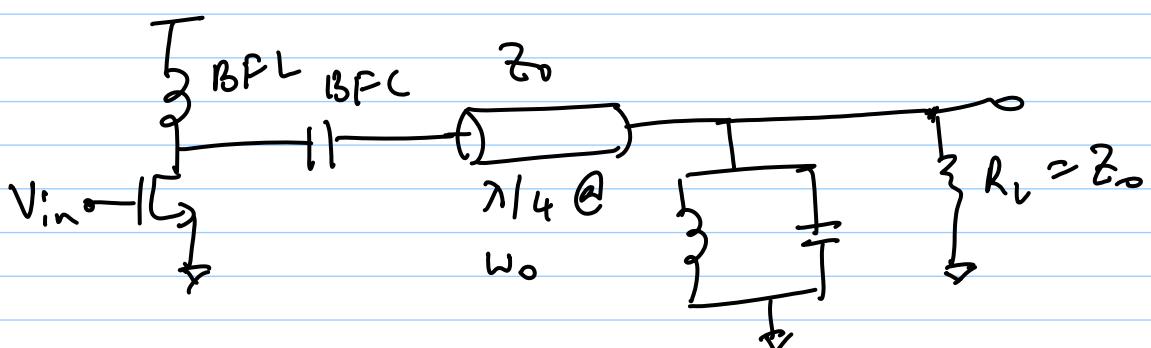

$\lambda/4 \times \text{freq}$

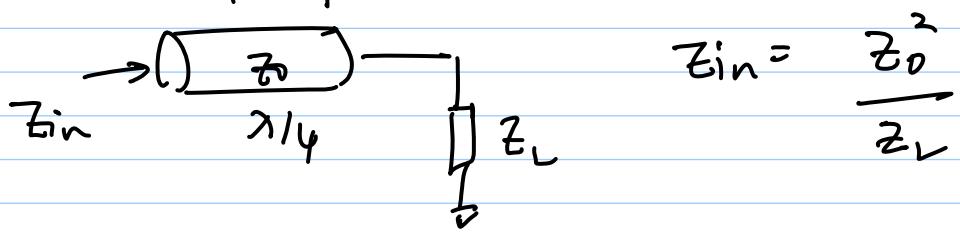

here $Z_{in} = R_L \oplus \omega_0$


LC tank $\Rightarrow Z(\omega) = 0$ for $\omega \neq \omega_0$ (short circuit)

$$@ \omega = 2n\omega_0, \text{T-line } l = 2n \frac{\lambda}{4} = n \frac{\lambda}{2}$$

\Rightarrow short circuit - @ Drain

$$@ \omega = (2n+1)\omega_0, \text{T-line } l = (2n+1)\lambda/4$$

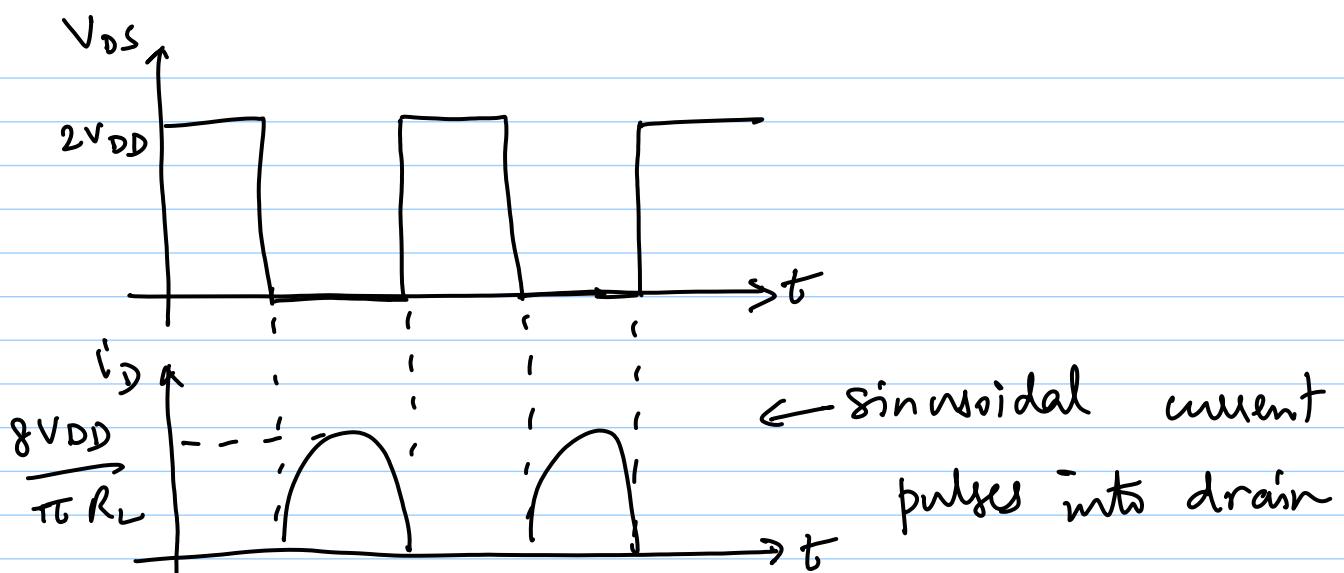LC - tank short circuit \Rightarrow open circuit - @ Drain



$$V_{fund.} = \frac{4}{\pi} (V_{DD})$$

$$P_o = \left[\frac{4}{\pi} \left(\frac{V_{DD}}{\sqrt{2}} \right) \right]^2 \cdot \frac{1}{R_L} = \frac{8V_{DD}^2}{\pi^2 R_L}$$


$$\eta_{\text{ideal}} = 100\%$$

in practice $\eta > \eta_{\text{Class-E}}$

$$P_N = \frac{P_o}{V_{DS\text{pk.}} \cdot I_{D\text{pk.}}} = \frac{8V_{DD}^2 / \pi^2 R_L}{2V_{DD} \cdot \frac{8V_{DD}}{\pi R_L}}$$

$$= \frac{1}{2\pi} \approx 0.16 \quad (\text{better than Class-E})$$

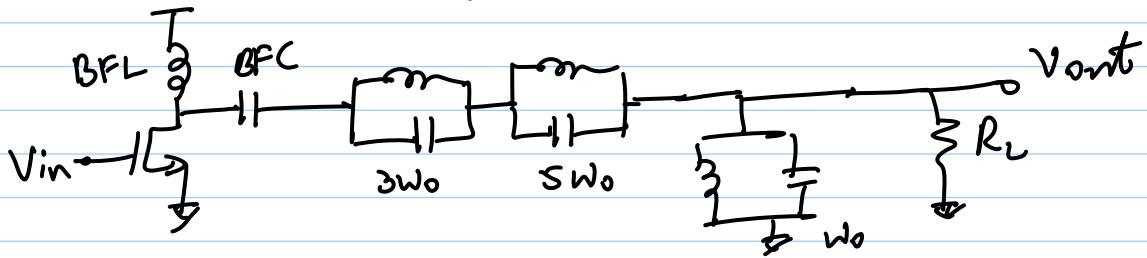alternative topology: replace T-lines with L-C



* Note: Switching PAs are constant envelope PAs

$$V_{out} = f(V_{DD}), \text{ & not } f(V_{in})$$

Other design considerations:

1) Power-added Efficiency:

$$\text{PAE} = \frac{P_{out} - P_{in}}{P_{DC}}$$

$$\text{obviously } \text{PAE} < \eta$$

→ takes power gain into account

- 2) Stability: * C_{gd} is very important (layout)
* stability-gain trade off

3) Breakdown

* Output swings upto $2V_{DD}$

* BV reduces as tech. scales

→ DB & SB diode breakdown (A)

→ D-S punchthrough (B)

→ Time-dependent dielectric breakdown (TDDB) (C)

→ Gate oxide rupture (D)

(A) : Diode $BV \sim$ few V ($2-3 \times V_{DD}$)

(B) : If V_D is large, depletion region extends to source, eliminating the channel

(C) : Gate oxide damage due to energetic carriers - @ high fields, high energy e⁻s create oxide traps ; charge trapped here shift device V_T (cumulative)

(D) : Gate oxide rupture occurs @ high gate fields

4) Large-signal impedance matching