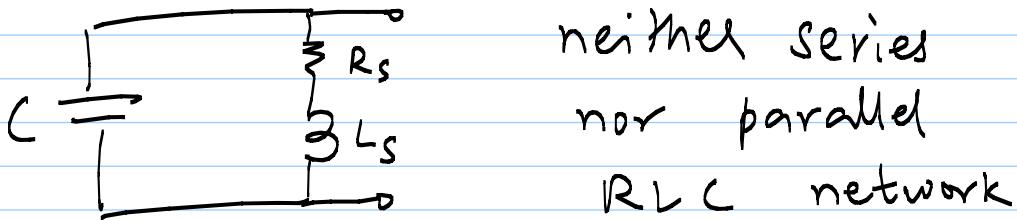


Lecture #4 - Impedance Transformations & Matching ; L-matches

why?

- * RF input and output impedances are standardized to 50Ω (75Ω for TV components)
- * 50Ω is approx. tradeoff between max. power handling capability and min. loss
- * on-chip - try to minimise 50Ω impedances (large power needed to drive 50Ω)
- * match at LNA input and DA/PA output

Series - parallel transformations :



make series-parallel conversion at resonance \Rightarrow



$$R_s + j\omega_0 L_s = \frac{R_p \cdot j\omega_0 L_p}{R_p + j\omega_0 L_p}$$

$$= \frac{(j\omega_0 L_p)^2 R_p + j\omega_0 L_p R_p^2}{R_p^2 + (\omega_0 L_p)^2}$$

Equate real and imaginary components:

Real part:

$$R_s = \frac{(\omega_0 L_p)^2 R_p}{R_p^2 + \omega_0^2 L_p^2};$$

$$\text{we know } Q_p = \frac{R_p}{\omega_0 L_p}$$

$$Q_s = \frac{\omega_0 L_s}{R_s}$$

$$\text{and } Q_p = Q_s = Q$$

$$\therefore R_s = \frac{R_p}{1 + \frac{R_p^2}{(\omega_0 L_p)^2}}$$

$$R_p = R_s (1 + Q^2)$$


Imaginary part:

$$\omega_0 L_s = \frac{\omega_0 L_p R_p^2}{R_p^2 + (\omega_0 L_p)^2}$$

$$L_s = L_p \cdot \frac{R_p^2 / (\omega_0 L_p)^2}{1 + \left(\frac{R_p}{\omega_0 L_p}\right)^2} = L_p \cdot \frac{Q^2}{1+Q^2}$$

$$L_p = \frac{L_s (1+Q^2)}{Q^2}$$

Note: HW 1 will include:

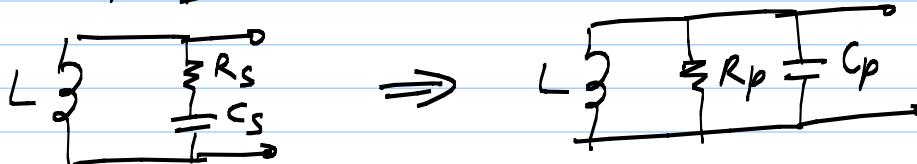

$$R_p = R_s (1 + Q^2)$$

$$C_p = C_s \cdot \frac{Q^2}{1+Q^2}$$


In general:

$$R_p = R_s (1+Q^2)$$

$$X_p = X_s \cdot \frac{1+Q^2}{Q^2}$$

Maximum Power Transfer Theorem:

"conjugate match"

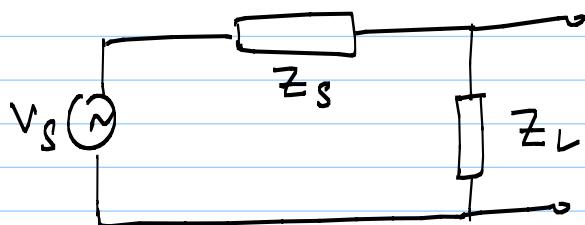

$$Z_s = R_s + jX_s$$

$$Z_L = R_L + jX_L$$

Max power in Z_L is achieved when


$$R_L = R_s \quad \& \quad X_L = -X_s$$

Note: in LNAs, optimum noise match \neq optimum power match

Impedance matching:

Traditional mmWave techniques:

1) $\lambda/4$ transformer:

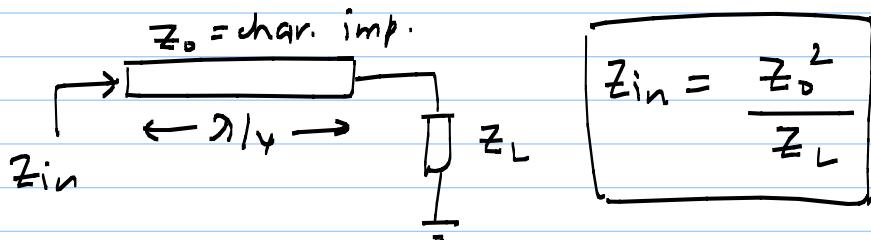


2) Stub matching:

* Use open and short T-Lines to rotate impedance in Smith Chart, to obtain desired Z_{in}


* Use series or shunt stub depending on whether Z or γ is being manipulated

L-match networks: use lumped components

(A) Upward impedance transformer:

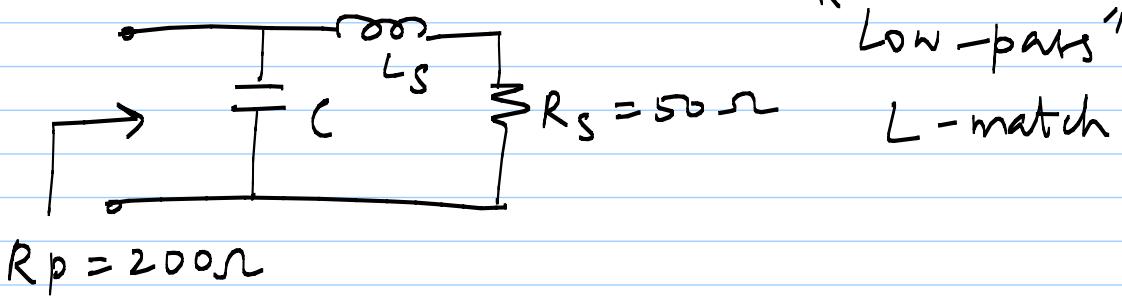

1

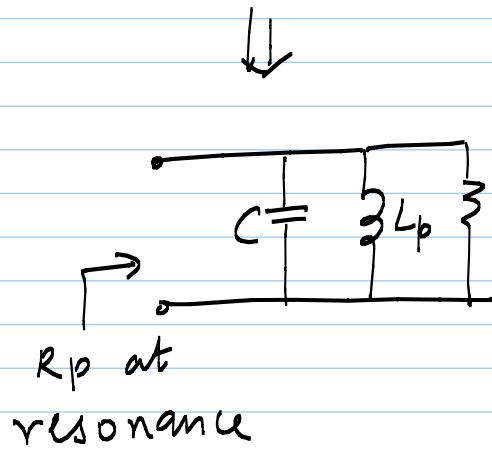

$$L_p = L_s \frac{1+q^2}{q^2}$$

$$R_p = R_s (1 + Q^2)$$

$$\text{i.e. } Q = \sqrt{\frac{R_P}{R_S} - 1} \quad \dots \quad (1)$$

$$Q = \frac{R_p}{w_0 L_p} \Rightarrow L_p = \frac{R_p}{w_0 Q} \quad \text{--- (2)}$$

$$L_s = \frac{Q^2 L_p}{1 + Q^2} \quad \text{--- } \textcircled{2}$$

$$C = \frac{1}{L_0 \omega_0^2} \quad \text{--- } 4$$

Use these 4 equations to determine C_s , L_s

e.g. Match $50\ \Omega$ to $200\ \Omega$ at 2.46 GHz

We know: R_s , R_p , ω_0


$$50\Omega \quad | \quad 200\Omega \quad | \quad 2\pi \cdot 2 \cdot 46\text{Hz}$$

$$Q = \sqrt{\frac{200}{50} - 1} = \sqrt{3} = 1.73$$


reasonable
values
for λ
implementation

$$\Rightarrow L_p = 7.67 \text{ nH} \Rightarrow L_s = 5.75 \text{ nH} \Rightarrow C = 0.573 \text{ pF}$$

Alternative upward transformer:

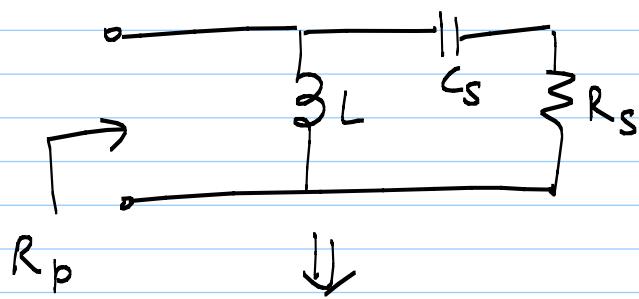

"High-pass" L-match

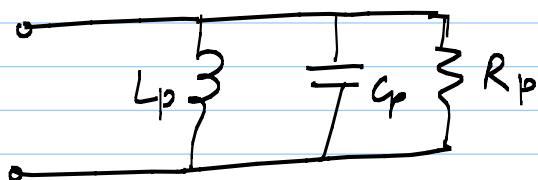

$$C_p = C_s \cdot \frac{Q^2}{1+Q^2}$$

$$R_p = R_s (1 + Q^2)$$

$$\text{i.e. } Q = \sqrt{\frac{R_p}{R_s} - 1}$$

e.g. $50\Omega \rightarrow 200\Omega$ at 2.4GHz

$$Q = \sqrt{3} = 1.73$$

$$Q = \omega_0 C_p R_p \Rightarrow C_p = \frac{Q}{\omega_0 R_p} = \frac{1.73}{2\pi \times 2.4\text{GHz} \times 200} \\ = 0.574\text{ pF}$$

$$C_s = C_p \cdot \frac{1+Q^2}{Q^2} = 0.765\text{ pF}$$


$$L = \frac{1}{\omega_0^2 C_p} = 7.66\text{nH}$$

High-pass
or
Low-pass?

Considerations for choice:

1) Die area: Smaller inductor (low-pass is also lower loss in this case)

2) Quality of match vs. frequency

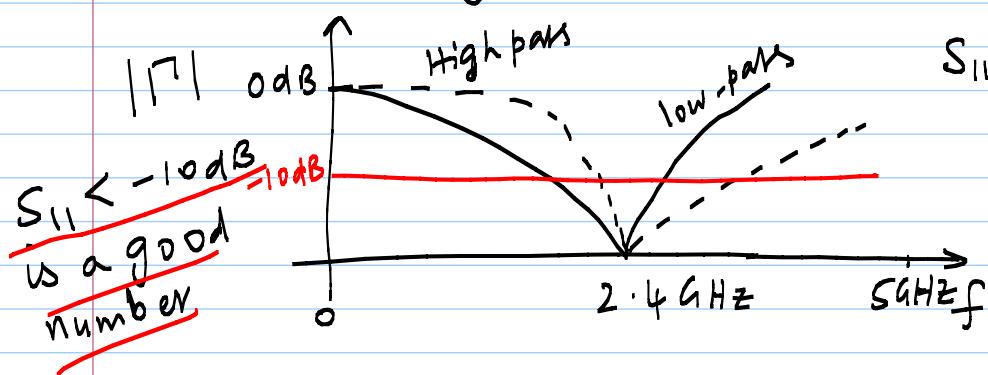

$S_{11} = \Gamma$ (for a 1-port)
reflection coefficient

$$= \frac{Z_L - Z_0}{Z_L + Z_0} \quad \text{where} \\ Z_0 = \text{source imp.}$$

3) Relationship to parasitics (e.g. output bondwires etc.)


Note: Matching to complex load

e.g. $Z_L = 50 - j25 \Rightarrow \frac{50}{j25} \parallel C_L$

at 2.4 GHz ,

$$\frac{-j}{\omega_0 C_L} = -j25$$

$$\Rightarrow C_L = 2.65 \text{ pF}$$

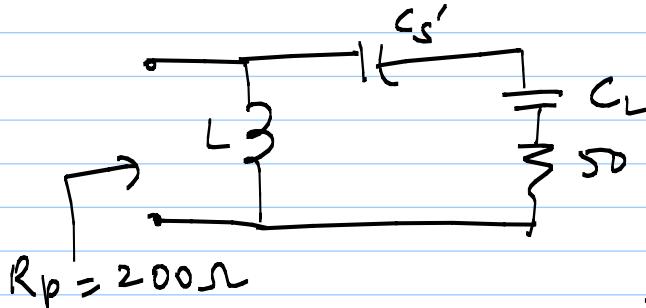

Total $C_s = C_L$ series C_s'



we know $C_s = 0.765 \text{ pF}$
from before

$$\Rightarrow C_s = \frac{C_s' C_L}{C_s' + C_L}$$

$$\Rightarrow C_s' = \frac{C_L C_s}{C_L - C_s} = \frac{(2.65 \text{ pF})(0.765 \text{ pF})}{2.65 \text{ pF} - 0.765 \text{ pF}} = \underline{\underline{1.08 \text{ pF}}}$$

(B) Downward Impedance Transformers:

Switch ports!

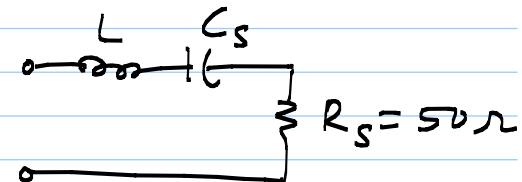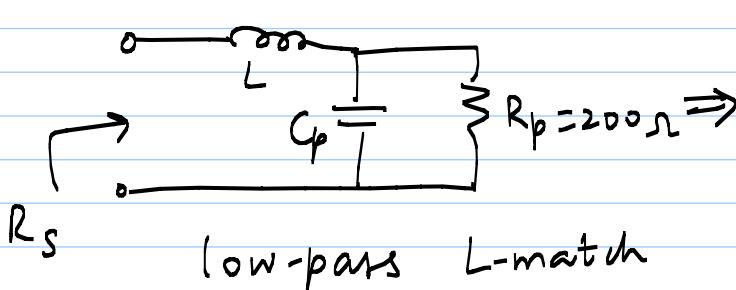

$$R_p = R_s(1+Q^2)$$

$$C_p = C_s \left(\frac{Q^2}{Q^2 + 1} \right)$$

e.g. $R_p = 200 \Omega$, $R_s = 50 \Omega$ at $f_0 = 5.6 \text{ GHz}$


$$Q = \sqrt{\frac{R_p}{R_s} - 1} = \sqrt{3} = 1.73$$

$$Q = \frac{1}{\omega_0 R_s C_s} \Rightarrow C_s = \frac{1}{\omega_0 Q R_s} = \frac{1}{2\pi \cdot 5.6 \text{GHz} \cdot 1.73 \cdot 50} = 0.329 \text{ pF}$$

$$\Rightarrow C_p = C_s \frac{Q^2}{1+Q^2} = 0.246 \text{ pF}$$

$$L = \frac{1}{\omega_0^2 C_s} = 2.46 \text{nH}$$

High-pass L-match:

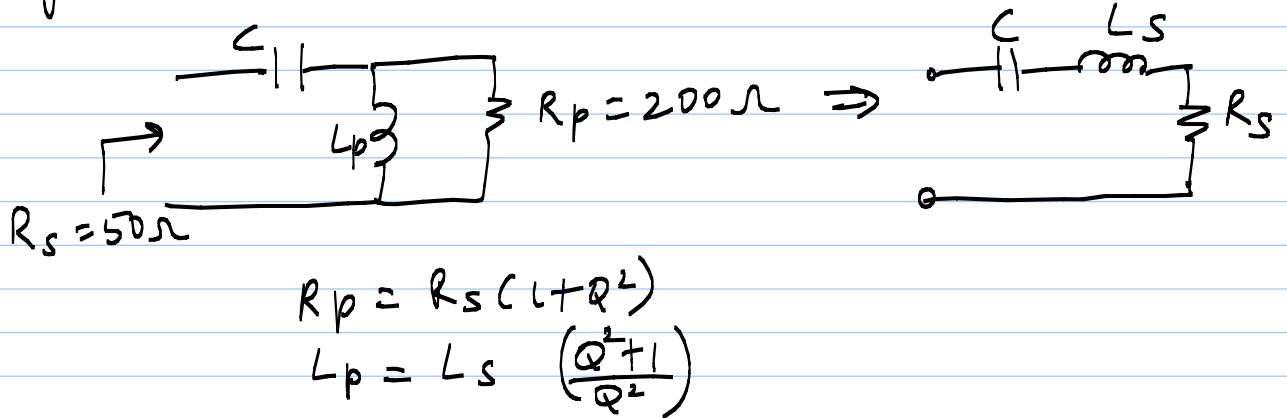

$$Q = \sqrt{\frac{R_p}{R_s} - 1} = \sqrt{3} = 1.73$$

$$Q = \frac{\omega_0 L_s}{R_s} \Rightarrow L_s = \frac{Q R_s}{\omega_0} = \frac{1.73 \times 50}{2\pi \times 5.6 \text{GHz}} = 2.46 \text{nH}$$

$$\Rightarrow L_p = \left(2.46 \text{nH} \right) \cdot \left(\frac{4}{3} \right) = \underline{\underline{3.28 \text{nH}}}$$

$$C = \frac{1}{\omega_0^2 L_s} = \underline{\underline{0.328 \text{ pF}}}$$

What was common to all L-matches?

$$Q = \sqrt{\frac{R_p}{R_s} - 1}$$

Quality of match is fixed once R_{in} , R_L are known!