


Lecture #5 : π and T-matches; Other matches

L-match - 2 degrees of freedom ($L \ll c$)

But, we want to fin } 3 parameters } ω_0 , $\frac{R_p}{R_s}$ and Q


Remember that $Q \leftrightarrow BW$ } $Q = \frac{\omega_0}{BW}$

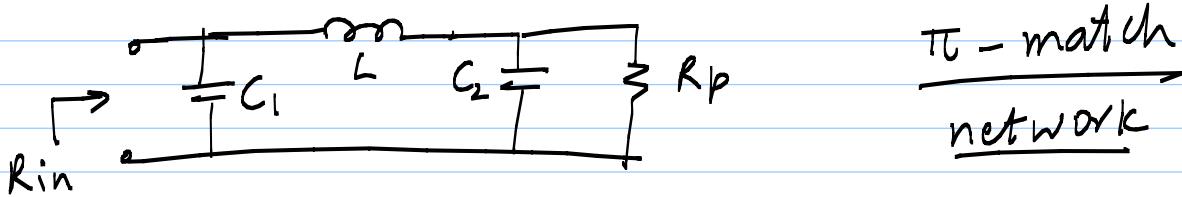Solution: add a third element to the matching network - one more degree of freedom



π -match
network


Decompose into
2 L-matches

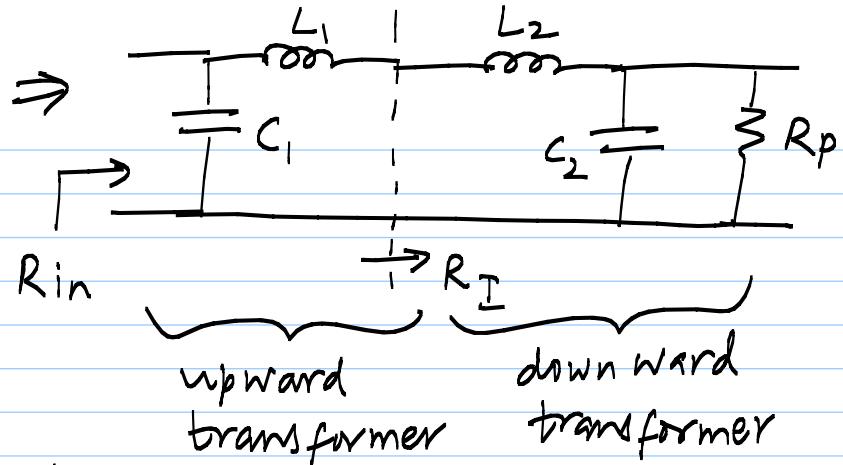


$R_I \equiv$ intermediate

resistance

R.H.S. Section \Rightarrow

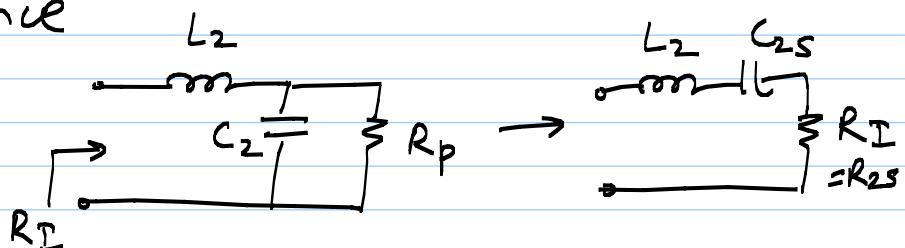
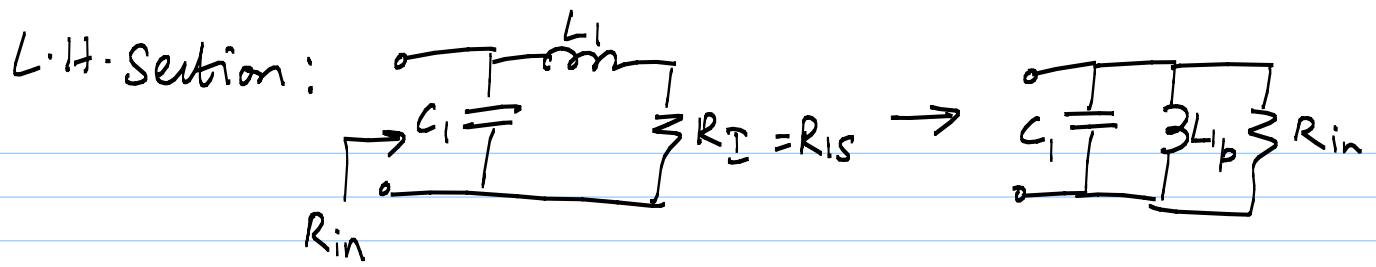
$$Q_{\text{right}} = \sqrt{\frac{R_p}{R_I} - 1} = \frac{\omega_0 L_2}{R_I}$$



$$Q_{left} = \sqrt{\frac{R_{in}}{R_2}} - 1 = \frac{\omega_0 L_1}{R_2}$$

It can be shown that

$$\begin{aligned} \text{overall } Q &= Q_{left} + Q_{right} \\ &= \frac{\omega_0 (L_1 + L_2)}{R_2} \end{aligned}$$

see posted
document
for this
derivation

$$Q = \sqrt{\frac{R_{in}}{R_2}} - 1 + \sqrt{\frac{R_p}{R_2} - 1}$$

e.g. $R_p = 200\Omega$, $R_{in} = 50\Omega$, $f_0 = 2.4\text{kHz}$, $Q = 10$

* Need to find out R_2 first.

$$Q = Q_{left} + Q_{right}$$

$$10 = \sqrt{\frac{50}{R_2} - 1} + \sqrt{\frac{200}{R_2} - 1}$$

solve using 1) quadratic equations
or 2) iteration

$$\text{try } R_2 = 10\Omega \Rightarrow \sqrt{4} + \sqrt{19} = 6.36$$

$$\text{try } R_2 = 4\Omega \Rightarrow \sqrt{11.5} + \sqrt{49} = 10.39$$

after several iterations, $R_2 = 4.3\Omega$

$$Q_{left} = \sqrt{\frac{50}{4.3} - 1} = 3.26$$


$$Q_{right} = \sqrt{\frac{200}{4.3} - 1} = 6.74$$

$$L_1 = \frac{Q_{left} \cdot R_I}{\omega_0} = \frac{(3.26)(4.3)}{2\pi \cdot 2.4 \text{ Hz}} = 0.93 \text{ nH}$$

$$L_2 = \frac{Q_{right} \cdot R_I}{\omega_0} = \frac{(6.74)(4.3)}{2\pi \cdot 2.4 \text{ Hz}} = 1.92 \text{ nH}$$

$$L = L_1 + L_2 = \underline{\underline{2.85 \text{ nH}}}$$


left side

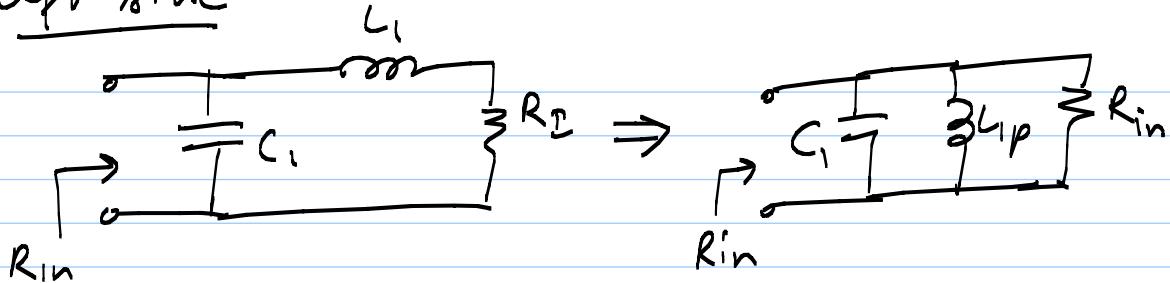

$$Q_{left} = \omega_0 R_{in} C_1$$

$$C_1 = \frac{Q_{left}}{\omega_0 R_{in}} = \frac{3.26}{(2\pi \cdot 2.4 \text{ Hz}) \cdot (50)} = 4.32 \text{ pF}$$


Right side

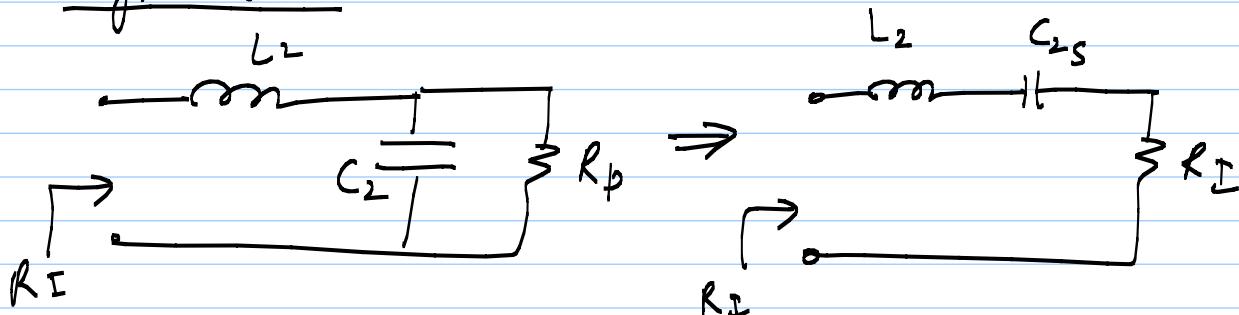



$$Q_{right} = \omega_0 R_p C_2$$

$$C_2 = \frac{Q_{right}}{\omega_0 R_p} = \frac{6.74}{(2\pi \cdot 2.4 \text{ GHz}) \cdot (200)} = 2.24 \text{ pF}$$

Final matching network:

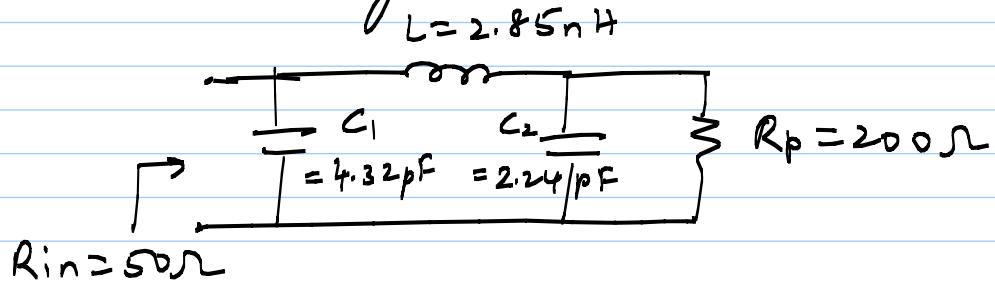

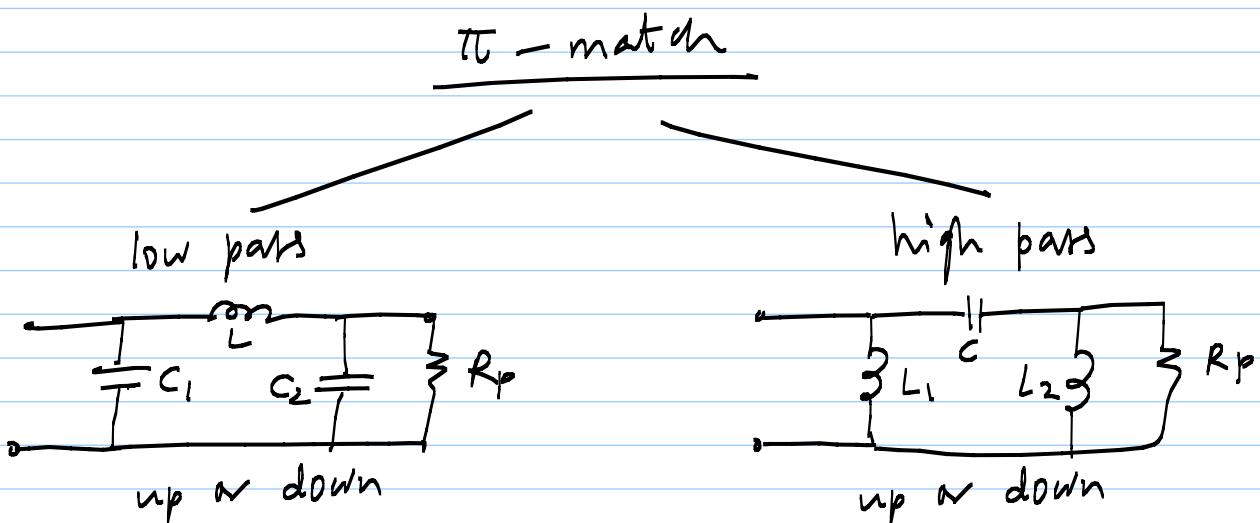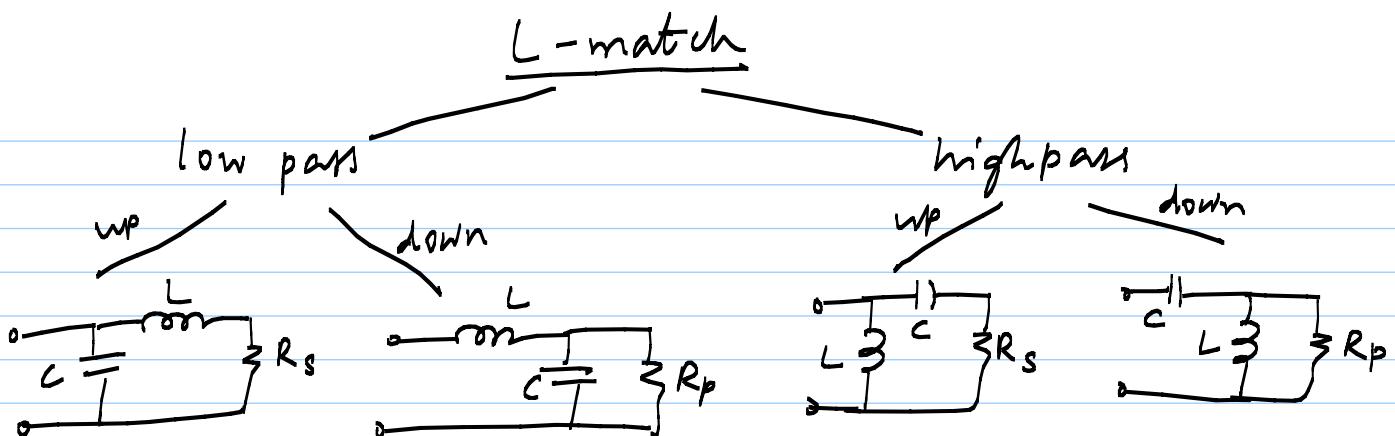
- * Capacitive parasitics (including from L) are absorbed into C_1 & C_2 !
- * $R_I < Rin, R_p$ for a π -match






T-match

(will have a problem on
T-match in HW1)

low pass

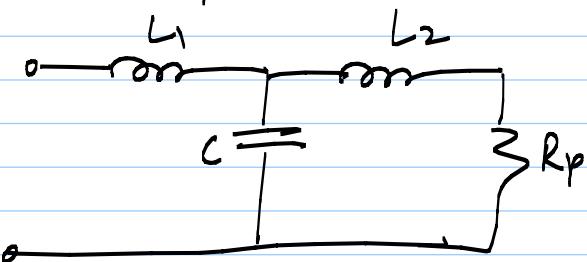


high pass

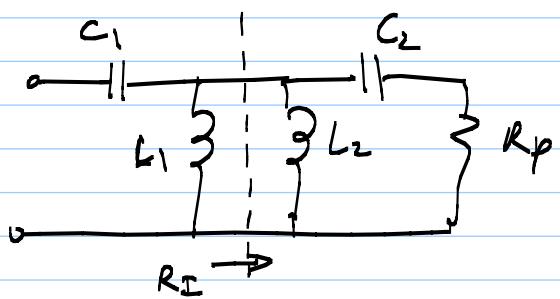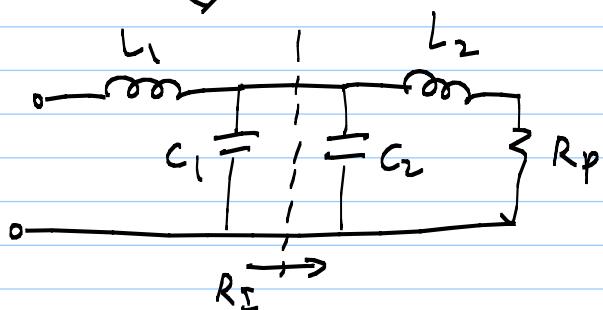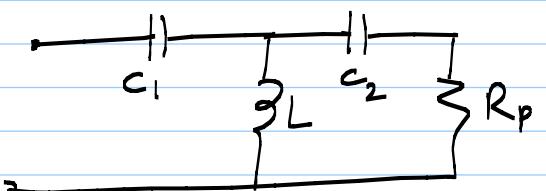

Note : $R_I > R_{in}$, R_p for T-match


Tapped Capacitor Match

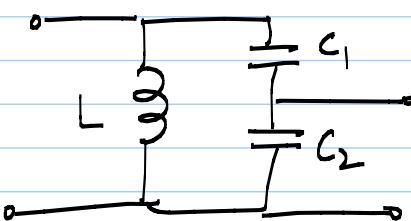3 degrees of freedom: L, C_1, C_2
 \Rightarrow can set w_o, R
 and $\frac{R_{out}}{R_{in}}$




up

down

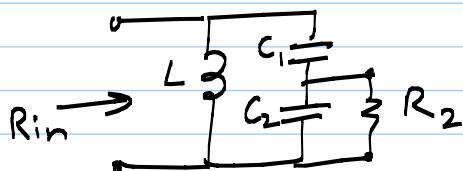


$R_{in} > R_2$

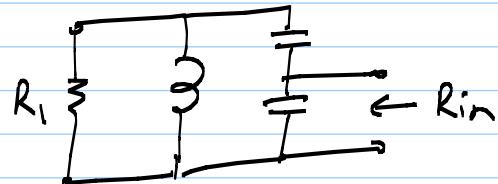

$R_{in} < R_1$

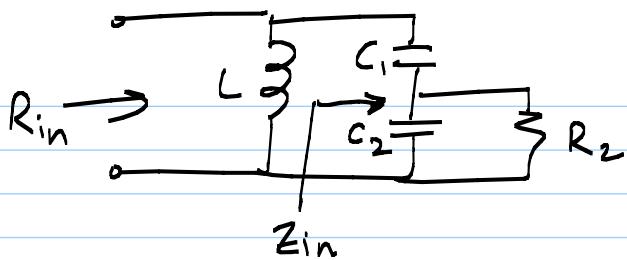* You will see this type of circuit used in certain types of oscillators.



$$Z_{in} = \frac{1}{sC_1} + \frac{R_2}{1 + sC_2 R_2}$$

$$= \frac{1 + sC_2 R_2 + sC_1 R_2}{sC_1 + s^2 C_1 C_2 R_2}$$

$$Y_{in}(j\omega) = \frac{j\omega C_1 - \omega^2 C_1 C_2 R_2}{1 + j\omega R_2 (C_1 + C_2)}$$

$$= \frac{j\omega C_1 - \omega^2 C_1 C_2 R_2 + \omega^2 C_1 R_2 (C_1 + C_2) + j\omega^3 C_1 C_2 R_2^2 (C_1 + C_2)}{1 + [\omega R_2 (C_1 + C_2)]^2}$$



Real part:

$$G_{in} = \frac{\omega^2 R_2 C_1^2}{1 + [\omega R_2 (C_1 + C_2)]^2} \approx \frac{\cancel{\omega^2 R_2 C_1^2}}{\cancel{\omega^2 R_2^2} (C_1 + C_2)^2}$$

$$\approx G_2 \cdot \left(\frac{C_1}{C_1 + C_2} \right)^2 = \frac{G_2}{n^2}$$

$$\text{where } G_2 = \frac{1}{R_2}$$
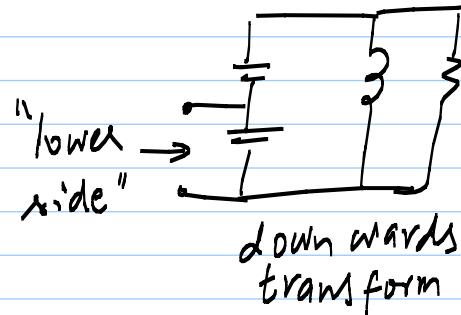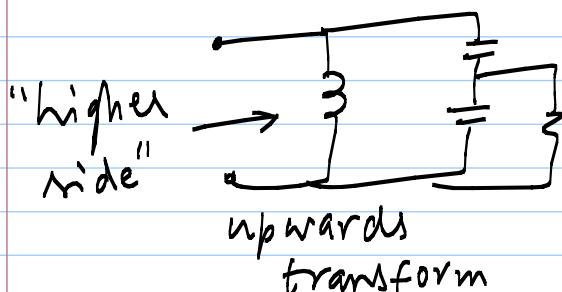
$$\text{and } n \equiv \text{trans ratio} = \frac{C_1 + C_2}{C_1}$$



Imaginary Part:

$$B_{in} = \frac{\omega C_1 + \omega^3 C_1 C_2 R_2^2 (C_1 + C_2)}{1 + \omega^2 R_2^2 (C_1 + C_2)^2}$$

$$\approx \frac{\omega^3 C_1 C_2 R_2^2 (C_1 + C_2)}{\cancel{\omega^2 R_2^2} (C_1 + C_2)^2} \text{ at high freq.}$$

$$\approx \omega \frac{C_1 C_2}{C_1 + C_2} = \omega C_{eq} \text{ as expected}$$

Matching Equations:

$$Q = \frac{R_{in}}{\omega_0 L} \Rightarrow \boxed{L = \frac{R_{in}}{\omega_0 Q}}$$

$$\Rightarrow \begin{array}{c} \xrightarrow{\hspace{1cm}} \\ \text{Circuit Diagram: } R_{in} \parallel \left(\frac{1}{j\omega C_1} \parallel \frac{1}{j\omega C_{2s}} \parallel R_2 \right) \end{array} \quad C_{2s} = C_2 \left(\frac{Q_2^2 + 1}{Q_2^2} \right)$$

$$Q_2 = \omega_0 C_2 R_2$$

$$R_{2s} = \frac{R_2}{Q_2^2 + 1}$$

$$C_{eqs} = \frac{C_1 C_{2s}}{C_1 + C_{2s}}$$

$$\Rightarrow \begin{array}{c} \xrightarrow{\hspace{1cm}} \\ \text{Circuit Diagram: } R_{in} \parallel \left(L \parallel \frac{1}{j\omega C_{eqs}} \parallel R_p \right) \end{array} \quad R_p = R_{in} = R_{2s} (Q^2 + 1)$$

$\neq Q_2$, $\therefore C_1$ is also included

$$\frac{R_2}{Q_2^2 + 1} = \frac{R_{in}}{Q^2 + 1} \Rightarrow Q_2 = \sqrt{\frac{R_2 (Q^2 + 1)}{R_{in}} - 1}$$

$$Q_2 = \omega_0 R_2 C_2 \Rightarrow C_2 = \frac{Q_2}{\omega_0 R_2}$$

$$C_2 = \boxed{\frac{\sqrt{\frac{R_2(Q^2+1)}{R_{in}} - 1}}{\omega_0 R_2}}$$

$$C_{eqS} = \frac{C_1 C_{2S}}{C_1 + C_{2S}} \Rightarrow Q = \frac{1}{\omega_0 C_{eqS} R_{2S}} = \frac{(C_1 + C_{2S})}{\omega_0 C_1 C_{2S} R_{2S}}$$

$$\Rightarrow \boxed{C_1 = \frac{C_2 (Q_2^2 + 1)}{Q_2 Q_2 - Q_2^2}}$$

e.g. $R_2 = 50 \Omega$, $R_{in} = 200 \Omega$, $f_0 = 2.4 \text{ GHz}$, $Q = 10$

$$L = \frac{R_{in}}{\omega_0 Q} = \frac{200}{2\pi \cdot 2.4 \text{ GHz} \cdot 10} = \underline{\underline{0.75 \text{ nH}}}$$

$$Q_2 = \sqrt{\frac{R_2}{R_{in}} (Q^2 + 1) - 1} = \sqrt{\frac{50}{200} (100 + 1) - 1} = 4.92$$

$$C_2 = \frac{Q_2}{\omega_0 R_2} = \frac{4.92}{2\pi \cdot 2.4 \text{ GHz} \times 50}$$

$$= \underline{\underline{6.53 \text{ pF}}}$$

$$C_1 = \frac{C_2 (Q_2^2 + 1)}{Q_2 Q_2 - Q_2^2} = \frac{6.53 (4.92^2 + 1)}{10 \cdot 4.92 - 4.92^2} = \underline{\underline{6.61}}$$

$$\text{Recall : } R_{in} \approx R_2 \left(\frac{c_1 + c_2}{c_1} \right)^2 = n^2 R_2$$

in this case, $R_{in} = 200$, $R_2 = 50$

$$\Rightarrow n = 2 \quad (\text{"turns ratio" } \neq 2)$$

$$\Rightarrow c_1 \approx c_2 \quad (\text{as computed})$$