

## Lecture #7: RF inductors, Transformers (contd.)


Figures of Merit:

- 1) Q: usually want this to be maximised  
in the frequency range of interest  
- Note that the model is not a simple series or parallel RLC

how is Q determined?

a) Physical definition:  $2\pi \cdot \frac{E_{stored}(\text{peak})}{E_{loss \text{ per cycle}}}$


b)

 

$$Q = \frac{\text{Im}(Z_{in})}{\text{Re}(Z_{in})} = \frac{\text{Im}(Y_{in})}{\text{Re}(Y_{in})}$$


$$Z_{in} = \frac{1}{Y_{in}}$$
 
$$Q = f(L_s, R_s, C_c, C_o, C_{si}, R_{si})$$



$$Q_{ind} = \frac{\frac{1}{\omega L} - \omega C}{\frac{1}{R}} \quad \left\{ \begin{array}{l} \text{in} \\ \text{inductive} \\ \text{region} \end{array} \right\}$$

- \* SOI processes show much higher Q than regular CMOS processes
- \* Substrate losses reduce with distance from substrate — Use highest possible metal (these are also usually thicker than lower metals)
- \* Use Patterned Ground Shield, if appropriate
  - better Q : a) current loops are broken by slotting — eddy currents ↓
  - also reduces substrate noise coupling
  - more shunt capacitance (shield is now closer than substrate)

 


## 2) Self-resonant frequency $f_{SR}$

- Frequency at which inductance of spiral resonates with its own capacitive parasitics
- \* Real inductors have capacitive parasitics
- \* Real capacitors have inductive parasitics
- \* Remember — tank circuits have both inductors & capacitors
- \* Patterned ground shield reduces  $f_{SR}$

- at  $f_{SR}$ , inductor impedance is purely resistive, and  $Q_{ind} = 0$
- Beyond  $f_{SR}$ , the inductor behaves capacitively
- $f_{SR}$  depends on spiral area


3) Total area occupied on chip A

 

### Transformers :


- \* Used in differential circuits (usually)
- \* Need to be symmetric
- \* Coupling factor to be maximized (usually)
  - there are cases where you would design for a specific coupling factor

$P_1$

 
 
### Planar Transformer - I

- \* Sideways coupling,  $n=2$
- \* Primary & secondary are symmetric
- \* Ports  $P_1 \& P_2$  ( $S_1 \& S_2$ ) are not symmetric



### Planar Transformer - 2

\*  $n=1$

\* P & S symmetric

\*  $P_1 - P_2$  &  $S_1 - S_2$  are more symmetric than case 1  
— under park causes asymmetry




### Vertical Transformer

\*  $n=1$

\* P & S are completely asymmetric (different metal layers)

### Transformer $\pi$ -model

 

\* Can cascade coils on multiple metal layers to make a spiral with large L in a given area  
— larger series resistance due to higher  $\rho$  of lower metal layers

— useful to create "RF chokes" for PAs and wideband RF amplifiers

## Other things to remember

- \* Overall LC tank Q is often limited by inductor Q
- \* Don't place anything close to a spiral inductor (inductor & fmr.)
- \* Use a guard ring around inductor for noise isolation and to provide good EM boundary conditions
- \* No metal fill inside/ inductor (what is this?)
- \* maintain symmetry - gives higher Q
- \* Via resistance matters - use lots of vias in parallel if you need to change metal layers

Note: \* Project 1 will involve spiral inductor design using ASITIC

- \* You will be designing your own inductors using ASITIC for projects 2, 3 & 4 also. The design of the inductor will impact circuit performance, so learn this well.
- \* HW2 will include an impedance matching problem with a real inductor.