

## **EE6240 Homework 1: Due Wednesday 31/08/2011**

1. Impedance transformation networks are widely used in power amplifier designs to enable a specific amount of power to be delivered to a load. Owing to supply voltage limitations, a downward impedance transformation of the antenna resistance is usually necessary. Suppose we wish to deliver 1W of power to a  $50\Omega$  antenna at 2.4GHz, but the power amplifier has a maximum peak-to-peak output swing of only 4V.

a) What is the maximum power that can be delivered to the load without a matching network?

b) Design a high-pass T-match network with a  $Q=5$  using ideal passive components that can deliver the desired power to the load.

c) Verify the above results using any appropriate simulator of your choice: Eldo (preferred), Spectre or Hspice. Plot  $S_{11}$  (magnitude in dB) and  $Z_{in}$  (magnitude in  $\Omega$  and phase in  $^\circ$ ) versus frequency from 10MHz-10GHz. Also, determine the  $-3\text{dB}$  bandwidth from your simulation, and compare the  $Q$  derived from the BW definition with the  $Q$  that you designed for.

d) Design the inductor of the above T-match network in ASITIC. You may use either square or octagonal spirals (i.e. no circular spirals), and maximum outer diameter is  $200\mu\text{m}$ .

e) Re-run the matching network simulation after replacing the ideal inductor with the  $\pi$ -model generated from ASITIC to see how the impedance matching has been affected. Again, plot  $S_{11}$  (magnitude in dB) and  $Z_{in}$  (magnitude in  $\Omega$  and phase in  $^\circ$ ) versus frequency from 10MHz-10GHz. Try to maximise  $Q$  and  $f_{SR}$  in (d) above, as that will reduce the deviation from ideal behaviour.