

EE5390 Homework 1: Due Wednesday 08/02/2012

1. a) Derive the analytical expression for output current in the circuits shown in Figures 1 & 2.
b) In each case, determine the sensitivity of output current to supply voltage given the following parameters: $V_{DD} = 1.3V$; $V_{T1,2} = 0.3V$; $k' = 200\mu A/V^2$; $(W/L)_1 = (W/L)_2 = 25$; $R_1 = 8k\Omega$; $R_2 = 4k\Omega$; {sensitivity $S = (V_{DD}/I_{OUT})(\partial I_{OUT}/\partial V_{DD})$ }
2. Consider the circuit shown in Figure 3. Assume that Q_2 has a saturation current of I_S , while Q_3 and Q_4 have a saturation current of nI_S . Neglect the portion of I_0 flowing through the resistors, and neglect all base currents. Determine the expression for bias current I_{BIAS} in terms of other circuit parameters.
3. Consider the circuit shown in Figure 4. Assume the MOSFETs follow the long-channel device equation $I_D = \beta(V_{GS} - V_T)^2$. You are given the following parameters: $I_0 = 1mA$; $V_{DD} = 5V$; $\beta_2 = 5mA/V^2$; $V_{T1,2} = 1V$; $R_1 = 1k\Omega$; $R_2 = 5k\Omega$; $n=3$. Determine the values of V_{OUT} , V_X and I_X .
4. a) Design an NMOS high-swing cascode current mirror using device parameters from the IBM 0.13 μm process file supplied to you. The circuit specifications are: $V_{OUT, min} = 0.3V$; $R_{OUT, min} = 100k\Omega$; $I_{IN} = 1\mu A$; $I_{OUT} = 100\mu A$.
b) Calculate the output current noise spectral density in A/\sqrt{Hz} (neglect flicker noise)
c) Simulate the circuit in (a) and compare with your calculations. If you observe significant differences between calculated and simulated results, explain why there is a difference and modify your design to meet the specifications. {final $I_{OUT} = 100\mu A \pm 0.1\%$ }
d) Plot R_{OUT} when V_{OUT} is varied from 0.1V to 1.3V. What behaviour do you see and why?
e) Plot output current noise spectral density in A/\sqrt{Hz} between 100Hz and 100MHz, and compare the value in the white noise region with that from (b). If there is a discrepancy, explain why.

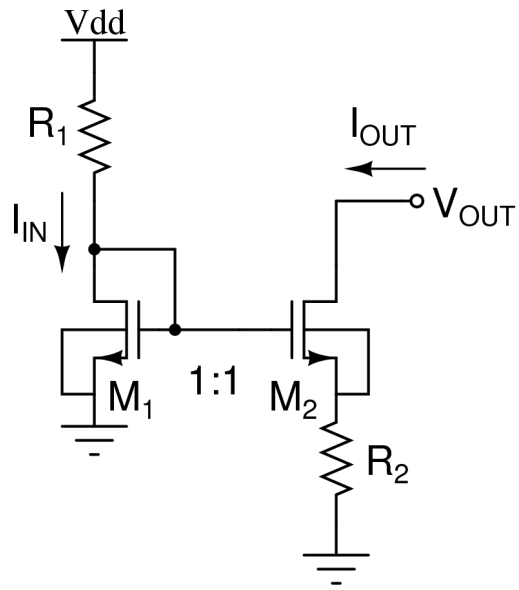


Figure 1

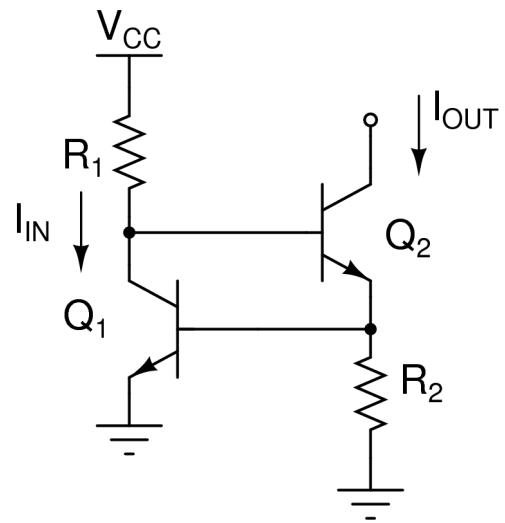


Figure 2

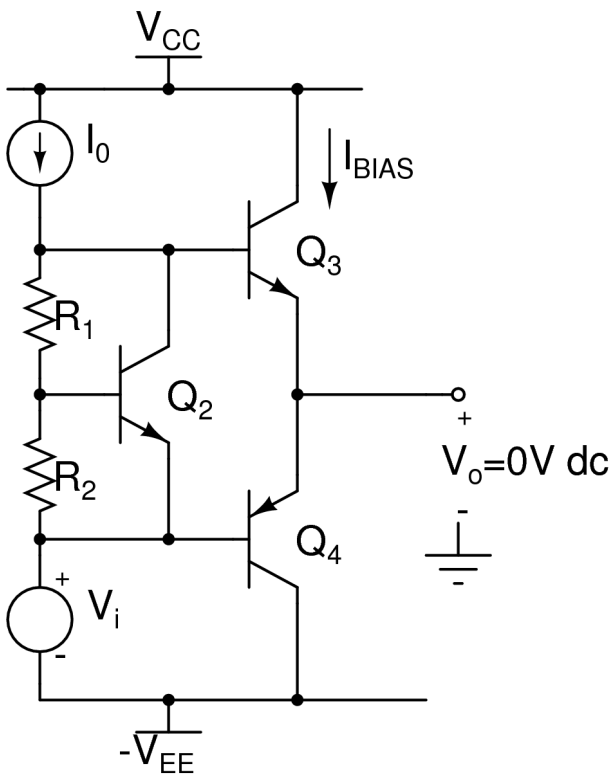


Figure 3

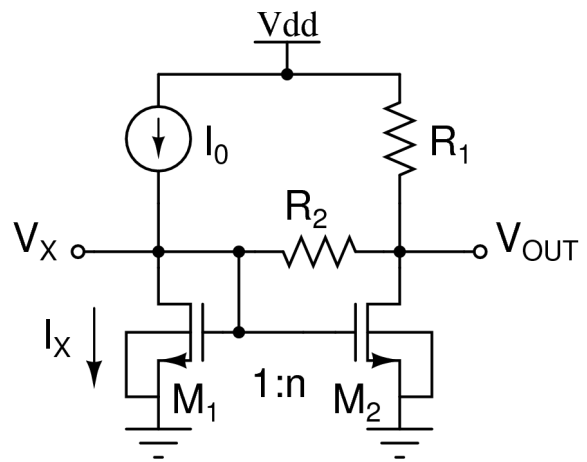


Figure 4