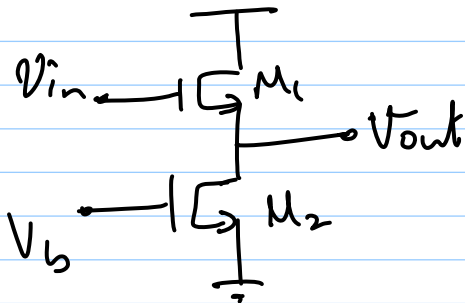


25/1/12

Lec 10

Source Follower



recall $g_{out} = g_{m1} + g_{mbs1} + g_{ds1} + g_{ds2}$

$$a_v = \frac{g_{m1}}{g_{out}}$$


$$\frac{\overline{v_{n_{out}}^2}}{\Delta f} = (4kT \gamma_1 g_{m1} + 4kT \gamma_2 g_{m2}) \cdot \frac{1}{g_{out}^2}$$

$$\frac{\overline{v_{n_{in}}^2}}{\Delta f} = \frac{4kT \gamma_1}{g_{m1}} + \frac{4kT \gamma_2 g_{m2}}{g_{m1}^2}$$

{ very similar to C.S. with PMOS current source }

* Source followers add noise & gain $< 1 \Rightarrow$ not preferred in LNAs

Cascode

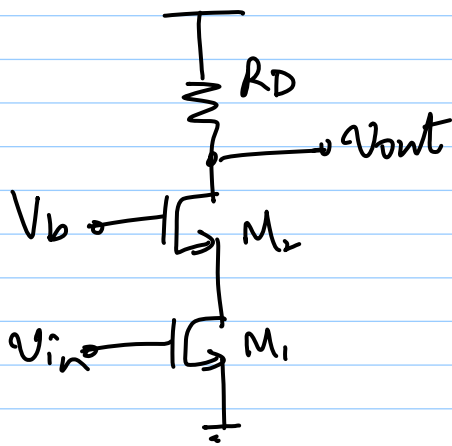


$$\frac{\overline{v_{n,out}^2}}{\Delta f}(M_1, R_D) = \left[4kTg_D + 4kT\gamma_1 g_{m1} \right] R_D^2$$

(ignore $1/f$ noise)

$$a_v = -g_{m1} R_D$$

$$\Rightarrow \frac{\overline{v_{n,in}^2}}{\Delta f}(M_1, R_D) = 4kT \left[\frac{\gamma_1}{g_{m1}} + \frac{1}{g_{m1}^2 R_D} \right]$$

noise of M_2 ?

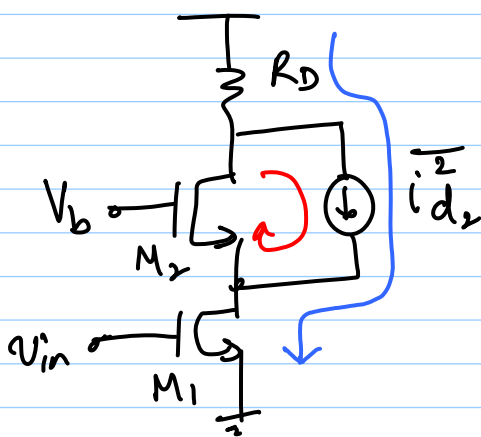


$$Z_{in1} \approx \frac{1}{g_{m2}}$$

$$Z_{in2} = r_{ds1}$$

Most of $\overline{i_{d2}^2}$ flows through M_2

$\Rightarrow \overline{v_{n,out}^2}(M_2)$ (and therefore $\overline{v_{n,in}^2}(M_1)$) are very very small

another way to look at it:

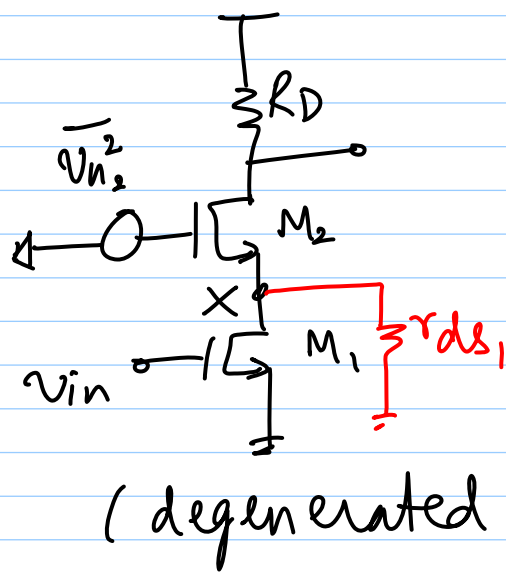


Effective transconductance
of M_2

$$= \frac{g_{m2}}{1 + g_{m2} \underline{r_{ds1}}}$$

= very very small

(degenerated with large resistance)

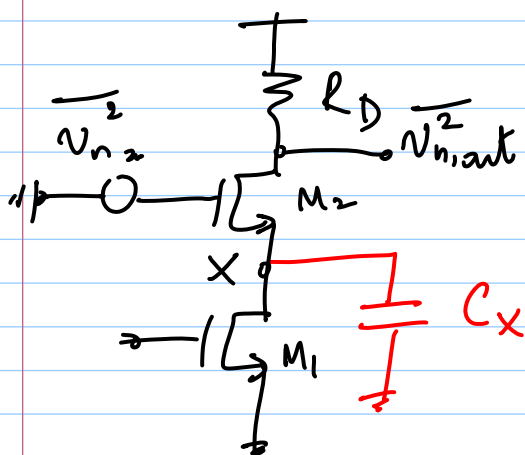

(a) high freq., C_x becomes prominent



$$G_{m2} = \frac{g_{m2}}{1 + g_{m2} \left(\frac{1}{j\omega C_x} \right)}$$

$$= \frac{1}{\frac{1}{g_{m2}} + \frac{1}{j\omega C_x}}$$

$$\frac{\overline{v_{n,out}^2}}{\overline{v_{n2}^2}} \approx \frac{R_D^2}{\left(\frac{1}{g_{m2}} \right)^2 + \left(\frac{1}{\omega C_x} \right)^2}$$


i.e. $\overline{v_{n,out}^2} \uparrow$

Differential Pairs

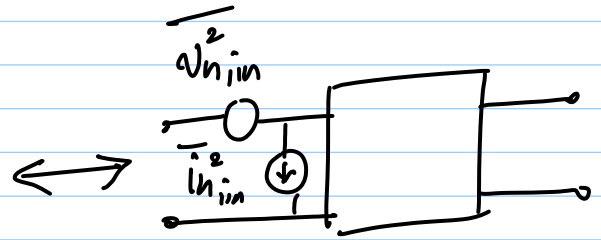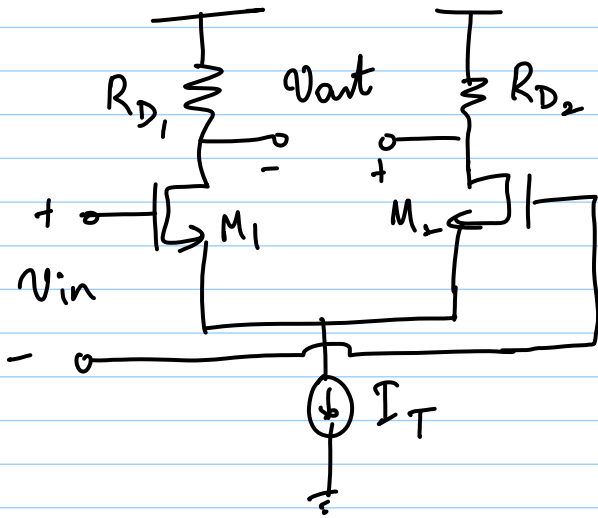

* $\overline{id_1^2}$ & $\overline{id_2^2}$ are uncorrelated

→ cannot use half-circuit concepts!

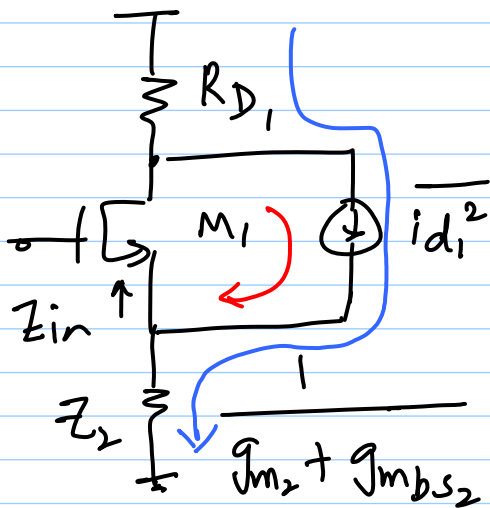

$$Z_{in} = \frac{1}{g_{m1} + g_{mbs1}}$$

⇒ $\frac{\overline{id_1}}{2}$ flows through M_1 & R_{D1}

* $\frac{\overline{id_1}}{2}$ flowing into Z_2 flows into R_{D2}

$$\overline{v_{n,out}(M_1)} = \frac{\overline{id_1}}{2} \cdot R_{D1} + \frac{\overline{id_1}}{2} R_{D2}$$

(uncorrelated, so currents add)

$$\therefore \overline{v_{n,out}^2} (M_1) = \overline{i_{d_1}^2} \cdot R_D^2$$

$$\begin{aligned} \therefore \overline{v_{n,out}^2} &= (\overline{i_{d_1}^2} + \overline{i_{d_2}^2}) R_D^2 + 2(4kTR_D) \\ &= 8kT(\gamma g_{m_{1,2}} R_D^2 + R_D) \end{aligned}$$

$$|a_{vd}|^2 = g_m^2 R_D^2$$

$$\Rightarrow \overline{v_{n,in}^2} = 8kT \left(\frac{\gamma}{g_{m_{1,2}}} + \frac{1}{g_{m_{1,2}}^2 R_D} \right)$$

$$= 2 \overline{v_{n,in,CS}^2}$$

$$\therefore \overline{v_{n,in}} = \sqrt{2} \overline{v_{n,in,CS}} \quad \left(\begin{array}{l} 2 \times \text{devices,} \\ \text{uncorrelated noise} \end{array} \right)$$

How about noise from I_T ? (call it $\overline{i_n}$)

1) $v_{in} = 0$ (no diff. input)

$\overline{i_n}$ (noise) divides equally between diff paths $\Rightarrow$ Common-mode noise only

2) Δv_{in}

$$\Delta I_{D_1} - \Delta I_{D_2} = g_m \Delta v_{in}$$


$$= \sqrt{2 \mu C_{ox} \left(\frac{W}{L} \right) \left(\frac{I_T + \overline{i_n}}{2} \right)} \cdot \Delta v_{in}$$

$$\approx \sqrt{2\mu \ln\left(\frac{W}{L}\right) \left(\frac{I_T}{2}\right) \left(1 + \frac{\bar{i}_n}{2I_T}\right)} \Delta v_{in}$$


$$= g_{m_0} \Delta v_{in} \left(1 + \frac{\bar{i}_n}{2I_T}\right)$$

$\Rightarrow$ diff. noise @ output
 $\rightarrow$ this effect is usually negligible
 (multiplied by Δv_{in})

Cascode

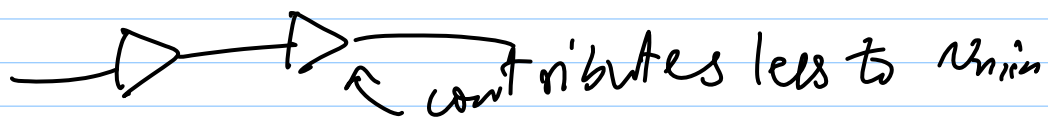

Noise scaling :

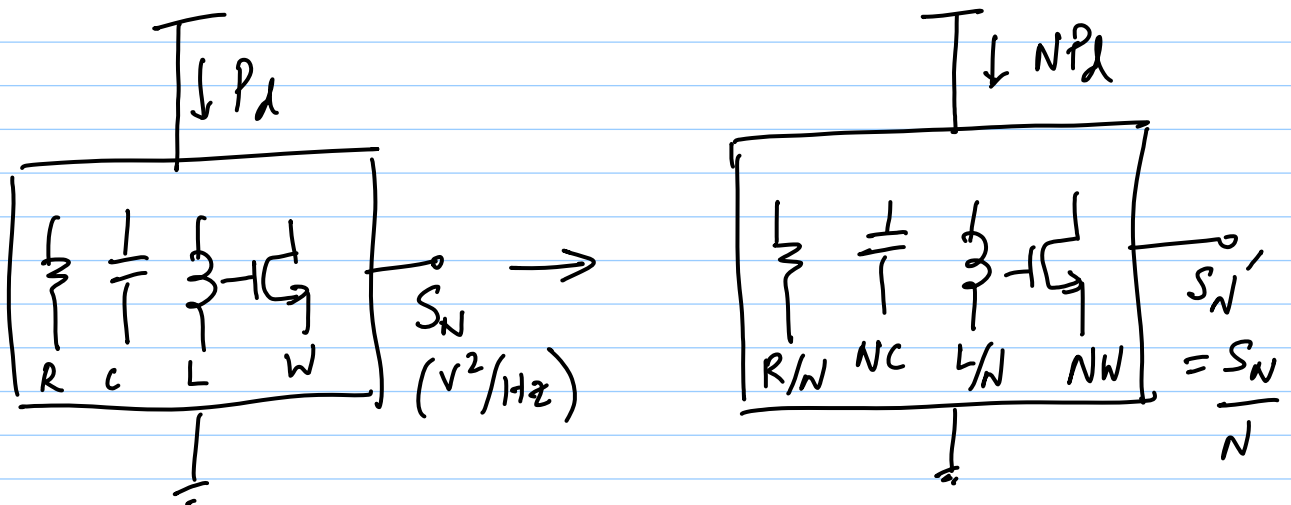

Move on noise when we get to opamps!


Mismatch

Systematic

Random

Systematic mismatch:

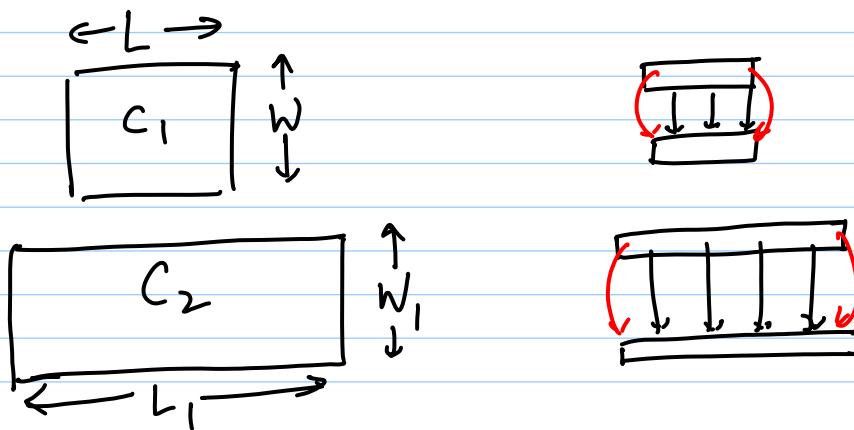Say you want cap ratio $\frac{C_2}{C_1} = \frac{2}{1}$



$$C = C_{\text{Area}} \cdot WL + C_{\text{Fringe}} (2W + 2L)$$

$$C_1 \quad \boxed{\text{DUM}} \quad \boxed{\text{Unit}} \quad \boxed{\text{DUM}}$$

$$C_2 \quad \boxed{\text{DUM}} \quad \boxed{\text{Unit}} \quad \boxed{\text{Unit}} \quad \boxed{\text{DUM}} \quad C_2 = 2C_1$$


You can achieve fractional ratios like $4/3$ etc.

resistors :

$$\frac{R_2}{R_1} = \frac{2}{1}$$

* Process directionality R
due to temp, mask, pressure
etc.
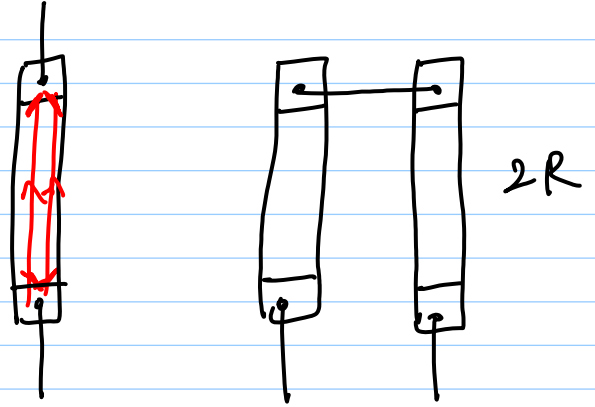
$$R = 2R_{\text{end}} + R_{\text{intrinsic}}$$



General idea : (to reduce systematic mism.)

- * use identical units (different numbers)
- * use dummy devices to create identical surroundings
- * same orientation