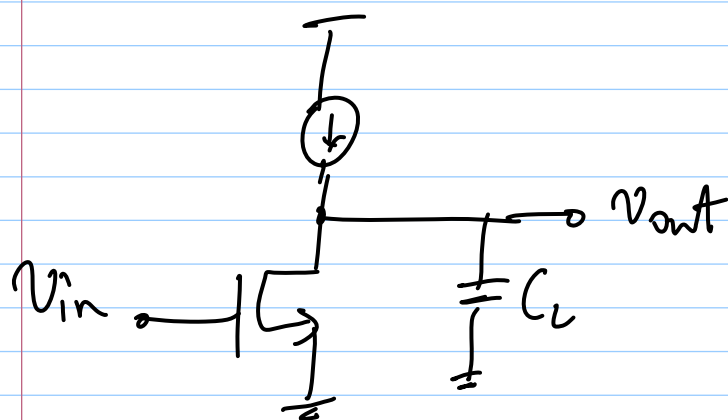


3-2-12

Lec 13


Freq. response

C.S. amp:



$v_{bs} = 0 \Rightarrow$ no effect from g_{mb} & C_{sb}

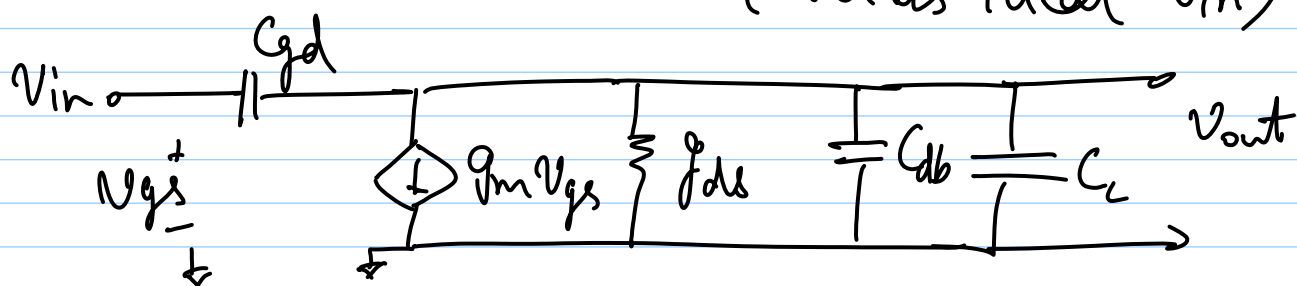neglect C_{gs} , C_{gb}
(across ideal V_{in})



$$H(s) = \frac{V_{out}(s)}{V_{in}(s)}$$

$$= \frac{g_m}{I_{ds}} \frac{(1 - sC_{gd}/g_m)}{1 + \frac{s(C_{gd} + C_{db} + C_L)}{I_{ds}}}$$


(low-freq. gain)

$$\omega_z = \frac{g_m}{C_{gd}}$$

RHP zero

$$\omega_p = - \frac{I_{ds}}{C_{gd} + C_{db} + C_L}$$

LHP pole

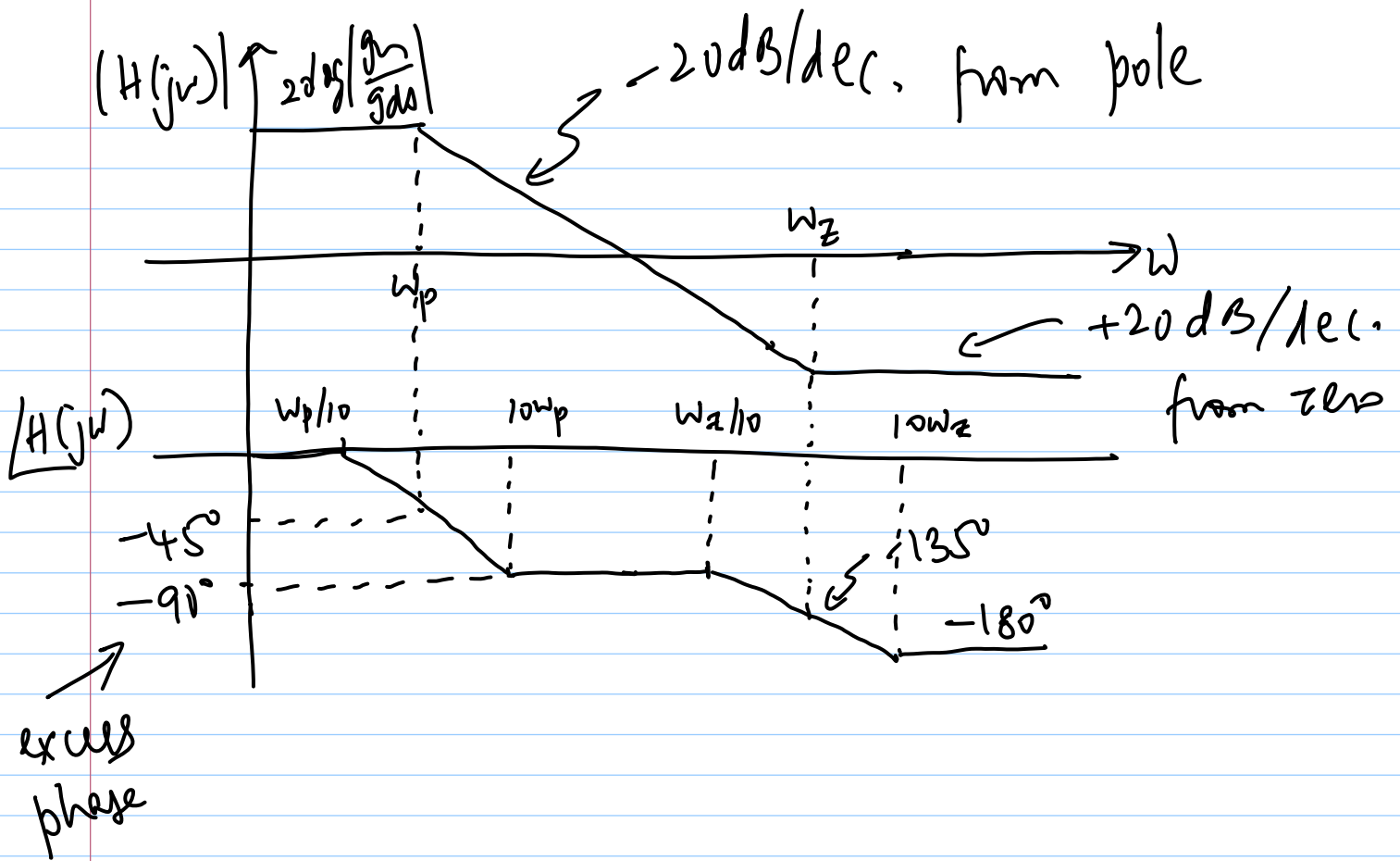


* LHP poles: (approx) every node in signal path


$$w_{pi} = \frac{g_i}{C_i} = \frac{1}{R_i C_i} \left[\begin{matrix} g_i \\ R_i \\ C_i \end{matrix} \right] @ \text{ node } i$$

$\rightarrow$ high impedance node $\equiv$ low - freq. pole and vice versa

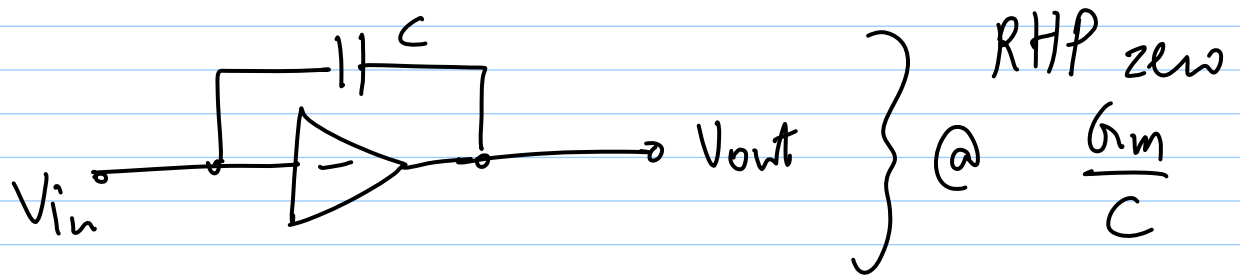* RHP zero: occurs if there is a capacitive path from input to output




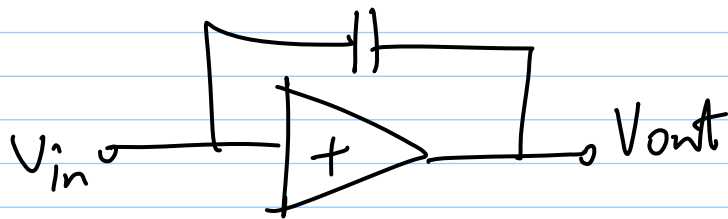g_m = effective transconductance between V_{in} and V_{out}





$\Rightarrow$ LHP zero @ $\frac{g_m}{C}$

Source follower

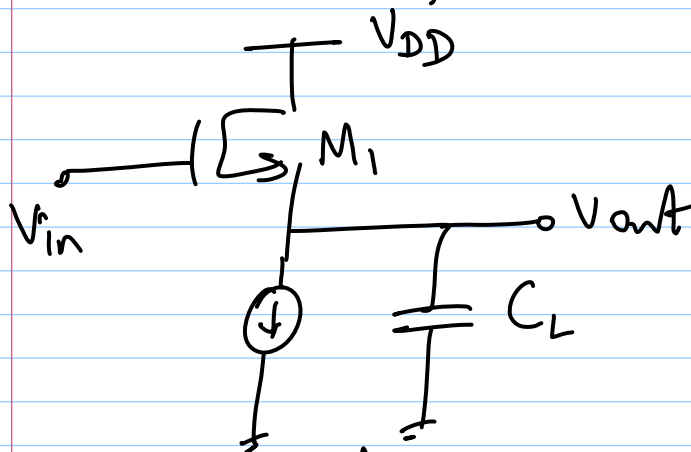

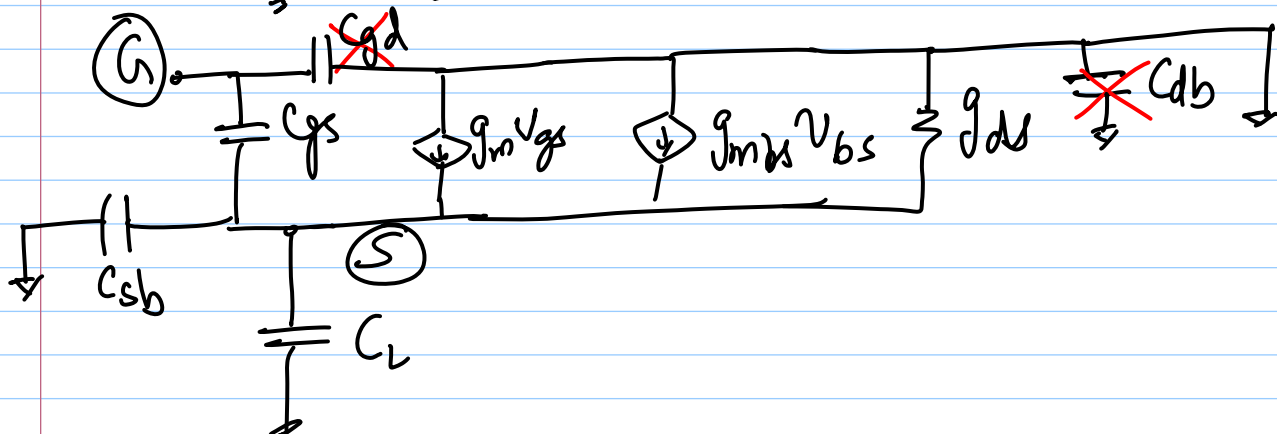* neglect C_{db} (shared)
* neglect C_{gd} (V_{in})



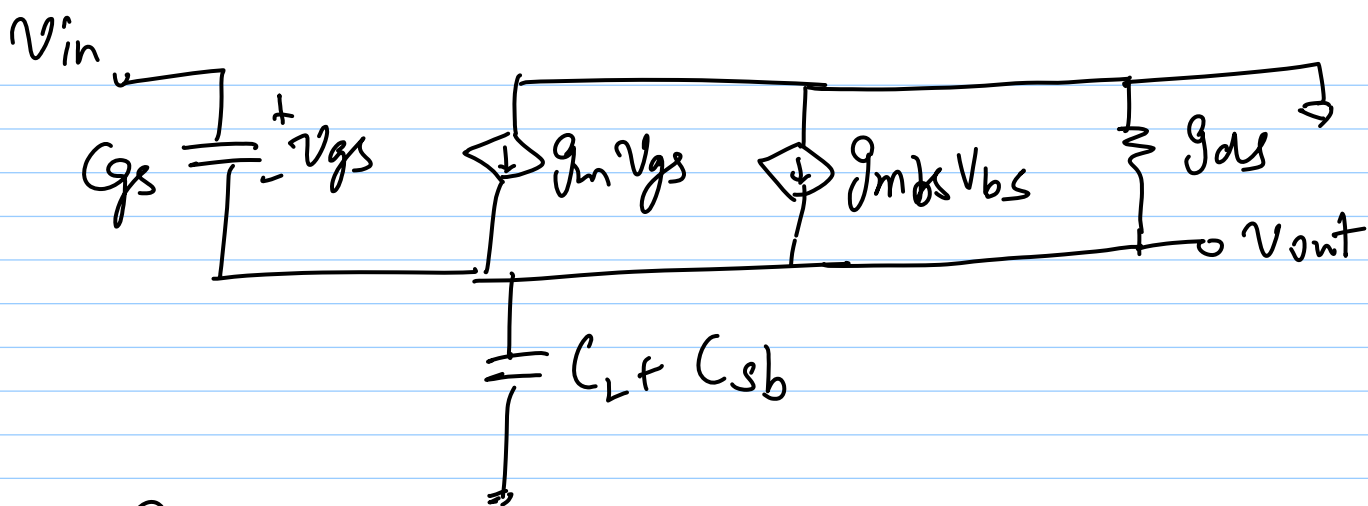

KCL @ S

$$sC_{gs}(V_{in} - V_{out}) + g_m(V_{in} - V_{out}) + g_{mbs}(-V_{out}) + g_{ds}(-V_{out}) = s(C_L + C_{sb}) \cdot V_{out}$$

$$\begin{aligned} \frac{V_{out}}{V_{in}}(s) &= \frac{g_m + sC_{gs}}{g_m + g_{mbs} + g_{ds} + s(C_{gs} + C_{sb} + C_L)} \\ &= \frac{g_m}{g_m + g_{mbs} + g_{ds}} \cdot \frac{(1 + sC_{gs}/g_m)}{\left[1 + \frac{s(C_{gs} + C_{sb} + C_L)}{g_m + g_{mbs} + g_{ds}}\right]} \end{aligned}$$



$$\text{LHP zero: } \omega_z = -\frac{g_m}{C_{gs}}$$

LHP pole :


$$\omega_p = \frac{-(g_m + g_{mbs} + g_{ds})}{(C_{gs} + C_{sb} + C_L)} \approx \frac{-g_m}{C_{gs} + C_{sb} + C_L}$$

Note that since $g_m \gg g_{mbs}, g_{ds}$

$$|\omega_p| < |\omega_z|$$

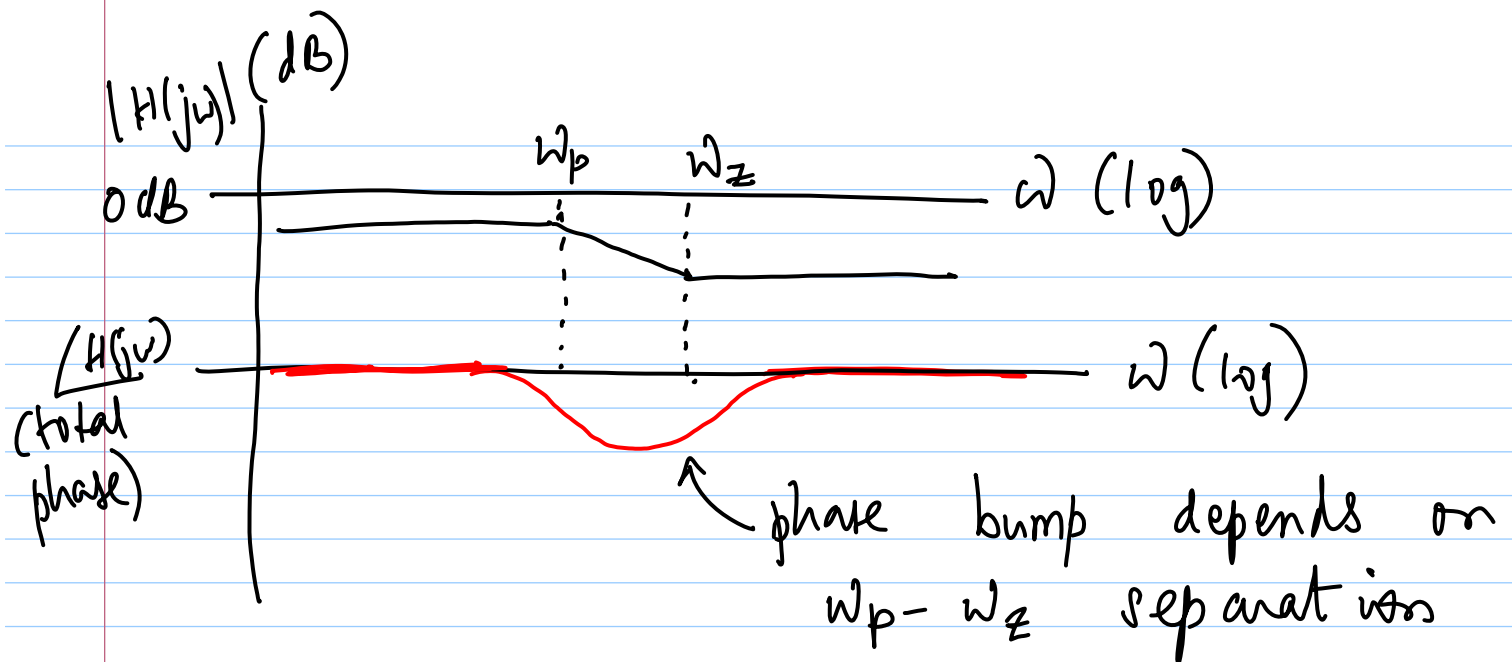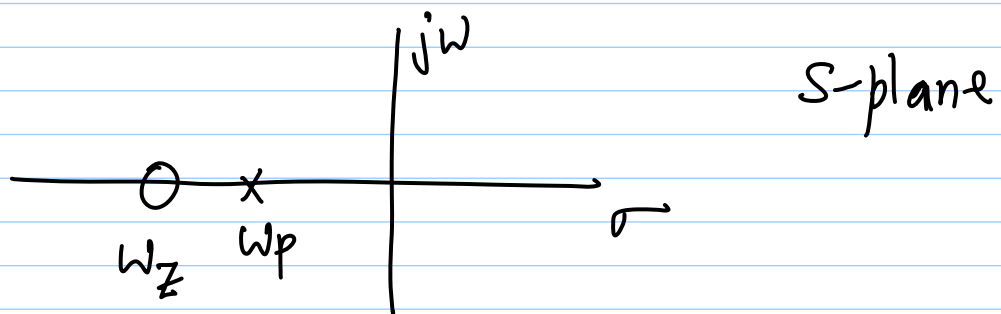

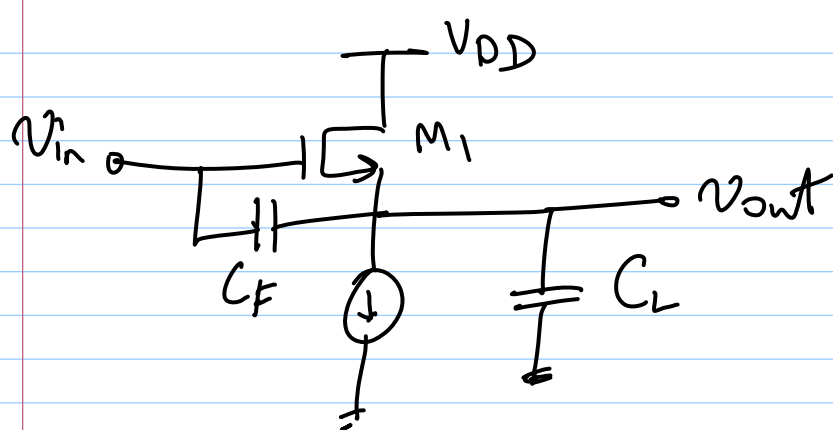* If we increase C_{gs} , ω_z moves more than ω_p
→ increase C_{gs} so that $\omega_p = \omega_z$!
⇒ Pole - zero cancellation



$$C_{gs}' \rightarrow C_{gs} + C_F$$


$$\omega_p = - \frac{(g_m + g_{mbs} + g_{ds})}{C_{gs} + C_F + C_{sb} + C_L}$$

$$\omega_z = \frac{-g_m}{C_{gs} + C_F}$$

set $\omega_p = \omega_z$

$$\Rightarrow \frac{g_m + g_{mbs} + g_{ds}}{C_{gs} + C_F + C_{sb} + C_L} = \frac{g_m}{C_{gs} + C_F}$$
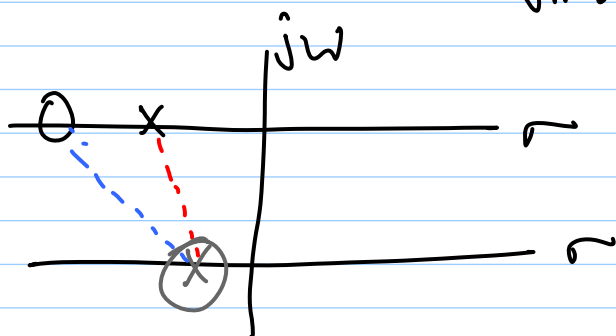
$$\Rightarrow C_F = \frac{g_m}{g_{mbs} + g_{ds}} (C_{sb} + C_L) - C_{gs}$$



why?

$\Rightarrow$ broad band response!

Issues:

1) C_F is large $\sim 10 C_L$


$$\left\{ \text{note } C_F = \frac{g_m}{g_{mbs} + g_{ds}} \times \dots \right\}$$

2) If $\omega_p \neq \omega_z$ (inexact cancellation)

$\Rightarrow$ pole-zero doublet

$\Rightarrow$ very slowly settling transient response

Cascode freq. response

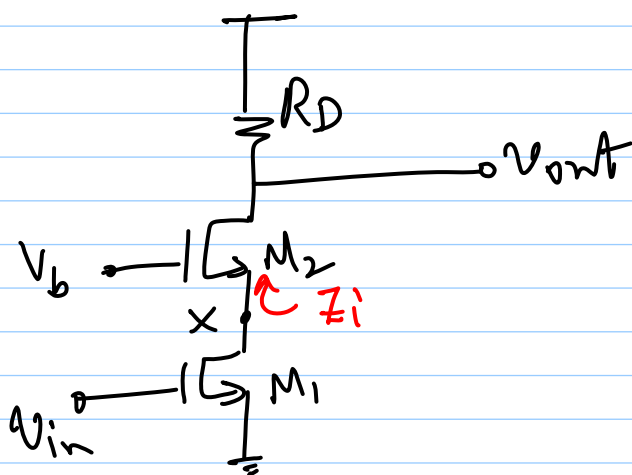

$$\frac{v_{out}}{v_{in}} \approx -g_m R_D$$

$\Rightarrow$ same as normal CS amp.

$$Z_i \approx \frac{1}{g_{m2}} \quad \text{if } r_{ds2} \text{ is large}$$

If same (W/L) $\Rightarrow g_{m1} = g_{m2}$

$$\frac{v_x}{v_{in}} \approx \frac{g_{m1}}{g_{m2}} \approx 1$$

⇒ very little miller effect

If r_{ds2} is finite,

$$Z_i \approx \frac{1}{g_{m2}} + \frac{1}{g_{m2}} \cdot \frac{R_D}{r_{ds2}}$$

e.g. R_D is derived from a cascode current mirror

$$\Rightarrow R_D \gg r_{ds2}$$

$$\Rightarrow Z_i \gg \frac{1}{g_{m2}}$$



$$\frac{v_x}{v_{in}} \gg 1, \text{ but still } < \frac{v_o}{v_{in}}$$

⇒ Miller effect with cascode is still lower than without

* Miller effect can be reduced further by using active cascode

* Cascode has low reverse-transmission

Multi-stage freq. response

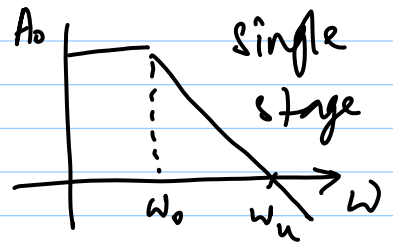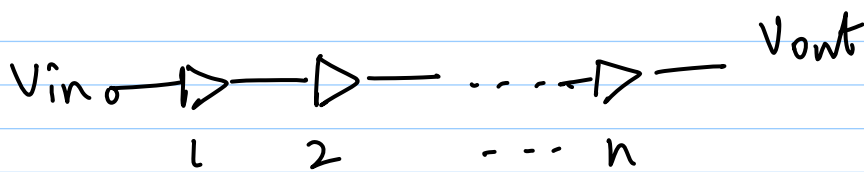

* All n amplifiers are identical

* Each stage has single-pole response

$$A(s) = \frac{A_0}{1 + s/\omega_0}$$

Overall cascade TF is

$$H(s) = \left(\frac{A_0}{1 + s/\omega_0} \right)^n$$

* find -3 dB BW of the cascade (ω_{on}):
at $\omega = \omega_{on}$, $|H(j\omega)| = \frac{1}{\sqrt{2}} |H(0)|$

$$\Rightarrow \left[\frac{A_0}{\sqrt{1 + \left(\frac{\omega_{on}}{\omega_0}\right)^2}} \right]^n = \frac{1}{\sqrt{2}} A_0^n$$

$$\Rightarrow \boxed{\omega_{on} = \omega_0 \sqrt{2^{1/n} - 1}}$$

BW shrinkage

Recall that $A_0 \omega_0 = \omega_u \Rightarrow \boxed{\omega_{on} = \frac{\omega_u}{A_0} \sqrt{2^{1/n} - 1}}$