

7-2-12

Lec - 14

Optimum gain per stage

* Given total gain $A_{tot.}$, we want to find optimal n & maximise BW

$$A_0^n = A_{tot.} \Rightarrow A_0 = A_{tot.}^{1/n}$$

$$W_{on} = \frac{W_u}{A_{tot.}^{1/n}} \sqrt{2^{1/n} - 1}$$

apply $\frac{dW_{on}}{dn} = 0$

after some algebra:

$$n_{opt.} = \frac{\ln 2}{\ln \left\{ 1 + \frac{\ln 2}{2 \ln A_{tot.}} \right\}}$$

for large $A_{tot.}$,

$$\ln \left\{ 1 + \frac{\ln 2}{2 \ln A_{tot.}} \right\} \approx \frac{\ln 2}{2 \ln A_{tot.}}$$

$$\ln(1+x) \approx x \text{ for } x \ll 1$$

$$\Rightarrow \boxed{n_{opt.} \approx 2 \ln A_{tot.}}$$

optimum gain / stage:

$$A_{0, \text{opt.}} = (A_{\text{tot.}})^{1/n_{\text{opt.}}} = \exp \left\{ \frac{1}{n_{\text{opt.}}} \ln A_{\text{tot.}} \right\}$$

$$\approx e^{1/2}$$

$$\boxed{A_{0, \text{opt.}} = \sqrt{e}}$$

optimum BW:


$$\omega_{0, \text{opt.}} = \frac{\omega_u}{A_{\text{tot.}}^{1/n_{\text{opt.}}}} \sqrt{2^{1/n_{\text{opt.}}} - 1}$$

$$\approx \frac{\omega_u}{\sqrt{e}} \left[\exp \left\{ \frac{1}{n_{\text{opt.}}} \ln 2 \right\} - 1 \right]^{1/2}$$

$$\boxed{\omega_{0, \text{opt.}} \approx \omega_u \sqrt{\frac{\ln 2}{2e \ln A_{\text{tot.}}}}}$$


Summary of freq. response

LHP zero:

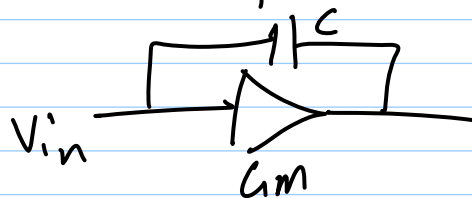


$$\left(-\frac{G_m}{C} \right)$$

RHP zero:

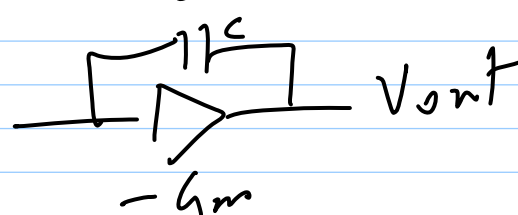

$$\left(\frac{G_m}{C} \right)$$


LHP pole:

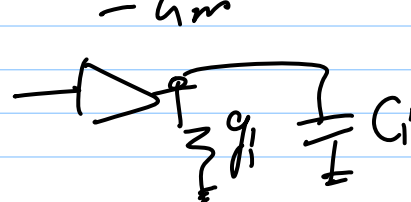


$$\left(-\frac{g_i}{C_i} \right)$$

not the only source of zeros

RHP pole

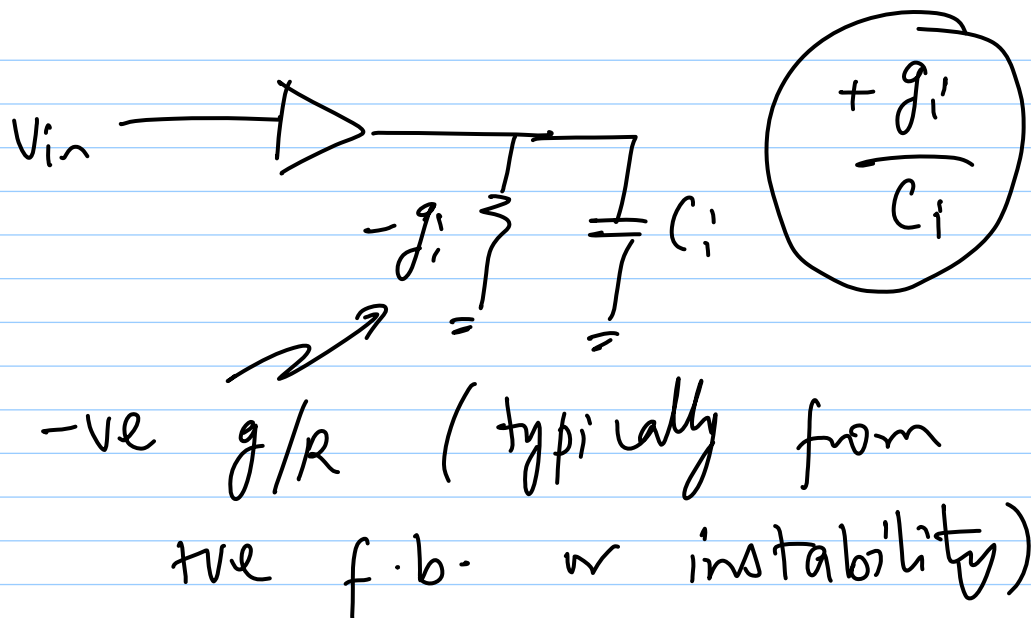

Zeros

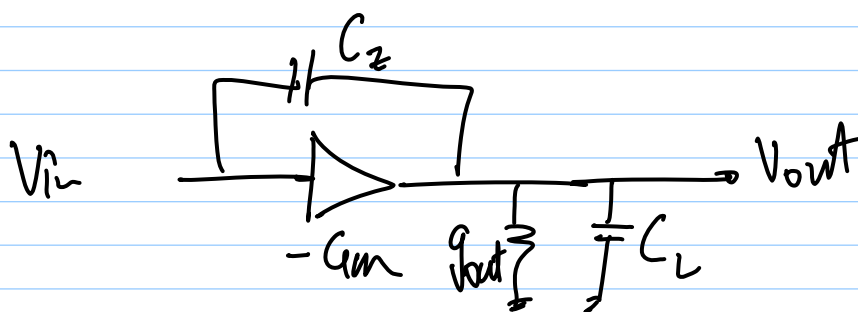

$$V_{out} = i_{out} Z_{out}$$

$$= \left\{ -G_m \cdot V_{in} + (V_{in} - V_{out}) \cdot s C_z \right\} R_{out}$$

$$Y_{out} V_{out} = (-G_m + s C_z) V_{in} - s C_z V_{out}$$


$$V_{out} [g_{out} + s(C_z + C_L)] = (-G_m + s C_z) V_{in}$$

$$\frac{V_{out}}{V_{in}} = \frac{-(G_m - s C_z)}{g_{out} + s(C_z + C_L)}$$

$$= -\frac{G_m}{g_{out}} \left[\frac{1 - s C_z / G_m}{1 + \frac{s(C_z + C_L)}{g_{out}}} \right]$$

* presence of zero is not always obvious

1)

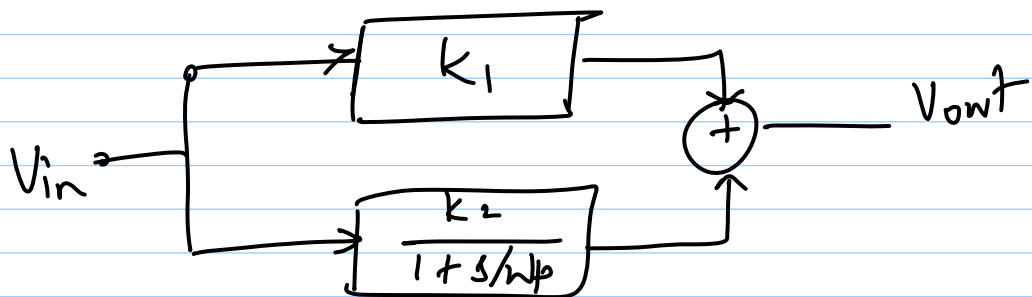

$$V_{out}(s) = k_1 V_{in}(s) + \frac{k_2}{1 + s/w_p} V_{in}(s)$$


$$\frac{V_{out}}{V_{in}}(s) = k_1 + \frac{k_2}{1 + s/w_p}$$

$$= \frac{(k_1 + k_2) + k_1 s/w_p}{1 + s/w_p}$$

$$= (k_1 + k_2) \cdot \frac{(1 + s/w_z)}{(1 + s/w_p)}$$

$$w_z = w_p \cdot \frac{(k_1 + k_2)}{k_1}$$

2)

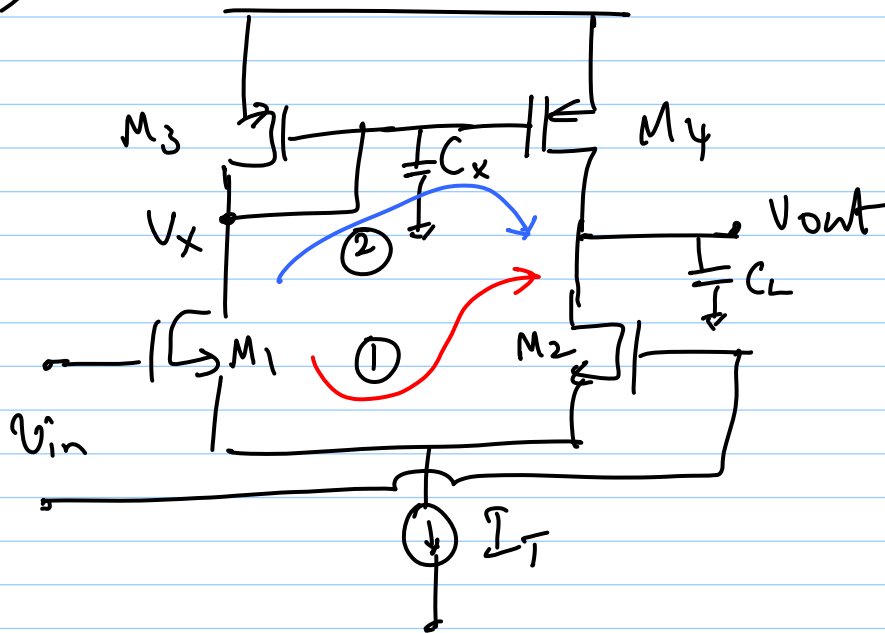

Read
Razavi;
Section 6.6

$$\omega_{p1} \approx - \frac{g_{ds1} + g_{ds3}}{C_L}$$

$$\omega_{p2} \approx - \frac{g_{m3}}{C_x}$$

$$\textcircled{1} : \frac{A_o}{1 + s/\omega_{p1}}$$

$$\textcircled{2} : \frac{A_o}{(1 + s/\omega_{p1})(1 + s/\omega_{p2})}$$


$$\Rightarrow A_{tot.}(s) = A_{\textcircled{1}} + A_{\textcircled{2}}$$

$$= \frac{A_0}{(1 + s/\omega_{p1})} \left[1 + \frac{1}{1 + \frac{s}{\omega_{p2}}} \right]$$


$$= \frac{A_0 (2 + s/\omega_{p2})}{(1 + s/\omega_{p1}) (1 + s/\omega_{p2})}$$

$$\omega_z = 2\omega_{p2}$$

Diff pairs

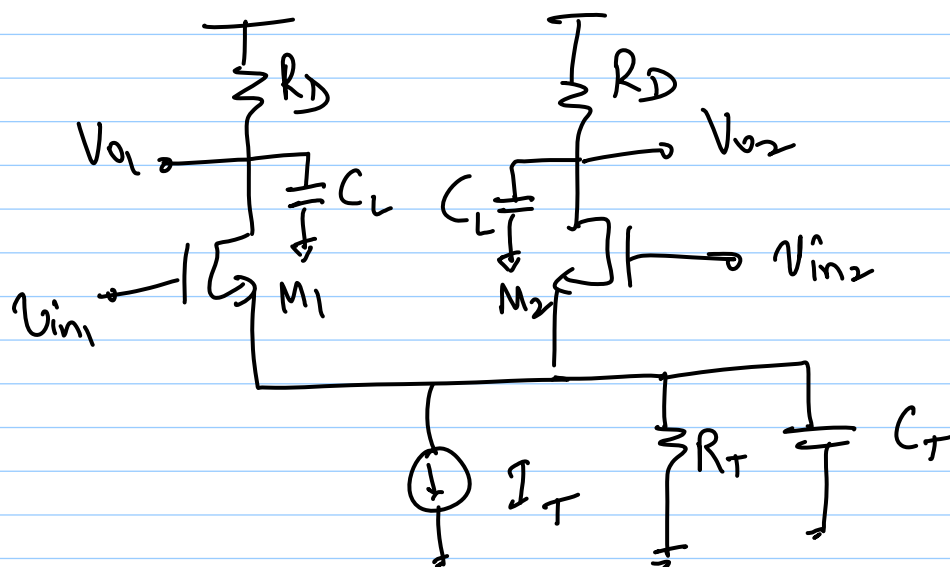

DM half ckt

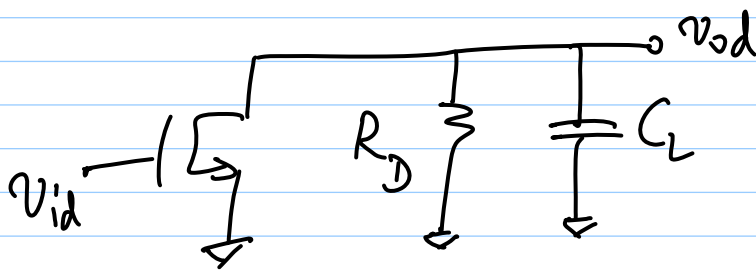


(neglect device caps for simplicity)

$$g_{out} = g_D + g_{ds}$$

$$a_{dm}(s) = \frac{-g_m}{g_{out}} \cdot \frac{1}{1 + \frac{sC_L}{g_{out}}}$$

in reality C_{gd} causes a zero
($|w_z| \gg |w_p|$ here)

CM half ckt

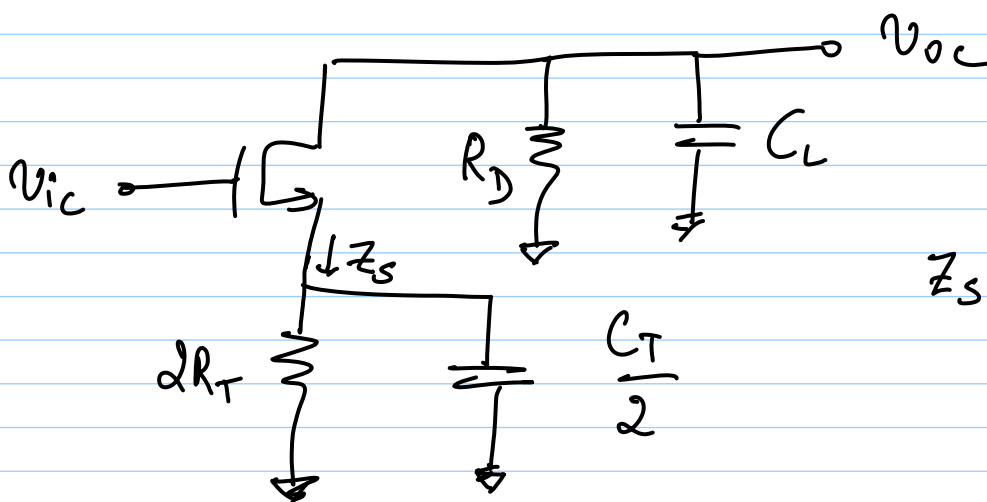

$$Z_S = \frac{2R_T / (sC_T/2)}{2R_T + \frac{2}{sC_T}} = \frac{2R_T}{1 + sC_T R_T}$$

$$a_{cm}(s) = - \underbrace{\left(\frac{g_m}{1 + g_m Z_S} \right)}_{A_{mc}} \cdot \frac{1}{g_{out}} \cdot \frac{1}{1 + \frac{sC_L}{g_{out}}}$$

$w_p \rightarrow$

$$\begin{aligned}
 A_{m_c} &= \frac{g_m}{1 + g_m z_s} \\
 &= \frac{g_m}{1 + g_m \cdot \frac{(2R_T)}{(1 + s C_T R_T)}} \\
 &= \frac{g_m (1 + s C_T R_T)}{(1 + 2g_m R_T) + s C_T R_T}
 \end{aligned}$$

$\swarrow \omega_z$
 $\nwarrow \omega_{p2}$

$$A_{cm}(s) = \left(\frac{g_m}{1 + 2g_m R_T} \right) \cdot \left(\frac{1}{g_D + g_{Ds}} \right) \cdot \frac{(1 + s/\omega_z)}{(1 + s/\omega_{p1}) (1 + \frac{s}{\omega_{p2}})}$$

$$\omega_z = - \frac{1}{R_T C_T} \quad \text{LHP zero}$$

$$\omega_{p1} = - \frac{(g_{Ds} + g_D)}{C_L} \quad \text{LHP pole}$$


$$\omega_{p2} = - \frac{1 + 2 g_m R_T}{R_T C_T}$$

LHP pole

$$\approx - \frac{g_m}{(C_T/2)} \quad \text{if } 2 g_m R_T \gg 1$$

(cap in signal path)

Another way to look at it: (approx.)

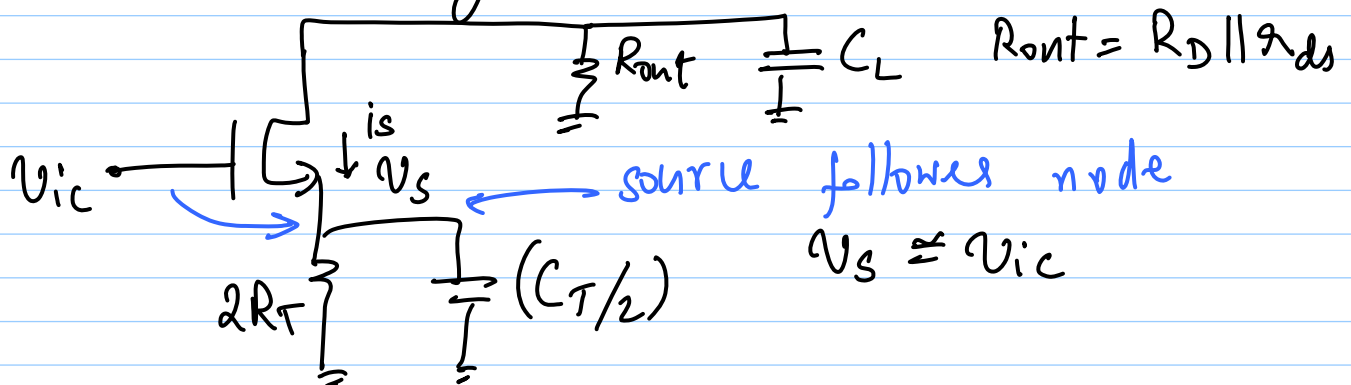

$$\Rightarrow i_S = V_S \cdot Y_S$$

$$= V_{IC} \cdot \left[\frac{1}{2R_T} + \frac{s C_T}{2} \right]$$

$$V_{OC} = -i_S \cdot Z_{out} = -Z_{out} \cdot \left(\frac{1}{2R_T} + \frac{s C_T}{2} \right) V_{IC}$$

$$A_{cm}(s) = \frac{V_{ol}}{V_{ic}}$$


$$= - \left(\frac{R_{out}}{1 + s C_L R_{out}} \right) \left(\frac{1}{2 R_T} + \frac{s C_T}{2} \right)$$

$$= \left(\frac{-R_{out}}{2 R_T} \right) \left(\frac{1}{1 + s C_L R_{out}} \right) \cdot (1 + s C_T R_T)$$

ω_{p1}

ω_z

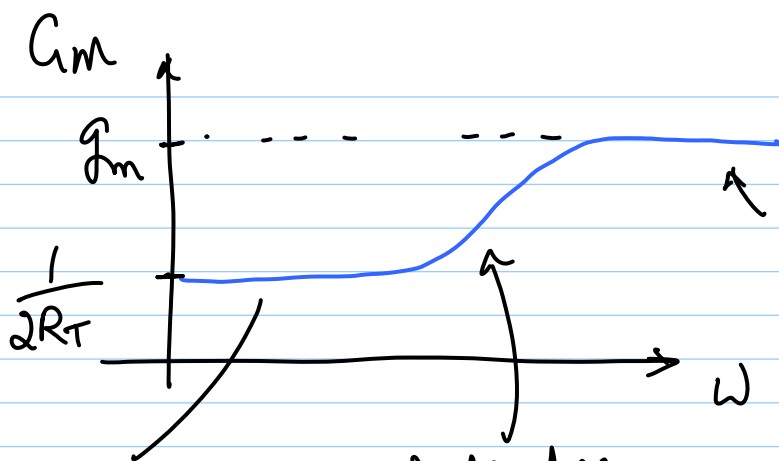$V_s = V_{ic} \rightarrow$ caused us to neglect ω_{p2}



assuming

$$2 g_m R_T \gg 1$$

$$\Rightarrow g_m \gg \frac{1}{2 R_T}$$

indicates presence of zero

1) increase in gain $\Rightarrow$ zero

2) @ ω_z , $V_{out} = 0 \rightarrow$ use this to find out ω_z

CMRR = Common-mode Rejection ratio

$$\equiv 20 \log \left(\frac{|a_{dm}|}{|a_{cm}|} \right) \text{ in dB}$$

(a) low freq.:

$$\begin{aligned} \text{CMRR} &= 20 \log \frac{(g_m/g_{out})}{(R_{out}/2R_T)} \\ &= 20 \log (2g_m R_T) \end{aligned}$$

