


8-2-12

Lec 15

Feedback

Why?

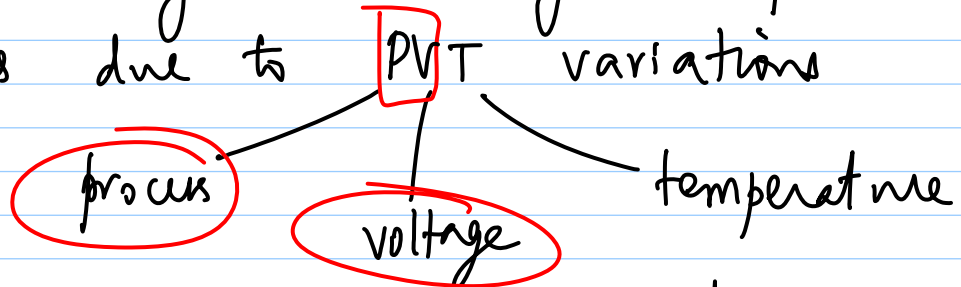* stabilise gain etc. against parameter changes due to PVT variations



* modify input & output impedances

* reduction in distortion


* Increase -3dB BW of ckt's

disadvantages of FB:

* gain of ckt is reduced

→ extra stages = area, power

* stability issues

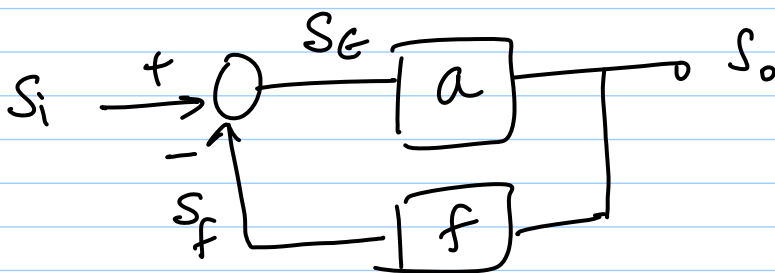

note the
signs of the
summer inputs

$$S_o = a S_e$$

$$S_f = f \cdot S_o$$

$$S_e = S_i - f S_o$$

$$\Rightarrow S_o = a S_i - a f S_o$$

$$\Rightarrow \frac{S_o}{S_i} = A = \frac{a}{1 + a f}$$

Closed loop gain = A

Loop gain = $T = a f$ $\left\{ \begin{array}{l} = \text{total} \\ \text{gain around} \\ \text{f.b. loop} \end{array} \right\}$

$$\text{If } T \gg 1, A \approx \frac{1}{f}$$

$f \rightarrow$ often based on stable,
passive elements
 $\rightarrow$ well-defined

$$S_e = S_i - f S_o = S_i - \frac{f a S_i}{1 + a f}$$

$$\frac{S_e}{S_i} = \frac{1}{1 + a f}$$

$$\frac{S_f}{S_i} = \frac{a f}{1 + a f} \quad \left. \vphantom{\frac{S_f}{S_i}} \right\} \text{If } T \gg 1, S_f \approx S_i$$

$$\Rightarrow S_o = \frac{1}{f} S_f = \frac{S_i}{f}$$

$|f| < 1 \Rightarrow S_o = \text{amplified replica of } S_i$

Gain sensitivity

$$\frac{dA}{da} = \frac{(1+a_f) - a_f}{(1+a_f)^2} = \frac{1}{(1+a_f)^2}$$

$$\Rightarrow \delta A = \frac{\delta a}{(1+a_f)^2}$$


$$\begin{aligned} \frac{\delta A}{A} &= \frac{1+a_f}{a} \cdot \frac{\delta a}{(1+a_f)^2} \\ &= \frac{(\delta a/a)}{(1+a_f)} \end{aligned}$$

$\Rightarrow$ fractional change in A is reduced by $(1+T)$

e.g. $T = 100$, $\delta a/a = 10\%$


$$\Rightarrow \frac{\delta A}{A} = 0.1\%$$

Effect on distortion

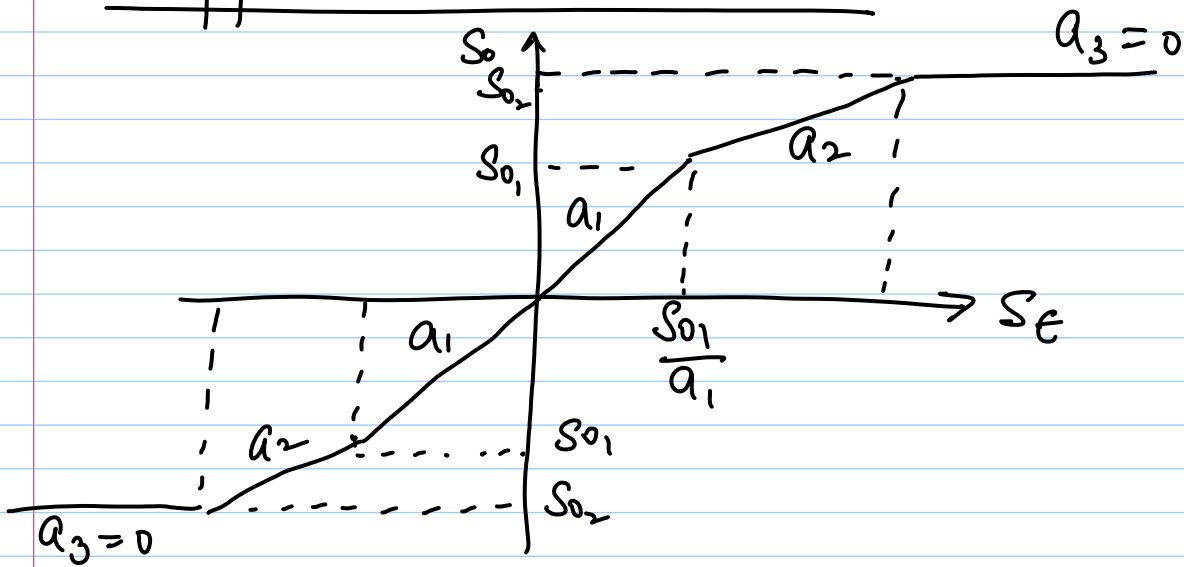

$$A_1 = \frac{a_1}{1 + a_1 f} \approx \frac{1}{f}$$
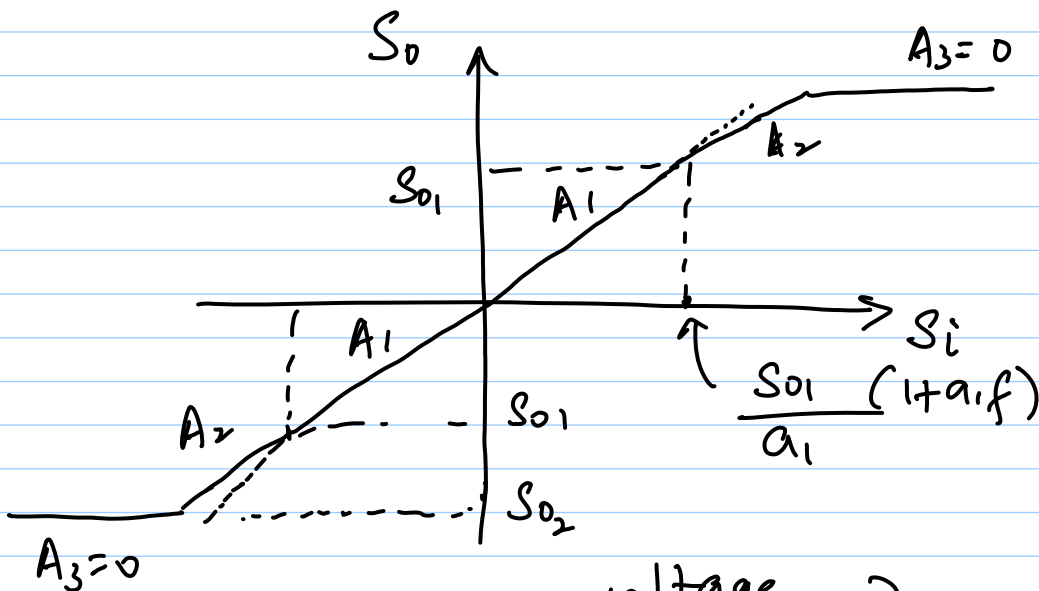
$$A_2 = \frac{a_2}{1 + a_2 f} \approx \frac{1}{f}$$



S_i — voltage
 S_i — current
 S_o — voltage
 S_o — current

four configs.

Effect on gain-BW


$$a(s) = \frac{a_0}{1 + s/\omega_{p1}} \quad (1\text{-pole})$$


$f =$ constant & freq. independent

$$\begin{aligned} A(s) &= \frac{a(s)}{1 + a(s) \cdot f} \\ &= \frac{a_0}{1 + a_0 f} \cdot \frac{1}{1 + \frac{s}{\omega_{p1}(1 + a_0 f)}} \end{aligned}$$

$$\Rightarrow A_0 = \frac{a_0}{1 + a_0 f}$$
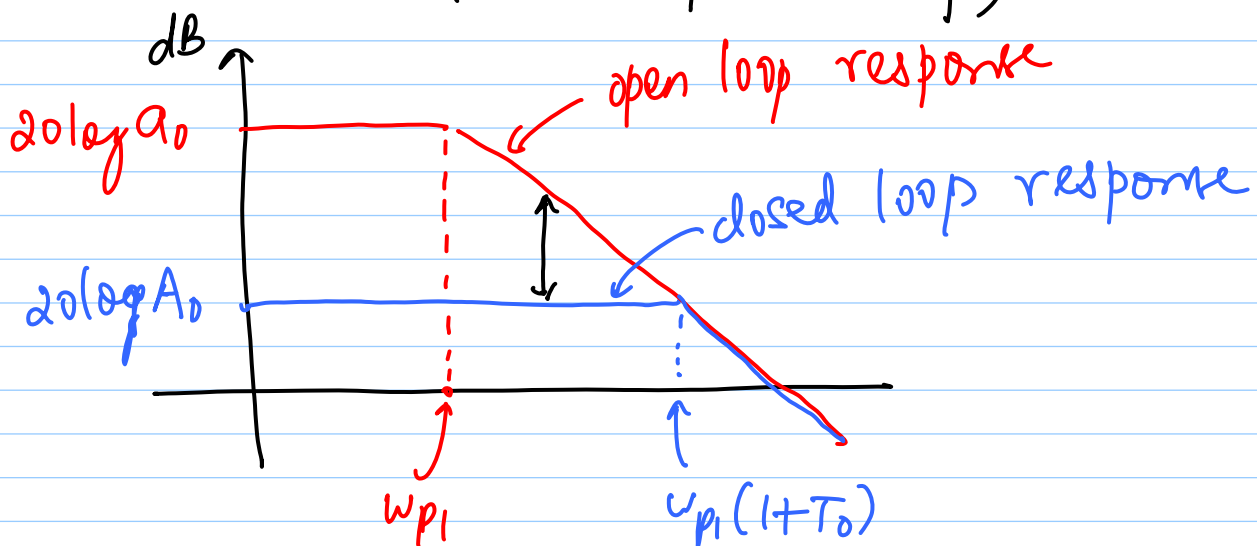
$$\omega_{s-dB} = \omega_{p1}(1 + a_0 f)$$




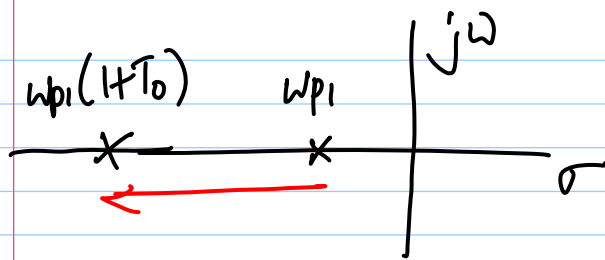

$$\textcircled{a} \omega_0 = \omega_{p1} (1 + A_0)$$

$$T(\omega) = 0 \text{ dB} = 1 \quad (\text{unity loop gain freq.})$$

↓ Series-shunt f.b.
(i/p) (o/p)

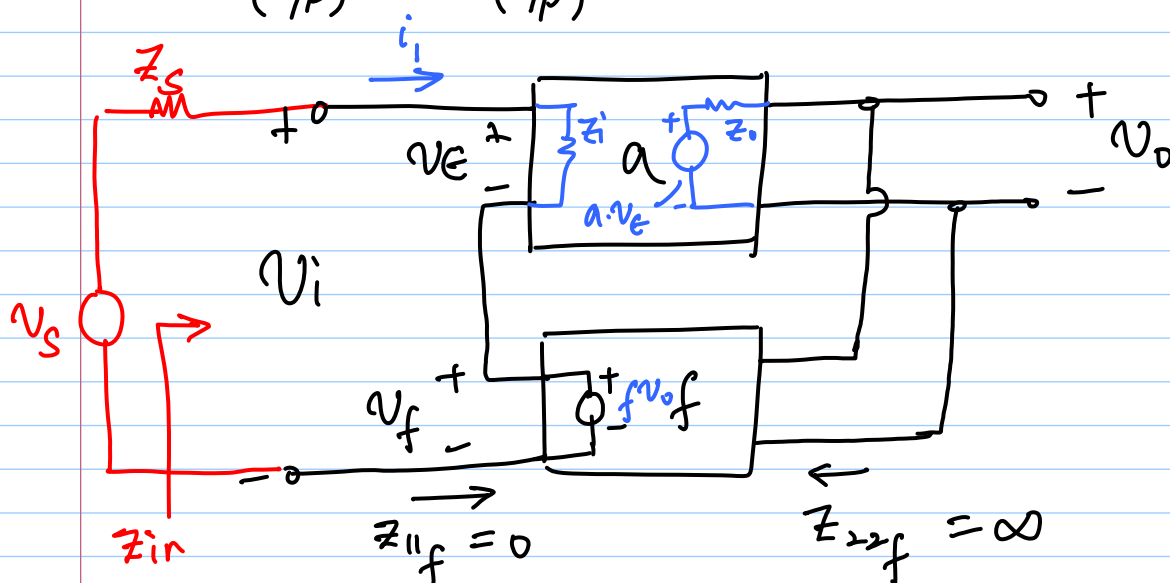

$$\frac{v_o}{v_i} = \frac{a}{1 + a_f} ; v_i = \frac{Z_{in}}{Z_{in} + Z_s} \cdot v_s$$

$$\Rightarrow \text{If } Z_s \sim Z_{in}$$

$$v_i = f(Z_{in})$$

↖ not very well-defined

$$\Rightarrow \frac{v_o}{v_i} \text{ will not be stabilised}$$

$\therefore$ ideal driving source is a voltage source (low impedance)

$$v_o = a v_e$$


$$v_i = v_e + f v_o$$

$$i_i = \frac{v_e}{Z_i} = \frac{v_i}{Z_i} \frac{1}{(1 + a_f)}$$

$$\Rightarrow Z_{in} = \frac{v_i}{i_i} = (1 + T) Z_i$$

* Series f.b. @ input always raises

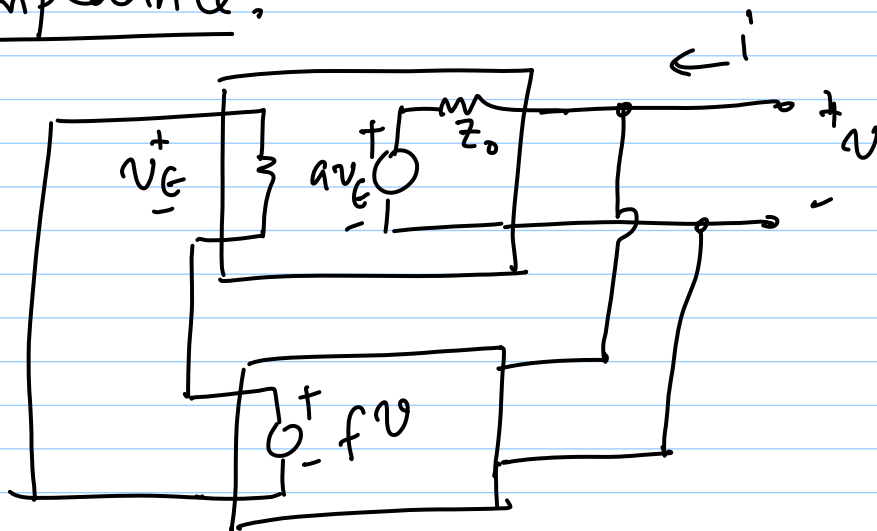the input impedance by $(1 + T)$
o/p impedance:



$$v_e + f v = 0$$

$$i = \frac{v - a v_e}{z_o}$$

$$= \frac{v + a f v}{z_o}$$

$$z_{out} = \frac{v}{i} = \frac{z_o}{1+T}$$

* Shunt f.b. always lowers output impedance by $(1+T)$

series-shunt f.b. $\Rightarrow$ good voltage amp

other types

II Shunt-shunt $\begin{pmatrix} \text{sense} = V \\ \text{f.b.} = I \end{pmatrix}$


III Shunt-series $\begin{pmatrix} \text{sense} = I \\ \text{f.b.} = I \end{pmatrix}$

IV Series-series $\begin{pmatrix} \text{sense} = I \\ \text{f.b.} = V \end{pmatrix}$

z_i, z_o etc. get modified appropriately

Effect of loading


e.g. Shunt-shunt

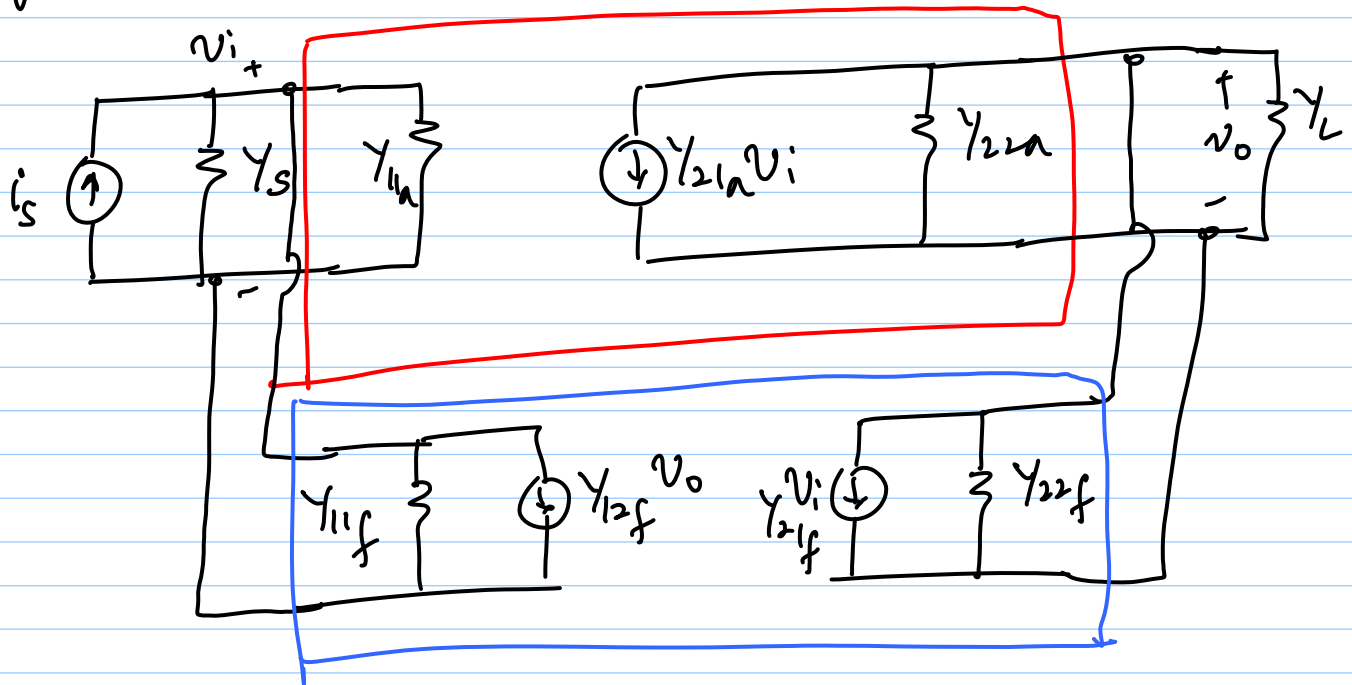

$$|Y_{21a}| \gg |Y_{21f}|$$



$$|Y_{12f}| \gg |Y_{12a}|$$

Re draw!

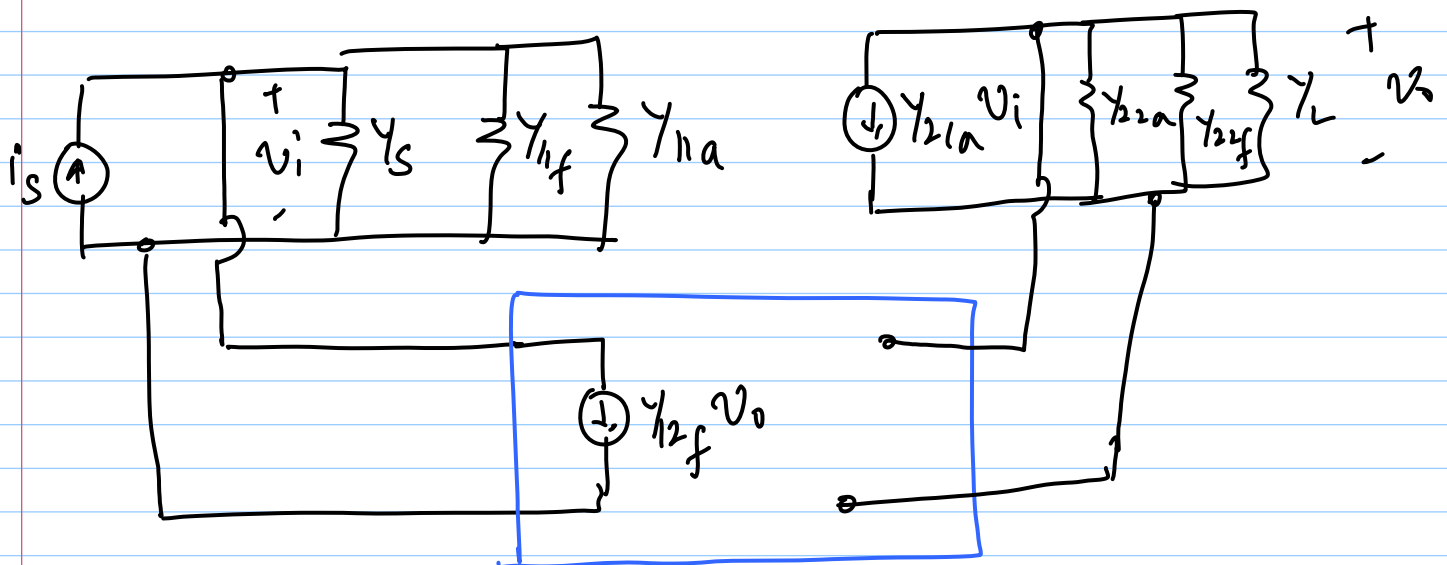


* Further analysis with y -param is not necessary

e.g.

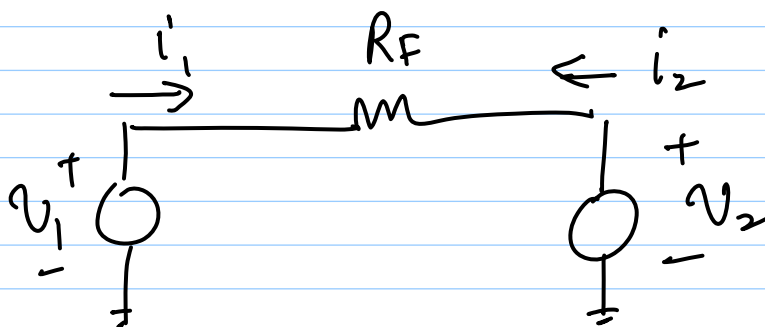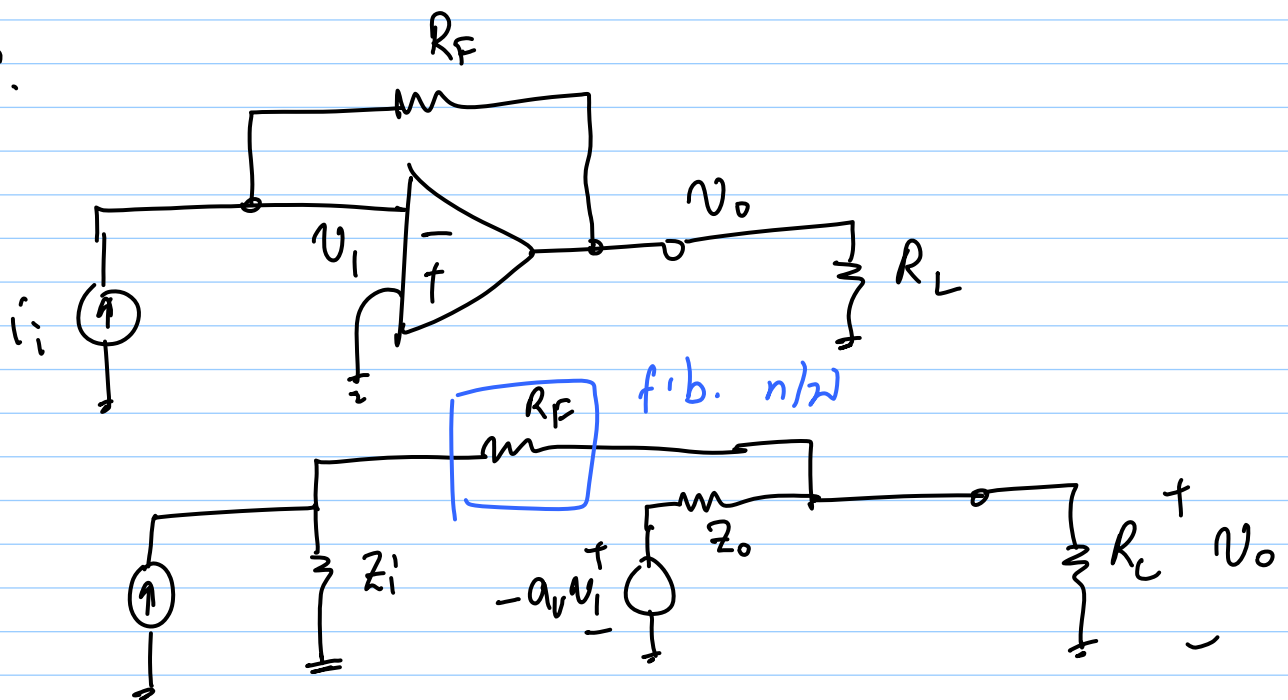
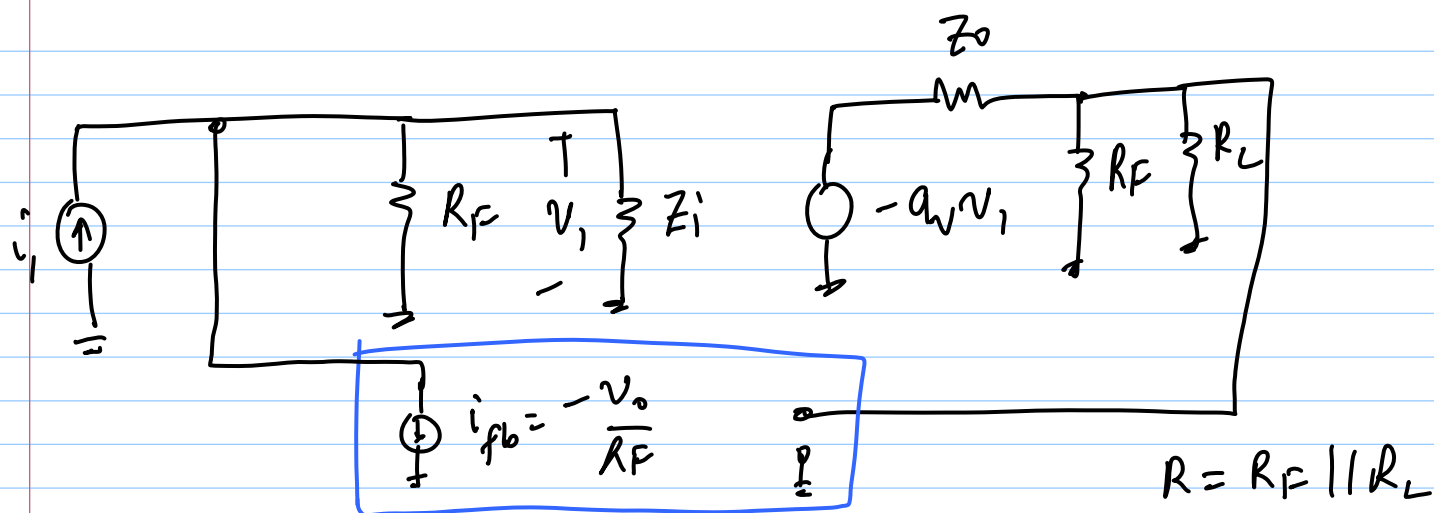
$$\left. \begin{aligned} Y_{11f} &= \frac{1}{R_F} \\ Y_{22f} &= \frac{1}{R_F} \\ Y_{12f} &= -\frac{1}{R_F} = f \end{aligned} \right\} \text{neglect } Y_{21f}$$



$$v_i = \frac{Z_i R_F}{Z_i + R_F} \cdot i_i$$

$$v_o = - \frac{R}{R + Z_o} \cdot a_v v_i$$

$$\frac{v_o}{i_i} = a = - \frac{R}{R + Z_o} \cdot a_v \cdot \frac{Z_i R_F}{Z_i + R_F}$$

impedances w/ γ_{12f} etc. are divided
by $(1+T)$ based on orig. theory