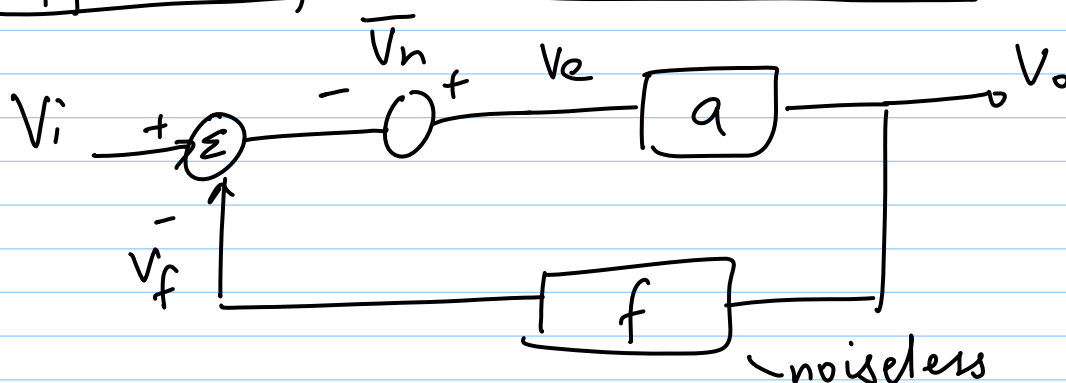


9-2-12

Lec 16


Note Title

08-02-2012

Effect of f.b. on noise

$$\left[(V_i - f V_o) + V_n \right] a = V_o$$
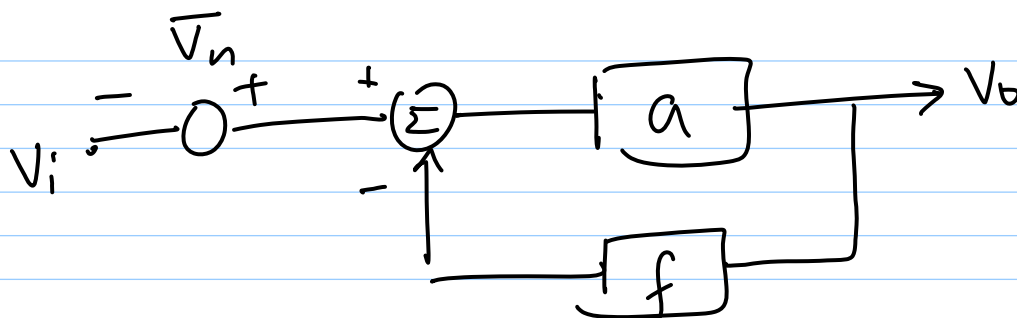
$$\Rightarrow V_o = (V_i + V_n) \cdot \frac{a}{1 + a f}$$




$\Rightarrow$ input-referred noise stays the same even w/ f.b.

* If f is noisy, overall noise gets worse

* If f.b. is not applied between input-output, $\overline{v_{i,n}^2}$ changes

Negative feedback theory


* from control system point of view

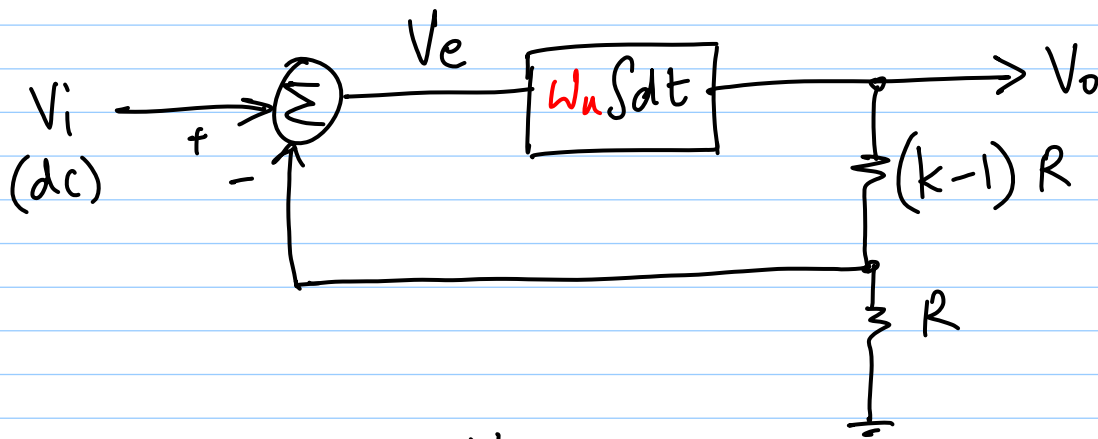


$$V_e = V_i - \frac{V_o}{k}$$

* Steady state : $V_o = k V_i$ or $V_e = 0$ for DC (otherwise integrator o/p $\uparrow$ or $\downarrow$)

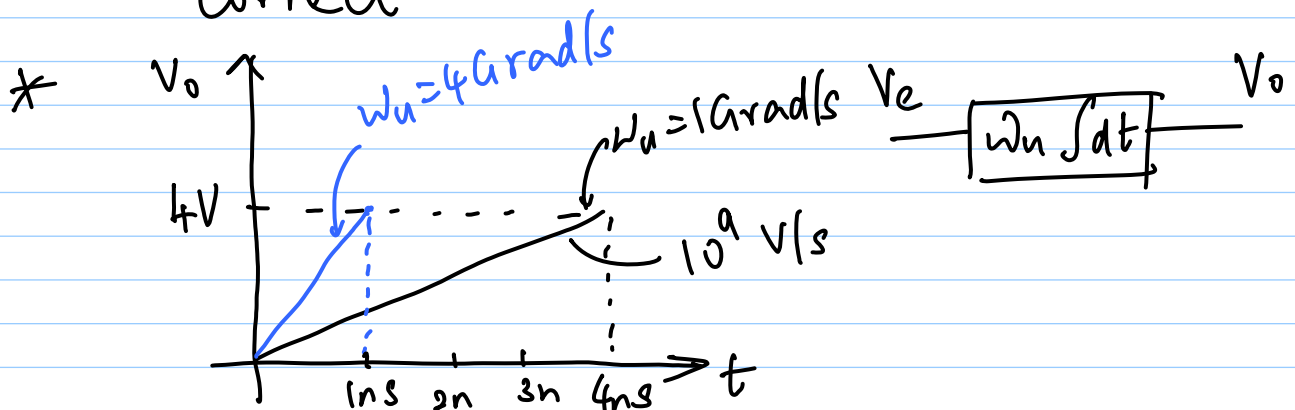* $w_u \Rightarrow$ needed to keep dimensions correct



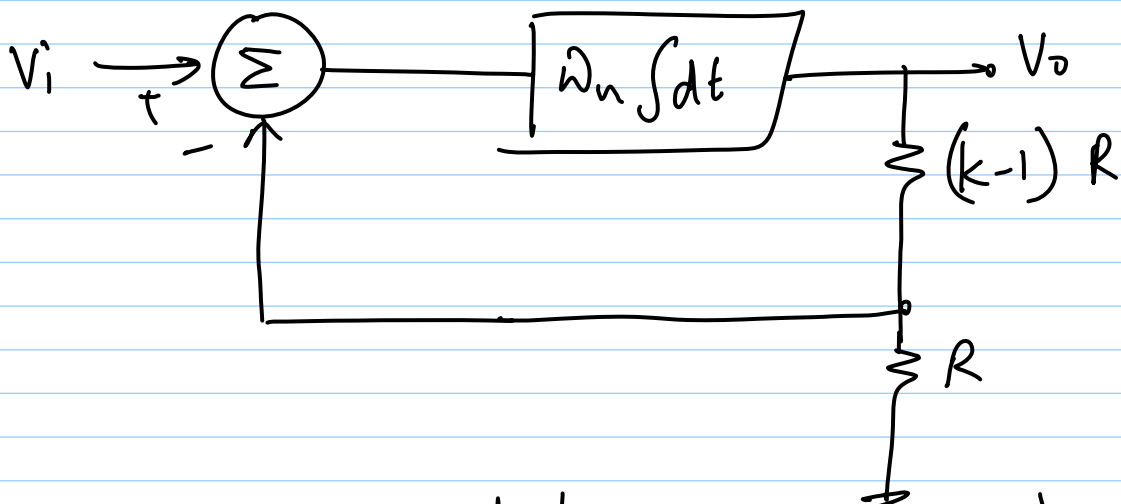

$V_i = 1V$, $V_o = kV$ (steady state)

if $V_o(0) = 0$, what does o/p look like?

write equations in differential form!

$$V_e = \frac{1}{\omega_n} \frac{dV_o}{dt}$$

also, $V_e = V_i - \frac{V_o}{k}$

$$V_i - \frac{V_o}{k} = \frac{1}{\omega_n} \frac{dV_o}{dt}$$

$$\frac{dV_o}{V_i - \frac{V_o}{k}} = \omega_n dt$$

easy case: $V_i = 0$

$$\frac{dV_o}{dt} = -\frac{\omega_n}{k} V_o$$

$$\Rightarrow V_o = e^{-(\omega_n/k)t}$$

If $V_i \neq 0$

$$\frac{dV_o}{V_i - \frac{V_o}{k}} = \omega_n dt$$

$$-k \ln \left(V_i - \frac{V_o}{k} \right) \bigg|_{V_o(0)}^{V_o(t)} = \omega_n t \bigg|_0^t$$

$$V_o(t) = V_o(0) \exp \left(-\frac{\omega_n}{k} t \right)$$

$$+ k V_i \left[1 - \exp \left(-\frac{\omega_n}{k} t \right) \right]$$

* group into two terms

→ effect of $V_o(0)$

→ effect of V_i



If equation was

$$\frac{1}{\omega_n} \frac{dV_o}{dt} = V_i + \frac{V_o}{k}$$

← what happens?

$V_0 = -kV_i$ is a potential solution;

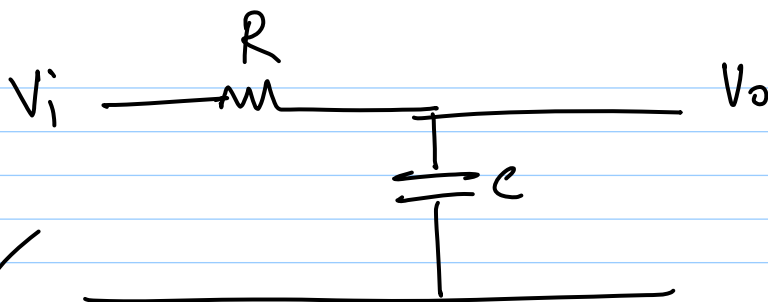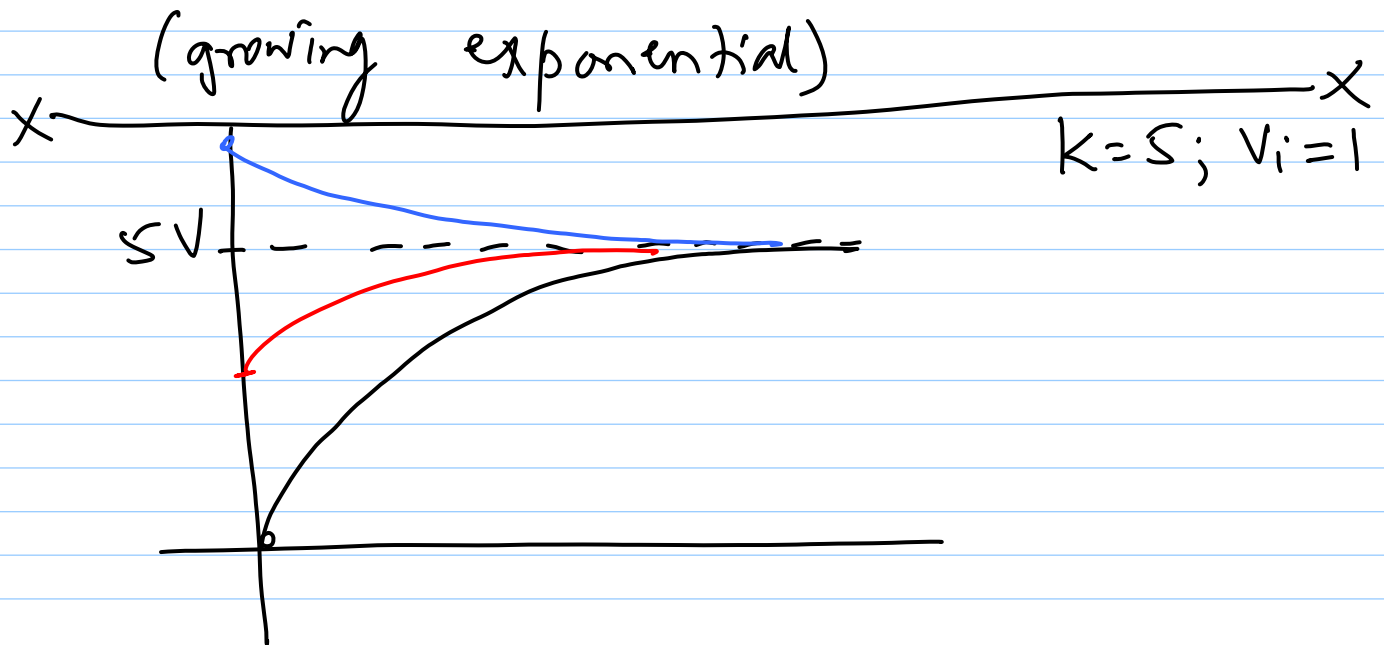In a real case: voltage blows up with time



constant V_i

$$\rightarrow V_o = V_i \left[1 - \exp\left(-\frac{t}{RC}\right) \right] + V_o(0) \exp\left(-\frac{t}{RC}\right)$$

time constant = RC

F.B.: $V_o = kV_i \left[1 - \exp\left(-\frac{\omega_n}{k} t\right) \right] + V_o(0) \exp\left(-\frac{\omega_n}{k} t\right)$


time constant = $\frac{k}{\omega_n}$

1) $I_f \omega_u \uparrow, \tau \downarrow \Rightarrow \text{why?}$

integrating faster, so get to steady state faster!

2) $I_f k \uparrow, \tau \uparrow \Rightarrow \text{why?}$

$$V_o = k V_i \leftarrow$$

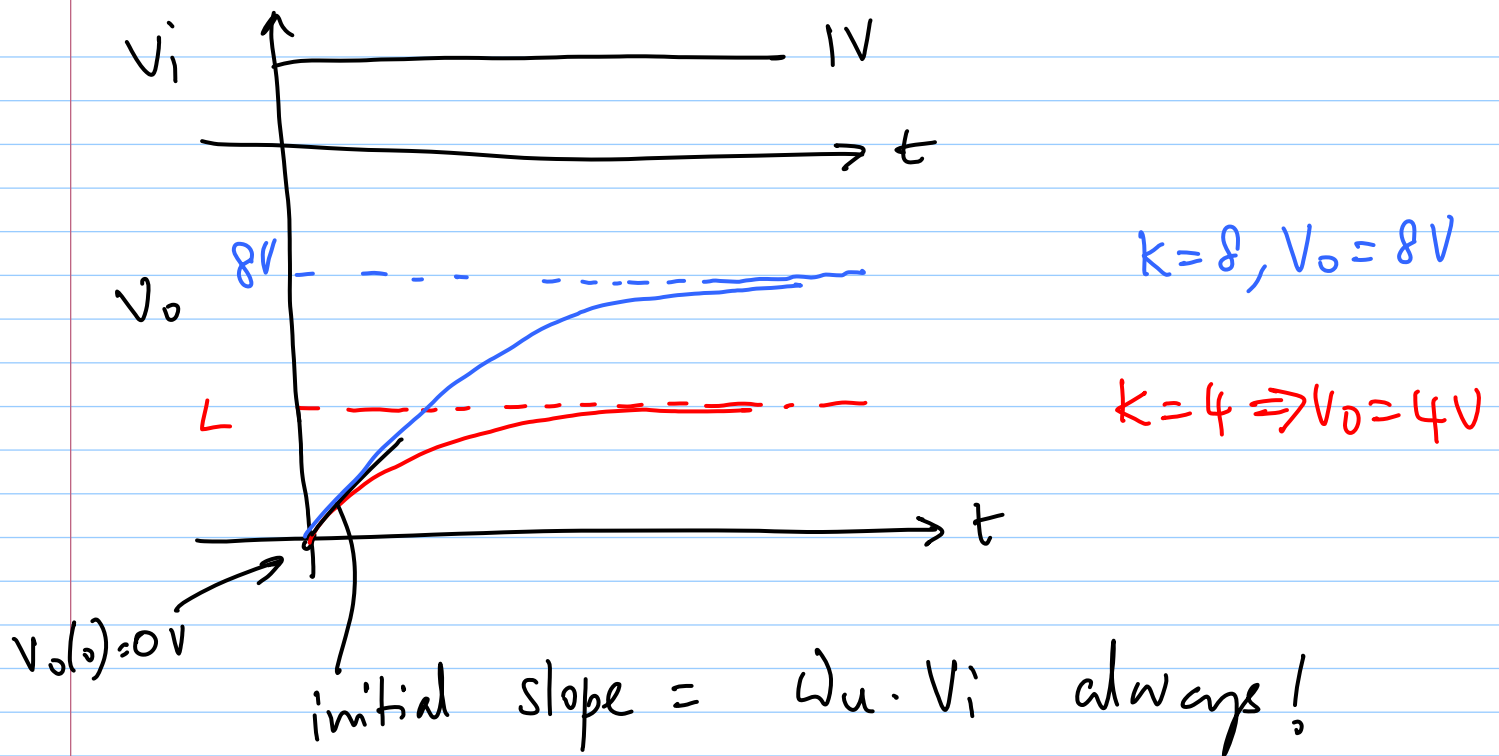

initial slope = $\omega_u \cdot V_i$ always!
why? at $t=0 \quad V_e = V_i - 0 = V_i$

$$\frac{1}{\omega_u} \frac{dV_o}{dt} \rightarrow \frac{V_e}{\omega_u} \boxed{\omega_u \int dt} \rightarrow V_o$$

initial slope = $\omega_n \cdot V_i$ always
final voltage = $k V_i$ ($\uparrow$ with k)

$\therefore \tau \uparrow$ with k

$$\tau = \frac{k}{\omega_n}$$

problem — @ higher freq. ω_n is not
easy
 τ cannot be increased
arbitrarily


* $V_i = \text{constant}$

$$\rightarrow V_o = k V_i$$

$\rightarrow$ initial condition not a problem

$$\rightarrow \tau = k / \omega_n$$

Laplace domain

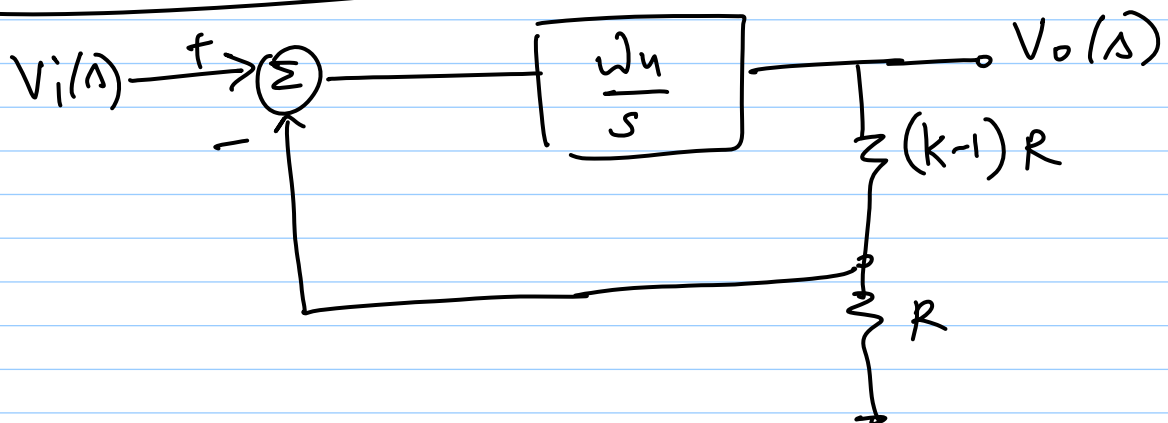


* Laplace domain
differential eqn $\rightarrow$ algebraic eqn!

$$V_o(s) = V_i(s) \frac{\omega_n}{s + \frac{\omega_n}{k}}$$

$$\frac{V_o(s)}{V_i(s)} = k \frac{1}{1 + \frac{s}{(\omega_n/k)}}$$

constant $V_i \Rightarrow s=0 \Rightarrow \frac{V_o}{V_i} = k$ ✓
(DC)


Freq. response (Sinusoidal steady state)

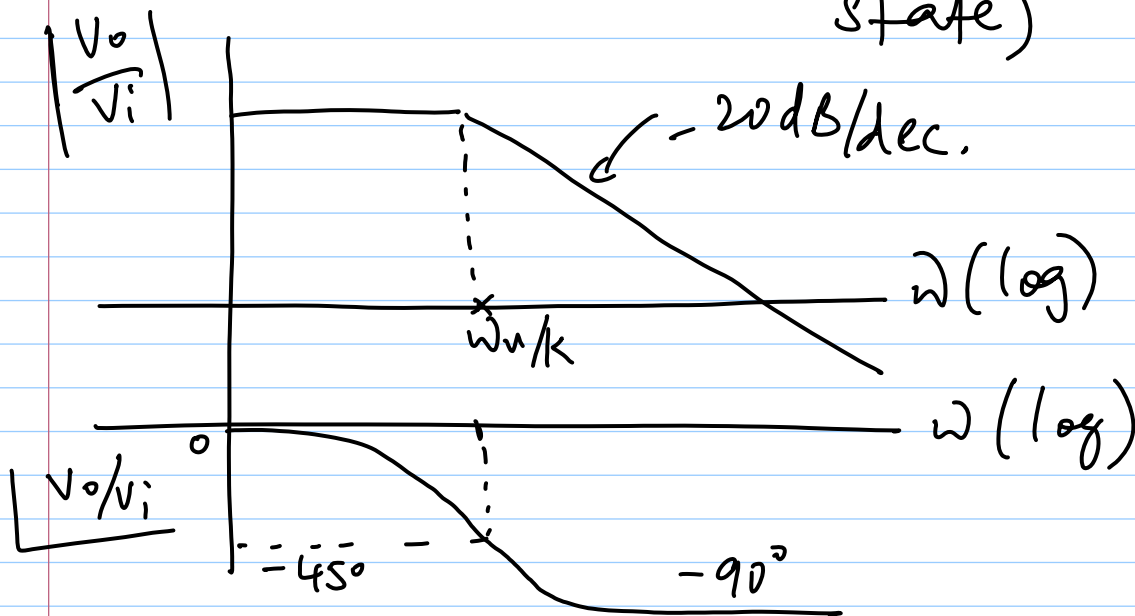

$$V_i = A \cos \omega t$$

$$\left| \frac{V_o}{V_i} \right| = \frac{k}{\sqrt{1 + \frac{k^2 \omega^2}{\omega_n^2}}}$$
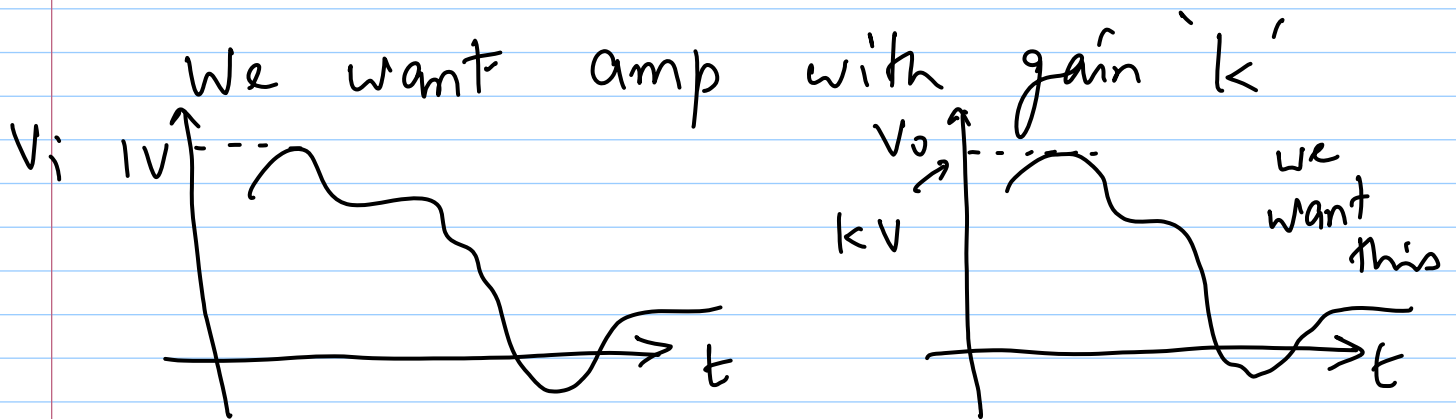
$$\angle \frac{V_o}{V_i} = -\tan^{-1} \left(\frac{k\omega}{\omega_n} \right)$$



till what freq. do you get exact same shape?

* each freq component has a different gain & phase

based on $\left| \frac{V_o}{V_i} \right|$ & $\angle \frac{V_o}{V_i}$

"Linear phase" system
phase $\propto$ freq.

$\Rightarrow$ every sine component has same delay

* phase is linear only for small ω (note that plot has log axis)

$$v_i = A \cos \omega t$$


$$v_o = \frac{k A}{\left(1 + \frac{k^2 \omega^2}{\omega_n^2}\right)^{1/2}} \cdot \cos \left[\omega t - \tan^{-1} \left(\frac{\omega k}{\omega_n} \right) \right]$$

$$\omega \ll \frac{\omega_n}{k} \Rightarrow v_o \approx k A \cdot \cos \left[\omega \left(t - \frac{k}{\omega_n} \right) \right]$$

If $\omega \gg \frac{\omega_n}{k}$

$$v_o \approx \frac{A \omega_n}{\omega} \cdot \cos \left(\omega t - \pi/2 \right)$$

looks like an integrator

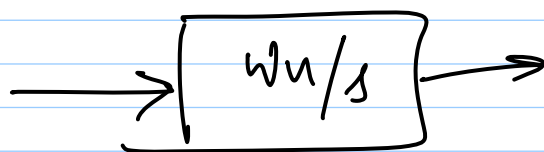

f.b. is not working!

$$\omega \ll \frac{\omega_n}{k} \Rightarrow \text{amplification} = k$$

$$\text{delay} = \frac{k}{\omega_n}$$

$$\omega \gg \frac{\omega_n}{k} \Rightarrow \text{gain} \propto 1/\omega$$

90° phase wrt input

approx.
BW

$$BW = \frac{\omega_n}{k}$$

how to increase BW?
(given ampl. value)

$\Rightarrow \omega_n$ should increase (faster integrator)