

22-2-12

Lec 19

Additional poles & zeroes

* Integrator

* F.b. network

How do you analyse it? (stability)

* all poles should be in LHP
(may be too complicated)


$$\frac{V_o}{V_i(s)} = \frac{1}{f} \cdot \frac{T(s)}{1+T(s)}$$

poles of $\frac{V_o}{V_i}(s) = \text{zeros of } 1+T(s)$


→ Use Nyquist plot to
analyse stability - polar plot of
Tutorial problem on: $T(s)$

Order	$T(s)$	Unstable?	phase margin
1	$\frac{\omega_{u,loop}}{s}$	No	90°
2	$\frac{\omega_{u,loop}}{s} \cdot \frac{1}{1+\frac{s}{p_2}}$	Stable for: $3 < 1$ for $p_2 < 4 \omega_{u,loop}$	76° for $p_2 = 4 \omega_{u,loop}$
3			
4			

 How to design for stability for different gains (k)?



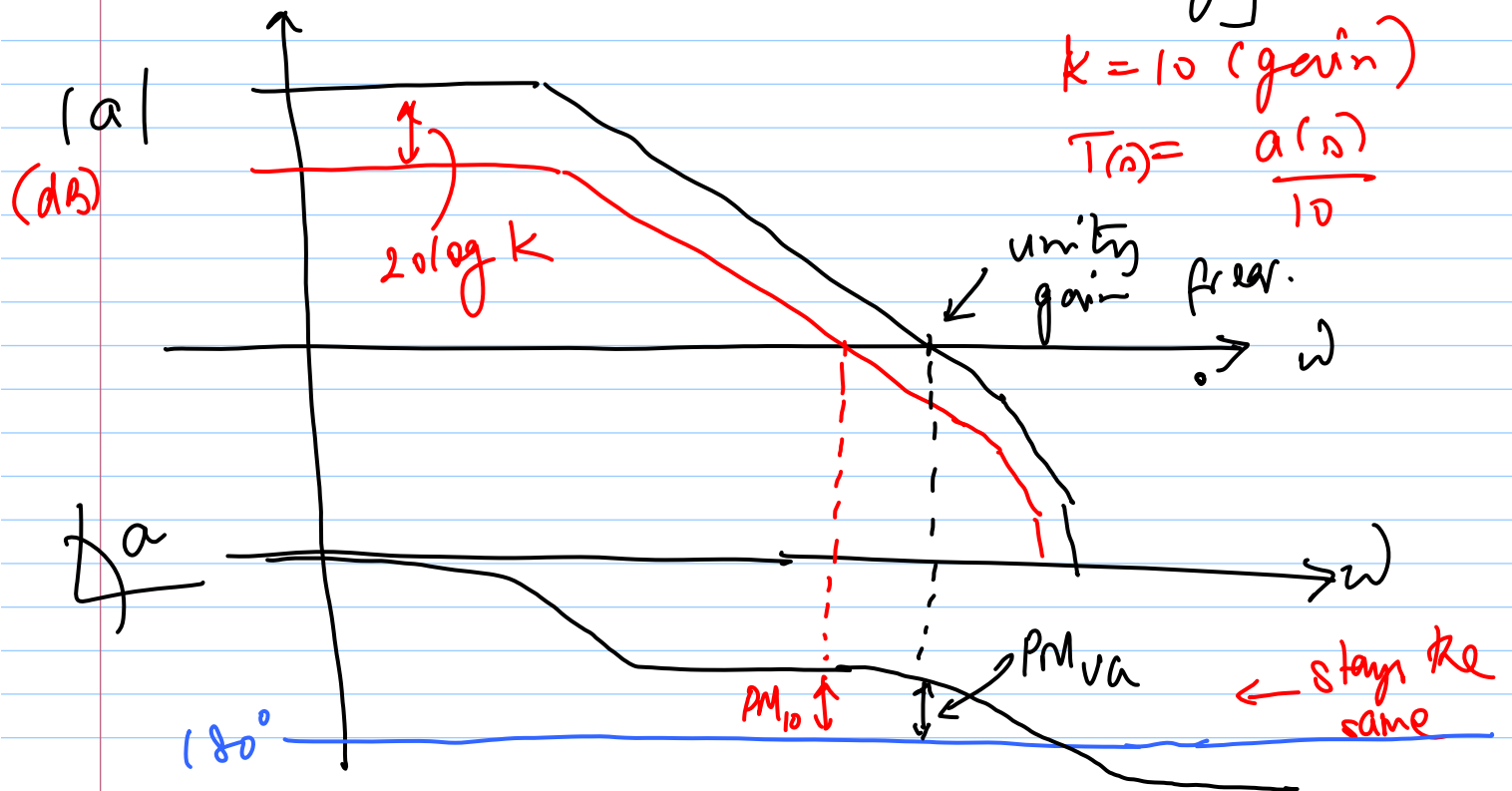$a(s)$ is what decides stability [not $a(s)$ only]



Worst-case:

$k=1$ $\leftarrow$ highest unity gain
freq.

$\Rightarrow$ lowest PM.

assumption: all-pole systems (no
zeros)

If $a(n)$ satisfies PM condition,



other k 's will be stable

$\Rightarrow$ Unity Gain Compensated Opamp

Many general purpose opamps are
UG compensated (e.g. 741)




Issue: Unity gain freq. is lower
for higher gain cases

  If you know that it is going
to be used only in high gain config,
can do a custom design for high BW
(Typical IC design case)



$$V_c = \frac{g_m}{C} \int (V_1 - V_2) dt$$

$$\Rightarrow \omega_u = \frac{g_m}{C}$$

  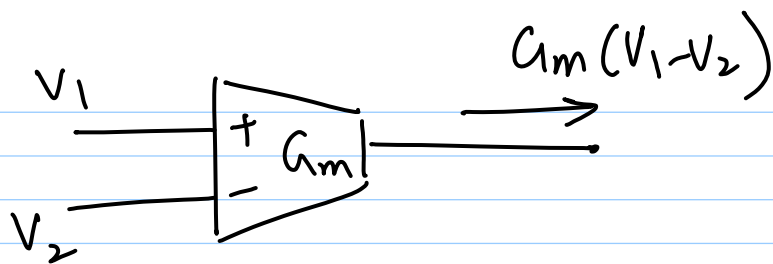

Non-idealities

- 1) parasitic caps @ nodes : (HW3)
- 2) Output impedance of G_m -stage

old
$$\frac{V_o}{V_i} = \frac{k}{1 + \frac{sC}{G_m} \cdot k}$$

new
$$\frac{V_o}{V_i} = \frac{k}{1 + \frac{G_o}{G_m} \cdot k + \frac{sC}{G_m} \cdot k}$$


$$sC \rightarrow sC + G_o$$

$$\left. \frac{V_o}{V_i} \right|_{dc} = \frac{k}{1 + \frac{G_o}{G_m} k} < k$$

finite dc gain

$V_i =$ unit step
 
$$\text{error} = \frac{1}{1 + \frac{G_o}{G_m} k}$$




Opamp

$$\frac{G_m}{sC}$$


$\rightarrow$

$$\frac{G_m}{sC + G_o}$$
 
$$\omega_u \Rightarrow \frac{G_m}{\sqrt{\omega^2 C^2 + G_o^2}} = 1$$


 
$$\text{or } \frac{1}{\frac{\omega^2 C^2}{G_m^2} + \frac{G_o^2}{G_m^2}} = 1$$



what should G_o be?

$$\frac{V_o}{V_i} \rightarrow k \Rightarrow \frac{G_o}{G_m} \cdot k \ll 1$$



$$\Rightarrow G_o \ll \frac{G_m}{k}$$

$$\text{or } \frac{G_m}{G_o} \gg k$$

e.g. error in $k < 1\%$; $k=10$

$$\Rightarrow 1 + \frac{G_o}{G_m} \cdot k \approx 1.01$$

$$\Rightarrow \frac{G_m}{G_o} = 1000$$

  


$\frac{V_o}{V_i}$ went from

$$\frac{k}{1 + \frac{sC}{G_m} \cdot k} \rightarrow \frac{k}{1 + \frac{sC}{G_m} \cdot k + \frac{G_o}{G_m} \cdot k}$$

Loop gain: $\frac{G_m}{sC \cdot K} \rightarrow$

$$\frac{G_m}{(sC + G_0) \cdot K}$$

 

Finite dc gain : because $R_o \neq \infty$

$$\ast \quad \frac{W_u}{s} \rightarrow \frac{1}{\frac{s}{W_u} + \frac{1}{A_0}} \quad \leftarrow \text{dc gain}$$

$\ast$ Steady state gain error or relative error $\approx \frac{1}{\text{DC LG}}$

$\ast$ How to increase $\frac{G_m}{G_0}$?


$G_0 \Rightarrow$ typically from rds

→ dependence on I (reduce)
but $G_m \downarrow \Rightarrow G_m/C \downarrow$


→ dependence on L (increase)
but area $\uparrow$ too; also C will
increase due to device cap

Gain $\uparrow$ by large factors (e.g.
100 times)

 Basic problem: all of $G_m \cdot \Delta V_{in}$ current does not
flow thro' cap






2) $I-V$ converter.

 

$$I_f R_o < \infty,$$

$$V < IR$$

⇒ use a CCVS

   


can add CCCS to improve G_m stage

can be replaced with more complex arch.

e.g.

typically not more than 3-stages

 

problem: each G_m has R_o
each node has C

$\Rightarrow$ extra delay

Opamp

- $\rightarrow$ Differentiating of voltage ($V_1 - V_2$)
- $\rightarrow$ integration of $V_1 - V_2$
- $\Rightarrow$ transconductor + capacitor
- $\rightarrow R_o \Rightarrow$ finite DC gain
 - $\rightarrow \uparrow L$
 - $\rightarrow \uparrow R_o$ (CCCS)
 - $\rightarrow$ transimp. amp. (I-V)