

24-2-12

Lec 21


1-stage opamp w/ output cap C

$$\text{DC gain: } \frac{g_{mn}}{g_{dspt} + g_{dsn}}$$

$$\omega_u = \frac{g_{mn}}{C}$$

Stab: $\frac{g_{mp}}{C_1} \gg \frac{g_{mn}}{C}$

Noise

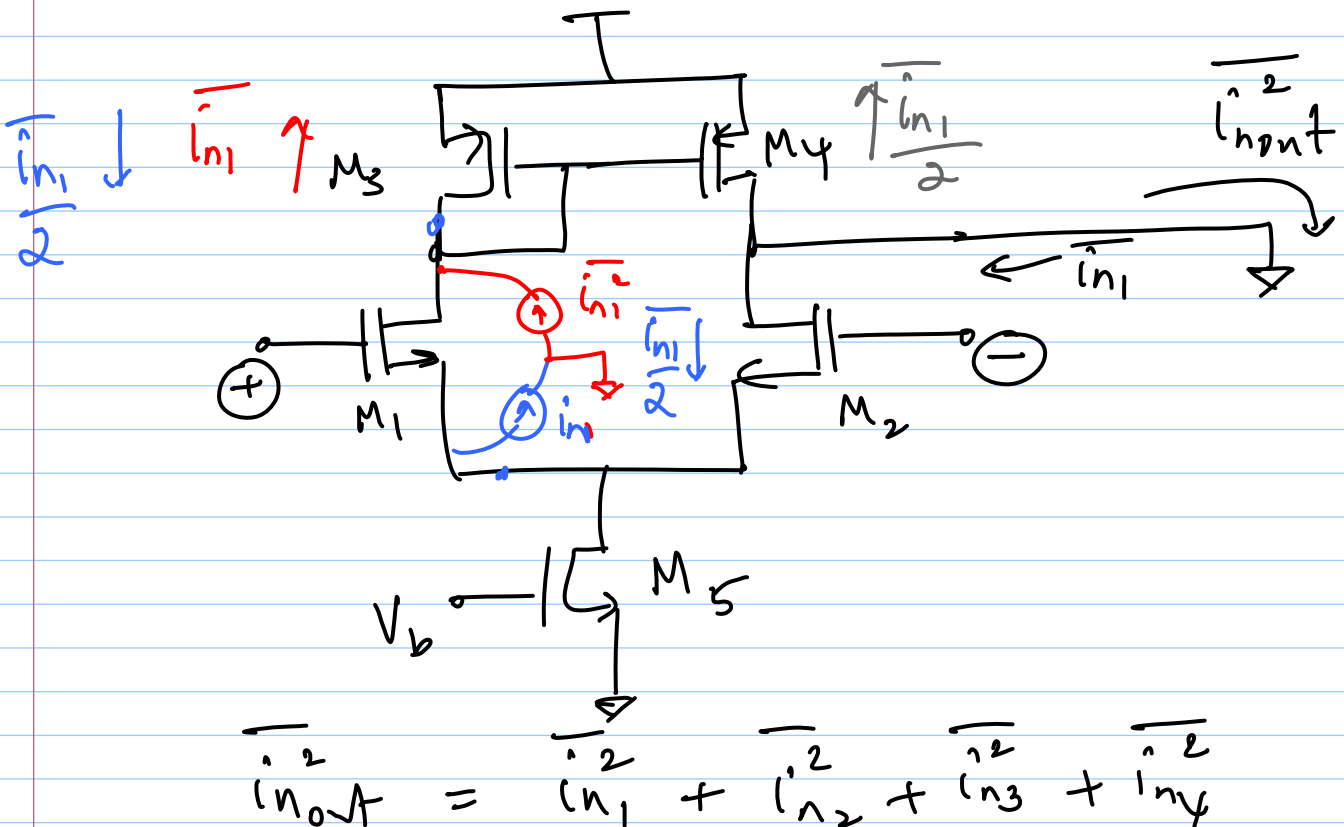

$$S_{out} = \frac{16}{3} kT (g_{m1} + g_{m3})$$

$$G_m = g_{m1}$$

$$S_{Vin} = \frac{S_{out}}{G_m^2}$$

$$= \frac{16}{3} \frac{kT}{g_{m1}} \left(1 + \frac{g_{m3}}{g_{m1}} \right)$$

Optimising noise : reduce g_{m3}
 $\Rightarrow \downarrow (W/L)$


$\Rightarrow V_{DSAT_P} \uparrow \Rightarrow \text{swing limits} \downarrow$
 g_{m1} cannot change $\therefore \omega_u = \frac{g_{m1}}{C}$

Offset

$$\Delta i_{out} = g_{m1} \Delta V_{T1} + g_{m3} \Delta V_{T3}$$

$$\sigma_{V_{OS, in}}^2 = \frac{g_{m1}^2 \sigma_{V_{T1}}^2 + g_{m3}^2 \sigma_{V_{T3}}^2}{g_{m1}^2}$$
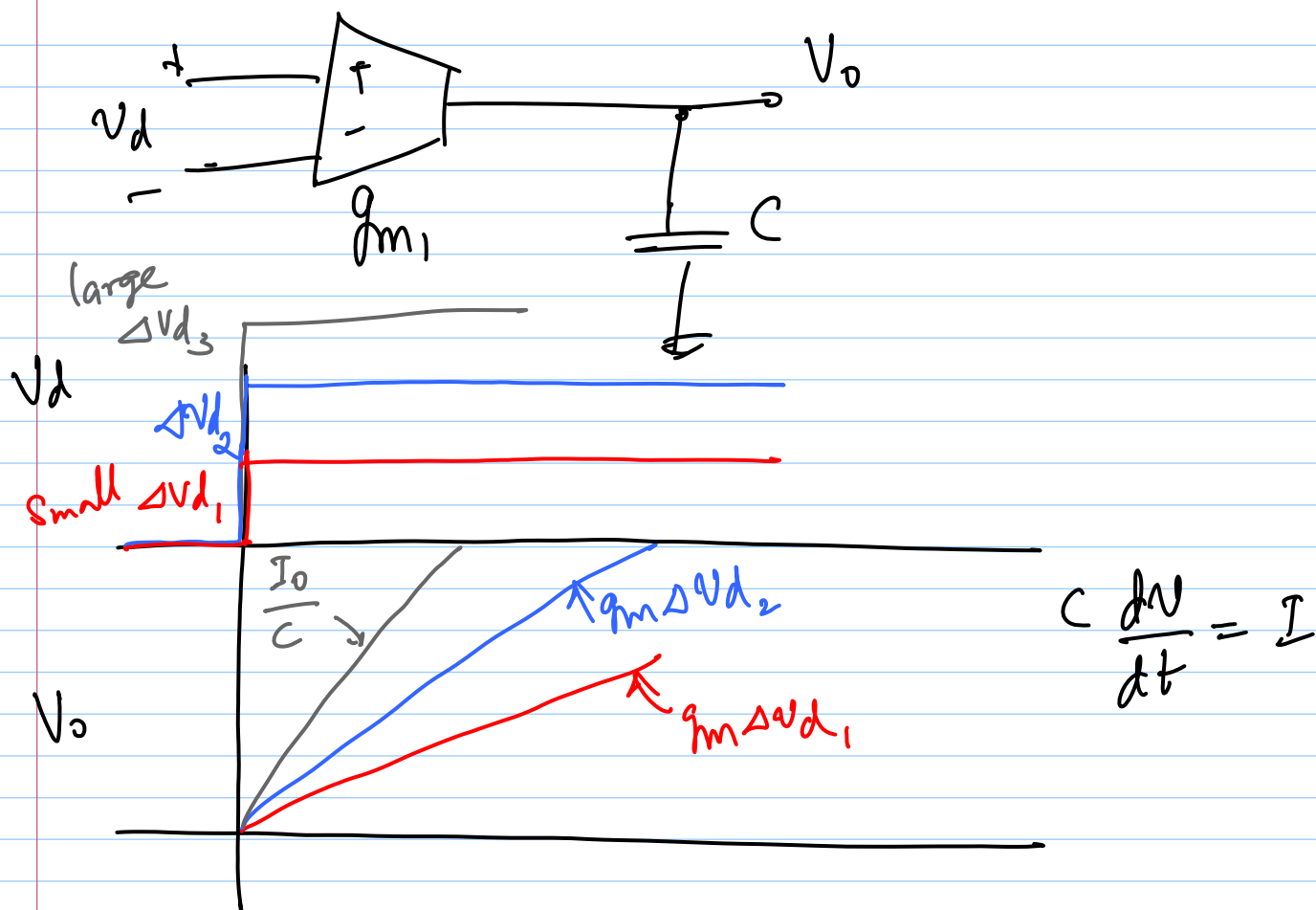
$$= \sigma_{V_{T1}}^2 + \left(\frac{g_{m3}}{g_{m1}} \right)^2 \sigma_{V_{T3}}^2 \quad \left(\begin{array}{l} \text{compare} \\ \text{w/} \\ \text{noise} \end{array} \right)$$



at some large v_d

$$\left. \begin{array}{l} I_1 = I_o \\ I_2 = 0 \end{array} \right) v_d = \sqrt{2} (V_{as1} - V_{T1})$$

$\Rightarrow I_3 = I_o$; $I_4 = I_o$ flows through output cap C

$$\Rightarrow \text{slope} = \frac{I_o}{C} \quad (\text{SLEW RATE})$$

max. current pulled in from $C = I_o$

($I_1 = 0$, $I_2 = I_o$) (-ve slew rate)


How to $\uparrow$ slew rate (given ω_n)

$\Rightarrow \uparrow I_0, \downarrow V_{ov}$

otherwise $g_m \uparrow, \omega_n \uparrow$

$\Rightarrow$ stability gets affected

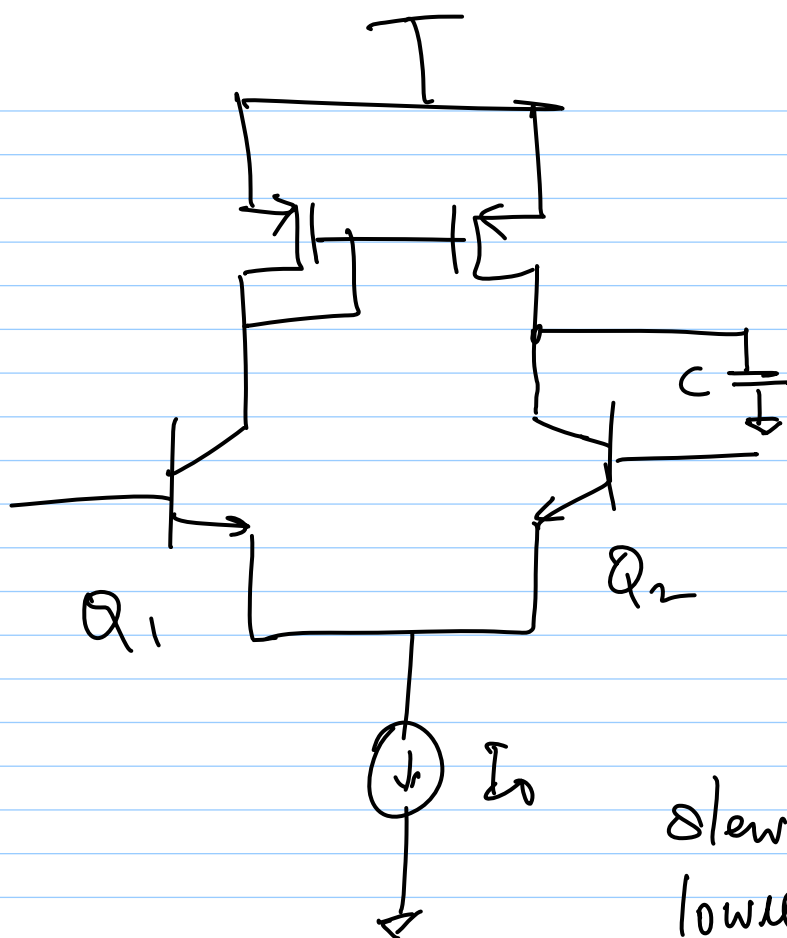larger slew rate $\Rightarrow$ larger power
& larger V_{ov}




$$g_{m1} = \frac{I_0}{2V_{t1}}$$

$$V_{t1} = \frac{kT}{q}$$

$$\text{slew rate} = \frac{I_0}{C}$$

slew rate maybe
lower for BJT designs
 $\therefore I_0$ is lower for same g_m

CM range

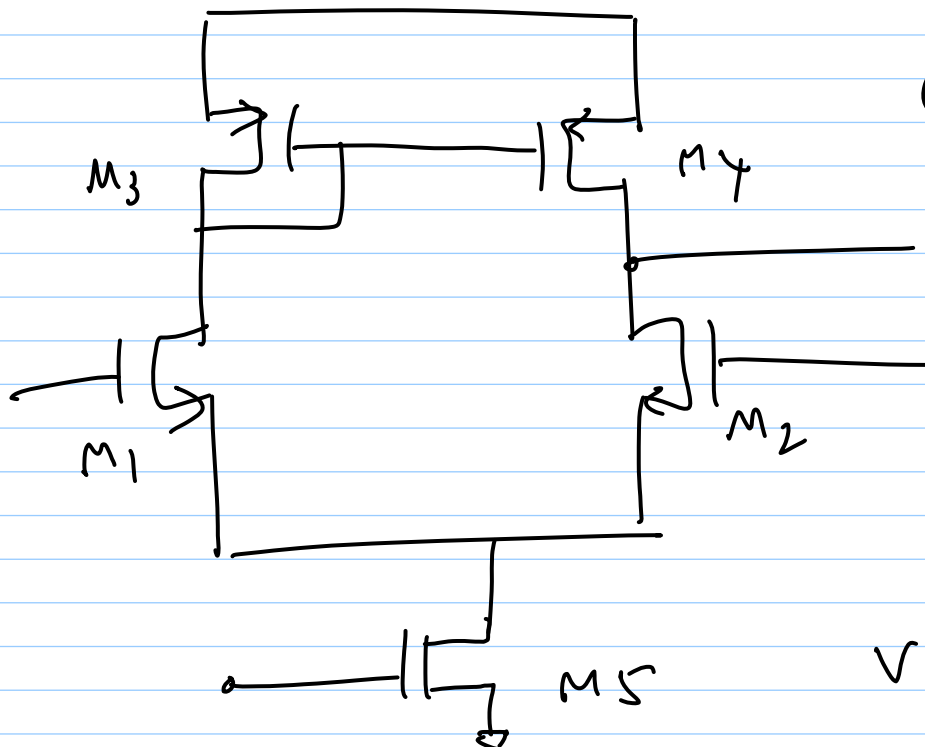

CM range @
input :

$$V_{CM, max} = V_{DD} - V_{DSAT3} + V_{T1} \quad (M_1 - \text{triode})$$

$$V_{CM, min} = V_{DSAT5}$$

$$V_{DD} - V_{DSAT4} > V_o > V_{CM, in} - V_{T1} + V_{DSAT1}$$

Data sheet

1) DC gain $= \frac{g_{m1}}{g_{ds1} + g_{ds3}}$

2) UAF $W_u = \frac{g_{m1}}{C_L}$

3) Non-dominant poles & zeroes

$$p_2 = -\frac{g_{m3}}{C_1} ;$$


$$z_1 = -2 \frac{g_{m3}}{C_1}$$

4) Input referred offset

$$\sigma_{os, in}^2 = \sqrt{V_{T1}}^2 + \left(\frac{g_{m3}}{g_{m1}} \right)^2 \sqrt{V_{T3}}^2$$

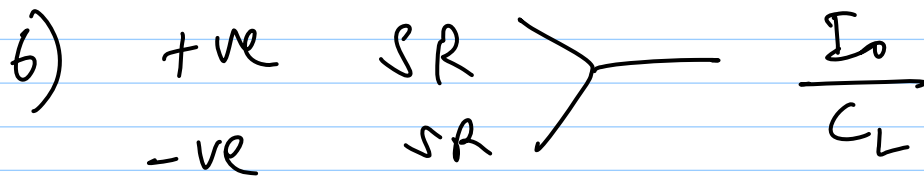5) Input-ref. Noise PSD

$$= \frac{16kT}{g_{m1}} \left[1 + \frac{g_{m3}}{g_{m1}} \right]$$




7) Output swing limit

$$V_{DD} - V_{DSAT3} > V_O > V_{CM,in} - V_{T1}$$

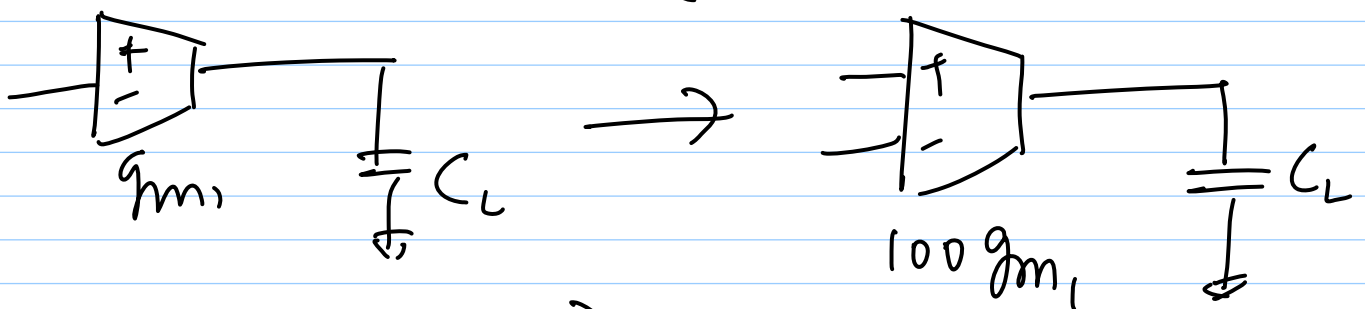8) Input CM swing limit

$$V_{DD} - V_{A13} > V_{CM,in} > V_{A51} + V_{DSAT5} + V_{T1}$$

Ckt scaling $\left(\frac{W}{L}\right)_i \rightarrow 100 \times \left(\frac{W}{L}\right)_i$



$g_{m1} \rightarrow 100 \times$
 $C_i \rightarrow 100 \times$) β_2 & Z_2 also scale 100 times

$\omega_u \sim 100 \frac{g_{m1}}{C_L}$, but parasitics exist
 actual $C_c = C + C_{par}$ & $C_{par} \rightarrow 100 C_{par}$

⇒ ultimate limit to scaling in
a given technology (parasitic limited)