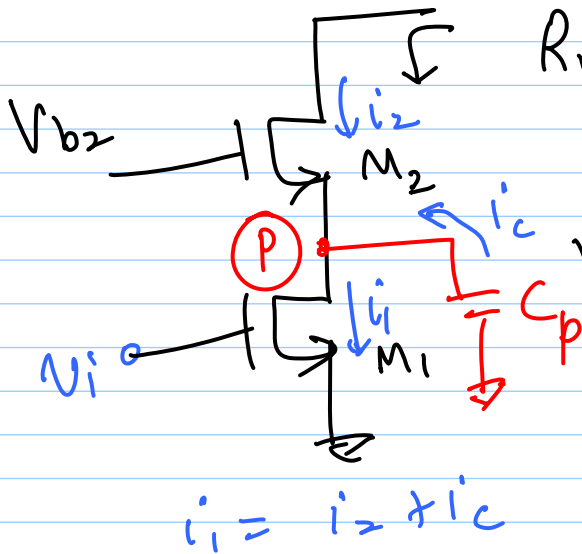


28-2-12

Lec - 22

Cascode (Telescopic opamp)



$$R_{out} = r_{ds1} + r_{ds2} + (g_{m2} r_{ds2}) r_{ds1}$$

$$V_{b2} = V_{DSAT1} + V_{GS2} = V_{T2} + V_{DSAT1} + V_{DSAT2}$$

↑
backgate effect

$$C_p \approx C_{gs2} + C_{db1} \quad (\text{ignore } C_{gd})$$

Extra pole @ P: $\frac{g_{m2}}{C_p}$



at every cascode node

(but much better than $\uparrow L$
 $\Rightarrow$ par. cap. $\uparrow$ a lot more)

$$* \quad C_{in} \approx C_{gs1} + C_{gd1}$$

$$\text{gain from } G_1 \text{ to } D_1 = \frac{g_{m1}}{g_{m2}} \approx 1$$

for normal opamp, C_{in} is much larger

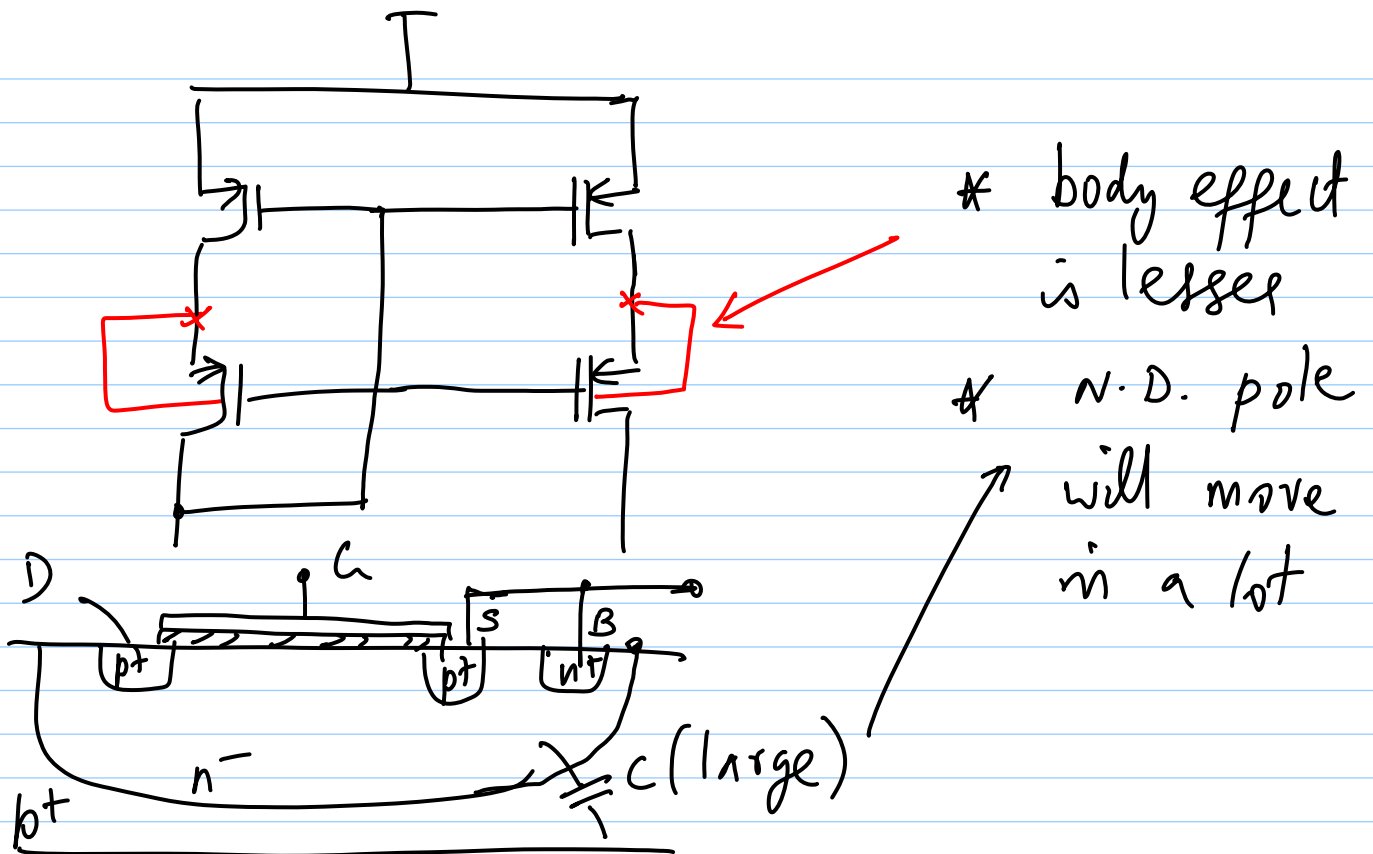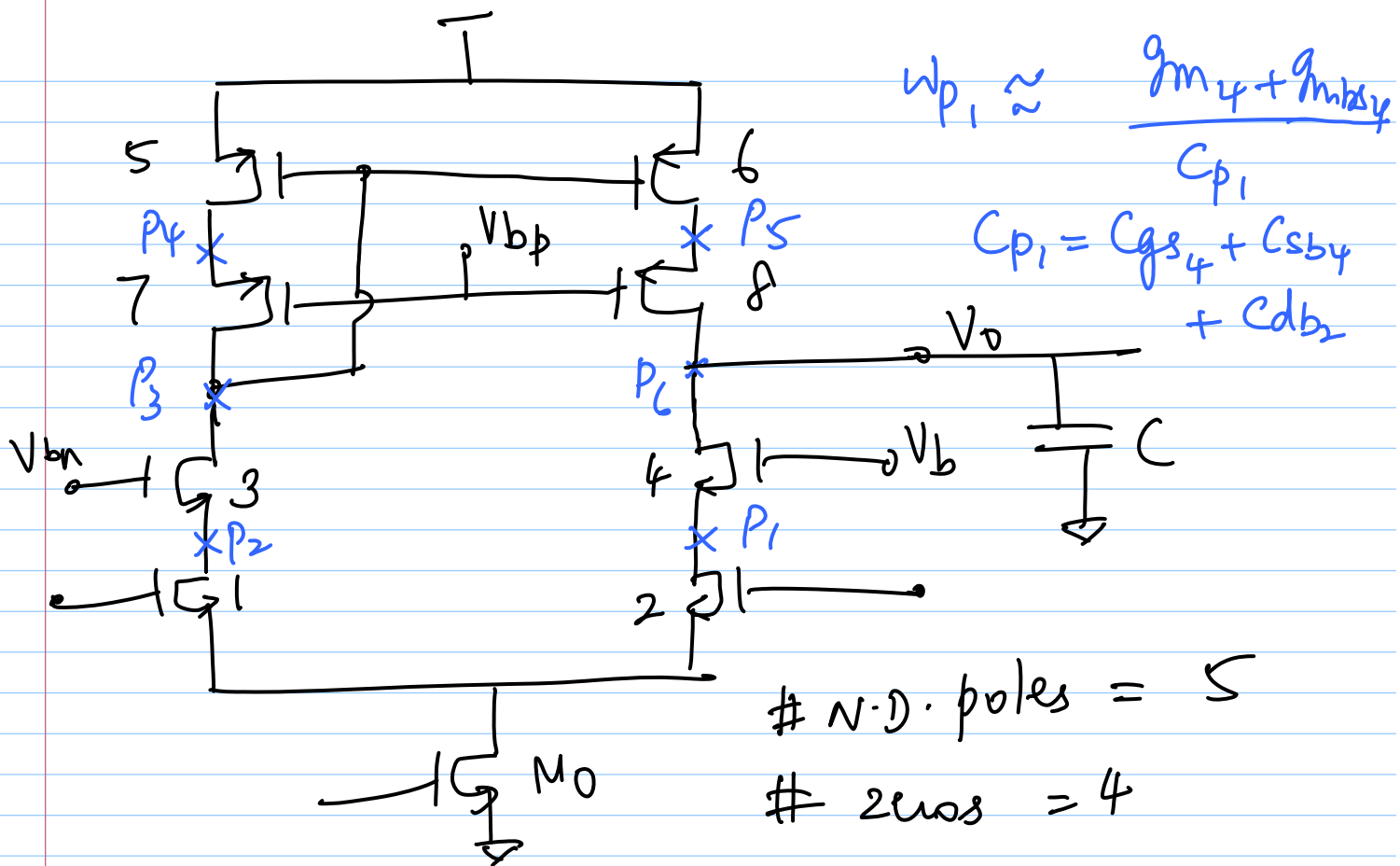

$$1) \text{ DC gain} = g_{m1} (g_{m3} r_{ds3} r_{ds1} || g_{m7} r_{ds7} r_{ds5})$$

$$2) \text{ VAF} = \frac{g_{m1}}{C_L}$$

3) non-dominant poles
zeros

$$4) \sqrt{v_{OS,in}^2} \leftarrow \text{1st W (similar to noise)}$$

5) Noise PSD $\leftarrow$ same as before
@ low freq.

$$6) \text{ SR} \leftarrow I_0 / C_L$$

7) Output swing limit
— lower (more trans stacked up)

$$V_{out,max} : V_{DD} - V_{DSAT_6} - V_{DSAT_8}$$


$$V_{out,min} : V_{bn} - V_{T_4}$$

8) Input swing limit — lower

$$V_{CM,in} (\text{min.}) = V_{AS1} + V_{DSAT_0}$$

$$V_{CM,in} (\text{max.}) = V_{DD} - V_{AS5} - V_{DSAT_3} + V_{T_1}$$

Can you short input to output?

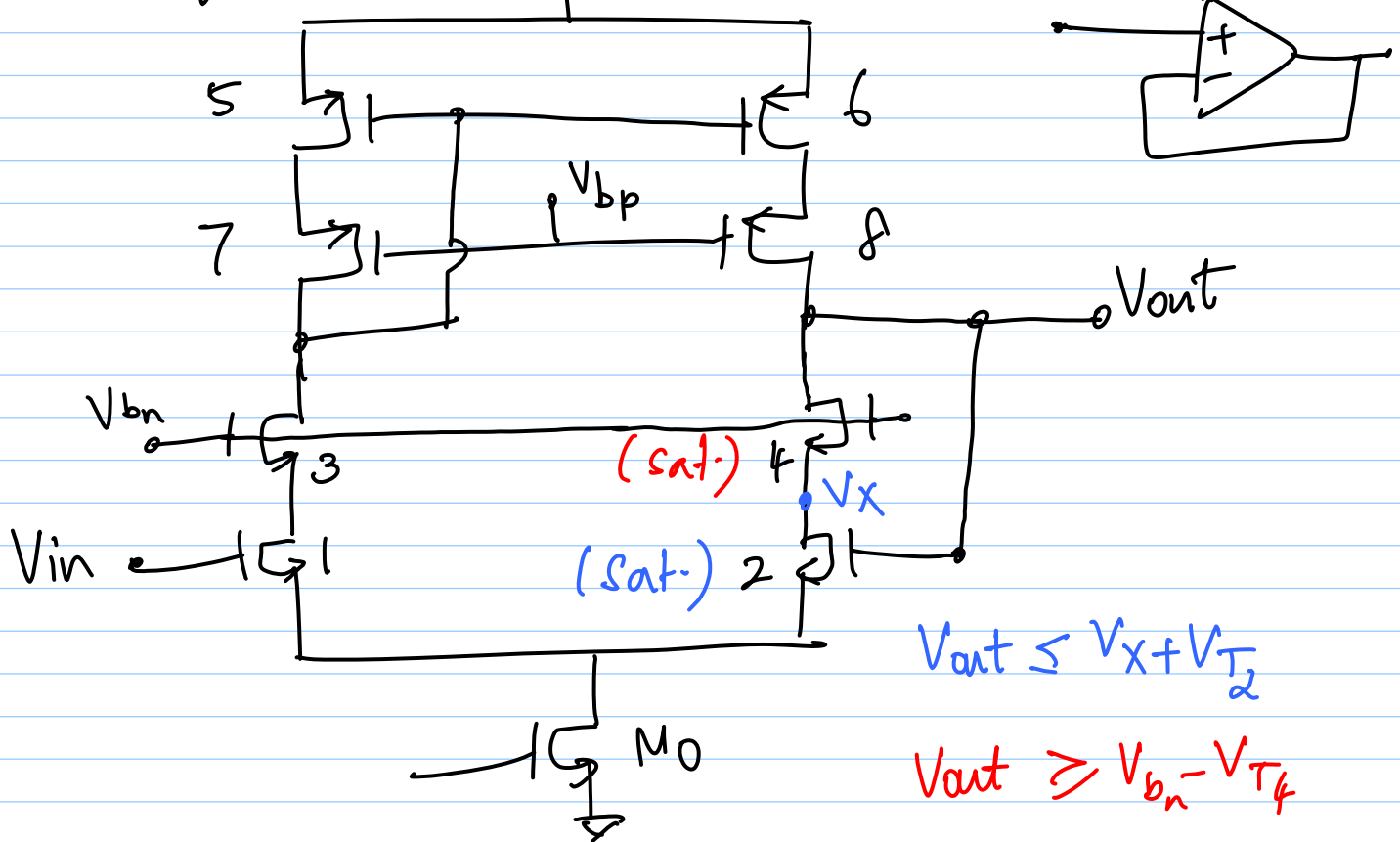


$$V_x = V_{bn} - V_{A54}$$

$$\Rightarrow \underbrace{V_{bn} - V_{T4}}_{V_{min.}} \leq V_{out} \leq \underbrace{V_{bn} - V_{A54} + V_{T2}}_{V_{max.}}$$

$$\begin{aligned}
 V_{max} - V_{min.} &= V_{T4} + V_{T2} - V_{A54} \\
 &= V_{T2} - V_{DSAT4} \\
 &< V_{T2}
 \end{aligned}$$

$\therefore$ Unity gain buffers are different!

Conditions on V_{bp}

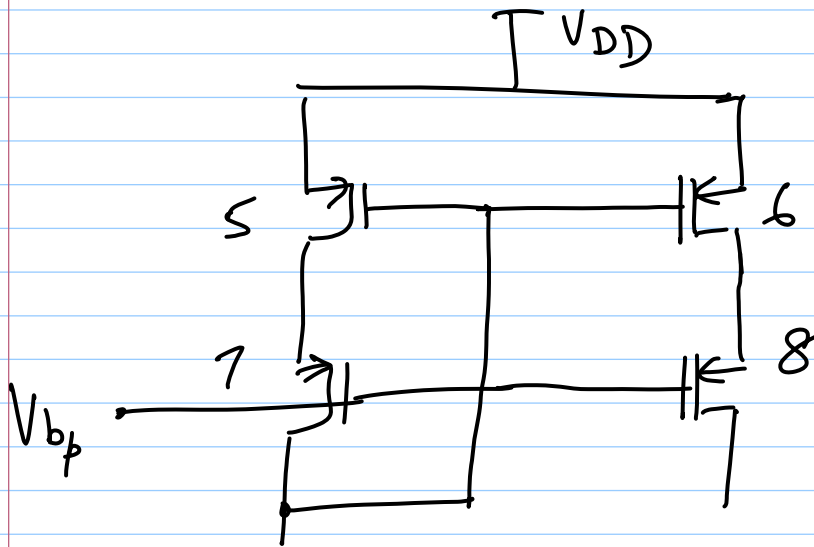


$$V_{bp} < V_{DD} - V_{DSAT5} - V_{SG7}$$

$$V_{bp} > V_{DD} - V_{SG5} - V_{T7}$$

Design example : see Razavi' example 9.5 (fully diff. circ.)


Output CM

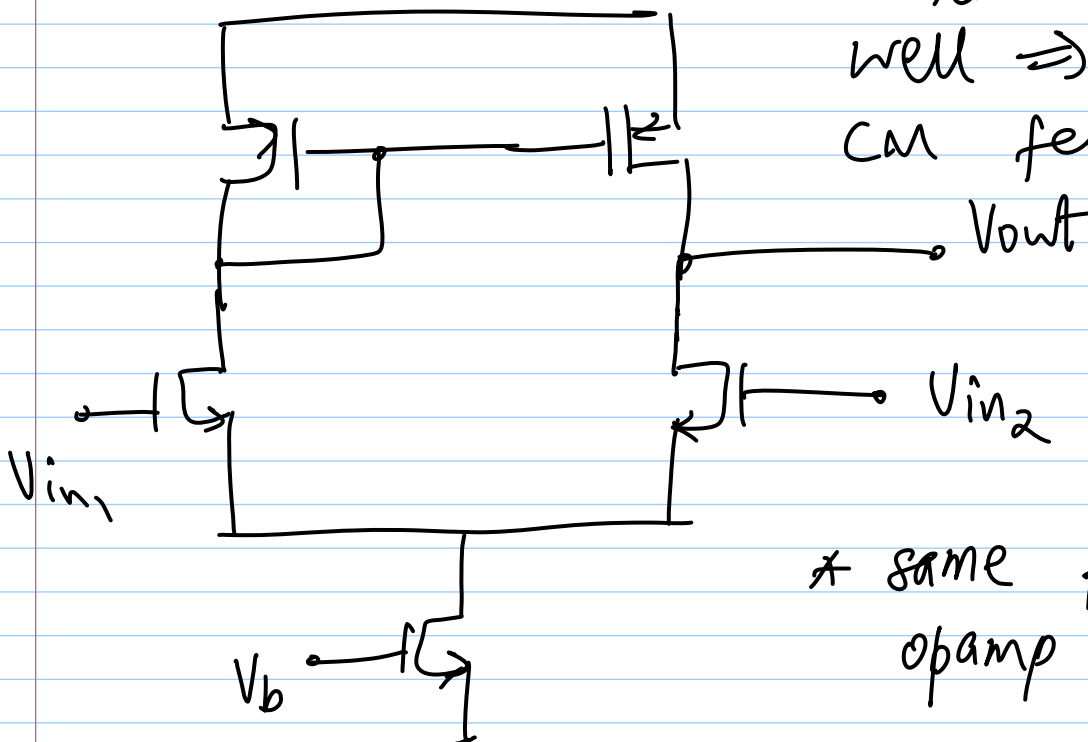* $V_{out,cm}$ is not set well $\Rightarrow$ requires CM feedback.



* same for telescopic opamp

Add buffer?

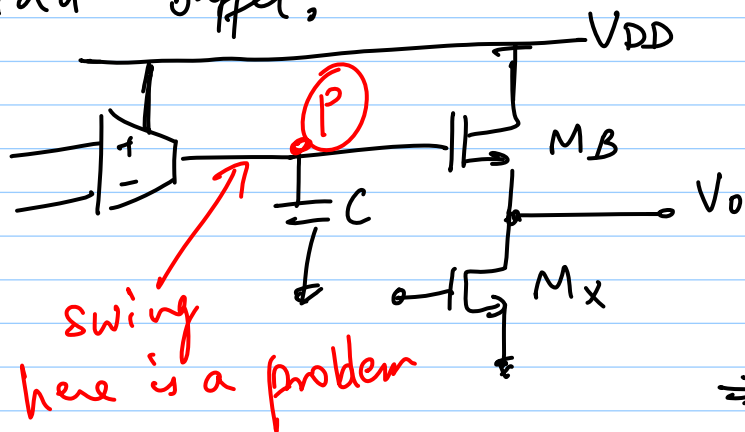

$$V_{DSAT_X} < V_O < V_{DD} - V_{DSAT_B}$$

$$V_{DSAT} \sim 200\text{mV}$$

$$V_{DD} \sim 1.2\text{V}$$

$$\Rightarrow V_O \text{ range} = 0.8\text{V}$$

For $V_O = V_{DD} - V_{DSAT_B}$,

$$V_P = V_{DD} + V_T \rightarrow \text{not possible}$$

e.g. $V_T = 0.4\text{V}$, $V_{DSAT} = 0.2\text{V}$, $V_{DD} = 1.2\text{V}$

$$V_{P_{max.}} = V_{DD} - V_{DSAT} = 1\text{V}$$

$$V_{O_{max.}} = V_{P_{max.}} - V_{GSB}$$

$$= V_{P_{max.}} - (V_T + V_{DSAT})$$

$$= 1 - (0.4 + 0.2) = 0.4\text{V}!$$