
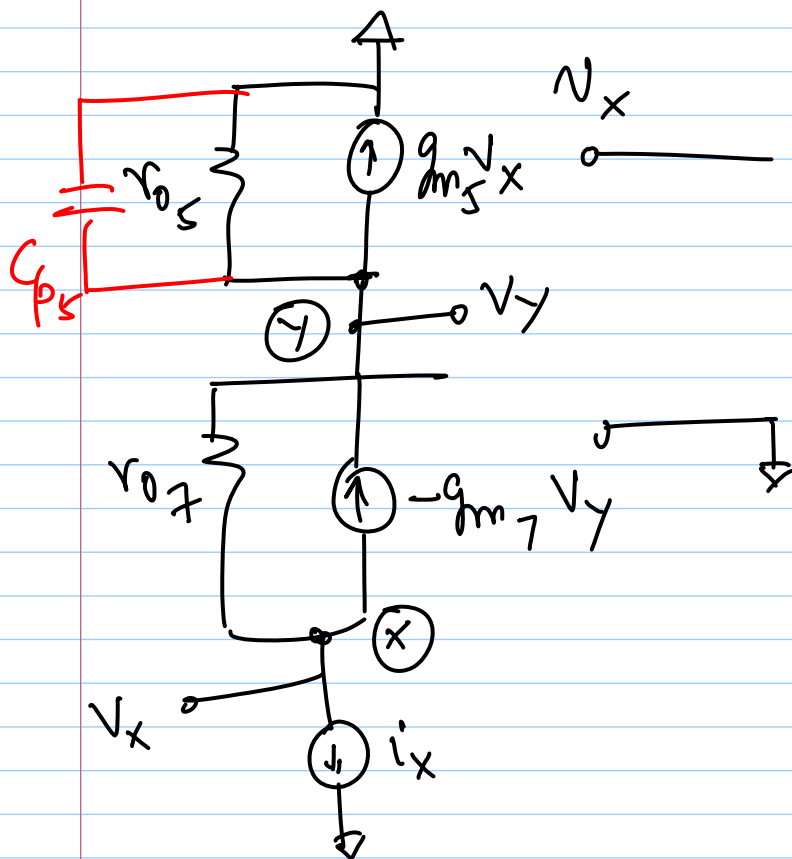


29.2-12

Lec 23

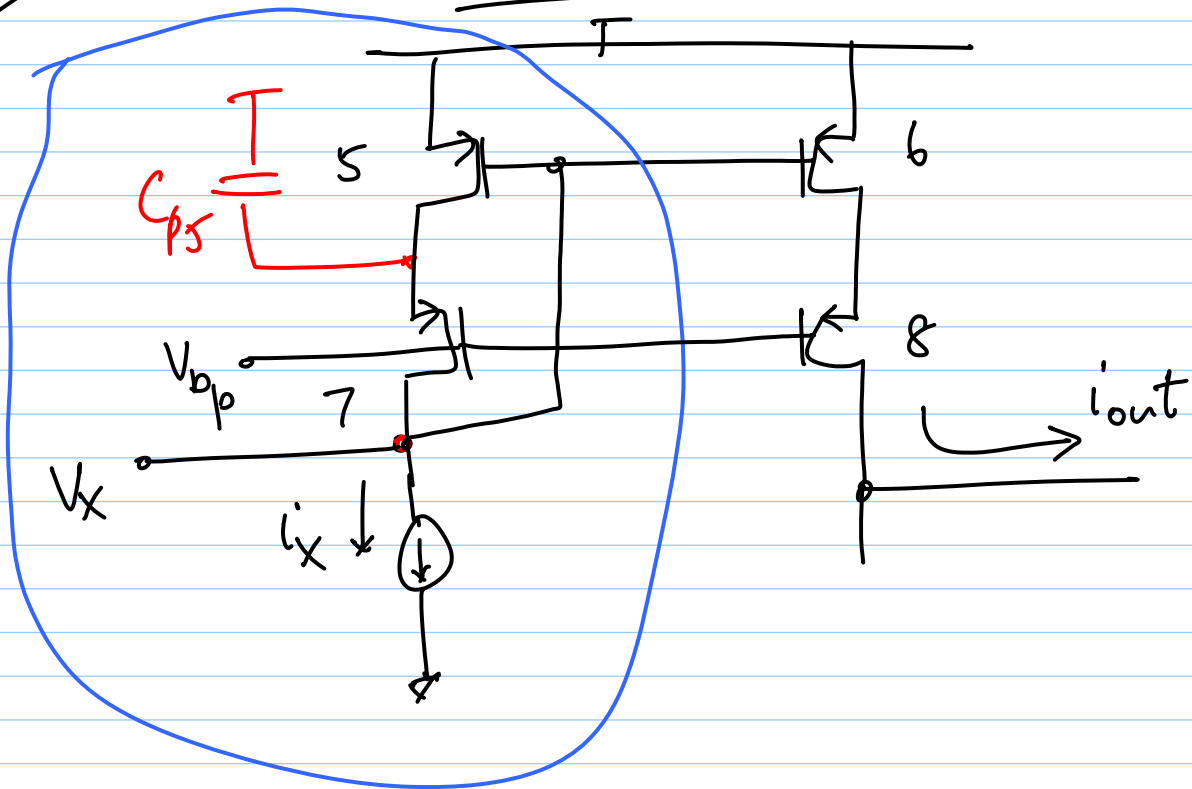

$$\frac{V_x}{i_x} (s)$$

@ $\hat{x}$

$$(V_x - V_y) g_{o7} - g_{m7} V_y = -i_x$$

$$V_y = \frac{g_{o7} V_x + i_x}{(g_{m7} + g_{o7})}$$

@ (Y),

$$V_Y (sC_{p5} + g_{o5}) + g_{m5} V_X = -i_x$$


$$\frac{(g_{o7} V_X + i_x)}{g_{m7}} (sC_{p5} + g_{o5}) + g_{m5} V_X = -i_x$$

$$V_X \left[g_{m5} + \frac{g_{o7}}{g_{m7}} (sC_{p5} + g_{o5}) \right] = -i_x \left[1 + \frac{sC_{p5} + g_{o5}}{g_{m7}} \right]$$

$$\frac{V_X}{i_x} = - \frac{g_{m7} + g_{o5} + sC_{p5}}{g_{m5} g_{m7} + g_{o7} (sC_{p5} + g_{o5})}$$

$$= - \frac{g_{m7} + sC_{p5}}{g_{m5} g_{m7} + g_{o7} sC_{p5}}$$
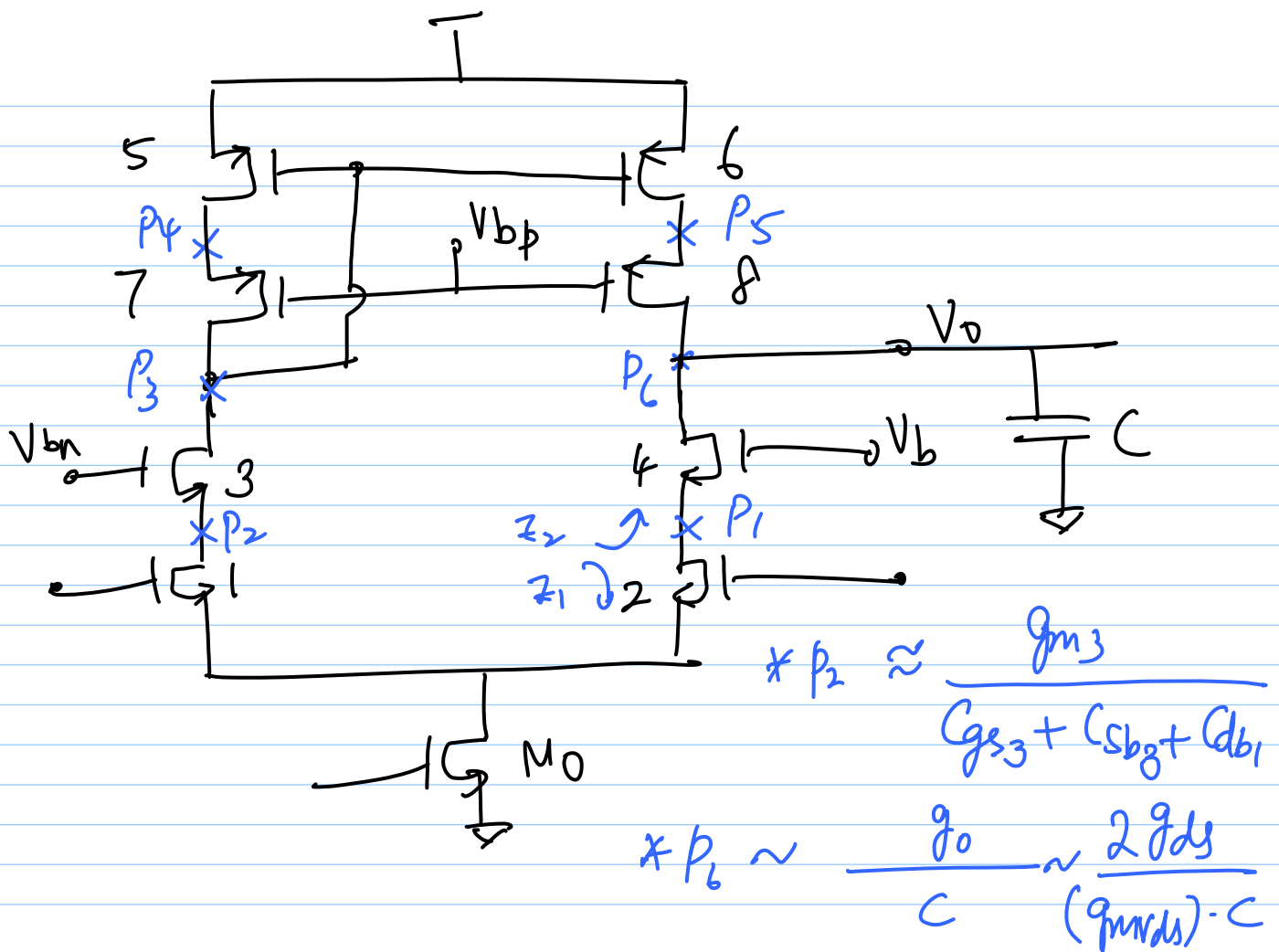
$$= - \frac{1}{g_{m5}} \cdot \frac{1 + sC_{p5}/g_{m7}}{1 + \frac{sC_{p5} \cdot g_{o7}}{g_{m5} g_{m7}}}$$



$$z_1 \approx r_{ds2}$$

$$z_2 = \frac{1}{g_{m4}} \left[1 + \frac{g_{m8} r_{ds8} \cdot r_{ds6}}{r_{ds4}} \right]$$

$$\approx \frac{g_{m8} r_{ds8} r_{ds6}}{g_{m4} r_{ds4}} \sim r_{ds}$$


$$\Rightarrow z = z_1 \parallel z_2 \sim r_{ds}/2 \sim \left(\frac{1}{2g_{ds}} \right)$$

$$\Rightarrow p_1 \sim \frac{2g_{ds}}{C_{gs4} + C_{sb4} + C_{db2}} \Rightarrow p_1 \ll p_2$$


but


Folded Cascode opamp

→ pmos cascode for nmos diff pair

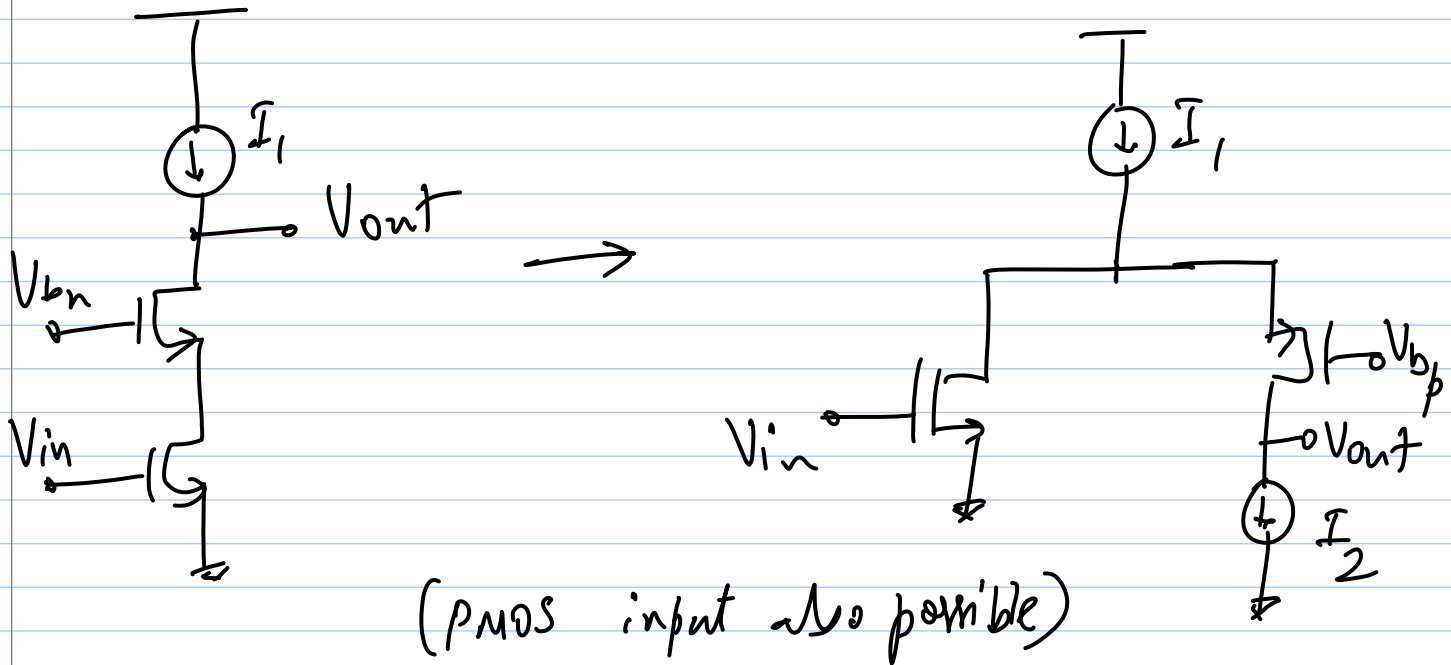

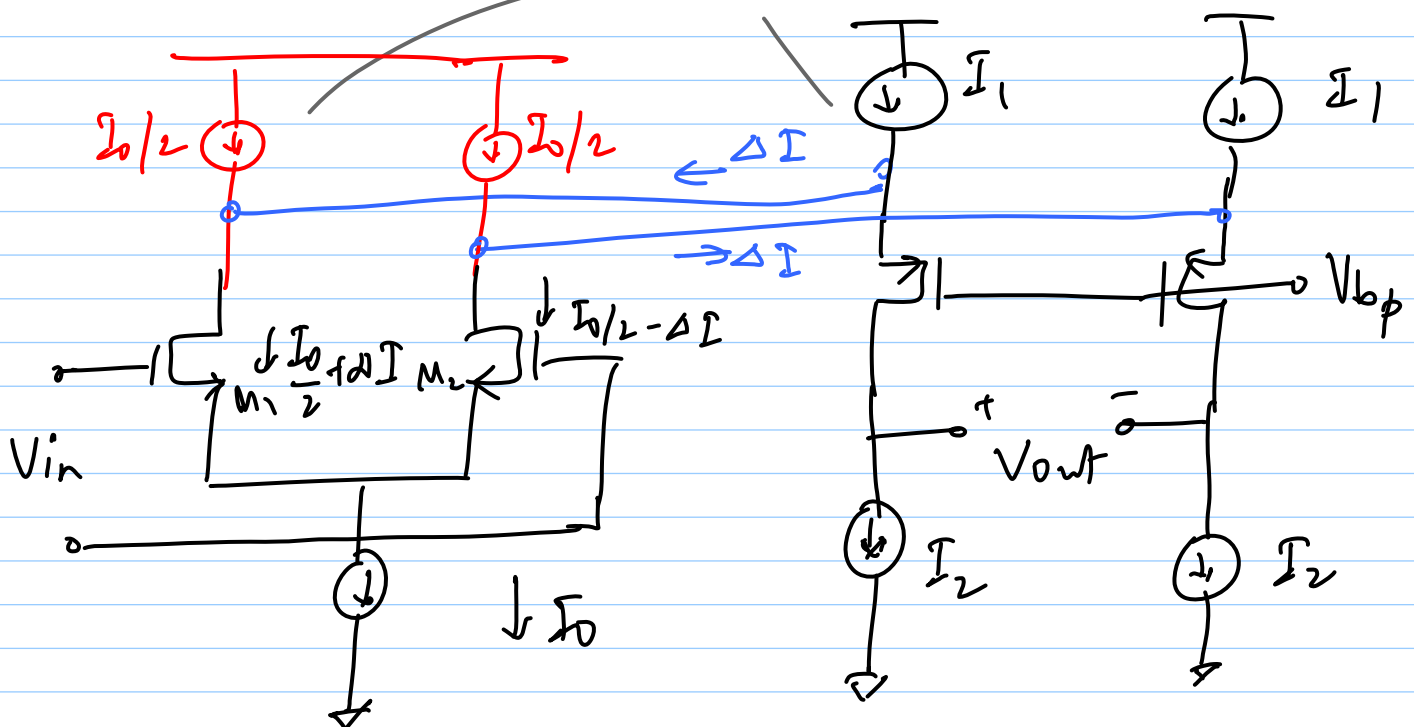In parallel
combine into one source
 $I \rightarrow I_0/2$



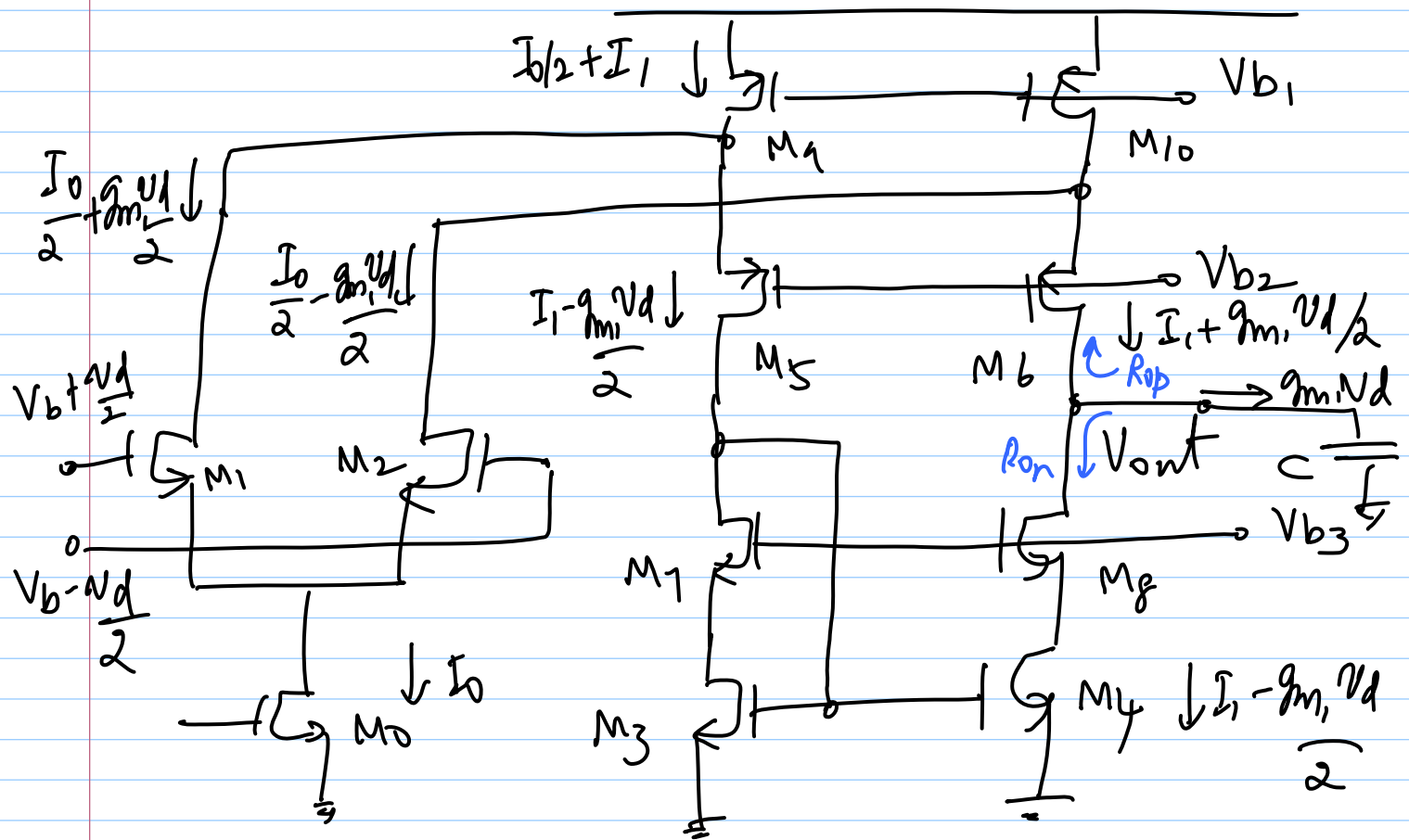

$$G_m \approx g_{m1}$$

$$R_{out} = R_{op} \parallel R_{on}$$

$$= \left(g_{m6} r_{o6} (r_{o10} \parallel r_{o2}) \right) \parallel g_{m8} r_{o8} r_{o4}$$

$$a_v = g_{m1} \cdot \left[\left\{ g_{m6} r_{o6} (r_{o10} \parallel r_{o2}) \right\} \parallel g_{m8} r_{o8} r_{o4} \right]$$

DC gain is slightly lower (extra term in cascode R_{out} term)

Advantage: swing limits are better

* V_o limits are not dependent on $V_{CM,in}$

* M_1 & M_2 can be biased independently

$$V_{DD} - V_{DSAT_{10}} - V_{DSAT_6} \geq V_o \geq V_{DSAT_4} + V_{DSAT_8}$$

1) DC gain

$$= g_{m1} \left[\left\{ g_{m_6} r_{o_6} (r_{o_{10}} \parallel r_{o_2}) \right\} \parallel g_{m_8} r_{o_8} r_{o_4} \right]$$


2) $UGF = \frac{g_{m1}}{C}$ (same as before)

3) N.D. poles

M_9 & M_{10} are probably larger

(more current) $\Rightarrow$ more cap @ p_1 & p_2

* same # of poles

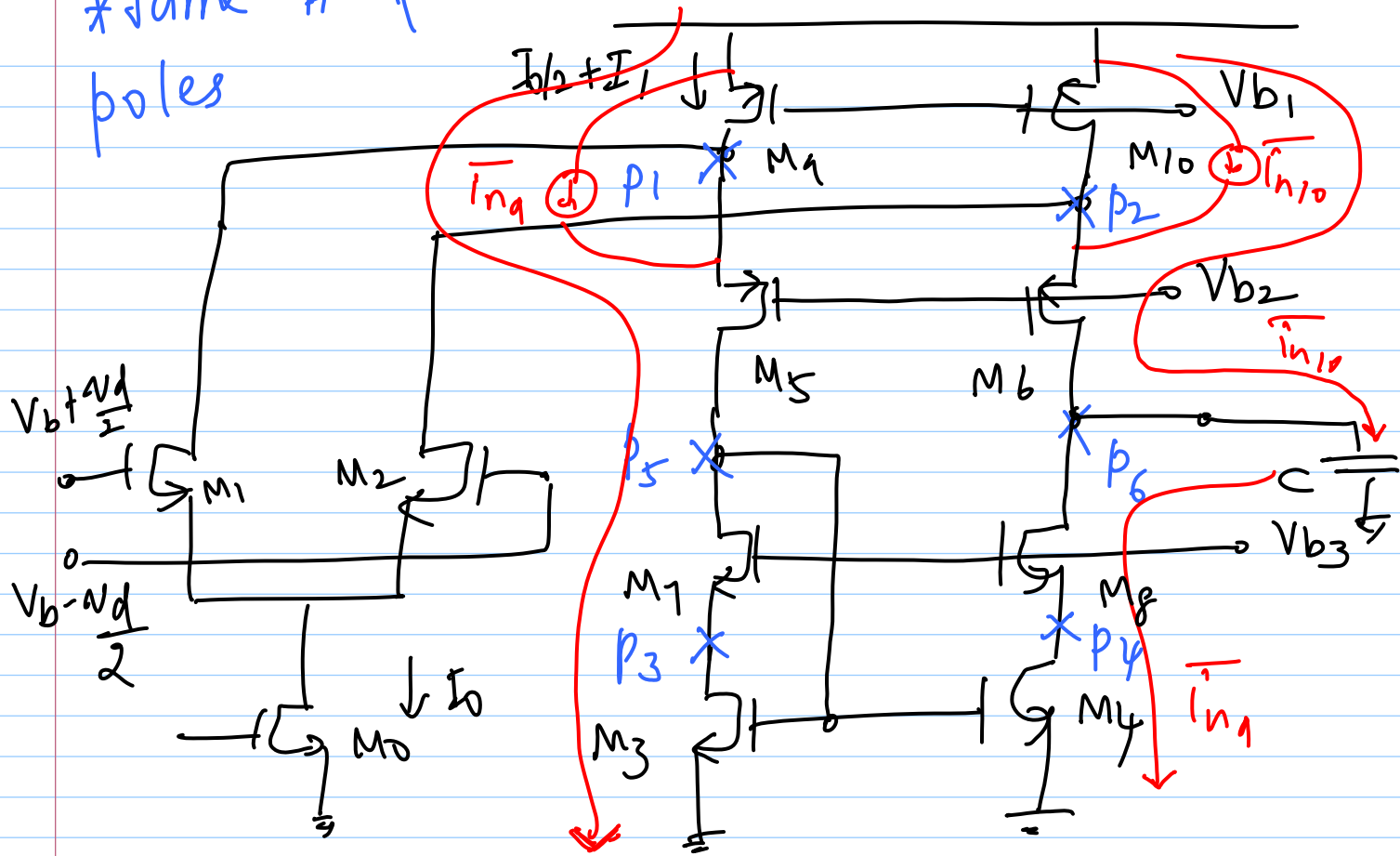

4) Noise

No noise from: M_5, M_6, M_7, M_8
(cascode)

noise from: $M_1, M_2, M_3, M_4, M_9, M_{10}$

$\Rightarrow$ larger than telescopic opamp

$$S_{out} = \frac{16kT}{3} (g_{m1} + g_{m3} + g_{m9})$$

telescopic

$\uparrow$ larger I
 $\Rightarrow$ larger noise

$$S_{i,in} = \frac{16 kT}{3 g_{m1}} \left(1 + \frac{g_{m3}}{g_{m1}} + \frac{g_{m9}}{g_{m1}} \right)$$

$$5) \sigma_{V_{os}}^2 = \sigma_{V_{T_{1,2}}}^2 + \sigma_{V_{T_{3,4}}} \cdot \left(\frac{g_{m3}}{g_{m1}} \right)^2 \\ + \sigma_{V_{T_{9,10}}} \cdot \left(\frac{g_{m9}}{g_{m1}} \right)^2$$

6) Output swing

$$V_{DD} - 2V_{DSAT} > V_o > V_{DSAT}$$