

1-3-12

Lec 24

7) Input CM range:

$$V_{min} = V_{GS1} + V_{DSAT0}$$


$$V_{max} = V_{b2} + V_{SG5} + V_{T1} \quad (\text{can be } > V_{DD})$$

8) Slew Rate


$$I = \text{smaller} \left(I_1, \frac{I_0}{2} \right)$$

$$SR = \min. \left(\frac{I_0}{C}, \frac{2I_1}{C} \right)$$
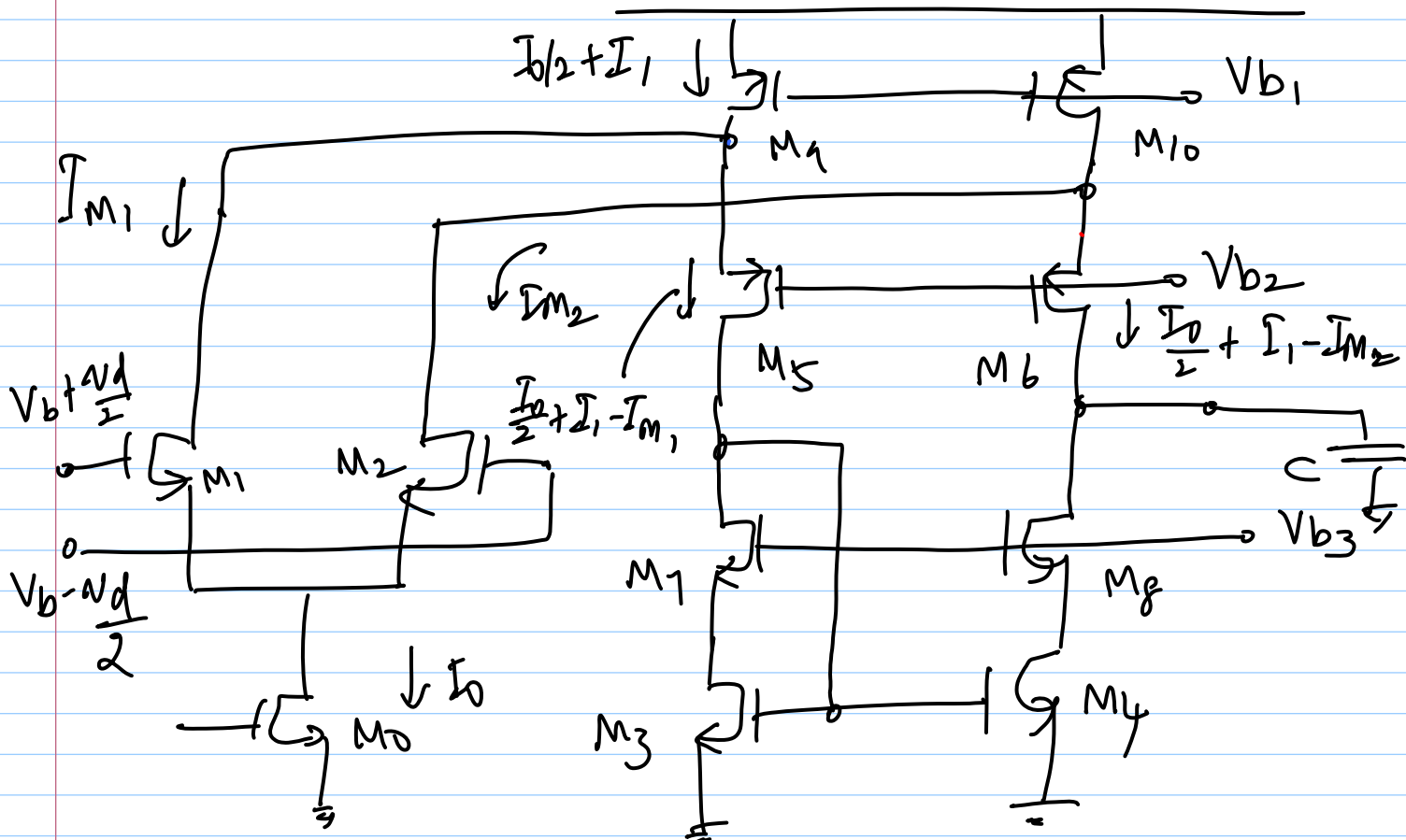
$$\text{ideal case} \Rightarrow I_1 = \frac{I_0}{2} \quad (\text{rest is wasted})$$



Trans impedance Topology (2-stage opamp)

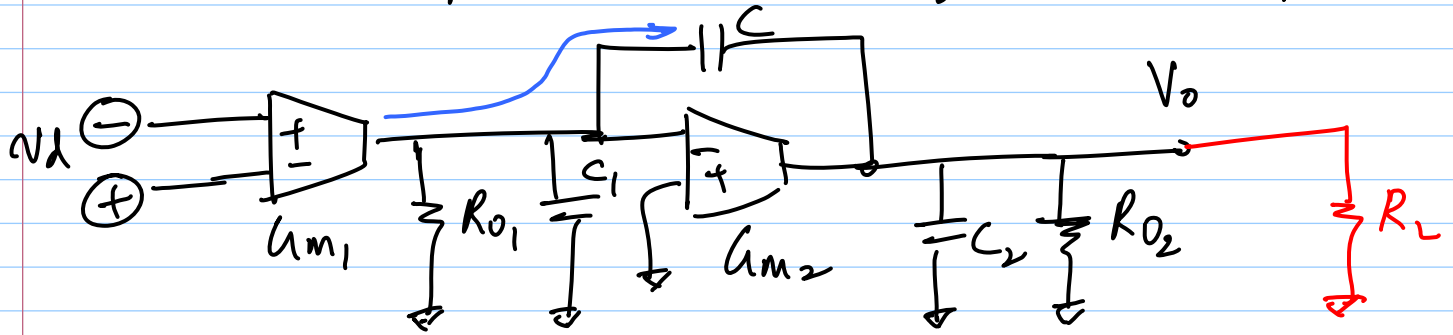

$$\left. \frac{V_o}{V_d} \right|_{DC} = G_{m1} R_{o1} \cdot G_{m2} R_{o2}$$

$$\left. \frac{V_o}{V_d} \right|_{DC} \approx \underbrace{G_{m1} R_{o1}}_{\text{boosts DC gain}} (G_{m2} R_L)$$

$\Rightarrow$ better than before

* Stage 1 DC gain is not changed
 $\rightarrow$ optimise stage 1 for DC gain

$\Rightarrow$ 2-stage opamp most common opamp

1) DC gain $A_0 = G_{m1} R_{o1} G_{m2} R_{o2}$

2) $V_o(s) \approx \frac{G_{m1}}{sC} \cdot V_i(s) \left\{ \begin{array}{l} \text{to a} \\ \text{first order} \end{array} \right\}$

$\Rightarrow \omega_u \approx \frac{G_{m1}}{C}$

2 poles, 1 zero

$$\frac{V_o}{V_i} = \frac{G_{m1}(G_{m2} - sC)}{\left\{ s^2(C_1C_2 + C_1C_2) + s(C(G_{m2} + G_{o1} + G_{o2}) + G_{o2}C_1 + G_{o1}C_2) + G_{o1}G_{o2} \right\}}$$

$$\left. \frac{V_o}{V_i} \right|_{DC} = \frac{G_{m1}G_{m2}}{G_{o1}G_{o2}} \quad \checkmark$$

$$z_1 = +\frac{G_{m2}}{C} \quad (\text{RHP zero})$$

$$ax^2 + bx + c = 0$$

If x_1 & x_2 (roots are far apart),

$$x_1 \approx -\frac{c}{b}; \quad x_2 = -\frac{b}{a}$$

$$x_1 \ll x_2 \quad \{p_1 \ll p_2\}$$


For an opamp, p_2 = dominant pole, p_1 = N.D. pole

$$p_1 \approx -\frac{c}{b} = -\frac{G_{o1}G_{o2}}{C(G_{m2} + G_{o1} + G_{o2}) + G_{o2}C_1 + G_{o1}C_2}$$

$$\approx - \frac{G_{o1}}{C \left(\frac{G_{m2}}{G_{o2}} + 1 + \frac{G_{o1}}{G_{o2}} \right) + C_1 + \frac{G_{o1} C_2}{G_{o2}}}$$

originally $\rightarrow \frac{G_{o1}}{C_1}$ Miller Effect

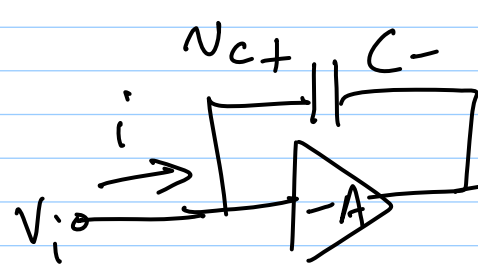now $\rightarrow C_{ap} = C \left(1 + \frac{G_{m2}}{G_{o2}} \right)$



$i = (A+1) \Delta C \cdot v_i$

$v_c = (A+1) v_i$

Other terms: * Non ideal G_m stages (G_{out} etc.)

* probably negligible compared with first terms

* this expression is approx. (quadratic solution)

as $C \uparrow \Rightarrow p_1 \downarrow$


$$p_1 \approx \frac{G_{o1}}{\text{eff. cap. across } G_{o1}}$$

$$p_2 \approx \frac{-b}{a} = - \frac{C(G_{m2} + G_{o1} + G_{o2}) + C_1 G_{o2} + C_2 G_{o1}}{C_1 C + C C_2 + C_1 C_2}$$

divide Nr. & Dr. by $(C + C_1)$


$$p_2 = - \frac{\frac{C}{C+C_1} G_{m2} + G_{o2} + G_{o1} \cdot \frac{C+C_2}{C+C_1}}{C_2 + \frac{C_1 C}{C+C_1}}$$

cap. clkt does look
like this @ o/p node

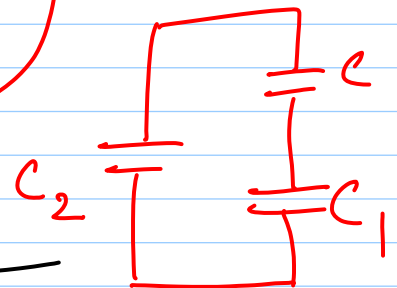

$G_{o2} \rightarrow$ directly @ o/p

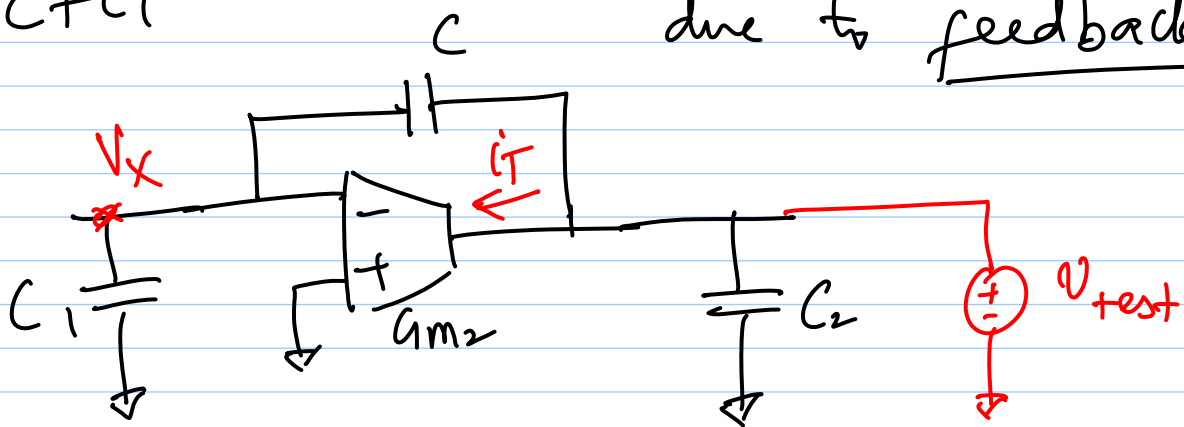$\frac{C}{C+C_1} G_{m2}$ is dominant term
due to feedback




$$V_x = \frac{C}{C+C_1} V_{test}$$

$$i_T = \frac{C}{C+C_1} V_{test} \cdot G_{m2}$$

$$G_{eff} = \frac{i_+}{v_{tot}} = \frac{C}{C+C_1} \cdot G_{m2}$$

Note:

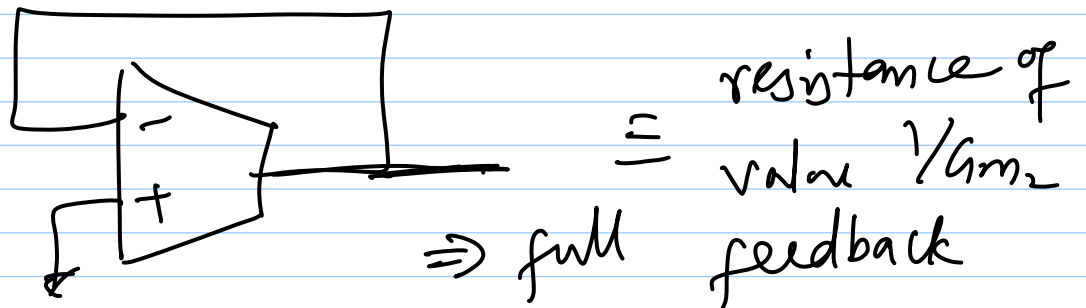


$$C=0, \text{ no f.b. } \Rightarrow G_{eff} = 0$$


G_{01} term $\Rightarrow$ because of finite G @ G_{m1} output in 11^k with C_1

If $C=0$, no zero,
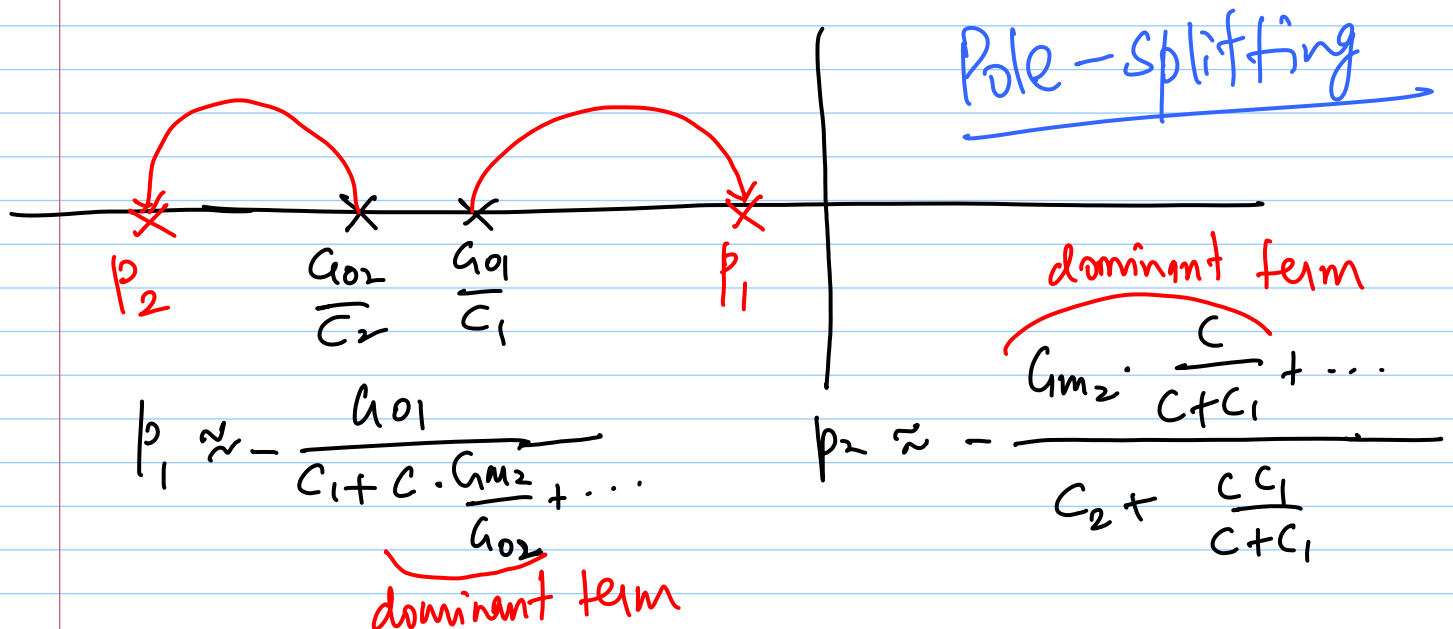
$$\text{poles @ } -\frac{G_{01}}{C_1} \text{ \& } -\frac{G_{02}}{C_2}$$



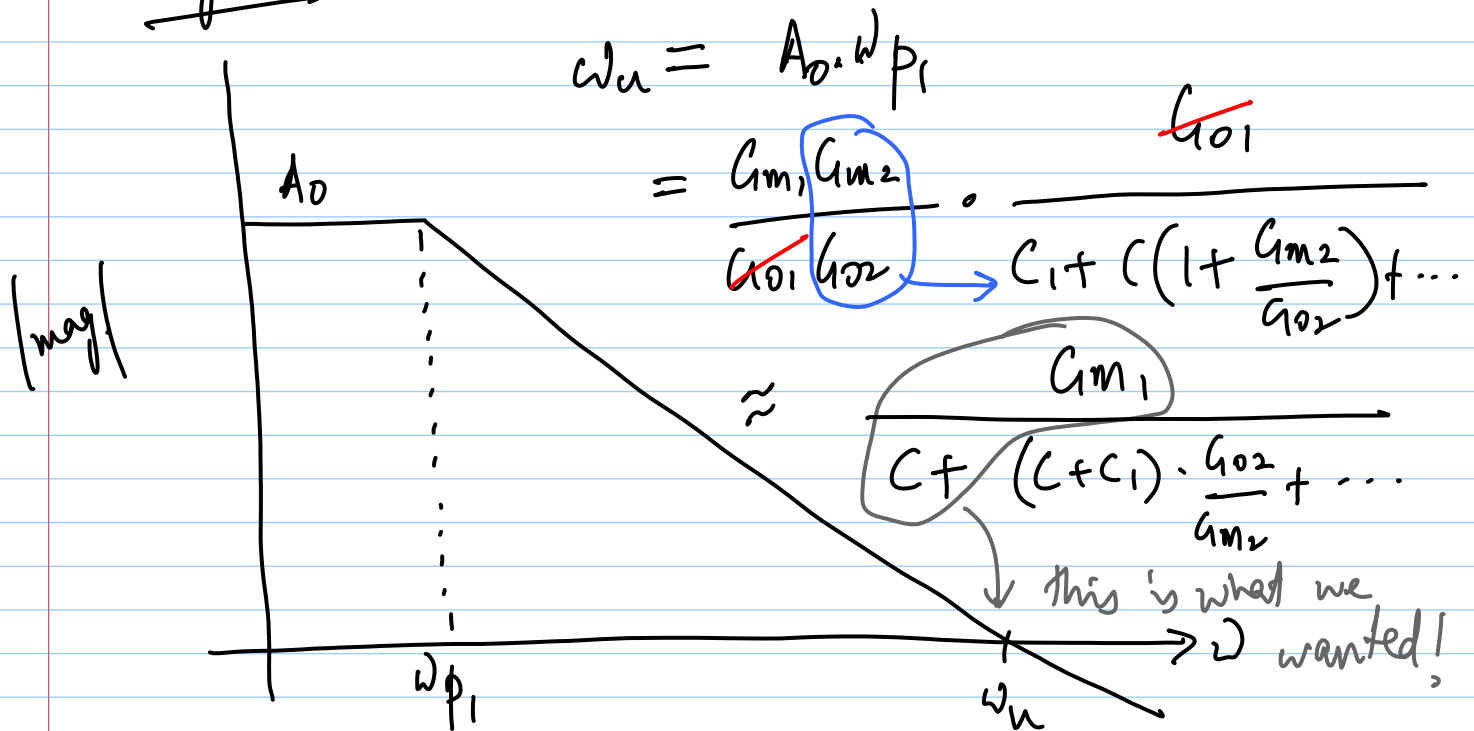Pole splitting is a feature of a coupled system.



Two-stage opamp

$$\omega_u = \frac{G_{m1}}{C}$$

$$z_1 = + \frac{G_{m2}}{C} \text{ (RHP)}$$

bad! phase lag

$$|p_1| \approx \frac{G_{o1}}{C_1 + C \left(\frac{G_{m2}}{G_{o1}} + 1 \right) + \dots} \text{ (LHP)}$$

$$|p_2| \approx \frac{G_{m2} \cdot \frac{C}{C + C_1} + G_{o2} + \dots}{C_2 + \frac{CC_1}{C + C_1}} \text{ (LHP)}$$

conditions:

$$|\omega_{p2}| > \omega_u$$

$$\phi_{UG} = \underbrace{\frac{-\pi}{2}}_{\omega_{p1} \text{ (Dominant pole)}} - \underbrace{\tan^{-1}\left(\frac{\omega_u}{\omega_{p2}}\right)}_{\omega_{p2}} - \underbrace{\tan^{-1}\left(\frac{G_{m1}}{G_{m2}}\right)}_{\omega_z \text{ (not good)}}$$

1) ω_z

$G_{m1} = G_{m2}$ is not good $\because$ zero already

gives -45° phase @ ω_u

$G_{m2} \gg G_{m1}$ is good (3-4x)

$$G_{m2} < G_{m1} \Rightarrow \text{unstable}$$

2) ω_{p2}

$\frac{\omega_u}{\omega_{p2}}$ should be small $\left\{ \omega_{p2} \gg \omega_u \right\}$

$\Rightarrow G_{m2}$ should be large

$\therefore$ Given ω_u (i.e. $G_{m1} \& c$), to improve PM, increasing G_{m2} is the only option

$\uparrow W \Rightarrow C_1, C_2 \uparrow \Rightarrow$ affects cap (denominator) too

$\therefore \uparrow$ current (while keeping W small)

$\Rightarrow V_{ov} \downarrow \Rightarrow$ swing limits $\downarrow$

* You want $C \gg C_1, C_2$, so choose G_{m1} & C carefully so that

$$\omega_u = \frac{G_{m1}}{C}$$

* What to do about the zero?