

6-3-12

Lec -25

Telescopic opamp Dis cussion

Design a telescopic opamp w/ the following specs:


$V_{DD} = 3V$; Output swing = $2V$ (pk-pk)


Voltage gain = 2000 ; Power diss. = $10mW$

	NMOS	PMOS	no backgate effect
μC_{ox}	$60 \mu A/V^2$	$30 \mu A/V^2$	
$ V_T $	$0.7V$	$0.7V$	
$L_{min.}$	$0.5 \mu m$	$0.5 \mu m$	
λ	$0.1 V^{-1}$	$0.2 V^{-1}$	

* Do not setup equations in 'n' variables

* There is no unique solution

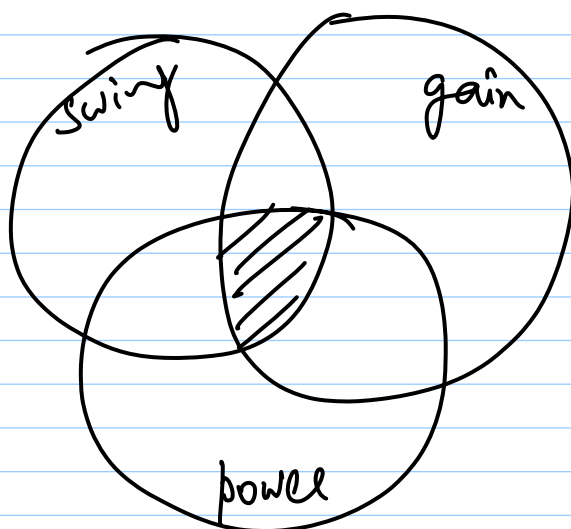

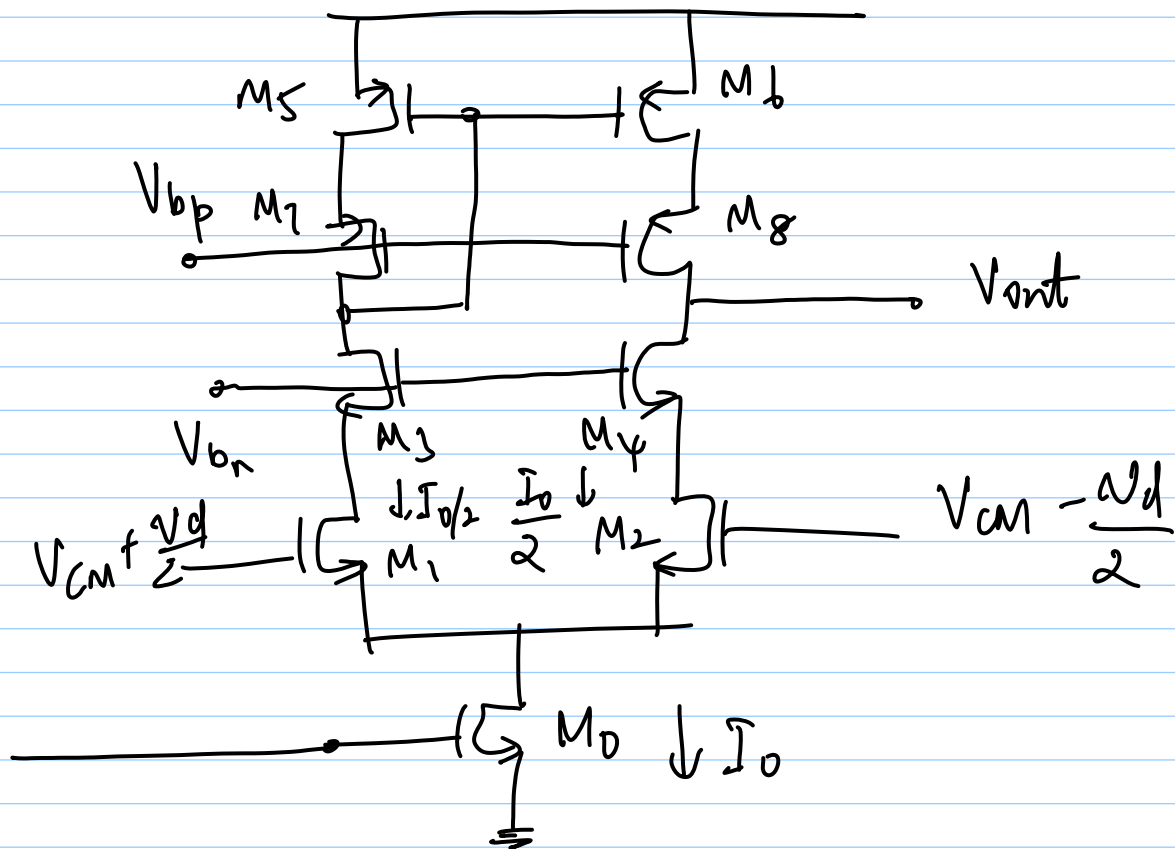

Simplify : assume $M_1 - M_4$ identical
 $M_5 - M_8$ "

$$V_{CM_{min}} = V_{GS1} + V_{DSAT2}$$

$$V_{bn} = V_{DSAT_0} + V_{DS1} + V_{as3}$$

$$V_{b_n}(\text{min.}) = V_{DSAT_0} + V_T + 2V_{DSAT_n}$$
$$= V_T + 3V_{DSAT_n}$$

$$V_{out, max.} = V_{DD} - 2V_{DSATp}$$

$$V_{out, min.} = V_{bn} - V_T = 3V_{DSATn}$$

say, $V_{DSATp} = 250\text{mV}$

$\Rightarrow V_{out\ max.} = 2.5\text{V}$

say, $V_{DSATn} = 166.67\text{mV}$

$\Rightarrow V_{out\ (min.)} = 0.5\text{V}$

2V
pk-pk
swing

$P_d = 10\text{mW} \Rightarrow I_{tot.} = 3.33\text{mA}$

say $I_0 = 3\text{mA}$, $330\mu\text{A}$ for bias

$M_0 \Rightarrow V_{DSAT_0} = \sqrt{\frac{2 I_0}{\mu_n C_{ox} \left(\frac{W}{L}\right)_0}} \Rightarrow \left(\frac{W}{L}\right)_0 = 3600 = \frac{1800\mu\text{m}}{0.5\mu\text{m}}$

$\left(\frac{W}{L}\right)_{1-4} = \frac{900\mu\text{m}}{0.5\mu\text{m}}$

$\left(\frac{W}{L}\right)_{5-8} = 1600 = \frac{800\mu\text{m}}{0.5\mu\text{m}}$

$r_{dsn} = \frac{1}{\lambda_n I_{Dn}} = 6.66\text{k}\Omega$

$r_{dsp} = \frac{1}{\lambda_p I_{Dp}} = 3.33\text{k}\Omega$

$g_{mn} = \mu_n C_{ox} \left(\frac{W}{L}\right)_n \cdot V_{DSATn} = 18e^{-3}\text{S}$

$$g_{mp} = \mu_{plox} \left(\frac{W}{L} \right)_p \cdot V_{DSATp} = 12 e^{-3} S$$

$$\begin{aligned} A_0 &= g_{mn} \left[g_{mn} r_{dsn}^2 \parallel g_{mp} \cdot r_{dsp}^2 \right] \\ &= 18 e^{-3} \left[18 e^{-3} \cdot (6.66 k)^2 \parallel 12 e^{-3} (3.33 k)^2 \right] \\ &= 18 e^{-3} \left[798.4 e^3 \parallel 133.07 e^3 \right] \\ &= \underline{\underline{2053}} \text{ meets spec.} \end{aligned}$$

If you need 2x gain (e.g. 4000)

$$1) \frac{\Delta L}{L} = \lambda V_{DS} \Rightarrow \lambda L \approx \text{constant}$$

$$\Rightarrow \uparrow L \Rightarrow \downarrow \lambda \Rightarrow \uparrow r_{ds}$$

keep (W/L) constant

here $\uparrow r_{dsp}$ is more important

$$\text{e.g. } r_{dsp} = 798.4 e^3 = r_{dsn}$$

$$\Rightarrow A_0 = 7186$$

$$2) \downarrow I_0 \Rightarrow \begin{matrix} g_m \uparrow \text{ as } \sqrt{I_0} \\ r_{ds} \downarrow \text{ as } 1/I_0 \end{matrix} A_0 \uparrow$$

but $\omega_n \downarrow$ & $SR \downarrow$

here for 4X gain $\Rightarrow \downarrow I$ by 16X

$$3) \uparrow g_{mn} \Rightarrow \uparrow \left(\frac{\omega}{L}\right)_n$$

here $\uparrow \left(\frac{\omega}{L}\right)_n$ by 16X

$\Rightarrow$ non-dominant poles move in

2-stage opamp

$$(p_2) \approx \frac{g_{m2} \cdot \frac{C}{C+C_1} + \dots}{C_2 + \frac{CC_1}{C+C_1}} \approx \frac{g_{m2}}{C_2}$$

(LHP)


if $C_2 \gg C_1$ & $C \gg C_2, C_1$

For 45° PM, $p_2 = a_0 \cdot p_1 = \omega_n$

$$\frac{g_{m2}}{C_2} = \left(\frac{g_{m1}}{C_{01}} \cdot \frac{g_{m2}}{C_{02}} \right) \cdot \frac{C_{01} C_{02}}{g_{m2} C}$$

$$\Rightarrow C = \left(g_{m1} / g_{m2} \right) \cdot C_2$$

RC - pole splitting compensation

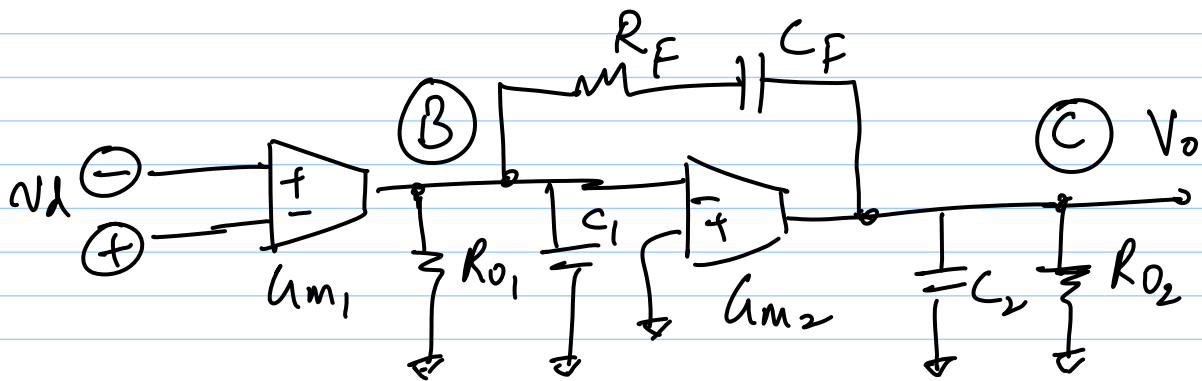

Basic idea: @ high freq., develop a small-signal voltage across R_F that cancels small-signal voltage @ output

after long analysis:

$$p_1 = \frac{G_{o1} \cdot G_{o2}}{G_{m2} \cdot C_F} ;$$

$$p_2 = \frac{G_{m2} C_F}{C_1 C_2 + C_F (C_1 + C_2)} \approx \frac{G_{m2}}{G_{o2}} \cdot \frac{G_{o2}}{C_2}$$

$$p_3 = \frac{1}{R_F C_1} ; \quad z_1 = \frac{1}{\left(\frac{C_F}{G_{m2}} - R_F C_F \right)}$$

case(i) move Z_1 to infinity

$$\Rightarrow R_F = \frac{1}{G_{m2}}$$

$$p_1 \approx \frac{G_{o1} G_{o2}}{G_{m2} C_F} ; p_2 \approx \frac{G_{m2}}{G_{o2}} \cdot \frac{G_{o2}}{C_2}$$

$$p_3 \approx \frac{1}{R_F C_1} = \frac{G_{m2}}{C_1} \approx p_2 \cdot \left(\frac{C_2}{C_1} \right) \gg 1$$

due to
load cap

