

7-3-12

Lec 26

For $\geq 45^\circ$ PM, (neglect p_3)

$$p_2 \geq -\omega_0 p_1$$


$$\Rightarrow C_F \geq \frac{G_{m1}}{G_{m2}} C_2$$

same
value
as simple
compensation

case (ii) $z_1 = \frac{1}{C_F/G_{m2} - R_F C_F}$

If $R_F > \frac{1}{G_{m2}}$, zero moves into LHP

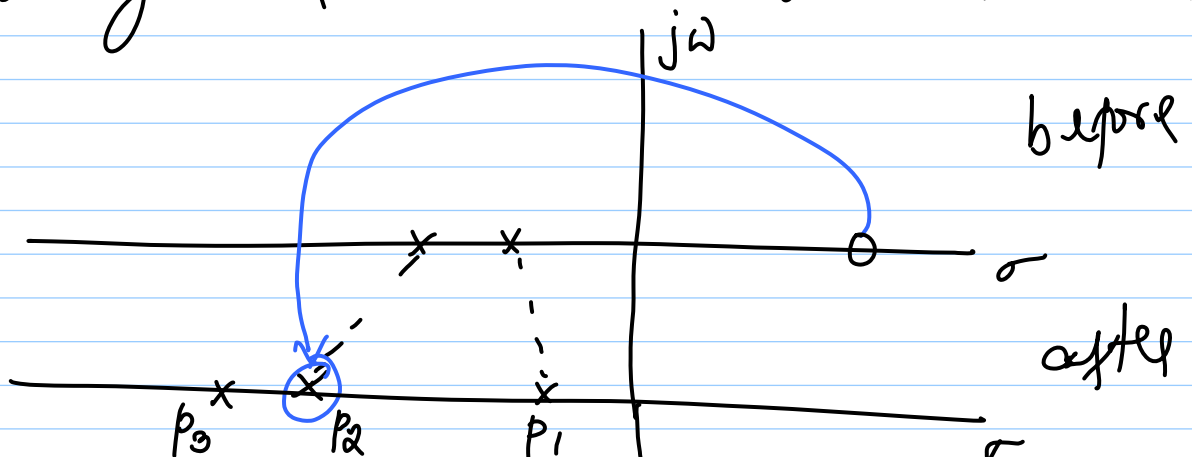$\Rightarrow$ bring z_1 around to cancel p_2



$$z_1 = p_2 \Rightarrow R_F = \frac{1}{g_{m2}} \left(\frac{C_F + C_2}{C_F} \right)$$

for $PM > 45^\circ$, $p_3 \geq a_0 p_1$

$$\Rightarrow C_F \geq \frac{g_{m1}}{g_{m2}} \cdot C_1 \cdot \left(\frac{C_F + C_2}{C_F} \right)$$

Solve quadratic in C_F

$$\Rightarrow C_F \approx \sqrt{\frac{g_{m1}}{g_{m2}} \cdot C_1 \cdot C_2}$$

$$C_F \approx \underbrace{\frac{g_{m1}}{g_{m2}} \cdot C_2}_{C_F(z_1 = \infty)} \cdot \underbrace{\sqrt{\frac{g_{m2}}{g_{m1}}}}_{\approx 1} \cdot \underbrace{\sqrt{\frac{C_1}{C_2}}}_{< 1}$$

Smaller C_F than $z_1 = \infty$

* How do you guarantee exact cancellation?


p_2 & z_1 may be below ω_u

* If they don't cancel exactly $\Rightarrow$ pole-zero doublet...


* over PVT variations, $1/G_{m2}$ & R_F vary differently.

→ We want R_F to track $1/G_{m2}$


Ckt implementation of blocks

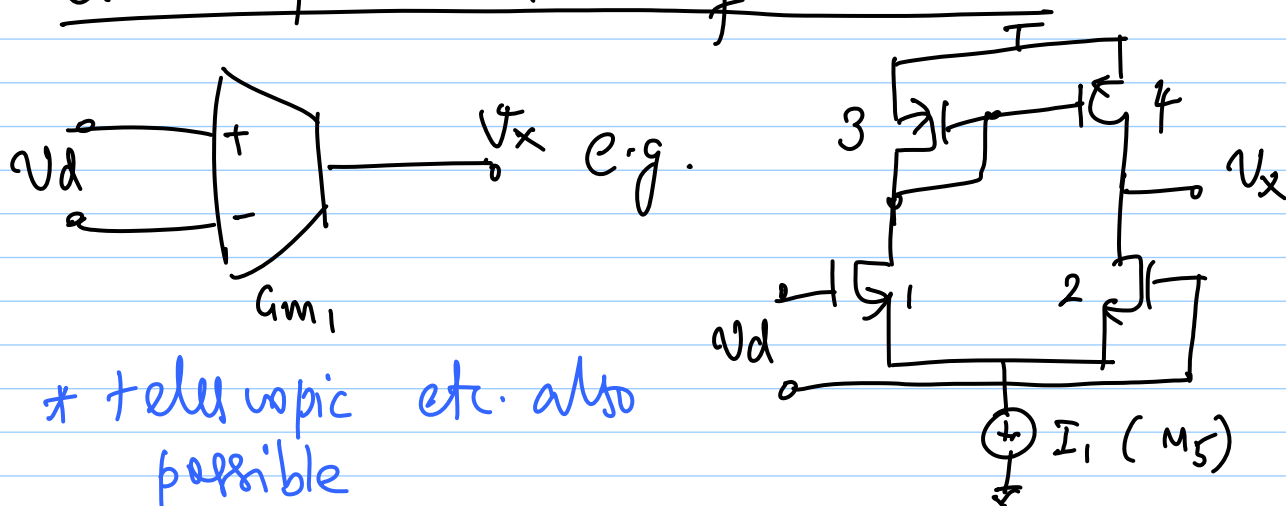


* telescopic etc. also possible

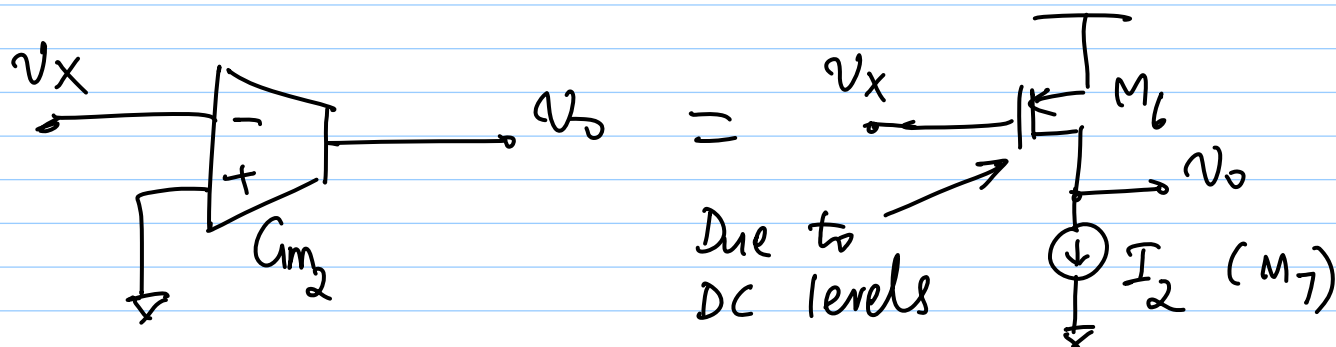

2-stage opamp

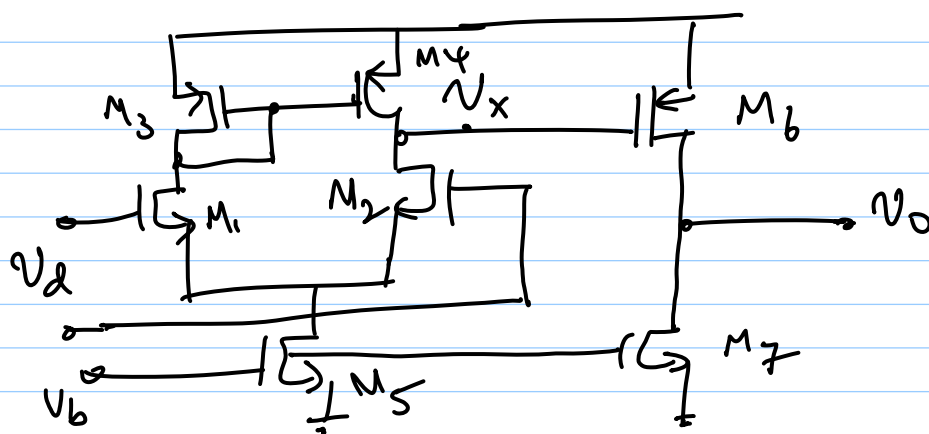

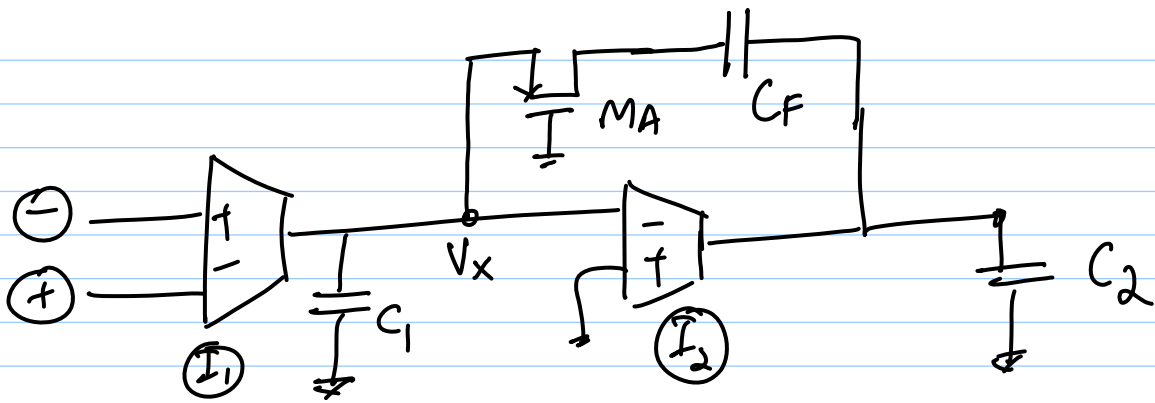

* Use MOSFET as a resistor

→ PMOS, NMOS, T-gate

→ Use PMOS $\because$ G_{m1} is a PMOS

→ MA operates in triode region

If I_2 (bias current through G_{m2}) $\uparrow$

due to PVT variations

$$p_2 = \frac{G_{m2}}{C_2} \uparrow$$


$$z_1 \propto \frac{1}{R_F C_F} \quad \text{as } I_2 \uparrow \Rightarrow V_x \downarrow \Rightarrow R_F \uparrow$$

$$\Rightarrow |z_1| \downarrow$$

$\therefore z_1$ changes in the wrong direction

Tracking Compensation

1) MOS in triode region

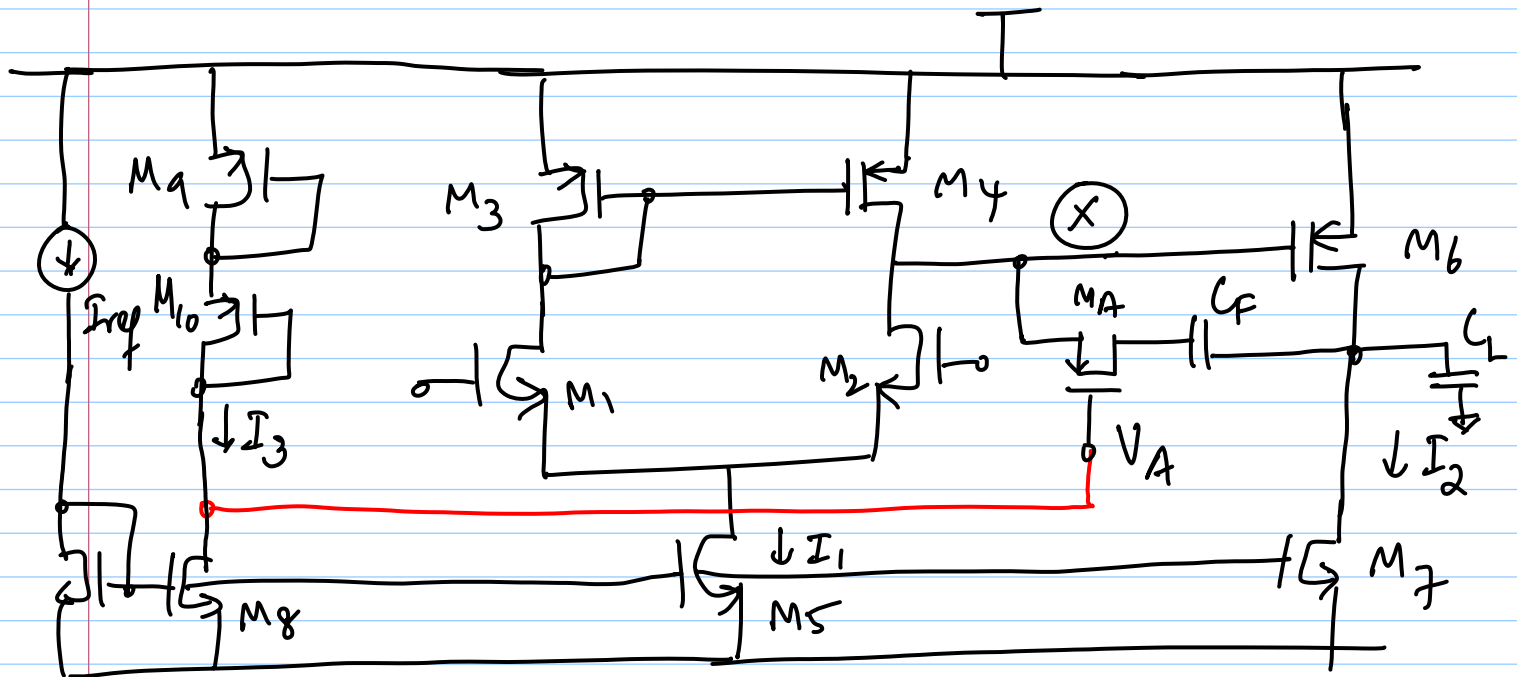

* For two identically biased transistors

$$\rightarrow \text{sat: } g_m = \mu C_{ox} \left(\frac{W}{L} \right) (V_{ds} - |V_{T1}|)$$

$$\rightarrow \text{non-sat: } g_{ds} = \mu C_{ox} \left(\frac{W}{L} \right) (V_{ds} - |V_{T1}|)$$

We want $R_F = \frac{1}{g_{m6}} \left(1 + \frac{C_L}{C_F} \right)$

$$\frac{1}{\mu C_{ox} \left(\frac{W}{L} \right)_A (V_{dsA} - |V_{T1}|)} = \frac{1}{\mu C_{ox} \left(\frac{W}{L} \right)_6 (V_{ds6} - |V_{T1}|)} \cdot \left(1 + \frac{C_L}{C_F} \right)$$

$$\begin{aligned}
 V_{SGA} - |V_T| &= V_X - V_A - |V_T| \\
 &= (V_{DD} - V_{SGb}) - (V_{DD} - V_{SGq} - V_{SG10}) \\
 &\quad - |V_T|
 \end{aligned}$$

$$= V_{SG10} + (V_{SGq} - V_{SGb}) - |V_T|$$

If M_q & M_b are identically biased,

$$V_{SGq} = V_{SGb}$$

$$\Rightarrow V_{SGA} - |V_T| = V_{SG10} - |V_T|$$

$$\Rightarrow \left(\frac{W}{L}\right)_A [V_{SG10} - |V_T|] = \left(\frac{W}{L}\right)_b (V_{SGb} - |V_T|) \cdot \frac{C_F}{C_L + C_F}$$

$$\left(\frac{W}{L}\right)_A = \left(\frac{W}{L}\right)_b \cdot \frac{V_{SGb} - |V_T|}{V_{SG10} - |V_T|} \cdot \frac{C_F}{C_L + C_F}$$

$$= \left(\frac{W}{L}\right)_b \frac{\sqrt{\frac{2I_2}{\mu_p C_{ox} (W/L)_b}}}{\sqrt{\frac{2I_3}{\mu_p C_{ox} (W/L)_{10}}}} \cdot \frac{C_F}{C_L + C_F}$$

$$\left(\frac{W}{L}\right)_A = \left[\left(\frac{W}{L}\right)_i \left(\frac{W}{L}\right)_{io} \frac{I_2}{I_3} \right]^{1/2} \cdot \frac{C_F}{C_L + C_F}$$