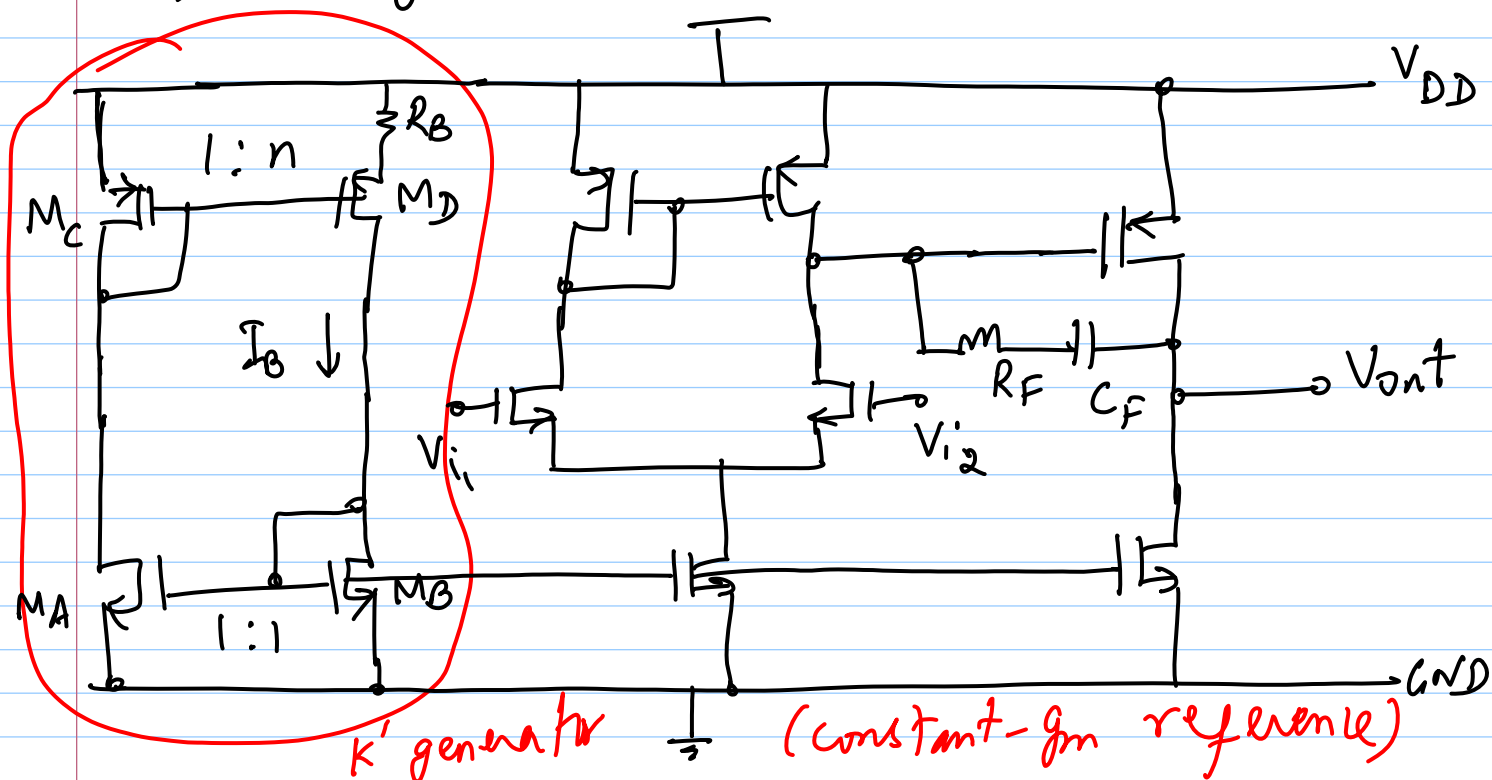


13-3-2022

Lec 27

2) Using a real resistor



* requires a startup ckt (all $I=0$ is a stable state)

$$V_{SAC} = V_{SGD} + I_B R_B$$

$$\Rightarrow V_{ovc} = V_{ovD} + I_B R_B \quad \text{--- (1)}$$

$$(W/L)_D = n (W/L)_C \Rightarrow V_{ovD} = \frac{V_{ovc}}{\sqrt{n}}$$

$$\text{we also know } g_m = \frac{2I_D}{V_{ov}}$$

$$\therefore (1) \Rightarrow V_{ovc} = \frac{V_{ovc}}{\sqrt{n}} + I_B R_B$$

$$\Rightarrow \frac{2I_B}{g_{m_c}} = \frac{2I_B}{\sqrt{n} g_{m_c}} + I_B R_B$$

$$\Rightarrow g_{m_c} = \frac{2(1 - 1/\sqrt{n})}{R_B}$$

$$\sqrt{2k_p' \left(\frac{W}{L}\right)_c \cdot I_B} = \frac{2(1 - 1/\sqrt{n})}{R_B}$$

$$I_B = \frac{2}{k_p' R_B^2} \left(\frac{1}{\sqrt{(W/L)_c}} - \frac{1}{\sqrt{(W/L)_D}} \right)^2$$

$$= \frac{2}{k_p' R_B^2} \cdot \alpha$$

* I_B is mirrored into opamp 1st & 2nd stages

$$I_2 = m I_B$$

$$g_{m_6} = \sqrt{2k_p' (W/L)_6 I_2}$$

$$= \sqrt{2k_p' (W/L)_6 \cdot m I_B}$$

$$= \sqrt{2k_p' (W/L)_6 \cdot m \cdot \frac{2}{k_p' \cdot R_B^2} \cdot \alpha} = \frac{\beta}{R_B}$$


For accurate pole-zero cancellation,
we want

$$R_F = \frac{1}{g_{m6}} \left(1 + \frac{C_L}{C_F} \right) = \frac{R_B}{\beta} \left(1 + \frac{C_L}{C_F} \right)$$

$$\Rightarrow \frac{R_F}{R_B} = \frac{1}{\beta} \left(1 + \frac{C_L}{C_F} \right)$$

* R_B & R_F are of same type
 $\Rightarrow$ very well controlled //

Design Example - pole-splitting comp.

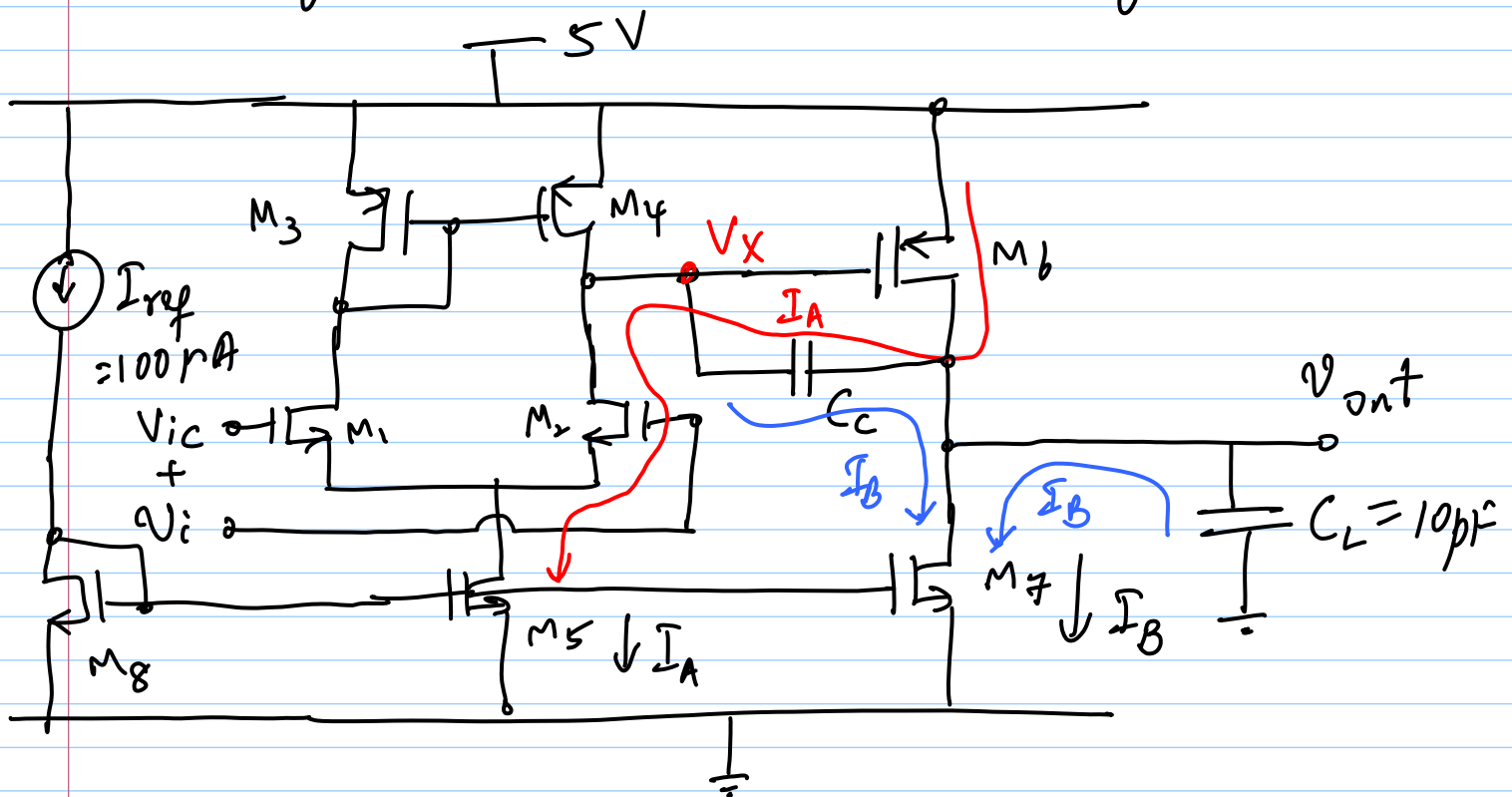

$$\text{Specs} \begin{cases} \overbrace{a_0 \geq 80 \text{ dB}}^{\text{DC gain}} ; f_u > 5 \text{ MHz} ; V_{o \text{ p-p}} = 4 \text{ V} \\ SR \geq 10 \text{ V}/\mu\text{s} ; \text{phase margin} = 60^\circ \end{cases}$$

$$V_{DD} = 5 \text{ V} ; C_L = 10 \text{ pF}$$

$$\mu_n \epsilon_{ox} = 50 \mu\text{A}/\text{V}^2 ; \mu_p \epsilon_{ox} = 25 \mu\text{A}/\text{V}^2$$

$$V_{TN} = |V_{TP}| = 1.0 \text{ V} ; L_{\min} = 2 \mu\text{m}$$

$$(\lambda L)_n = 0.04 \text{ mm/V} ; (\lambda L)_p = 0.1 \text{ mm/V}$$

$$G_{m1} = g_{m1} ; G_{m2} = g_{m2}$$

$$1) \underline{60^\circ \text{ PM}} : \text{other p/z are } > 10\omega_u$$

$$\omega_z = \frac{g_{m6}}{C_c} ; \omega_u = \frac{g_{m1}}{C_c}$$

$$\text{we want } \omega_z \geq 10 \cdot \omega_u \Rightarrow g_{m6} \geq 10 g_{m1}$$

$$C_c \geq 2.2 \left(\frac{g_{m1}}{g_{m6}} \right) \cdot C_L$$

$$\underline{\text{choose } C_c \approx 0.25 C_L}$$

2) Slew rate - decides I_A & I_B

(i) Input stage limited SR (-)

Since g_{m1} is very large,
 $V_x \sim$ virtual ground

$$\Rightarrow I_A = C_c \frac{dV_o}{dt} \Rightarrow \frac{dV_o}{dt} = SR = \frac{I_A}{C_c}$$

$$\frac{I_A}{C_c} \geq 10 \text{ V}/\mu\text{s} \Rightarrow I_A \geq 25 \mu\text{A}$$

(ii) Output stage limited SR (-)

$$I_B = (C_c + C_L) \frac{dV_o}{dt}$$

$$\Rightarrow \frac{dV_o}{dt} = SR = \frac{I_B}{C_c + C_L} \geq 10 \text{ V}/\mu\text{s}$$

$$\Rightarrow I_B \geq 125 \mu\text{A}$$

2) Output swing - decides (W/L) ratios

$$V_{out} \geq 4 \text{ V}_{p-p} \Rightarrow V_{DSAT6} \leq 0.5 \text{ V}$$

$$V_{DSAT7} \leq 0.5 \text{ V}$$

to minimize area, choose

$$V_{DSAT6} = V_{DSAT7} = 0.5V$$

$$= V_{DSAT5} = V_{DSAT8}$$

$$I_7 = \frac{K_n'}{2} \left(\frac{W}{L}\right)_7 (V_{in7} - V_T)^2$$

$$\Rightarrow \left(\frac{W}{L}\right)_7 = 20$$

$$I_5 = 25\mu A \Rightarrow (W/L)_5 = 4$$

$$I_8 = 100\mu A \Rightarrow (W/L)_8 = 16$$

$$I_6 = 125\mu A \Rightarrow (W/L)_6 = 40$$

$$I_3 = I_4 = I_A/2 = 12.5\mu A$$

$$\Rightarrow (W/L)_3 = (W/L)_4 = 4$$

3) W_u (VGF) - sets input stage (W/L)

$$W_u \approx \frac{g_{m1}}{C_c} \geq 5 \text{ MHz} \times 2\pi$$

$$\Rightarrow g_{m1} \geq 78.5\mu S$$

$$g_{m1} = \sqrt{2k_n' \left(\frac{W}{L}\right)_1 \left(I_A/2\right)}$$

$$\Rightarrow \left(\frac{W}{L}\right)_1 = 4.93$$

$$\text{choose } \left(\frac{W}{L}\right)_{1,2} = 5$$

4) DC gain - devices lengths

$$a_0 = a_1 \cdot a_2$$

$$= \frac{g_{m1}}{g_{ds2} + g_{ds4}} \cdot \frac{g_{m2}}{g_{ds6} + g_{ds7}}$$

$$a_1 = \frac{g_{m1}}{g_{ds2} + g_{ds4}} = \frac{\sqrt{K_n' (W/L)_1}}{(\lambda_2 + \lambda_4)} \cdot \frac{1}{\sqrt{\frac{I_A}{2}}}$$

$$= \frac{6.32}{\lambda_2 + \lambda_4}$$

$$a_2 = \frac{g_{m2}}{g_{ds6} + g_{ds7}} = \frac{\sqrt{K_p' (W/L)_2}}{\lambda_6 + \lambda_7} \cdot \frac{1}{\sqrt{I_B}}$$

$$= \frac{4.00}{\lambda_6 + \lambda_7}$$

Let us choose all λ 's to be equal

$$a_0 = \frac{25.28}{4\lambda^2} = 10,000$$

$$\Rightarrow \lambda = 2.514 \times 10^{-2} \text{ V}^{-1}$$