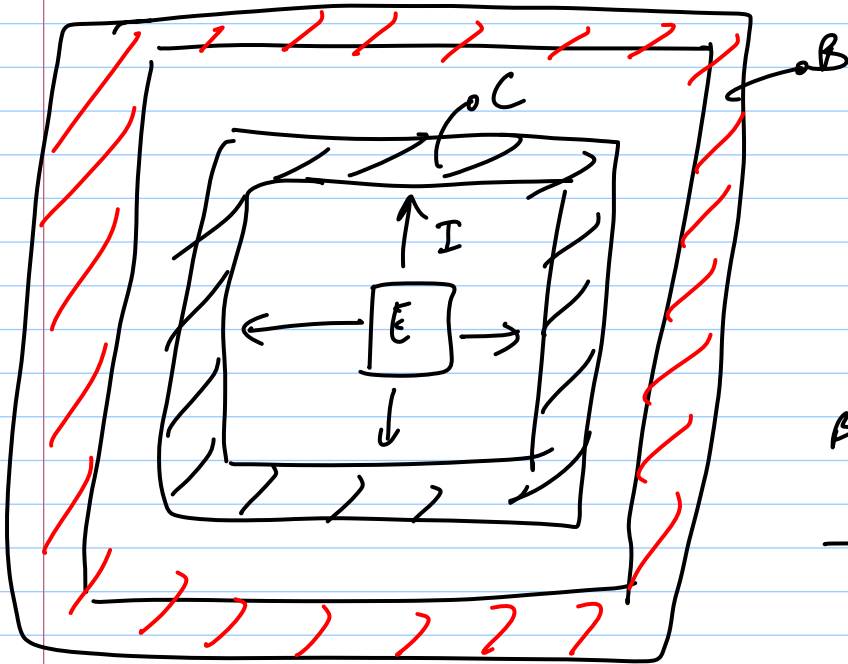



15-3-12

Lec 29

lateral pnp layout



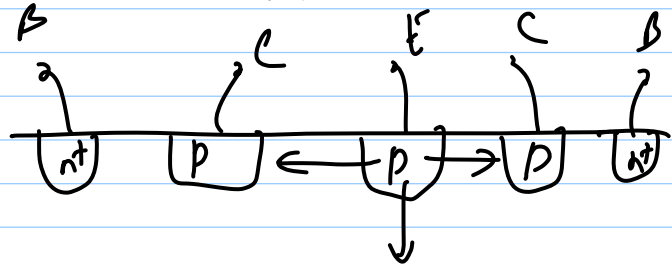'don't' layout
 $\Rightarrow$ larger β
only vertical
component of I_E
is lost




741 opamp

- * stand-alone opamp
- * internally compensated
- * simple ckt, small area
- * large gain, good CM & DM voltage ranges
- * Dual supply ($+V_{CC}$, $-V_{EE}$)
- * Differential input, SE o/p
- * high R_{in}

- * gain in input stage
→ noise & offset voltage of later stages is reduced
- * large gain from second stage
- * output stage that can drive large loads (low R_{out})

Evolution of 741 Input stage

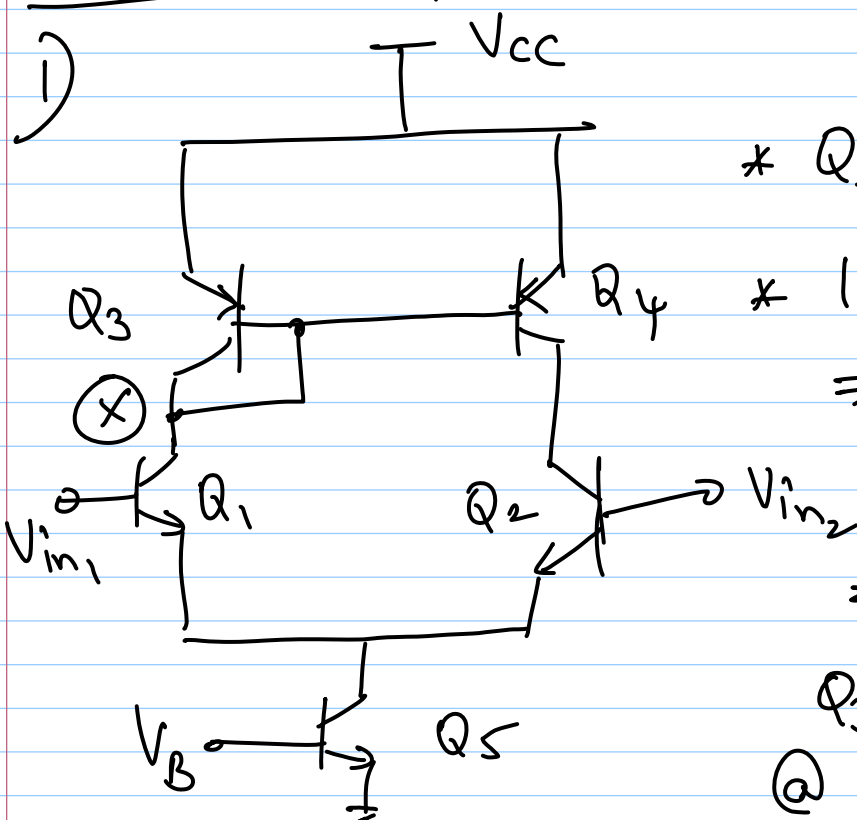

* Q_3, Q_4 - diff. to $\pm E$

* lat. prop's are slow

$\Rightarrow C_B = \tau_F \cdot g_m$ is large

$\Rightarrow C_{B3} + C_{B4}$ large


Q_3, Q_4 to be slow

@ node (X) -

key point

- * pnp - o/c for dc bias & dc level shifting
 - too slow for use in signal path (CE config.)

2) Use npn inputs & npn mirror stages

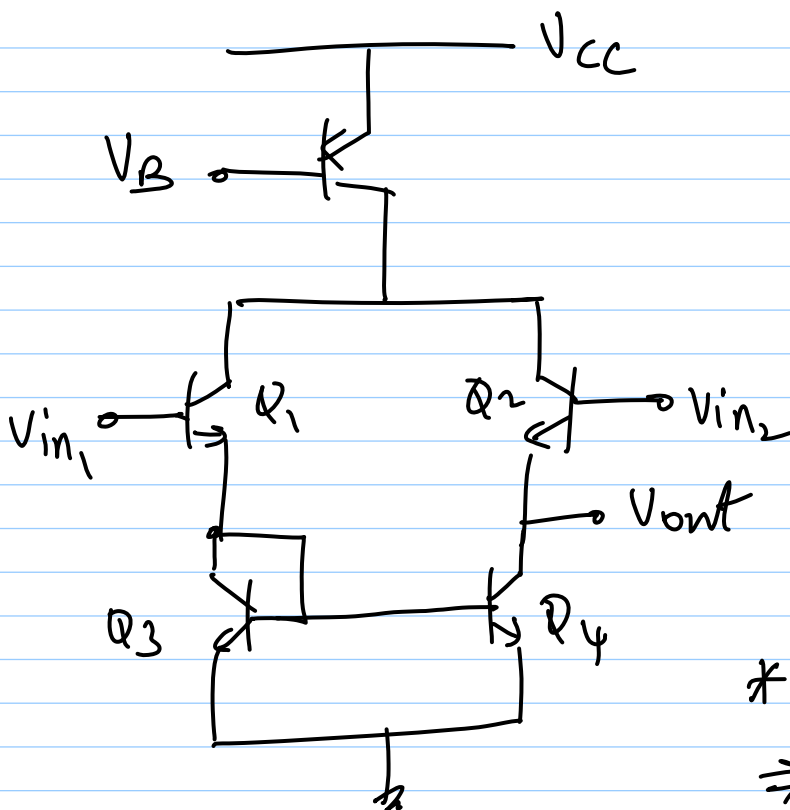


* all devices in signal path are npn

$$* V_{in1} = V_{BE3} + V_{BE1} \approx 1.4V$$

- no input CM range!

$$* r_{out} = low$$
$$\Rightarrow gain = low$$

3)

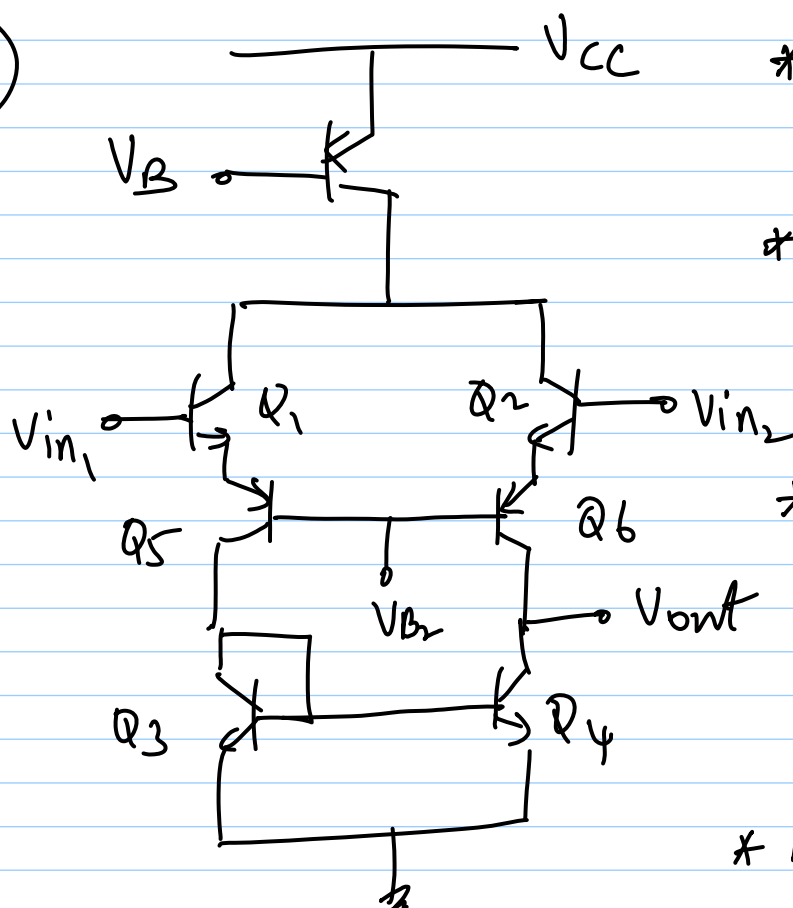

* Use pnp in CB config

* r_{out} is higher $\Rightarrow$ higher gain

* $V_{in1} = V_{B2} + V_{BE5} + V_{BE1}$

$\Rightarrow$ still zero i/p cm range

* high R_{in} , low I_{in}


4) Don't fix V_{B2}

let V_{B2} float w.r.t. V_{icm}
 $\rightarrow$ design so that

$$V_{B2} = V_{ic} - V_{BE1} - V_{BE5}$$

$\Rightarrow$ indirect biasing scheme

741 input stage

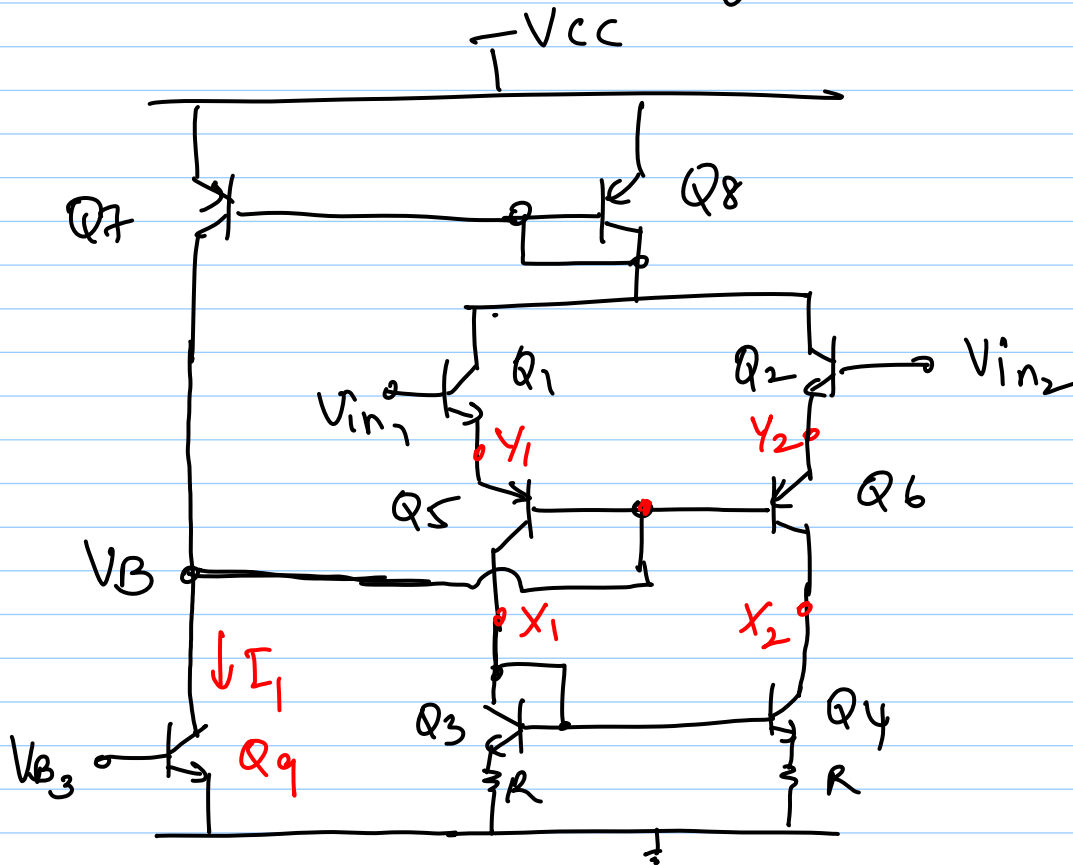

* f.b. loop around $Q_7 - Q_8 - Q_9$

& input Q_{1-2} , Q_{5-6} will automatically adjust V_B so that


$$I_7 = I_8 = I_1 \quad (\text{neglecting base current errors})$$

* degeneration resistors improve R_{out} for higher gain & improve $Q_3 - Q_4$ matching

Other details

- * β -helper for CM load improves mirroring
- * $Q_5 - Q_6$ provide DC level shifting
 - Emitters (Y_1, Y_2) are near V_{in}
 - Collectors (X_1, X_2) are near $-V_{EE}$
- * Generate bias current using Widlar source

Full input stage

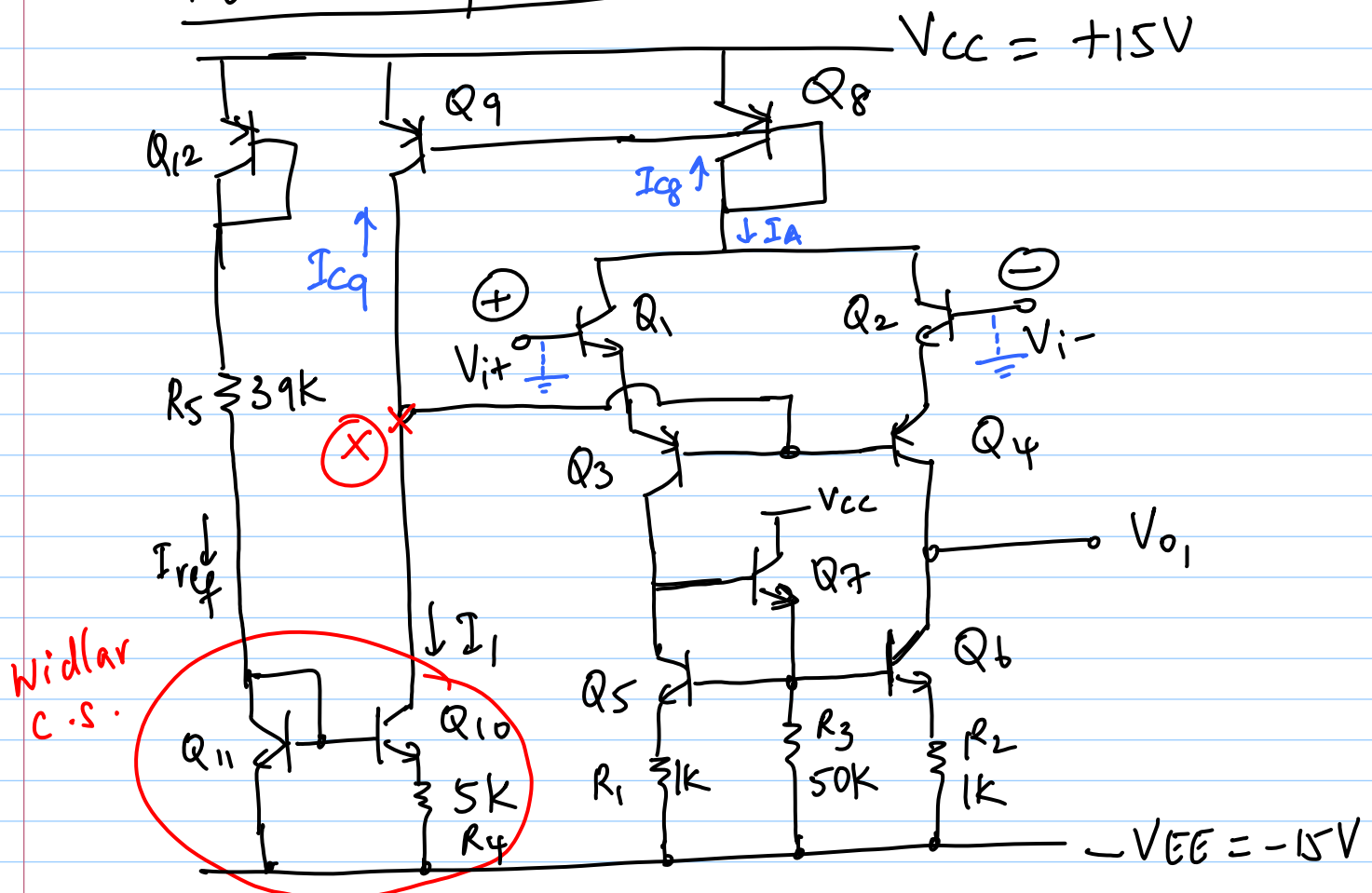

DC Analysis

- * Assume that dcl is in f.b. so that overall $V_{out} = 0$
- * neglect Early effect for DC
- * assume $\beta_{dc, npn}$ is large but $\beta_{dc, pnp}$ is not
- * neglect npn I_B 's, but not pnp I_B 's
- * assume all devices in F.A.R

$$1) I_{ref} = \frac{V_{CC} + V_{EE} - V_{EB12}(ON) - V_{BE11}(ON)}{R_5}$$

$$\approx \frac{30 - 1.4}{39K} = 733 \mu A$$

$$2) \text{ large } \beta_{nnp} \Rightarrow I_{C10} \approx I_{E10} \approx I_1$$

$$V_{BE11} - V_{BE10} - I_{E10} R_4 = 0$$

$$V_T \ln \frac{I_{ref}}{I_1} = I_1 R_4$$

iteration :

$$I_1 = 19 \mu A$$

$$3) \quad I_A = -I_{CQ} \left(1 + \frac{2}{\beta_{PNP}} \right) \quad \text{--- (1)}$$

$$\left. \begin{array}{l} I_{C1} = I_{E1} \\ I_{C2} = I_{E2} \end{array} \right\} \beta_{PNP} \text{ is large}$$

$$\begin{aligned} \Rightarrow I_A &= I_{C1} + I_{C2} = I_{E1} + I_{E2} \\ &= I_{E3} + I_{E4} = -I_{CQ} \left(1 + \frac{2}{\beta_{PNP}} \right) \end{aligned}$$

$$\text{KCL @ (X)} : I_{CQ} + I_1 = I_{B3} + I_{B4}$$

$$\Rightarrow 19 \mu A = -I_{CQ} + \frac{1}{1 + \beta_{PNP}} (I_{E3} + I_{E4})$$

$$19 \mu A = -I_{CQ} + \frac{1}{\beta_{PNP} + 1} \cdot \left[-I_{CQ} \cdot \left(1 + \frac{2}{\beta_{PNP}} \right) \right]$$

$$19 \mu A = -I_{CQ} \left[1 + \frac{1 + 2/\beta_{PNP}}{1 + \beta_{PNP}} \right]$$

$$-I_{CQ} = \frac{19 \mu A}{\left[1 + \frac{1 + 2/\beta_{PNP}}{1 + \beta_{PNP}} \right]} \quad \text{--- (2)}$$

(2) in (1)

$$\Rightarrow I_A = -I_{CQ} \cdot \left(1 + \frac{2}{\beta_{PNP}} \right)$$

$$I_A = \frac{.19 \mu A}{\left[1 + \frac{(1 + 2/\beta_{pnp})}{(1 + \beta_{pnp})} \right]} \cdot (1 + 2/\beta_{pnp})$$

$$\approx 19 \mu A \cdot \left(1 + \frac{1}{\beta_{pnp}} \right)$$

Finally,

$$I_{C3} + I_{C4} = \frac{(I_{E3} + I_{E4}) \cdot \beta_{pnp}}{\beta_{pnp} + 1}$$

$$\approx \frac{I_A \cdot \beta_{pnp}}{1 + \beta_{pnp}} \approx +19 \mu A //$$

$\Rightarrow I_{C3} + I_{C4}$ is insensitive to β_{pnp}
due to biasing method

* This is an example of Common mode negative feedback