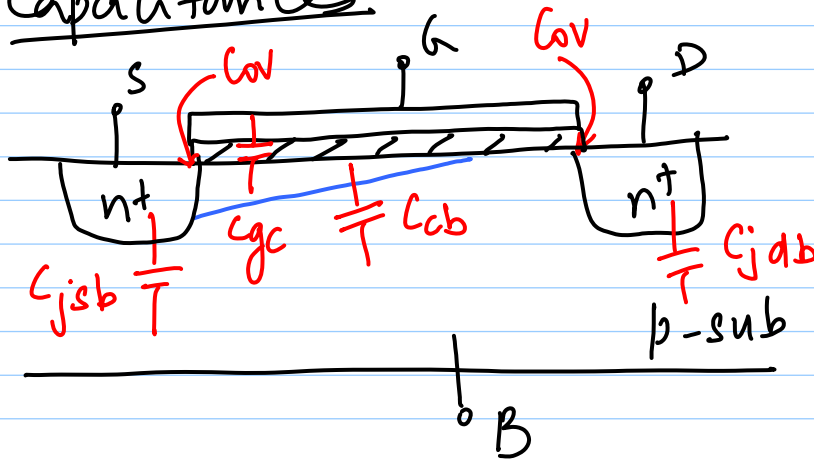


5/1/12

Lec 3 - MOS caps; s.c. effects

Simple amplifier ckt

Capacitance



* $L_D =$ overlap of h over D-S


* $L_{eff} = L - 2L_D$

$$C_{gc} = W L_{eff} C_{ox} ; C_{ox} = \epsilon_{ox} / t_{ox}$$

$$C_{cb} = (\epsilon_{si} / x_d) \cdot W L_{eff}$$

$$C_{ov} = W L_D C_{ox}$$

Cap	OFF	TRIODE	SAT
C_{gs}	C_{ov}	$C_{ov} + C_{gc}/2$	$C_{ov} + \frac{2}{3} C_{gc}$
C_{gd}	C_{ov}	$C_{ov} + C_{gc}/2$	C_{ov}
C_{gb}	$C_{gc} \parallel C_{sb} < C_{gb}$	0	0
C_{sb}	C_{jsb}	$C_{jsb} + C_{cb}/2$	$C_{jsb} + \frac{2}{3} C_{cb}$
C_{db}	C_{jdb}	$C_{jdb} + C_{cb}/2$	C_{jdb}

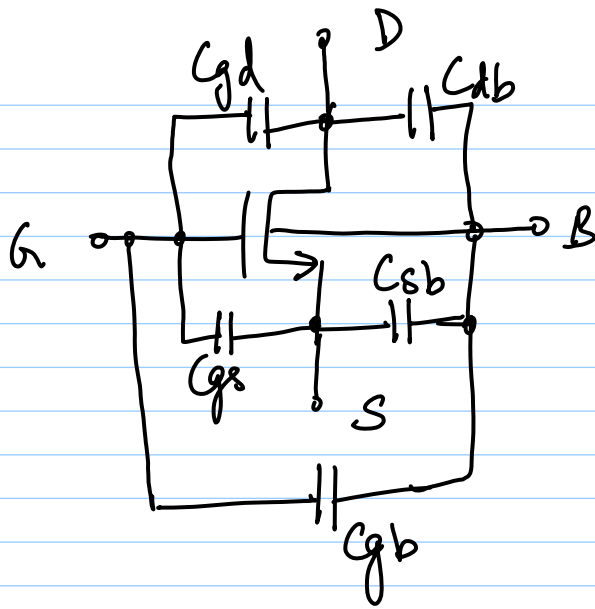

Short-channel Effects


"Long" channel device equation

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_T)^2$$

→ derived using drift velocity expression:

$$v_d(y) = \mu_n E(y)$$

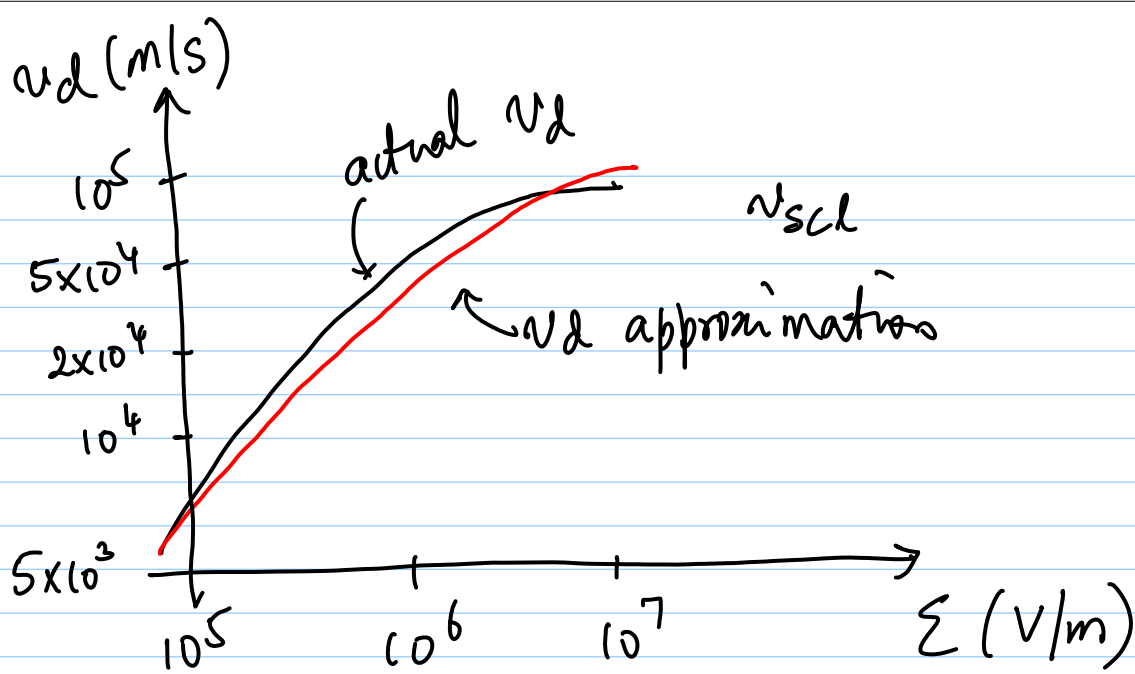drift velocity (pointing to $v_d(y)$)
 mobility (pointing to μ_n)
 horizontal E -field (pointing to $E(y)$)
 length along channel (pointing to the channel length L in the equation above)



At high fields,

$$v_d = \frac{\mu_n E}{1 + E/E_c}$$

scattering limited velocity

$$v_{scl} = \mu_n E_c$$

typical values:

$$E_c \sim 1.5 \times 10^6 \text{ V/m}$$

$$\mu_n \sim 0.07 \text{ m}^2/\text{V.s.}$$

$$v_{scl} \sim 1 \times 10^5 \text{ m/s}$$

Long channel $V_{DSAT} = (V_{GS} - V_T)$

write

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_T) V_{DSAT}$$

In general,

$$V_{DSAT} = (V_{GS} - V_T) \parallel (L \cdot E_c)$$

$$= \frac{(V_{GS} - V_T) - (L \cdot E_c)}{(V_{GS} - V_T) + (L \cdot E_c)}$$

$$I_D = \frac{1}{2} \mu_n \text{cox} \frac{W}{L} (V_{GS} - V_T) \cdot [(V_{GS} - V_T) \parallel (L \cdot E_c)]$$

How to determine S.C. operation?

* compare $\frac{V_{GS} - V_T}{L}$ and E_c

ratio is small $\Rightarrow$ Long channel ok

* actual length of gate is irrelevant!

However,

$\rightarrow$ as $L \downarrow$, smaller $(V_{GS} - V_T)$ is required to exhibit S-C. effects!

In deep vel. sat.,

$$I_D = \frac{1}{2} \mu_n \text{cox} \frac{W}{L} \cdot (V_{GS} - V_T) \cdot (L \cdot E_c)$$

$$= \frac{1}{2} \mu_n \text{cox} W E_c (V_{GS} - V_T)$$

→ I_D indep. of L !

→ $I_D - V_{DS}$ relationship is linear

$$g_m = \frac{\partial I_D}{\partial V_{DS}} = \frac{1}{2} \mu_n C_{ox} \cdot W \cdot E_c$$

$$C_{gs} = \frac{2}{3} W L C_{ox} \quad (\text{same as before})$$

$$W_T = \frac{g_m}{C_{gs}} = \frac{3}{4} \frac{\mu_n E_c}{L}$$

$$\Rightarrow W_T \propto \frac{1}{L} \quad \left\{ \begin{array}{l} \text{was } 1/L^2 \text{ for L-C.} \\ \text{device} \end{array} \right\}$$

⇒ W_T independent of bias conditions




* PMOS devices - vel. sat. happens
@ higher fields

Simple Amp ckt's


Objectives:

- 1) Visualise propagation of V & I signals through the ckt
- 2) Develop insight into ckt performance based on (1)

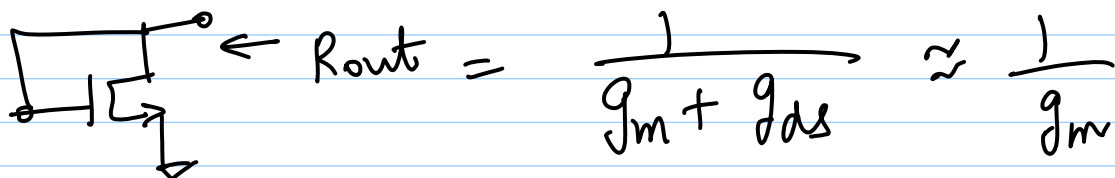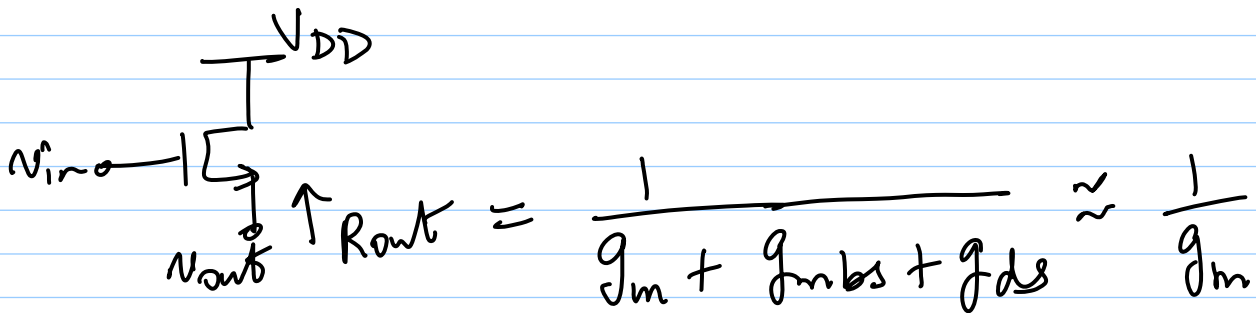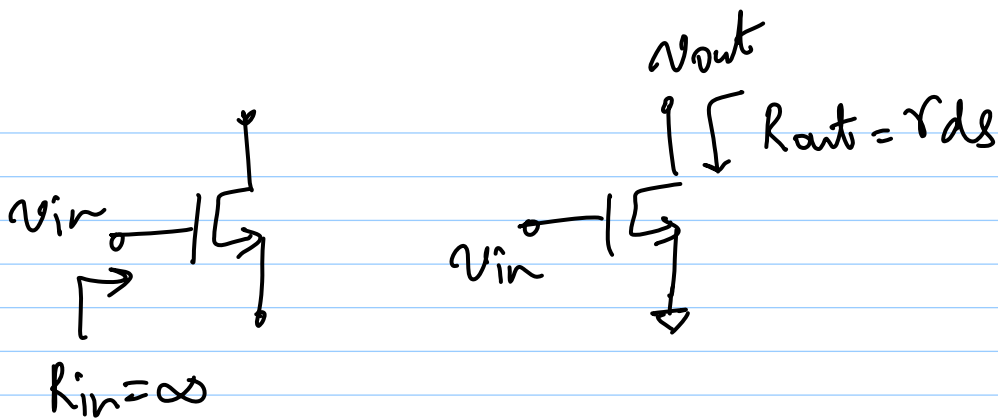
- 3) Identify relative impedance levels at all nodes in signal path
- 4) Freq. response: identify relative position of poles & zeroes based on impedances & caps @ each node in signal path
- 5) VTC of ckt can give insights into output voltage range (i.e. output swing)




C-S. Amp.

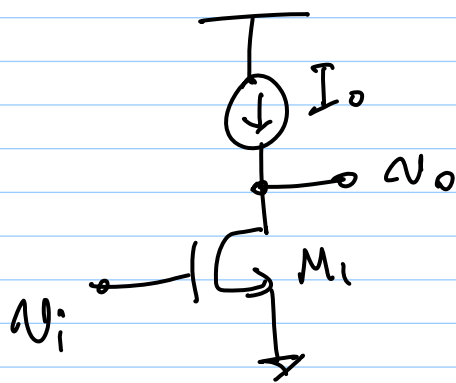

$$a_v = g_{m1}/g_{ds1}$$

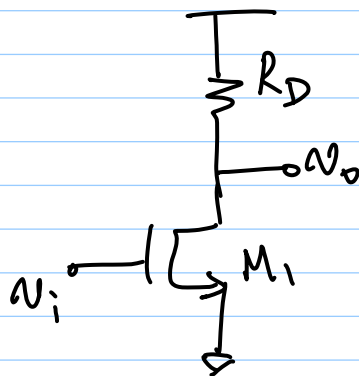


$$a_v = \frac{g_{m1}}{g_{ds1} + g_D}$$

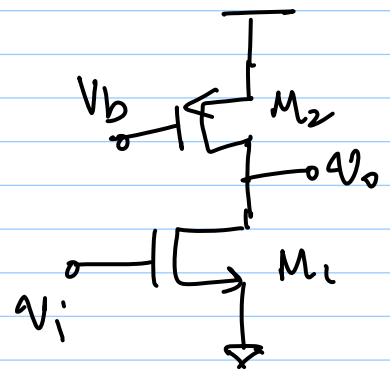


$$a_v = \frac{g_{m1}}{g_{ds1} + g_{ds2}}$$

note! $V_{BS} = 0 = v_{bs}$

$$\Rightarrow g_{mbs} v_{bs} = 0$$

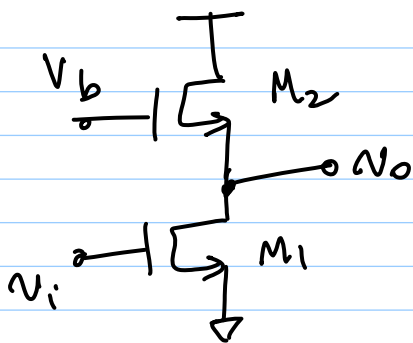
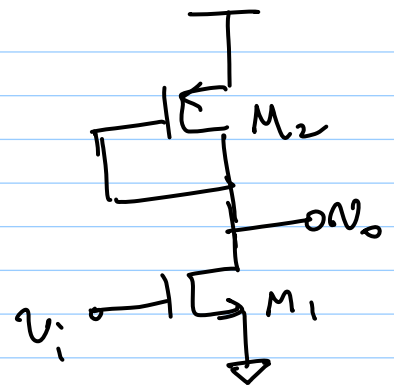
$$a_v = \frac{g_{m1}}{g_{m2} + g_{mbs2} + g_{ds2} + g_{ds1}}$$



$$a_v = \frac{g_{m1}}{g_{m2} + g_{ds2} + g_{ds1}}$$

* All of the form

$$a_v = \frac{g_m}{g_{out}}$$