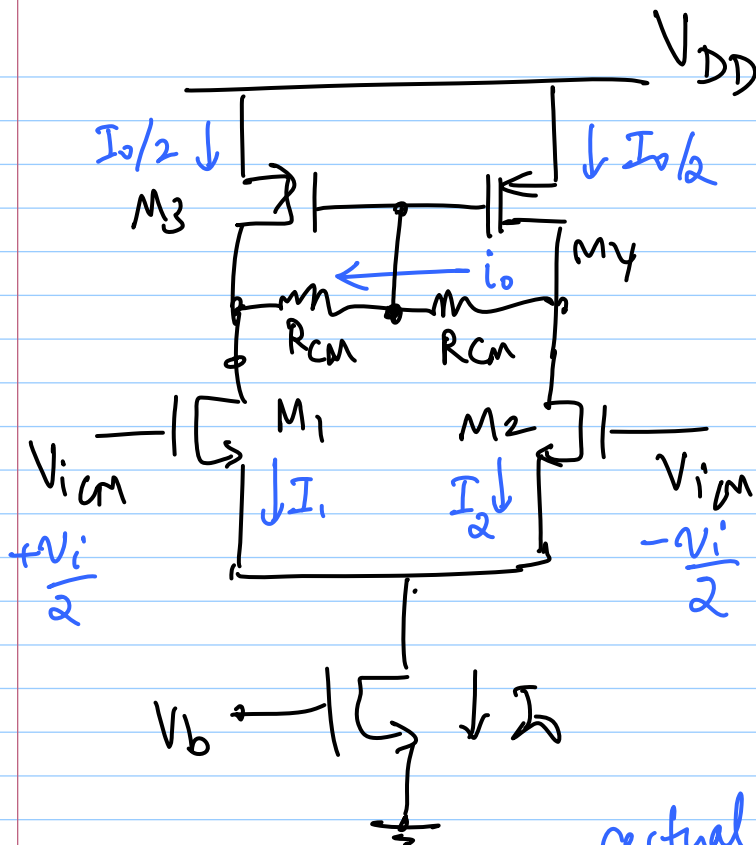


22-3-12

Lec 33

Common-mode feedback (CMFB)

- * Measure o/p CM
- * feedback in the right direction
- * CM loop gain $= \infty \Rightarrow V_{o,cm} = V_{cm,ref}$





$$V_{o,cm} = V_{DD} - V_{S_{M3,4}}$$

$$I_1 = \frac{I_0}{2} + g_{m1} \frac{v_i}{2}$$

$$I_2 = \frac{I_0}{2} - g_{m1} \frac{v_i}{2}$$

$$i_o = g_{m1} \frac{v_d}{2} \quad (\text{neglecting } r_{ds})$$

$$\text{actual gain} = g_{m1} (r_{ds1} || r_{ds3} || R_{cm})$$

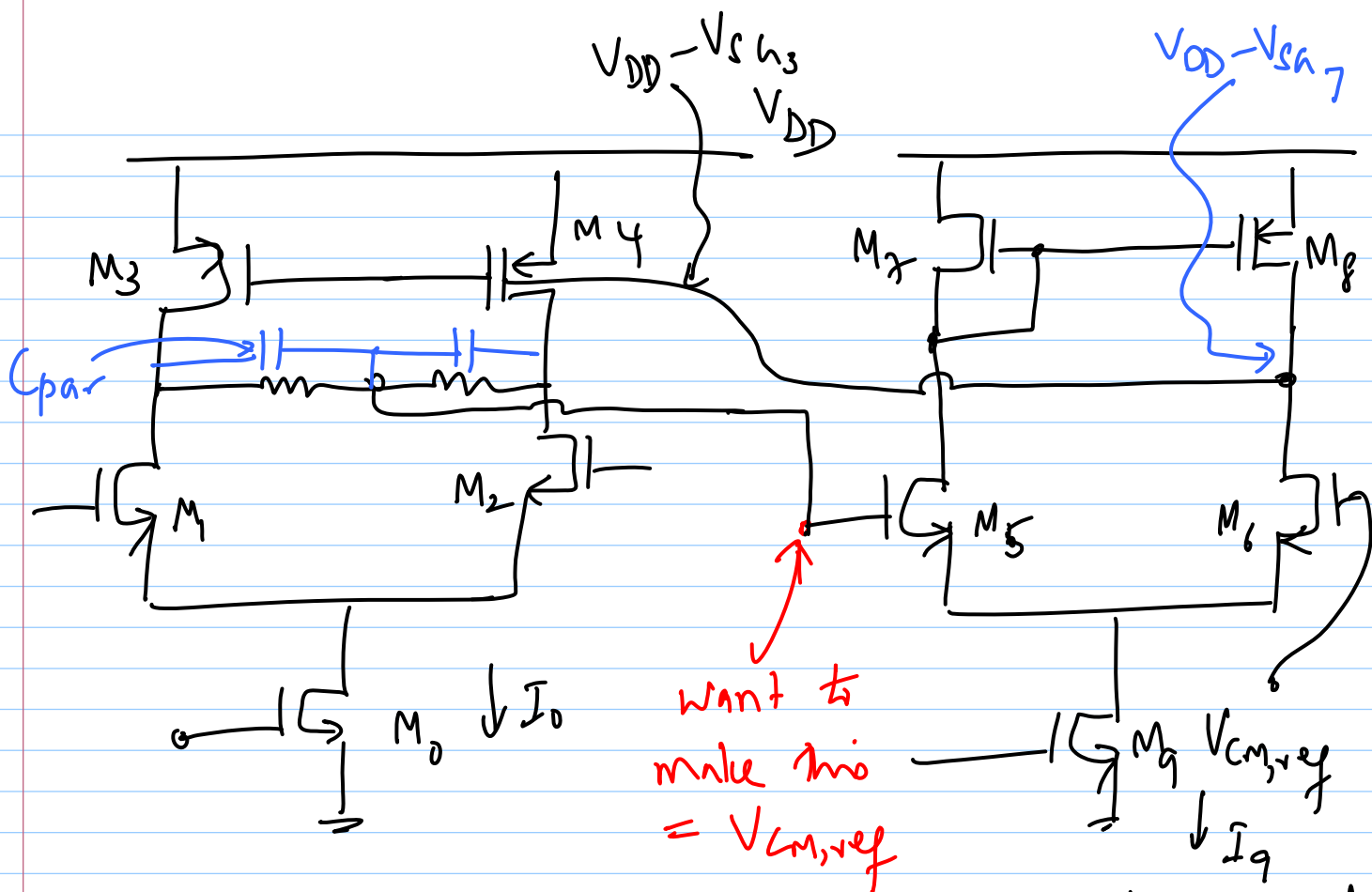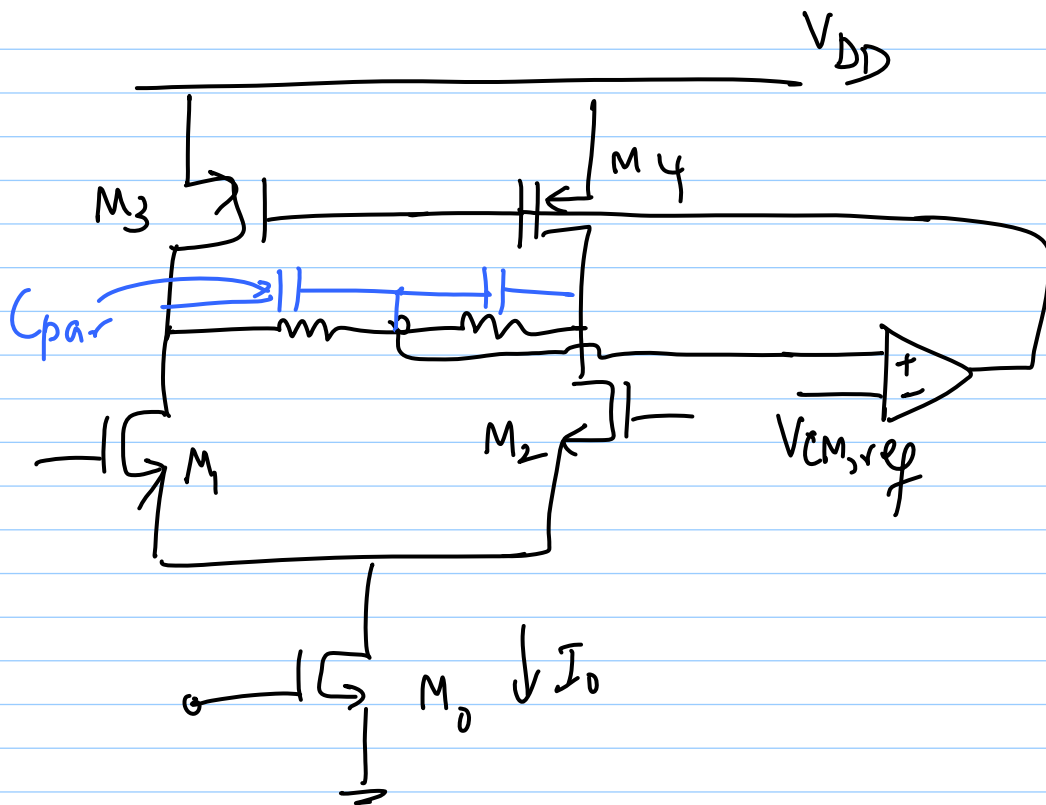

$\Rightarrow V_{DD} - V_{GS4} = V_{DD} - V_{GS8}$ so that no offset

$$\Rightarrow V_{SG3}|_{I_{D/2}} = V_{SG7}|_{I_{D/2}}$$

$\Rightarrow$ same current density

$$\frac{W_3}{I_{D/2}} =$$

$$\frac{W_9}{I_{D/2}}$$

replica
bias

very
imp!



* opamp2 does not need to burn same amt. of current as opamp1
 $\rightarrow$ just scale down original opamp.

* If you use a diff. current density,

$$V_{oCM} = V_{CM,ref} + \frac{V_{SG3}|_{I_{D/2}} - V_{SG7}|_{I_{D/2}}}{A_{CMFB}}$$

Stability

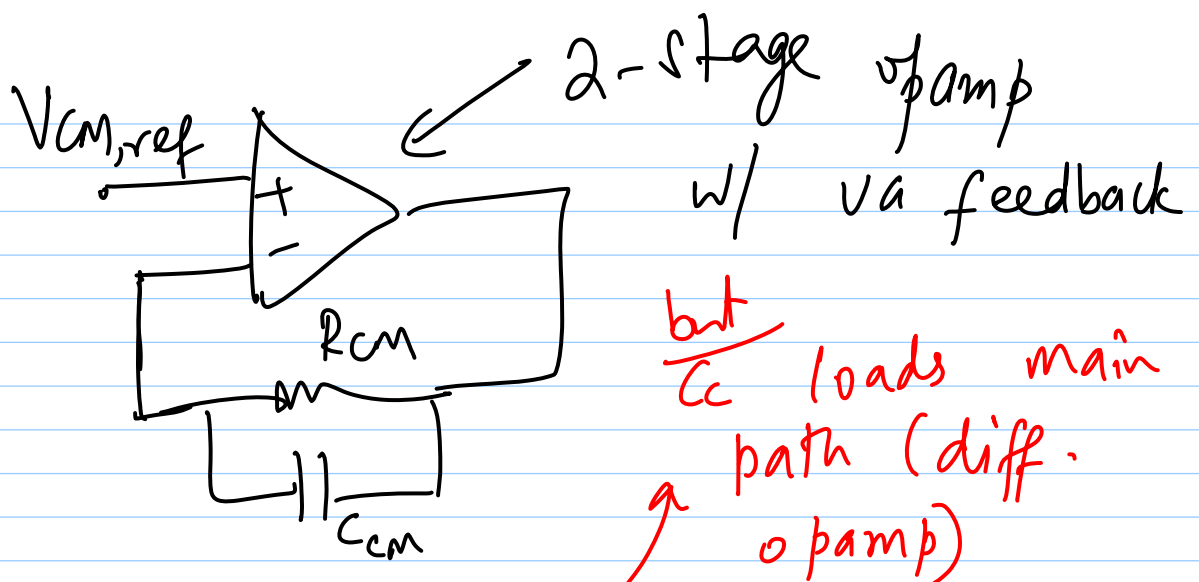
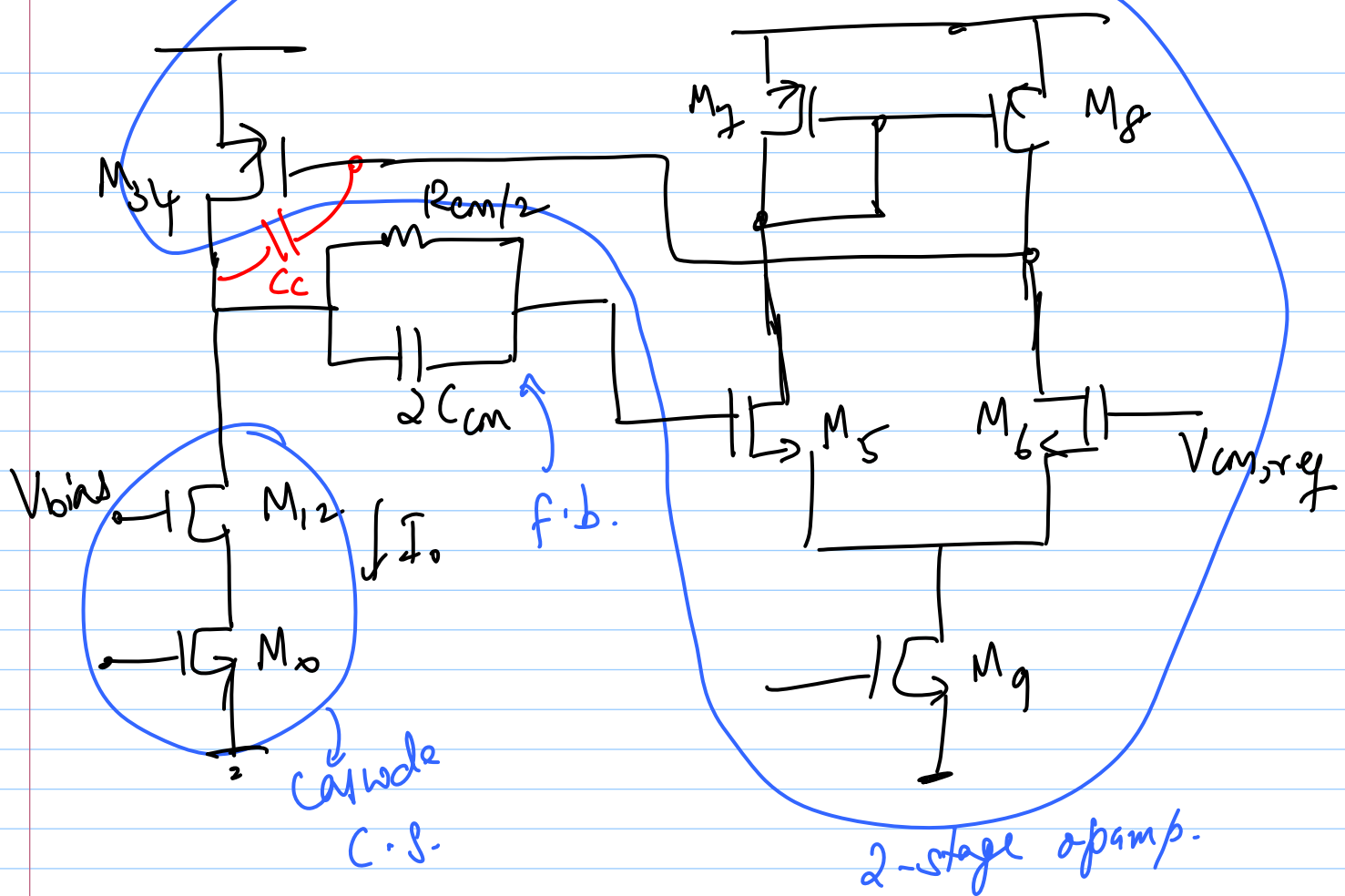
* Calculate L_n of CMFB loop
 $\rightarrow$ draw CM equivalent ckt.



* compensation cap. is missing

→ L to D of M_{34} in CM picture


→ 2 caps $C_c/2$ from L to D of M_{34} & M_7 in overall ckt.

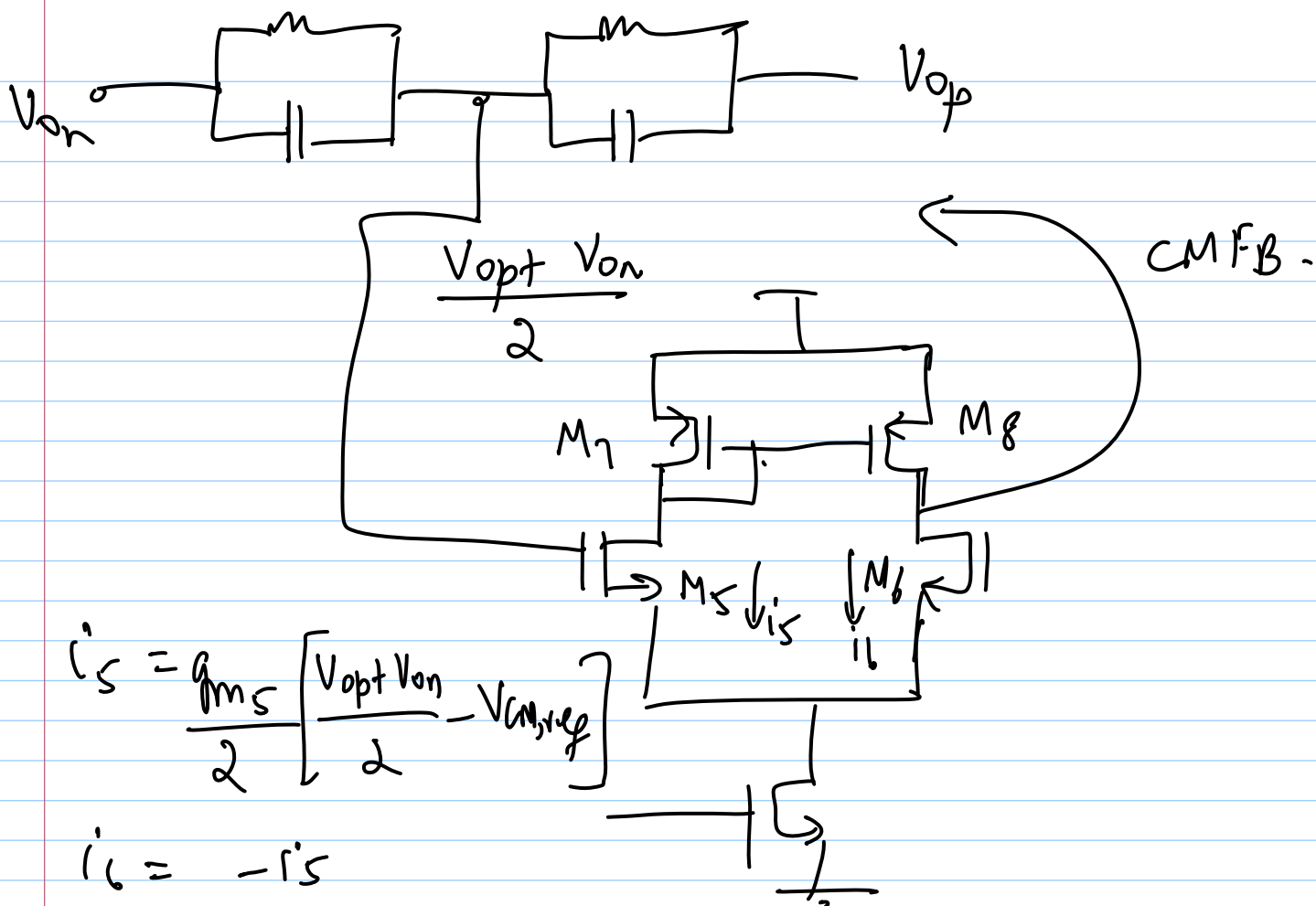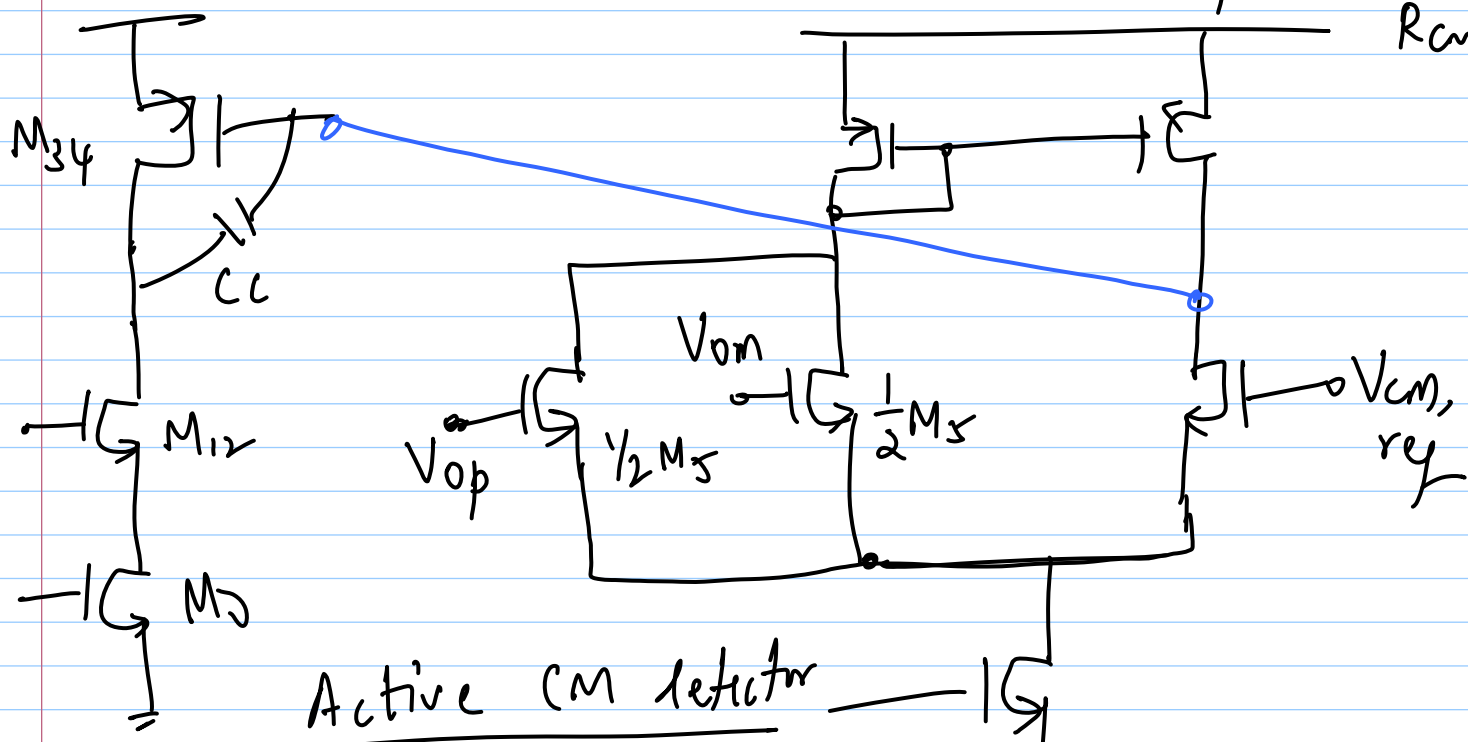
$$i_6 = -i_5$$


→ DC gain is not affected (if $k_{in} = \infty$)

But :

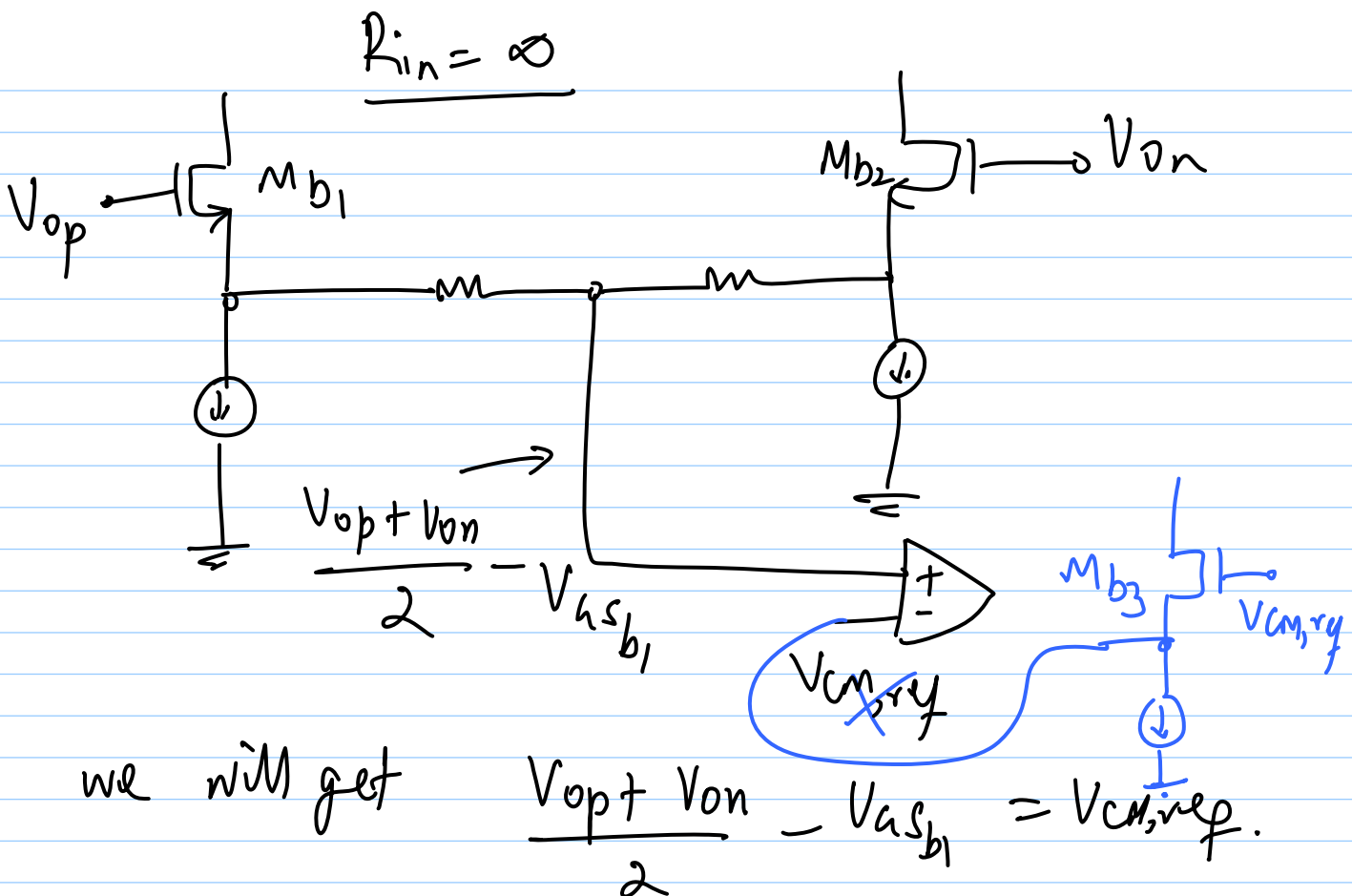- R_{cm} is linear (even for large V_{op}, V_{on})
- this detector is linear only for small V_{op}, V_{on}
- * can be used in 1st stage of a 2-stage opamp (small swing)
- 2nd stage can have resistive detector (can drive res. loads)



$\Rightarrow * V_{TC} \xrightarrow{\text{replica}} \xrightarrow{\text{bias}} \text{make}$
 $V_{GS_{b1}} = V_{GS_{b3}} \leftarrow \text{current density equal}$

S.F. gain $< 1 \Rightarrow$ affects all
equally & just changes overall
CMFB LH.