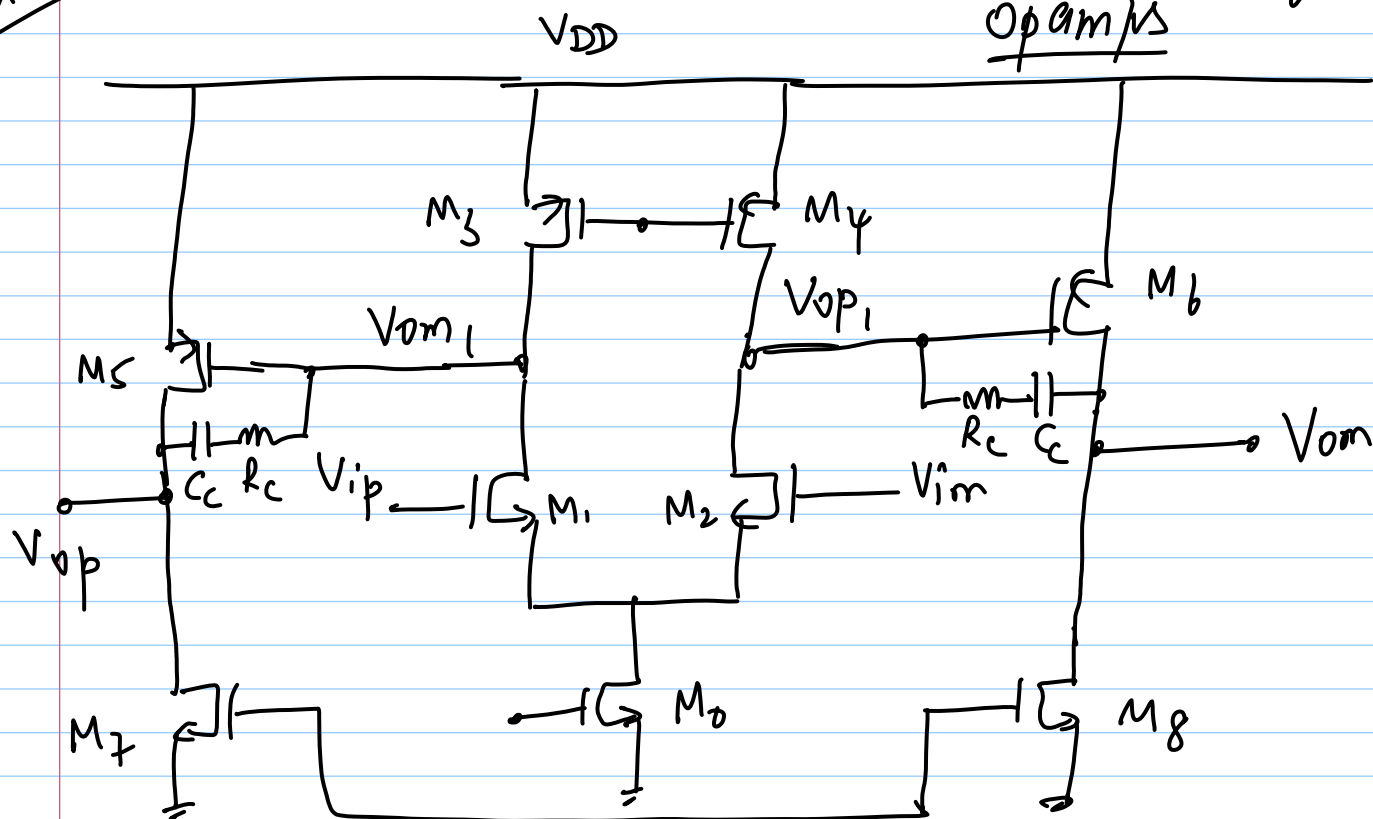


28-03-2012

Lec 34 - Two-stage, fully diff. Opamps




* V_{ocm1} $\leftarrow$ control M_0 or M_3/M_4 gates
through CMFB $(V_{op1} + V_{om1})/2$

* V_{ocm2} $\leftarrow$ control gate of M_7/M_8 ,
or M_0 or M_3/M_4

through V_{op1}/V_{om1} & M_5-M_6

$\Rightarrow M_5$ & M_6 are pseudo differential
amp. $\Rightarrow$ non-zero CM gain

Stage 1 CMFB

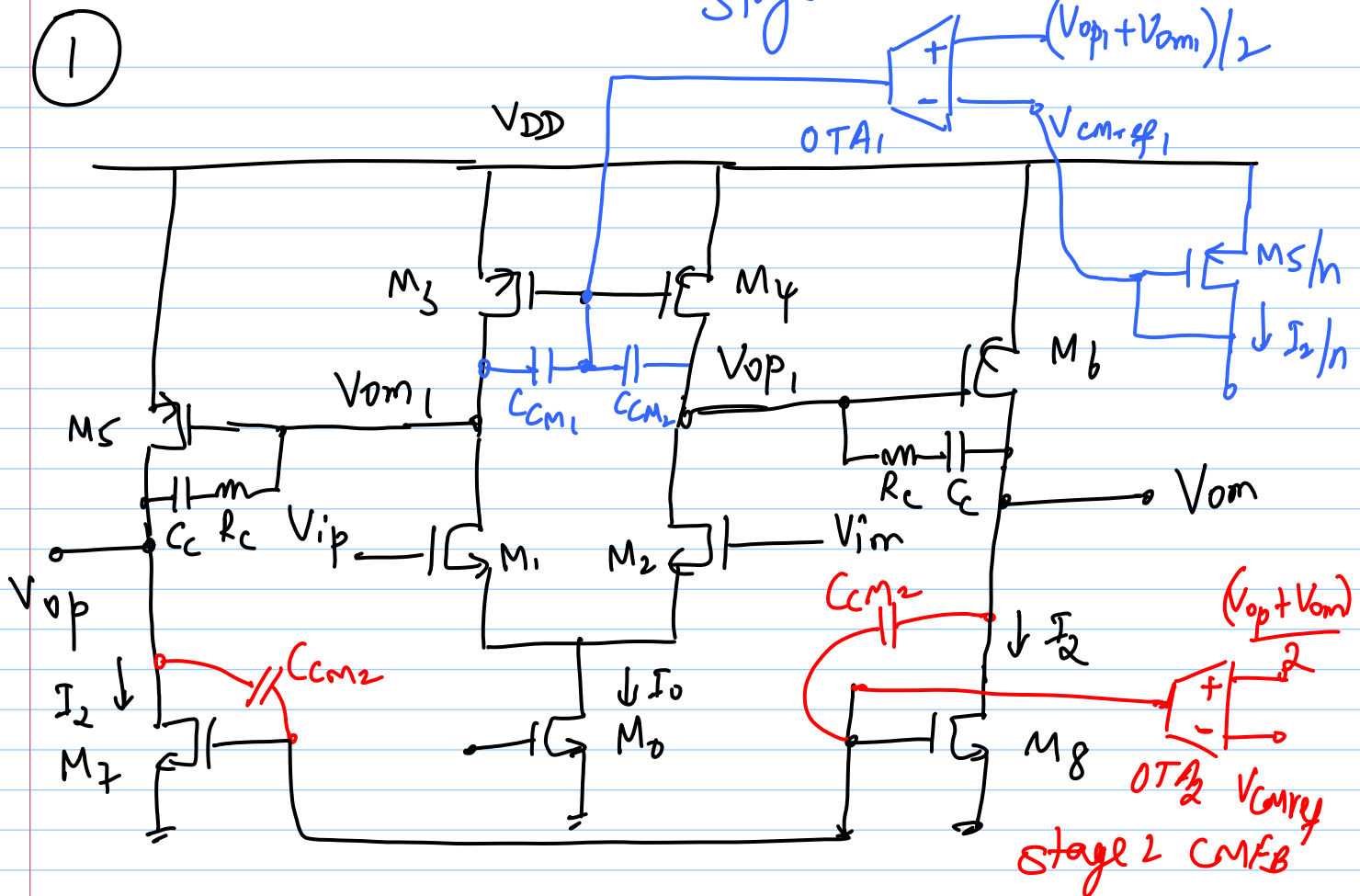

* How do you choose V_{CMref1} ?

$$\rightarrow V_{CMref1} = V_{DD} - V_{S_{M5}}|_{I_2}$$

$\rightarrow$ cannot be chosen independently
(e.g. @ $V_{DD}/2$)

$\rightarrow$ M_7 & M_8 gates get adjusted automatically through CMFB₂

* Generate V_{CMref1} through replica

* How to choose $V_{cm,ref}$?

→ choose to maximise swing
i.e. $V_{cm,ref} = V_{DD}/2$

Separate CMFB for stages 1 & 2

stage 1 : * control gates of $M_{3,4}$
* set $\frac{V_{op1} + V_{om1}}{2}$ to $V_{DD} - V_{GS1}/I_2$
($= V_{cm,ref1}$)

→ derive from a replica branch

* Use a CM detector w/o
resistive loading @ the input
(maintain gain)

Stage 2 : * $V_{cm,ref} \approx V_{DD}/2$ to
maximise swings

* resistive CM detector (high swings)


* Use single-stage opamps to complete CM
feedback

* Do compensation for CMFB loops
→ C_{cm1}, C_{cm2} (can also have R_{cm1}, R_{cm2})

* $OTA_1 \leftarrow$ nmos i/p pair with pmos loads (M_3/M_4 replica)

* $OTA_2 \leftarrow$ pmos i/p pair with nmos loads (M_7/M_8 replica)

(2)

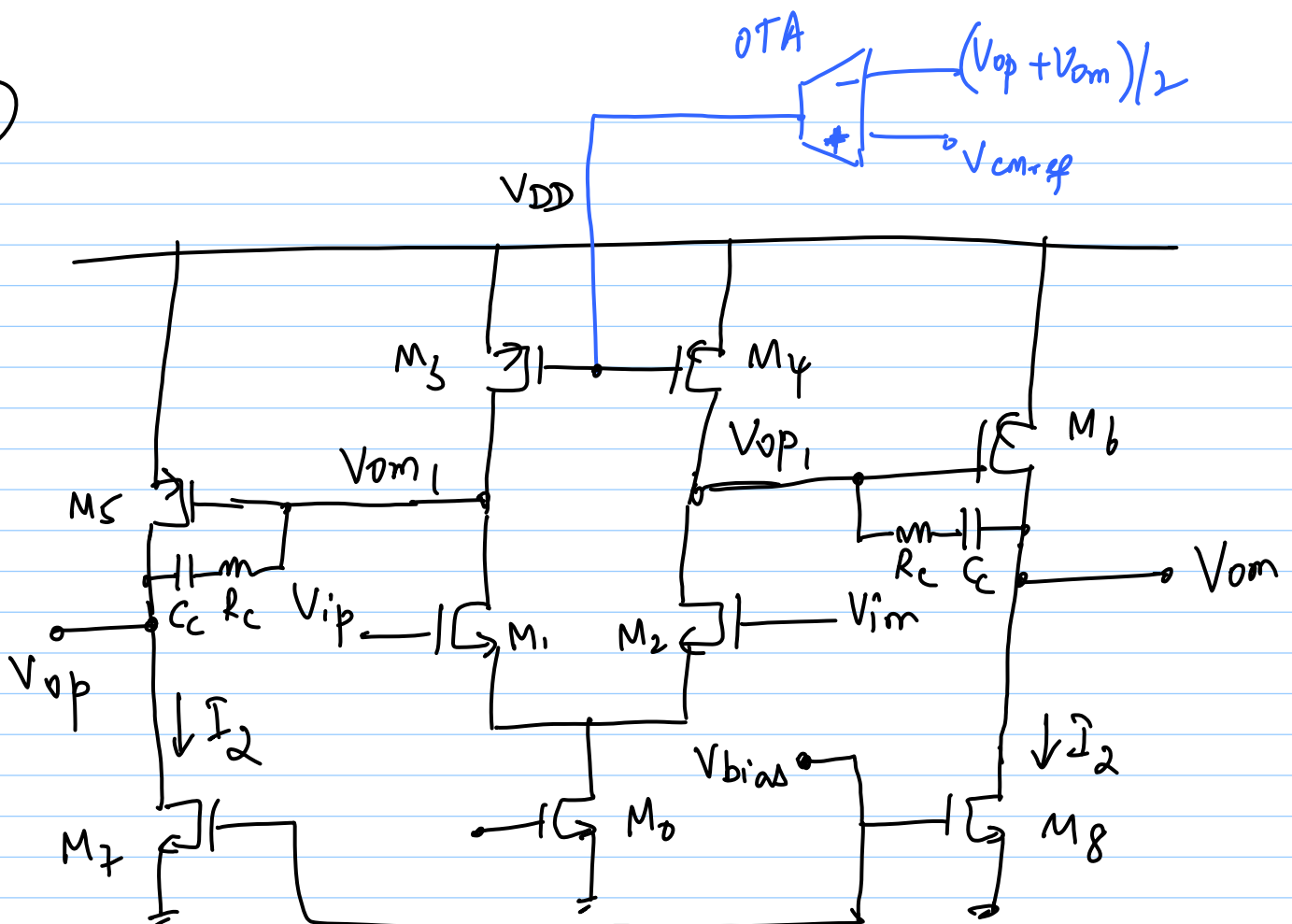

- * single f.b. loop
 - stages 1 & 2 are both in f.b. loop
- * fundamentally possible because M_5 & M_6 have CM gain
- * Vbias such that I_2 in M_7, M_8
- * Once CMFB loop settles,
 - $V_{op} = V_{om} = V_{CM,ref}$
 - $I_{M_5} = I_{M_6} = I_2$
 - $V_{op1} = V_{om1} = V_{DD} - V_{SA_{S,1}} / I_2$

Stability

- * 3 stages in f.b. $\Rightarrow$ harder to stabilise
- * Make OTA low-gain
 - e.g. use diode loads instead of mirror so that gain ~ 1
- * C_c - can be designed to stabilise CM loop as well (difficult)