
 


29-3-12



Lec - 35


3-stage Opamp

Hacker design

 


better design: BW of later stages wider

  

 

= 2-stage opamp


1) Nested Miller

 

$$\omega_u = \frac{G_{m1}}{C} \quad (\text{desired})$$

$$\text{dc gain } A_0 = \frac{G_{m1} G_{m2} G_{m3}}{G_{o1} G_{o2} G_{o3}} \quad (\text{large})$$

 
$$\text{dominant pole } \omega_d \approx \omega_u / A_0$$




$$G_{m1} V_d = sC (V_o + V_o/A)$$

neglecting G_{o1} (at hi-freq.)
 
$$\Rightarrow \frac{V_o}{V_d}(s) = \frac{G_{m1}}{sC} \frac{1}{\left(1 + \frac{1}{A}\right)} = \frac{G_{m1}}{sC} \cdot \frac{A}{1+A}$$



$$|A| \gg 1 \Rightarrow \frac{A}{1+A} \approx 1 ; |A| \ll 1 \Rightarrow \frac{A}{1+A} \approx A$$

 

- * Non-dominant poles & zeroes of A appear as they are in $A/(1+A)$
- * There will be a pole of $A/(1+A)$ at VGF of A


Conditions

$$* \quad \frac{G_{m1}}{C} < \omega_u' < p_2' - \frac{G_{m2} \frac{C'}{C'+C_2}}{\frac{C'C_2}{C'+C_2} + C_3}$$


→ 3-stage opamps will be slower than 2-stage opamps

→ steady state error will be very smaller

 
* This analysis assumes inner opamp is ideal VCVS (zero positions are inaccurate)



 
* add $C' \Rightarrow p_3$ & p_2 get split



* add C $\Rightarrow$ Second splitting

 

 $\rightarrow$ analytic design can become quite difficult



* large gain, but lower speed


$$\omega_u = \frac{g_{m1}}{C} = \frac{1}{4} p_3'$$

$$\text{2-stage opamp: } \omega_u = \frac{1}{2} p_3'$$

p_3'' & p_1'
(complex pair)


2) Multipath NMC :

* multi-stage with feedforward stages

 

* C & C' values will be different

 * @ low freq. $\Rightarrow$ main path ; @ high freq. $\Rightarrow$ f.f. path



$$p_3'' = \frac{p_3'}{2} + \frac{p_3'}{2} \sqrt{1 - \frac{4}{p_3'} \cdot \frac{g_{m2}}{C'}}$$

$$\frac{g_{m2}}{C'} = 0 \Rightarrow p_3'' = p_3'$$

$$\frac{g_{m2}}{C'} \approx 0.1 p_3' \text{ is optimal}$$

→ ~ 10% BW reduction w.r.t. 2-stage

→ pole-zero trading is implicit over PVT

* g_{mf} adds noise directly @ input
+ offset

* Can move g_{mf} across $g_{m2} - g_{m3}$
→ g_{mf} must drive V_{out} (slew + settle)
⇒ more power dissipation

* nested + f.f. is also possible

Band gap references

* Reference V/I that are independent of temperature (& therefore process)

$$\text{Let } V = \alpha_1 V_1 + \alpha_2 V_2$$

$$\frac{\partial V}{\partial T} = 0 \Rightarrow \alpha_1 \frac{\partial V_1}{\partial T} + \alpha_2 \frac{\partial V_2}{\partial T} = 0$$

→
+ve T.C.

↑
-ve T.C.

* Bipolar (or diode) BE voltage temp. var:

$$V_{BE} = V_T \ln \left(\frac{I_C}{I_S} \right)$$

$$V_T = kT/q$$

$$I_S \propto \mu kT n_i^2$$

μ = mobility of minority carriers
 n_i = intrinsic minority carrier conc. of Si

$$\mu \propto \mu_0 T^m, \quad m \approx -3/2$$

$$n_i^2 \propto T^3 \exp \left[-E_g / (kT) \right]$$

$$E_g = \text{Bandgap of Si} \approx 1.12 \text{ eV}$$

energy

$$\Rightarrow I_S = b T^{4+m} \exp \left[\frac{-E_g}{kT} \right]$$

$$\frac{\partial V_{BE}}{\partial T} = \frac{\partial V_T}{\partial T} \ln \frac{I_C}{I_S} - \frac{V_T}{I_S} \frac{\partial I_S}{\partial T}$$

$$\begin{aligned} \frac{\partial I_S}{\partial T} &= b(4+m) T^{3+m} \exp \left[\frac{-E_g}{kT} \right] \\ &\quad + b T^{4+m} \exp \left[\frac{-E_g}{kT} \right] \cdot \left(\frac{E_g}{kT^2} \right) \end{aligned}$$

$$= \frac{(4+m)}{T} I_S + \frac{E_g}{kT^2} \cdot I_S$$