

31-3-12

lec 36


$$\frac{V_T}{I_S} \frac{\partial I_S}{\partial T} = (4+m) \frac{V_T}{T} + \frac{E_g}{kT^2} \cdot V_T$$

$$\begin{aligned} \frac{\partial V_{BE}}{\partial V_T} &= \frac{V_T}{T} \ln \frac{I_C}{I_S} - (4+m) \frac{V_T}{T} - \frac{E_g}{kT^2} \cdot V_T \\ &= \frac{V_{BE} - (4+m)V_T - E_g/q}{T} \end{aligned}$$

When $V_{BE} \approx 0.75V$ @ $T = 300K$,

$$\frac{\partial V_{BE}}{\partial T} \approx -1.5 \text{ mV/K} \quad \left[\begin{array}{l} \text{note that this} \\ \text{depends on } T \end{array} \right]$$

positive TC :

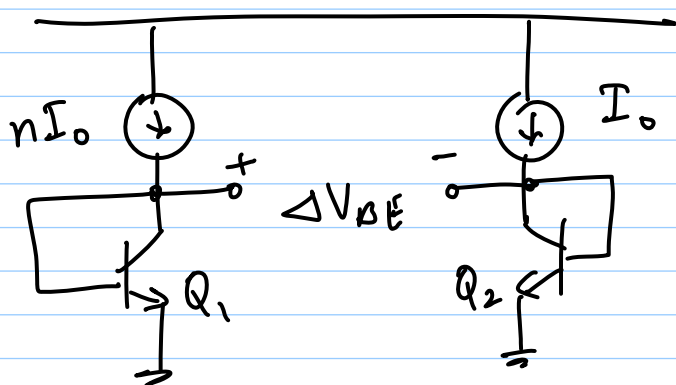

neglect I_{B1}

$$\Delta V_{BE} = V_{BE1} - V_{BE2}$$

$$\begin{aligned} \Delta V_{BE} &= V_T \ln \left(\frac{n I_0}{I_{S1}} \right) - V_T \ln \left(\frac{I_0}{I_{S2}} \right) \\ &= V_T \ln n \end{aligned}$$

$$\Rightarrow \frac{\partial \Delta V_{BE}}{\partial T} = \frac{k}{q} \ln n \quad \left[\begin{array}{l} \text{positive T-c.,} \\ \text{independent of } T \text{ \& } I_C \end{array} \right]$$

Bandgap ref.

$$V_{ref} = \alpha_1 V_{BE} + \alpha_2 \underbrace{(V_T \ln n)}_{\Delta V_{BE}}$$

$$\frac{\partial V_{BE}}{\partial T} \approx -1.5 \text{ mV/K} \quad @ 300 \text{ K}$$

$$\frac{\partial V_T}{\partial T} = \frac{k}{q} \approx 0.087 \text{ mV/K}$$


$$\text{Set } \alpha_1 = 1$$

$$\Rightarrow (\alpha_2 \ln n) (0.087 \text{ mV/K}) = 1.5 \text{ mV/K}$$

$$\Rightarrow \alpha_2 \ln n \approx 17.2$$

$$V_{ref} = V_{BE} + 17.2 V_T$$
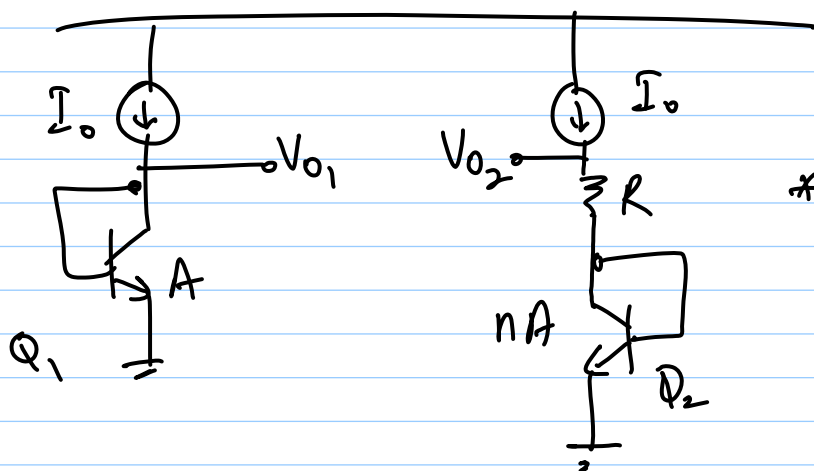
$$\approx 1.25 \text{ V} \quad @ 300 \text{ K}$$



* neglect I_B ,
* Force $V_{01} = V_{02}$


$$V_{BE1} = I_0 R + V_{BE2}$$

$$\Rightarrow I_0 R = V_{BE1} - V_{BE2} = V_T \ln n$$

$$V_{O2} = V_{BE2} + V_T \ln n \leftarrow V_{ref}$$

* $\ln n = 17.2 \Rightarrow$ extremely large n

* we need to force $V_{O1} = V_{O2}$

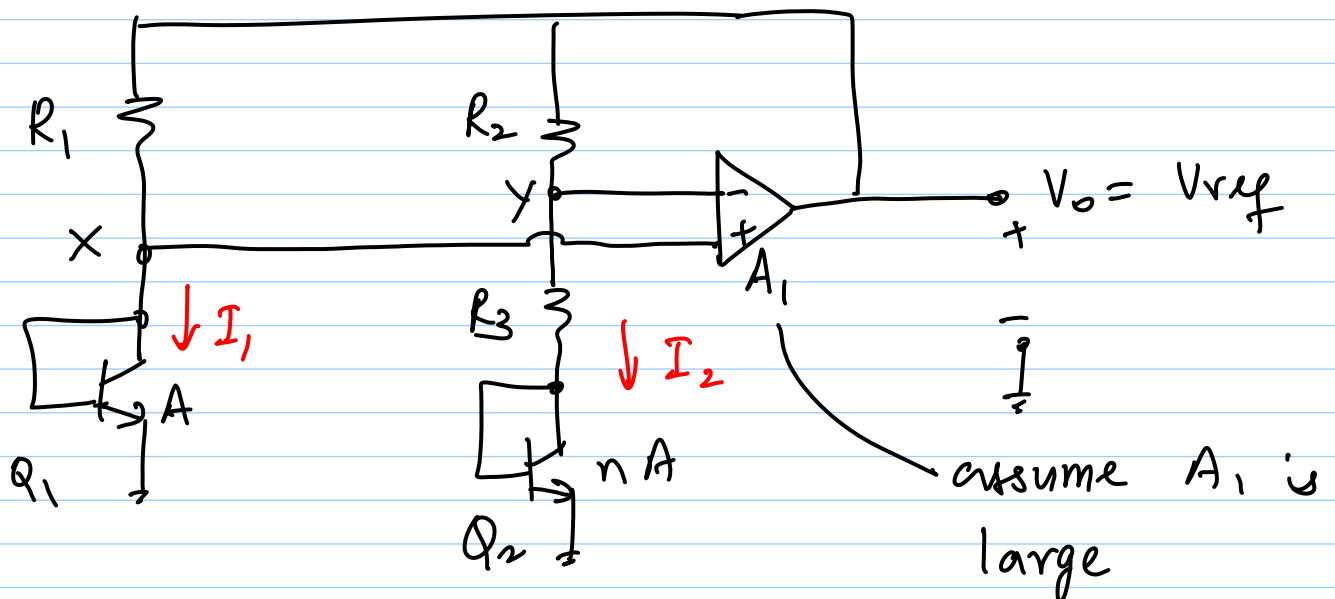

$$\Rightarrow V_X = V_Y \quad (\text{due to f.b. loop})$$

$$V_{BE1} - V_{BE2} = V_T \ln n$$

$$\Rightarrow I_2 = \frac{V_T \ln n}{R_3}$$

$$V_o = V_{BE2} + \frac{V_T \ln n}{R_3} (R_3 + R_2)$$

$$= V_{BE2} + V_T \ln n \left(1 + \frac{R_2}{R_3} \right)$$

for zero T.C.

$$\left(1 + R_2/R_3 \right) \ln n \approx 17.2$$

e.g. $n = 31$ & $\frac{R_2}{R_3} = 4$

also ratio of
R's, so indep.
of res. temp

I_C variation

$$I_{C1,2} \propto \frac{V_T \ln n}{R_3} \propto T$$

we assumed I_C indep. of T

here assume $I_{C1} = I_{C2} = \frac{V_T \ln n}{R_3}$

$$\frac{\partial V_{BE}}{\partial T} = \frac{\partial V_T}{\partial T} \ln \frac{I_C}{I_S} + V_T \left[\frac{1}{I_C} \frac{\partial I_C}{\partial T} - \frac{1}{I_S} \frac{\partial I_S}{\partial T} \right]$$

$$\frac{\partial I_C}{\partial T} \approx \frac{V_T \ln n}{R_3 T} = \frac{I_C}{T}$$

$$\therefore \frac{\partial V_{BE}}{\partial T} = \frac{\partial V_T}{\partial T} \ln \frac{I_C}{I_S} + \frac{V_T}{T} - \frac{V_T}{I_S} \frac{\partial I_S}{\partial T}$$

earlier:
$$\frac{\partial V_{BE}}{\partial T} = \frac{V_{BE} - (4+m)V_T - E_g/q}{T}$$


Now, with I_C :

$$\frac{\partial V_{BE}}{\partial T} = \frac{V_{BE} - (3+m)V_T - E_g/q}{T}$$


→ V_{BE} T-C. is slightly less than -1.5 mV/K

⇒ iterate, simulate for accuracy

In CMOS technology

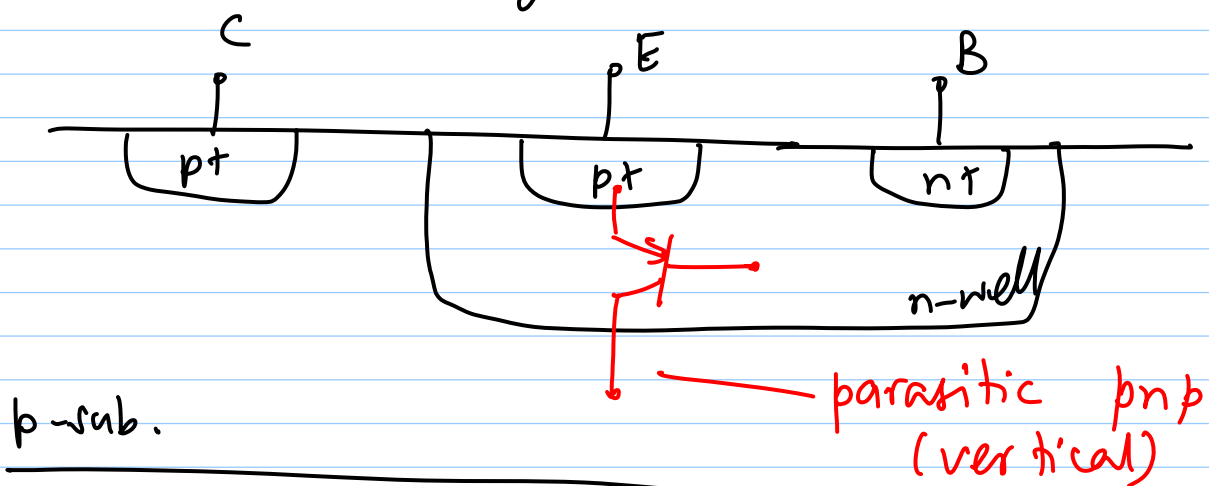

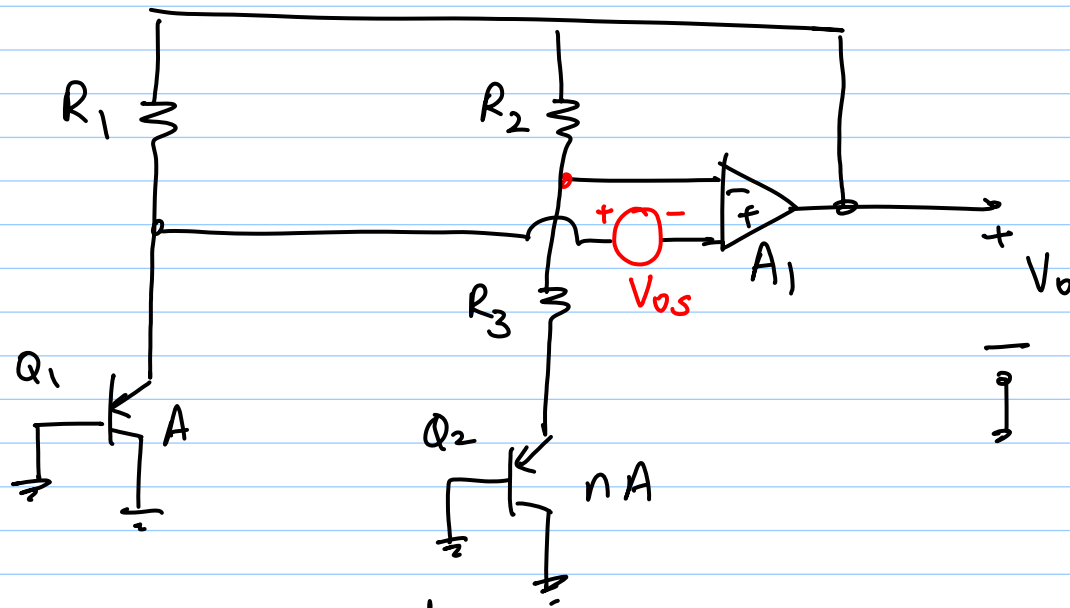- * substrate connected to gnd (C)
- * ckt to be modified to include pnp



Opamp offsets

$$V_{BE1} - V_{os} = V_{BE2} + R_3 I_{C2}$$

$$V_o = V_{BE1} + (R_3 + R_2) I_{C2}$$

$$V_o = V_{BE2} + (R_3 + R_2) \left[\frac{V_{BE1} - V_{BE2} - V_{os}}{R_3} \right]$$


$$= V_{BE2} + \left(1 + \frac{R_2}{R_3} \right) (V_T \ln n - V_{os})$$

* V_{os} is amplified by $(1 + R_2/R_3)$

* We have assumed $I_{C1} \approx I_{C2}$ even in presence of offset

* V_{os} varies with temperature

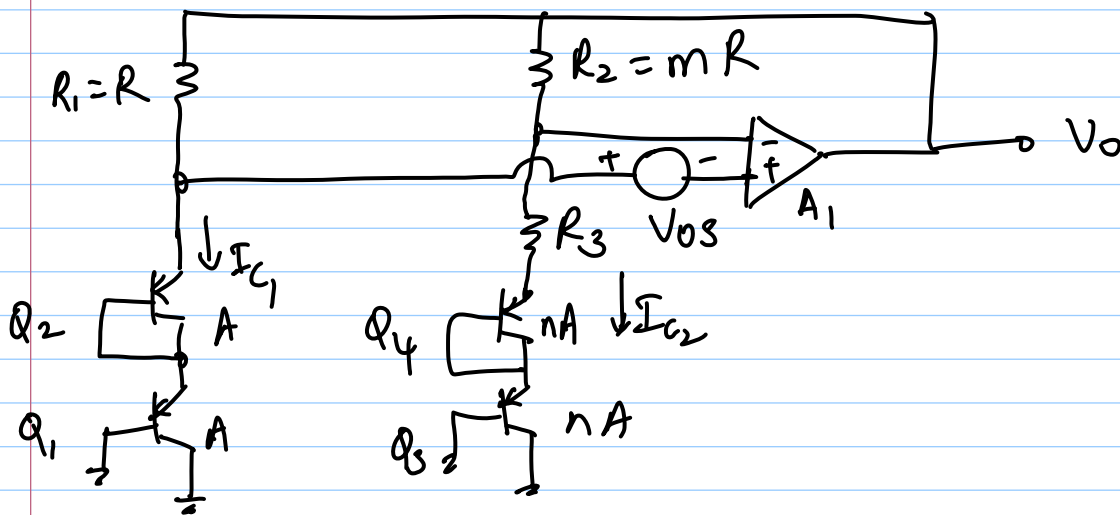- 1) Use opamp with large devices
- 2) make $I_{C1} = m \cdot I_{C2}$
- 3) Use 2 pn junctions in series



$$R_2 = m R_1 \Rightarrow I_{C1} \approx m I_{C2}$$

$$\Rightarrow \Delta V_{BE} \approx V_T \ln(mn)$$

$$\Rightarrow V_{BE1} + V_{BE2} - V_{OS} = V_{BE3} + V_{BE4} + R_3 I_{C2}$$

$$V_{out} = V_{BE3} + V_{BE4} + (R_3 + R_2) I_2$$

$$= V_{BE3} + V_{BE4} + (R_3 + R_2) \left[\frac{2V_T \ln(mn) - V_{OS}}{R_3} \right]$$

$$= 2V_{BE} + \left(1 + \frac{R_2}{R_3} \right) [2V_T \ln(mn) - V_{OS}]$$