

10-4-12

Lec 39


Fractional BE reference


So far, $V_{ref} = V_{BE} + k \cdot \Delta V_{BE}$
 $\approx 1.25V$

What if $V_{DD} < 1.25V$?

$$V_{ref, fr} = \frac{V_{ref}}{k} = \frac{V_{BE}}{k} + \Delta V_{BE}$$

$< 0.4V$ (typically)

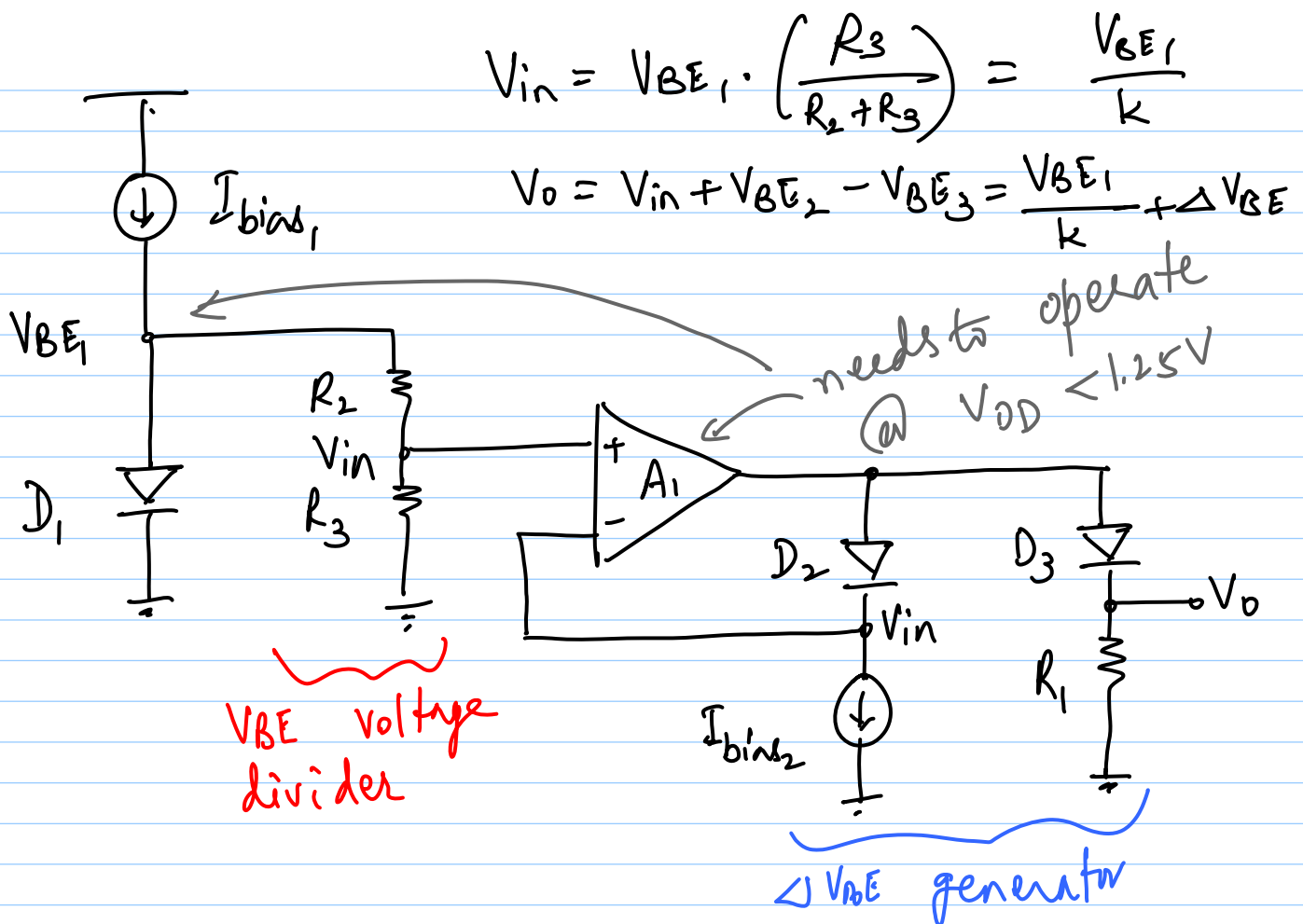

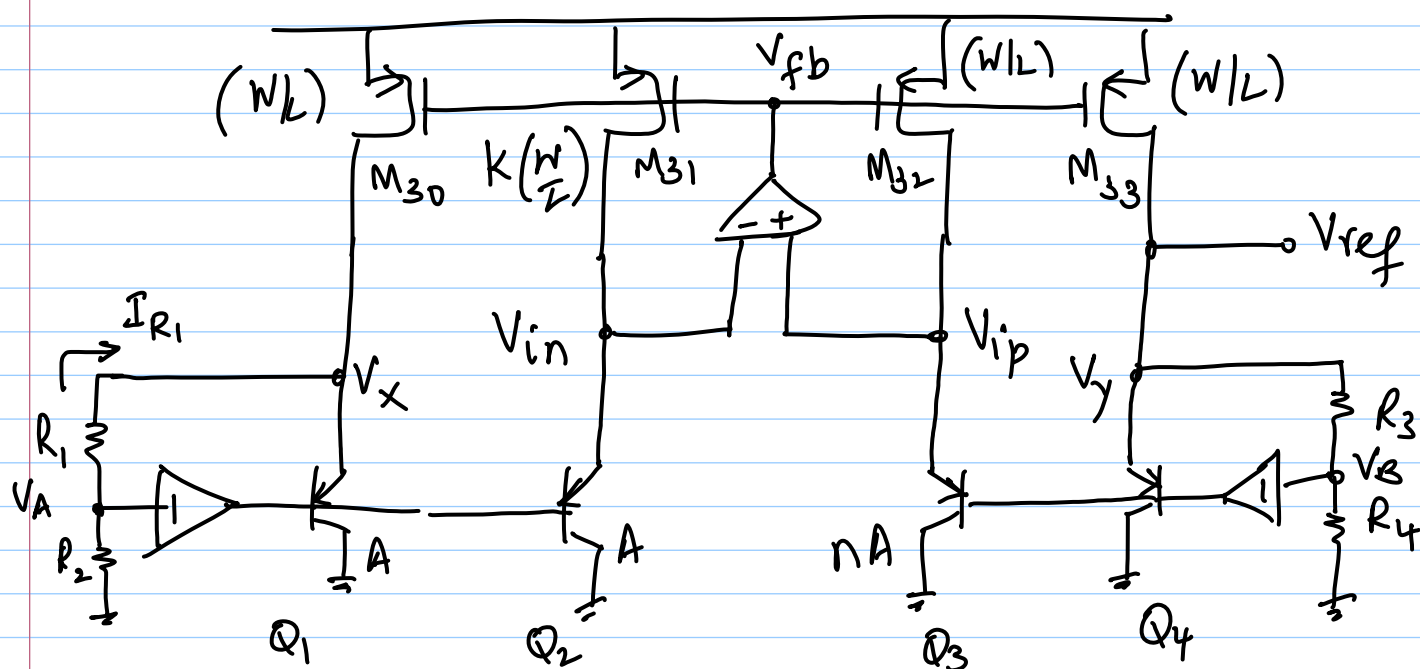

$$\frac{R_1}{R_2} = m > 1$$

$$I_{R_1} = \frac{V_{EB1}}{R_1} \Rightarrow V_A = \frac{V_{EB1}}{R_1} \cdot R_2 = \frac{V_{EB1}}{m}$$

$$V_{in} = \frac{V_{EB1}}{m} + V_{EB2}$$

-ve feedback drives $V_{ip} = V_{in}$

$$\Rightarrow V_B = V_{ip} - V_{EB3}$$

$$= \frac{V_{EB1}}{m} + V_{EB2} - V_{EB3}$$

$$\text{Since } I_{Q2} \neq I_{Q3} \left\{ M_{31} = k M_{32} \right\}$$

$$V_{EB2} - V_{EB3} = \Delta V_{EB} \propto T \quad (\text{PTAT})$$

* choose m so that

$$\frac{\partial}{\partial T} \left(\frac{V_{EB1}}{m} \right) + \frac{\partial}{\partial T} (\Delta V_{EB}) = 0$$



$\Rightarrow V_{R4}$ is temp. insensitive

$$V_{R4} = \frac{V_{EB1}}{m} + \Delta V_{EB} = \frac{V_{B4}}{m}$$

$$V_{Ref} = \frac{V_{B4}}{m} \left(1 + \frac{R_3}{R_4} \right) = \frac{V_{B4}}{m} (1 + \alpha)$$

can easily get $V_{Ref} < 1V$

Output Stages

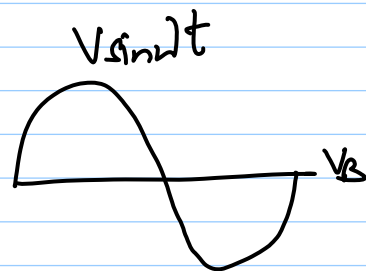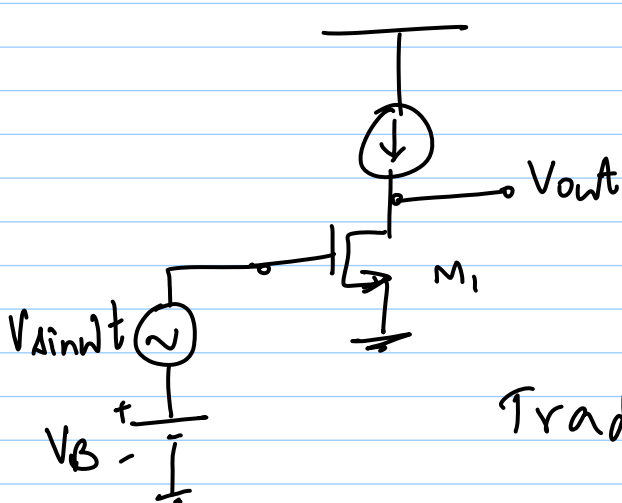

class A


Tradeoffs: Gain, Power efficiency, distortion

* class A $\Rightarrow$ M_1 is always ON

$$(V_B - V_T) > V_T \quad \text{or} \quad (V_B - V_T) > V$$

"Conduction angle" = 360°

* class B : M_1 ON for half cycle

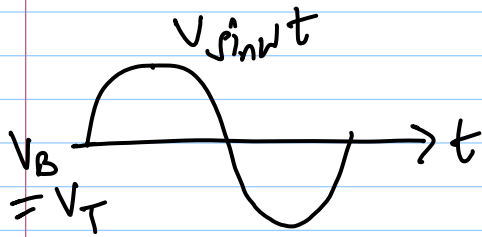


$$\rightarrow V_B = V_T$$

$\rightarrow$ conduction angle $= 180^\circ$

$\rightarrow$ filtering may be required




* class C : $V_B < V_T < V_B + V$

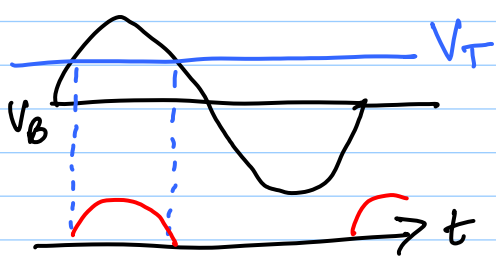

$\rightarrow$ conduction angle $< 180^\circ$

$\rightarrow$ filtering may be required

Class A stage (Emitter follower)

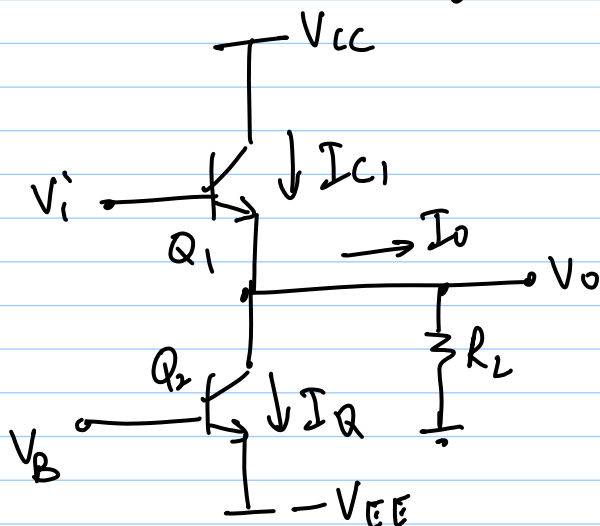

* assume β_0 is large

$$\Rightarrow I_C = I_E$$

$$V_i = V_{be1} + V_o$$

$$V_{be1} = V_T \ln \left(\frac{I_{C1}}{I_{S1}} \right)$$


$$I_{C1} = I_Q + I_O$$

$$= I_Q + \frac{V_o}{R_L}$$

$$* I_{C1} = f(V_o) \Rightarrow V_{be1} = f(V_o)$$

$\Rightarrow$ weak non-linearity
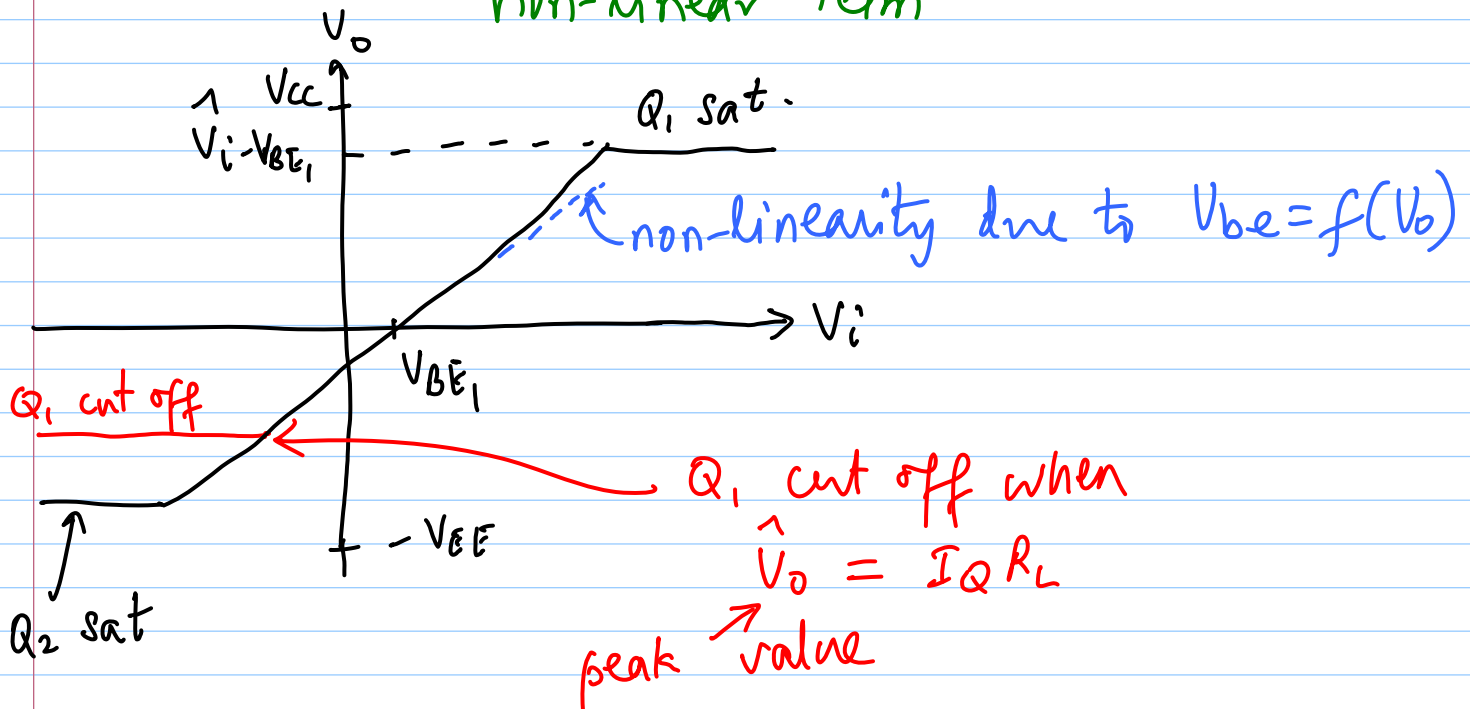
$$V_i = \underbrace{V_T \ln \left[\frac{I_Q + V_o/R_L}{I_{S1}} \right]}_{\text{non-linear term}} + V_o$$



Output range:

* $V_o > 0 \Rightarrow Q_1$ always ON

$$V_{i\max} - V_{BE1} = V_{CC} - V_{SAT1}$$

$$V_{i\max} = V_{CC} + \underbrace{V_{BE1}}_{\sim 0.7V} - \underbrace{V_{SAT1}}_{\sim 0.2V}$$

$\rightarrow V_i$ can exceed V_{CC}

* $V_o < 0 \Rightarrow$ 3 cases:

R_L large, R_L small, R_L/I_Q for max. range

$$I_{C1} = I_Q + \frac{V_o}{R_L}$$

(i) R_L very large $\Rightarrow I_O \approx 0$

$$\Rightarrow I_{C1} \approx I_Q$$

$$V_{i_{min}} - V_{BE1} = -V_{EE} + V_{SAT2}$$

$$\Rightarrow V_{i_{min}} = -V_{EE} + V_{BE1} + V_{SAT2}$$

(ii') R_L small $\Rightarrow I_{C1} = 0$ is possible

this happens @

$$\frac{V_O}{R_L} = -I_Q \Rightarrow V_O = -I_Q R_L$$

$$\Rightarrow V_i = V_{BE1} - I_Q R_L$$

(iii) For max. o/p range $\Rightarrow -I_Q R_L = -V_{EE} + V_{SAT2}$

$$\therefore I_Q = \frac{V_{EE} - V_{SAT2}}{R_L} \quad \left\{ \text{optimum design case} \right\}$$