
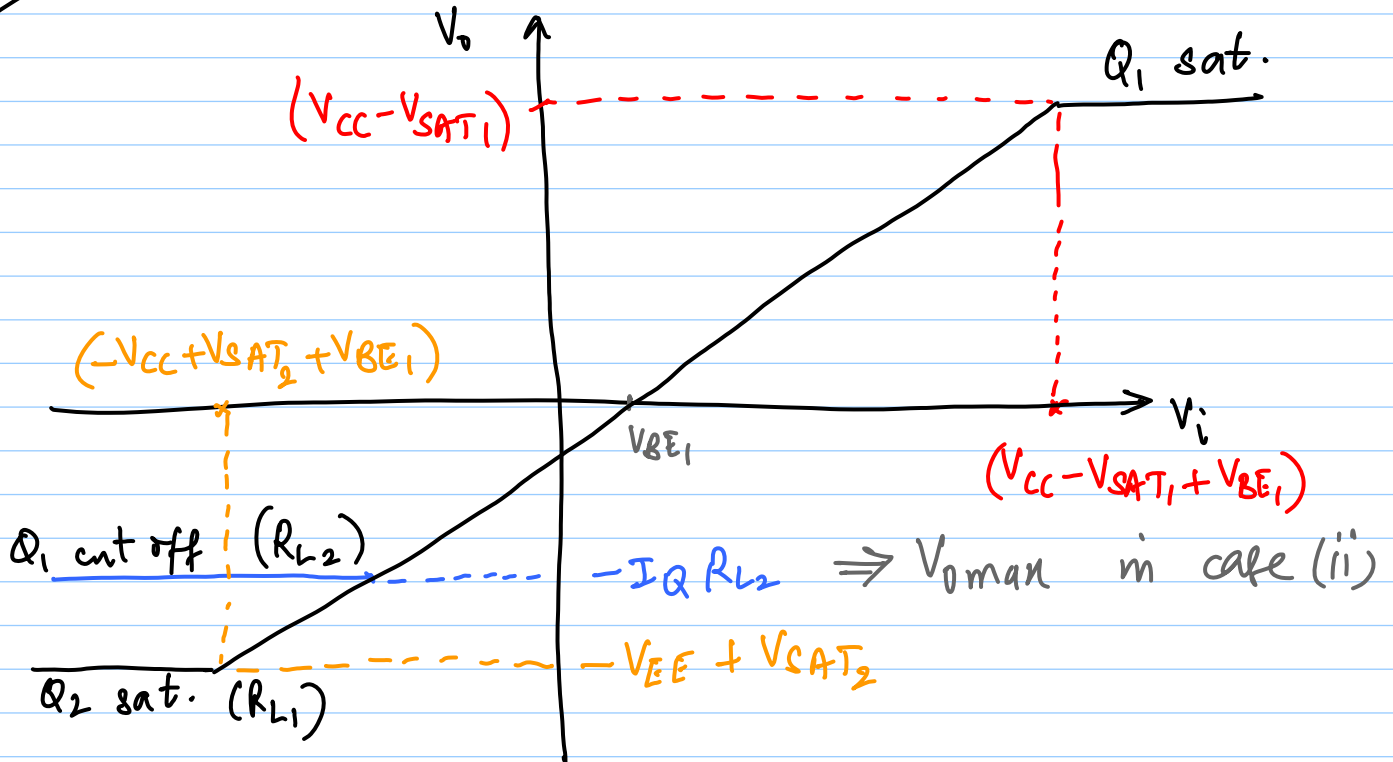


11-4-12

Lec 40

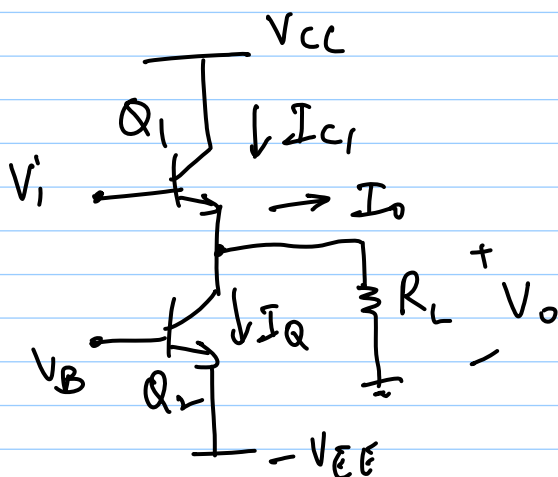



Power Output & Efficiency



$$\begin{aligned}
 V_{CE1} &= V_{CC} - V_o \\
 &= V_{CC} - I_o R_L \\
 &= V_{CC} - (I_{C1} - I_Q) R_L
 \end{aligned}$$

- * Draw load lines for the 3 different cases
- R_{L1} - large R_L
 - R_{L2} - small R_L
 - R_{L3} - optimum R_L

load lines

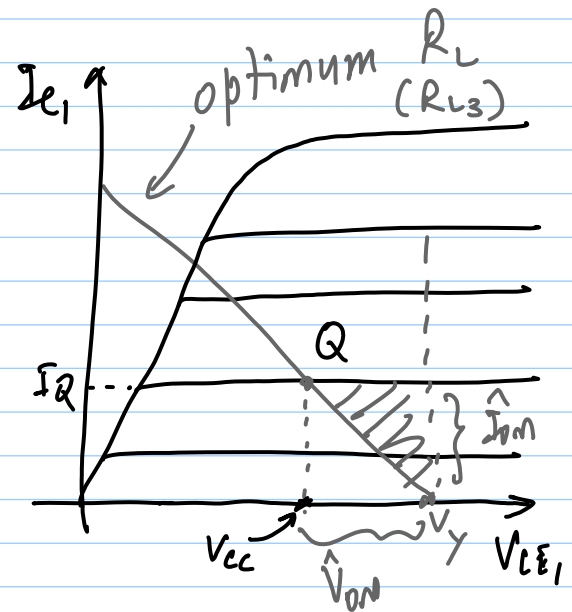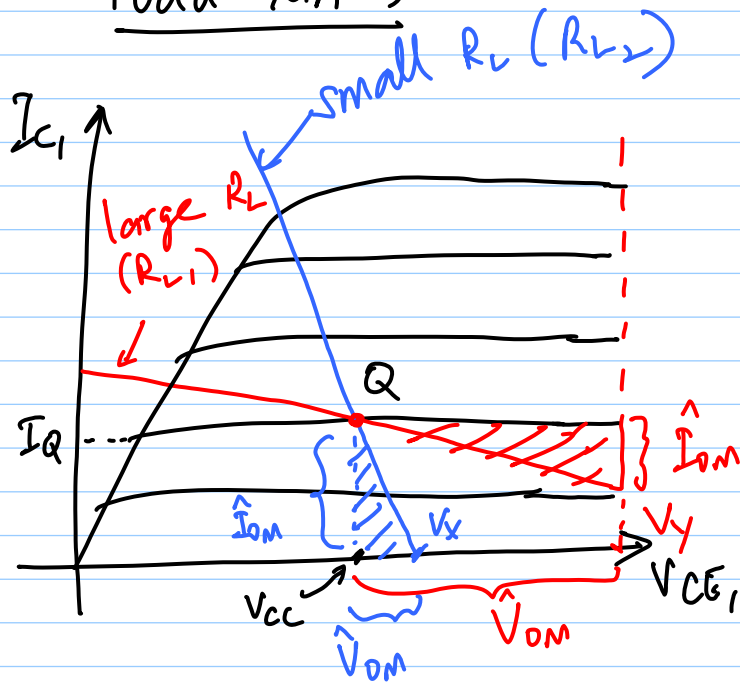

$$V_x = V_{CC} + I_Q R_{L2}$$


$$V_y = 2V_{CC} - V_{SAT2} \quad (V_{CE1, \text{ max.}})$$

$$P_{av.} = \frac{\hat{V}_{om}}{\sqrt{2}} \cdot \frac{\hat{I}_{om}}{\sqrt{2}} = \frac{1}{2} \hat{V}_{om} \hat{I}_{om} \left\{ \begin{array}{l} \text{shaded} \\ \text{area} \\ = \text{power} \end{array} \right\}$$

(i) large R_L - max. V-swing
 $<$ max. I-swing
 $\Rightarrow <$ max. P

(ii) small R_L - max. I-swing
 $<$ max. V-swing
 $\Rightarrow <$ max. P

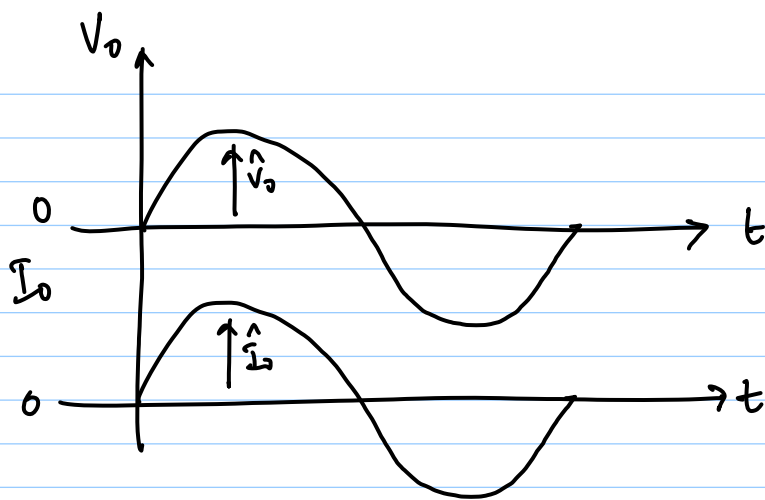(iii) Optimum R_L - max. I-swing
 $\&$ max. V-swing
 $\Rightarrow$ max. P



$$P_L = \text{power delivered to } R_L$$

$$= \frac{1}{2} \hat{V}_o \hat{I}_o$$

$$P_{L, \text{max.}} (\text{case iii}) = \frac{1}{2} \cdot \underbrace{(V_{CC} - V_{SAT})}_{\text{max. swing}} \cdot \underbrace{I_Q}_{\text{max. current}}$$

* Q₁ just cuts-off @ max I-swing

$$P_{\text{supply}} = [V_{CC} - (-V_{EE})] \cdot I_Q = 2V_{CC} I_Q$$



$\eta_c \equiv$ power conversion efficiency

$$= \frac{P_L}{P_{\text{supply}}}$$

$$\eta_c (\text{max.}) = \frac{P_{L, \text{max.}}}{P_{\text{sup.}}} = \frac{\frac{1}{2} (V_{CC} - V_{SAT}) \cdot I_Q}{2V_{CC} I_Q}$$


$$= \frac{1}{4} \left[1 - \frac{V_{SAT}}{V_{CC}} \right] \approx 25\% \quad \{ V_{SAT} \ll V_{CC} \}$$

power dissipated in Q_1 :

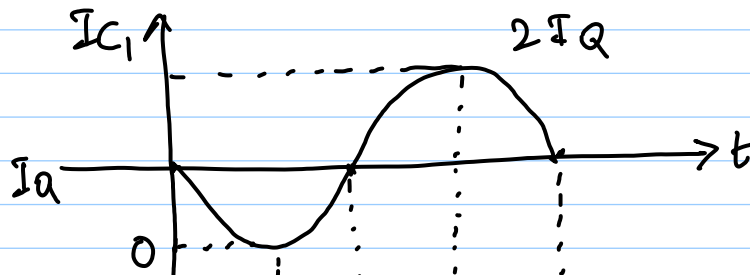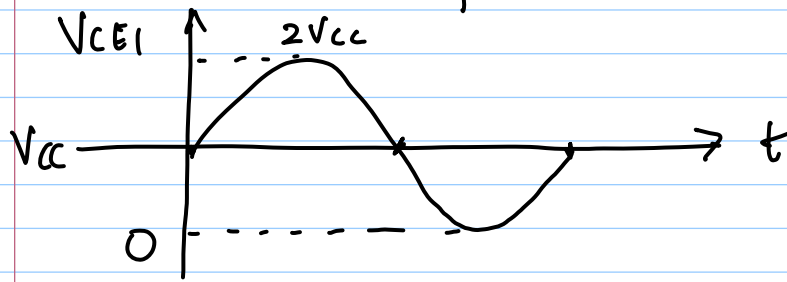

Power cycles

@ 2x input freq.

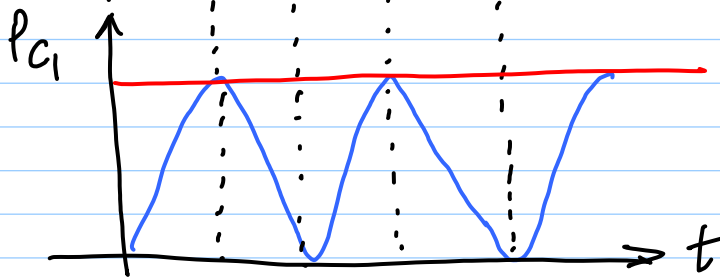

$$P_Q = I_Q \cdot V_{CC}$$

* need to consider both P_{pk} & P_{ave} for device