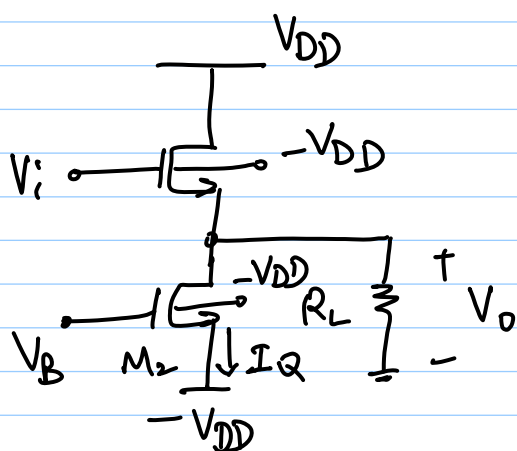


12-4-12

Lec 41

Source follower



$$V_i = V_o + V_{as1}$$

$$= V_o + V_{T1} + V_{ov1}$$

$V_T = \text{fn. of body effect}$

$V_{ov1} = \text{fn. of current}$
(not constant)

$$V_{SB} = V_o + V_{DD}$$


$$I_{D1} = I_Q + V_o/R_L$$

$$\Rightarrow V_i = V_o + V_{T0} + \gamma \left[\sqrt{2\phi_F + V_o + V_{DD}} - \sqrt{2\phi_F} \right] + \sqrt{\frac{2(I_Q + V_o/R_L)}{k'(W/L)_1}}$$

* M_1 & M_2 in active region

* $R_L \gg r_{ds1}, r_{ds2}$

$$V_i|_{V_o=0} = V_{as1} = V_{T0} + \gamma \left[\sqrt{2\phi_F + V_{DD}} - \sqrt{2\phi_F} \right] + \sqrt{\frac{2I_Q}{k'(W/L)_1}}$$

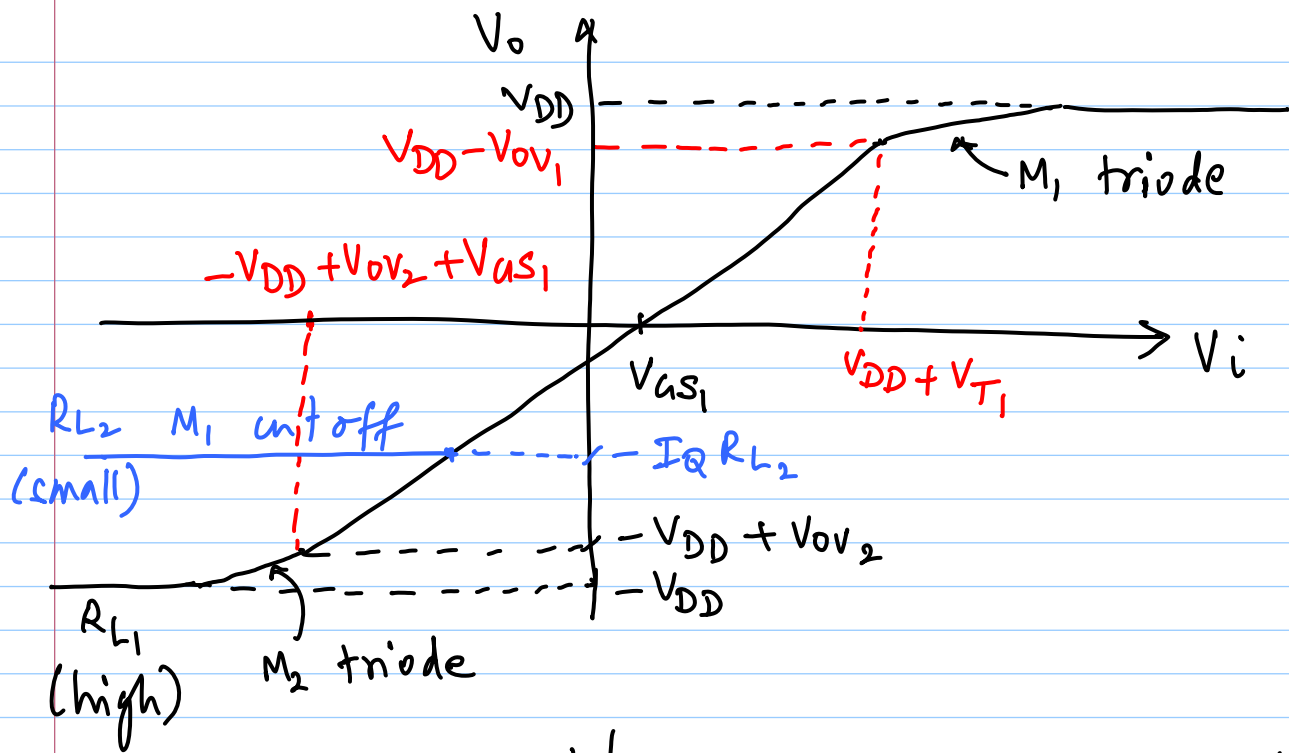

slope @ $V_i/V_o = 0$ point = incremental gain

as $r_o \rightarrow \infty$

$$\frac{v_o}{v_i} = \frac{g_m R_L}{1 + (g_m + g_{mbs}) R_L}$$

as $R_L \rightarrow \infty$,

$$\frac{v_o}{v_i} = \frac{g_m}{g_m + g_{mbs}}$$

* gain = $f(g_{mbs}) = f(V_o + V_{DD})$

$\Rightarrow$ distortion

Distribution in source-follower

Use a Taylor series

$$V_i = V_I + v_i = \sum_{n=0}^{\infty} \frac{f^{(n)}(V_0 = V_\theta)(V_0 - V_\theta)^n}{n!}$$

signal $v_0 =$ total $V_0 - V_\theta$ DC

$$\Rightarrow V_i = V_I + v_i = \sum_{n=0}^{\infty} b_n (v_0)^n$$

$$b_n = f^{(n)}(V_0 = V_\theta) / n!$$

Assume $R_L \rightarrow \infty$ for simplicity

$$V_i = f(V_0)$$

$$= V_0 + V_{T0} + \gamma \left[\sqrt{V_0 + V_{DD} + 2\phi_F} - \sqrt{2\phi_F} \right] + V_{ov1}$$

$$f'(V_0) = 1 + \frac{\gamma}{2} (V_0 + V_{DD} + 2\phi_F)^{-1/2}$$

$$f''(V_0) = -\frac{\gamma}{4} (V_0 + V_{DD} + 2\phi_F)^{-3/2}$$

$$f'''(V_0) = \frac{3\gamma}{8} (V_0 + V_{DD} + 2\phi_F)^{-5/2}$$

$$b_0 = f(V_0 = V_\theta) = V_\theta + V_{T0} + \gamma \left[\sqrt{V_\theta + V_{DD} + 2\phi_F} - \sqrt{2\phi_F} \right] + V_{ov1}$$

$$b_1 = f'(V_0 = V_\theta) = 1 + \frac{\gamma}{2} \left(\overbrace{V_\theta + V_{DD} + 2\phi_f}^x \right)^{-1/2}$$

$$b_2 = \frac{f''(V_0 = V_\theta)}{2} = -\frac{\gamma}{8} (x)^{-3/2}$$

$$b_3 = \frac{f'''(V_0 = V_\theta)}{3!} = \frac{\gamma}{16} (x)^{-5/2}$$

$$b_0 = V_I = \text{DC input voltage}$$

$$\Rightarrow v_i = \sum_{n=1}^{\infty} b_n (V_0)^n = b_1 V_0 + b_2 V_0^2 + b_3 V_0^3 + \dots$$

To find distortion, we want

$$V_0 = \sum_{n=1}^{\infty} a_n (v_i)^n = a_1 v_i + a_2 v_i^2 + \dots$$

$$\Rightarrow v_i = b_1 (a_1 v_i + a_2 v_i^2 + \dots) + b_2 (a_1 v_i + a_2 v_i^2 + \dots)^2 + \dots$$

Match coefficients on both sides

$$1 = b_1 a_1$$

$$0 = b_1 a_2 + b_2 a_1^2$$

$$0 = b_1 a_3 + 2 b_2 a_1 a_2 + b_3 a_1^3$$

$$\Rightarrow \left. \begin{array}{l} a_1 = 1/b_1 \\ a_2 = -\frac{b_2}{b_1^3} \end{array} \right| a_3 = \frac{2b_2^2}{b_1^5} - \frac{b_3}{b_1^4}$$

$$\therefore a_1 = \frac{1}{1 + \frac{\gamma}{2} (x)^{-1/2}}$$

$$a_2 = \frac{\frac{\gamma}{8} (x)^{-3/2}}{\left[1 + \frac{\gamma}{2} (x)^{-1/2}\right]^3}$$

$$a_3 = -\frac{\frac{\gamma}{16} (x)^{-5/2}}{\left[1 + \frac{\gamma}{2} (x)^{-1/2}\right]^5}$$

can be
used to
calculate
distortion
of MOS
source follower
stage

* Amplifier non-linearity specified by
Harmonic Distortion (HD)

$$\text{let } v_i = \hat{v}_i \sin \omega t$$

$$v_o = a_1 \hat{v}_i \sin \omega t + a_2 \hat{v}_i^2 \sin^2 \omega t$$

$$+ a_3 \hat{v}_i^3 \sin^3 \omega t + \dots$$

$$= a_1 \hat{v}_i \sin \omega t + \frac{a_2 \hat{v}_i^2}{2} (1 - \cos 2\omega t)$$

$$+ \frac{a_3 \hat{v}_i^3}{4} (3 \sin \omega t - \sin 3\omega t) + \dots$$

* o/p contains freq. components @
 $\omega, 2\omega, 3\omega \dots$

distortion products

$$HD_2 = \frac{\text{amplitude of } 2\omega \text{ component}}{\text{" " } \omega \text{ " "}}$$

$$HD_2 \approx \frac{a_2 \hat{v}_i^2}{2} \cdot \frac{1}{a_1 \hat{v}_i} = \frac{1}{2} \frac{a_2}{a_1} \hat{v}_i$$

$\rightarrow HD_2$ varies linearly with $\hat{v}_i$

$$HD_2 \approx \frac{\frac{\gamma}{16} (x)^{-3/2} \cdot \hat{v}_i}{\left[1 + \frac{\gamma}{2} (x)^{-1/2}\right]^2}$$

$$\text{If } \gamma \ll 2 \sqrt{V_0 + V_{DD} + 2\phi_F},$$

$$HD_2 \approx \frac{\gamma}{16} (V_0 + V_{DD} + 2\phi_F)^{-3/2} \hat{v}_i$$

* $HD_2 \downarrow$ if $V_0 \uparrow$ (DC level @
 output $\uparrow$)

$\rightarrow \therefore$ distortion produced from body effect

* $HD_2 \propto \gamma$

$$HD_3 = \frac{\hat{v}_o(3\omega)}{\hat{v}_o(\omega)}$$

$$= \frac{\frac{a_3 \hat{v}_i^3}{4}}{a_1 \hat{v}_i} = \frac{1}{4} \cdot \frac{a_3}{a_1} \hat{v}_i^2$$

* $HD_3 \uparrow$ as $\hat{v}_i^2$

$$HD_3 \approx \frac{-\frac{\gamma}{64} (x)^{-5/2} \hat{v}_i^2}{\left[1 + \frac{\gamma}{2} (x)^{-1/2}\right]^4}$$

Class-B push-pull stage

