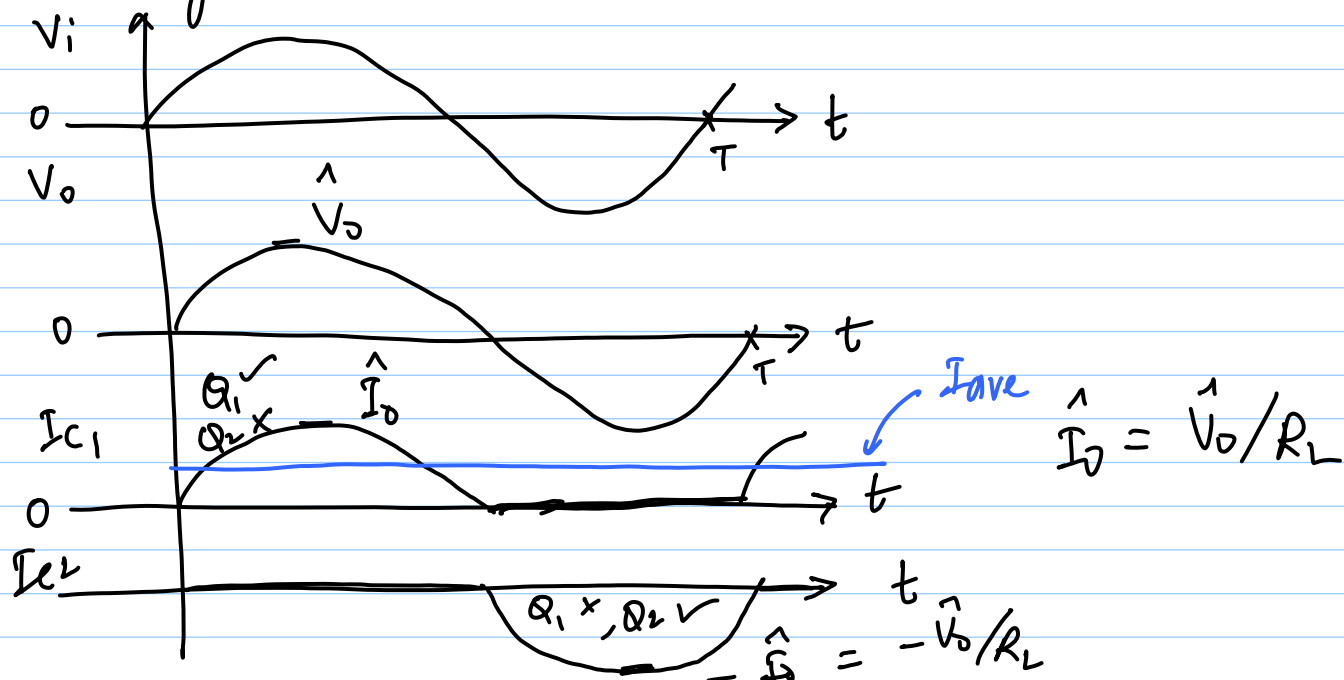


17-4-12

Lec 42

Class-B Pont & η_c

* neglect dead band



$I_{supply} \equiv$ average value of I_{c1}

$$= \frac{1}{T} \int_0^T I_{c1}(t) dt$$

$$= \frac{1}{T} \int_0^{T/2} \frac{V_o}{R_L} \sin\left(\frac{2\pi t}{T}\right) dt$$

$$= \frac{1}{\pi} \frac{V_o}{R_L} = \frac{1}{\pi} \hat{I}_o = \text{average value of } I_{c2}$$

$$P_{supply} = 2V_{cc} I_{sup} = \frac{2}{\pi} V_{cc} \cdot \frac{V_o}{R_L}$$

* $P_{\text{supply}} \propto \hat{V}_o$ for class B stage

$P_L \equiv$ average power delivered to load

$$= \frac{1}{2} \frac{\hat{V}_o^2}{R_L}$$

$$\eta_c = \frac{P_L}{P_{\text{sup}}} = \frac{\frac{1}{2} \frac{\hat{V}_o^2}{R_L}}{\frac{\pi}{2} \frac{V_{CC}}{R_L} \hat{V}_o}$$

$$= \frac{\pi}{4} \frac{\hat{V}_o}{V_{CC}}$$

* $\eta_c \propto \hat{V}_o/V_{CC}$ but is independent of R_L

$$\eta_c (\text{max.}) = \frac{P_L (\text{max.})}{P_{\text{sup}}}$$


$$= \frac{\pi}{4} \frac{\hat{V}_{\text{om}}}{V_{CC}}$$

$$= \frac{\pi}{4} \frac{(V_{CC} - V_{\text{SAT}})}{V_{CC}}$$

$$= \frac{\pi}{4} \left[1 - \frac{V_{\text{SAT}}}{V_{CC}} \right]$$

$\approx 78.6\%$ $\leftarrow$ much larger than class A

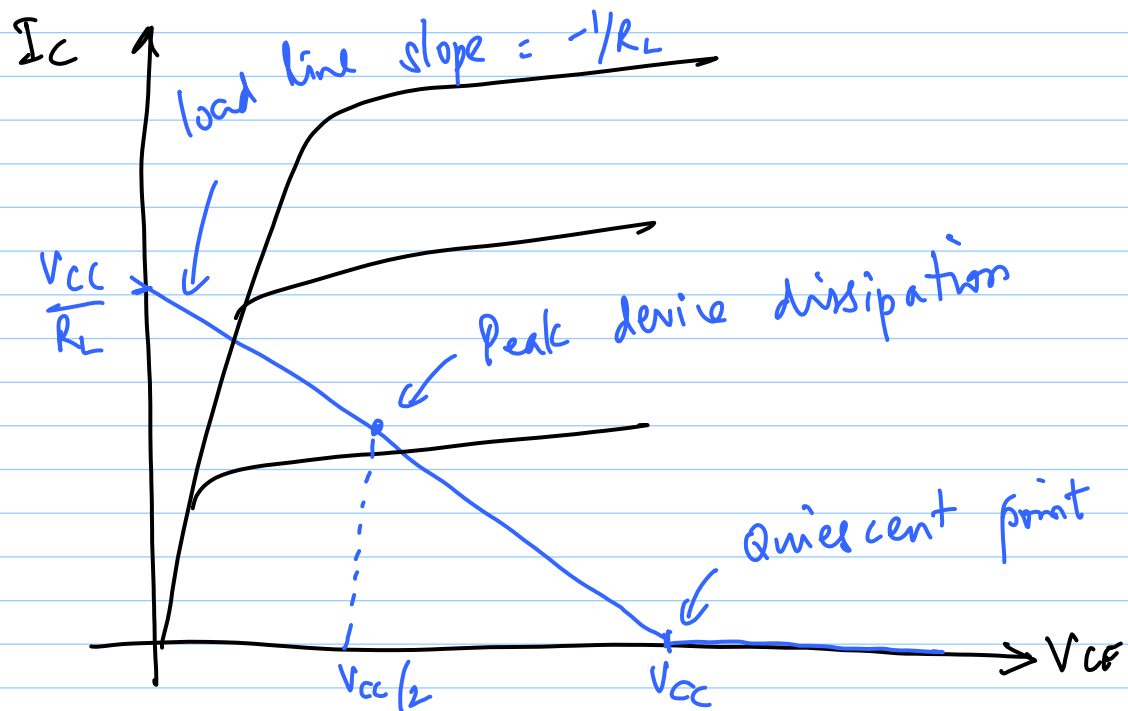- * Standby power consumption is zero
- * very high eff. η_c ($\Rightarrow$ class A)




$$P_c = I_c \cdot V_{ce}$$

$$= I_c [V_{cc} - I_c R_L]$$


$$= I_{cc} V_{cc} - I_c^2 R_L$$

$$\frac{\partial P_c}{\partial I_c} = 0 \Rightarrow I_c \Big|_{P_{cmax.}} = \frac{V_{cc}}{2R_L}$$

$$\Rightarrow V_o \Big|_{P_{cmax.}} = \frac{V_{cc}}{2}$$

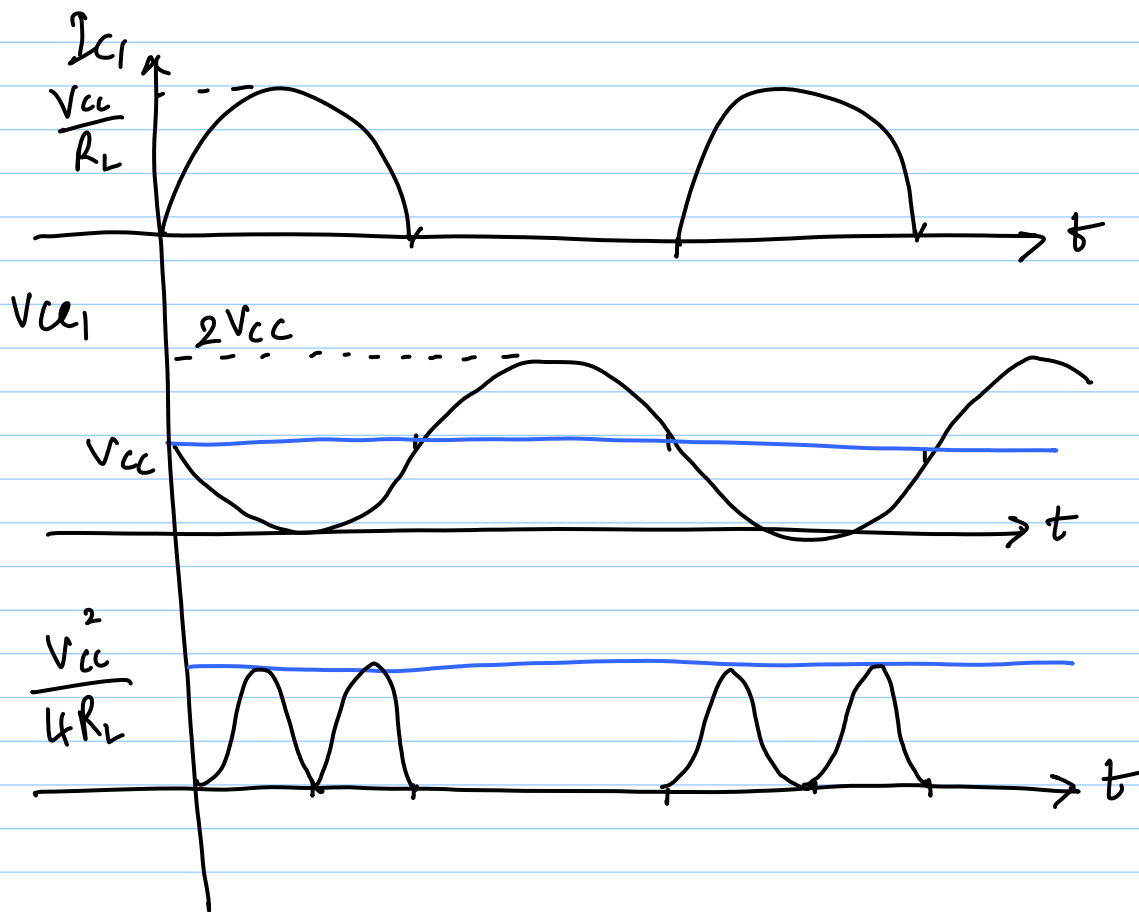


Crossover Distortion

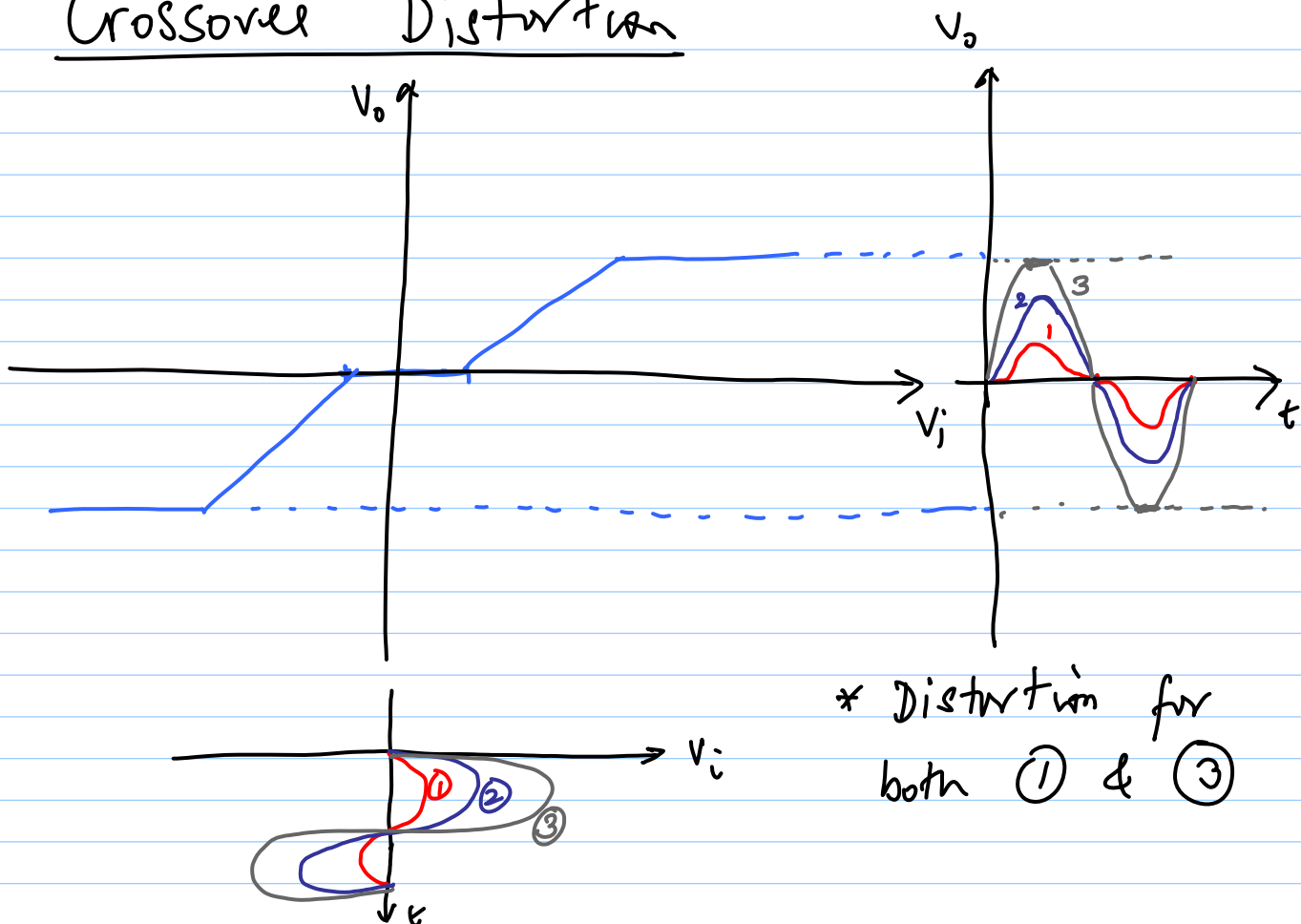


* Distortion for both ① & ③

Class AB output stage

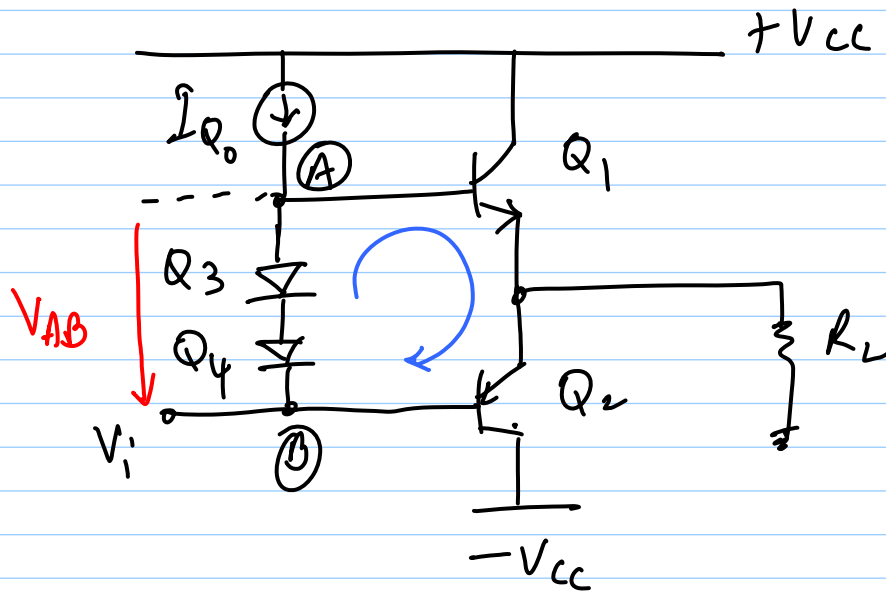- * Q_1 & Q_2 should conduct with small I_Q
- @ $V_i = 0$



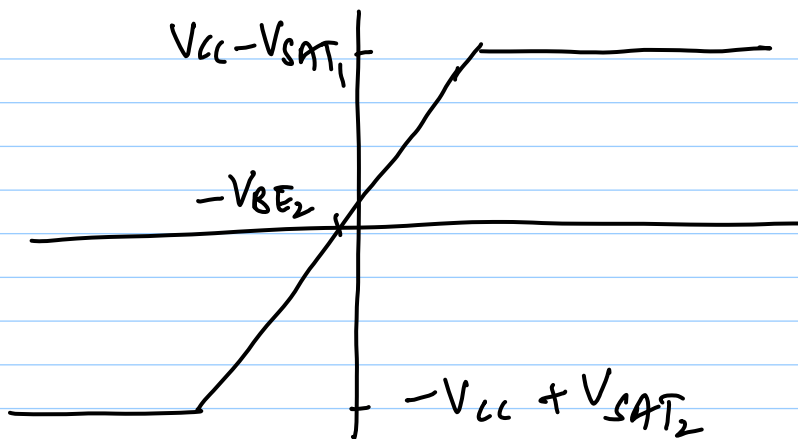* $I_{Q1,2}$ depends on area ratios of $Q_1 - Q_4$




* $V_{AB} = \text{constant} \Rightarrow |V_{BE1}| = |V_{BE2}|$

* When $V_o < 0$, Q_1 is on, but delivers no power (I_{E1} is very small)


$V_i/V_o > 0 \Rightarrow Q_1$ delivers power

Q_2 is on, but small I_{E2}

741 output stage

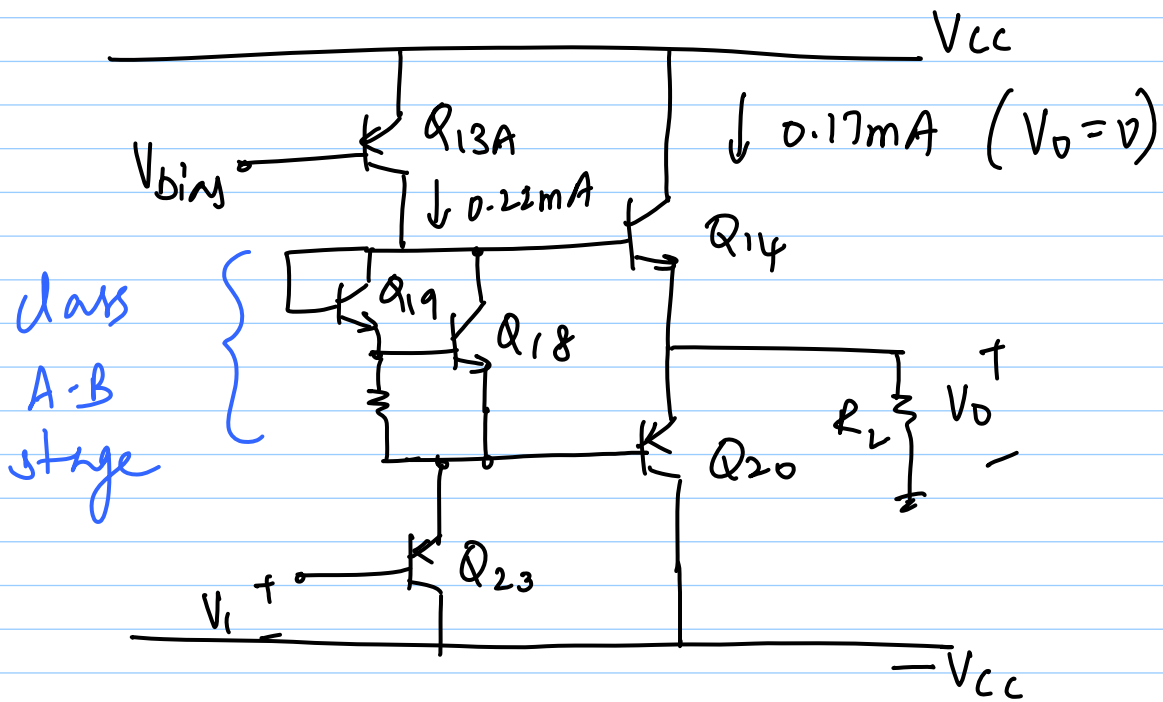

CMOS class AB stages

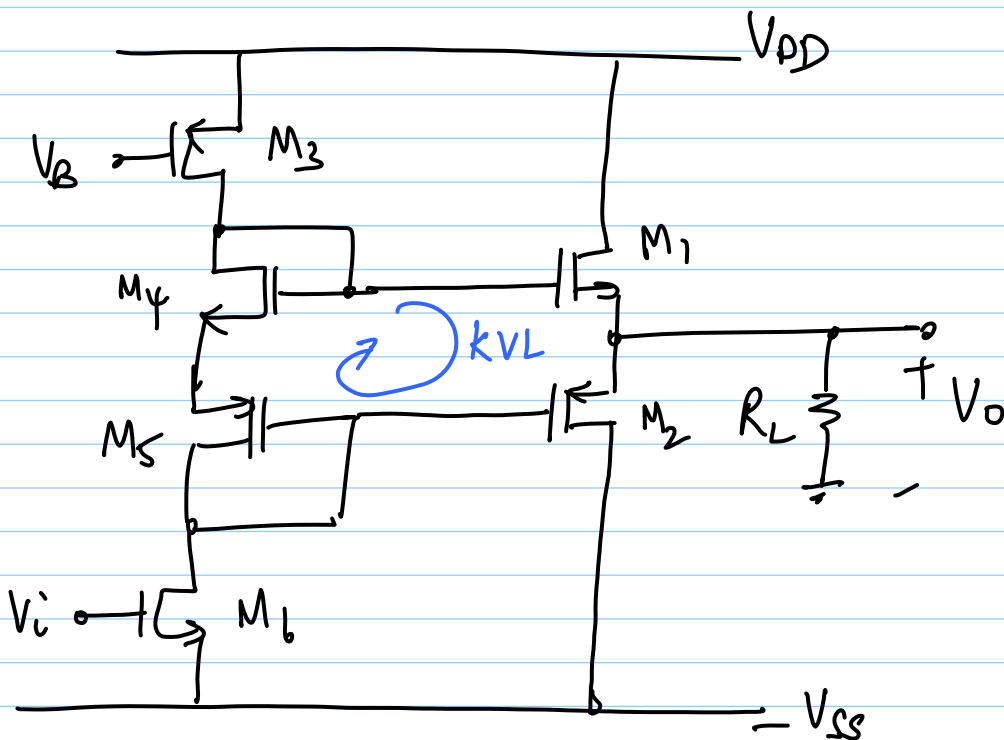

KVL $V_{S_{n5}} + V_{A_{S4}} = V_{gs1} + V_{gs2}$

* ignore Body Effect

If $I_{D3} = \text{constant}$, $V_{S_{n5}} + V_{A_{S4}} = \text{constant}$

* Initially assume $V_{S_{n5}} + V_{A_{S4}} = 0$

$$\Rightarrow V_{gs1} = V_{gs2}$$

M_1 is ON when

$$V_{gs1} > V_{T1}$$

M_2 " " "

$$V_{gs2} < V_{T2}$$

$$V_{T1} > 0$$

$$V_{T2} < 0$$

$\Rightarrow$ class B stage

* If $V_{S_{n5}} + V_{A_{S4}} > 0 \Rightarrow M_1 \& M_2$ are

ON when $V_o = 0 \Rightarrow$ class AB operation

1) assume $V_{T1} = V_{T4}$ & $V_{T2} = V_{T5}$

2) $I_{D5} = -I_{D4}$

$$\sqrt{\frac{2I_{D4}}{k_p'(W/L)_5}} + \sqrt{\frac{2I_{D4}}{k_n'(W/L)_4}} = \sqrt{\frac{2I_{D1}}{k_n'(W/L)_1}} + \sqrt{\frac{2|I_{D2}|}{k_p'(W/L)_2}}$$

$$V_o = 0 \Rightarrow I_{D2} = -I_{D1}$$

$$\therefore I_{D1} = I_{D4} \cdot \frac{\frac{1}{k_n'(W/L)_4} + \frac{1}{k_p'(W/L)_5}}{\frac{1}{k_n'(W/L)_1} + \frac{1}{k_p'(W/L)_2}}$$


for $V_o > 0$,

$$V_o = V_{DD} - V_{sd3} - V_{gs1}$$

$$\Rightarrow V_{om}^+ = V_{DD} - |V_{ov3}| - V_{gs1}$$

(Worse than bipolar case)

Error Amplifiers (CS config.)

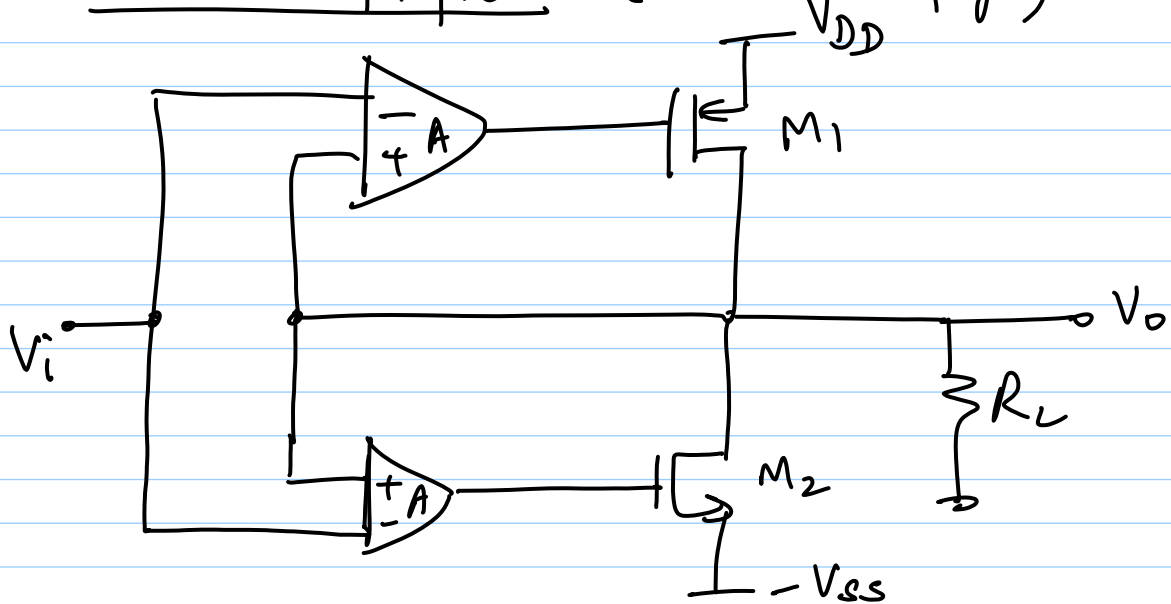

* Error amps drive $V_i = V_o$ (-ve f.b.)

$$* R_o = r_{o1} \parallel r_{o2} \parallel \frac{1}{(g_{m1} + g_{m2})A}$$

$$\uparrow A \Rightarrow \downarrow R_o$$

$$* V_o = \frac{V_i}{1 + \frac{1}{2A_{gm}R_L}} \approx V_i \left[1 - \frac{1}{2A_{gm}R_L} \right]$$

$$* LG = 2A_{gm}R_L$$

* Analyse errors due to offsets