
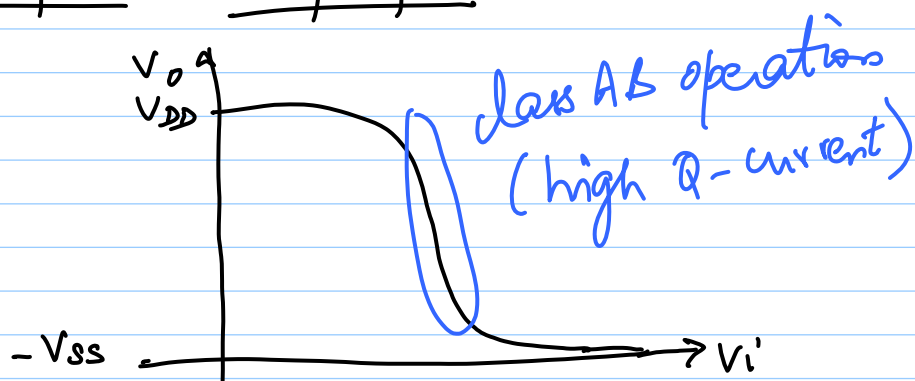



18-4-12

Lec 43

CMOS push-pull amplifier

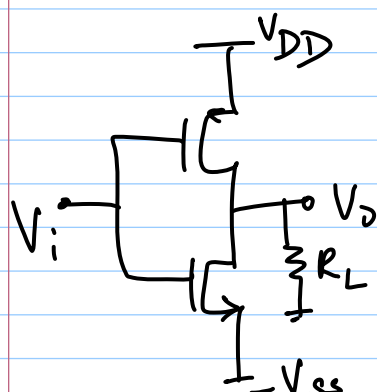

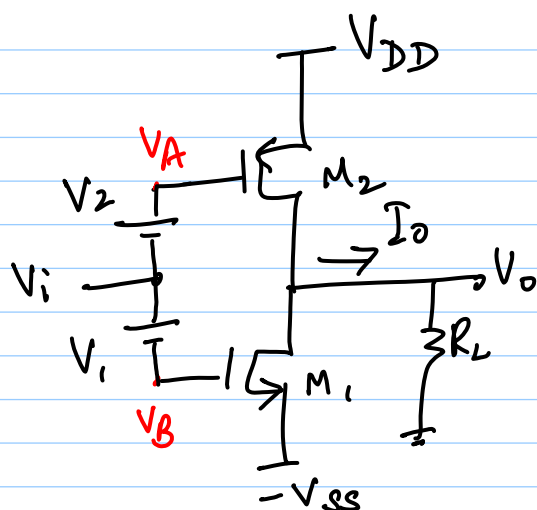* high $I_Q \Rightarrow$ low η in high gain region



* η is improved by adding V_1, V_2

* $V_i = V_{T1}$ &

V_1 & V_2 are such that


$$V_A = V_{DD} - V_{T2}$$

* If V_i is +ve $\Rightarrow$ M_2 OFF, M_1 sinks I_o

* If V_i is -ve $\Rightarrow$ M_1 OFF, M_2 supplies I_o

$\rightarrow$ no current is wasted, all I flows thro' R_L

$\rightarrow R_o$ is not reduced

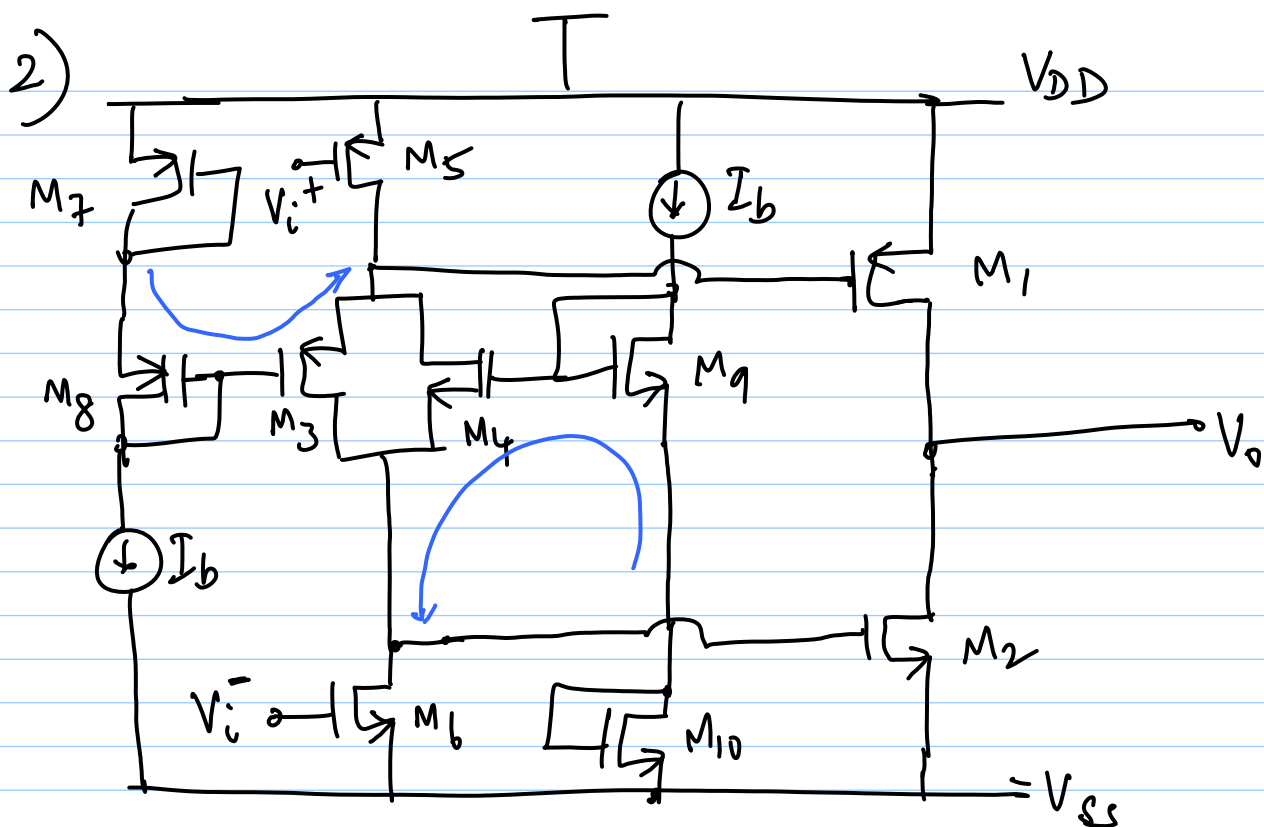

* Steady state : $I_s = I_b = 2I_b$

$$\{M_4 = M_9 \text{ \& } M_3 = M_8\}$$

$$I_1 = I_2 = I_b \cdot \frac{(W/L)_1}{(W/L)_7} = I_b \cdot \frac{(W/L)_2}{(W/L)_{10}}$$

* $V_{i+} \downarrow \Rightarrow M_5$ pulls V_{n1} & V_{n2} high

$\Rightarrow M_4$ turns OFF

$\Rightarrow 2I_b$ flows through M_3


$\Rightarrow M_1$ turns OFF & M_2 is strongly ON

* $V_{i-} \uparrow \Rightarrow M_6$ pulls V_{n1} & V_{n2} low

$\Rightarrow M_2$ OFF & M_1 is ON

Reducing R_o (-ve feedback)

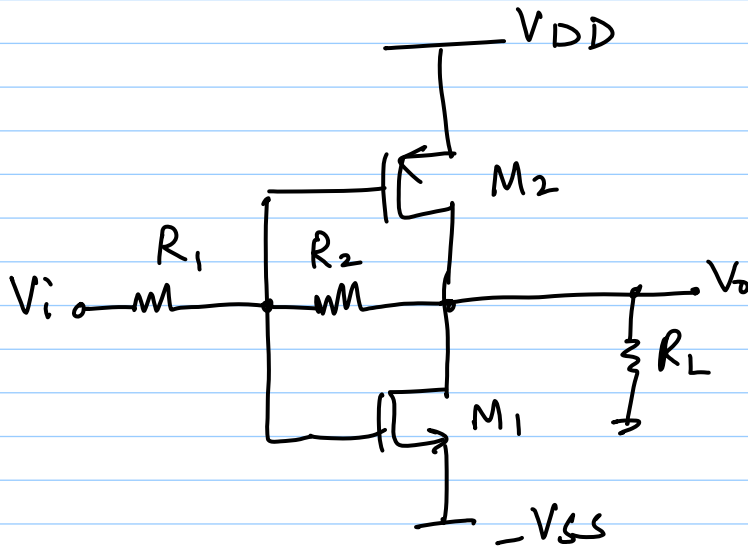
- * Use of error amps (last class)
- * Can also use resistive f.b.



$$R_o \approx \frac{R_{o\text{original}}}{(g_m R_L / 2)}$$


when $R_1 = R_2$
(HW)

For Source follower :

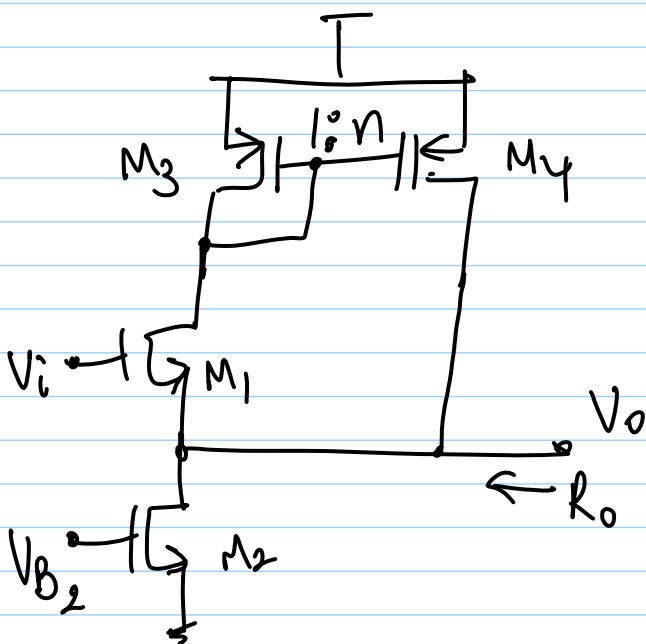

$$R_o = \frac{1}{g_{m1} \cdot n}$$

All-npn class B output stage

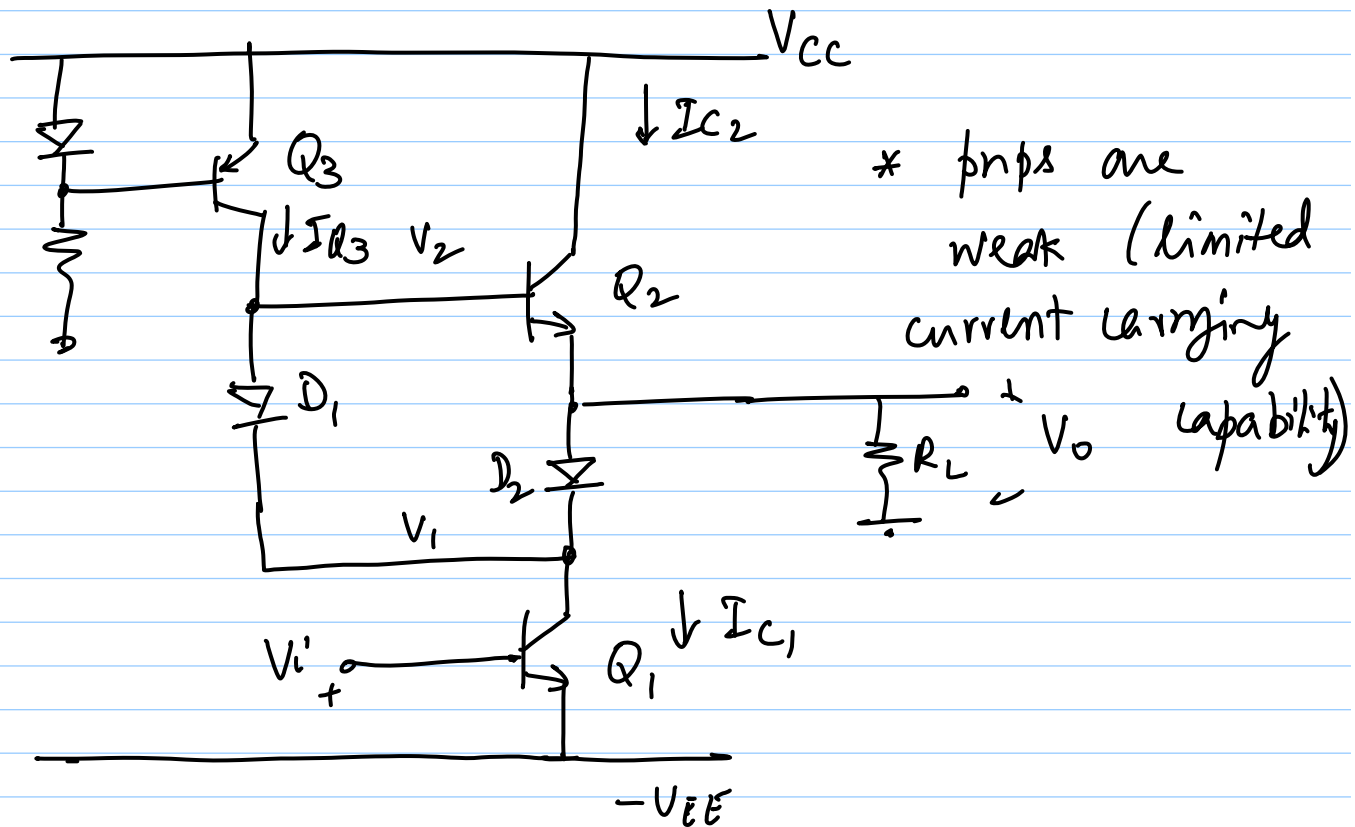

* npns have low current-carrying capability
 $\Rightarrow$ Use npn in both halves of class B ckt

* $V_i < V_{iQ} \Rightarrow Q_1 \text{ OFF}, I_{C1} = 0$
 $\rightarrow D_1 \text{ \& } D_2 \text{ OFF}$
 $\rightarrow I_{Q3} = I_{b2}$
 $\rightarrow V_o = V_o(\text{max.})$) Q_2 in emitter follower config.

* If R_L is large, Q_3 goes into SAT.

$$V_{om}^+ = V_{cc} - V_{SAT3} - V_{be2}$$

$Q_2 \rightarrow$ cannot saturate

$$V_{om}^+ = -I_{e2} R_L = (\beta_2 + 1) I_{b2} R_L$$

for Q_3 to be saturated,

$$I_{Q3} (Q_3 \text{ not in SAT}) > I_{b2}$$

$$\Rightarrow I_{Q3} > \frac{V_{CC} - V_{SAT3} - V_{be2}}{(\beta_2 + 1) R_L} \quad \text{optimum point}$$

* $V_i > V_{iQ}$ (+ve) $\Rightarrow Q_1$ ON, $I_{c1} > 0$

$\rightarrow D_1$ turns ON first

$$V_{D1} = V_{be2} + V_{D2}$$

$\rightarrow V_2 \downarrow \Rightarrow V_o$ follows V_2 (emitter follower)

$\Rightarrow Q_1$ acts as driver & Q_2 is o/p device

$$* V_o = 0 \Rightarrow I_o = 0 \Rightarrow I_{c2} = 0$$

$$\Rightarrow I_{c1} = I_{Q3}$$

as $I_{c1} \uparrow$, V_o stays @ 0 till $V_2 = 0$


$\rightarrow D_2$ turns ON

$$* V_o < 0 \Rightarrow I_{D1} = I_{Q3}$$

$\rightarrow I_{c1} - I_{Q3}$ flows through D_2 & R_L

Q_1 acts as o/p device
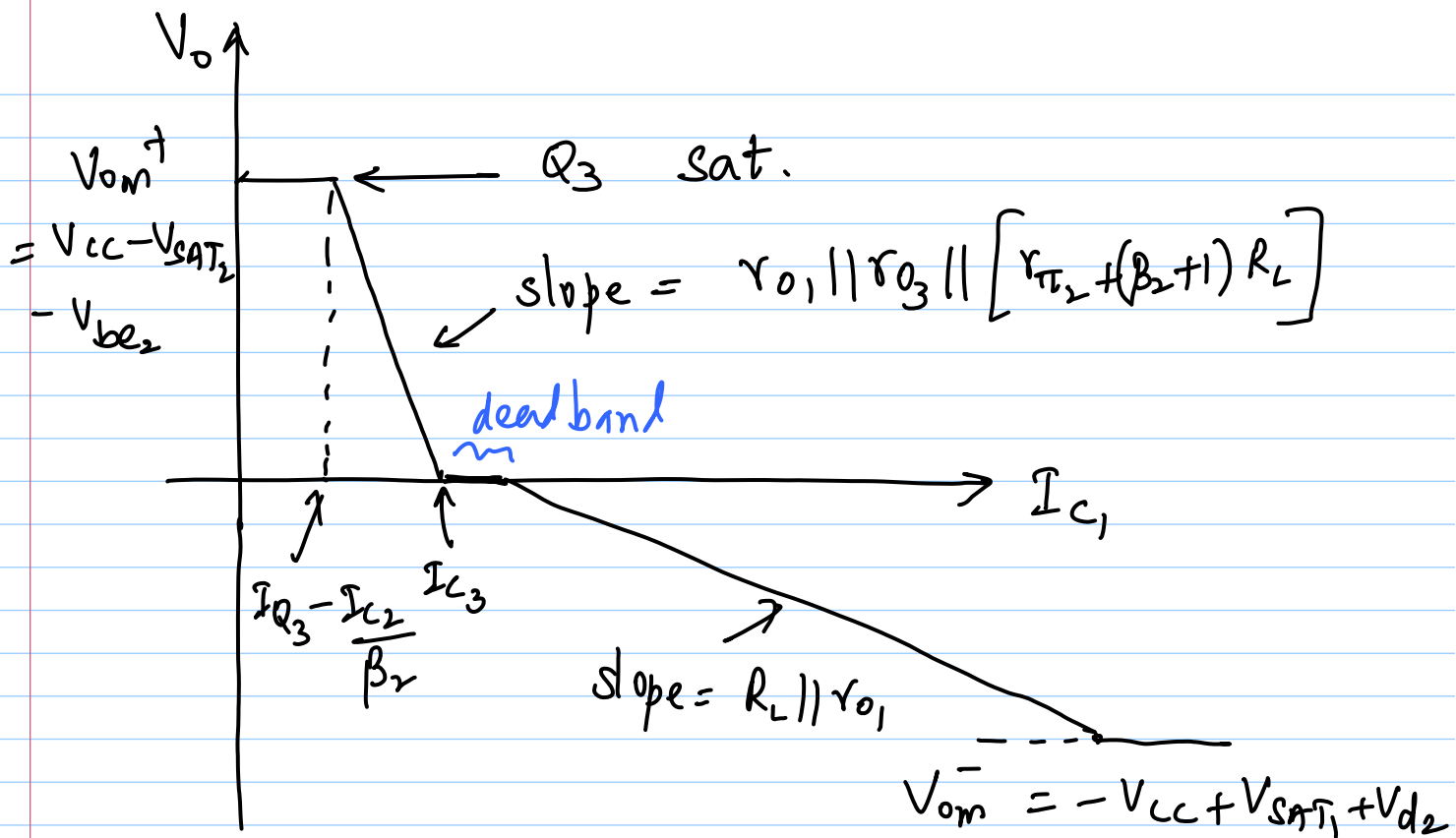
$$V_{om}^- = -V_{CC} + V_{SAT1} + V_{d2}$$




* eliminate deadband $\rightarrow$ add another diode in series with D_1

* highly non-linear

$\rightarrow$ use feedback to linearise

* $V_i - V_o$ is even more non-linear (exponential relation I_{c1} to V_{be1})

Quasi-complementary

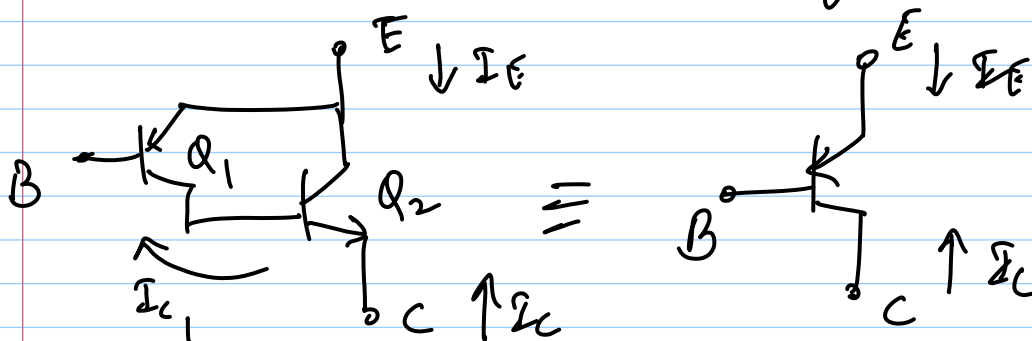

$$I_{C1} = -I_S \exp\left(-\frac{V_{BE}}{V_T}\right)$$

$$I_C = (\beta_2 + 1) I_{C1}$$

$$= -(\beta_2 + 1) I_S \exp\left(-\frac{V_{BE}}{V_T}\right)$$

* high current is sourced by npn

$$* V_{SAT} = |V_{SAT1}| + V_{BE2}$$

* local f.b. can cause instability with cap loads

