
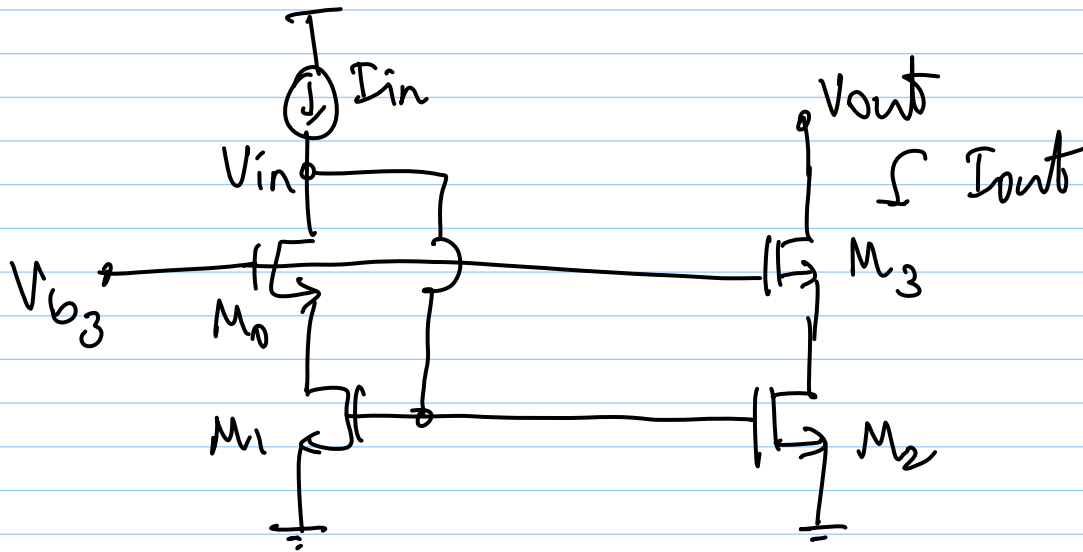


12/1/12

## Lec 6

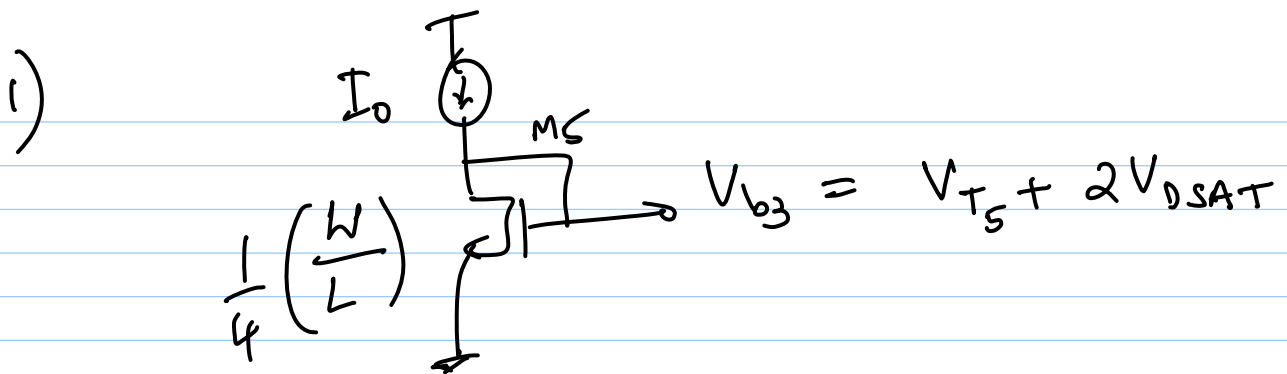

How to generate  $V_{b3}$ ?




$$V_{b3} = V_{T5} + 2V_{DSAT}$$

$\rightarrow V_{T5} < V_{T3}$  due to body effect

$$\Rightarrow V_{DS2} < V_{DSAT}$$

$\therefore$  some margin is required

2)

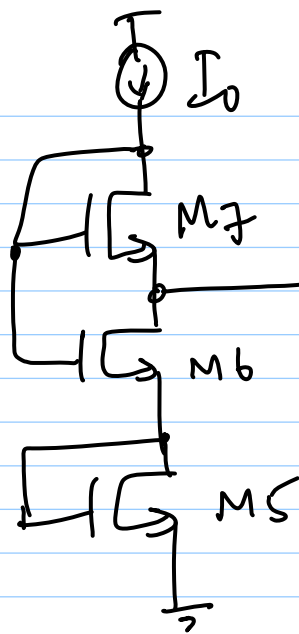

\*  $M_7$  has very large  $W/L$

$$\Rightarrow V_{as7} \approx V_{T7}$$

$$V_{b3} = V_{as5} + V_{DS6}$$

$$= V_{as5} + V_{as6} - V_{T7}$$

$$\approx V_{T5} + 2V_{DSAT}$$



however, note that  $V_{T7} \neq V_{T6}$

\* For more types, see

Razavi - figs 5.14 & 5.15

Gray & Meyer - figs 4.11, 4.12 & 4.13

## Bipolar Devices

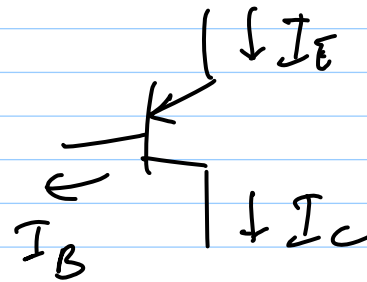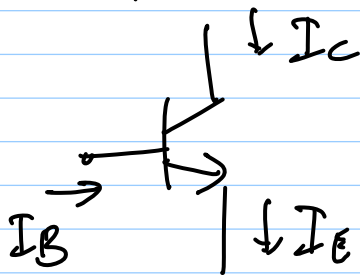

$$I_E = I_B + I_C$$



$$I_C = I_S e^{V_{BE}/V_T} \left( 1 + \frac{V_{CE}}{V_A} \right)$$

$-V_A$  = early voltage

$$V_T = \frac{kT}{q} \approx 26 \text{ mV}$$

\* due to base width modulation


$$1) r_o = \frac{\partial I_C}{\partial V_{CE}} ; \quad V_A = \frac{I_C}{\partial I_C / \partial V_{CE}}$$

$$\Rightarrow r_o \approx \frac{I_C}{V_A}$$

$V_A$  is independent of  $I_C$  etc. & is a fixed process parameter

$$2) g_m = \frac{\partial I_C}{\partial V_{BE}} = \frac{I_C}{V_T}$$
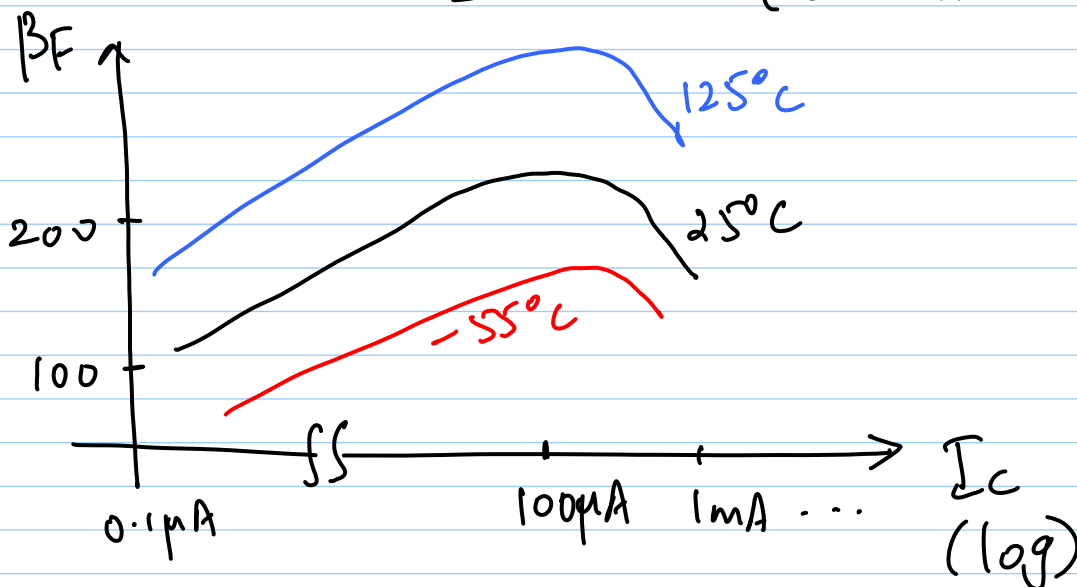
$$\beta_F = \frac{I_C}{I_B} \leftarrow \text{function of } I_C \text{ (current density)}$$



$$I_B = I_C / \beta_F \Rightarrow \Delta I_B = \frac{d}{dI_C} \left( \frac{I_C}{\beta_F} \right) \cdot \Delta I_C$$

$$\Rightarrow \beta_0 = \frac{\Delta I_C}{\Delta I_B} = \frac{i_c}{i_b} = \left[ \frac{d}{dI_C} \left( \frac{I_C}{\beta_F} \right) \right]^{-1}$$


small-signal  
current gain

$\beta_0 \neq \beta_F$  in general

3) Input res.  $r_{\pi} = \left( \frac{\partial I_b}{\partial V_{be}} \right)^{-1}_{Q-pt.}$


$$r_{\pi} = \frac{\beta_0}{g_m}$$

low-freq model:

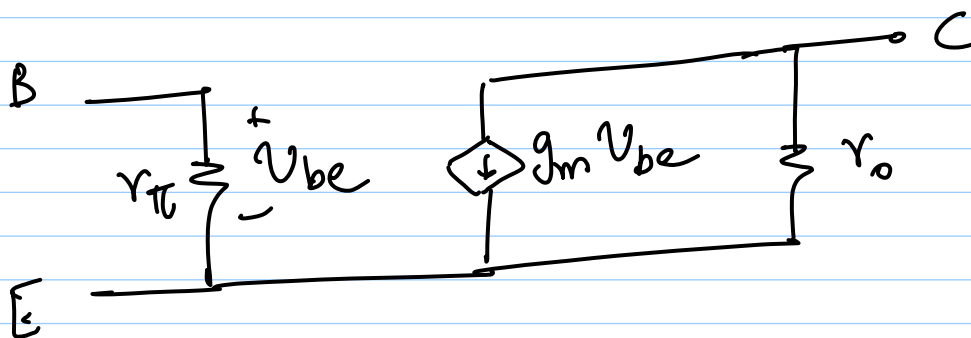

Bipolar CMOs

Simple CM:

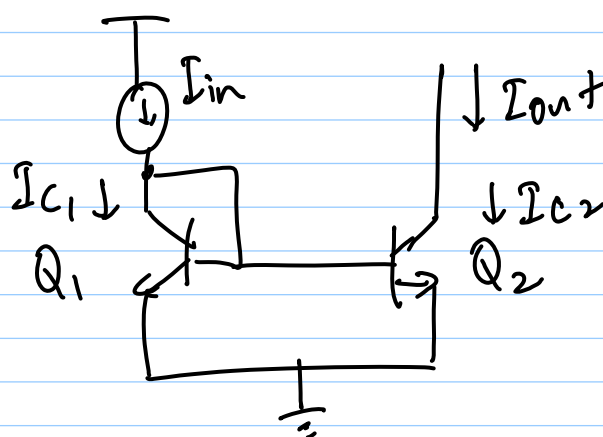

$$I_{C2} = I_{out}$$

$$V_{be1} = V_{be2}$$

$$V_T \ln \frac{I_{C1}}{I_{S1}} = V_T \ln \frac{I_{C2}}{I_{S2}}$$

$$\Rightarrow \frac{I_{C2}}{I_{C1}} = \frac{I_{S2}}{I_{S1}}$$

$$I_S \propto A_{EB} \leftarrow \text{EB jn. area} \\ \text{— design parameter}$$

assume identical transistors

$$I_{S1} = I_{S2} \Rightarrow I_{C1} = I_{C2} = I_{out}$$

$$I_{in} = I_{C1} + I_{b1} + I_{b2}$$

$$= I_{C1} + \frac{I_{C1}}{\beta_F} + \frac{I_{C2}}{\beta_F}$$

$$= I_{out} \left[ 1 + \frac{2}{\beta_F} \right]$$

$$I_{out} = \frac{I_{in}}{1 + \frac{2}{\beta_F}} \leftarrow \text{gain error due to finite } \beta_F$$

If you have  $n$  mirror legs,

$$I_{out} = \frac{I_{in}}{1 + \frac{(n+1)}{\beta_F}}$$

If  $Q_1 \neq Q_2$ ,  $I_{S1} \neq I_{S2}$

$$\begin{aligned} \Rightarrow I_{in} &= I_{C1} \left( 1 + \frac{1}{\beta_F} \right) + \frac{I_{C2}}{\beta_F} \\ &= I_{out} \left[ \frac{1}{\beta_F} + \frac{I_{S1}}{I_{S2}} \left( 1 + \frac{1}{\beta_F} \right) \right] \end{aligned}$$


$$I_{out} = \frac{\left( I_{S2}/I_{S1} \right) I_{in}}{1 + \frac{\left( 1 + I_{S2}/I_{S1} \right)}{\beta_F}}$$

Output impedance errors:

$$I_{C1} = I_{S1} e^{V_{BE1}/V_T} \left( 1 + V_{CE1}/V_{A1} \right)$$

$$I_{C2} = I_{S2} e^{V_{BE2}/V_T} \left( 1 + V_{CE2}/V_{A2} \right)$$
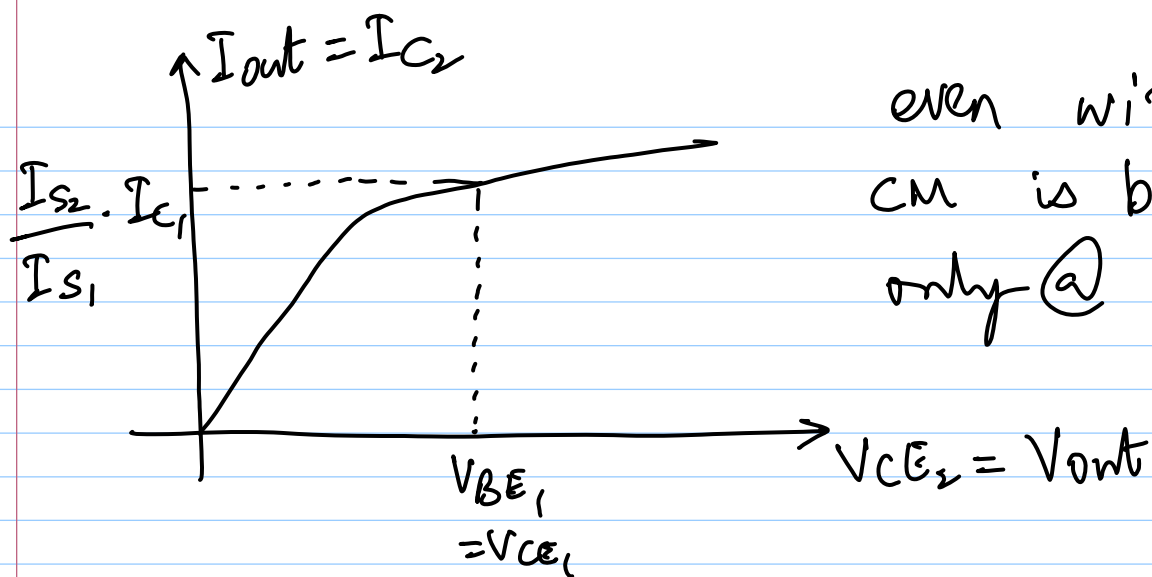
$$\Rightarrow I_{out} = \frac{\left( I_{S2}/I_{S1} \right) \cdot I_{in}}{1 + \frac{\left( 1 + I_{S2}/I_{S1} \right)}{\beta_F}} \cdot \left[ 1 + \frac{V_{CE2} - V_{CE1}}{V_A} \right]$$




even with  $\beta_F = \infty$ ,  
CM is balanced  
only @ 1 pt.

Error term

$$\epsilon = \frac{1 - \left( \frac{V_{CE2} - V_{CE1}}{V_A} \right)}{1 + \frac{1 + I_{S2}/I_{S1}}{\beta_F}} - 1 \approx \frac{V_{CE2} - V_{CE1}}{V_A} - \frac{1 + I_{S2}/I_{S1}}{\beta_F}$$


$$V_{out_{min.}} = V_{CE_{SAT2}} \sim 0.2V$$
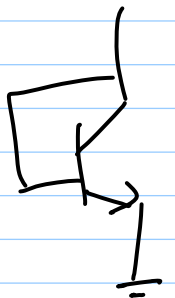
$$R_{in} = \frac{1}{\frac{1}{g_m} \left( 1 + \frac{1}{\beta_0} \right) + \frac{1}{r_o}} \approx \frac{1}{g_m}$$




$$R_{out} = r_o$$

## Simple CM with $\beta$ -helpes

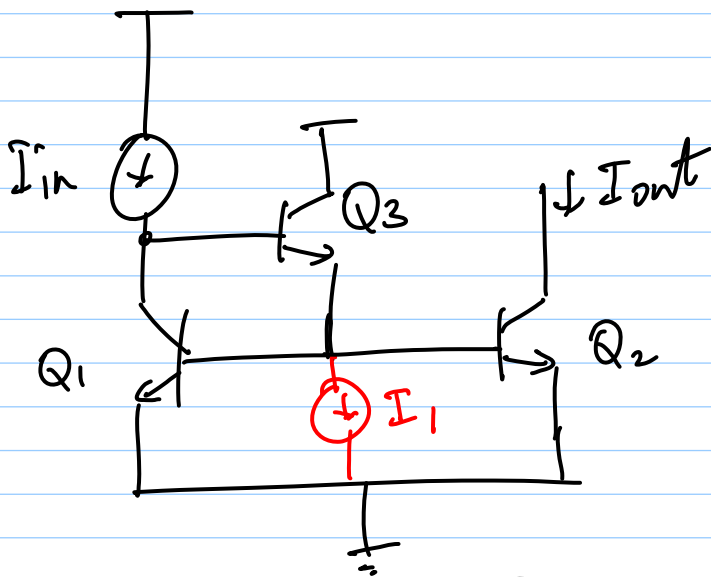

$$I_{out} = \frac{I_{in}}{1 + \frac{2}{\beta_F(\beta_F + 1)}} \approx I_{in} \left[ 1 - \frac{2}{\beta_F(\beta_F + 1)} \right]$$

$$\epsilon \propto \frac{1}{\beta_F^2}$$

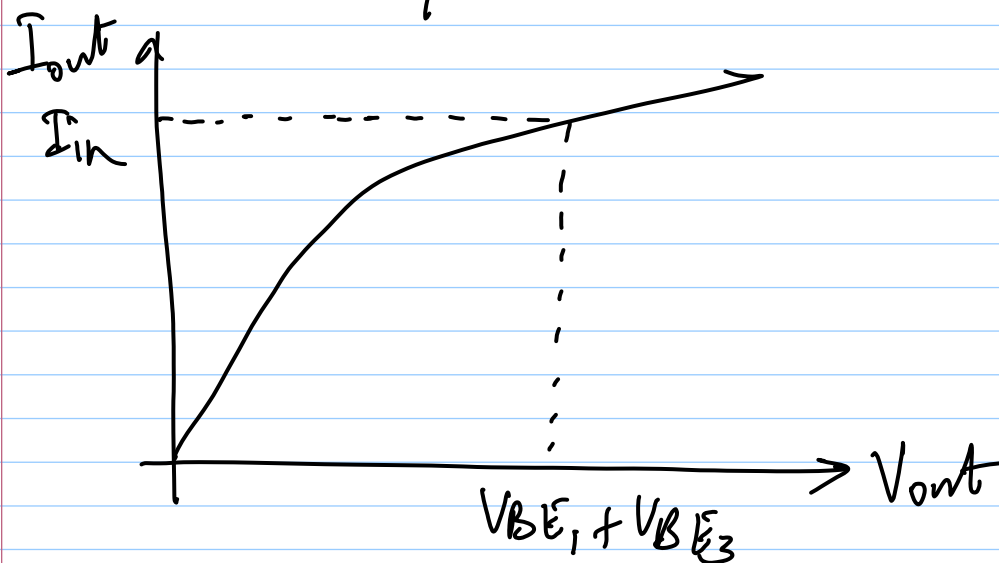


$\nwarrow$   $V_{in,DC}$  is different  
(different balance point)




$\beta_{F3}$  could be very small
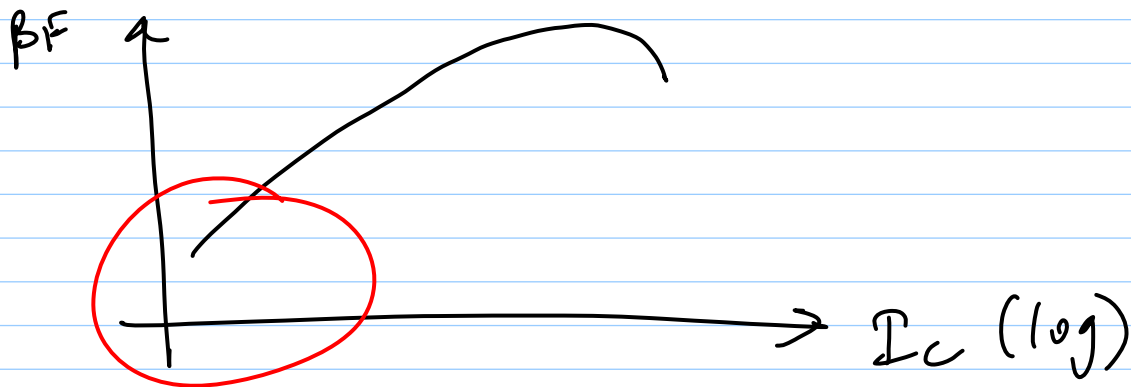
$$I_{E3} = I_{B1} + I_{B2} \leftarrow \text{very small}$$



$\Rightarrow$  add c.s. to increase  $I_{E3}$


BJT CM w/ emitter degen.:

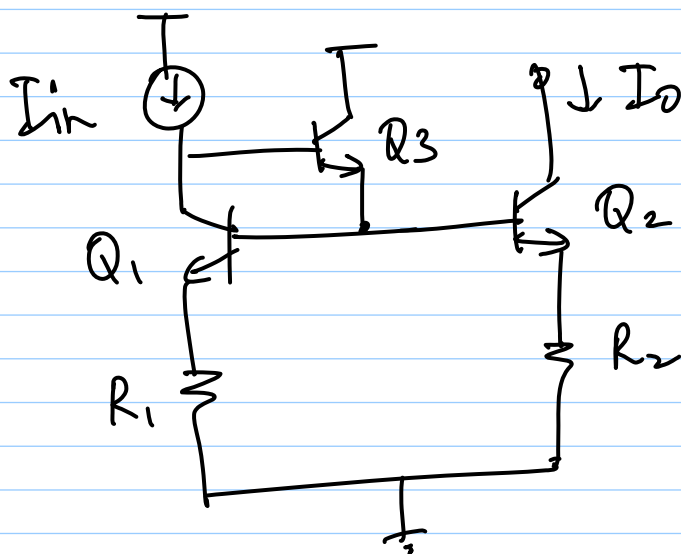

$\downarrow I_{out} \neq R_1 \& R_2$   
improve matching  
of  $I_{C1}$  &  $I_{C2}$   
 $\neq R_1 \& R_2$  increase  
 $R_{out}$

$$R_{out} \approx r_{o2} (1 + g_{m2} R_2)$$


$\in$  reduces (H.W.)

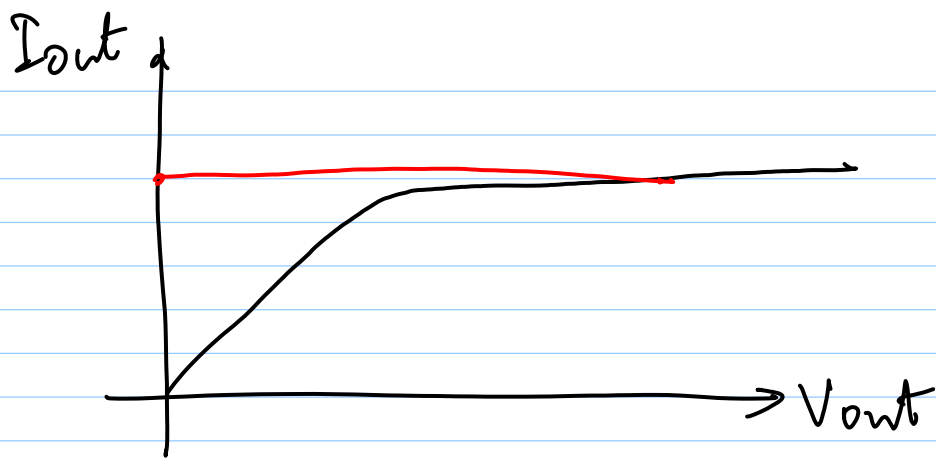

$$V_{in} = I_{in} R_1 + V_{BE1} + V_{BE3}$$

$$V_{out_{min.}} = I_{out} R_2 + V_{CE_{SAT2}}$$

### BJT cascode

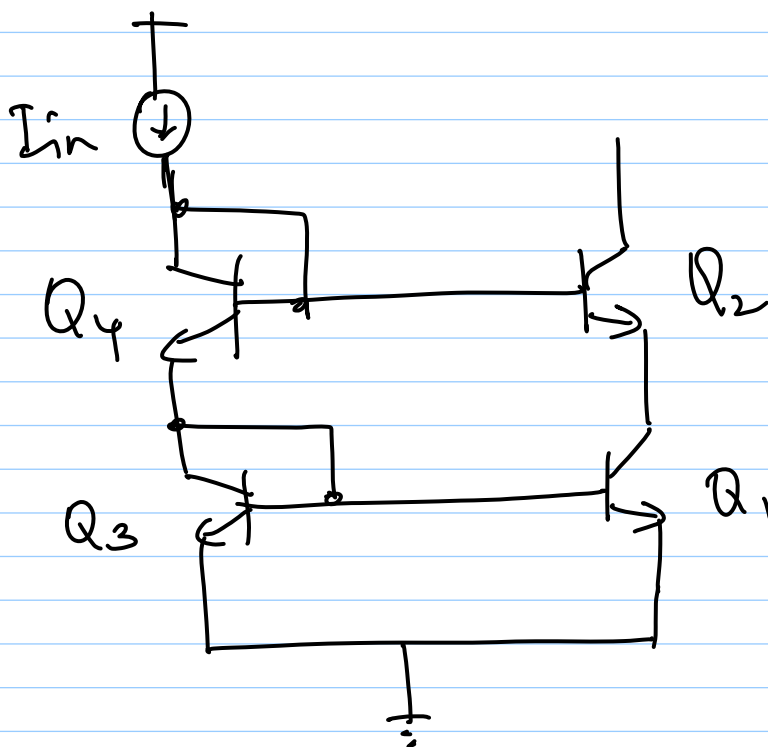

$$V_{in} = V_{BE3} + V_{BE4}$$

$$V_{CE1} = V_{BE3} + V_{BE4} - V_{BE2} \approx V_{BE3}$$

$$V_{out_{min.}} = V_{BE3} + V_{CE_{SAT2}} \approx 900mV$$

$$R_{out} \approx \frac{\beta_o r_{o2}}{2}$$

high  $R_{out} \leftrightarrow V_{out_{min.}}$  tradeoff

Other types :

→ Wilson & Balanced Wilson C.M.

→ Widlar C.S.

→ Bipolar peaking C.S.